

Section 10

Computer Arithmetic

Slides with white background courtesy of Mano text for this class

1

Digital Hardware Algorithms

- Arithmetic operations
 - Addition, subtraction, multiplication, division
- Data types
 - Fixed-point binary
 - ◆ Signed-magnitude representation
 - ◆ Signed-2's complement representation
 - Floating-point binary
 - Binary-coded decimal (BCD)


2

Add / Subtract Signed-Magnitude

Operation	Add Magnitudes	Subtract Magnitudes		
		When $A > B$	When $A < B$	When $A = B$
$(+A) + (+B)$	$+(A + B)$			
$(+A) + (-B)$		$+(A - B)$	$-(B - A)$	$+(A - B)$
$(-A) + (+B)$		$-(A - B)$	$+(B - A)$	$+(A - B)$
$(-A) + (-B)$	$-(A + B)$			
$(+A) - (+B)$		$+(A - B)$	$-(B - A)$	$+(A - B)$
$(+A) - (-B)$	$+(A + B)$			
$(-A) - (-B)$	$-(A + B)$			
$(-A) - (+B)$		$-(A - B)$	$+(B - A)$	$+(A - B)$

↑
Forces zero to be positive


3






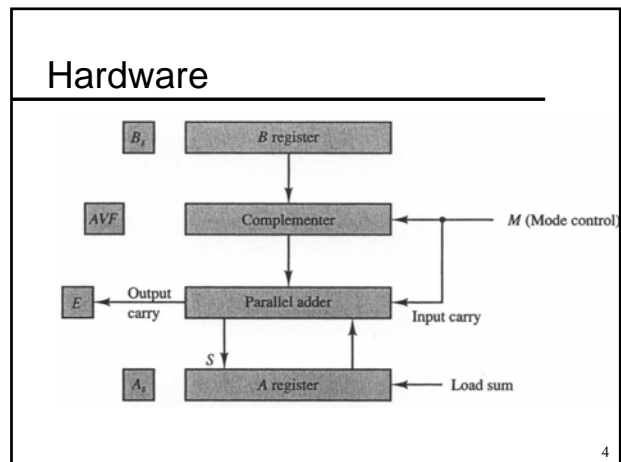


Description

- A_S Sign of A
- B_S Sign of B
- A_S & A Accumulator
- AVF Overflow bit for $A + B$
- E Output carry for parallel adder

5

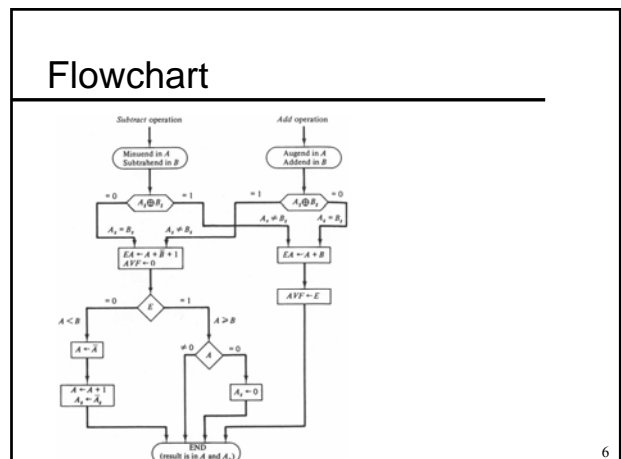

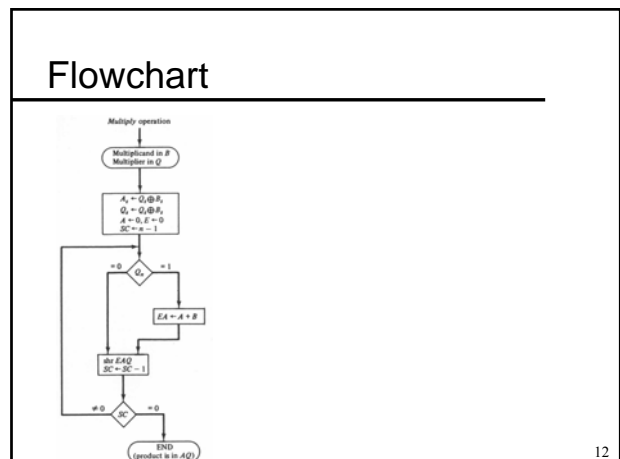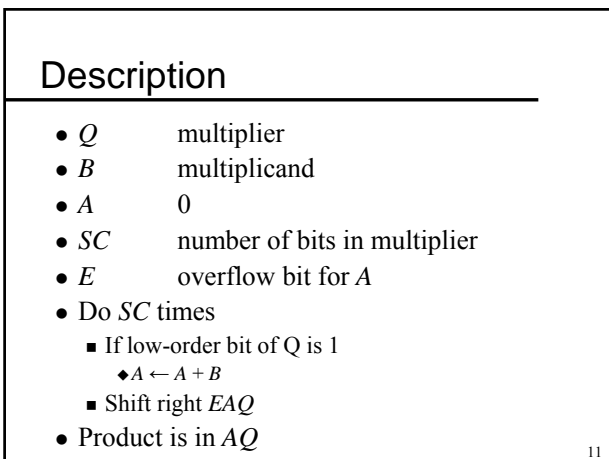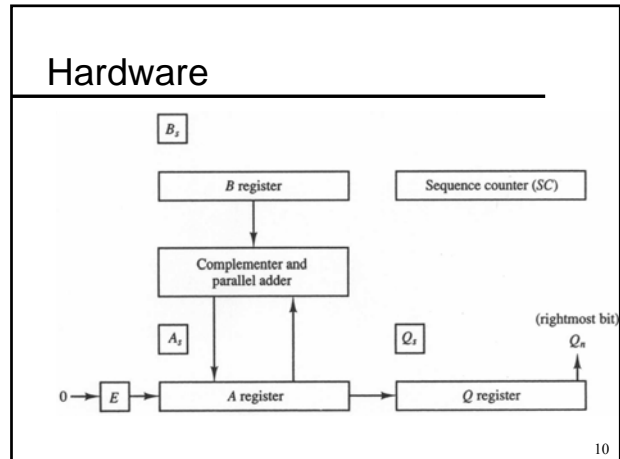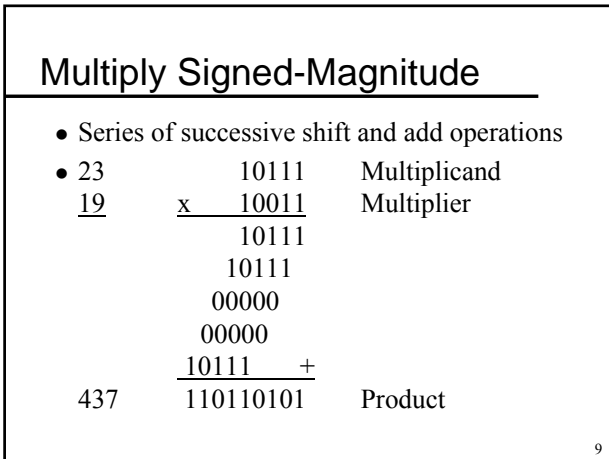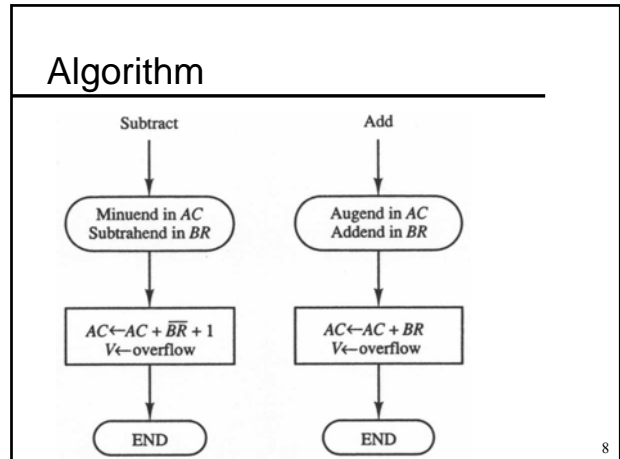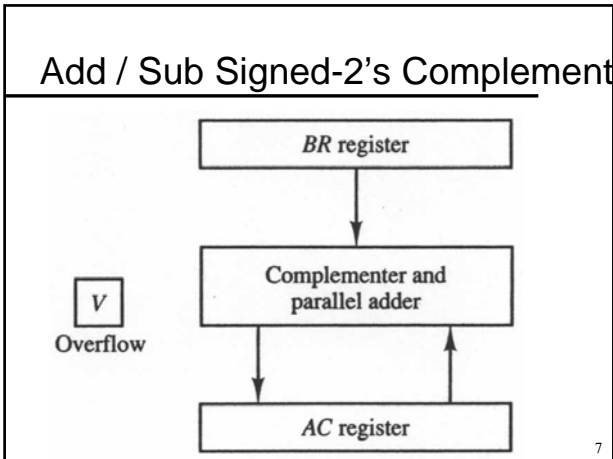

Example: 23 x 19 = 437

Multiplicand B = 10111	E	A	Q	SC
Multiplier in Q	0	0000	10011	101
$Q_n = 1$; add B		<u>10111</u>		
First partial product	0	10111		
Shift right EAQ	0	01011	11001	100
$Q_n = 1$; add B		<u>10111</u>		
Second partial product	1	00010		
Shift right EAQ	0	10001	01100	011
$Q_n = 0$; shift right EAQ	0	01000	10110	010
$Q_n = 0$; shift right EAQ	0	00100	01011	001
$Q_n = 1$; add B		<u>10111</u>		
Fifth partial product	0	11011		
Shift right EAQ	0	01101	10101	000
Final product in AQ = 0110110101				

13

Multiply Signed-2's Complement

- Booth algorithm
- QR multiplier
- Q_n least significant bit of QR
- Q_{n+1} previous least significant bit of QR
- BR multiplicand
- AC 0
- SC number of bits in multiplier


14

Algorithm

- Do $SC + 1$ times
 - $Q_n Q_{n+1} = 10$
 - ◆ $AC \leftarrow AC + \overline{BR} + 1$
 - $Q_n Q_{n+1} = 01$
 - ◆ $AC \leftarrow AC + BR$
 - Arithmetic shift right AC & QR
 - $SC \leftarrow SC - 1$


15

Hardware

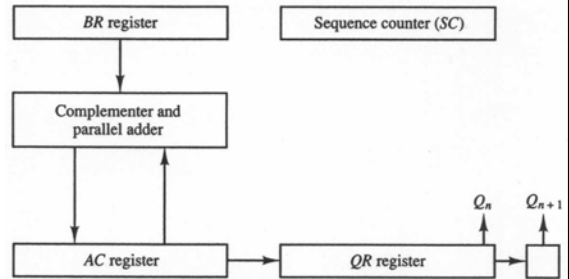

16

Flowchart

 

17

Example: -9 x -13 = 117

$Q_n Q_{n+1}$	$BR = 10111$ $\overline{BR} + 1 = 01001$	AC	QR	Q_{n+1}	SC
	Initial	00000	10011	0	101
1 0	Subtract BR	<u>01001</u> 01001			
	ashr	00100	11001	1	100
1 1	ashr	00010	01100	1	011
0 1	Add BR	<u>10111</u> 11001			
	ashr	11100	10110	0	010
0 0	ashr	11110	01011	0	001
1 0	Subtract BR	<u>01001</u> 00111			
	ashr	00011	10101	1	000


18

Array Multiplier

- Combination circuit
- Product generated in one microoperation
- Requires large number of gates
- Became feasible after integrated circuits developed
- Needed for j multiplier and k multiplicand bits
 - $j \times k$ AND gates
 - $j - 1$ k -bit adders to produce product of $j + k$ bits


19

2-bit by 2-bit Array Multiplier

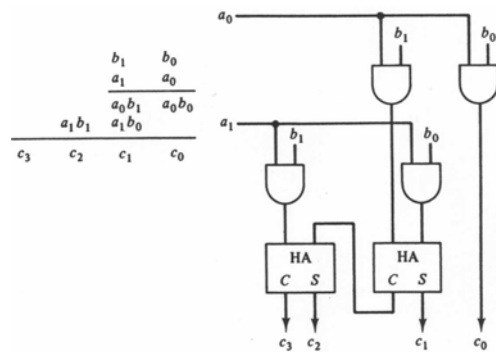

20

4-bit by 3-bit Array Multiplier

 

21

Divide Fixed-Point Signed-Mag

- Series of successive compare, shift, and subtract operations

Divisor:	11010	Quotient = Q
$B = 10001$	<pre> 0111000000 01110 011100 -10001 ----- -010110 -10001 ----- -001010 -010100 ---- -000110 -00110 ----- -00110 </pre>	<p>Dividend = A 5 bits of $A < B$, quotient has 5 bits 6 bits of $A \geq B$ Shift right B and subtract; enter 1 in Q 7 bits of remainder $\geq B$ Shift right B and subtract; enter 1 in Q Remainder $< B$; enter 0 in Q; shift right B Remainder $\geq B$ Shift right B and subtract; enter 1 in Q Remainder $< B$; enter 0 in Q Final remainder</p>

22

Example: $448 / 17 = 26 \text{ r } 6$

Divisor $B = 10001$,	$\bar{B} + 1 = 01111$	
Dividend:	01110	00000
shl E, AQ	11100	00000
add $B + 1$	01111	
$E = 1$	01011	
Set $Q_n = 1$	01011	00001
shl E, AQ	10110	00010
Add $B + 1$	01111	
$E = 1$	00101	
Set $Q_n = 1$	00101	00011
shl E, AQ	01010	00110
Add $B + 1$	01111	
$E = 0$; leave $Q_n = 0$	11001	00110
Add B	10001	
Restore remainder	01010	01100
shl E, AQ	10100	01100
Add $B + 1$	01111	
$E = 1$	00011	
Set $Q_n = 1$	00011	01101
shl E, AQ	00110	11010
Add $B + 1$	01111	
$E = 0$; leave $Q_n = 0$	10101	11010
Add B	10001	
Restore remainder	00110	11010
Neglect E		
Remainder in A :	00110	11010


Initially,
 AQ dividend
 B divisor

At end of operation,
 Q quotient
 A remainder
 DVF divide overflow


Figure 10-12 Example of binary division with digital hardware.

23

Algorithm

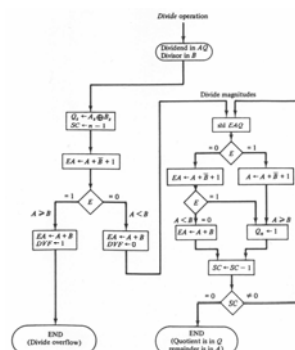

24

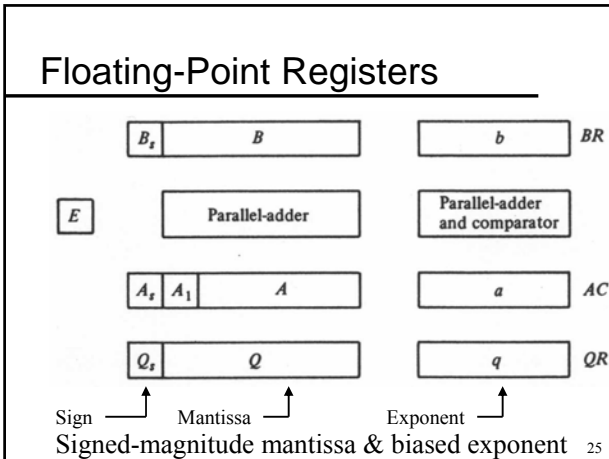

Biased Exponent

- Example
 - Real exponent range is -50 to +49
 - Add bias of 50 for new range of 0 to 99
 - Biased exponent is always a positive number
 - ◆ Easier to deal with

Floating-Point Add / Subtract

- Check for zeros
- Align the mantissas
- Add or subtract the mantissas
- Normalize the result

F-P Add / Subtract Flowchart

The flowchart details the steps for adding or subtracting floating-point numbers. It starts with "Add or subtract" and branches based on whether the numbers are zero. It includes decision points for $a < b$ and $a > b$, and operations like $AC \leftarrow AC + BR$ or $AC \leftarrow AC - BR$. The process concludes with normalization and rounding.

Floating-Point Multiply

- Check for zeros
- Add the exponents
- Multiply the mantissas
- Normalize the product

F-P Multiply Flowchart


The flowchart for multiplication starts with "Multiply" and "Multiplied in QR Mantissa in QR". It includes decision points for zero and non-zero values, followed by operations like $a \leftarrow a + b$, $a \leftarrow a - bias$, and "Multiply mantissa as in Fig. 10-6". The final step is "END (product in AC)".

Floating-Point Division


- Check for zeros
- Initialize registers and evaluate the sign
- Align the dividend
- Subtract the exponents
- Divide the mantissas

31


F-P Division Flowchart

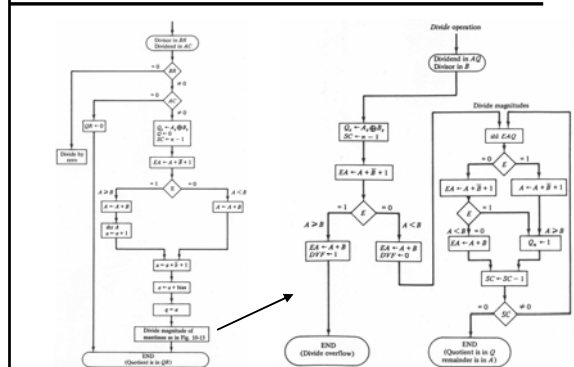


32

 

33

 

34

 

35

Booth Multiplication Algorithm

- Zeros in multiplier require no addition
 - But shifting still required
- String of 1s in the multiplier from weight 2^k to 2^m can be rewritten as $2^{k+1} - 2^m$
 - Example: 001110 [+14]
 - ◆ String of 1s from 2^3 to 2^1 : $2^4 - 2^1 = 16 - 2 = 14$
 - ◆ Multiplicand M : $M \times 14 = M \times 2^4 - M \times 2^1$
 - ◆ Product obtained by M 4 times to the left and subtracting M shifted left once


36

BCD Adder

- Output can't exceed $9 + 9 + 1 = 19$
- If binary sum in BCD digit > 1001 , add 0110
- Given
 - Output of binary adder is $Z_8Z_4Z_2Z_1$
 - Output carry K
 - BCD output carry $C = K + Z_8Z_4 + Z_8Z_2$

37

Block Diagram BCD Adder

 

38

Examples

- | | | | | | |
|----------|-------------|----------|-------------|----------|-------------|
| • 9 | 1001 | 9 | 1001 | 6 | 0110 |
| <u>7</u> | <u>0111</u> | <u>9</u> | <u>1001</u> | <u>4</u> | <u>0100</u> |
| 16 | 1 0000 | 18 | 1 0010 | 10 | 1010 |
| | <u>0110</u> | | <u>0110</u> | | <u>0110</u> |
| | 0110 | | 1000 | | 1 0000 |

39

BCD Subtraction

- Subtract by adding 9s complement of subtrahend to minuend
- First 9s complement algorithm
 - Complement bits
 - Add 1010 (decimal 10) and discard carry
- Second 9s complement algorithm
 - Add 0110 (decimal 6)
 - Complement bits


40

Examples

- | | |
|-------------------------|-----------------------------|
| • 0111 decimal 7 | 0111 |
| 1000 complement | + <u>0110</u> add decimal 6 |
| <u>+1010</u> decimal 10 | 1101 |
| 1 0010 decimal 2 | 0010 complement |

41

Stage of Decimal Arithmetic Unit

 

42


Decimal Arithmetic Microops

TABLE 10-5 Decimal Arithmetic Microoperation Symbols

Symbolic Designation	Description
$A \leftarrow A + B$	Add decimal numbers and transfer sum into A
\bar{B}	9's complement of B
$A \leftarrow A + \bar{B} + 1$	Content of A plus 10's complement of B into A
$Q_L \leftarrow Q_L + 1$	Increment BCD number in Q_L
dshr A	Decimal shift-right register A
dshl A	Decimal shift-left register A

43

Parallel Decimal Addition

 


(a) Parallel decimal addition: 624 + 879 = 1503

Fast

44

Digit-Serial, Bit-Parallel Dec Add

 


(b) Digit-serial, bit-parallel decimal addition

Slow

45

All Serial Decimal Addition

 


(c) All serial decimal addition

Very slow


46

Dec Arith Registers for Mult & Div

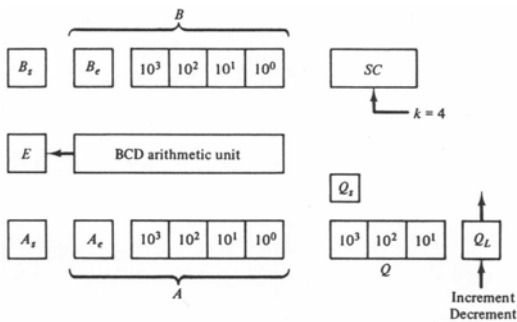

47

Decimal Multiplication Flowchart

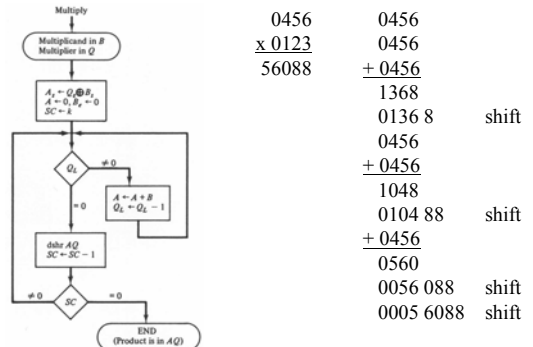

48

