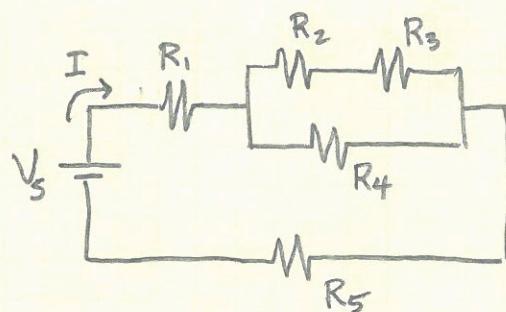


Given The network of resistors with known values shown in the sketch



$$V_s = 10 \text{ V}$$

$$R_1 = R_4 = 470 \Omega$$

$$R_2 = R_3 = R_5 = 330 \Omega$$

Find: The power dissipated by R_5 , R_2 and the total power dissipated by the circuit


Analysis: The power dissipated by individual resistors is computed with

$$V_i I_i \text{ or } I_i^2 R_i \text{ or } \frac{V_i^2}{R_i}$$

where V_i is the voltage drop across resistor i , I_i is the current through resistor i , and R_i is the resistance of resistor i

The current through R_5 is the same as I , the total current delivered by the power supply. To find I we need to know the equivalent resistance of the entire network

Start by combining R_2 , R_3 and R_4

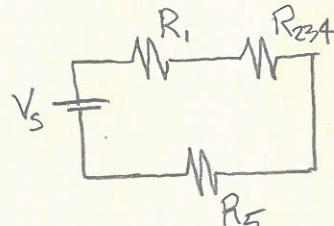


$$R_{234} = \left[\frac{1}{R_2 + R_3} + \frac{1}{R_4} \right]^{-1}$$

$$= \left[\frac{1}{660 \Omega} + \frac{1}{470 \Omega} \right]^{-1}$$

$$R_{234} = 274.5 \Omega$$

↑ carry extra digits through intermediate calculations

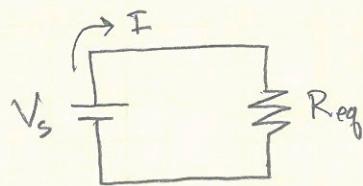Combine R_1 , R_{234} and R_5 to get the equivalent resistance of the entire network



$$\begin{aligned} R_{eq} &= R_1 + R_{234} + R_5 \\ &= R_1 + \underbrace{\frac{1}{\frac{1}{R_2+R_3} + \frac{1}{R_4}}}_{R_{234}} + R_5 \end{aligned}$$

Substitute known values and using the value of R_{234} computed above

$$R_{eq} = 470\Omega + 274.5\Omega + 330\Omega = 1074.5\Omega$$

$$R_{eq} = 1074.5\Omega$$

Apply Ohm's law to the equivalent circuit

$$V_s = I R_{eq} \Rightarrow I = \frac{V_s}{R_{eq}} = \frac{10V}{1074.5\Omega}$$

$$\therefore I = 9.31 \times 10^{-3} A = 9.31 \text{ mA}$$

↑ Continue to carry extra digits through intermediate calculations

$0.01 \text{ mA} = 1 \mu\text{A}$ which is very difficult to measure. We carry this last digit to avoid introducing unnecessary round-off in the intermediate calculations.

With $I_5 = I$ known, we can now compute the power dissipated by R_5

$$P_5 = I_5^2 R_5 = I^2 R_5 = (9.31 \times 10^{-3} A)(330\Omega) = 2.86 \times 10^{-2} W$$

$$P_5 = 29 \text{ mW}$$

↑ two significant digits in the final result is appropriate

Compute the total power dissipated by the resistor network


$$P_{\text{total}} = I^2 R_{\text{eq}} = (9.31 \times 10^{-3} \text{ A})^2 (1074.5 \Omega) = 9.31 \times 10^{-2} \text{ W}$$

$$\boxed{P_{\text{total}} = 93 \text{ mW}}$$

To compute the power dissipated by R_2 we need to find I_2 or V_2 .

We know R_{234} and I , so $V_4 = V_{23}$ can be computed from Ohm's law
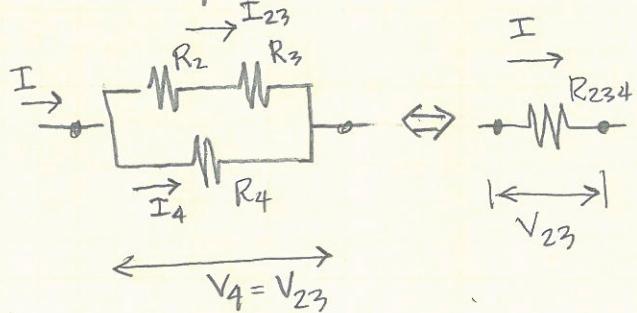
$$\begin{aligned} V_{23} &= IR_{234} \\ &= (9.31 \times 10^{-3} \text{ A})(274.5 \Omega) \\ &= 2.556 \text{ V} \end{aligned}$$



With V_{23} known we apply Ohm's law again to compute I_{23} , the current through R_2 and R_3

$$V_{23} = I_{23}(R_2 + R_3) \Rightarrow I_{23} = \frac{V_{23}}{R_2 + R_3} = \frac{2.556 \text{ V}}{330 + 330 \Omega}$$

$$I_{23} = 3.87 \times 10^{-3} \text{ A}$$

Finally, compute $P_2 = I_2^2 R_2$ with $I_2 = I_{23}$

$$P_2 = I_2^2 R_2 = (3.87 \times 10^{-3} \text{ A})^2 (330 \Omega) = 4.95 \times 10^{-3} \text{ W}$$

$$\boxed{P_2 = 5 \text{ mW}}$$

Discussion

The values of P_2 and P_5 are less than the total power dissipated by the network

$$P_2 = 5 \text{ mW} < P_{\text{total}} = 93 \text{ mW} \quad P_5 = 29 \text{ mW} < P_{\text{total}} = 93 \text{ mW}$$

While this doesn't prove that the values of P_2 , P_5 and P_{total} are correct, at least the relative magnitudes are consistent with common sense