

# **Using Excel in DC Circuit Analysis**

**EAS 199A Notes**

## The Goal

These slides provide a very brief analysis of a DC circuit.

The goal is to set up an analysis that is performed in Excel.



There are no Excel computations in these slides.

There is nothing special about Excel. Once the equations are obtained these computations could be performed using any number of tools, including

- Excel or other spreadsheets
- MathCAD
- MATLAB
- Maple, Mathematica
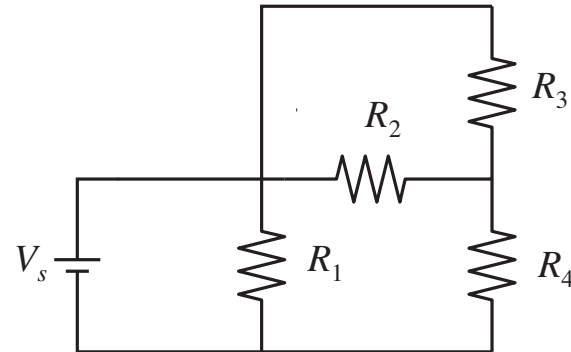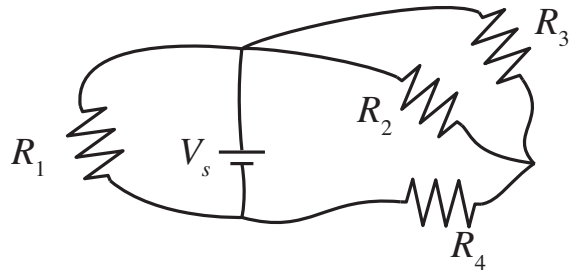
## The Problem


What is the total power consumed by the circuit, and the power consumed by resistor  $R_4$  for the following two circuits?



Use  $R_1 = R_2 = 330 \Omega$ ,  $R_3 = 500 \Omega$ ,  $V_s = 12 \text{ V}$  and let  $R_4$  vary from  $50 \Omega$  to  $500 \Omega$ .
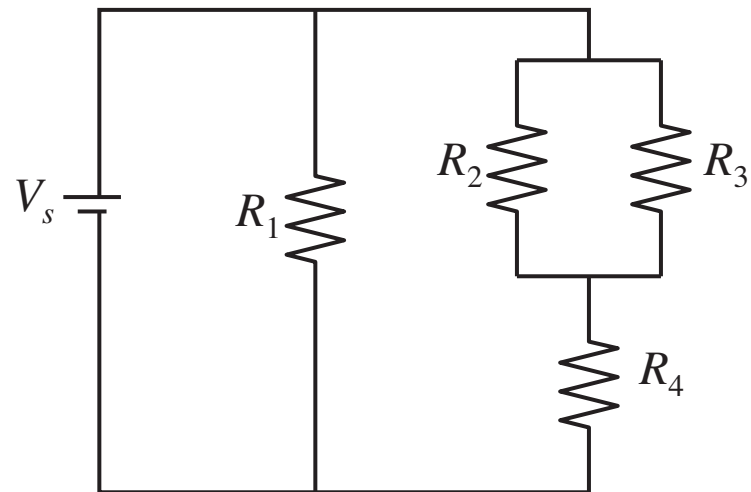
## The Problem in Standard Form



Examination of the two circuits shows that they are both equivalent to the following.


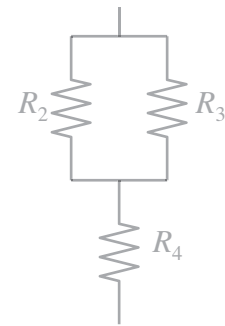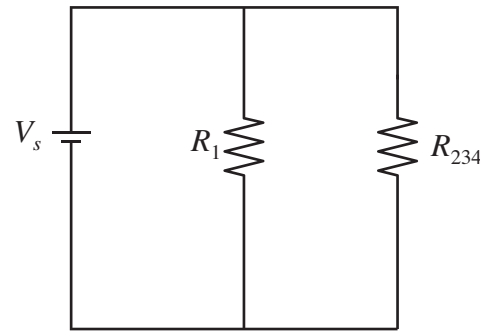
## Circuit Simplification


Resistors  $R_2$ ,  $R_3$ , and  $R_4$  can be combined to yield the equivalent resistance  $R_{234}$ .

$$R_{234} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} + R_4$$



$R_1$  and  $R_{234}$  can be further combined to give the equivalent resistance for the circuit
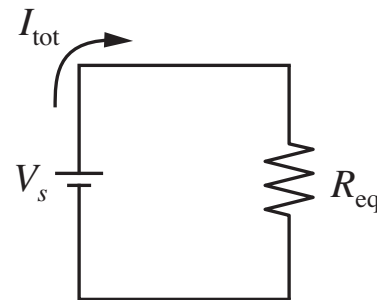
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_{234}}}$$




## Total Current and Power

With  $R_{\text{eq}}$  known, the total current and total power from the voltage supply can be computed

$$V_s = I_{\text{tot}} R_{\text{eq}} \implies I_{\text{tot}} = \frac{V_s}{R_{\text{eq}}}$$
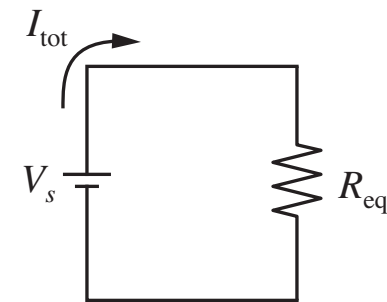
$$P_{\text{tot}} = I_{\text{tot}}^2 R_{\text{eq}}$$



## Current and Power through $R_4$

$R_1$  and  $R_{234}$  are in parallel with  $V_s$ , therefore

$$V_s = I_{234}R_{234} \implies I_{234} = \frac{V_2}{R_{234}}$$

Finally, with  $I_{234}$  known, the power dissipated by  $R_4$  is

$$P_4 = I_{234}^2 R_4$$

