

## Cascade switching of an LED

EAS 199B  
Winter 2013

---

---

---

---

---

---

---

## Objectives

- Be able to describe the circuit that uses an NPN transistor to switch an LED on and off
- Be able to describe the circuit that uses an NPN transistor and a relay to switch an LED on and off
- Be able to describe the role of a fly-back diode on a relay coil or solenoid valve
- Be able to describe the cascade switching circuit used to control the solenoid valves for the fish tank.

---

---

---


---

---

---

---
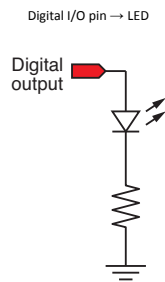
## Use Digital I/O pin to switch LED on/off



---

---

---

---

---

---

---

### Code to blink the LED

```
int LED_pin = 11; // array of pins for digital output

void setup() {
  pinMode( LED_pin, OUTPUT );
}

void loop() {
  digitalWrite( LED_pin, HIGH);
  delay(1000);
  digitalWrite( LED_pin, LOW);
  delay(1000);
}
```

In the following examples, the Arduino code does not need to change when the electrical circuit is changed. The Arduino code only needs to use a single digital output pin, which in this code is LED\_pin.

---

---

---

---

---


---

---

---

### Use a Transistor to switch LED on/off

Digital I/O pin → Transistor → LED

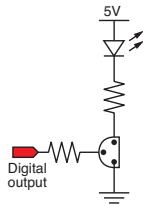

---

---

---

---

---


---

---

---
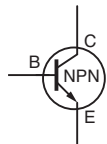
### NPN Transistors as Switches

Transistors can be used as switches: By applying relatively small voltage to the Base, electrical current will flow from the collector to the base.



C is the collector.  
B is the base  
E is the emitter

---

---

---

---

---


---

---

---
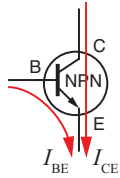
### NPN Transistors as Switches

When used as a switch,  $I_{CE}$ , the current from the collector to the emitter is large compare to  $I_{BE}$ , the current from the base to the emitter.



C is the collector.  
B is the base  
E is the emitter

---

---

---

---

---


---

---

---
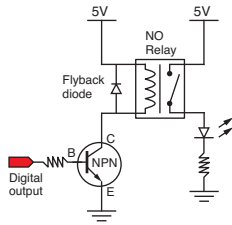
### Use a Relay switch the LED on/off

Digital I/O pin → Transistor → Relay → LED




---

---

---

---


---

---

---

---

### Compare switching circuits

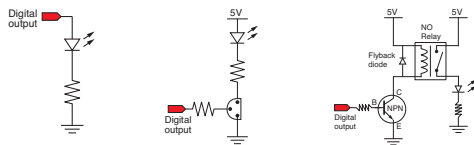


---

---

---

---


---

---

---

---

### Application to solenoid switching

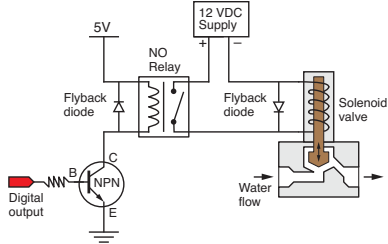

---

---

---

---

---

---

---