

## Basic Concepts Overview

---

- SI Prefixes
- Definitions: Current, Voltage, Power, & Energy
- Passive sign convention
- Circuit elements
- Ideal Sources

## SI Prefixes

---

These are used throughout the curriculum and by engineers

| Multiplier | Prefix | Symbol | Example    |
|------------|--------|--------|------------|
| $10^{12}$  | tera   | T      | TB         |
| $10^9$     | giga   | G      | GB         |
| $10^6$     | mega   | M      | MHz        |
| $10^3$     | kilo   | k      | k $\Omega$ |
| $10^0$     |        |        | V          |
| $10^{-3}$  | milli  | m      | mH         |
| $10^{-6}$  | micro  | $\mu$  | $\mu$ A    |
| $10^{-9}$  | nano   | n      | ns         |
| $10^{-12}$ | pico   | p      | pF         |
| $10^{-15}$ | femto  | f      |            |
| $10^{-18}$ | atto   | a      |            |


## Circuit Analysis: Introduction

---

- An **electric circuit** is an interconnection of electrical elements
- **Charge** is an electrical property of the atomic particles which matter consists, measured in coulombs (C)
- 1 C of charge requires  $6.24 \times 10^{18}$  electrons
- **Law of conservation of charge:** charge cannot be created or destroyed, only transferred.

## Flashlight Circuit

---

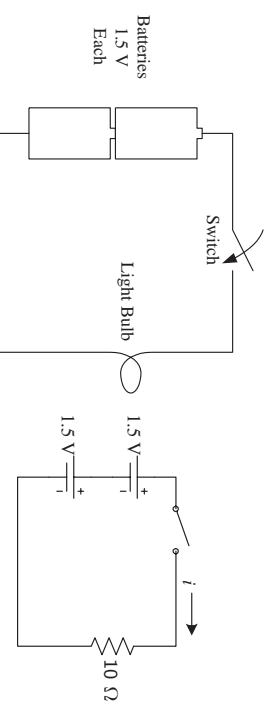

- A flashlight circuit has 4 circuit elements
- We will use symbols for circuit elements
- Facilitates analysis

### Electric Current

- **Electric Current** is the rate of change of charge, measured in amperes (A)
  - $1 \text{ A} = 1 \text{ C/s}$
- Two main types
  - **Direct Current (DC)**: Current remains constant
  - **Alternating Current (AC)**: Current varies sinusoidally with time


$$i = \frac{dq}{dt}$$

where


- $i$  = current in amperes
- $q$  = charge in coulombs
- $t$  = time in seconds
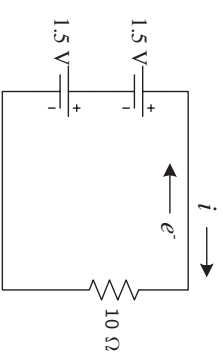
### Notes on Current

- Current in circuits physically realized by movement of electrons
- Direction of current must be specified by an **arrow**
- By convention, current direction defined as flow of **positive** charge
- Note positive charge is not flowing physically
- Electrons have a negative charge
- They move in the opposite direction of current



### Propagation Rate

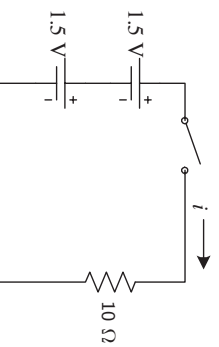

- Average drift velocity is very small (mm/sec)
- Propagation is very fast (close to speed of light)
- Effects appear to be instantaneous
- Similar to a hose full of water

### Key Assumptions

For the duration of this class, we will make the following assumptions.

- Propagation is instantaneous (lumped-parameter system)
- Net charge stored by all circuit elements is 0 (zero)
  - Nothing can store electrons
- No magnetic coupling between wires or circuit elements

### Voltage

- Voltage is the energy absorbed or expended as a unit charge moves through a circuit element
- Analogous to pressure in a hydraulic system
- Sometimes called potential difference
- Can be created by a separation of charge
- Is a measure of the potential between **two points**
- Voltage pushes charge in one direction
- We use polarity (+ and – on batteries) to indicate which direction the charge is being pushed


$$v = \frac{dw}{dq}$$

where


- $v$  = voltage in volts
- $w$  = energy in Joules
- $q$  = charge in coulombs
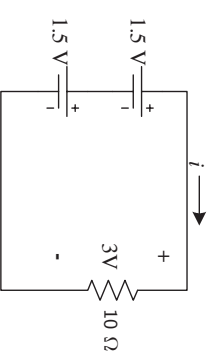
### Voltage Concept

- The voltage sources push current through the circuit
- The current is the rate of flow of charge (i.e. electrons)
- The light bulb (resistor) resists the flow of current




### Example 1: Voltage Concept

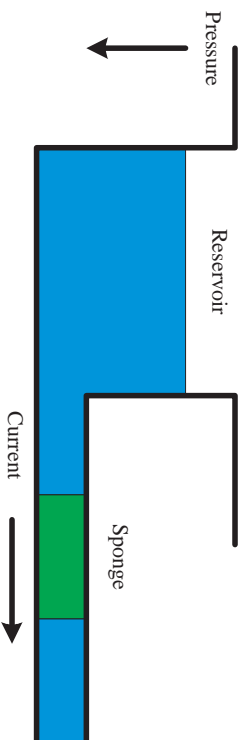

- Voltage  $\sim$  Pressure
- Electric Current  $\sim$  Water Current
- Sponge Porosity  $\sim$  Resistance

### Example 2: Voltage Concept

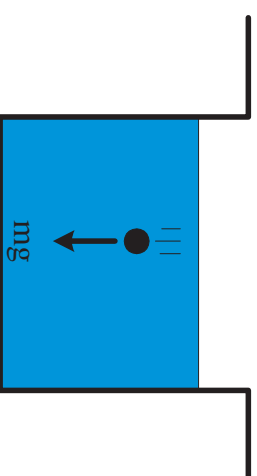

- Voltage  $\sim$  Force due to gravity ( $mg$ )
- Electric Current  $\sim$  Marble velocity
- Viscosity  $\sim$  Resistance

## Power

- Power: time rate of expending or absorbing energy
- Denoted by  $p$
- By convention
  - Circuit elements that **absorb** power have a **positive** value of  $p$
  - Circuit elements that **produce** power have a **negative** value of  $p$

$$p = \frac{dw}{dt}$$

$$p = \pm vi$$

where

|       |                          |
|-------|--------------------------|
| $p =$ | power in watts (W = J/s) |
| $w =$ | energy in joules (J)     |
| $t =$ | time in seconds (s)      |
| $v =$ | voltage in volts (V)     |
| $i =$ | current in amperes (A)   |

## Energy

- **Law of Conservation of Energy**: the net power absorbed by a circuit is equal to 0
- In other words
  - The total energy produced in a circuit is equal to the total energy absorbed
  - Every Watt absorbed by an element must be produced by some other element(s)
- **Energy**: capacity to do work, measured in joules (J)

$$w = \int_{t_0}^t p(t) dt = \int_{t_0}^t \pm v(t)i(t) dt$$

If current and voltage are constant (DC),


$$w = \int_{t_0}^t p dt = p(t - t_0)$$

## Passive Sign Convention

- **Passive Sign Convention (PSC)**: Current enters the positive terminal of an element
  - Equivalent: Current leaves the negative terminal
- Most two-terminal circuit elements (e.g. batteries, light bulbs, resistors, switches) are characterized by a single equation that relates voltage to current:  $v = \pm f(i)$  or  $i = \pm g(v)$
- Called the **defining equation**
- The PSC determines the sign of the relationship
  - If PSC is satisfied:  $v = f(i)$  or  $i = g(v)$
  - If PSC is not satisfied:  $v = -f(i)$  or  $i = -g(v)$
- This is also true of power
  - If PSC is satisfied:  $p = +vi$
  - If PSC is not satisfied:  $p = -vi$

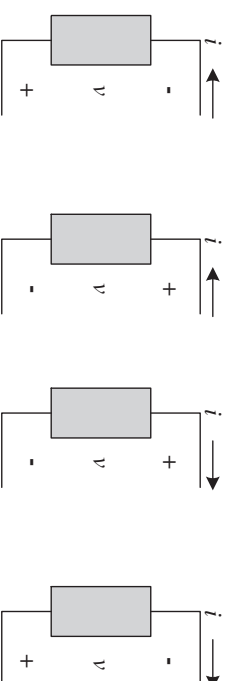
## Example 3: Passive Sign Convention

Suppose the circuit element shown below is characterized by  $v = \pm f(i)$  and  $i = \pm g(v)$ . Determine whether the PSC is satisfied and write the equations for the voltage, current, and power for each of the diagrams below.



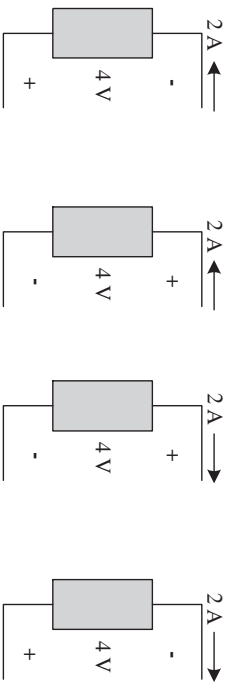
### Example 4: Passive Sign Convention

Find the power (absorbed) for each element.


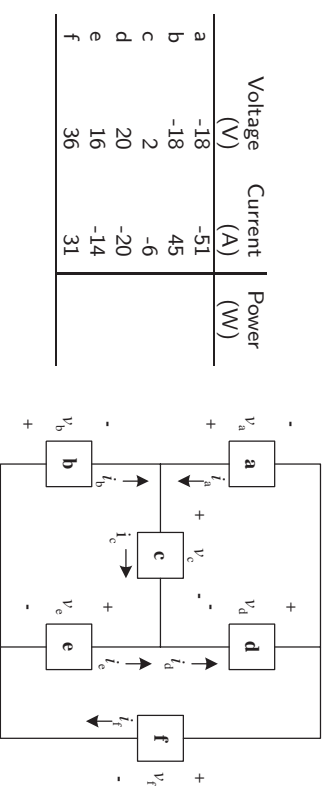
### Example 5: Passive Sign Convention

Find the total power absorbed in the circuit.




### Passive Sign Convention Remarks


- Failure to comply with the PSC will result in a wrong equation in the early stages of circuit analysis
- All of the results that follow will be wrong
- This translates to many lost points on exams
- One of the key ideas is that the defining equations depend on the voltage polarity and current direction
- Example:  $p = \pm vi$
- You must examine how the polarity of  $v$  and the direction of  $i$  is labeled on the circuit diagram to determine the sign
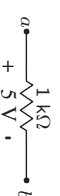
### Voltage Drops & Rises Defined

- The following statements are true and equivalent
  - There is a 5 V **drop** from  $a$  to  $b$
  - There is a 5 V **rise** from  $b$  to  $a$
  - There is a  $-5$  V **rise** from  $a$  to  $b$
  - There is a  $-5$  V **drop** from  $b$  to  $a$
- The first expression is the most common
- In most cases, we will be concerned with voltage drops




### Ideal Voltage Sources

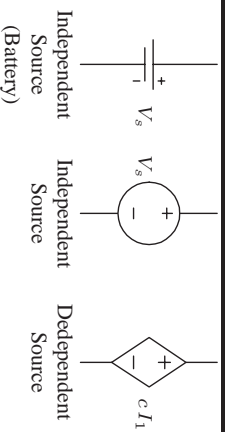


- **Ideal Voltage Source:** produces  $V_s$  volts regardless of the current absorbed or produced by the device
- The voltage produced may depend on some other circuit variable (current or voltage)

- The sign of  $V_s$  can be negative

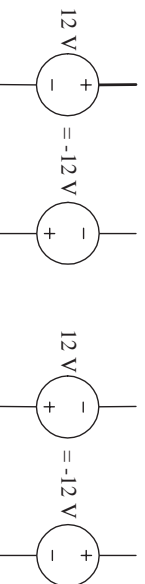


### Ideal Current Sources

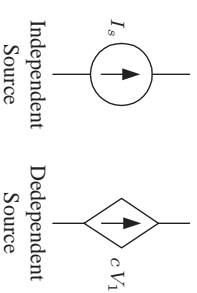

- **Ideal Current Source:** produces  $I_s$  amps regardless of the current in the device
- The current produced may depend on some other circuit variable (current or voltage)

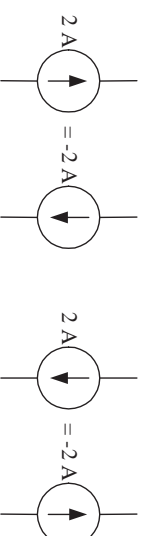- Note the sign of  $I_s$  can be negative



### Notes on Ideal Sources

- Ideal sources are models used to simplify analysis
- These devices do not exist physically
  - How much power can an ideal source produce?
  - How much power can a battery produce?
- Ideal models serve as a good approximation of physical devices, but only over a limited operating range
- We will use and discuss more accurate models later in the term