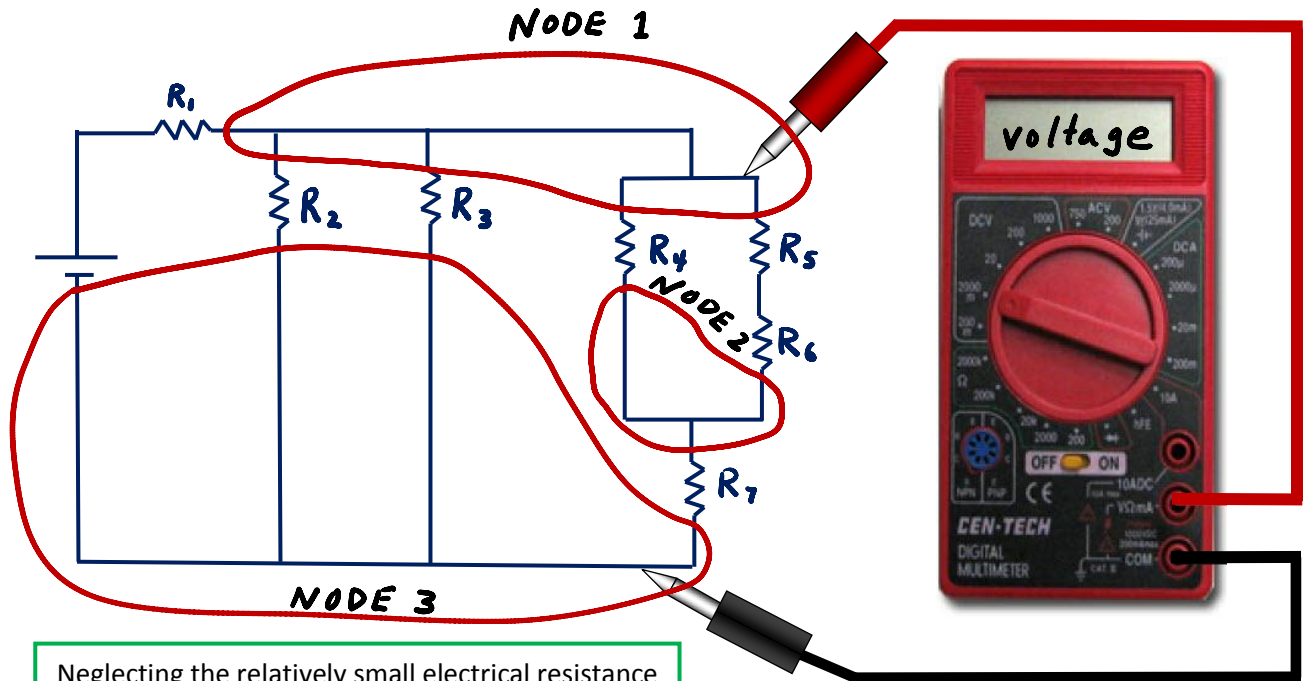



Implications of Kirchoff's Voltage Law (KVL):



Neglecting the relatively small electrical resistance of the "wires," the areas inside the circles can be considered "nodes."

Moving the multimeter probe to any part of the wire within a given red circle will not significantly influence the measured voltage.

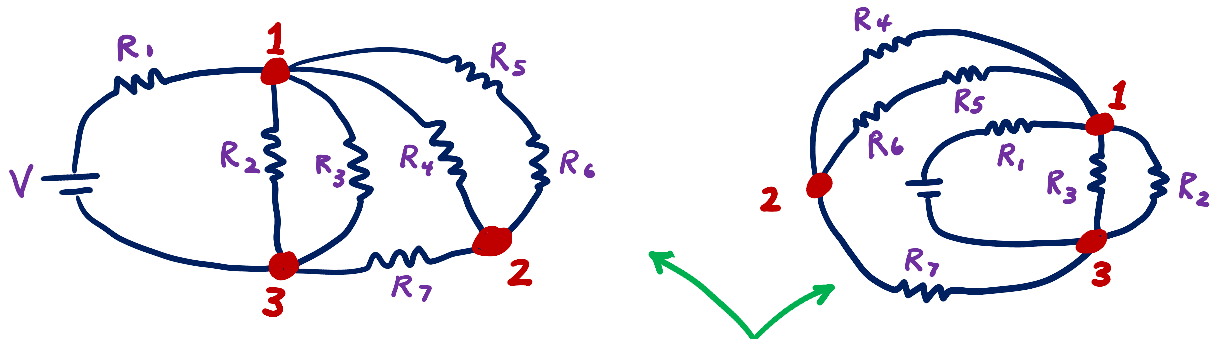We can redraw the circuit in various ways...



R_3 is between nodes 1 and 3
 R_7 is between nodes 2 and 3

Due to KVL, sets of circuit elements between two nodes are in **PARALLEL** and have **EQUAL** voltage drops:


$$\begin{aligned} \Delta V_{R3} &= \Delta V_{R2} & \text{and} & & \Delta V_{R4} &= \Delta V_{R5} + \Delta V_{R6} \\ \text{between nodes 1 and 3} & & & & \text{between nodes 1 and 2} \end{aligned}$$

$$\Delta V_{R5} + \Delta V_{R6} + \Delta V_{R7} = \Delta V_{R2}$$

between nodes 1 and 3

CLASS PROBLEM: Consider the circuit below where R_2 is a variable resistor (a resistor whose value can be changed by turning a knob). We would like to understand the variation of the total current leaving the power sources as a function of R_2 .

- Redraw the circuit so it is easier to tell which resistors are in parallel.
- Develop a function for the current I in terms of the resistance R_2 , and embed this function into Mathcad.
- Plot the current versus the value of R_2 , where R_2 varies from $100\ \Omega$ to $10,000\ \Omega$.
- Find the current when R_2 is equal to $220\ \Omega$, $470\ \Omega$, $1\ \text{k}\Omega$, and $10\ \text{k}\Omega$.

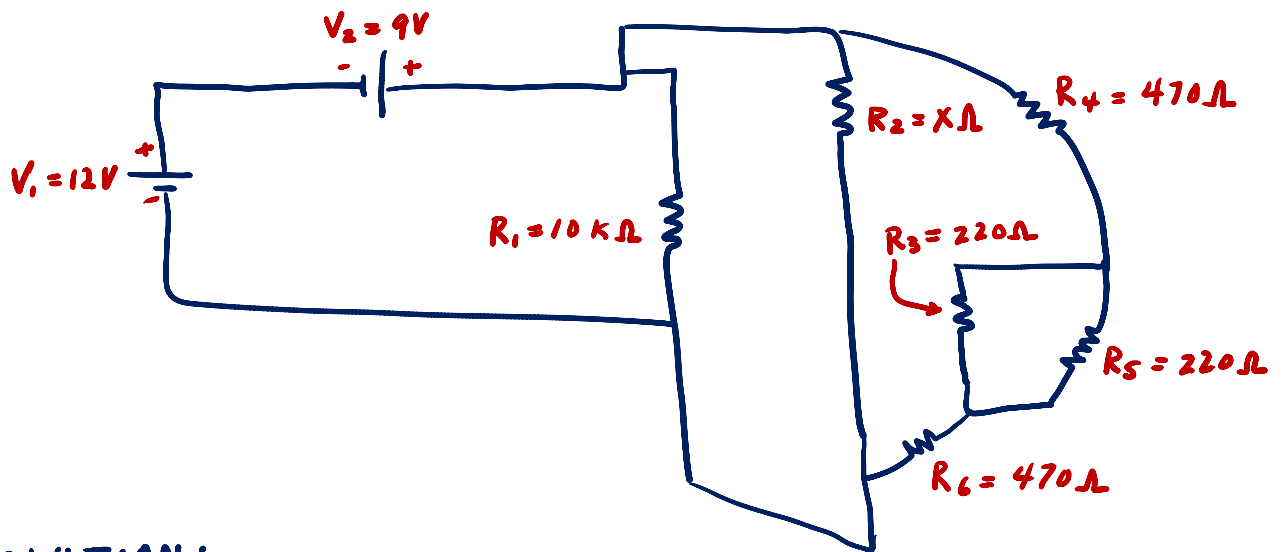

SOLUTION:

