

# Review of DC Circuit Analysis

EAS 199A Notes

EAS 199A: DC Circuit Summary

## Overview

1. Ohm's Law
2. Power dissipation
3. Resistors in series
4. Resistors in parallel

## Ohm's Law (1)


$$V = IR$$

where

$V$  = voltage drop across the resistor (V)


$I$  = current *through* the resistor (A)

$R$  = resistance ( $\Omega$ )

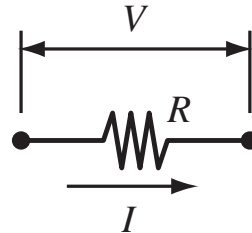
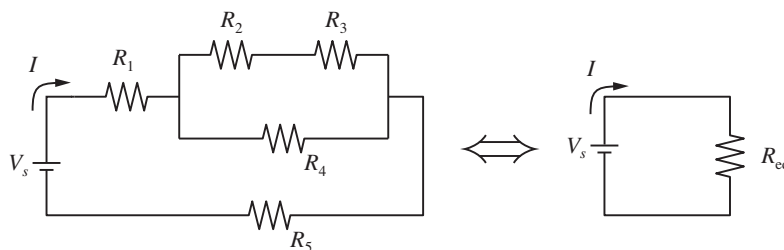
## Ohm's Law (2)

Complex arrangements of resistors can be reduced to an equivalent resistance,  $R_{\text{eq}}$ , and then Ohm's law can be applied to the equivalent circuit.




$$R_{\text{eq}} = R_1 + \frac{1}{\frac{1}{R_2+R_3} + \frac{1}{R_4}} + R_5$$

$$V_s = IR_{\text{eq}}$$
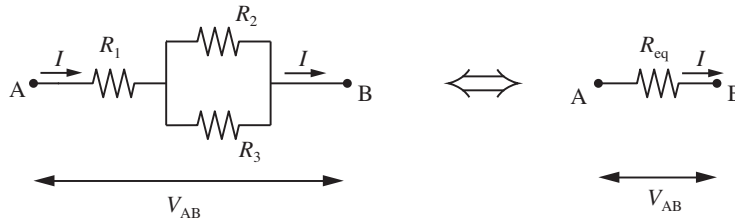
### Ohm's Law (3)

Ohm's law can be applied to any continuous segment of a circuit.




Ohm's law *cannot* be applied to LEDs, capacitors, inductors.

Ohm's law can only be applied to devices that act like simple resistors: e.g., simple resistors, incandescent light bulbs, and long lengths of wire.
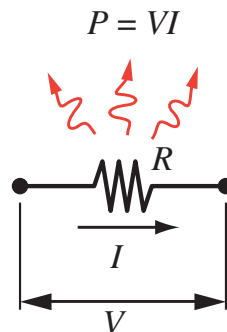
### Power Dissipation (1)

When electrical current flows through resistor, electrical power is dissipated.



$$P = VI$$


## Power Dissipation (2)

Power dissipation can be computed from one of three formulas

$$P = VI \quad P = I^2R \quad P = \frac{V^2}{R}$$

In each case, the  $V$ ,  $I$ , and  $R$  refer to the values *for the circuit element under consideration*

## Resistors in Series

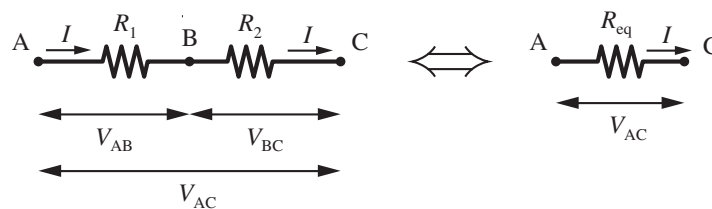

$$R_{eq} = R_1 + R_2$$


Kirchoff's voltage law tells us that the voltages across the resistors adds:

$$V_{AC} = V_{AB} + V_{BC}$$


Kirchoff's current law tells us that the current through the resistors is the same:

$$I_1 = I_2$$

## Resistors in Series on a Breadboard

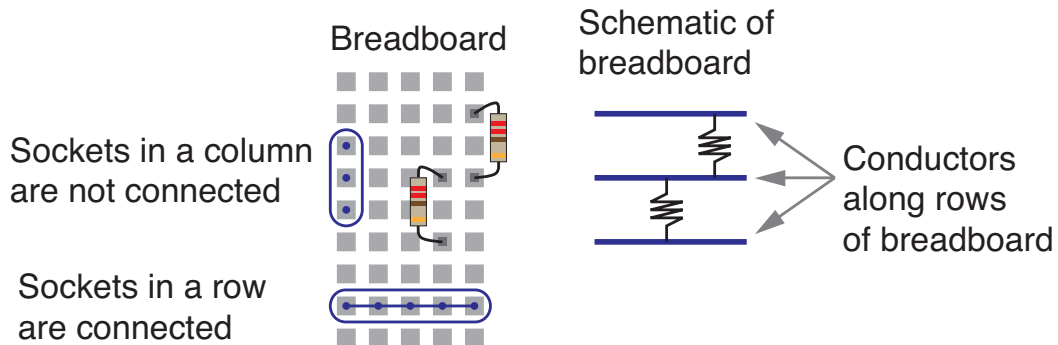

## Resistors in Parallel

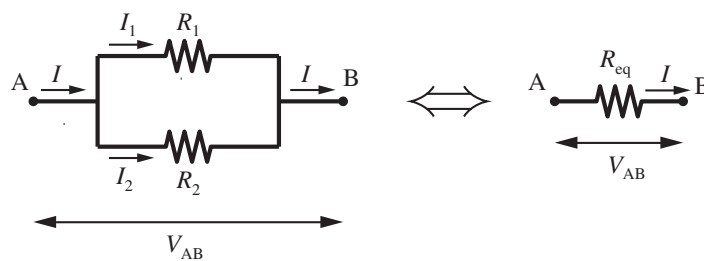

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$


Kirchoff's voltage law tells us that the voltages across the resistors is the same

$$V_1 = V_2 = V_{AB}$$

Kirchoff's current law tells us that the current through the resistors adds:

$$I = I_1 + I_2$$

## Resistors in Parallel on a Breadboard

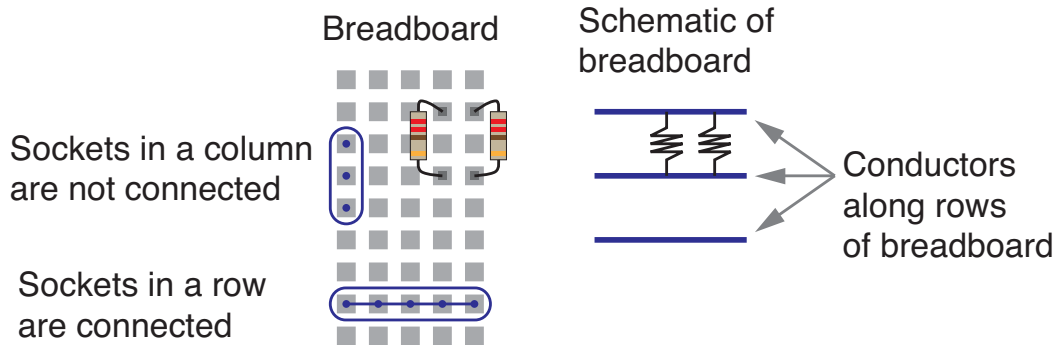


## Example: Power dissipation for one resistor in a circuit (1)

What power is dissipated by  $R_5$  in the circuit to the right? What is the *total* power dissipation of the circuit? Use the following system parameters.

$$V_s = 10 \text{ V}$$

$$R_1 = R_4 = 470 \ \Omega$$

$$R_2 = R_3 = R_5 = 330 \ \Omega$$

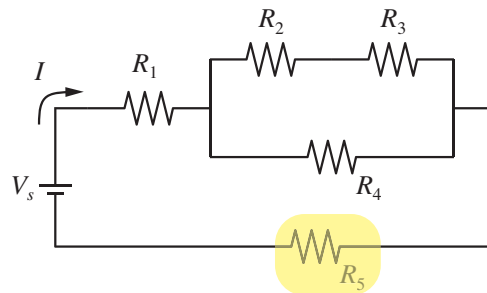


The power is  $P_5 = V_5 I_5$ , but neither  $V_5$  nor  $I_5$  is known.

Use the alternative formula  $P_5 = I_5^2 R_5$ . Since  $R_5$  is known, the first step is to determine the current  $I_5$ . Note that the current through  $R_5$  is the same as the total current leaving the battery, i.e.,  $I_5 = I$ .
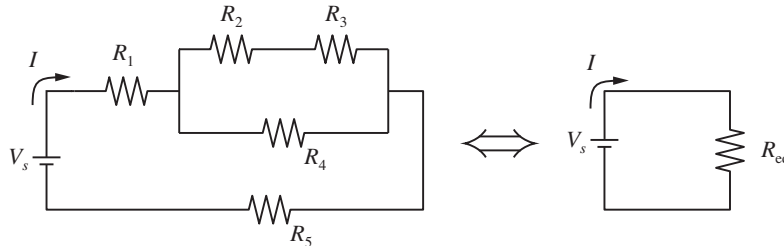
### Example: Power dissipation for one resistor in a circuit (2)

**Solution Step 1:** Replace the resistor network with a single equivalent resistor.



$$R_{\text{eq}} = R_1 + \frac{1}{\frac{1}{R_2 + R_3} + \frac{1}{R_4}} + R_5 \quad V_s = IR_{\text{eq}}$$

### Example: Power dissipation for one resistor in a circuit (3)

**Solution Step 2:** Substitute the known values to compute  $R_{\text{eq}}$ .

$$\begin{aligned} R_{\text{eq}} &= R_1 + \frac{1}{\frac{1}{R_2 + R_3} + \frac{1}{R_4}} + R_5 \\ &= 470 \, \Omega + \frac{1}{\frac{1}{330 + 330 \, \Omega} + \frac{1}{470 \, \Omega}} + 330 \, \Omega \\ &= 1074.5 \, \Omega \end{aligned}$$

**Solution Step 3:** Apply Ohm's law to the equivalent circuit to compute the total current,  $I$ .

$$V_s = IR_{\text{eq}} \implies I = \frac{V_s}{R_{\text{eq}}} = \frac{10 \, \text{V}}{1074.5 \, \Omega} = 0.00931 \, \text{A}$$

### Example: Power dissipation for one resistor in a circuit (4)

**Solution Step 4:** Now that  $I$  is known, it is easy to calculate the power dissipated by  $R_5$

$$P_5 = I_5^2 R_5 = (0.00931 \text{ A})^2 (330 \Omega) = 0.0286 \text{ W} = 28.6 \text{ mW}$$

**Solution Step 5:** The total power dissipated in the entire circuit is

$$P_{\text{total}} = V_s I = (10 \text{ V}) (0.00931 \text{ A}) = 0.0931 \text{ W} = 93.1 \text{ mW}.$$

Of course, the power dissipated at  $R_5$  must be less than the total power dissipated in the circuit.

$$P_5 = 28.6 \text{ mW}, \quad P_{\text{total}} = 93.1 \text{ mW}, \quad \text{and} \quad P_5 < P_{\text{total}} \quad (\text{as expected}).$$

### Example: Power dissipation for one resistor in a circuit (5)

**Practice:** What is the power dissipated by  $R_2$ ? *Answer:* 4.9 mW.

