

Combined series and parallel circuits

TIPS

- ① Combine all series resistors.
- ② Combine all parallel resistors.
- ③ Repeat ① and ② until R_{eq} is found.