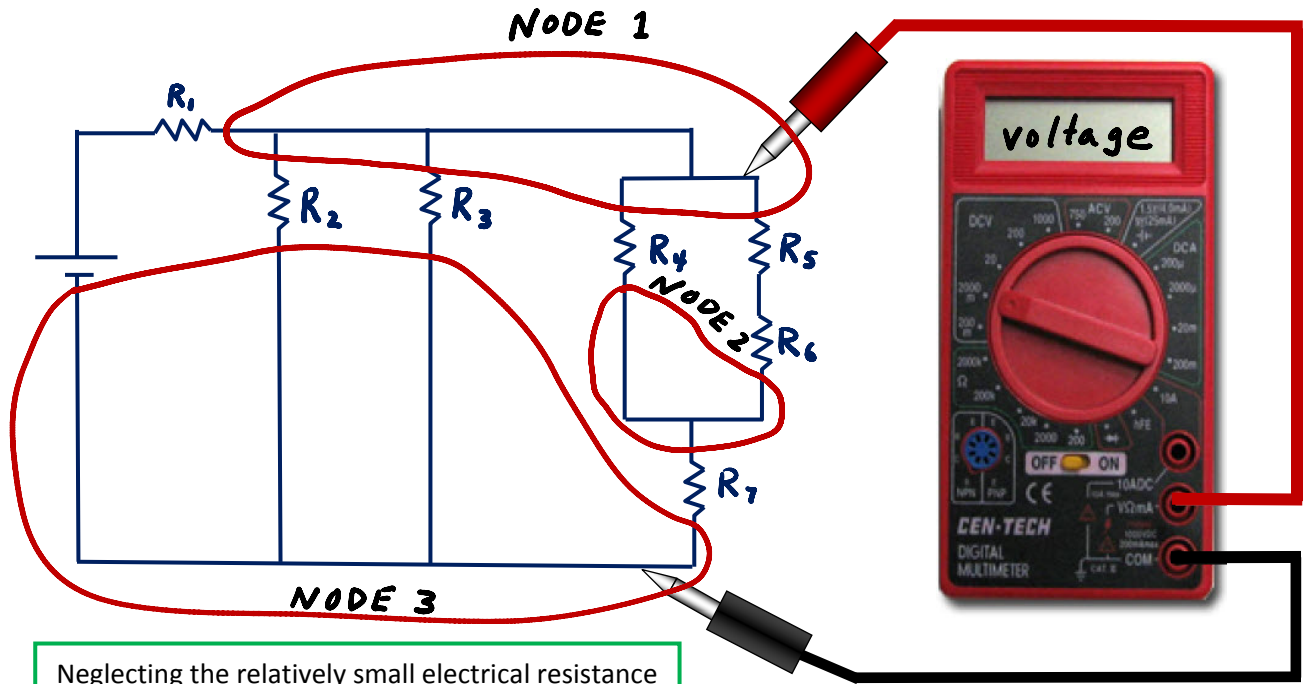



Implications of Kirchoff's Voltage Law (KVL):



Neglecting the relatively small electrical resistance of the "wires," the areas inside the circles can be considered "nodes."

Moving the multimeter probe to any part of the wire within a given red circle will not significantly influence the measured voltage.

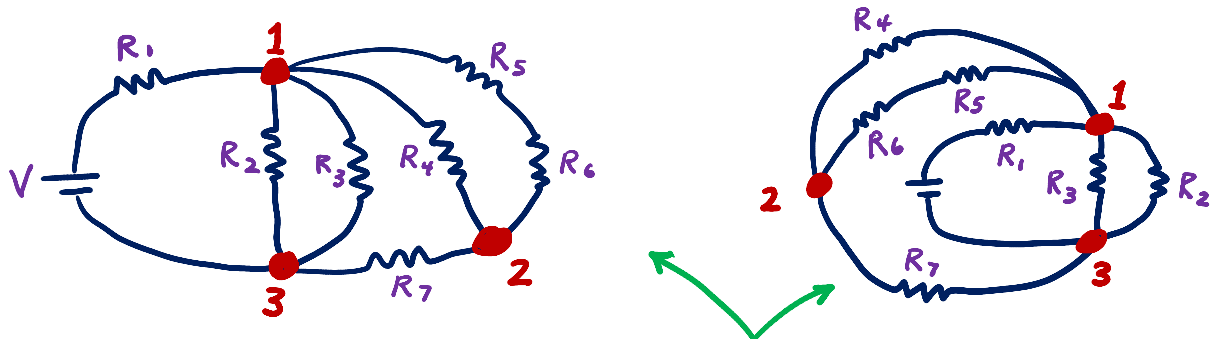We can redraw the circuit in various ways...



R_3 is between nodes 1 and 3
 R_7 is between nodes 2 and 3

Due to KVL, sets of circuit elements between two nodes are in **PARALLEL** and have **EQUAL** voltage drops:


$$\begin{aligned} \Delta V_{R3} &= \Delta V_{R2} & \text{and} & & \Delta V_{R4} &= \Delta V_{R5} + \Delta V_{R6} \\ \text{between nodes 1 and 3} & & & & \text{between nodes 1 and 2} \end{aligned}$$

$$\Delta V_{R5} + \Delta V_{R6} + \Delta V_{R7} = \Delta V_{R2}$$


between nodes 1 and 3

CLASS PROBLEM: Consider the circuit below where R_2 is a variable resistor (a resistor whose value can be changed by turning a knob). We would like to understand the variation of the total current leaving the power sources as a function of R_2 .

- Redraw the circuit so it is easier to tell which resistors are in parallel.
- Develop a function for the current I in terms of the resistance R_2 , and embed this function into Mathcad.
- Plot the current versus the value of R_2 , where R_2 varies from $100\ \Omega$ to $10,000\ \Omega$.
- Find the current when R_2 is equal to $220\ \Omega$, $470\ \Omega$, $1\ \text{k}\Omega$, and $10\ \text{k}\Omega$.

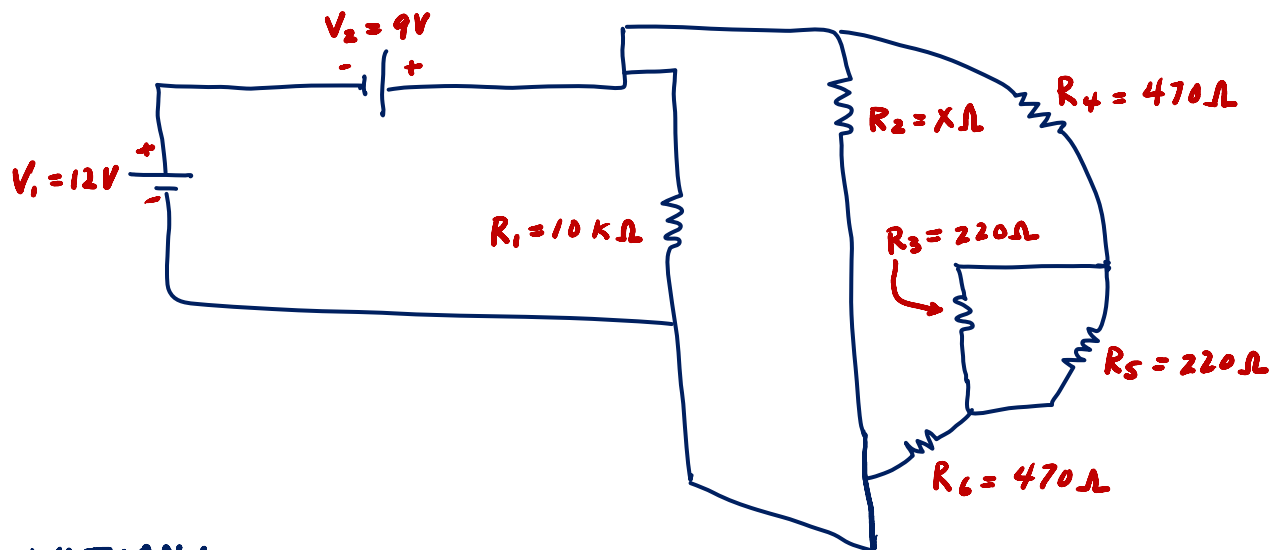

SOLUTION:

 

Mathcad Example of Functions and Plots:

Keystrokes

$$R_1 := 10000\Omega$$

R.1 : 10000* <enter>

$$R_3 := 220\Omega$$

R.3 : 220* <enter>

$$R_4 := 470\Omega$$

R.4 : 470* <enter>

$$R_5 := 220\Omega$$

R.5 : 470* <enter>

$$R_6 := 470\Omega$$

R.6 : 470* <enter>

$$V_1 := 12 \cdot V$$

V.1 : 12*V <enter>

$$V_2 := 9 \cdot V$$

V.2 : 9*V <enter>

$$V_3 := V_1 + V_2$$

V.3 : V.1 + V.2

$$R_{eq1} := \frac{1}{\frac{1}{R_3} + \frac{1}{R_5}}$$

R.eq1 : 1 / 1 / R.3 <space> + 1 / R.5 <enter>

$$R_{eq2} := R_4 + R_{eq1} + R_6$$

R.eq2 : R.4 + R.eq1 + R.6

$$R_{eq3}(R_2) := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2 \cdot \Omega} + \frac{1}{R_{eq2}}}$$

R.eq3(R.2) : 1 / 1 / R.1 <space> + 1 / R.2* <space> +
1 / R.eq2 <enter>

$$I(R_2) := \frac{V_3}{R_{eq3}(R_2)}$$

I(R.2) : V.3 / R.eq3(R.2) <enter>


$$R_2 := 100, 110.. 10000$$

R.2 : 100 , 110 ; 10000 <enter>

To insert the plot:

Insert > Graph > XY Plot

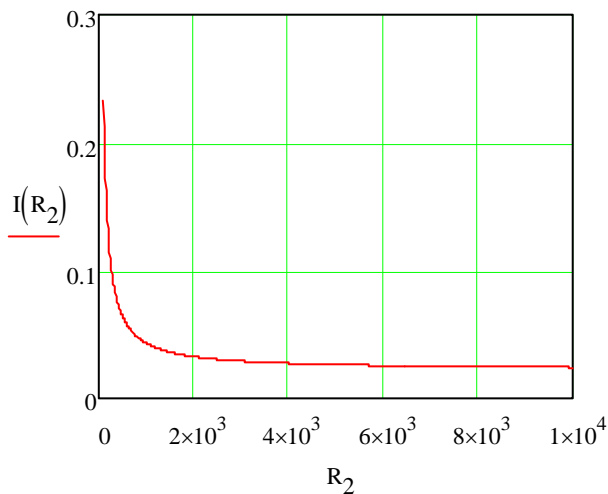Type in R.2 and I(R.2) in the placeholders



Keystrokes

$$I(220) = 0.118A$$

$$I(220) =$$

$$I(470) = 0.067A$$

$$I(470) =$$

$$I(1000) = 0.043A$$

$$I(1000) =$$

$$I(10000) = 0.024A$$

$$I(10000) =$$