

Homework #3

Figure 7-56 gives the outputs for each state,
no 2 states have the same outputs
 $\therefore$ no equivalent states exist

The state transition table is given in
Table 7-14 (pg 576). Since there
are 3 FFs and 3 inputs you can't
use 1 K-map.

Fortunately, Q_1 and Q_0 are simple
enough so that K-maps may not be req'd.

e.g., Q_0 (equivalently D_0) = 1 when

$$D_0 = \bar{Q}_2 \cdot \bar{Q}_1 \cdot \bar{Q}_0 \cdot [L \cdot \bar{R} \cdot \bar{H} + \bar{L} \cdot R \cdot \bar{H}] \\ + \underbrace{\bar{Q}_2 \cdot \bar{Q}_1 \cdot Q_0 \cdot \bar{H} + Q_2 \cdot \bar{Q}_1 \cdot Q_0 \cdot \bar{H}}_{\bar{Q}_1 \cdot Q_0 \cdot \bar{H}}$$

$$= \bar{Q}_2 \cdot \bar{Q}_1 \cdot \bar{Q}_0 \cdot \bar{H} \cdot [L \oplus R]$$

$$D_1 = \underbrace{\bar{Q}_2 \cdot \bar{Q}_1 \cdot Q_0 \cdot \bar{H} + \bar{Q}_2 \cdot Q_1 \cdot Q_0 \cdot \bar{H}}_{\bar{Q}_2 \cdot Q_0 \cdot \bar{H}} \\ + \underbrace{Q_2 \cdot \bar{Q}_1 \cdot Q_0 \cdot \bar{H} + Q_2 \cdot Q_1 \cdot Q_0 \cdot \bar{H}}_{Q_2 \cdot Q_0 \cdot \bar{H}}$$

$$= Q_0 \cdot \bar{H}$$

for D_3 notice that 6 of the 8 times it is a logic 1 it is only a function of H , Q_2 , Q_1 and Q_0

$Q_1 Q_0$					
H	Q_2	00	01	11	10
	00				
	01		1	1	
	11		1	1	
	10		1	1	

$$D_{3A} = H \cdot Q_0 + Q_2 \cdot Q_0$$

for the last 2 instances $Q_2 = Q_1 = Q_0$, so

$Q_2 Q_1$					
H	Q_0	00	01	11	10
	0		1	1	
	1	1	1	1	1

$$D_{3B} = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 \cdot [H + R]$$

$$\therefore D = D_{3A} + D_{3B}$$

$$= H \cdot Q_0 + Q_2 \cdot Q_0 + \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 H + \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 R$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0				1
	1	1			

$$LC = Q_2 \bar{Q}_1 \bar{Q}_0 + \bar{Q}_2 Q_1 \bar{Q}_0$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0			1	1
	1	1			

$$LB = Q_2 \bar{Q}_1 \bar{Q}_0 + \bar{Q}_2 Q_1$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0		1	1	1
	1	1			

$$LA = Q_2 \bar{Q}_1 \bar{Q}_0 + \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0				
	1	1	1	1	1

$$RA = Q_2$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0				
	1	1		1	1

$$RB = Q_2 \bar{Q}_0 + Q_2 Q_1$$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0				
	1	1			1

$$RC = Q_2 \bar{Q}_0$$