

/*

The arbiter desgin shown below uses the dataflow level of abstraction. Of course you could also have done this at the behavioral level using if-then-else or case statements.

To illustrate the behavior, the eight inputs and eight outputs are declared individually to illustrate the behavior on the timing diagram. You did NOT have to do this; you could have declared the inputs and outputs as bus variables.

The assumption is the request inputs (r0 thru r7) and the grant outputs (g0 thru g7) are active high signals.

*/

```
module arbiter(r0, r1, r2, r3, r4, r5, r6, r7, g0, g1, g2, g3,
              g4, g5, g6, g7);
```

```
  input r0,r1,r2,r3,r4,r5,r6,r7; // request signals
  output g0,g1,g2,g3,g4,g5,g6,g7; // grant signals
```

```
  // define the grant outputs (active high)
```

```
  assign g0 = r0;           // highest priority
  assign g1 = ~r0 & r1;
  assign g2 = ~r0 & ~r1 & r2;
  assign g3 = ~r0 & ~r1 & ~r2 & r3;
  assign g4 = ~r0 & ~r1 & ~r2 & ~r3 & r4;
  assign g5 = ~r0 & ~r1 & ~r2 & ~r3 & ~r4 & r5;
  assign g6 = ~r0 & ~r1 & ~r2 & ~r3 & ~r4 & ~r5 & r6;
  assign g7 = ~r0 & ~r1 & ~r2 & ~r3 & ~r4 & ~r5 & ~r6 & r7; // lowest priority
```

```
endmodule
```

```
module top;
  reg R0,R1,R2,R3,R4,R5,R6,R7;
```

```
  wire G0, G1, G2, G3, G4, G5, G6, G7;
```

```
  // instantiate arbiter
```

```
  arbiter g2(R0,R1,R2,R3,R4,R5,R6,R7,G0,G1,G2,G3,G4,G5,G6,G7);
```

```
  // conduct exhaustive test
```

```
  initial
```

```
  begin
```

```
    R0=0; R1=0; R2=0; R3=0; R4=0; R5=0; R6=0; R7=0; // no request case
```

```
    #5 R0=1; R1=1'bx; R2=1'bx; R3=1'bx; R4=1'bx; R5=1'bx;
```

```
      R6=1'bx; R7=1'bx;
```

```
    #5 R0 = 0; R1=1;
```

```
    #5 R1 = 0; R2=1;
```

```
    #5 R2 = 0; R3=1;
```

```
    #5 R3 = 0; R4=1;
```

```
    #5 R4 = 0; R5=1;
```

```
    #5 R5 = 0; R6=1;
```

```
    #5 R6 = 0; R7=1;
```

```
    #5 R7 = 0; // no request case
```

```
    #5 $finish;
```

```
  end
```

```
endmodule
```

