

Example 7-17 Use of @ Operator*

@*
@(*)

```
//Combination logic block using the or operator
//Cumbersome to write and it is easy to miss one input to the block
always @(a or b or c or d or e or f or g or h or p or m)
begin
    out1 = a ? b+c : d+e;
    out2 = f ? g+h : p+m;
end

//Instead of the above method, use @(*) symbol
//Alternately, the @* symbol can be used
//All input variables are automatically included in the
//sensitivity list.
always @(*)
begin
    out1 = a ? b+c : d+e;
    out2 = f ? g+h : p+m;
end
```

Example 7-20 Case Statement with x and z

```
module demultiplexer1_to_4 (out0, out1, out2, out3, in, s1, s0);

// Port declarations from the I/O diagram
output out0, out1, out2, out3;
reg out0, out1, out2, out3;
input in;
input s1, s0;

always @(s1 or s0 or in)
case ({s1, s0}) //Switch based on control signals
    2'b00 : begin out0 = in; out1 = 1'bz; out2 = 1'bz; out3 = 1'bz; end
    2'b01 : begin out0 = 1'bz; out1 = in; out2 = 1'bz; out3 = 1'bz; end
    2'b10 : begin out0 = 1'bz; out1 = 1'bz; out2 = in; out3 = 1'bz; end
    2'b11 : begin out0 = 1'bz; out1 = 1'bz; out2 = 1'bz; out3 = in; end

    //Account for unknown signals on select. If any select signal is x
    //then outputs are x. If any select signal is z, outputs are z.
    //If one is x and the other is z, x gets higher priority.
    2'bx0, 2'bx1, 2'bxz, 2'bxz, 2'b0x, 2'bx, 2'bzx :
        begin
            out0 = 1'bx; out1 = 1'bx; out2 = 1'bx; out3 = 1'bx;
        end
    2'bz0, 2'bz1, 2'bzz, 2'b0z, 2'b1z :
        begin
            out0 = 1'bz; out1 = 1'bz; out2 = 1'bz; out3 = 1'bz;
        end
    default: $display("Unspecified control signals");
endcase

endmodule
```

Example 7-26 *Sequential Blocks*

```
//Illustration 1: Sequential block without delay
reg x, y;
reg [1:0] z, w;

initial
begin
    x = 1'b0;
    y = 1'b1;
    z = {x, y};
    w = {y, x};
end

//Illustration 2: Sequential blocks with delay.
reg x, y;
reg [1:0] z, w;

initial
begin
    x = 1'b0; //completes at simulation time 0
    #5 y = 1'b1; //completes at simulation time 5
    #10 z = {x, y}; //completes at simulation time 15
    #20 w = {y, x}; //completes at simulation time 35
end
```

Example 7-27 *Parallel Blocks*

```
//Example 1: Parallel blocks with delay.
reg x, y;
reg [1:0] z, w;

initial
fork
    x = 1'b0; //completes at simulation time 0
    #5 y = 1'b1; //completes at simulation time 5
    #10 z = {x, y}; //completes at simulation time 10
    #20 w = {y, x}; //completes at simulation time 20
join
```

Example 7-35

Behavioral 4-to-1 Multiplexer

```
// 4-to-1 multiplexer. Port list is taken exactly from
// the I/O diagram.
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);

// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;
//output declared as register
reg out;

//recompute the signal out if any input signal changes.
//All input signals that cause a recomputation of out to
//occur must go into the always @(...) sensitivity list.
always @(s1 or s0 or i0 or i1 or i2 or i3)
begin
    case ({s1, s0})
        2'b00: out = i0;
        2'b01: out = i1;
        2'b10: out = i2;
        2'b11: out = i3;
        default: out = 1'bx;
    endcase
end

endmodule
```

Example 7-36 Behavioral 4-bit Counter Description

```
//4-bit Binary counter
module counter(Q , clock, clear);

// I/O ports
output [3:0] Q;
input clock, clear;
//output defined as register
reg [3:0] Q;


always @( posedge clear or negedge clock)
begin
    if (clear)
        Q <= 4'd0; //Nonblocking assignments are recommended
                    //for creating sequential logic such as flipflops
    else
        Q <= Q + 1; // Modulo 16 is not necessary because Q is a
                    // 4-bit value and wraps around.
end

endmodule
```

Note:
Initial value "
for reg is "x"

Let's talk about modeling FSMs

Moore

 

```

module moore_fsm (r, clock, Z);
input r, clock;
output Z;
reg Z;
  
```

```

//make state assignment (full encoded)
parameter A=0, B=1, C=2, D=3;
reg [1:0] state;
  
```

```

always @(posedge clock) // update state
case(state)
A: if(r) state=B;
B: if(r) state=C;
C: if(r) state=D;
D: if(r) state=B else state=A;
endcase
  
```

```

always@(state) // update output
case(state)
A,D: Z=0;
B,C: Z=1;
endcase
  
```

```

endmodule
  
```

If (!reset)
state = A;

else

Mealy

	next		Output	
	r=0	r=1	r=0	r=1
A	A	D	0	1
B	B	A	1	0
C	C	B	0	1
D	C	B	0	0

```
Module Mealy-FSM (r, clock, reset, z);
```

```
  input r, clock, reset;
```

```
  output z;
```

```
  reg z;
```

```
  parameter A=1, B=2, C=3, D=4;
```

```
  reg [1:0] present, next;
```

```
  // sequential part
```

```
  always @(posedge clock or  
          negedge reset)
```

```
    if (!reset)
```

```
      present = A;
```

```
    else
```

```
      present = next;
```

always @ (present or r) // must check for both

begin: combinational-part

case (present)

A: if (r)
begin z=1; next=D; end
else z=0;

B: if (r)
begin z=0; next=A; end
else z=1;

C: if (r)
begin z=1; next=B; end
else z=0;

D: if (r)
begin z=0; next=B; end
else
begin z=0; next=C; end

endcase

end // comb-part

endmodule

 


Figure 8-8 Two interacting processes.

```

`timescale 1ns/100ps
module interacting (serial_in, clk_rx, parallel_out);
  input serial_in, clk_rx;
  output reg [7:0] parallel_out;

  reg ready, ack;
  reg [0:7] data;

  `include "read_word.v" // Task read_word is defined in
                        // this file.

  always
  begin: RX
    read_word (serial_in, clk_rx, data);
    // The task read_word reads the serial data on every
    // clock cycle and converts to a parallel data in
    // signal data. It takes 10ns to do this.
    ready <= 1;
    wait (ack);
    ready <= 0;
    #40;
  end

  always
  begin: MP
    #25;
    parallel_out <= data;
    ack <= 1;
    #25 ack <= 0;
    wait (ready);
  end
end
endmodule

```

Handshaking example