

You are to design and build a LFSR that implements the generating polynomial $G(X) = 1 + X^3 + X^4$

Connect the output of your LFSR to LEDs and record the output as you apply clock pulses. In your report specify the test pattern sequence generated by your circuit. Also, comment on whether or not the generating polynomial is primitive.