 


2-1

```
module Continuous (StatIn, StatOut);  
  input StatIn;  
  output StatOut;  
  
  assign StatOut = ~ StatIn; // Continuous assignment.  
endmodule  
// Synthesized netlist is shown in Figure
```




2-2

```

module Blocking (Preset, Count);
    input [0:2] Preset;
    output [3:0] Count;
    reg [3:0] Count;

    always @ (Preset)
        Count = Preset + 1;
        // Blocking procedural assignment.
endmodule
    
```

 // Synthesized netlist is shown in Figure 2.1.



Count 3 = 0 ✓✓
 Count 2 = 1 ✓✓
 Count 1 = 0 ✓✓
 Count 0 = 0 ✓✓


2-3

```

module NonBlocking (RegA, Mask, RegB);
  input [3:0] RegA, Mask;
  output [3:0] RegB;
  reg [3:0] RegB;

  always @ (RegA or Mask)
    RegB <= RegA & Mask;
    // Non-blocking procedural assignment.
endmodule
// Synthesized netlist is shown in Figure

```

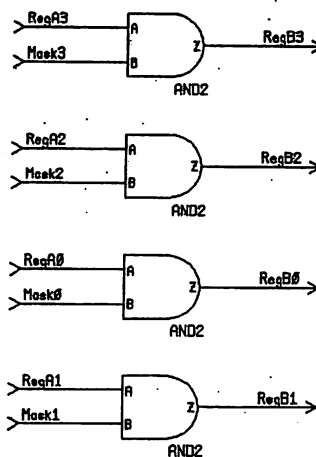

2-3

```

module Target (Clk, RegA, RegB, Mask);
  input Clk;
  input [3:0] RegA, Mask;
  output [3:0] RegB;
  reg [3:0] RegB;


```

```

  always @ (posedge Clk)
    RegB <= RegA & Mask;
endmodule

```

 // Synthesized netlist is shown in Figure




```

module FullAdder (A, B, CarryIn, Sum, CarryOut);
  input A, B, CarryIn;
  output Sum, CarryOut;

  assign Sum = (A ^ B) ^ CarryIn;
  assign CarryOut = (A & B) | (B & CarryIn) |
                    (A & CarryIn);
endmodule
// Synthesized netlist is shown in Figure

```

 


2-11

```

module ConstantShift (DataMux, Address);
input [0:3] DataMux;
output [0:5] Address;

    assign Address = (~ DataMux) << 2;
endmodule
// Synthesized netlist is shown in Figure

```

 


2-12

```

module VariableShift (MemDataReg, Amount, InstrReg);
input [0:2] MemDataReg;
input [0:1] Amount;
output [0:2] InstrReg;

assign InstrReg = MemDataReg >> Amount;
endmodule
// Synthesized netlist is shown in Figure

```

 


2-12

```

module VectorOperands (Bi, Stdy, Tap);
input [0:3] Bi, Stdy;
output [0:3] Tap;

    assign Tap = Bi ^ Stdy;
endmodule
// Synthesized netlist is shown in Figure

```

 

```
module PartSelect (A, C, ZCat);
```


```
input [3:0] A, C;
```

```
output [3:0] ZCat;
```

```
assign ZCat[2:0] = {A[2], C[3:2]};
```

```
endmodule
```

 // Synthesized netlist is shown in Figure 2




```

module ConstantIndex (A, C, Reg_File, ZCat);
input [3:0] A, C;
input [3:0] Reg_File;
output [3:0] ZCat;

    assign ZCat[3:1] = {A[2], C[3:2]};
    assign ZCat[0] = Reg_File[3];
endmodule
// Synthesized netlist is shown in Figure

```

 

```

module NonComputeRight (Data, Index, Dout);
  input [0:3] Data;
  input [1:2] Index;
  output Dout;

  assign Dout = Data [Index];
endmodule
// Synthesized netlist is shown in Figure 2-17.

```

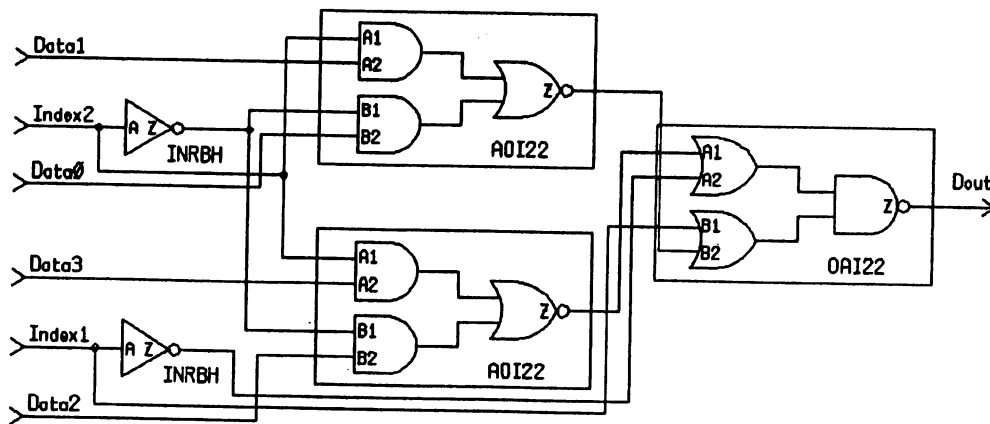



Figure 2-17 Non-constant bit-select generates a multiplexer.

```

module NonComputeLeft (Mem, Store, Addr);
  output [7:0] Mem;
  input Store;
  input [1:3] Addr;

  assign Mem [Addr] = Store;
endmodule
// Synthesized netlist is shown in Figure

```

 

(a decoder)

```

module ConditionalExpression (StartXM, ShiftVal,
                             Reset, StopXM);
  input StartXM, ShiftVal, Reset;
  output StopXM;

```

```

  assign StopXM = (! Reset) ? StartXM ^ ShiftVal :
                  StartXM | ShiftVal;


```


```

endmodule

```

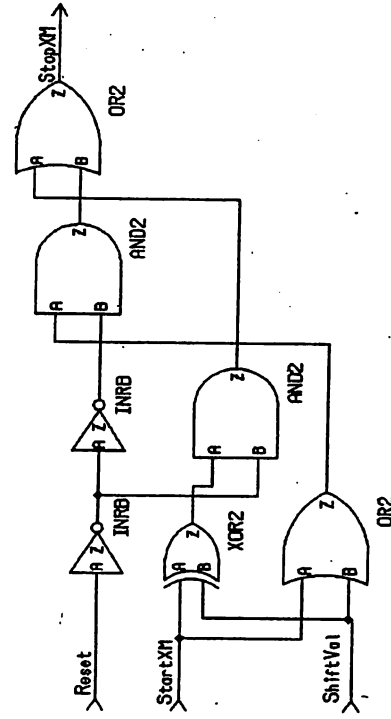// Synthesized netlist is shown in Figure



 

```

module my_and1(a,b,y);
input a,b;
output y;
reg y;

always@(a) ✓
    if(a & b)
        y = 1;
    else
        y = 0;

endmodule

```

```

module my_and2(a,b,y);
input a,b;
output y;
reg y;

always@(a or b) ✓
    if(a & b)
        y = 1;
    else
        y = 0;

endmodule

```

```

module test;
reg A,B;
wire Y1,Y2;

integer i;

my_and1 g2(A,B,Y1);
my_and2 g3(A,B,Y2);

initial
begin
    for(i=0;i<=3;i=i+1)
        begin
            {A,B}=i;
            #5;
        end
    end
end

initial #20 $finish;

endmodule

```


2-23

```

module SelectOneOf (A, B, Z);
  input [1:0] A, B;
  output [1:0] Z;
  reg [1:0] Z;

  always @ (A or B)
    if (A > B)
      Z = A;
    else
      Z = B;
endmodule

```

 

2-23

2-26


```

module Compute (Marks, Grade);
  input [1:4] Marks;
  output [0:1] Grade;
  reg [0:1] Grade;

  parameter FAIL = 1, PASS = 2, EXCELLENT = 3;

  always @ (Marks)
    if (Marks < 5)
      Grade = FAIL;
    else if ((Marks >= 5) & (Marks < 10))
      Grade = PASS;
endmodule

```

 

2-26


2-27

```

module ComputeNoLatch (Marks, Grade);
  input [1:4] Marks;
  output [0:1] Grade;
  reg [0:1] Grade;
  parameter FAIL = 1, PASS = 2, EXCELLENT = 3;

  always @ (Marks)
    if (Marks < 5)
      Grade = FAIL;
    else if ((Marks >= 5) && (Marks < 10))
      Grade = PASS;
    else
      Grade = EXCELLENT;
endmodule

```

 

2-27


```

module StateUpdate (CurrentState, Zip);
  input [0:1] CurrentState;
  output [0:1] Zip;
  reg [0:1] Zip;

  parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;

  always @ (CurrentState)
    case (CurrentState)
      S0,
      S3: Zip = 0;
      S1: Zip = 3;
    endcase
endmodule

```

 

```

...
always @ (CurrentState)
begin
  Zip = 0;          // This statement added.

  case (CurrentState)
  ...
  endcase
end

```

2-34


```

module NextStateLogic (NextToggle, Toggle);
  input [1:0] Toggle;
  output [1:0] NextToggle;
  reg [1:0] NextToggle;

  always @ (Toggle)
    case (Toggle)
      2'b01 : NextToggle = 2'b10;
      2'b10 : NextToggle = 2'b01;
    endcase

endmodule

```

 

2-34

2-35

```


module NextStateLogicFullCase (NextToggle, Toggle);
  input [1:0] Toggle;
  output [1:0] NextToggle;
  reg [1:0] NextToggle;

```

```

  always @ (Toggle)
    case (Toggle) // synthesis full_case
      2'b01 : NextToggle = 2'b10;
      2'b10 : NextToggle = 2'b01;
    endcase
endmodule

```

 

2-35

```

module PriorityLogic (NextToggle, Toggle);
  input [2:0] Toggle;
  output [2:0] NextToggle;
  reg [2:0] NextToggle;


  always @ (Toggle)
    casex (Toggle)
      3'bxx1 : NextToggle = 3'b010;
      3'bx1x : NextToggle = 3'b110;
      3'b1xx : NextToggle = 3'b001;
      default : NextToggle = 3'b000;
    endcase
endmodule

```

```

if (Toggle[0] == 'b1)
  NextToggle = 3'b010;
else if (Toggle[1] == 'b1)
  NextToggle = 3'b110;
else if (Toggle[2] == 'b1)
  NextToggle = 3'b001;
else
  NextToggle = 3'b000;

```

 

2-37

```

module ParallelCase (NextToggle, Toggle);
  input [2:0] Toggle;
  output [2:0] NextToggle;
  reg [2:0] NextToggle;

  always @ (Toggle)
    casex (Toggle)          // synthesis parallel_case
      3'bxx1 : NextToggle = 3'b010;
      3'bx1x : NextToggle = 3'b110;
      3'b1xx : NextToggle = 3'b001;
      default : NextToggle = 3'b000;
    endcase
endmodule

```

```


if (Toggle[0] == 'b1)
  NextToggle = 3'b010;

if (Toggle[1] == 'b1)
  NextToggle = 3'b110;

if (Toggle[2] == 'b1)
  NextToggle = 3'b001;

if ((Toggle[0] != 'b1) &&
    (Toggle[1] != 'b1) &&
    (Toggle[2] != 'b1))
  NextToggle = 3'b000;

```

 

2-37

2-44


```

output [3:0] Line;
reg [3:0] Line;

integer J;

always @ (Address)
  for (J = 3; J >= 0; J = J - 1)
    if (Address == J)
      Line[J] = 1;
    else
      Line[J] = 0;
endmodule

```

 


When the for-loop is expanded, the following four if statements are obtained.

```

if (Address == 3) Line[3] = 1; else Line[3] = 0;
if (Address == 2) Line[2] = 1; else Line[2] = 0;
if (Address == 1) Line[1] = 1; else Line[1] = 0;
if (Address == 0) Line[0] = 1; else Line[0] = 0;

```

2-44

 

Constraining combinational outputs that drive combinational inputs

Assume CLK period = 10 ns

Assume $t_{su} = t_h = 0$