


```

module NextStateLogic (NextToggle, Toggle);
input [1:0] Toggle;
output [1:0] NextToggle;
reg [1:0] NextToggle;

always @ (Toggle)
case (Toggle)
2'b01 : NextToggle = 2'b10;
2'b10 : NextToggle = 2'b01;
endcase

endmodule

```

 


```

module NextStateLogicFullCase (NextToggle, Toggle);
  input [1:0] Toggle;
  output [1:0] NextToggle;
  reg [1:0] NextToggle;

  always @ (Toggle)
    case (Toggle)                                // synthesis full_case
      2'b01 : NextToggle = 2'b10;
      2'b10 : NextToggle = 2'b01;
    endcase
endmodule

```

 

```

module PriorityLogic (NextToggle, Toggle);
  input [2:0] Toggle;
  output [2:0] NextToggle;
  reg [2:0] NextToggle;


  always @ (Toggle)
    case (Toggle)
      3'bxx1 : NextToggle = 3'b010;
      3'bx1x : NextToggle = 3'b110;
      3'blxx : NextToggle = 3'b001;
      default : NextToggle = 3'b000;
    endcase
endmodule

```

```

if (Toggle[0] == 'b1)
  NextToggle = 3'b010;
else if (Toggle[1] == 'b1)
  NextToggle = 3'b110;
else if (Toggle[2] == 'b1)
  NextToggle = 3'b001;
else
  NextToggle = 3'b000;

```

 

```

module ParallelCase (NextToggle, Toggle);
  input [2:0] Toggle;
  output [2:0] NextToggle;
  reg [2:0] NextToggle;

  always @ (Toggle)
    case (Toggle) // synthesis parallel_case
      3'bxx1 : NextToggle = 3'b010;
      3'bx1x : NextToggle = 3'b110;
      3'b1xx : NextToggle = 3'b001;
      default : NextToggle = 3'b000;
    endcase
endmodule

```

```


if (Toggle[0] == 'b1)
  NextToggle = 3'b010;

if (Toggle[1] == 'b1)
  NextToggle = 3'b110;

if (Toggle[2] == 'b1)
  NextToggle = 3'b001;

if ((Toggle[0] != 'b1) &&
    (Toggle[1] != 'b1) &&
    (Toggle[2] != 'b1))
  NextToggle = 3'b000;

```

 


```

output [3:0] Line;
reg [3:0] Line;

integer J;

always @ (Address)
  for (J = 3; J >= 0; J = J - 1)
    if (Address == J)
      Line[J] = 1;
    else
      Line[J] = 0;
endmodule

```

 


When the for-loop is expanded, the following four if statements are obtained.

```

if (Address == 3) Line[3] = 1; else Line[3] = 0;
if (Address == 2) Line[2] = 1; else Line[2] = 0;
if (Address == 1) Line[1] = 1; else Line[1] = 0;
if (Address == 0) Line[0] = 1; else Line[0] = 0;

```

 

Constraining combinational outputs that drive combinational inputs