

Special Problem

A CPU uses two control lines (R/\overline{W} and \overline{STRB}) to communicate with a memory chip. Unfortunately, the memory chip has separate read/write lines (\overline{RD} and \overline{WR}).

Design a circuit that will convert the CPU control signals into signals compatible with the memory chip.