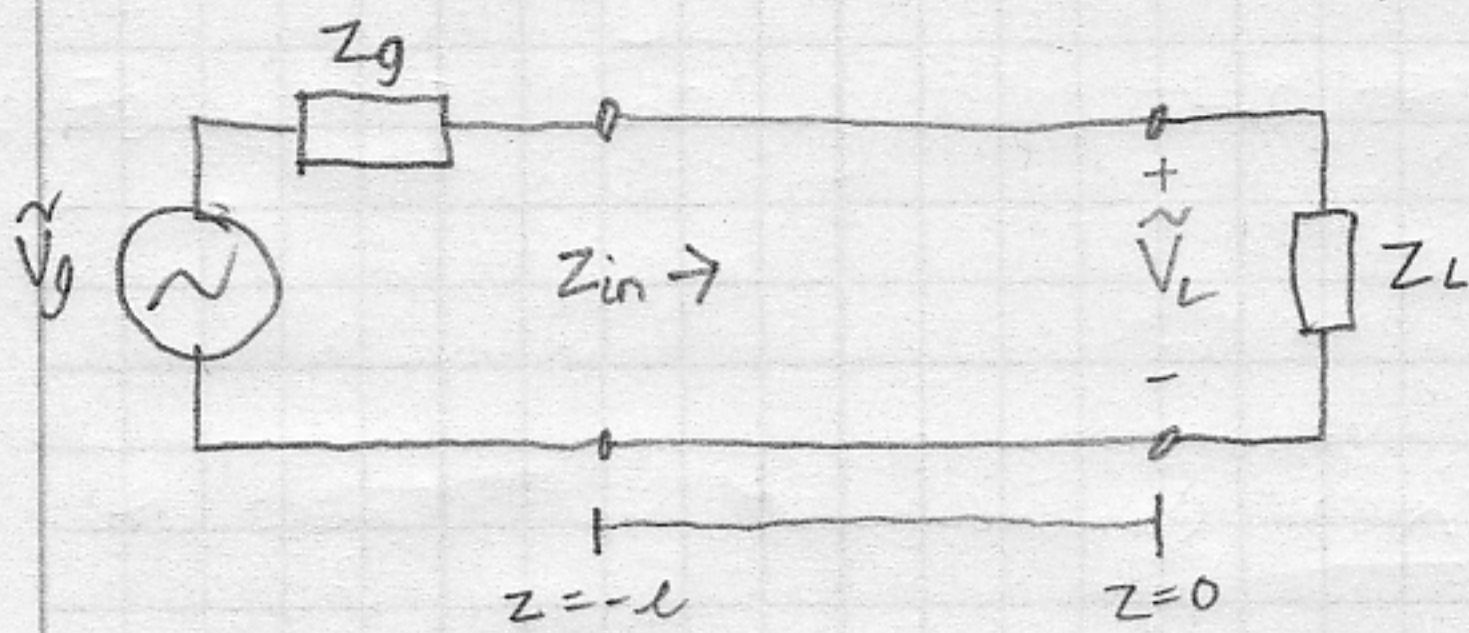


Tx-line Input Impedance



$$Z_{in}(-l) = \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} Z_0$$

Impedance at point $z = -l$ on the transmission line.

← waby equation (2.63)

Example

A lossless 50Ω air spaced tx-line 5 m in length is terminated by a load impedance $Z_L = 100 + j50 \Omega$. If the operating frequency of the generating source is 300 MHz what is the input impedance?

Air-spaced lossless line $\therefore \epsilon_r = 1$ and $v_p = c$

$$\lambda = c \cdot f = 3 \times 10^8 / 100 \times 10^6 = 1 \text{ m}$$

$$\beta = 2\pi / \lambda = 2\pi / 1 = 2\pi \text{ rad/m}$$

$$Z_{in}(-5) = \frac{(100 + j50) + j50 \tan((2\pi)(5))}{50 + j(100 + j50) \tan((2\pi)(5))} \cdot 50$$

$$= \frac{(100 + j50) + j50(0)}{50 + j(100 + j50)(0)} \cdot 50$$

$$= \underline{100 + j50 \Omega}$$

Notice that because β is a multiple of π that it doesn't matter what length the tx-line is this equation will always simplify to Z_L .