

ECE414/514
Electronics Packaging
Spring 2012 Lecture 5
Electrical C: Transmission lines
(Transmission line reflections)

James E. Morris
Dept of Electrical & Computer
Engineering
Portland State University

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

1

Lecture topics

- Reflection concepts
- Reflection coefficients
- Basic cases:
 - Matched and open circuit
- Generalized mismatches
 - Source and load
- Bounce chart/lattice diagram
- Reflections from discontinuities
- EMI and EMC

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

2

Objectives


- Understand origins of reflections
- Determine reflection waveforms by bounce chart
- Calculate effects of discontinuities
- Calculate EM radiation and susceptibility in basic case

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

3

1. Reflection Coefficient

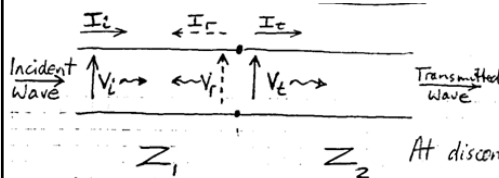

At discontinuity $Z_1 \rightarrow Z_2$
and the relationships of the incident wave $V_i = I_i Z_1$
cannot be maintained in the transmitted wave $V_t = I_t Z_2$
without changes in V, I . Solution requires
reflected wave $V_r = I_r Z_1$

Boundary conditions $V_i + V_r = V_t$
 $I_i - I_r = I_t$

Gives $V_r = \frac{Z_2 - Z_1}{Z_2 + Z_1} V_i = \Gamma_V V_i$
(Voltage) Reflection Coefficient
& $I_r = \Gamma_I I_i = -\Gamma_V I_i$
(Current) Reflection Coefficient


Voltage transmission coefficient $V_t/V_i = 1 + \Gamma_V$

Voltage reflection at load $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow 0$ for $Z_L = Z_0 = R_0$

4/15/2012



" " " source $\Gamma_S = \frac{R_S - Z_0}{R_S + Z_0} \rightarrow 0$ for $R_S = Z_0$



4

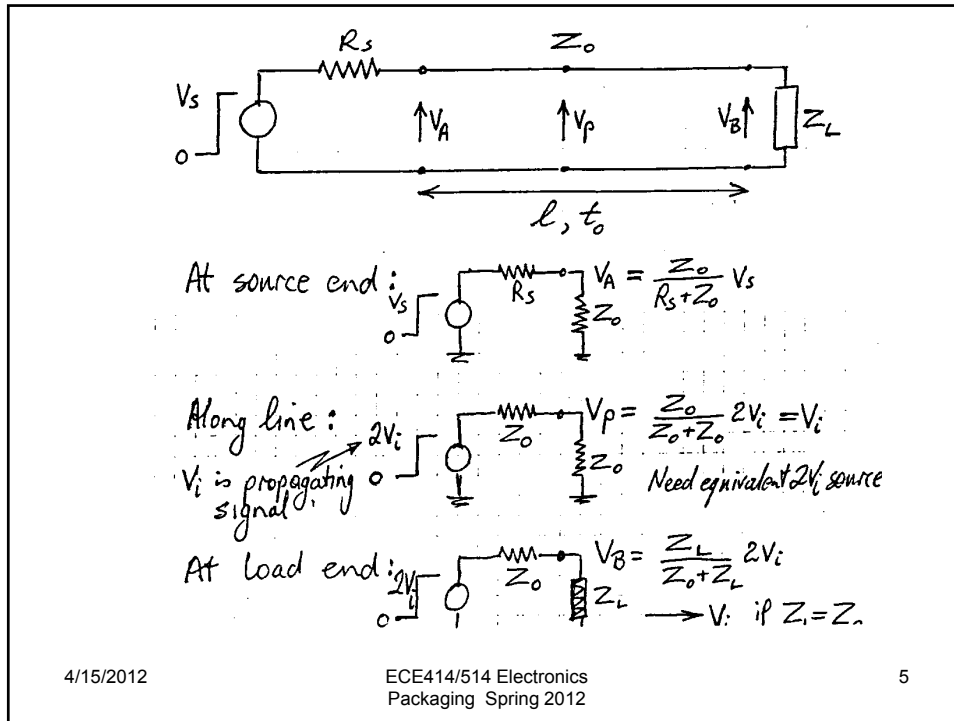

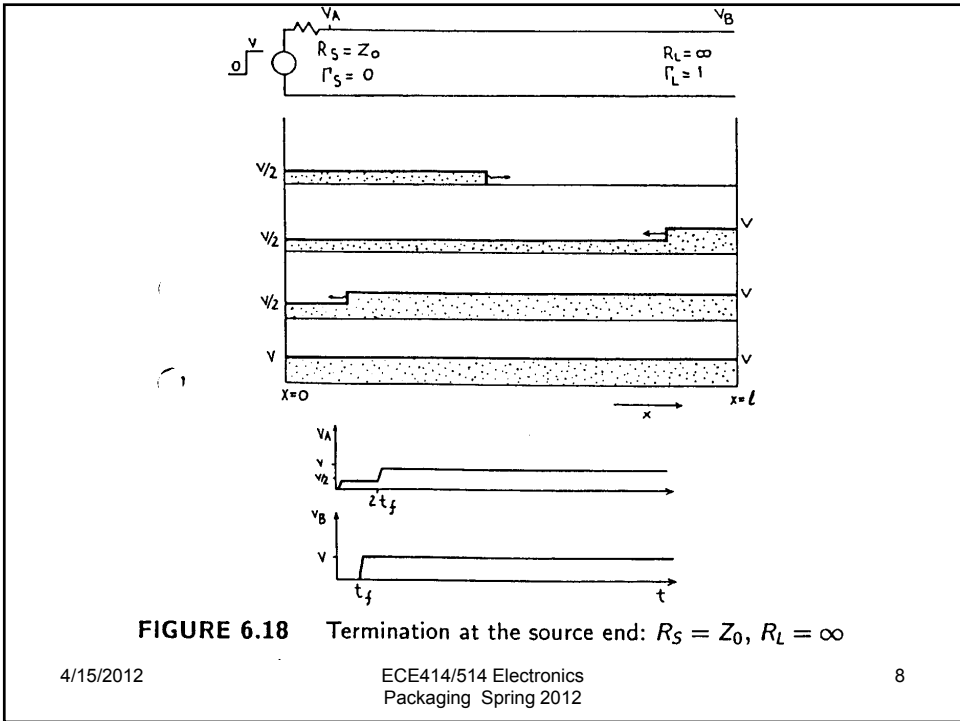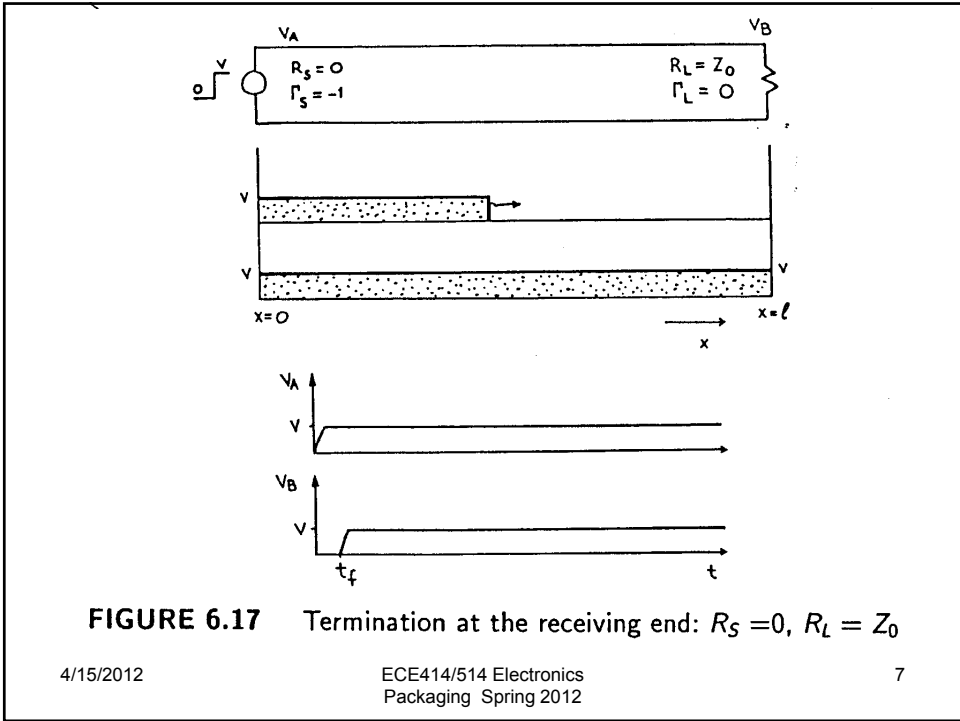2. Basic examples

- 3 significant cases: $\Gamma_{VL} = (R_L - Z_0) / (R_L + Z_0)$
 - Matched load $R_L = Z_0 \rightarrow \Gamma_{VL} = 0$
 - Open circuit load $R_L = \infty \rightarrow \Gamma_{VL} = +1$
 - Short circuit load $R_L = 0 \rightarrow \Gamma_{VL} = -1$
- Similarly at the source end:
 - $\Gamma_{VS} = (R_S - Z_0) / (R_S + Z_0)$ $R_S = Z_0 \rightarrow \Gamma_{VS} = 0$
 - $R_S = \infty \rightarrow \Gamma_{VS} = +1$ $R_S = 0 \rightarrow \Gamma_{VS} = -1$



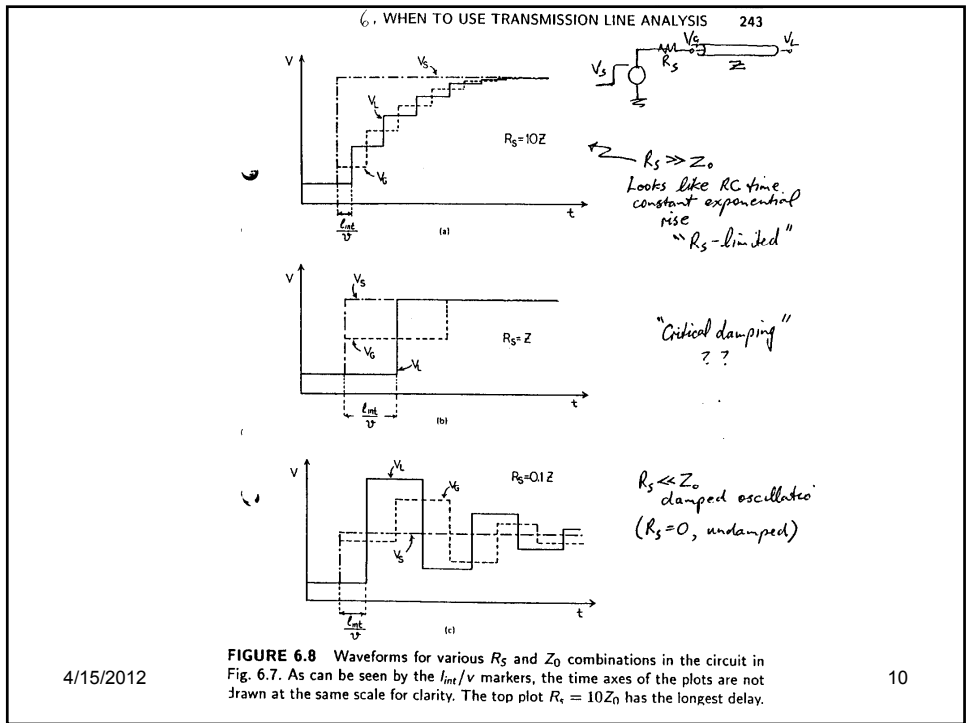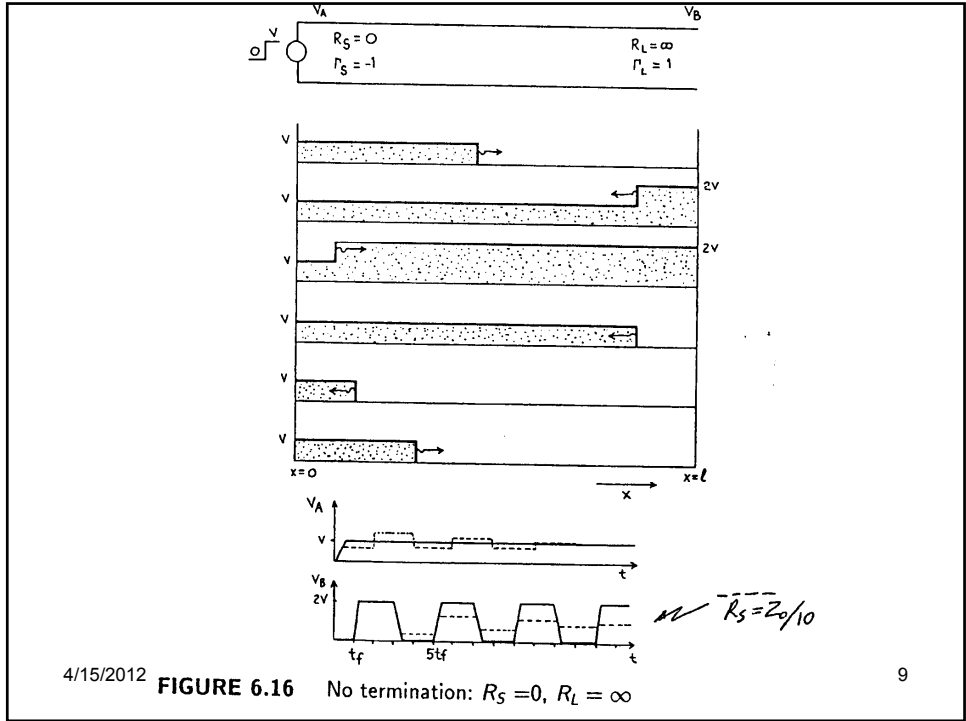


3. Mismatched load &/or source



- 1 volt pulse, $Z_0 = 78\Omega$
 - Consider $R_L = 78\Omega$ cases first, then vary R_L
- (a) $R_S = Z_0$
- (b) $R_S \ll Z_0$
- (c) $R_S \gg Z_0$

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

11

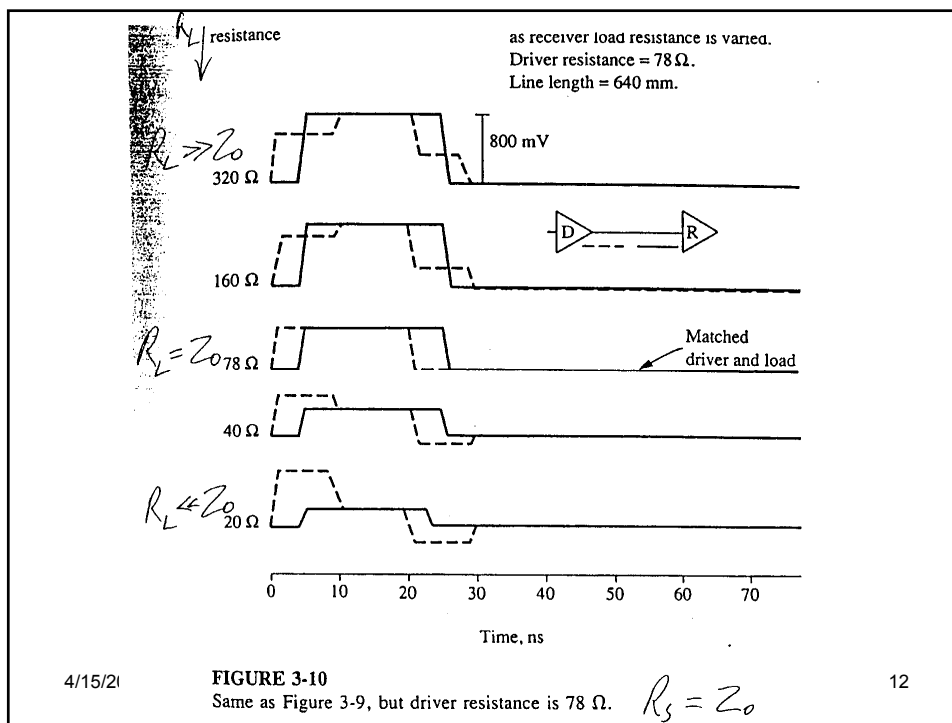

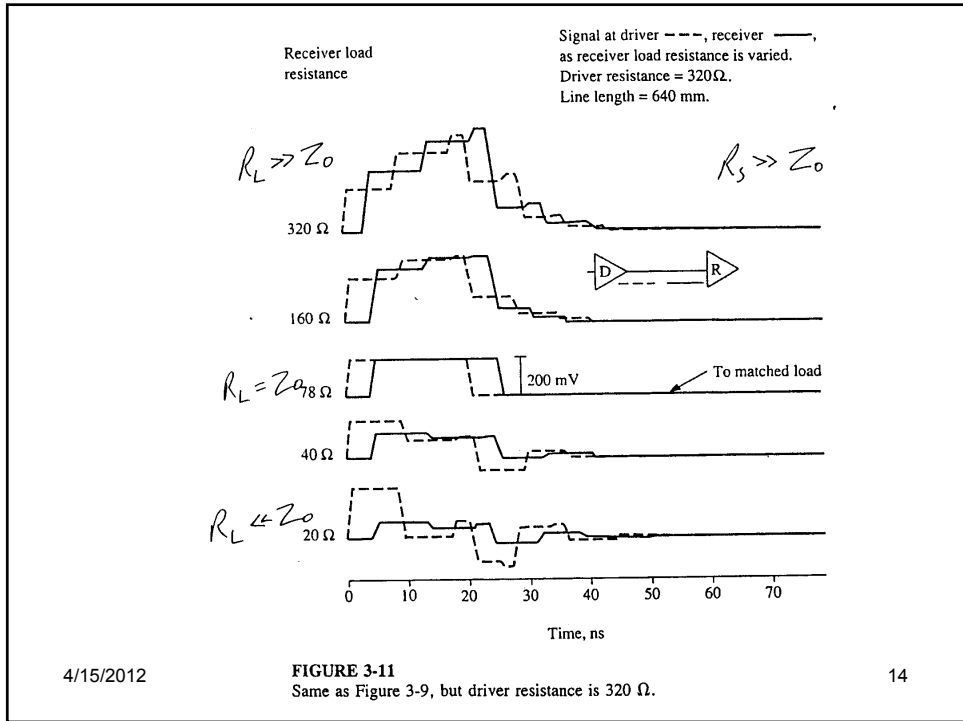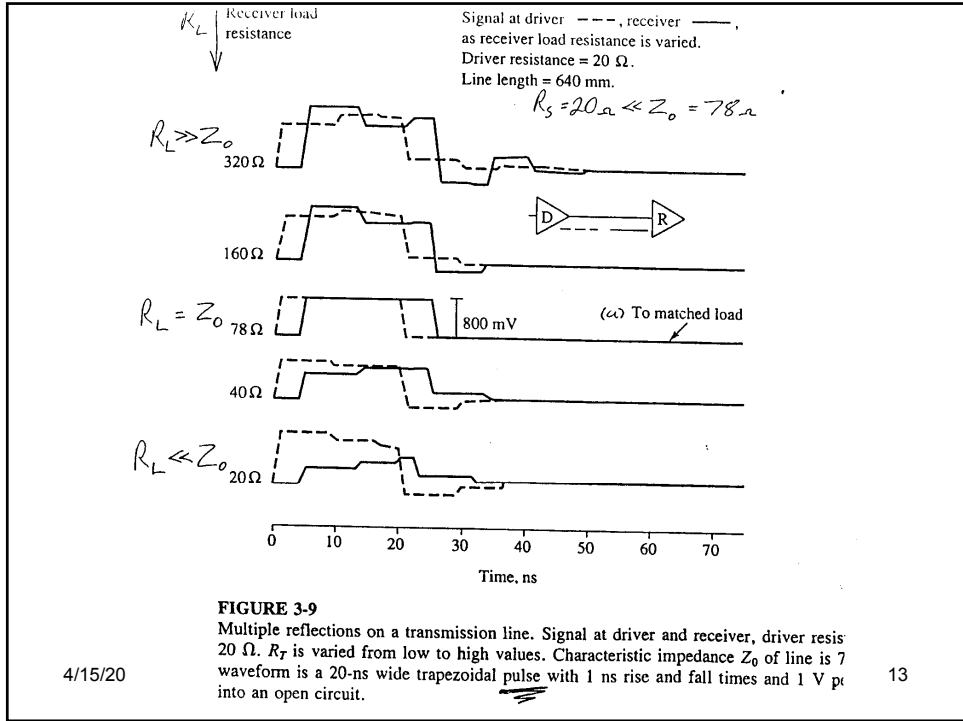

4. Bounce chart/lattice diagram


- Calculate reflection coefficients
- Distance / time diagram
- Transfer data to waveform plots
- Examples:
 - (1) Open circuit line
 - (2) Two segment line

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

15

(1)

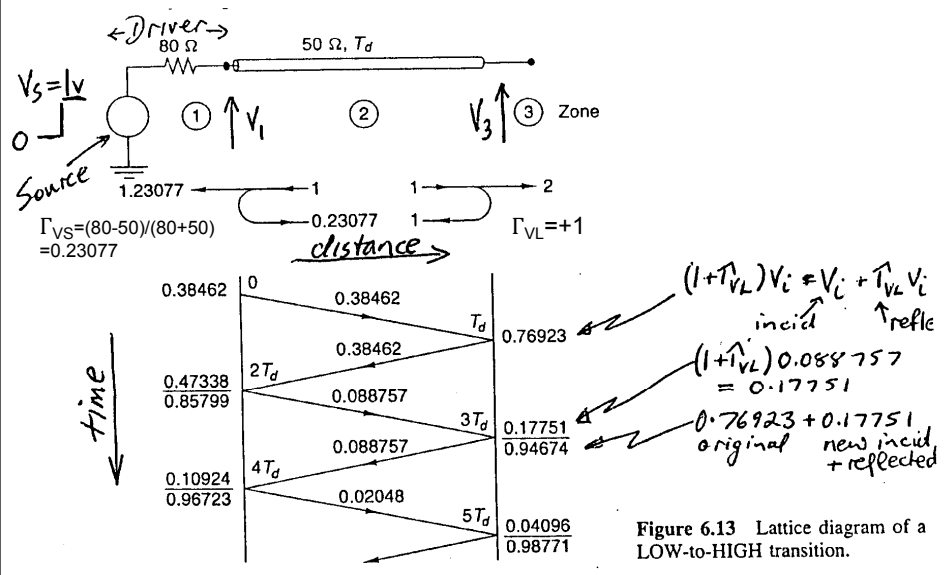

"BOUNCE" CHART / LATTICE DIAGRAM

(1) $R_s = 80 \Omega$ $Z_0 = 50 \Omega$ $R_L = \infty$

$\therefore \Gamma_{Vs} = \frac{80-50}{80+50} = \frac{3}{13}$ $\uparrow_{VL} = \frac{\infty-50}{\infty+50} = 1$
 $= 0.23077$

At $t=0$: $V_1 = \frac{50}{50+80} V_s = \frac{5}{13} V = 0.38462V$

$t=T_d$: Load $V_i = 0.38462V$ $V_r = \Gamma_{VL} V_i = 0.38462V$

& load voltage $V_3 = V_i + V_r = 0.76924V$

$t=2T_d$: Driver Reflected wave $V_r = \Gamma_{Vs} \cdot 0.38462V = 0.088757V$



$V_3 = 0.38462V + \underbrace{0.38462V}_{\text{original pulse}} + \underbrace{0.088757V}_{\text{reflection from load}} + \underbrace{0.088757V}_{\text{reflection back to load}} = 0.85799V$

$t=3T_d$: Load Reflected wave $= \Gamma_{VL} \cdot 0.85799V = 0.85799V$

$V_3 = 0.76924V + \underbrace{0.85799V}_{\text{previous value}} + \underbrace{0.088757V}_{(1+\Gamma_{VL})V_i = 0.17751V} + \underbrace{0.088757V}_{\text{Incid. reflection + next refl. back}} = 0.94674V$


$t=4T_d$: Driver Reflected wave $= \Gamma_{Vs} \cdot 0.85799V = 0.2048V$

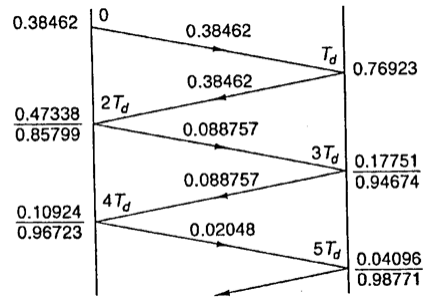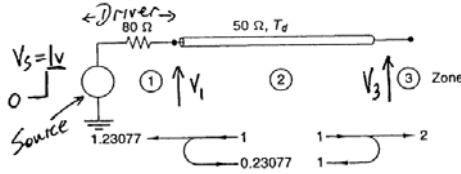$V_1 = 0.85799V + (0.088757V + 0.2048V) = 0.96723V$



ajnic
2012

17

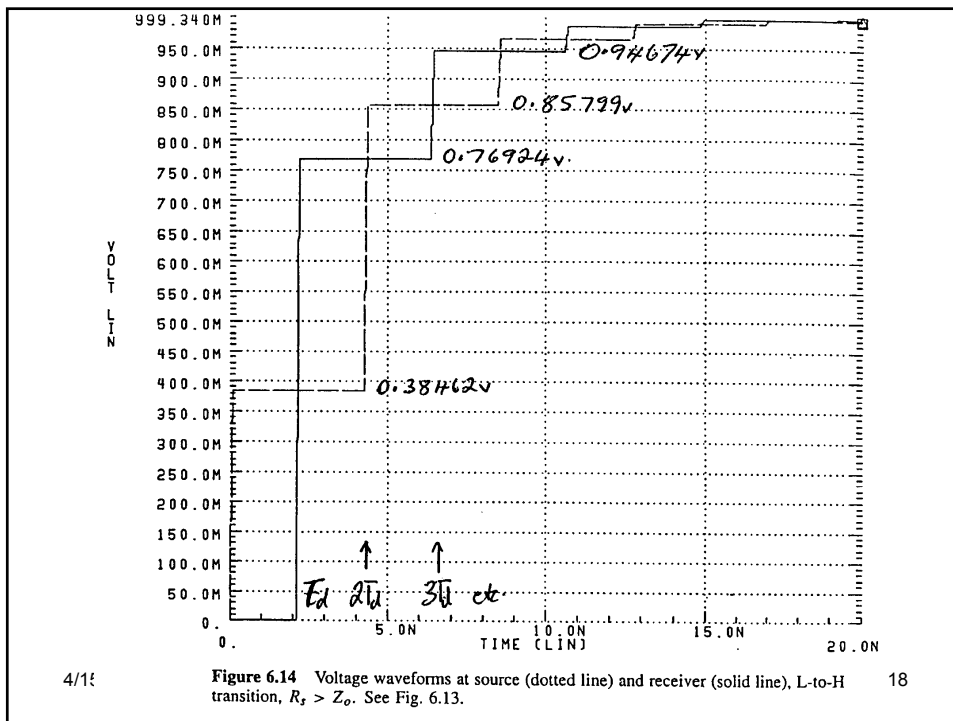


4/18

Figure 6.14 Voltage waveforms at source (dotted line) and receiver (solid line), L-to-H transition, $R_s > Z_0$. See Fig. 6.13.

18

(2)


(2) Two-segment line

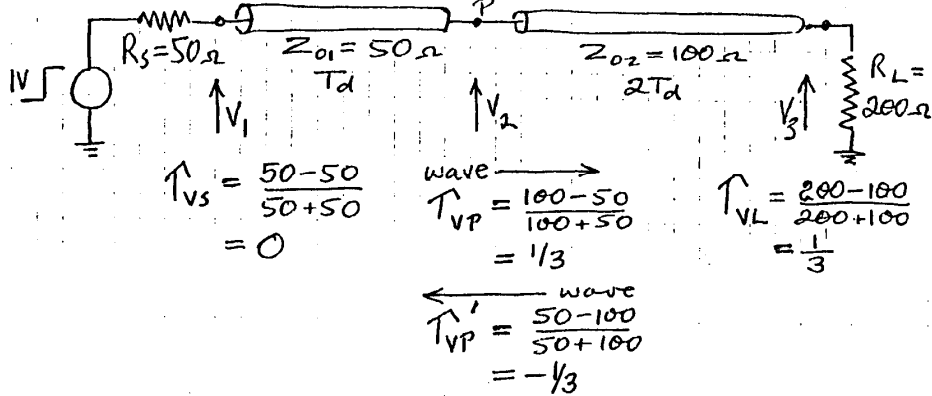


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

19

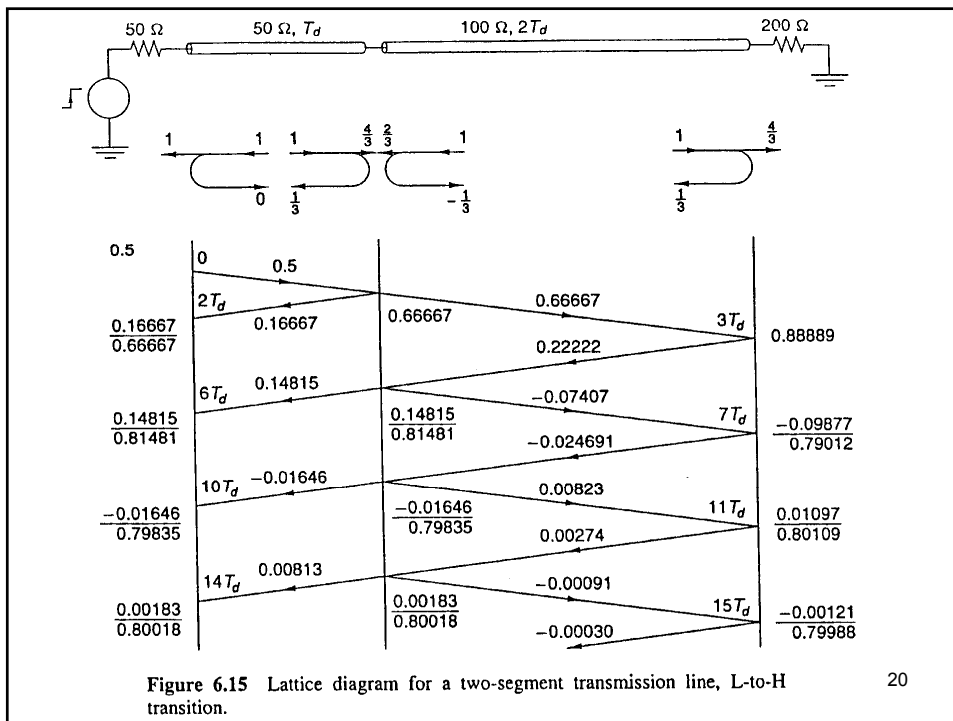

20

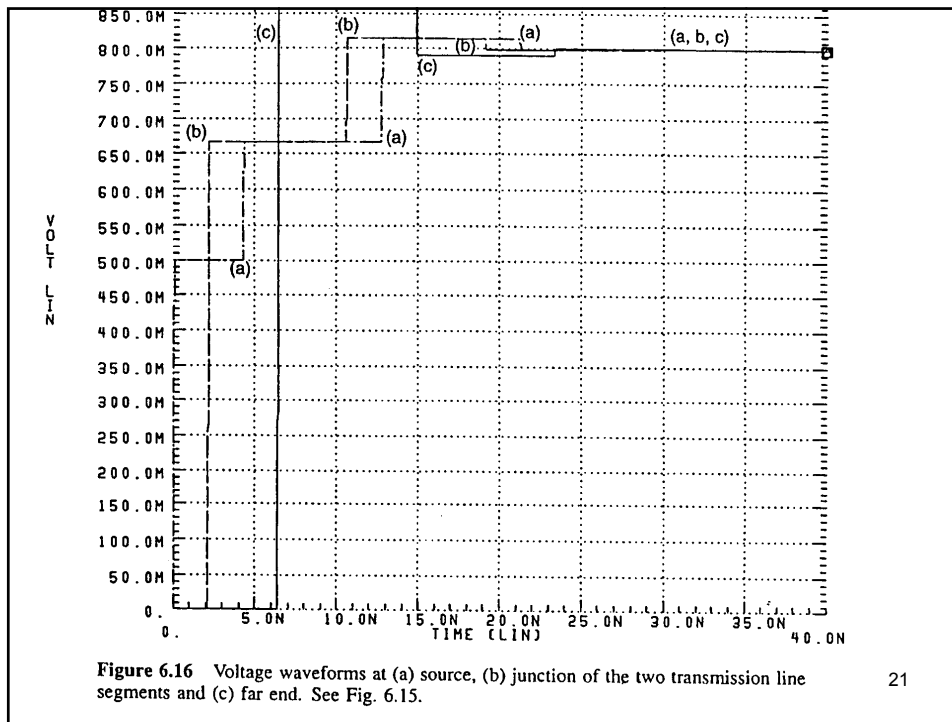

21



5. Discontinuities



- Capacitive loads (MOSFETs)
- Stubs
- Multiple loads
- Line geometry changes
 - bends
 - vias
- Non-linear loads



4/15/2012



ECE414/514 Electronics
Packaging Spring 2012



22

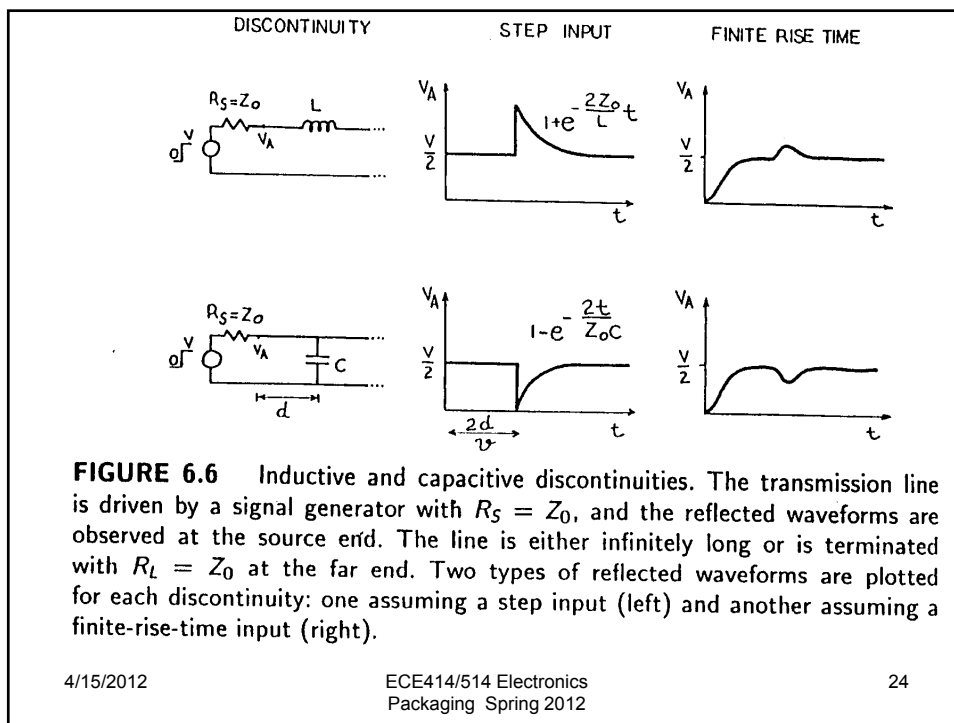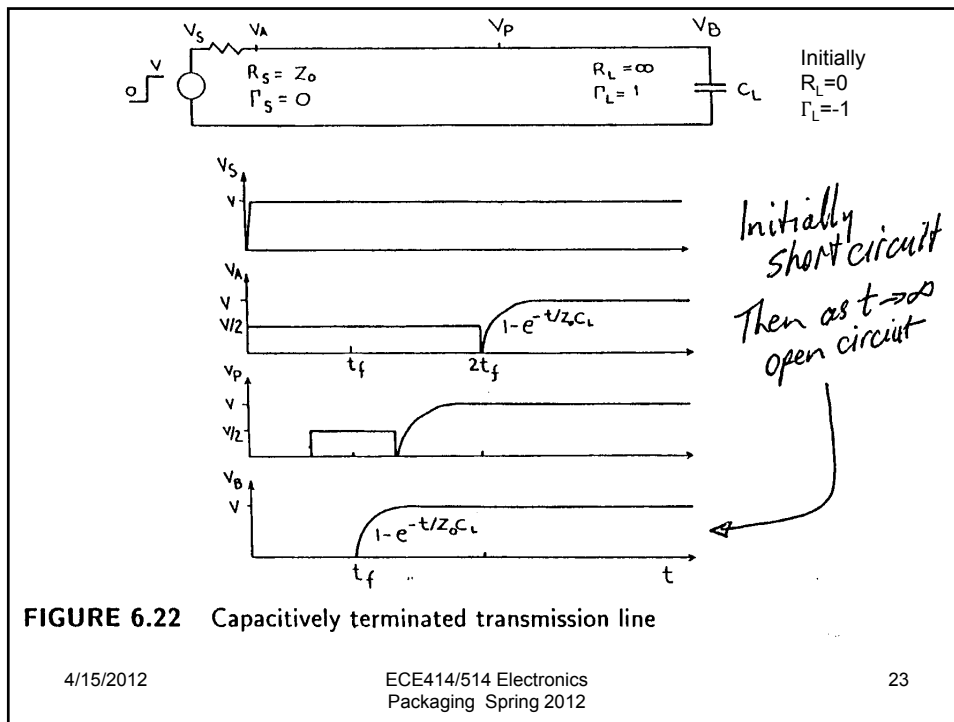

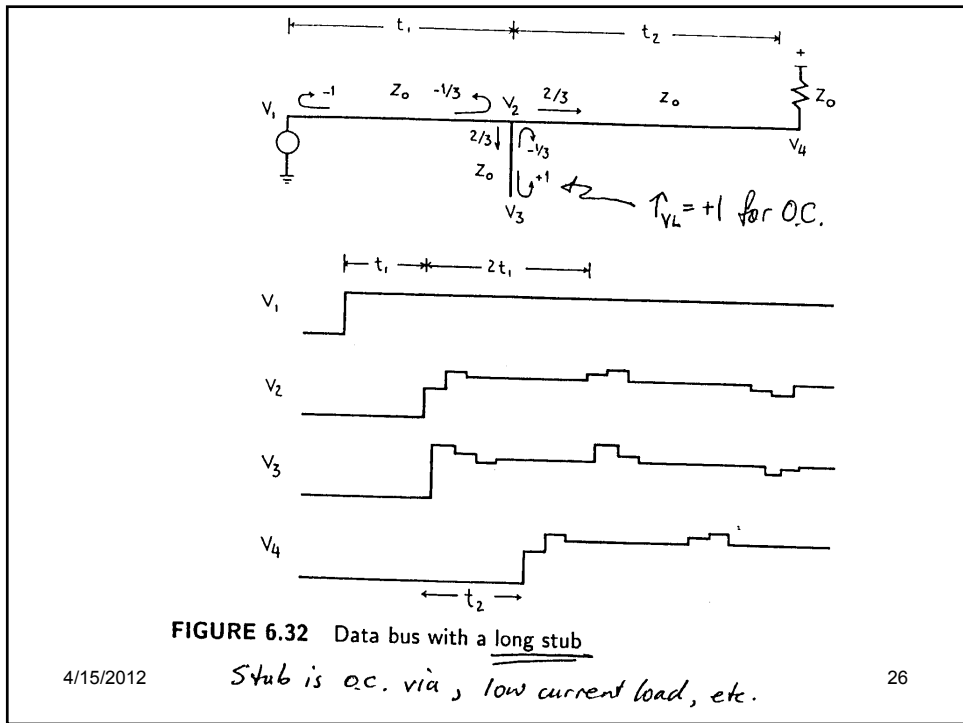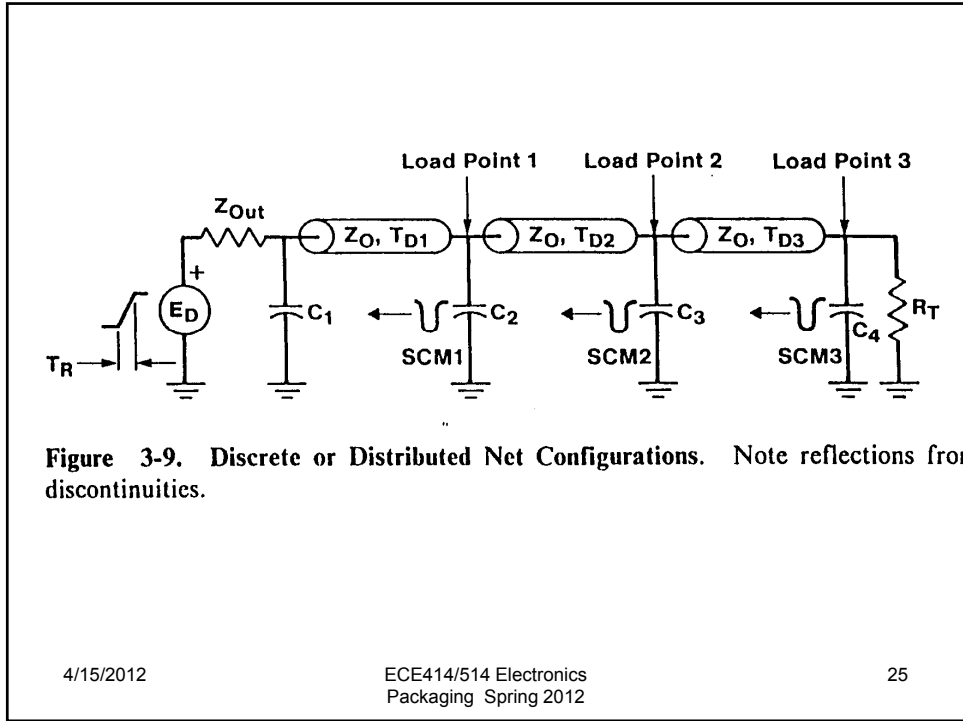

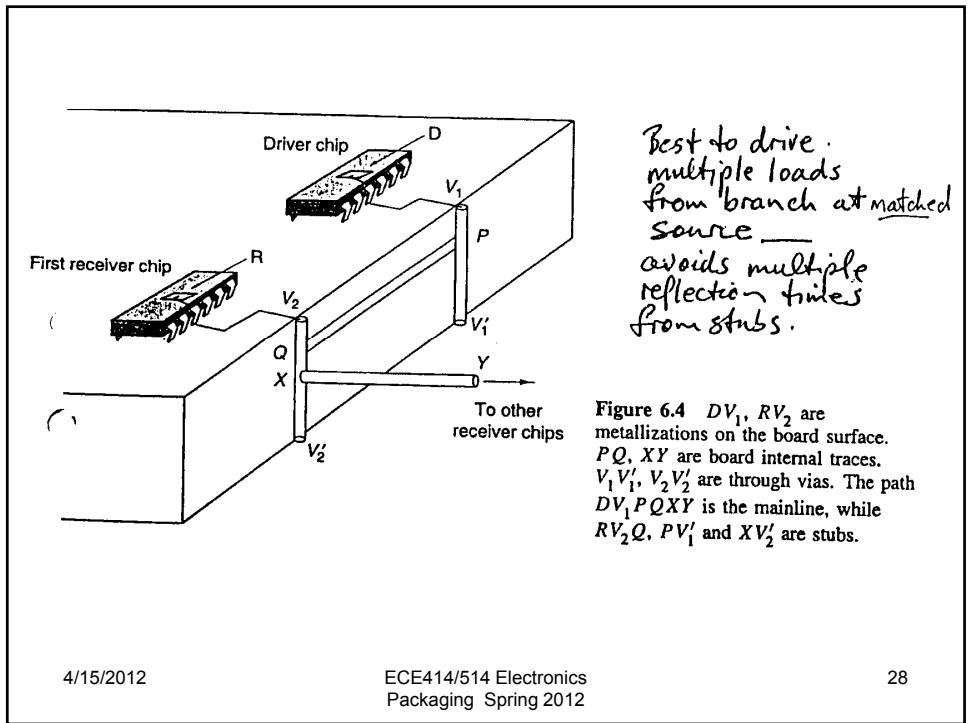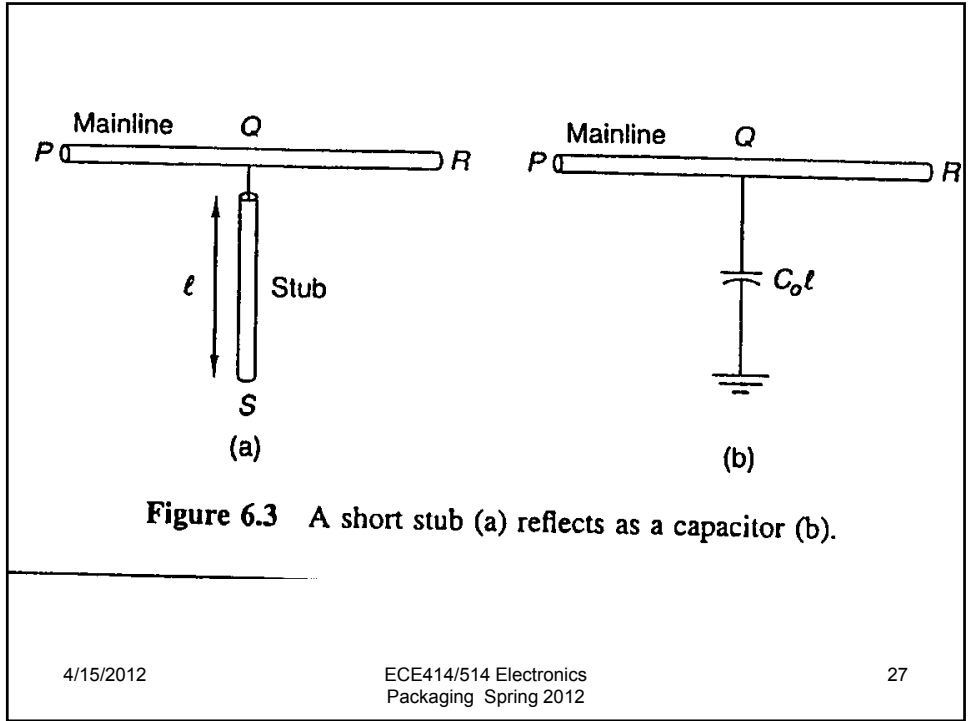

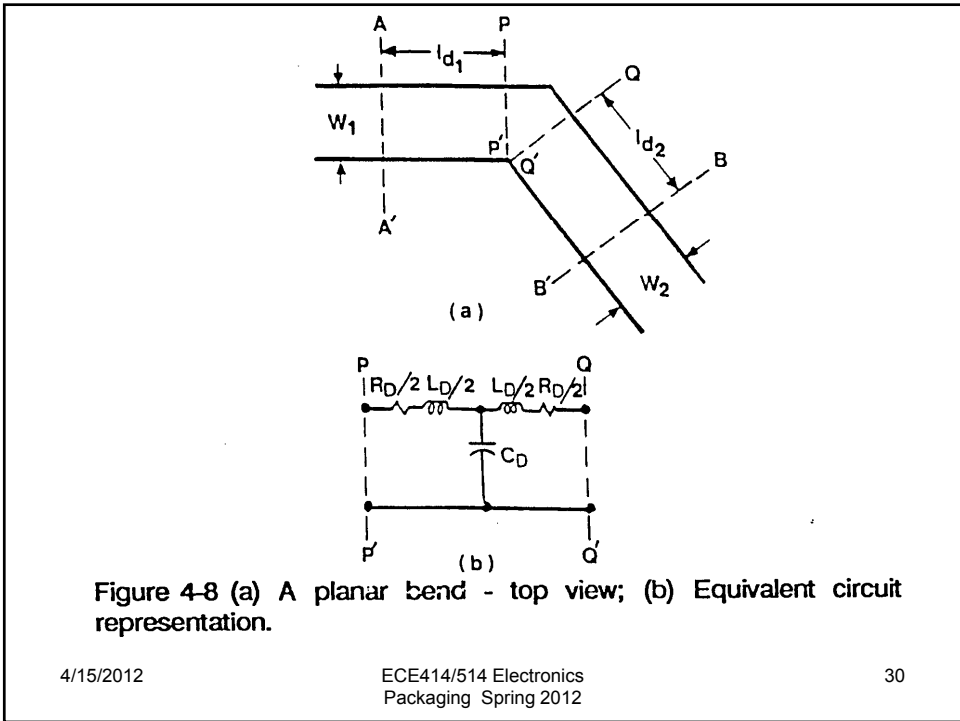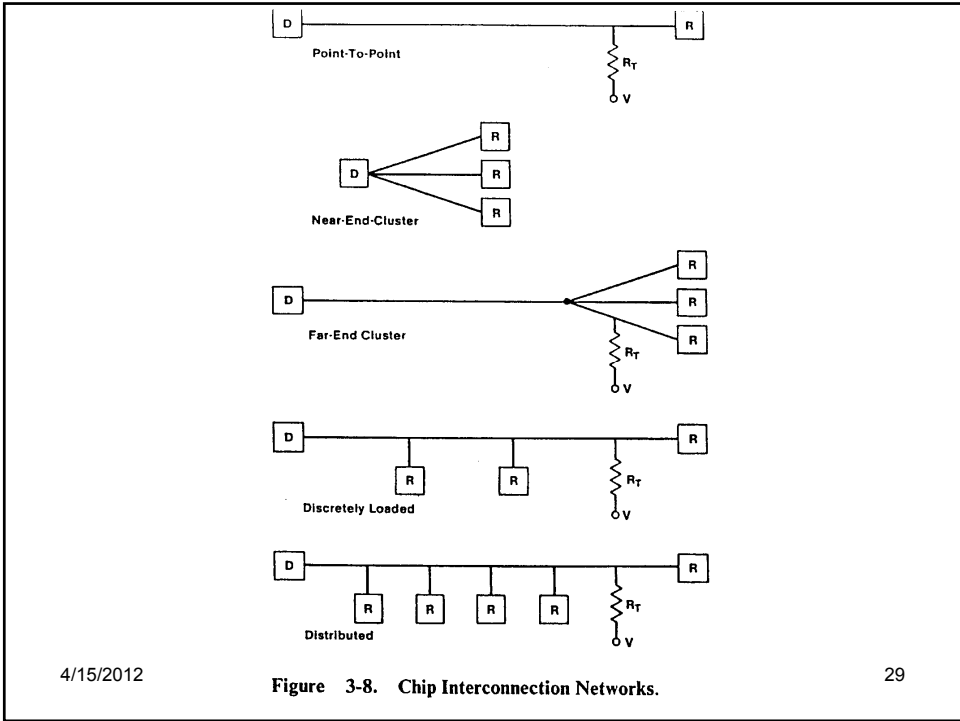

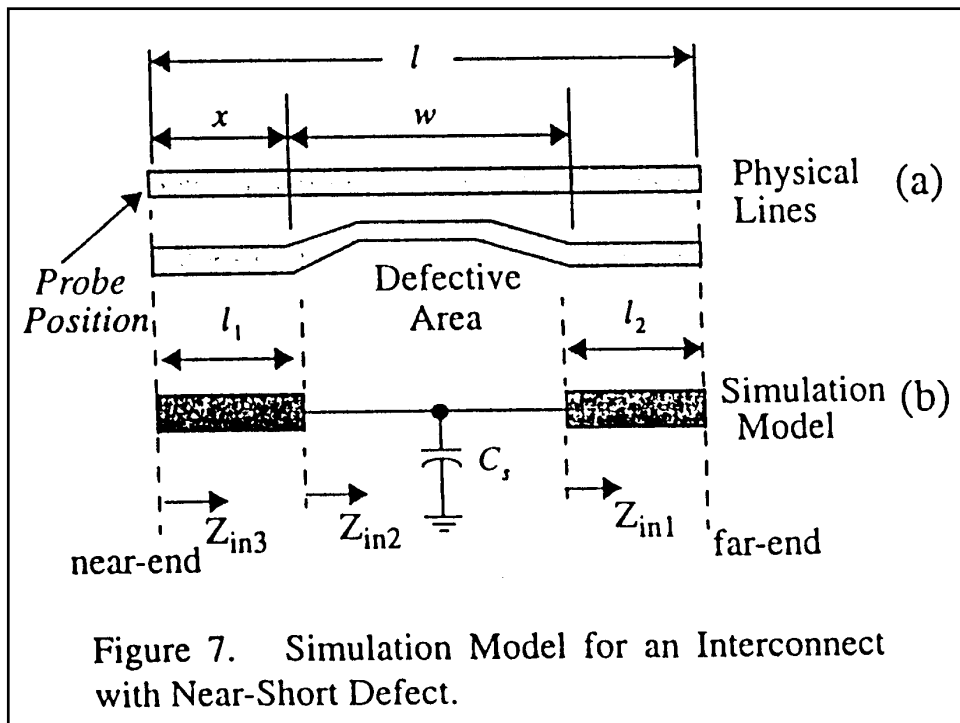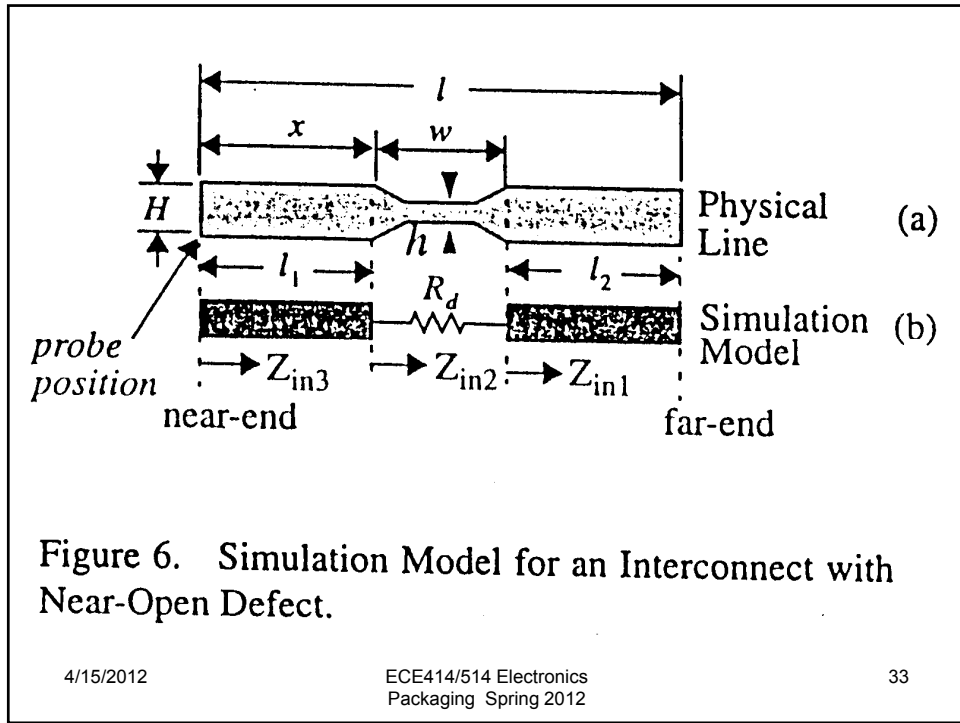


Summary

Waveform	Transmission line effect	Description/environment	Section
(1)	Propagation delay T_d Risetime degradation ($T_{r,r} > T_{r,s}$)	Line is distributed if $2T_d \geq T_r$	9.1.4
(2)	Ohmic drop (frequency-independent)	Steady-state attenuation	5.2
(3)	Skin effect (frequency dependent)	Slow dribble-up at transition	10.4
(4)	Reflection from lumped loads: (a) capacitor (b) inductor	Glitch accompanies every transition	6.2.2
(5)	Undershoot on (a) short line (b) long line	Parallel-terminated line: (at receiver): $R_t < Z_0$	6.4
(6)	Overshoot on (a) short line (b) long line	Parallel-terminated line (at receiver): $R_t > Z_0$ Series-terminated line (at source): $R_s > Z_0$	6.4
(7)	Spurious noises: • crosstalk • switching • oscillations • others	Non-deterministic association with every transition	Chap. 7, 8

4/15/2012

35


EMI/EMC Models: Loop/Dipole Antennas

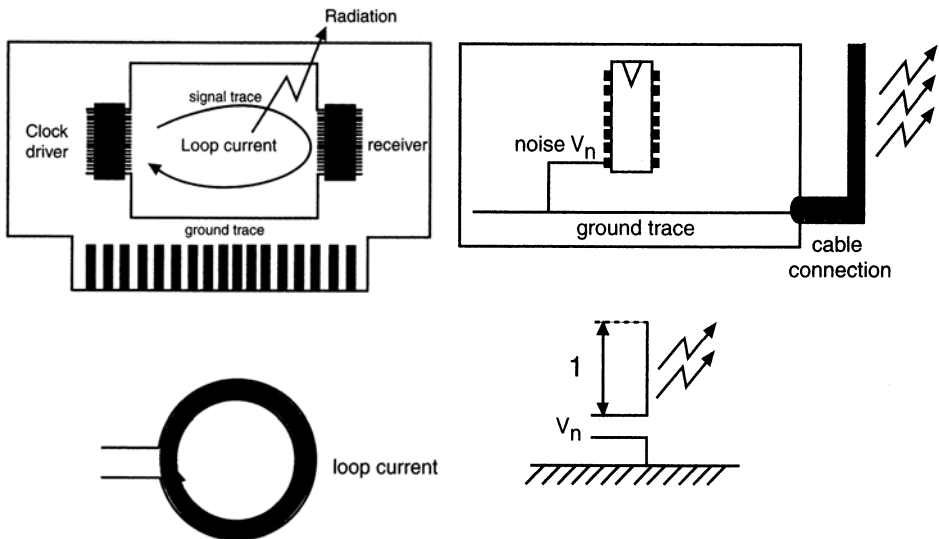

4/15/2012

ECE414/514 Electronics Packaging Spring 2012


36

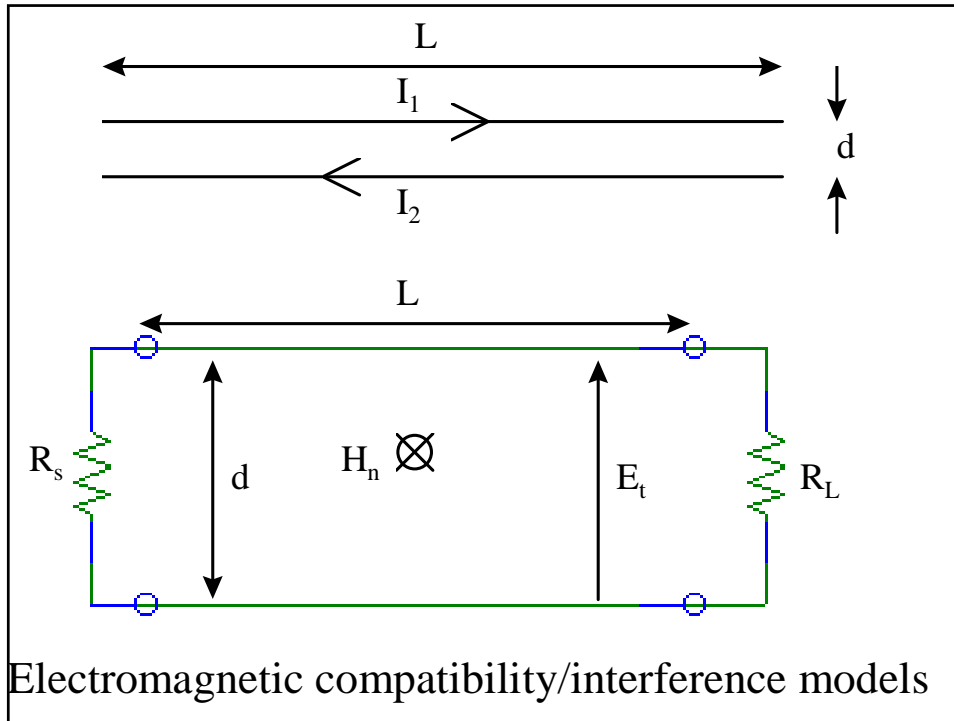

EMI/EMC Models: Emissions

- At “far field” distance r ($\geq \lambda = c/f$) from the line of length L and area $A = L \cdot d$, the radiated electric field strength is
 - $E = E_D + E_{CM}$
- where E_D due to the differential current I_D is
 - $E_D = 131.6 \times 10^{-16} f^2 A I_D / r \quad \text{V/m}$
- and E_{CM} due to the common mode current I_{CM} is (for $L \leq \lambda$)
 - $E_{CM} = 4\pi \times 10^{-7} f^2 L I_{CM} / r \quad \text{V/m}$
- where $I_D = (I_1 + I_2)/2$ and $I_{CM} = (I_1 - I_2)/2$. Common mode currents are ideally zero, but small values can lead to CM dominance over differential. For the differential current, the maximum value can be taken to be the supply current, but the user must specify a non-ideal common mode estimate. For digital systems, use $f = 2\pi/t_r$. For other geometries, other expressions for A are valid.
- There are many different standards for EM radiation limits, but for guidance the EU limit is $E \leq 100 \mu\text{V/m}$ at $r = 10\text{m}$ (class A) or 3m (class B).

EMI/EMC Models: Susceptibility

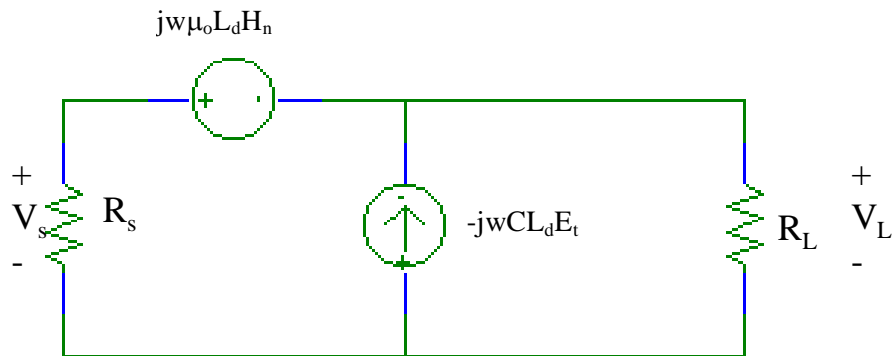

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

39

Susceptibility

- For the line shown, with capacitance C per unit length, e.g.
 - $C = \pi \epsilon_r \epsilon_0 / \ln(d/r_w)$
- for parallel wires, the induced voltages are
 - $V_s = -j\omega [R_L R_S / (R_L + R_S)] [Ld] [C - (\mu_0/\eta_0)/R_L]$
 - $V_L = -j\omega [R_L R_S / (R_L + R_S)] [Ld] [C + (\mu_0/\eta_0)/R_S]$
 - where $E = E_t = \eta_0 H_n$, and $\eta_0 = 120\pi = 377\Omega$.
 - As an example of an EU standard, the device must function in a field of $E = 3V/m$.

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

40