

ECE414/514
Electronics Packaging
Spring 2012 Lecture 6
Electrical D: Transmission lines
(Crosstalk)

James E. Morris
Dept of Electrical & Computer
Engineering
Portland State University

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

1

Lecture topics

- Inductive and capacitive coupling
- Forward and backward noise
- Far end and near end noise
- Incremental model and formulae
- Capacitive crosstalk systems
- No ground plane

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

2

Objectives


- Understand the origins of crosstalk
 - Inductive
 - Capacitive
- Calculate basic crosstalk noise levels
- Calculate signal crosstalk and delta-I noise in no ground systems

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

3

Incremental line model

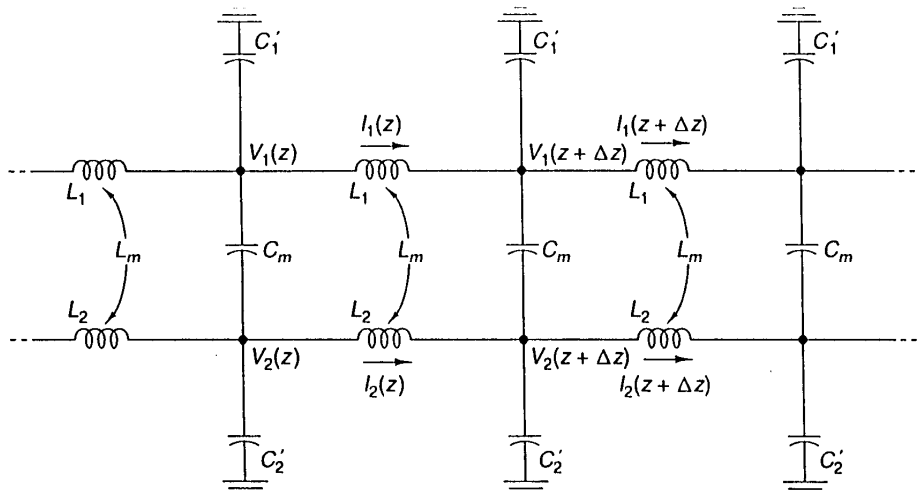


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

4

Crosstalk polarities

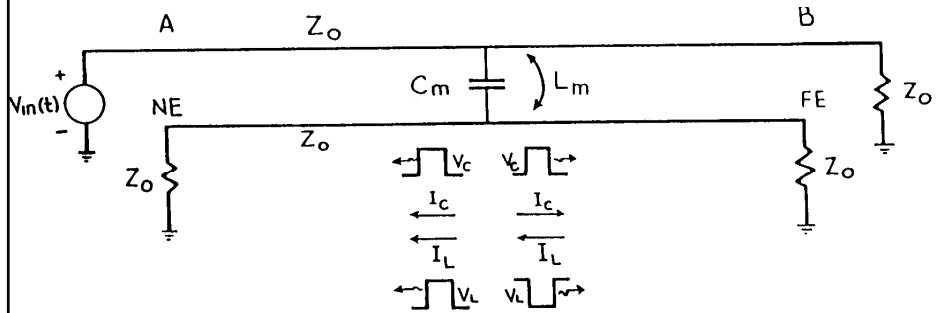


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012


5

Forward and backward noise

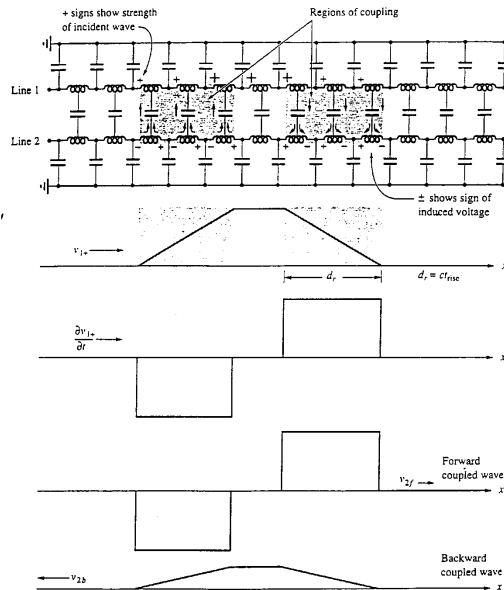


4/15/2012

6

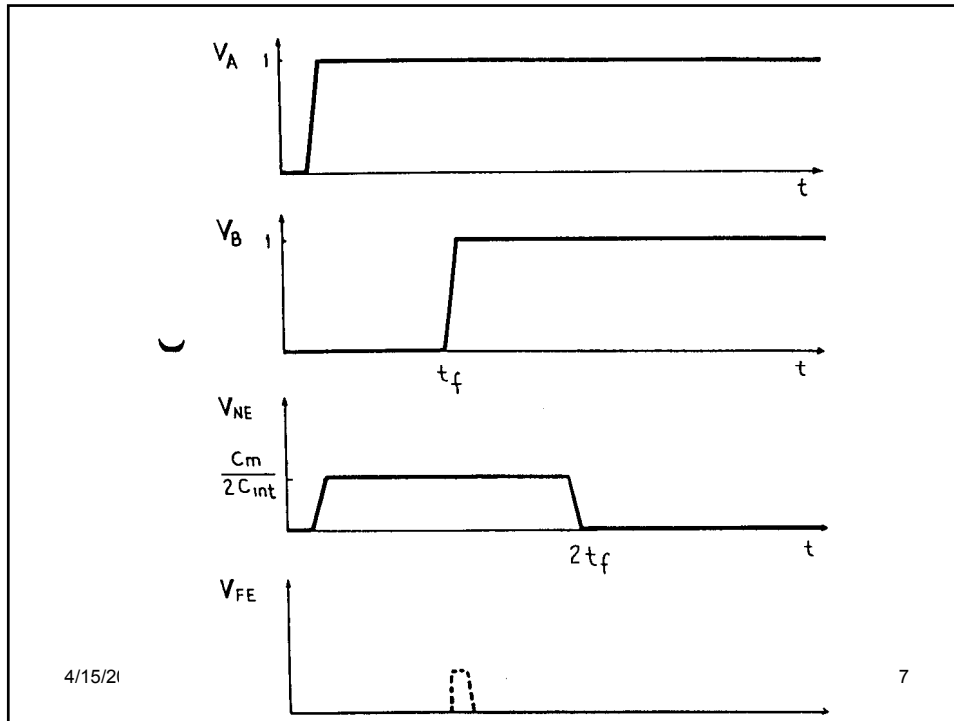

Theory: line segment

Consider line elements of length Δx

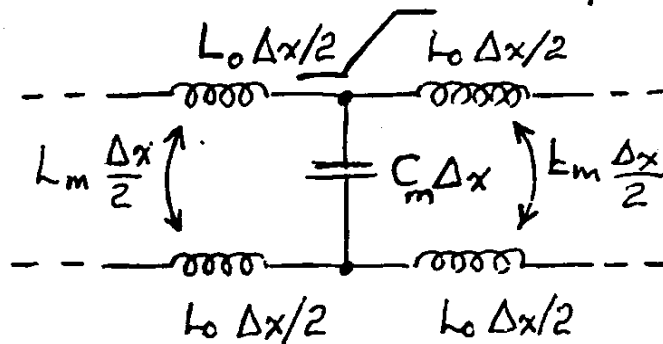


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

8

Capacitive noise

(a) Capacitive

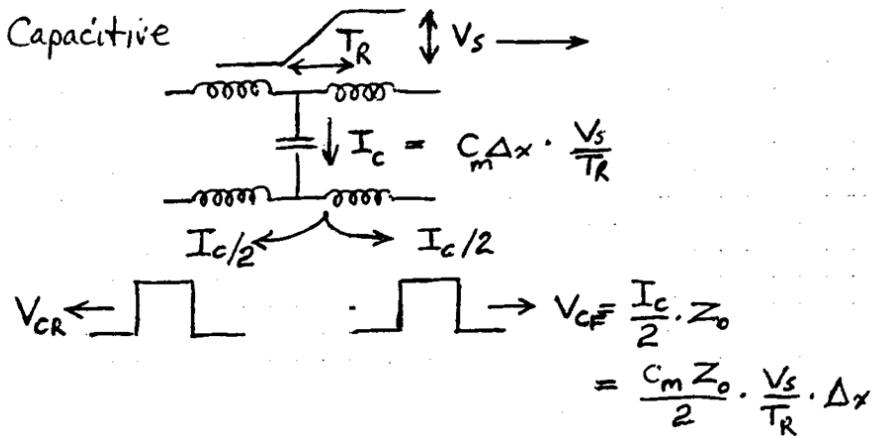


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

9

Inductive noise

(b) Inductive

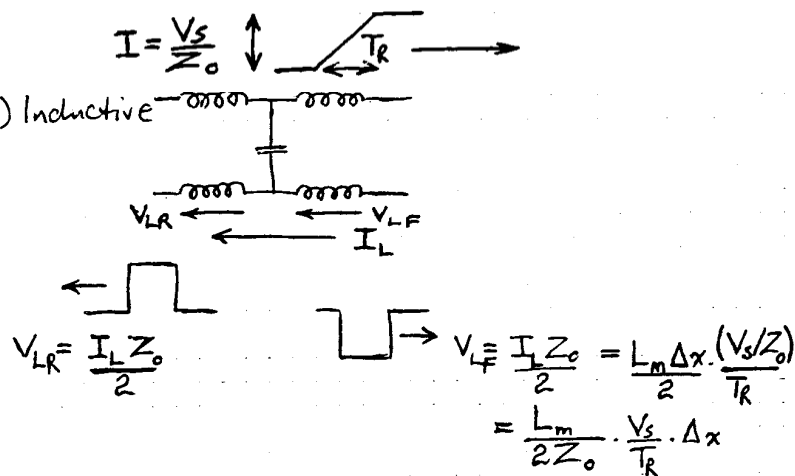


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

10

Incremental model

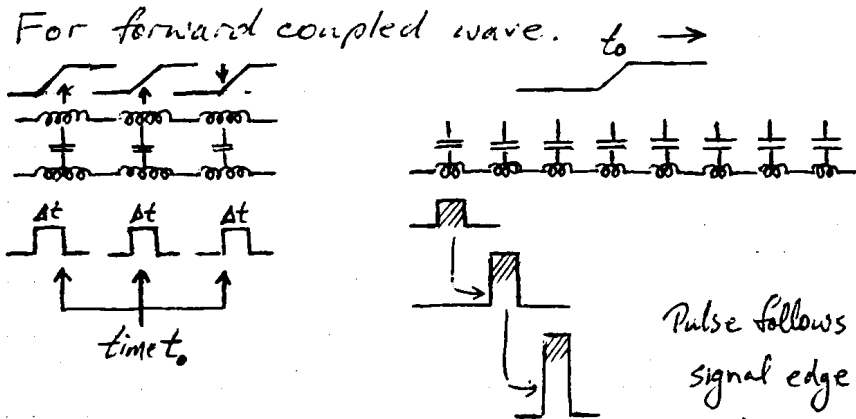


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

11

Far end formula

At far end (FE):

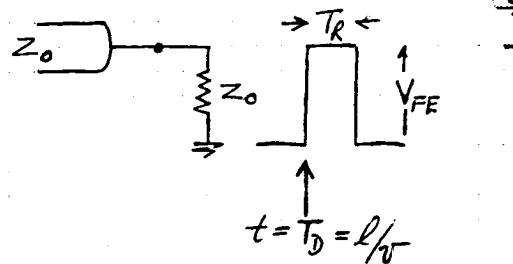

$$V_{FF} = \left(\frac{C_m Z_0}{2} - \frac{L_m}{2Z_0} \right) \frac{V_s}{T_R} \leq \Delta x$$

$$= \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{V_s}{T_R} \ell$$

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

12

Zero far end noise

$$= \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{V_s}{T_R} l$$


$$\rightarrow 0 \quad \text{if} \quad C_m Z_0 = L_m / Z_0$$

$$\text{ie. if} \quad \frac{L_m}{C_m} = Z_0^2 = \frac{L_0}{C_0}$$


This is so if medium is "homogeneous"

Approx true for most MCM "stripline" structures, etc. $\mu = \mu_0$ homogeneous ϵ_r constant.

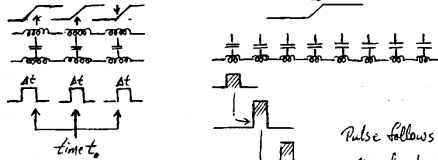For forward coupled wave. $t_0 \rightarrow$



At far end (FE):

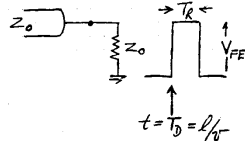


$$V_{FF} = \left(\frac{C_m Z_0}{2} - \frac{L_m}{2 Z_0} \right) \frac{V_s}{T_R} \leq \Delta x$$

$$= \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{V_s}{T_R} l$$

$$\rightarrow 0 \quad \text{if} \quad C_m Z_0 = L_m / Z_0$$

$$\text{ie. if} \quad \frac{L_m}{C_m} = Z_0^2 = \frac{L_0}{C_0}$$

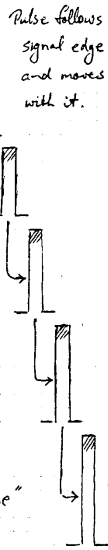
This is so if medium is "homogeneous"
Approx true for most MCM "stripline"
structures, etc. $\mu = \mu_0$ homogeneous ϵ_r constant.



Backward wave model

For reverse coupled wave

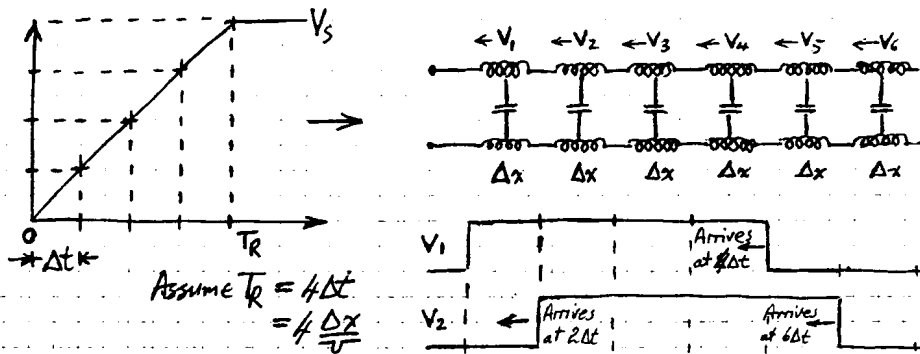Consider the near end (NE) as pulse starts:-




4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

15

Backward wave construct

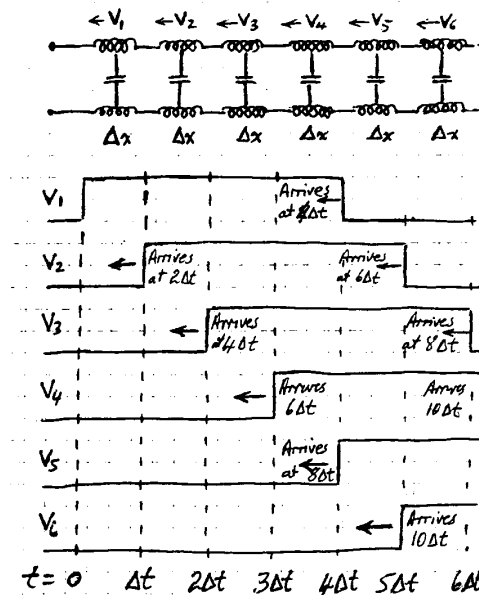


4/15/2012

16

Near end formula

Each pulse
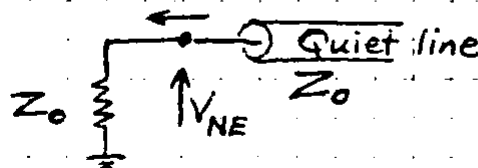
$$\Delta V = \left(\frac{C_m Z_0}{2} + \frac{L_m}{2Z_0} \right) \frac{V_s}{T_R} \Delta x$$




4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

17

Near end noise waveform

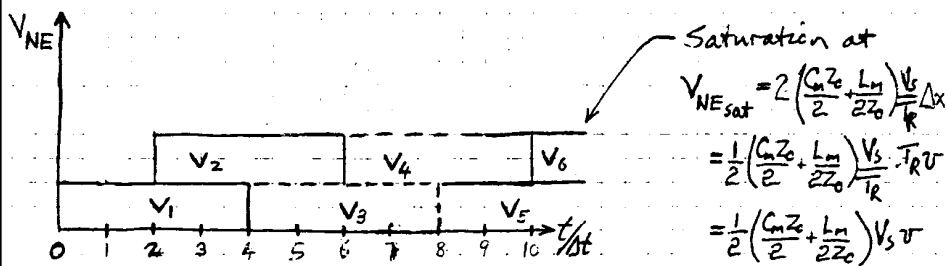

Note: Independent of T_R !!


Also independent of ϵ_r ... $C_m Z_0 \propto \epsilon_r \epsilon_r^{-1/2} \epsilon_r^{-1/2}$
 $v/Z_0 \propto \epsilon_r^{-1/2} (\epsilon_r^{-1/2})^{-1}$

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

18

Near end pulse shape

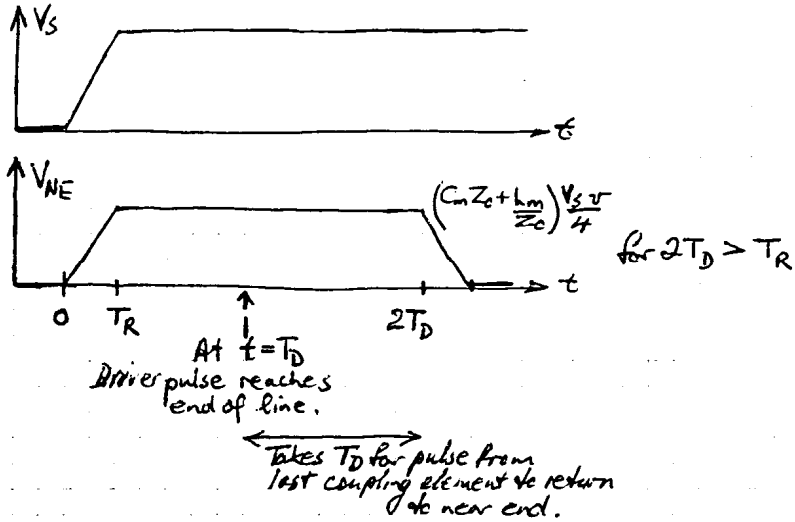


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

19

Near end saturation

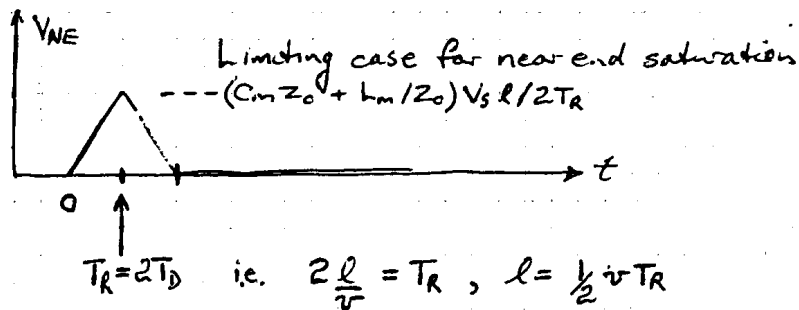


Need to reduce $(V_{NE})_{max}$, need to increase T_R &/or decrease l
(i.e. decrease l/T_R) so cannot saturate.

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

20

Near end saturation

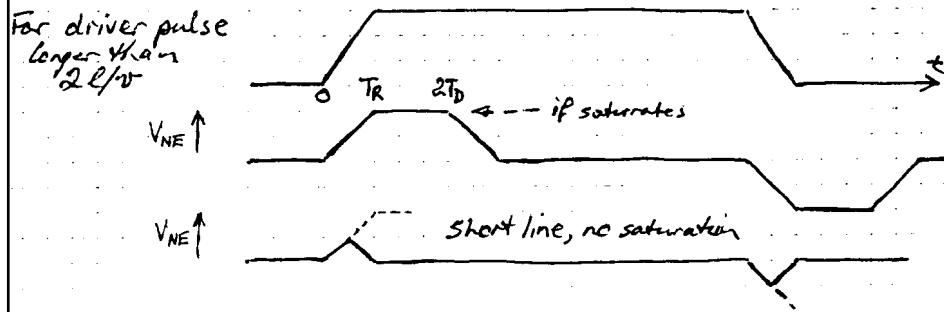

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

21



Pulse crosstalk noise examples



- Driver pulse
 - 0.5 volt amplitude
 - 20 ns pulse width
 - 1ns rise and fall times



4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

22

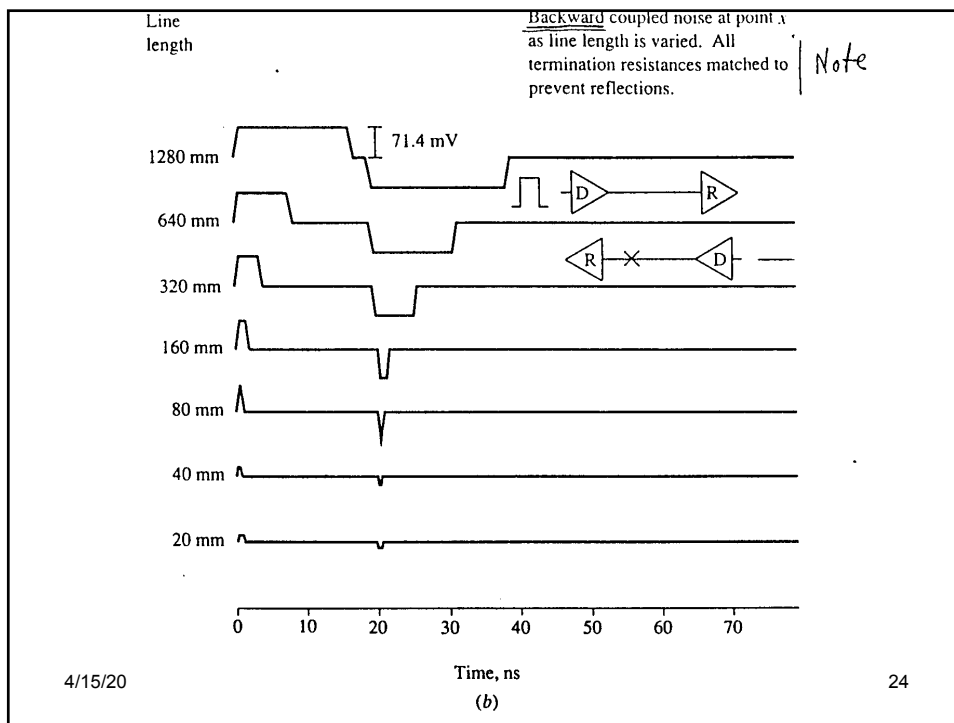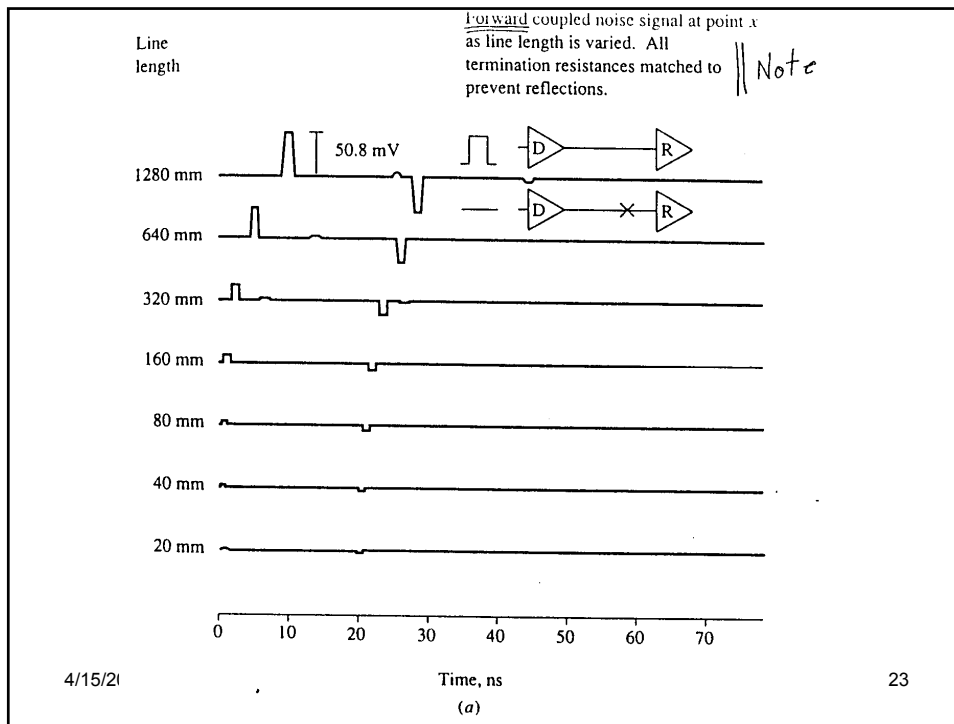

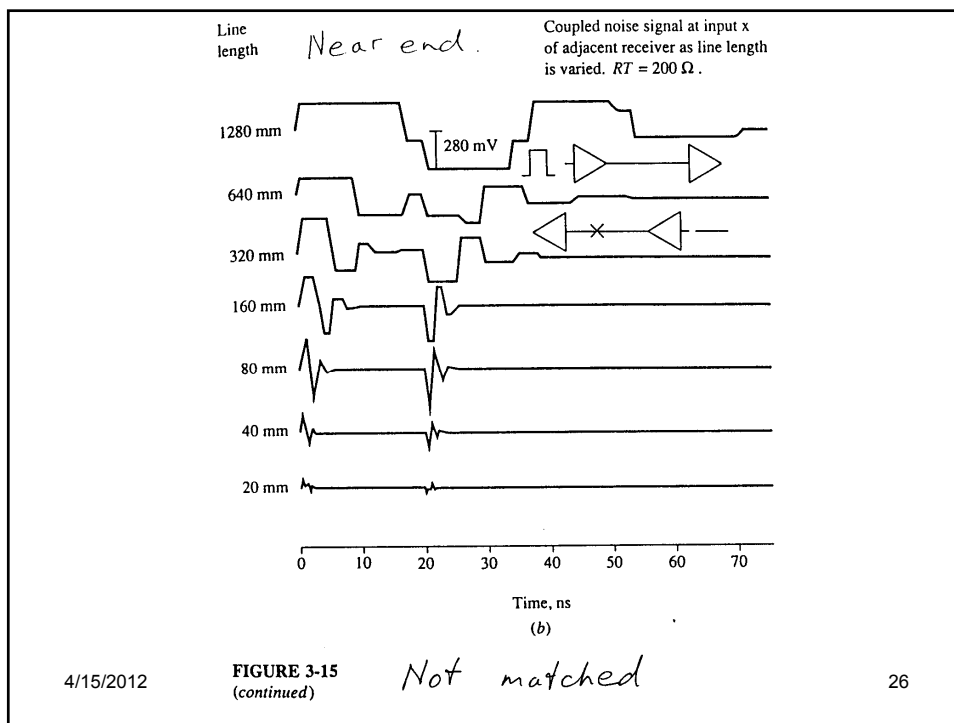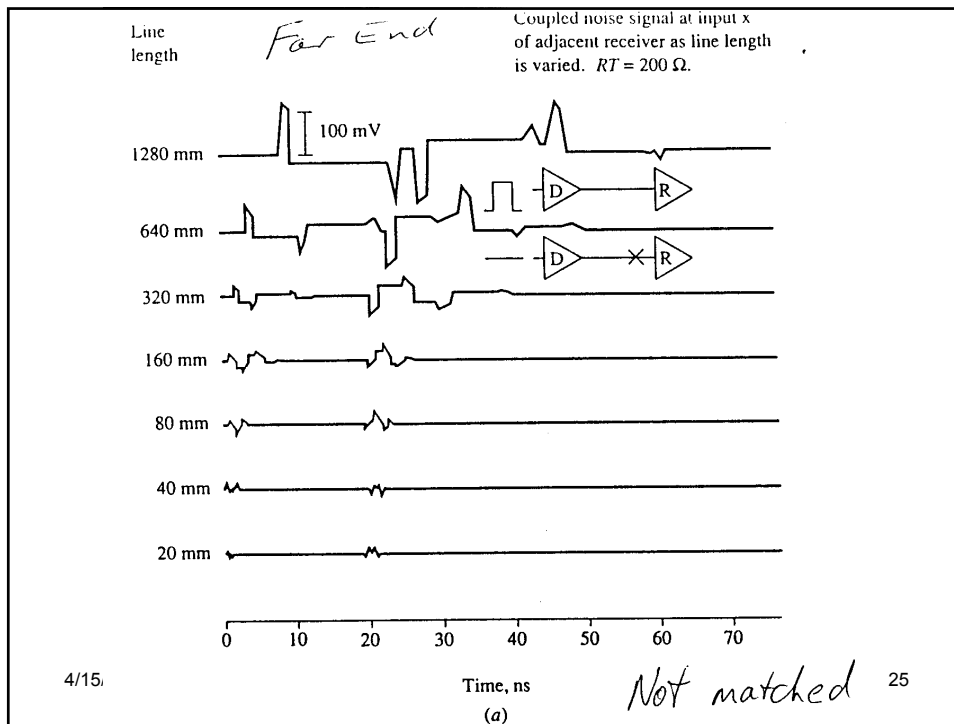

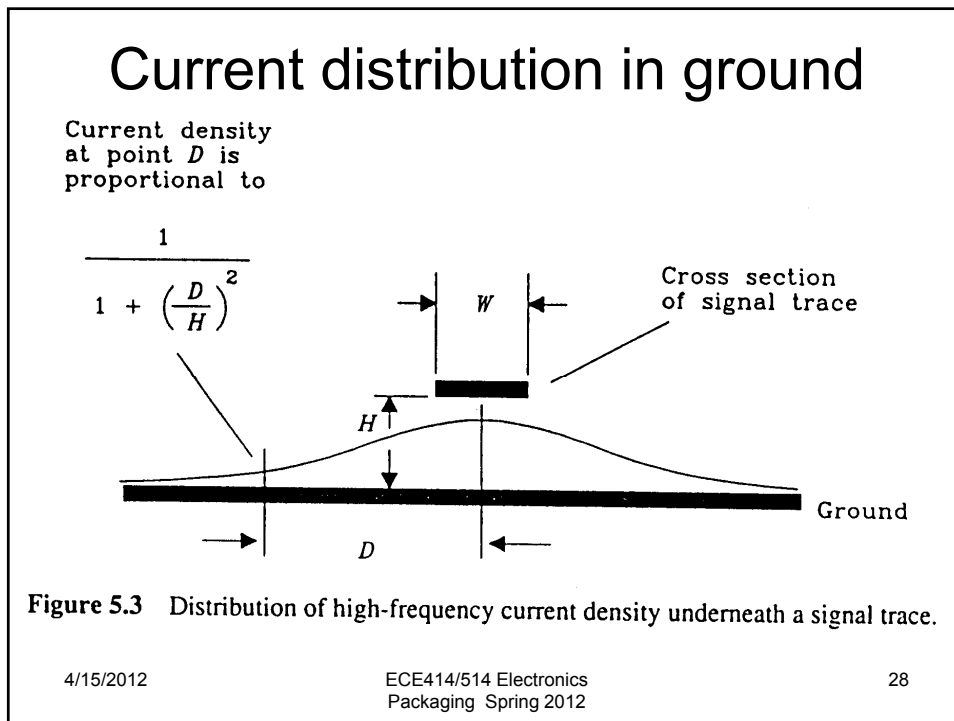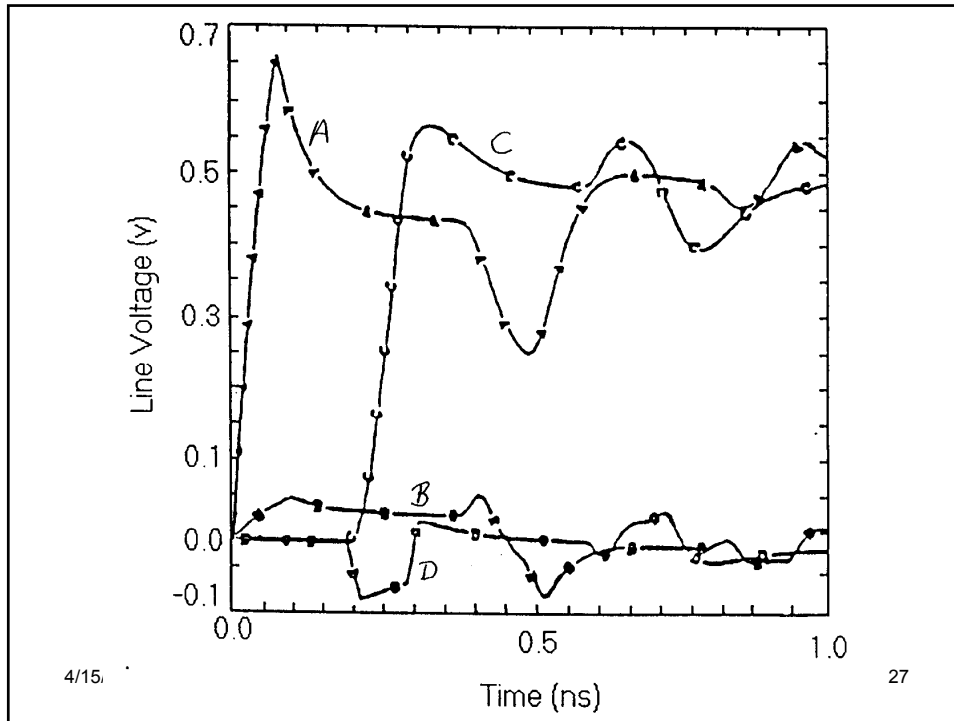

Ground coupled crosstalk

$$\text{Crosstalk} \approx \frac{K}{1 + (D/H)^2}$$

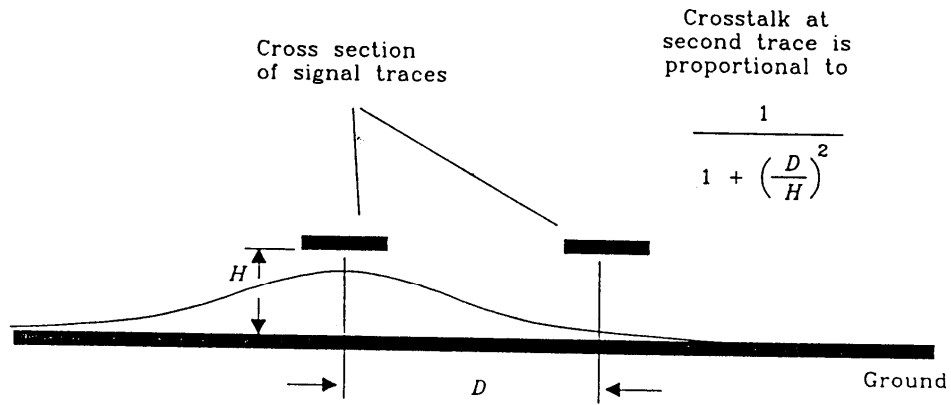


Figure 5.4 Cross section of two traces showing crosstalk.

Dielectric constant effect

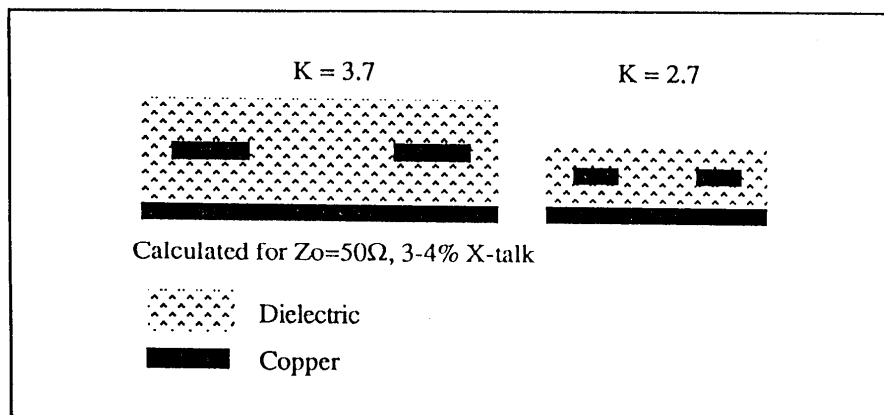


Figure 8.4 Increased circuit density through reduced dielectric constant.

Mutual capacitances

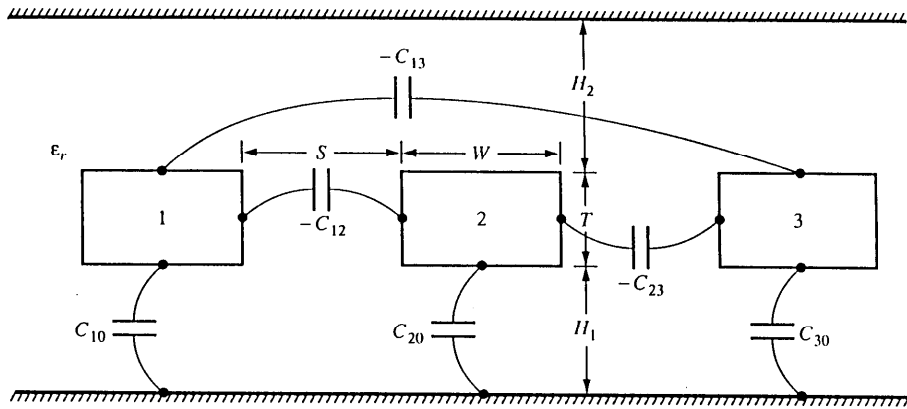



FIGURE 4-3
Cross section of three coupled lines in a homogeneous medium.

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

31

Even/odd modes

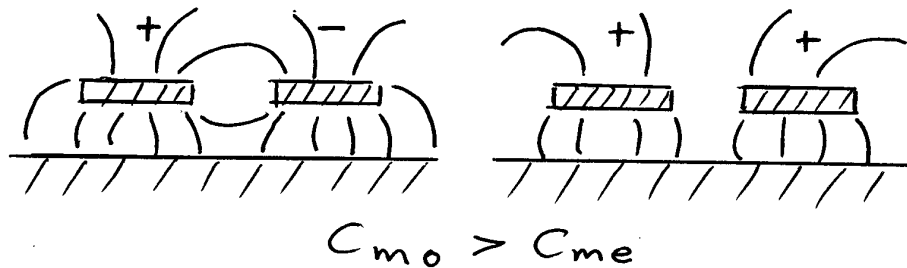


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

32

Wire/lead inductance

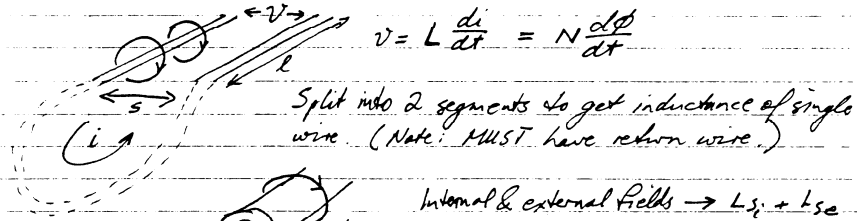

Internal & external fields $\rightarrow L_{si} + L_{se}$
 $L_{si} = \frac{\mu_0}{2\pi} \cdot \frac{l}{r} = \frac{\mu_0}{8\pi}$ / unit length
 $\mu_0 = 4\pi \times 10^{-7} \text{ H/m} \therefore L_{si} = 0.5 \text{ nH/cm}$
 $L_s = L_{si} + L_{se}$ and typically $L_{se} \gg L_{si}$
 $L_s \approx \frac{\mu_0}{2\pi} [\ln(2l/r) - 3/4] l$ for circular wire for $r \ll l$
 $\approx \frac{\mu_0}{2\pi} [\ln(4l/p) + 1/2] l$ for rectangular lead for perimeter p

Mutual inductance


$M = \frac{\mu_0}{2\pi} [\ln(\frac{l}{s} + \sqrt{1 + (\frac{l}{s})^2}) - \sqrt{1 + (\frac{s}{l})^2} + (\frac{s}{l})] l$

4/15/2012

ECE414/514 Electronics Packaging Spring 2012

33

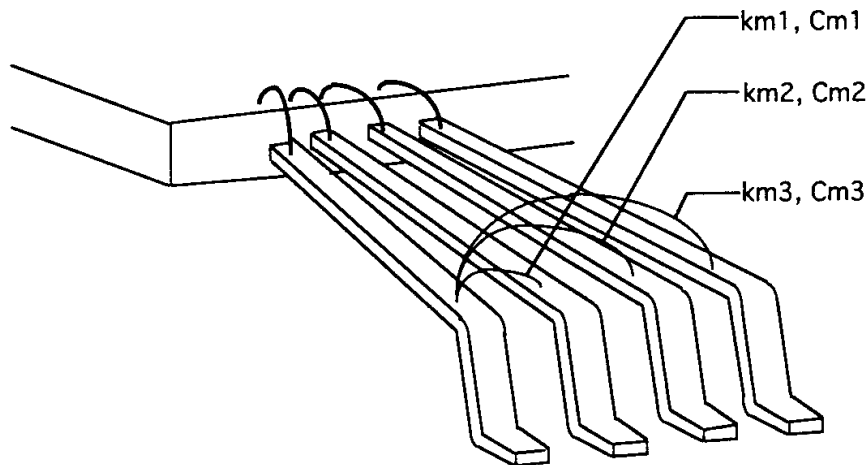Development of a SPICE model:
Package leads




4/15/2012

ECE414/514 Electronics Packaging Spring 2012

34

•User selectable configurations:

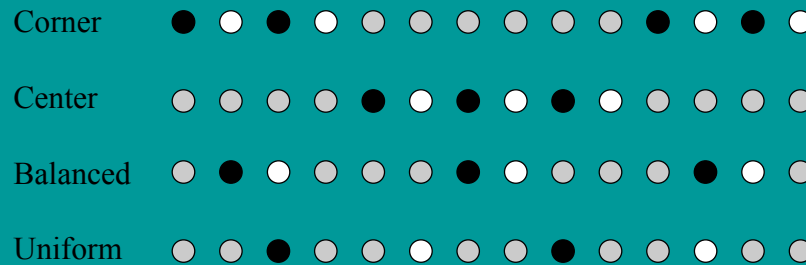

Power , ground, and signal line architectures

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

35

Analysis options

- 1. Delta-I noise model
- 2. Signal crosstalk model

V_P → ———

Signal → ———

G → ———

Specify: ΔI noise i.e. set I_P ($I_S=0$)
& assume all power lines same current I_P/n

OR signal crosstalk i.e. set I_S ($I_P=0$)
& assume all signal lines same current (i.e. $n_S I_S$ total)

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

36

Matrix calculations

- Induced voltages v_i due to changing currents I_i :
- $V_i = L_{i1}dI_1/dt + L_{i2}dI_2/dt + \dots + L_{ij}dI_j/dt + \dots + L_{in}dI_n/dt$
- $= \sum L_{ij} d(I_j)/dt$ for line $i = 1, 2, \dots, N$
- where $N =$ Number of leads/side
- $V_i =$ voltage at line i for $i = 1, 2, \dots, N$
- $I_i =$ current at line i for $i = 1, 2, \dots, N$
- $L_{ij} =$ mutual inductance between line i and line j
for $i, j = 1, 2, \dots, N$ and $i \neq j$
- $L_{ii} =$ self-inductance of line i for $i = 1, 2, \dots, N$

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

37

$$\begin{array}{c} \left| \begin{array}{c} v_1 \\ v_2 \\ v_3 \\ \vdots \\ v_N \end{array} \right| = \begin{array}{c} \left| \begin{array}{cc} L_{11} & L_{12} \\ L_{21} & L_{22} \\ \vdots & \vdots \\ L_{n1} & \vdots \end{array} \right| \end{array} \begin{array}{c} \left| \begin{array}{c} I_1 \\ I_2 \\ \vdots \\ I_N \end{array} \right| \end{array}$$

| L | symmetrical, $L_{ij} = L_{ji} = M_{ij}$ $L_{ii} \rightarrow L_i$

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

38

$$[(N+1) \text{ by } 1 \text{ matrix}] = [(N+1) \text{ by } N \text{ matrix}] * [N \text{ by } 1 \text{ matrix}]$$

$$\begin{array}{c}
 \left| \begin{array}{c} v_1 \\ v_2 \\ v_3 \\ \\ \\ v_N \\ 0 \end{array} \right|
 \end{array}
 =
 \begin{array}{c}
 \left| \begin{array}{ccc}
 L_{11} & L_{12} & \\
 L_{21} & L_{22} & \\
 & & \\
 \\ & & \\
 L_{N1} & & \\
 1 & 1 & 1
 \end{array} \right|
 \end{array}
 *
 \begin{array}{c}
 \left| \begin{array}{c} I_1 \\ I_2 \\ \\ \\ \\ \\ I_N \end{array} \right|
 \end{array}$$

Model choice

- According to the layout specified by the user,
- V_i 's and I_i 's are divided into three categories: power (V_p, I_p), signal (V_s, I_s), and ground (V_g, I_g)
- For delta-I noise model,
- 1. set I_p (assuming all power lines have the same current)
- 2. set $I_s = 0$
- For signal crosstalk model,
- 1. set I_s (assuming all signal lines have the same current)
 - 2. set $I_p = 0$
- Assuming pin 1 is ground,
- set V_g 's = V_1

$$|A| |y| = |X| |x| \rightarrow |y| = |A|^{-1} |X| |x|$$

- Rearranging the matrix equations by moving all L_{ij} 's (where I_j is I_g) to the left side results in:
- $[(N+1) \text{ by } (N+1) \text{ matrix}] * [(N+1) \text{ by } 1 \text{ matrix}] = [(N+1) \text{ by } (N-n) \text{ matrix}] * [(N-n) \text{ by } 1 \text{ matrix}]$


$$\begin{array}{c} \cdot \\ \cdot \\ \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \\ \cdot \end{array} \begin{array}{c} 1 \ 0 \ 0 \quad 0 \ 0 \ -L_{11} \\ 1 \ 0 \quad \quad 0 \\ \\ 1 \ 0 \quad \quad 0 \\ 0 \ 1 \ 0 \ 0 \quad 0 \\ 0 \ 0 \ 1 \ 0 \\ 0 \ 0 \ 1 \\ \\ \\ 0 \ 0 \quad \quad 1 \ 0 \\ 0 \ 0 \quad 0 \ 1 \ -L_{N1} \\ 0 \ 0 \ 0 \quad 0 \ 0 \ -1 \ -1 \quad -1 \end{array} \begin{array}{c} V_1 \\ V_2 \\ \\ V_N \\ I_1 \end{array} = \begin{array}{c} L_{12} \quad \quad L_{1N} \\ \\ \\ \\ L_{N2} \quad \quad L_{NN} \\ 1 \ 1 \quad 1 \ 1 \end{array} \begin{array}{c} I_2 \\ \\ \\ I_N \end{array}$$

4/15/2012

ECE414/514 Electronics Packaging Spring 2012

41

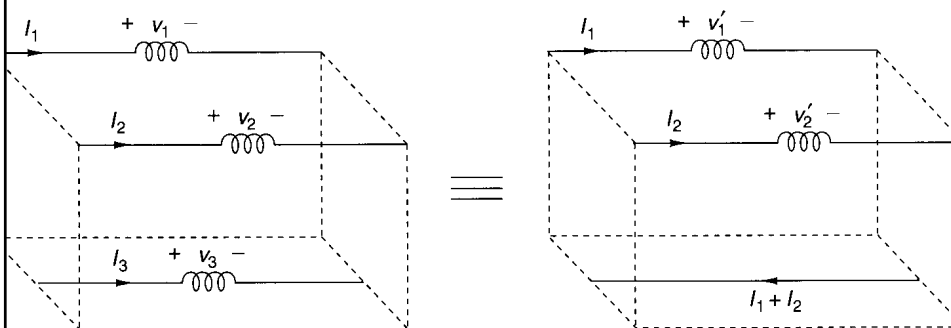Inductance/ground transform
(in practice for Spice, etc)
Need to reference a common ground



4/15/2012

ECE414/514 Electronics Packaging Spring 2012

42

Effective inductance

$$v_1 = L_{11}(di_1/dt) + L_{12}(di_2/dt) + L_{13}(di_3/dt)$$

$$v_3 = L_{31}(di_1/dt) + L_{32}(di_2/dt) + L_{33}(di_3/dt)$$

$$\text{and for ground return: } i_3 = -(i_1 + i_2)$$

$$v_1' = v_1 - v_3$$

$$= (L_{11} - L_{13} - L_{31} + L_{33})(di_1/dt) + (L_{12} - L_{13} - L_{32} + L_{33})(di_2/dt)$$

$$= L'_{11}(di_1/dt) + L'_{12}(di_2/dt)$$

$$\text{So have } L'_{ij} = L_{ij} - L_{ig} - L_{gj} + L_{gg} = 2(L_{ij} - L_{ig})$$

Use for inductive crosstalk $i \neq j$ $L'_{ij} \rightarrow M'_{ij}$
 and delta-I noise $i = j = s(\text{org})$ $L'_{ij} \rightarrow L_s, (L_g)$

Also: Mutual capacitance crosstalk \rightarrow crosstalk currents
 (Develop voltages if impedances high)



4/15/2012

ECE414/514 Electronics
 Packaging Spring 2012

43

Coplanar lines

Multiple co-planar lines

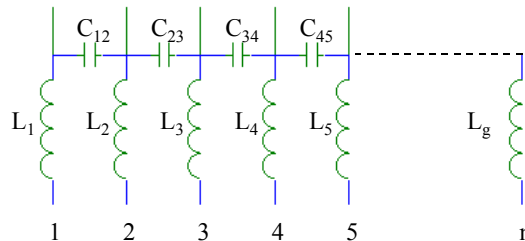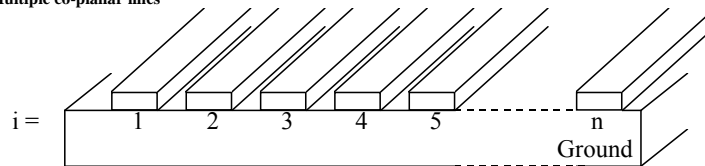

plus mutual inductance M_{ij}


where L_i is the self-inductance of an individual "isolated" wire.

4/15/2012

ECE414/514 Electronics
 Packaging Spring 2012

44

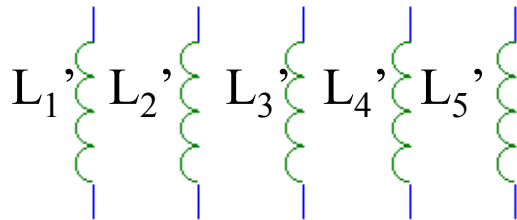Referencing all lines to v_n , taken
as $v_n = 0$ to define ground



ground

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

45

Effective L

- $L_s = L_i' = L_i + L_g - M_{ig} - M_{gi}$
- $M_{ig} = M_{gi}$ and if the lines are identical, $L_i = L_g$,
so
 - $L_i' = 2(L_i - M_{ig})$
- To evaluate crosstalk in the transmission line system, the mutual inductances become
 - $M_{ij}' = M_{ij} + (L_g - M_{ig} - M_{jg})$
- The self-inductance L_s includes both internal and external inductances $L_s = L_{si} + L_{se}$
- L_{si} varies with frequency (skin effect)


4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

46

Discrete wire to line model

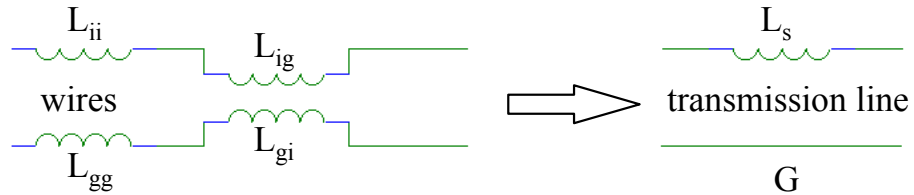Individual wires considered as a transmission line




4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

47

Coplanar lines with remote ground

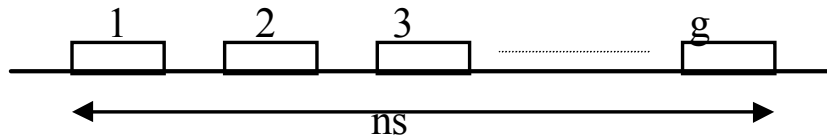4. Similarly, $M_{ij}' = L_{ij} - L_{ig} - L_{gj} + L_{gg}$, where



$$n = |i - j|$$

Co-planar lines with “remote” ground line

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

48

Assignment #3

1. Dally et al, Problem 3.17 (see text for τ)
2. Dally et al, Problem 3.19
3. A lossless 10cm long microstrip transmission line as shown in Dally et al Fig. 3.17, is terminated in a load R_L equal to impedance Z_0 and driven by an ideal 1 volt voltage step source. Use SPICE (or any other similar program with which you are familiar) to plot the load waveforms over a period of 2.5 line delays, representing the line by:
 - (a) a single lumped L-C section
 - (b) 10 lumped L-C sections
 - (c) 100 lumped L-C sections, and
 - (d) a transmission line model.
 - (e) Comment on your results.
4. For a transmission line of impedance 50Ω driven by a source of impedance 0Ω and terminated by load 100Ω , determine the source and load reflection coefficients. Draw the reflection diagram for a propagation time of $4T$, and label all the quantities at each time interval.
5. Two identical signal lines of $Z_0 = 50\Omega$ are terminated by 50Ω loads. The signal lines are 2cm long, and the ramp-step source to line 1 changes at 10^9V/s . The mutual inductance between the two signal lines is 2nH, and the mutual capacitance is 2pF. Determine the crosstalk magnitudes on line 2, and sketch the crosstalk waveforms.

4/15/2012

ECE414/514 Electronics
Packaging Spring 2012

49