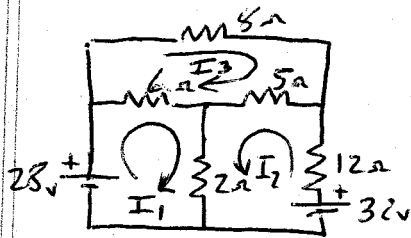


2.12(b)



Mesh equations

$$28 = 6(I_1 - I_3) + 2(I_1 + I_2)$$

$$32 = 12I_2 + 5(I_2 + I_3) + 2(I_1 + I_2)$$

$$8I_3 = 6(I_1 - I_3) + 5(-I_2 - I_3)$$

Rearrange as:

$$8I_1 + 2I_2 - 6I_3 = 28 \quad (1)$$

$$2I_1 + 19I_2 + 5I_3 = 32 \quad (2)$$

$$6I_1 - 5I_2 - 19I_3 = 0 \quad (3)$$

Solve by determinants or elimination

Eliminate I_1 , $4 \times (2) \rightarrow 8I_1 + 76I_2 + 20I_3 = 128$ $3 \times (2) \rightarrow 6I_1 + 57I_2 + 15I_3 = 96$

$4 \times (2) - (1) \rightarrow 74I_2 + 26I_3 = 100$ $3 \times (2) - (3) \rightarrow 62I_2 + 34I_3 = 96$

Rearrange to eliminate $I_2 = -\frac{13}{37}I_3 + \frac{50}{37} = \frac{48}{31} - \frac{17I_3}{31}$

$\therefore (50 - 13I_3)31 = 37(48 - 17I_3) \rightarrow I_3 = \frac{37 \times 48 - 31 \times 50}{37 \times 17 - 13 \times 31} = \frac{226}{226} = 1A$

$\therefore I_2 = \frac{96 - 34I_3}{62} = \frac{62}{62} = 1A$

$\therefore I_1 = \frac{32 - 5I_3 - 19I_2}{2} = 4A$ Hence $I = I_1 + I_2 = 5A$

2.12(c) Nodal analysis: Using the notation from 2.12(a) with $v_a = 28V$

$$\frac{28 - v_b}{6} + \frac{v_c - v_b}{5} = \frac{v_b}{2} \quad (1)$$

$$\frac{28 - v_c}{8} + \frac{v_b - v_c}{5} + \frac{32 - v_c}{12} = 0 \quad (2)$$

$(1) \times 30 \rightarrow 140 = 26v_b - 6v_c \quad \times 49/2 \rightarrow$ & Subtract to elim v_c

$(2) \times 120 \rightarrow 740 = -24v_b + 49v_c \quad \times 3 \rightarrow$



$$\left. \begin{array}{l} 13 \times 49v_b - 3 \times 49v_c = 49 \times 70 \\ 3 \times 24v_b - 3 \times 49v_c = -3 \times 740 \end{array} \right\}$$

$v_b = \frac{34 \times 30 + 2220}{565} = 10V \quad \therefore I = 10V / 2\Omega = 5A$

Conclusions:

- All 3 methods give the same result
- Mesh and nodal analyses are more efficient than the "brute force" element equations (and nodal is easier here because one begins with 2 unknowns instead of 3)


P2-22

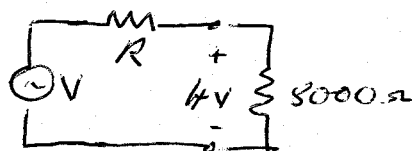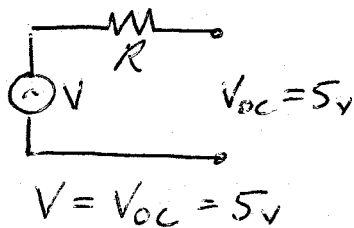


$$4V = \frac{8000}{8000 + R} V = \frac{8000 \times 5}{8000 + R}$$

$$\therefore R = \frac{40,000 - 8000 \times 4}{4} = 2000 \Omega$$

P2-26

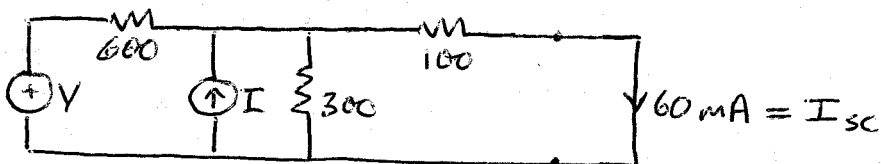


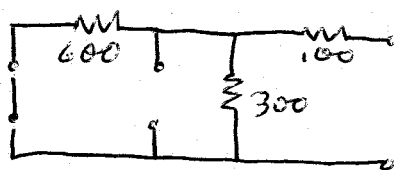No dependent sources, so can find $R_{Thermin}$ (ie R_T) by zeroing sources




$$\begin{aligned} R_T &= 100 + 300 // 600 \\ &= 100 + \frac{300 \times 600}{300 + 600} \\ &= 100 + 200 = 300 \Omega \end{aligned}$$

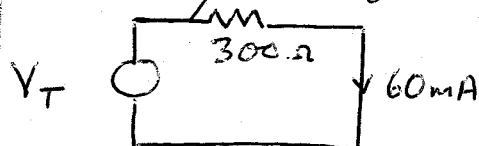[OR find R_T from V_{oc} , but to do this requires finding some relationship between V , I (unknown) and $I_{sc} = 60mA$] (see below)
Theremin equivalent:




$$\therefore V_T = 18V$$

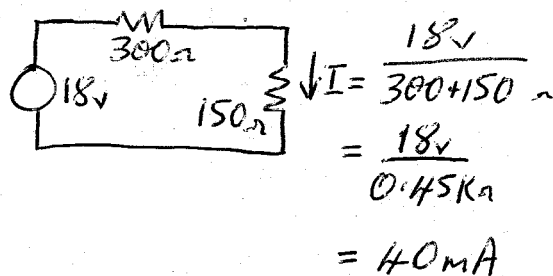


$$\begin{aligned} I &= \frac{18V}{300 + 150 \Omega} \\ &= \frac{18V}{0.45k\Omega} \\ &= 40mA \end{aligned}$$

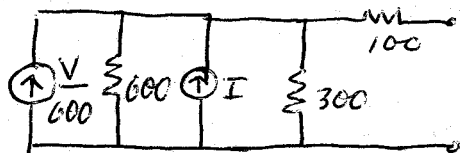By $R_T = V_{oc} / I_{sc}$, convert source to



$$\therefore V_{oc} = \left(I + \frac{V}{600} \right) 200 \Omega$$

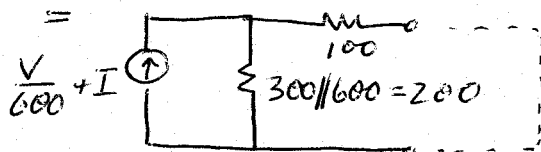
$$I_{sc} = \left(I + \frac{V}{600} \right) \frac{200}{200 + 100} = 60mA$$







$$\therefore R_T = V_{oc} / I_{sc} = \frac{200}{200/300} = 300 \Omega \text{ as before}$$

(Note also, can get $I + \frac{V}{600} = 60mA \times \frac{3}{2} = 90mA$)

2.33

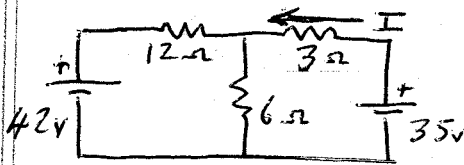

Find I by superposition

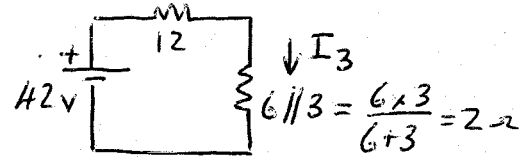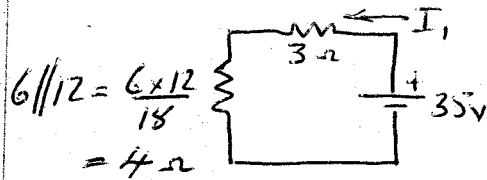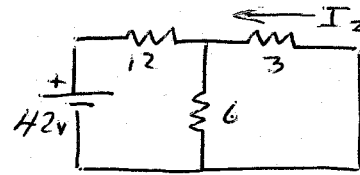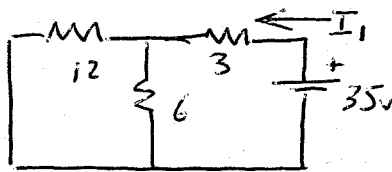


$$I_1 = \frac{35\text{V}}{3 + 4\Omega} = 5\text{A}$$

$$I_3 = 42 / (12 + 2) = 3\text{A}$$

$$\therefore I = I_1 + I_2 = 5 - 2 = 3\text{A}$$
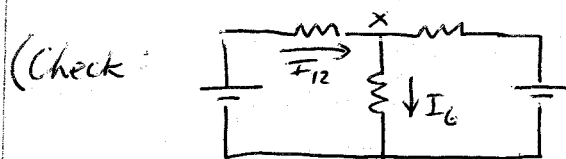
$$I_2 = -\frac{6}{3+6} I_3 = -\frac{2}{3}(3\text{A}) = -2\text{A}$$




$$V_x = 35 - 3\Omega \times 3\text{A} = 26\text{V}$$

$$I_6 = \frac{26}{6} = 4\frac{1}{3}\text{A} \quad I_{12} = \frac{42-26}{12} = 1\frac{1}{3}$$

$$\therefore I_6 = I + I_{12} = 3 + 1\frac{1}{3} = 4\frac{1}{3}\text{A} \text{ (Check.)}$$

P2.35

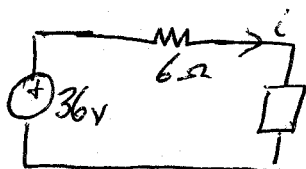

$$v = 6i + 4i^2$$

$$(a) \quad 36 = 6i + (6i + 4i^2)$$

$$4i^2 + 12i - 36 = 0$$

$$i = \frac{-12 \pm \sqrt{12^2 + 4 \times 4 \times 36}}{8}$$


$$= \frac{-12 \pm 12\sqrt{1+4}}{8}$$

(Note - in +/- not possible)



$$\therefore i = \frac{3}{2} (5^{1/2} - 1)$$

$$\approx \frac{3}{2} \cdot 1.24 = 1.92 \text{ A}$$

(b)

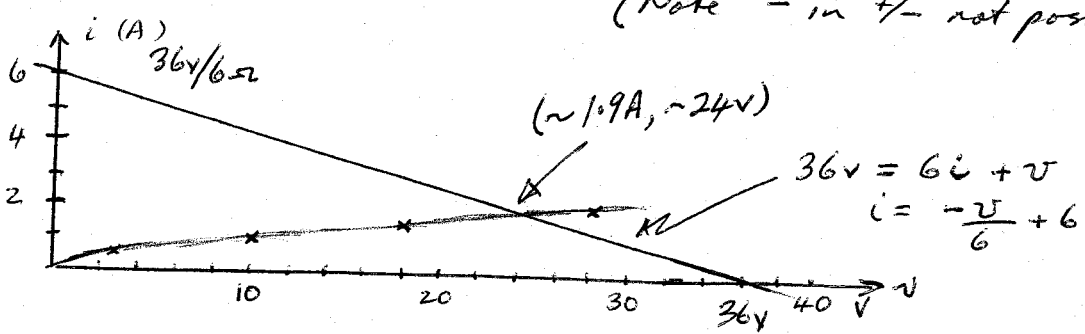

P2.36

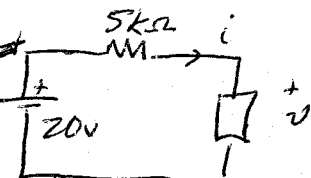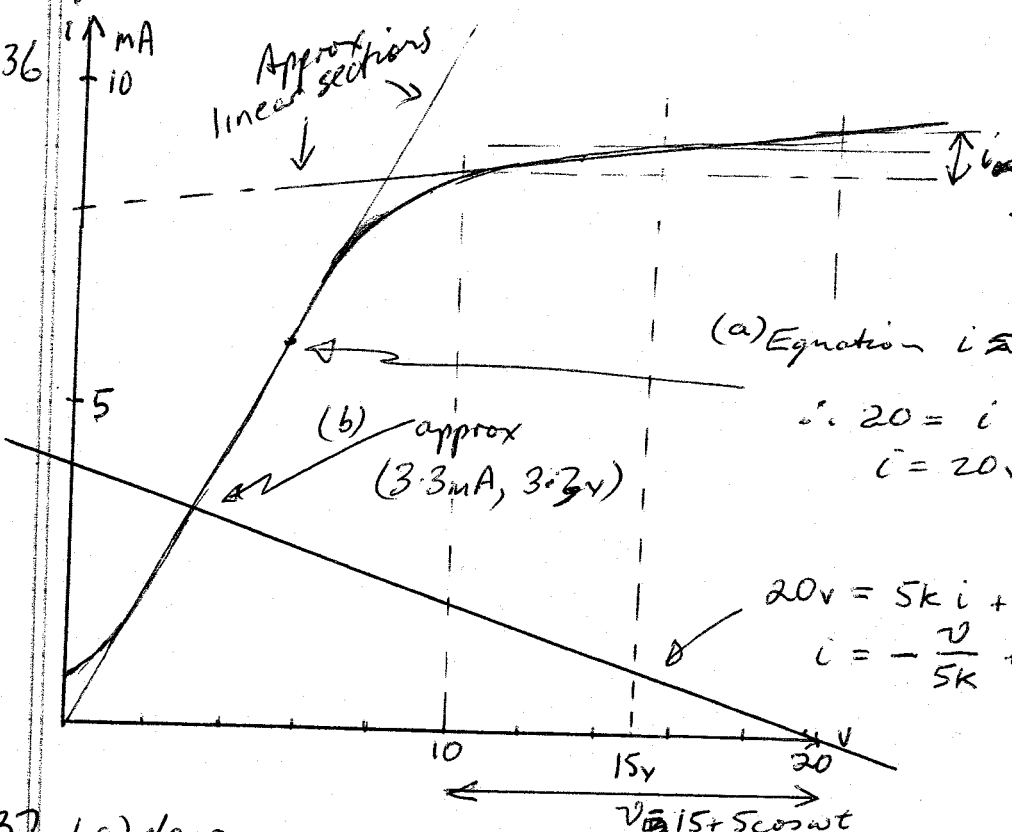

(a) Equation $i \approx \frac{6 \text{ mA}}{6 \text{ V}} v = 10^{-3} v$

$$\therefore 20 = i(5000 + 1000)$$

$$i = 20 \text{ V} / 6 \text{ k} = 3\frac{1}{3} \text{ mA}$$

$$20 \text{ V} = 5 \text{ k} i + v$$

$$i = -\frac{v}{5 \text{ k}} + \frac{20 \text{ V}}{5 \text{ k}} \leftarrow 4 \text{ mA}$$

P2.37


(a) done

(b) use upper section $i = 8 \text{ mA} + \frac{1 \text{ mA}}{13.5 \text{ V}} v$

$$\therefore i = 8 \text{ mA} + \frac{15}{13.5} \text{ mA} + \frac{5}{13.5} \cos wt \text{ mA}$$


$$\approx 9.1 \text{ mA} + 0.37 \text{ mA} \cos wt$$

AP2.6


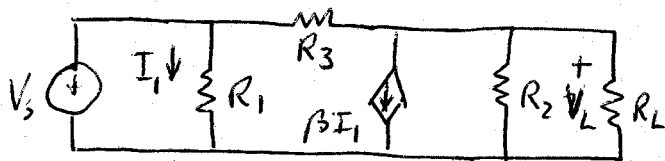


$R_1 = 10K$ $R_2 = 75K$ $R_3 = 150K$
 $\beta = 100$ $R_L = 20K$

(a) $I_1 = V_s/R_1$, simplify circuit

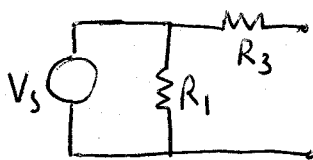

$V_{oc} = V_s$
 $I_{sc} = V_s/R_3$

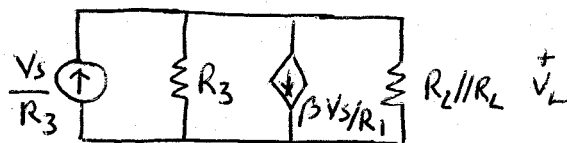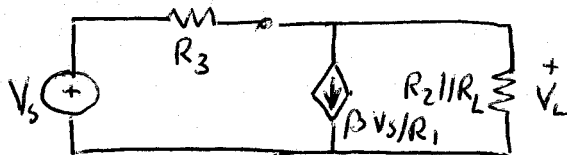

$$V_L = \left(-\beta \frac{V_s}{R_1} + \frac{V_s}{R_3} \right) (R_3 \parallel (R_2 \parallel R_L))$$

$$\frac{V_L}{V_s} = \left(-\beta \frac{1}{R_1} + \frac{1}{R_3} \right) \frac{R_3 R_2 R_L}{R_3 R_2 + R_2 R_L + R_L R_3}$$

$$= -\beta \frac{R_2 R_L}{R_1 (R_L + R_2) R_3 + R_2 R_L} + \frac{R_2 R_L}{R_3 (R_2 + R_L) + R_2 R_L}$$

$$= -\beta \frac{R_2 R_L}{R_1 (R_2 + R_L + \frac{R_2 R_L}{R_3})} + \frac{1}{R_3 \frac{(R_2 + R_L)}{R_2 R_L} + 1}$$

$$= -\beta \frac{(R_2 \parallel R_L)}{R_1 \left(1 + \frac{(R_2 \parallel R_L)}{R_3} \right)} + \frac{1}{1 + R_3 / (R_2 \parallel R_L)}$$

$\longrightarrow -\frac{\beta}{R_1} (R_2 \parallel R_L)$ for $R_3 \gg (R_2 \parallel R_L)$

(b)

$$\frac{V_L}{V_s} = -\frac{100}{10K} \frac{300K}{19} \frac{1}{1 + \frac{300}{19 \cdot 150}} + \frac{1}{1 + \frac{150}{300/19}}$$

$R_2 \parallel R_L$
 $= \frac{75 \times 20}{95} K$
 $= 300/19 K$


$$= -\frac{3000}{19} \frac{1}{1 + 2/19} + \frac{1}{1 + 19/2}$$

$$= -157.9/1.105 + 1/10.5 = -142.9 + 0.95$$

$$= -142.8$$

Approximation ($R_3 \rightarrow \infty$) gives -157.9

AP2.10

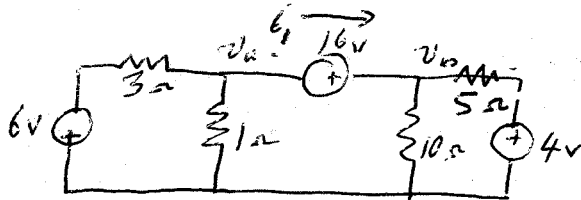

(b) Hence:

$$\frac{-6 - v_a}{3} - \frac{v_a}{1} - i_1 = 0$$

$$\frac{4 - v_b}{5} - \frac{v_b}{10} + i_1 = 0$$

$$\text{and (!)} \quad v_b - v_a = 16\text{V}$$

(a) when try to apply nodal analysis at v_a, v_b , cannot write the usual current equations through the sources because no defined resistance.

$$\left. \begin{aligned} \text{Solve } -6 - 4v_a &= 3i_1 \\ 8 - 3v_b &= -10i_1 \end{aligned} \right\}$$

$$v_a = \frac{-6 - 3i_1}{4} \quad v_b = \frac{8 + 10i_1}{3}$$

$$\text{So } v_b - v_a = 16 = \frac{-6 + 3i_1}{4} + \frac{8 + 10i_1}{3}$$

$$12 \times 16 = 32 + 40i_1 + 18 + 9i_1$$

$$49i_1 = 192 - 18 - 32 = 142$$

$$i_1 = 142/49 = 2 \frac{44}{49}$$

$$v_b = \frac{8 + \frac{1420}{49}}{3} = 12 \frac{16}{49}$$

$$\begin{aligned} \therefore v_a &= -\frac{3}{2} - \frac{3 \times 142}{4 \times 49} \\ &= -3 \frac{33}{49} \end{aligned}$$

