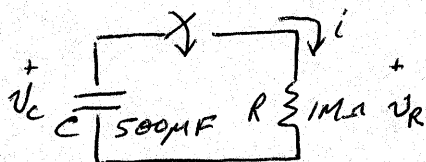


ECE 241 Assignment #2 Model Answers

Problems: P 3.7, 3.11, 3.13, 16.3, 16.6, 16.23, 16.29 AP/6.1

3.7



$$v_C(0) = 100 \text{ V}$$

Following Example 1

Current $i = I_0 e^{-t/\tau}$ and so $v = v_C = v_R = I_0 R e^{-t/\tau}$


But clearly $v(0) = I_0 R = 100 \text{ V}$ (given)

so $v(t) = 100 e^{-t/\tau}$ where $\tau = RC = 500 \times 10^{-6} \times 10^6 = 500 \text{ s}$.

If $v(T) = 14 \text{ V}$ at $t = T$ $14 = 100 e^{-T/500 \text{ s}}$

$$T = 500 \text{ s} \ln(100/14) = 983 \text{ s}$$

3.11

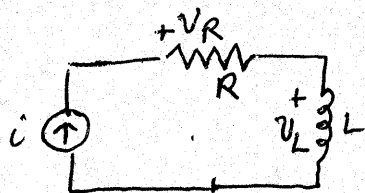


$$i = 2 \cos(2000t - \pi/4)$$

$$R = 20 \Omega \quad L = 10 \text{ mH}$$

$$v_R = iR = 40 \cos(2000t - \pi/4)$$

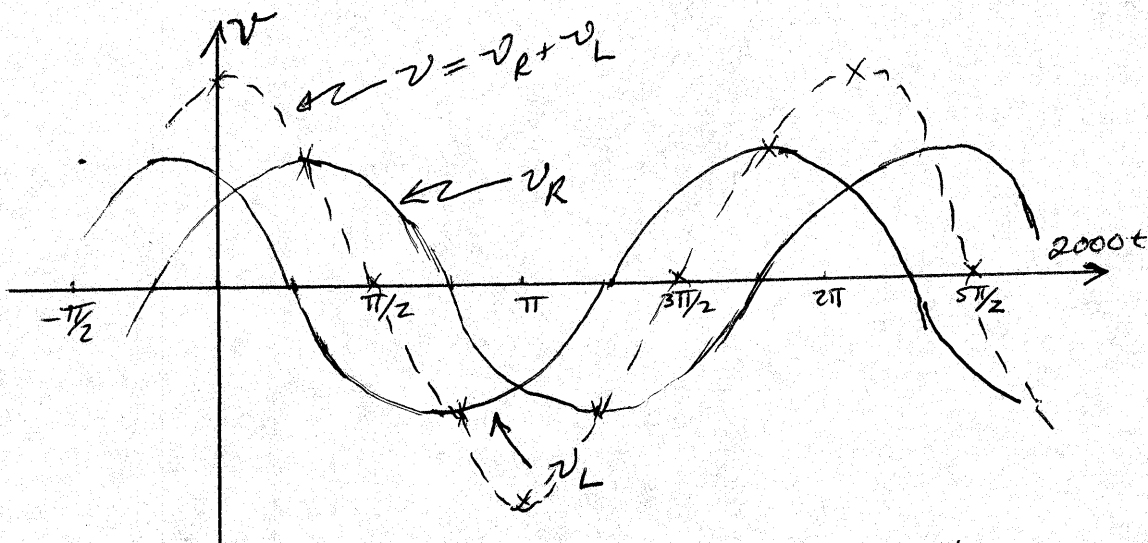
$$v_L = L \frac{di}{dt} = 2 \times 10^{-2} (-\sin(2000t - \pi/4)) 2000 = -40 \sin(2000t - \pi/4)$$



Amplitude of $v \approx \frac{3.2}{2} 40 = 64 \text{ V}$ (actually $\approx 57 \text{ V}$)
 so this plot not very good!

Phase of $v = 0^\circ$ (sine wave)

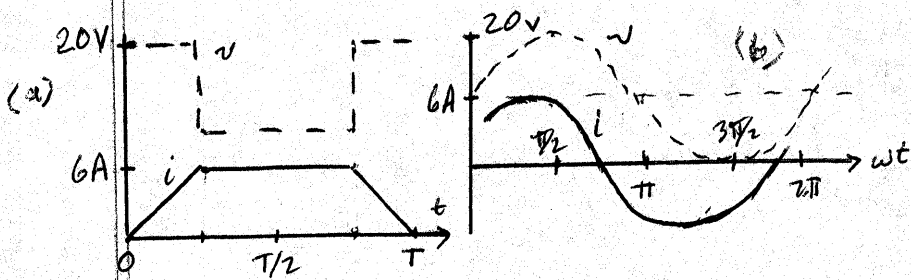3.13 Calculate average and effective values for each waveform



$$(a) v_{AV} = \frac{20 \frac{T}{4} + 10 \frac{T}{2} + 20 \frac{T}{4}}{T} = 15V$$

$$i_{AV} = \frac{\frac{1}{2} 6 \frac{T}{4} + 6 \frac{T}{2} + \frac{1}{2} 6 \frac{T}{4}}{T} = 4.5A$$

$$v_{eff} = \sqrt{(20^2 \frac{T}{4} + 10^2 \frac{T}{2} + 20^2 \frac{T}{4}) / T} = \sqrt{\frac{400}{4} + \frac{100}{2} + \frac{400}{4}}^{1/2} = \sqrt{250} = 15.81V$$

$$i_{eff} = \sqrt{(\frac{1}{3} 6^2 \frac{T}{4} + 6^2 \frac{T}{2} + \frac{1}{3} 6^2 \frac{T}{4}) / T} = \sqrt{24} = 4.90A$$

Graph (b) shows a linear ramp from 0 to a at time T.

$$y = \frac{a}{T} t$$

$$y^2 = \frac{a^2}{T^2} t^2$$


$$\int_0^T y^2 dt = \frac{a^2}{T^2} \int_0^T t^2 dt = \frac{a^2}{T^2} \cdot \frac{t^3}{3} \Big|_0^T = \frac{a^2}{3}$$

(b) $v_{AV} = 10V$ (DC component) $i_{AV} = 0A$ (DC component)

$$v_{eff} = \left[\frac{1}{T} \int_0^T (10 + 10 \sin \omega t)^2 dt \right]^{1/2} = \left[\frac{100}{T} \int_0^T (1 + \sin \omega t)^2 dt \right]^{1/2} = 10 \left[\frac{1}{T} \int_0^T (1 + 2 \sin \omega t + \frac{1}{2} - \frac{1}{2} \cos 2\omega t) dt \right]^{1/2}$$

$$= 10 \left(\frac{1}{T} \cdot \frac{3}{2} T \right)^{1/2} = 10 \sqrt{1.5} = 12.25V$$
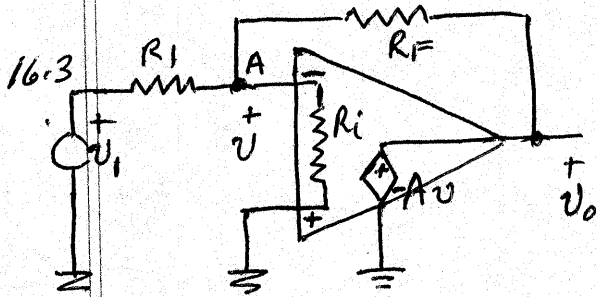
$$i_{eff} = i_{rms} = \frac{6}{\sqrt{2}} = 4.24A \quad (\text{for sine wave, even if phase shifted})$$



Note $v_0 = A(v^+ - v^-) = -Av$


$$\therefore v_0 = -Av = -A \frac{v_1}{\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_f} + \frac{A}{R_f}} = -\frac{R_f v_1}{1 + \left(\frac{R_f}{R_1} + \frac{R_f}{R_i} + 1\right) / A}$$

(b) $R_1 = 20k$ $R_f = 1M$ $R_i = 10M$ $A = 5 \times 10^4$
 Standard formula $\frac{v_0}{v_1} = -\frac{R_f}{R_1} = -\frac{10^6}{2 \times 10^4} = -50$


For $\frac{v_0}{v_1} = -\frac{R_f}{R_1} \frac{1}{1 + \left(\frac{R_f}{R_1} + \frac{R_f}{R_i} + 1\right) / A} = \frac{-50}{1 + \frac{50 + 0.1 + 1}{5 \times 10^4}} = \frac{-50}{1 + \frac{51.1}{5 \times 10^4}}$
 $= -50 / 1.001022 = -49.95$

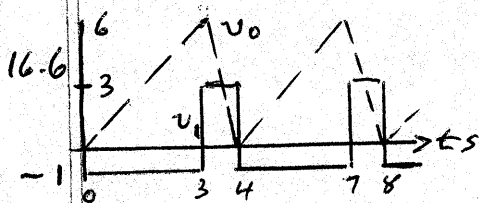(c) $R_i = 2M\Omega$ $A = 2 \times 10^4$
 $\frac{v_0}{v_1} = -50 / \left(1 + \frac{50 + 0.5 + 1}{2 \times 10^4}\right) = -50 / 1.002575 = -49.87$

In the approximation, A is more important than R_i , since large A forces a high effective R_i by negative feedback. Also, approximation reasonable for realistic A, R_i values.



v_0 is $-\int v_1 dt$

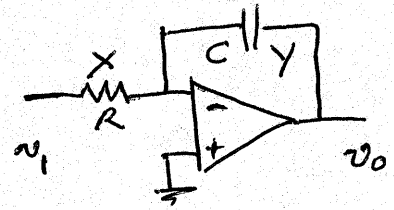


$$v_0 = -\frac{1}{RC} \int_0^t v_1 dt + IC \approx 0 \text{ at } t=0$$

$-\frac{1}{RC} \cdot \frac{-1v \times 3s}{1} = 6v \therefore \frac{1}{RC} = 2$ Select any reasonable values

- eg. $R = 1k\Omega$ $C = 500\mu F$
- $R = 10k\Omega$ $C = 50\mu F$
- $R = 100k\Omega$ $C = 5\mu F$


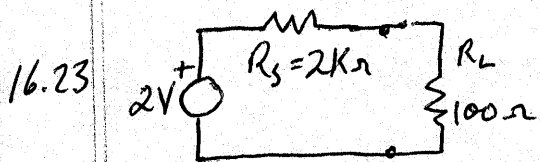
Probably best choice $\rightarrow R = 1M\Omega$ $C = 0.5\mu F$



(a)

$$v_L = \frac{100}{2100} 2V = 0.0952V$$

$$P_L = v_L^2 / R_L = 90.7 \mu W$$

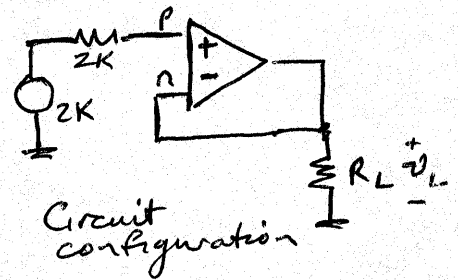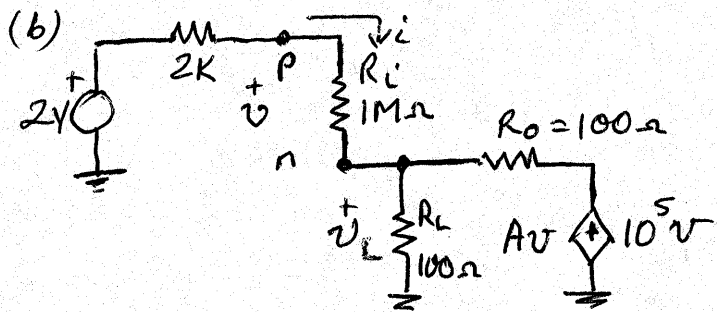

$$2V = 2000i + 10^6 i + v_L$$

$$i = \frac{v_L}{100} + \frac{v_L - 10^5 v}{100}$$


$$v = 10^6 i$$

$$\left. \begin{aligned} i &= \frac{v_L}{50} - 10^9 i \\ \therefore i &= \frac{v_L / 50}{1 + 10^9} \end{aligned} \right\} \left. \begin{aligned} 2 &= \frac{1002 \times 10^3 \times v_L}{50(1 + 10^9)} + v_L \end{aligned} \right\}$$



$$v_L = \frac{2}{1 + \frac{1.002 \times 10^6}{50 \times (1 + 10^9)}} \approx \frac{2}{1 + \frac{10^6}{5 \times 10^{10}}} = \frac{2}{1 + 2 \times 10^{-5}} \approx 2(1 - 2 \times 10^{-5})V \approx 2V$$

& $P_L \approx 2^2 / 100 = 40mW$

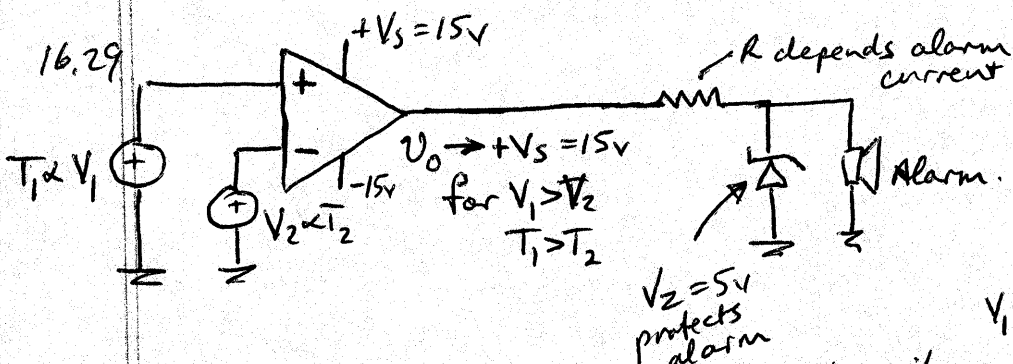Buffer is effective with practical opamp parameters



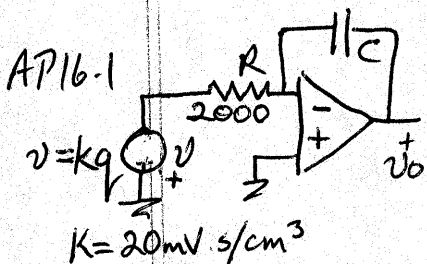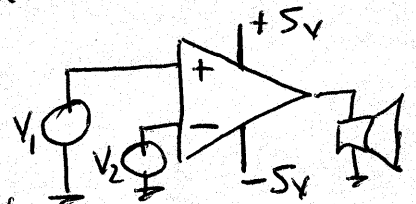Other possible output circuits eg. simplest



$$\int q dt = 200 cm^3 \rightarrow v_o = +10V$$

$$v_o = -\frac{1}{RC} \int -v dt = +\frac{K}{RC} \int q dt = \frac{20 \times 10^{-3} (200)}{2000 C} = 10V$$

$$\therefore C = \frac{4}{2 \times 10^4} F = 200 \mu F \text{ using the sensor } R_{out} \text{ as } R$$

OR increase R to say $200K - 2K = 198K$, $C = 2 \mu F$ etc.