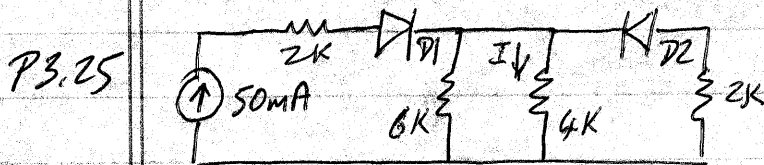



# FCE 241 Assignment #3 Model Answers

P3.25, 3.30, 3.32, 3.41, 3.48 AP3.6, 11.27, AP11.6



Assume  $D_1$  on,  $D_2$  off.  
For ideal Diodes:


redraw circuit!

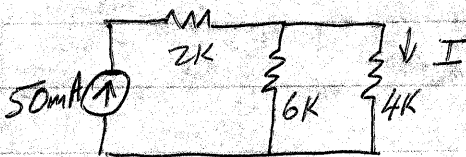

By current division,

$$I = \frac{6k}{6k+4k} 50mA = 30mA$$

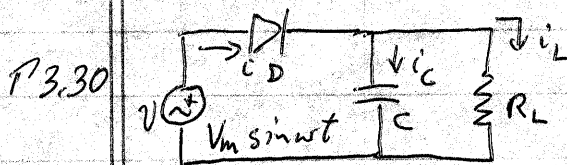Check:  $4k \times 30mA = +120V$ , reverse biasing  $D_2$ .



$C = 100\mu F$   $R_L = 10k\Omega$   $V_m = 20V$  at  $60Hz$

(a) DC load current  $i_L$

Time constant  $R_L C = 10^{-4} \times 10^4 = 1s \gg \frac{1}{60}s$  (sinusoid period)

$$\therefore \text{ripple } V_r \ll V_m \text{ and } i_L \approx \frac{V_m}{R_L} = \frac{20V}{10^4\Omega} = 2mA$$


$$(b) V_r = V_{DC} \frac{T}{R_L C} \approx \frac{V_m}{R_L} \frac{T}{C} = 2 \times 10^{-3} \frac{1/60}{10^{-4}} = \frac{1}{3} V$$

$$\% \text{ ripple} = \frac{1/3}{20} 100\% = \frac{100}{60}\% = 1.67\%$$



(c) Without  $C$ , circuit becomes simple  $\frac{1}{2}$  wave rectifier

$$\bar{I}_{DC} = \frac{I_m}{\pi} = \frac{V_m}{\pi R_L} = \frac{20}{\pi(10^4)} = 0.64mA$$


P3.32

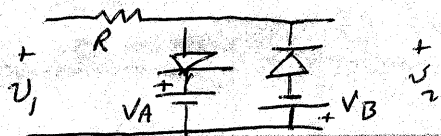

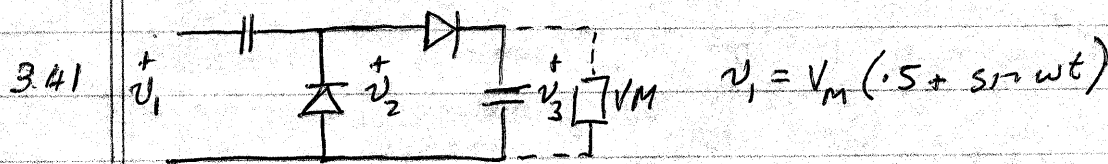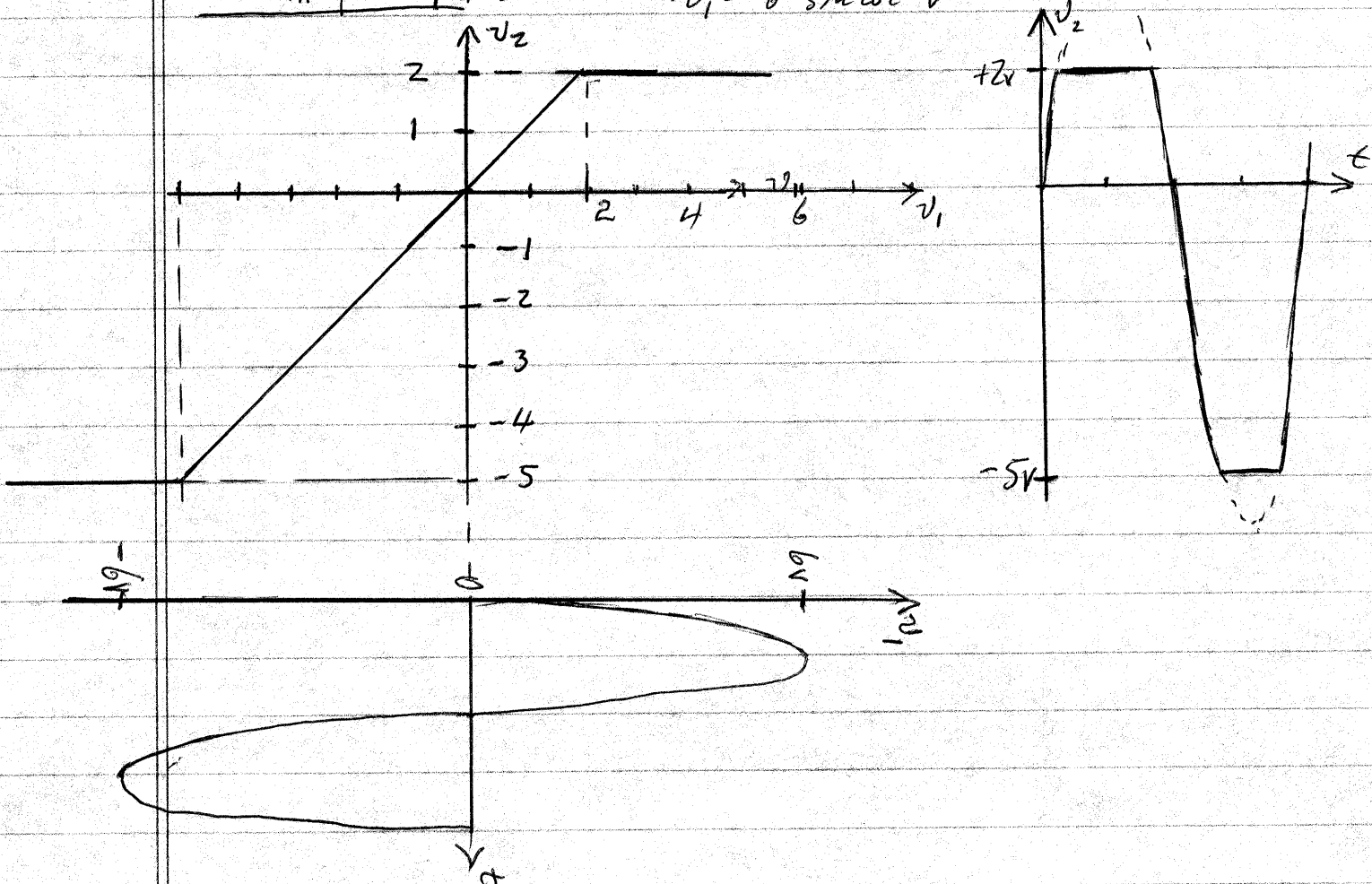
$R = 1K\Omega$   $V_A = 2V$   $V_B = 5V$   
 $v_1 = 6 \sin \omega t V$




(a) Voltage clamp. Peak rectifier

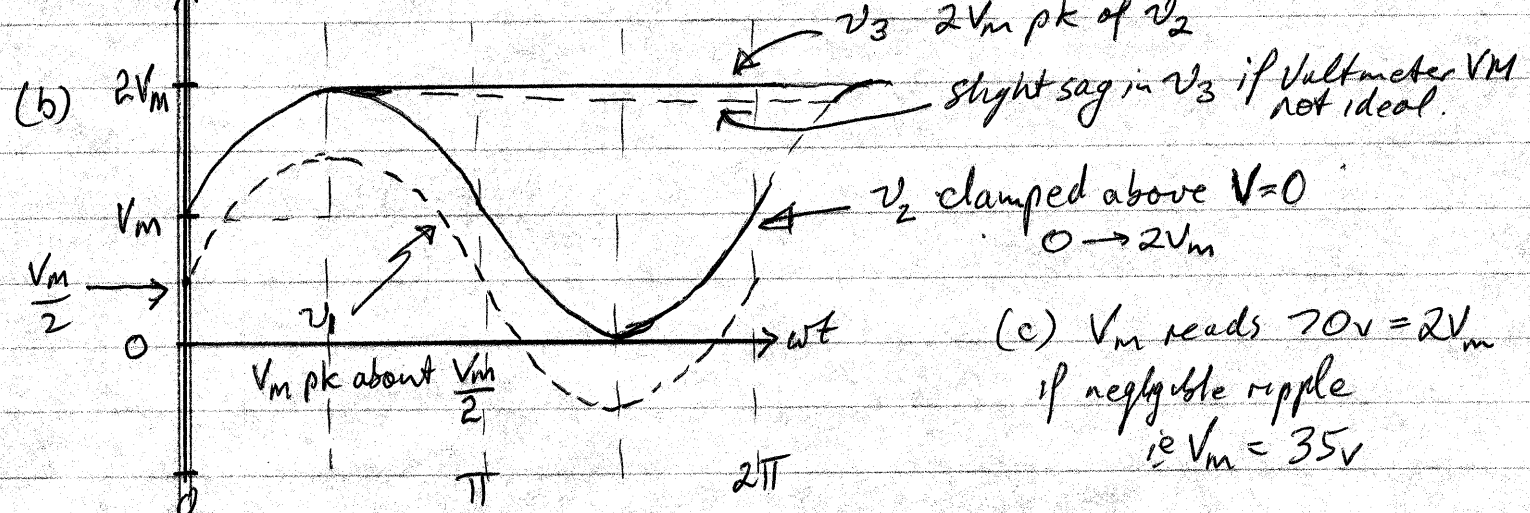


P3.48

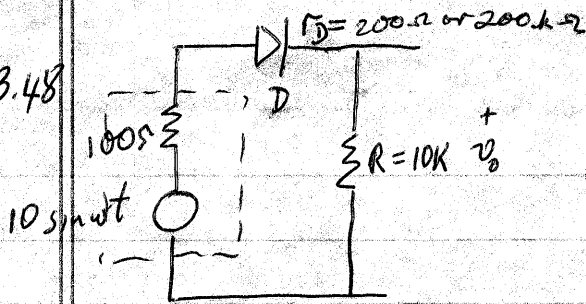



Diode model specified

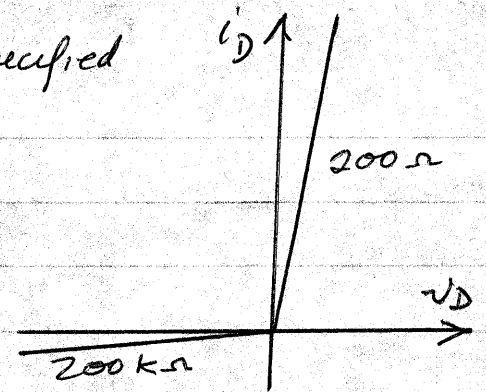


For  $v_i > 0$

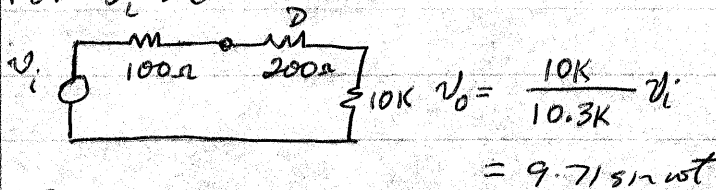

For  $v_i < 0$

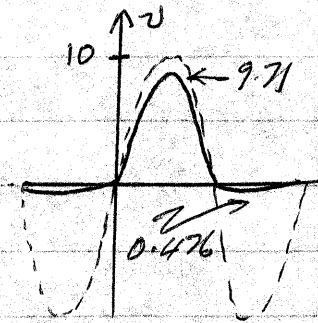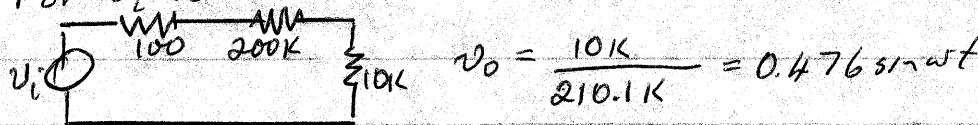

AP3.6

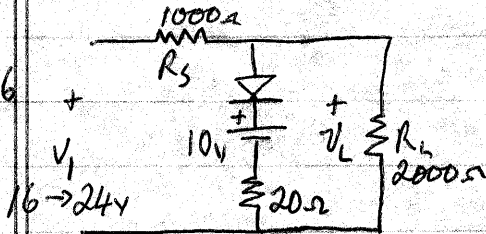

$$V_1 = V_L + \left( \frac{V_L - 10}{20} + \frac{V_L}{R_L} \right) R_s = V_L + \left[ \frac{V_L - 10}{20} + \frac{V_L}{2000} \right] 1000$$

$$= V_L + \frac{V_L}{2} + 50V_L - 500$$

$$\therefore V_L = \frac{V_1 + 500}{51.5}$$


$$V_1 = 16V \quad V_L = \frac{516}{51.5} = 10.02V$$

$$V_1 = 24V \quad V_L = \frac{524}{51.5} = 10.17V$$

$$\therefore \% \text{ change} = \frac{10.17 - 10.02}{10.02} 100\% = \frac{0.15}{10.02} 100\% \approx 1.5\%$$

ie. regulator working OK.

P11.28

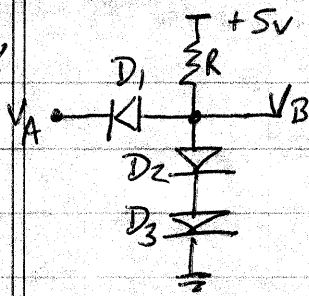


Assume 0.7 diode "on" voltage

$V_A$	$V_B$	
+2v	+1.4v	$D_2, D_3$ on $\therefore V_B = 1.4v$ & $D_1$ off
+1v	+1.4v	" " " " & $D_1$ off still (0.4v fwd bias)
0	+0.7v	$D_1$ on, 0.7v not enough to turn $D_2 + D_3$ on
-1v	-0.3v	" , $D_2, D_3$ off.

AP11.6

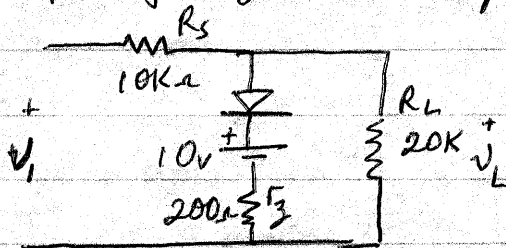Replacing the zener by its equivalent circuit



$$V_1 = 16 \rightarrow 24v$$

This is (inadvertently) almost a duplicate of AP3.6

$$V_1 = R_s \left( \frac{V_L - 10}{r_z} + \frac{V_L}{R_L} \right) + V_L$$

$$\rightarrow V_L = \frac{V_1 + 10 \frac{R_s}{r_z}}{1 + \frac{R_s}{r_z} + \frac{R_s}{R_L}} = \frac{V_1 + 10 \frac{10^4}{200}}{1 + \frac{10^4}{200} + \frac{10^4}{2 \times 10^4}} = \frac{V_1 + 500}{1 + 50 + 0.5}$$

$$= (V_1 + 500) / 51.5$$

$$\left. \begin{array}{l} V_1 = 16v \quad V_L = 516 / 51.5 \approx 10.02v \\ V_1 = 24v \quad V_L = 524 / 51.5 \approx 10.17v \end{array} \right\} \begin{array}{l} \% \text{ change} = \frac{0.15v}{10.02} 100\% \\ \approx 1.5\% \end{array}$$

$\therefore$  Regulator functioning.