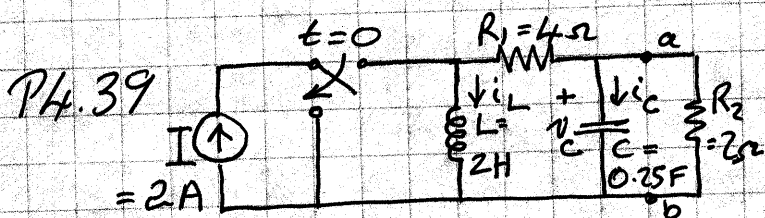


FCE 241 Assignment #4 Model Answers

Problems AP4.9, AP4.10, PH.39, PS.17, PS.38, APS.8



(a) At $t=0^+$
 $v_C(0^+) = 0$
 since $i_L(0) = I = 2A$


If $v_C(0^+) = 0$, $v_{R2}(0^+) = 0$ & $i_C(0^+) = -2A = C \frac{dv_C}{dt} \Big|_{t=0^+}$

$$\therefore \frac{dv_C}{dt} \Big|_{t=0^+} = \frac{-2}{0.25} = -8 \text{ v/s}$$

$$\begin{aligned} \text{(b)} \quad Y_{ab} &= \frac{1}{R_2} + sC + \frac{1}{R_1 + sL} = \frac{1}{2} + 0.25s + \frac{1}{4 + 2s} = \frac{1 + 2(s+2)(s+2)^{\frac{1}{4}}}{2(s+2)} \\ &= \frac{1 + \frac{1}{2}(s+2)^2}{2(s+2)} = 0.25 \frac{(s+2)^2 + 2}{(s+2)} = 0.25 \frac{(s+2 + j\sqrt{2})(s+2 - j\sqrt{2})}{(s+2)} \end{aligned}$$

Pole at $s = -2$

Zeros at $s_1, s_2 = -2 \pm j\sqrt{2}$

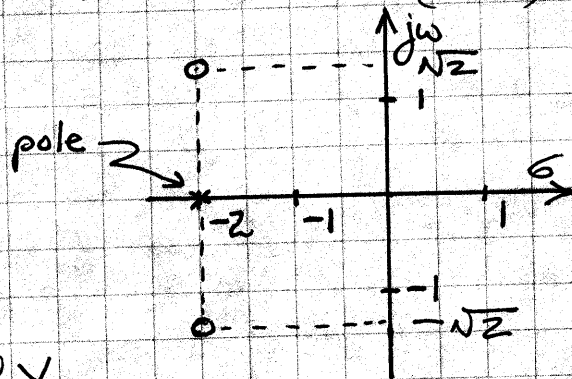

(c) Natural response of $v_C(t)$

depends on poles of Z_{ab} or zeros of Y_{ab}

i.e. $s_1, s_2 = -2 \pm j\sqrt{2}$

i.e. $v_C(t) = A e^{-2t} \cos(\sqrt{2}t + \phi)$


At $t=0^+$ $v_C(0^+) = 0 \therefore A \cos \phi = 0 \quad \phi = -90^\circ$ for $A \neq 0$

& $v_C(t) = A e^{-2t} \sin \sqrt{2}t$

At $t=0^+$ $\frac{dv_C}{dt} \Big|_{t=0^+} = -8 \text{ v/s} = A (e^{-2t} \sqrt{2} \cos \sqrt{2}t + e^{-2t} (-2) \sin \sqrt{2}t)$
 $= \sqrt{2}A \quad \therefore A = -8/\sqrt{2} = -5.66$

$\therefore v_C(t) = -5.66 e^{-2t} \sin \sqrt{2}t$

AP 4.9

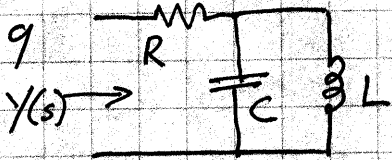


$$Y(s) = \frac{s^2 + 36}{s^2 + 6s + 36}$$

$$Z(s) = R + \frac{1}{sC + \frac{1}{sL}} = R + \frac{sL}{1 + s^2LC}$$

$$\begin{aligned} \therefore Y(s) &= \frac{1 + s^2LC}{s^2RLC + sL + R} = \frac{sL + R(1 + s^2LC)}{1 + s^2LC} \\ &= \frac{s^2 + 1/LC}{s^2R + s\frac{1}{C} + \frac{R}{LC}} = \frac{s^2 + 36}{s^2 + 6s + 36} \end{aligned}$$

ie. $R = 1 \quad C = \frac{1}{6} \quad L = \frac{1}{36C} = \frac{6}{36} = \frac{1}{6}$ Check: $\frac{R}{LC} = 1 \times 36$

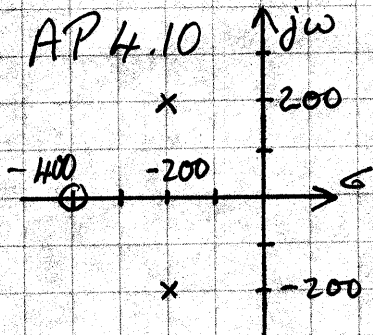$\therefore R = 1 \Omega \quad C = 0.17 F \quad L = 0.17 H$




Pole-zero diagram for $Z(s) = K \frac{s + 400}{(s + 200 - 200j)(s + 200 + 200j)}$

$$\begin{aligned} &= K \frac{s + 400}{(s + 200)^2 + 200^2} \\ &= K \frac{s + 400}{s^2 + 400s + 8 \times 10^4} \end{aligned}$$

Need a circuit with $Z(0) = \frac{K}{8 \times 10^4}$ ie. no series C or parallel L
 " " " " $Z(\infty) = 0$ ie. parallel C, not series L
 Looks like must be C || (R in series with L)
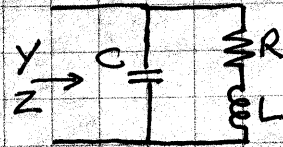
$$\begin{aligned} Y(s) &= sC + \frac{1}{R + sL} \\ &= \frac{1 + sC(R + sL)}{R + sL} \end{aligned}$$



$$\begin{aligned} Z(s) &= \frac{L}{LC} \frac{s + R/L}{s^2 + s\frac{RC}{LC} + \frac{1}{LC}} \\ &= \frac{1}{C} \frac{s + R/L}{s^2 + sR/L + 1/LC} \end{aligned}$$


Hence $R/L = 400$

$C = 1$

$\frac{1}{LC} = 8 \times 10^4 \therefore L = \frac{1}{8 \times 10^4} = 12.5 \mu H$


$R = 400 \times 12.5 \times 10^{-6} = 5 m\Omega$

P5.17

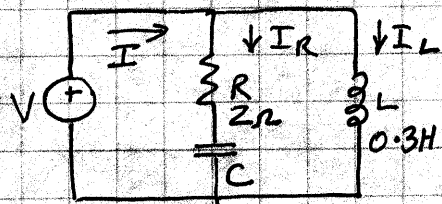

$$i_R = 10\sqrt{2} \cos(10t + 45^\circ) \text{ A}$$

(a) $\bar{I}_R = 10 \angle 45^\circ$

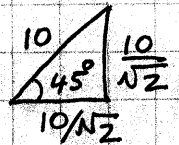


$$= 7.07 + 7.07j \text{ A}$$

$$\therefore \bar{V}_R = \bar{I}_R R = 14.14 + 14.14j \text{ V}$$

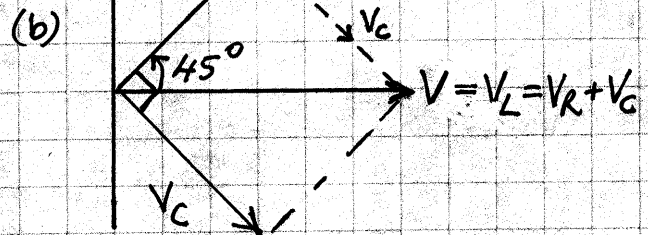
(c) $V = \frac{V_R}{\cos 45^\circ} = \frac{10 \times 2}{1/\sqrt{2}}$

$$= 20 \times 1.414 = 28.3 \text{ V}$$

$$v(t) = \frac{20}{\sqrt{2}} \sqrt{2} \cos 10t = 20 \cos 10t \text{ V}$$



P5.38

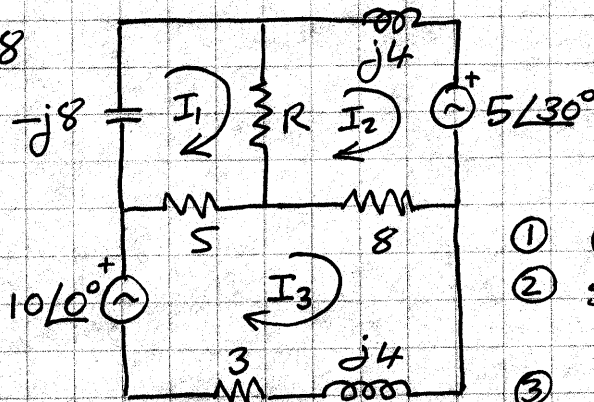

$$5 \angle 30^\circ = 5 \cos 30^\circ + j \sin 30^\circ = 5\sqrt{3}/2 + j 5/2$$

① $(I_1 - I_2)R = -(-j8)I_1 + 5(I_3 - I_1)$

② $5\sqrt{3}/2 + j 5/2 = -j4I_2 + R(I_1 - I_2) + 8(I_3 - I_2)$

③ $10 = 5(I_3 - I_1) + 8(I_3 - I_2) + I_3(3 + j4)$

$$I_1 (R + 5 - j8) + I_2 (-R) + I_3 (-5) = 0$$

$$I_1 (R) + I_2 (-R - j4 - 8) + I_3 (8) = 5\sqrt{3}/2 + j 5/2$$

$$I_1 (-5) + I_2 (-8) + I_3 (5 + 8 + 3 + j4) = 10$$

By determinants, terms in R do not disappear \therefore use $R = 5 \Omega$

$$I_1 (10 - j8) + I_2 (-5) + I_3 (-5) = 0$$

$$I_1 (5) + I_2 (-13 - j4) + I_3 (8) = 5\sqrt{3}/2 + 5/2j$$

$$I_1 (-5) + I_2 (-8) + I_3 (16 + j4) = 10$$

Solving by determinants gives $I = \frac{1000 + 100\sqrt{3} + 300j + 50\sqrt{3}j}{1851 + j1224}$



$$= \frac{1173.2 + 386.6j}{1851 + j1224} = \frac{1235.26 \angle 18.24^\circ}{2219.09 \angle 33.48^\circ}$$

$$= 0.56 \angle -15.24^\circ \text{ A}$$

AP 5.8

Assume the outside temperature varies sinusoidally
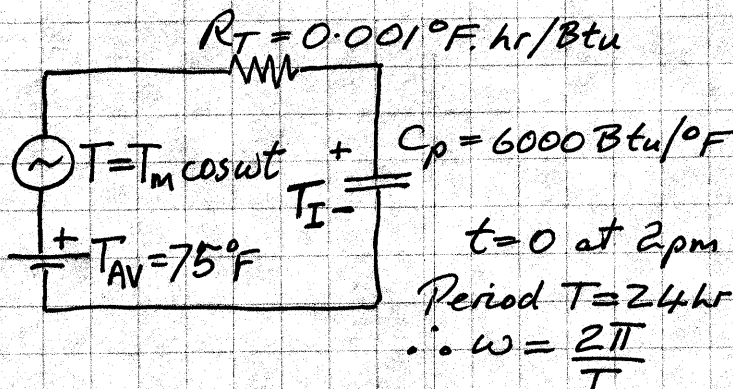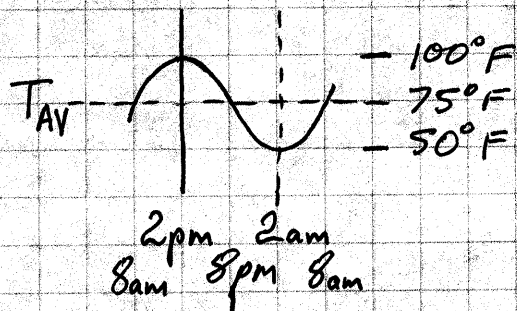
$$\left. \begin{array}{l} T_{\max} = 100^\circ\text{F at } 2\text{pm} \\ T_{\min} = 50^\circ\text{F at } 2\text{am} \end{array} \right\} \therefore T_{\text{AV}} = 75^\circ\text{F} \\ T_M = 25^\circ\text{F}$$



Consider DC $T_I)_{\text{DC}} = 75^\circ\text{F}$ (interior temperature)

Consider AC interior temperature $T_I)_{\text{AC}}$

$$\begin{aligned} T_I)_{\text{AC}} &= \frac{Z_c}{Z_c + Z_R} T = \frac{1/j\omega C_p}{R_T + 1/j\omega C_p} T \\ &= \frac{1}{1 + j\omega R_T C_p} T = \frac{1 - j\omega R_T C_p}{1 + (\omega R_T C_p)^2} T \end{aligned}$$

$$\begin{aligned} \omega R_T C_p &= \frac{2\pi}{24} 10^{-3} 6 \times 10^3 \frac{\text{rad}}{\text{hr}} \frac{^\circ\text{F hr}}{\text{Btu}} \frac{\text{Btu}}{^\circ\text{F}} \\ &= \frac{\pi}{2} \text{ radians} \end{aligned}$$

$$\begin{aligned} &= \frac{1 - j\pi/2}{1 + (\pi/2)^2} 25^\circ\text{F} \angle 0^\circ \\ &= \frac{25^\circ\text{F}}{\sqrt{1 + (\pi/2)^2}} \angle 0^\circ + \tan^{-1} \frac{-\pi/2}{1} \\ &= \frac{25^\circ\text{F}}{1.86} \angle -57.52^\circ \\ &= 13.44^\circ \angle -57.52^\circ \end{aligned}$$

So complete $T_I = 75^\circ\text{F} + 13.44^\circ \cos(\omega t - 57.52^\circ)$

$$\text{Minimum } T_I = 75 - 13.44 = 61.56^\circ\text{F}$$

occurring at $\omega t - 57.52^\circ = 180^\circ$
i.e. $t = \frac{237.52}{360} 24\text{hrs}$ after 2pm

$= 15.835\text{hrs}$ (or 15hr 50.1min) after 2pm
i.e. at 5:50.1am (3hrs 50min after the external min at 2am)