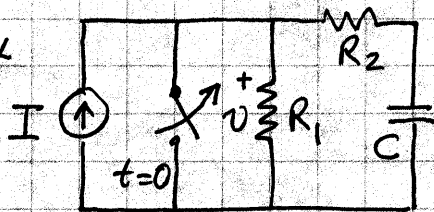


ECE 241 Assignment #5 Model Answers

Problems P6.14, 6.16, 6.20, 6.22, 7.3, 7.5, 7.9, 7.10

P6.14



$$(a) Y(s) = \frac{1}{R_1} + \frac{1}{R_2 + \frac{1}{sC}} = \frac{1}{R_1} + \frac{sC}{1 + sR_2C}$$

$$= \frac{1 + sR_2C + sR_1C}{R_1(1 + sR_2C)} = \frac{1}{R_1} \frac{1 + s(R_1 + R_2)C}{1 + sR_2C}$$

(b) Forced response: DC, $\therefore s=0$ $Y(0) = 1/R_1$ $v_F = I/Y(0) = IR_1$

(c) Natural response: Voltage from zeros of Y $s = -\frac{1}{(R_1 + R_2)C}$

$$\therefore v_N = A e^{-t/(R_1 + R_2)C}$$


(d) Complete response $v = v_F + v_N = IR_1 + A e^{-t/(R_1 + R_2)C}$

Initially $v_C(0) = 0$ $\therefore v(0^+) = I(R_1 \parallel R_2) = IR_1 + A$

$$\therefore A = I \left(\frac{R_1 R_2}{R_1 + R_2} - R_1 \right) = -I \frac{R_1^2}{R_1 + R_2}$$

$$\therefore v(t) = IR_1 \left(1 - \frac{R_1}{R_1 + R_2} \exp\left(-\frac{t}{(R_1 + R_2)C}\right) \right)$$

P6.16

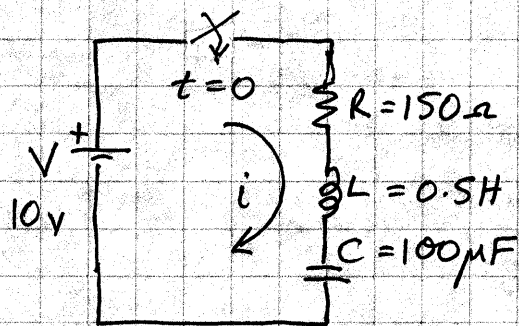

Find complete current response

$$Z(s) = 150 + 0.5s + \frac{1}{10^{-4}s}$$

$$= \frac{0.5s^2 + 150s + 10^4}{s}$$

Pole of $Z(s)$ at $s=0$

Forced (DC) response $i_F = 0$

Zeros of $Z(s) = 0.5 \frac{s^2 + 300s + 2 \times 10^4}{s}$ at $s = -150 \pm \sqrt{150^2 - 2 \times 10^4}$

$$= -150 \pm 50$$

$$= -100, -200$$

\therefore Natural response $i_N = Ae^{-100t} + Be^{-200t}$

& Complete response $i = i_F + i_N = Ae^{-100t} + Be^{-200t}$


At $t=0^+$ $i(0^+) = 0 \therefore A = -B$

and $v_C(0^+) = 0$ and $v_R(0^+) = 0 \therefore V = L \left. \frac{di}{dt} \right|_{t=0^+} = 10 = (0.5) \begin{bmatrix} -100A \\ -200B \end{bmatrix}$


$$\therefore \frac{20}{100} = -A + 2A$$

$$A = 0.2$$

$$i(t) = 0.2(e^{-100t} - e^{-200t})$$

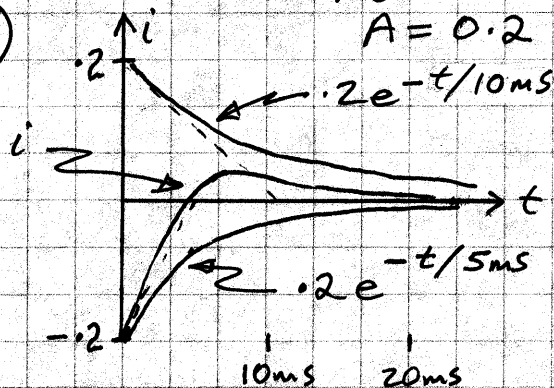

P6.20

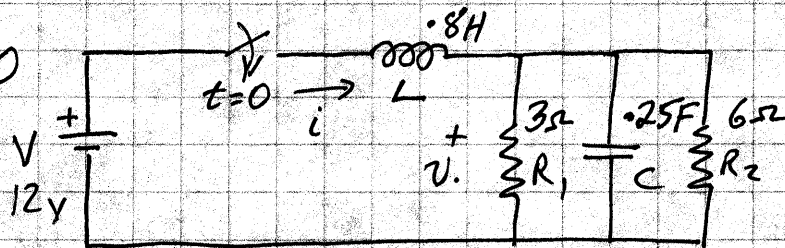

Find $i(t)$

$$R_p = \frac{3 \times 6}{3 + 6} = 2 \Omega$$

Forced (dc) response:

$$Z(0) = 0.8 \frac{V}{2} = 2 \Omega$$

$$\therefore i_F = 12V / 2\Omega = 6A$$

Zeros of $Z(s)$ for natural current response:

$$s_1, s_2 = -1 \pm \sqrt{1^2 - 5}$$

$$= -1 \pm j2$$

\therefore Natural response $i_N(t) = Ae^{-t} \cos(2t + \theta)$

\therefore Complete response $i = i_F + i_N = 6 + Ae^{-t} \cos(2t + \theta)$

At $t=0^+$ $i=0 \therefore 6 + A \cos \theta = 0 \quad A \cos \theta = -6$

$L \frac{di}{dt} = V \therefore \frac{12}{0.8} = A ([-\sin \theta]2 + (-1) \cos \theta)$

$$A(\cos \theta + 2 \sin \theta) = -15$$

$$-6 + 2A \sin \theta = -15$$

$$A \sin \theta = -9/2$$


$$\therefore \frac{A \sin \theta}{A \cos \theta} = \frac{-9/2}{-6} = \frac{3}{4} = \tan \theta \quad \therefore \theta = 36.87^\circ$$

$$A = -6 / \cos 36.87^\circ = -7.5$$

$$\therefore i(t) = 6 - 7.5 e^{-t} \cos(2t + 36.87^\circ)$$

$$\begin{aligned} Z(s) &= sL + \frac{R_1 R_2 / sC}{R_1 R_2 + (R_1 + R_2) / sC} \\ &= sL + \frac{1/sC}{1 + 1/sCR_p} \\ &= sL + \frac{R_p}{1 + sR_p C} \\ &= \frac{R_p + sL + s^2 R_p L C}{1 + sR_p C} \\ &= \frac{2 + 0.8s + .4s^2}{1 + s(2)} \\ &= \frac{.4}{.5} \frac{s^2 + 2s + 5}{s + 2} \end{aligned}$$

P6.22

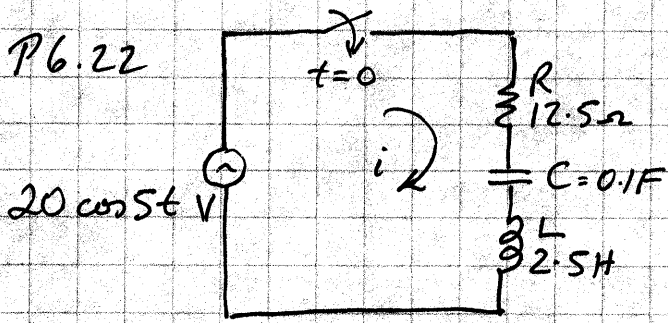

$$Z(s) = R + sL + \frac{1}{sC}$$

$$= 12.5 + 2.5s + \frac{10}{s}$$

$$= \frac{2.5s^2 + 12.5s + 10}{s}$$

$$= 2.5 \frac{s^2 + 5s + 4}{s} = \frac{2.5(s+4)(s+1)}{s}$$

Forced response $s = j5$

$$Z(j5) = 2.5 \frac{-25 + 25j + 4}{5j} = 2.5 \left(\frac{-21 + 25j}{5j} \right) = 12.5 + j10.5$$

$$= 16.325 \angle 40^\circ$$

$$\therefore i_F = \frac{20}{16.325} \angle -40^\circ = 1.225 \cos(5t - 40^\circ)$$

Natural response: Zeros of $Z(s)$ $s_1, s_2 = -1, -4$

$$\therefore \text{Natural response } i_N = Ae^{-t} + Be^{-4t}$$

$$\text{Total response: } i = 1.225 \cos(5t - 40^\circ) + Ae^{-t} + Be^{-4t}$$

$$\text{At } t=0^+ \quad i=0 \quad \therefore A+B = -1.225 \cos -40^\circ = -0.9384$$

$$V = 20V = L \left. \frac{di}{dt} \right|_{t=0} = 2.5 \left[-1.225 \cdot 5 \sin(5t - 40^\circ) - Ae^{-t} - 4Be^{-4t} \right]_{t=0}$$

$$= -2.5 [A + 4B - 3.937]$$


$$\therefore A + 4B - 3.937 = -8$$

$$A + 4B = -4.063 \quad \left. \begin{array}{l} 3B = -3.1246 \\ B = -1.0415 \\ A = 1.0415 - 0.9384 = +0.1031 \end{array} \right\}$$

$$A + B = -0.9384$$

$$A = 1.0415 - 0.9384 = +0.1031$$
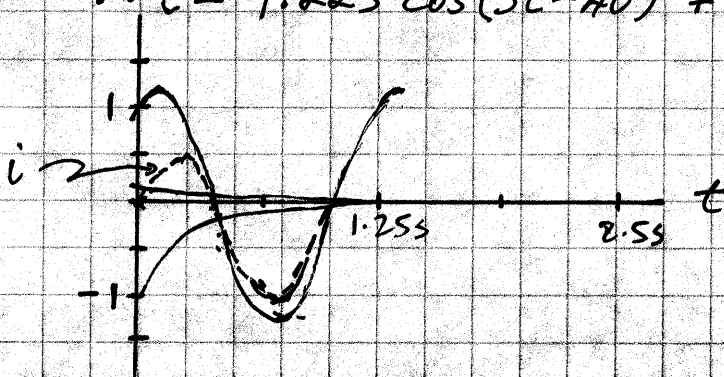
$$\therefore i = 1.225 \cos(5t - 40^\circ) + 0.1031 e^{-t} - 1.0415 e^{-4t}$$



$$\omega = 5 = 2\pi f$$

$$\therefore T = \frac{1}{f} \approx \frac{1}{8} \approx 1.25s$$

P7.3. (a) Current coil $i = 10\sqrt{2} \cos(\omega t + 45^\circ)$
 Voltage coil $v = 220\sqrt{2} \cos(\omega t - 15^\circ)$

$$I = 10 \angle 45^\circ \quad V = 220 \angle -15^\circ \quad P = VI \cos \theta, \quad \theta = 45^\circ - (-15^\circ)$$

$$\therefore P = 10 \times 220 \cos 60^\circ = 1100 \text{ W}$$

(b) $i = 5 \cos(\omega t - 120^\circ)$ $v = 20 \cos(\omega t - 75^\circ)$

$$I = \frac{5}{\sqrt{2}} \angle -120^\circ \quad V = \frac{20}{\sqrt{2}} \angle -75^\circ \quad \theta = -120^\circ - (-75^\circ) = -45^\circ$$

$$\therefore P = \frac{5}{\sqrt{2}} \times \frac{20}{\sqrt{2}} \cos -45^\circ = 50 \frac{1}{\sqrt{2}} = 35.4 \text{ W}$$

P7.5 200V 60Hz 10KW at leading pf = 0.55

(a) Current & reactive power: Av power $P = 10^4 \text{ W} = VI \cos \theta$
 $= 200I(0.55)$

Leading pf $\therefore \theta = \cos^{-1}(0.55) = -56.6^\circ$ $\therefore I = \frac{50}{0.55} = 90.9 \text{ A}$

& $P_x = VI \sin \theta = 200 \times 90.9 \sin -56.6^\circ$
 $= -15,177.5 \approx -15.2 \text{ KVAR}$

(b) Series elements for load: Leading pf \therefore capacitive

$$R = \frac{P}{I^2} = \frac{10^4 \text{ W}}{(90.9)^2 \text{ A}^2} = 1.21 \Omega$$



$$X_c = \frac{-15.2 \times 10^3}{(90.9)^2} = -1.84 \Omega = -\frac{1}{\omega C} \quad \therefore C = \frac{1}{1.84 \times 2\pi \times 60} = 1.44 \text{ mF}$$

(c) Parallel elements for load:

$$P = V^2/R \quad R = \frac{V^2}{P} = \frac{200^2}{10^4} = 4 \Omega$$

$$X_c = V^2/P_x = 200^2 / (-15.2 \times 10^3) = -2.63 \Omega$$
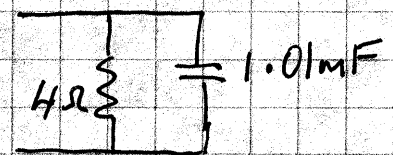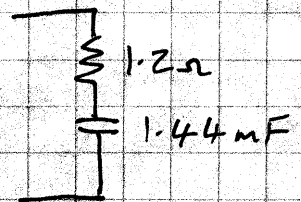
$$\text{so } C = \frac{1}{2.63 \times 2\pi \times 60} = 1.008 \text{ mF}$$



P 7.9 Load: 100 KVA at 0.7 pf lagging
20 KW at 0 pf

Lagging pf \rightarrow inductive load $\cos \theta = 0.7 \rightarrow \theta = 45.6^\circ$

$$P = VI \cos \theta = 100(0.7) = 70 \text{ KW}$$


$$P_x = VI \sin \theta = 100 \sin 45.6^\circ = 71.4 \text{ KVARs}$$

\therefore Apparent power

$$P_A = \left[(P_x)_{\text{tot}}^2 + P_{\text{tot}}^2 \right]^{1/2}$$

$$= \left[71.4^2 + (70+20)^2 \right]^{1/2}$$

$$= 114.88 \text{ KVA}$$

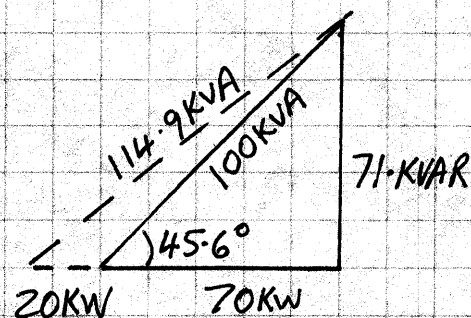


P 7.10 Specify reactive KVA for capacitor to correct pf of plant above (in P 7.9) to 0.85 lagging.

$$\theta = \cos^{-1} 0.85 = 31.79^\circ$$

$$\therefore \text{New } P_x' = 90 \tan 31.79^\circ = 55.78 \text{ KVARs}$$
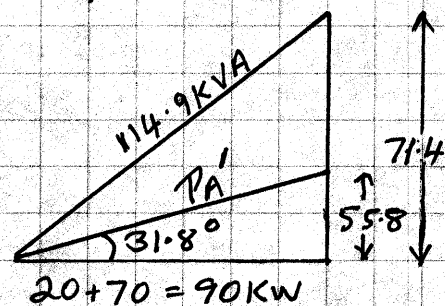
$$\therefore \text{New Apparent Power } P_A' = (90^2 + 55.8^2)^{1/2} = 105.9 \text{ KVA}$$



$$\& \text{ reactive KVARs of Capacitor} = 71.4 - 55.8 = 15.6 \text{ KVAR}$$

$$\frac{\text{New Power Loss}}{\text{Old Power Loss}} = \frac{I'^2 R}{I^2 R}$$

$$= \frac{(P_A'/V)^2}{(P_A/V)^2} = \left(\frac{P_A'}{P_A} \right)^2 = \left(\frac{105.9}{114.9} \right)^2 = 0.85$$