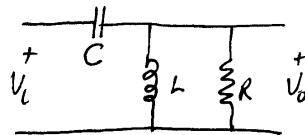


# ECE 241 ASSIGNMENT #6 MODEL ANSWERS

7.16



Input components  $\omega_1 = 10, \omega_2 = 100$   
 $\omega_3 = 1000, \omega_4 = 10,000$  rad/s

$$\begin{aligned}
 (a) \frac{V_o}{V_i} &= \frac{R//j\omega L}{R/j\omega L + j/\omega C} = \frac{j\omega L R}{j\omega L + R} = \frac{j\omega L R w C}{j\omega L R w C - j(Rj\omega L)} \\
 &= \frac{\omega^2 L R C}{\omega^2 L R C - R - j\omega L} = \frac{-\omega^2 R L C}{R(1 - \omega^2 L C) + j\omega L} \\
 \text{OR} \quad &= \frac{\omega^2 R L C}{[R^2(1 - \omega^2 L C)^2 + (\omega L)^2]^{1/2}} \tan^{-1} \frac{\omega L}{R(1 - \omega^2 L C)}
 \end{aligned}$$

(b) For  $C = 10\mu F, L = 1H, R = 20k\Omega$


$$\left| \frac{V_o}{V_i} \right| = \frac{20 \times 10^3 \times 1 \times 10 \times 10^{-6} \omega^2}{[(2 \times 10^4)^2 (1 - \omega^2 10^{-5})^2 + (\omega)^2]^{1/2}} = \frac{0.2 \omega^2}{\sqrt{(2 \times 10^4 - 0.2 \omega^2)^2 + \omega^2}}$$

$$\omega = \quad 10 \quad 100 \quad 1000 \quad 10,000$$

$$\begin{aligned}
 \left| \frac{V_o}{V_i} \right| &= \frac{20}{\sqrt{(2 \times 10^4 - 20)^2 + 100}} \quad \frac{2 \times 10^3}{\sqrt{(2 \times 10^4 - 2 \times 10^3)^2 + 10^4}} \quad \frac{2 \times 10^5}{\sqrt{(2 \times 10^4 - 2 \times 10^5)^2 + 10^6}} \quad \frac{2 \times 10^7}{\sqrt{(2 \times 10^4 - 2 \times 10^7)^2 + 10^8}} \\
 &\approx \frac{20}{2 \times 10^4} \quad = \frac{2 \times 10^3}{\sqrt{3.24 \times 10^4 + 10^4}} \quad \frac{2 \times 10^5}{\sqrt{3.24 \times 10^10 + 10^6}} \quad \frac{2 \times 10^7}{\sqrt{4 \times 10^{14}}} \\
 &= .001 \quad \approx .111 \quad \approx 1.011 \quad \approx 1
 \end{aligned}$$

$\therefore$  High pass filter.

7.28

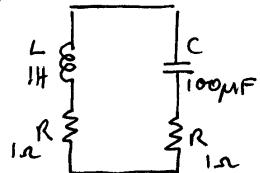

$$(a) Z = \frac{(R - j\frac{1}{\omega C})(R + j\omega L)}{R - j\omega C + R + j\omega L} = \frac{\left(R^2 + \frac{1}{C}\right) + j(\omega L - \frac{1}{\omega C})R}{2R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{[(R^2 + \frac{1}{C}) + jR(\omega L - \frac{1}{\omega C})][2R - j(\omega L - \frac{1}{\omega C})]}{4R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Resonance when  
Z purely real,  
i.e. when

$$\left. \begin{aligned} &= [2R(R^2 + \frac{1}{C}) + (\omega L - \frac{1}{\omega C})^2 R] \\ &\quad + j[2R^2(\omega L - \frac{1}{\omega C}) - (\omega L - \frac{1}{\omega C})] \end{aligned} \right\} \text{den}$$

$$(\omega L - \frac{1}{\omega C})(R^2 - \frac{1}{\omega C}) = 0 \quad \text{so} \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{1 \times 10^{-4}} \quad \therefore \omega_0 = 100 \text{ rad/s}$$

$$(b) Q_L = \frac{\omega L}{R} = \frac{\omega_0 L}{R} \text{ at resonance} = \frac{100 \times 1}{1} = 100$$

$$\text{Similarly } Q_C = \frac{1}{\omega RC} = \frac{1}{\omega_0 RC} \text{ at resonance} = \frac{1}{100 \times 1 \times 10^{-4}} = 100$$

$$\text{Complete circuit } Q_c = \frac{\omega_0 L}{2R} = 50$$

$$(c) \text{ For } V = 20V \text{ rms at } \omega_0 \quad Z = R \frac{(2(R^2 + \frac{1}{C}) + (\omega_0 L - \frac{1}{\omega_0 C})^2)}{4R^2 + (\omega_0 L - \frac{1}{\omega_0 C})^2}$$

$$= \frac{2R(R^2 + \frac{1}{C})}{4R^2} = \frac{1}{2}(R + \frac{1}{RC})$$


$$= \frac{1}{2}(1 + \frac{1}{10^4}) = 5,000.5 \approx Z_0$$

$$I \approx \frac{V}{Z_0} = \frac{20}{5000} = 4 \mu A$$

$$I_L = \frac{V}{R + j\omega L} = \frac{20}{1 + j100} \approx \frac{20 \angle 0^\circ}{100 \angle -89.4^\circ} = 0.2 \angle -89.4^\circ = 200 \mu A \angle -89.4^\circ$$

$$I_C = \frac{V}{R - j\omega_0 C} = \frac{20}{1 - j100} \approx \frac{20 \angle 0^\circ}{100 \angle 89.4^\circ} = 0.2 \angle 89.4^\circ = 200 \mu A \angle 89.4^\circ$$

7.33

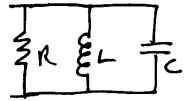


$$Z_0 = 50,000 \Omega = R$$

$$\omega_0 = \frac{1}{\sqrt{RC}} = 2\pi \times 2 \times 10^6$$

$$Q_p = \omega_0 R C = 80 \quad \therefore C = \frac{80}{5 \times 10^4 \times 2\pi \times 2 \times 10^6} = 127.3 \mu F$$

$$\therefore L = \frac{1}{\omega_0^2 C} = \frac{\omega_0 R}{\omega_0^2 \cdot 80} = \frac{R}{\omega_0 Q_p} = \frac{5 \times 10^4}{2\pi \times 2 \times 10^6 \times 80} = 49.7 \mu H$$

8.19

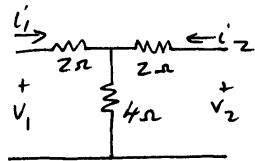

$$* V_1 = 2i_1 + 4(i_1 + i_2) = 6i_1 + 4i_2$$

$$* V_2 = 2i_2 + 4(i_1 + i_2) = 4i_1 + 6i_2$$


$$\text{So } \begin{cases} 3V_2 = 12i_1 + 18i_2 \\ 2V_1 = 12i_1 + 8i_2 \end{cases} \quad \begin{cases} 3V_2 - 2V_1 = 10i_2 \\ 3V_1 - 2V_2 = 10i_1 \end{cases}$$

$$\begin{cases} 3V_1 = 18i_1 + 12i_2 \\ 2V_2 = 8i_1 + 12i_2 \end{cases} \quad \begin{cases} 3V_1 - 2V_2 = 10i_1 \\ 3V_2 - 2V_1 = 10i_2 \end{cases}$$



$$\begin{cases} i_1 = 0.3V_1 - 0.2V_2 \\ i_2 = -0.2V_1 + 0.3V_2 \end{cases} \quad \therefore \begin{cases} k_5 = 0.3S & k_6 = -0.2S \\ k_7 = -0.2S & k_8 = 0.3S \end{cases}$$

$$\therefore Y_{11} = 0.3S \quad Y_{12} = -0.2S$$


$$Y_{21} = -0.2S \quad Y_{22} = 0.3S$$

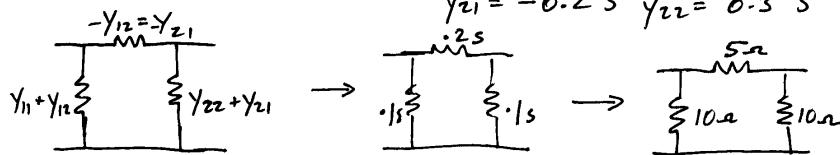

8.23

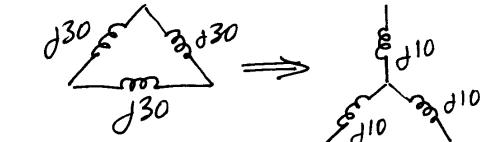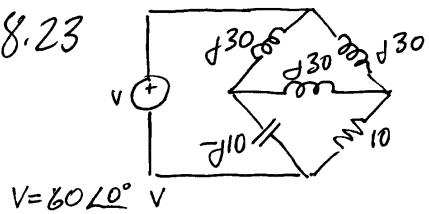

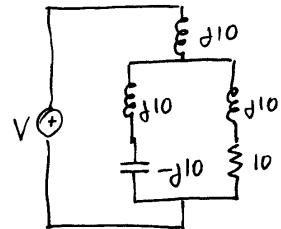
$$\text{From Example 4 } Z_Y = \frac{1}{3} Z_\Delta$$



$$I = \frac{V}{j10 + 0 \parallel 10(j+j)} = \frac{60}{j10} = 6 \angle -90^\circ$$

L-C arm is SC  $\therefore$  no current in the resistor.  $I_R = 0$

8.30

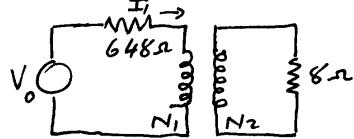


(a) Max power transfer

$$648 = \left(\frac{N_1}{N_2}\right)^2 8 \Omega \quad \frac{N_1}{N_2} = \sqrt{\frac{648}{8}} = 9$$

$$(b) V_o = 36V \quad I_1 = \frac{V_o}{2+648\Omega} = \frac{36}{2+648} \quad \therefore \text{Total power consumption}$$

$$P = \frac{(36)^2}{2+648} = 1W$$

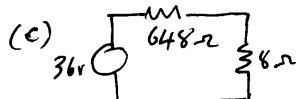$\frac{1}{2}$  power in load ( $8\Omega$ ) and  $\frac{1}{2}$  in  $648\Omega$   
 $\therefore P_{LX} = \frac{1}{2} W$




$$P_{LS} = I^2 R = \left(\frac{36}{648+8}\right)^2 8 = 24mW$$

$$\therefore \frac{P_{LX}}{P_{LS}} = \frac{1/2W}{0.024W} = 20.83$$

series  $\rightarrow$  transformer

AP 8.7

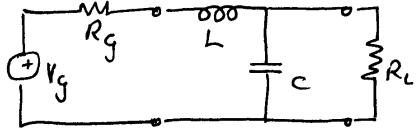

$$R_g = 500 \Omega$$

$$R_L = 5000 \Omega$$

Find  $L, C$  for max power transfer at  $\omega = 10^4 \text{ rad/s}$

$$\text{Need } Z_{RC} = 500 - jX_1 = R_L \parallel -jX_C = \frac{-jX_C R_L}{R_L - jX_C} = \frac{R_L X_C^2 - j R_L^2 X_C}{R_L^2 + X_C^2}$$

$$\therefore \frac{R_L X_C^2}{R_L^2 + X_C^2} = 500 \rightarrow 5000 X_C^2 = (5000^2 + X_C^2) 500 \\ 4500 X_C^2 = 5000^2 \rightarrow X_C = 5000 \sqrt{\frac{500}{4500}} = \frac{5000}{\sqrt{3}} = 1.67 \text{ kA}$$

$$\therefore C = \frac{1}{\omega X_C} = \frac{3}{5000 \times 10^4} = 0.06 \mu\text{F}$$

$$\text{Now need } X_L = X_1 = \frac{R_L^2 X_C}{R_L^2 + X_C^2} = \frac{(5000)^2 5000/3}{(5000)^2 + (\frac{5000}{3})^2} \\ = \frac{(5000)^2 5000 \times 3}{(5000)^2 (9+1)} = 1500 \Omega$$

$$\therefore L = \frac{X_L}{\omega} = \frac{1500}{10^4} = 150 \text{ mH}$$