

ECE 241 Assignment #8 Model Answers

21.5 Inductance coil: N turns High permeability core with air gap
 of area A length l_i length l_a

(a) Derive approx inductance:
 "High permeability core" \rightarrow assume R_{core} is negligible

$$\therefore \mathcal{F} \approx \frac{B}{\mu_a} l_a = NI \text{ gives } B = \mu_0 \frac{NI}{l_a}$$

$$\& L = N\phi/I = NBA/I = \frac{\mu_0 N^2 I A}{I l_a} = \mu_0 \frac{N^2 A}{l_a}$$

(b) $N=500$ $A=2\text{cm}^2$ $l_i=10\text{cm}$ $l_a=2\text{mm}$ $I=10\text{mA}$

$$\therefore L = 4\pi \times 10^{-7} \times (500)^2 \times 2 \times 10^{-4} / 2 \times 10^{-3} = 31.4 \mu\text{H}$$

(c) Cast steel core, $I=4\text{A}$ $H=NI/l \rightarrow \frac{500 \times 4}{10 \times 10^{-2}}$ for cast steel
 $= 20,000$ of all mmf dropped in steel.

Extrapolating from Fig 20.16, $B \sim 1.3\text{T}$ and core is saturated
 i.e. $\frac{\Delta B}{\Delta H} \sim \mu_0$

$$\text{For air gap, mmf} = H_a l_a = \frac{B}{\mu_0} 2 \times 10^{-3} \rightarrow \frac{1.3 \times 2 \times 10^{-3}}{4\pi \times 10^{-7}} = 2.07 \times 10^3 \text{ A.t}$$

$$\text{For core mmf} = H_i l_i = 2 \times 10^4 \cdot 10 \times 10^{-2} = 2 \times 10^3 \text{ A.t}$$

i.e. comparable.

$$\text{So } \mathcal{F} = NI = \phi R = \phi \left(\frac{1}{\mu_0} \frac{l_a}{A} + \frac{1}{\mu_{\text{eff}}} \frac{l_i}{A} \right) = \frac{\phi}{A} (\quad)$$

$$\& L = N\phi/I = \frac{N NI}{I \left(\frac{1}{\mu_0} \frac{l_a}{A} + \frac{H_i l_i}{B_i A} \right)} = \frac{N^2 A}{\left(\frac{l_a}{\mu_0} + l_i \frac{H_i}{B_i} \right)}$$


using $\mu_{\text{eff}} = \frac{B_i}{H_i}$ from above.

$$= \frac{500^2 \cdot 2 \times 10^{-4}}{\frac{2 \times 10^{-3}}{4\pi \times 10^{-7}} + 10^{-1} \frac{2 \times 10^4}{1.3}} = \frac{50}{1592 + 1200}$$

$$\approx 17.9 \mu\text{H}$$

This suggests $\sim 1/2$ mmf dropped in the iron, so $H \sim 1/2$ estimated value, B same,
 i.e. $\mu_{\text{eff}} \sim 2$ value used. If more accurate would give a better value OR linear...

21.16

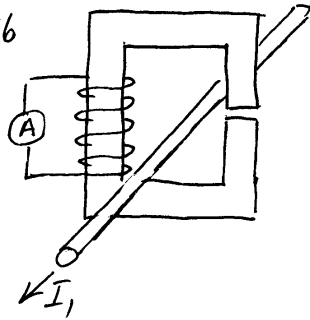

Single turn primary of the transformer
For negligible flux linkage

$$I_{\text{conductor}} = I_N = \left(\frac{N_2}{N_1} \right) I = 20 \times 1.5 = 30 \text{ A}$$

21.35. Transformer: 30 KVA 12,000:4,000
OC test: 4000 V, 1.1 A, 2000 W
SC test: 300 V, 25 A, 2800 W

(d) $V_{oc} = 4000 \text{ V}$, $V_{oc} = V_{LV}$ and OC test done with low voltage side OC

$$I_{sc} = 25 \text{ A} = \frac{300 \text{ KVA}}{12,000 \text{ V}} = \frac{\# \text{ KVA}}{V_{HV}} \text{ and SC test done with high voltage side SC.}$$

(b) For R_L load $P_L = 300 \text{ kW} \rightarrow \eta_1 = \frac{P_L}{P_L + P_{cu} + P_{Fe}} = \frac{300 \text{ kW}}{300 \text{ kW} + 2 \text{ kW} + 2.8 \text{ kW}} = 98.4\%$

(c) For Z_L load 300 KVA, $\rho F = 0.6$ lagging $= \frac{300 \times 0.6}{300 \times 0.6 + 2 + 2.8} = 97.4\%$

(d) To find voltage regulation for part (c) above:
Need $\text{Regulation} = \frac{V_{\text{no load}} - V_{\text{full load}}}{V_{\text{full load}}}$

$$= \frac{V_1 - V_2/a}{V_2/a} \text{ for the model of Fig 2.18(b)}$$

where $\tilde{V}_1 = \tilde{V}_2/a + a \tilde{I}_2 \tilde{Z}_{E1}$ from Fig 2.18(b) and find R_{E1} , X_{E1}


(e) $a = 4000/12000 = 1/3$ $R_{E1} = \frac{P_{sc}}{I_{1s}^2} = \frac{2800}{(25)^2} = 4.48 \Omega$

$$Z_{E1} = V_{1s}/I_{1s} = \frac{300}{25} = 12 \Omega \text{ so } X_{E1} = (Z_{E1}^2 - R_{E1}^2)^{1/2} = (12^2 - 4.5^2)^{1/2} = 11.13 \Omega$$

300 KVA & 0.6 pF lagging $\therefore a \tilde{I}_2 = I_{1sc} (0.6 - j0.8) = 25(0.6 - j0.8)$

$$\tilde{V}_1 = \tilde{V}_2/a + \tilde{I}_2 \tilde{Z}_{E1} = 12,000 + (15 - j20)(4.48 + j11.13) = 12,289 \angle 0.36^\circ \text{ V}$$

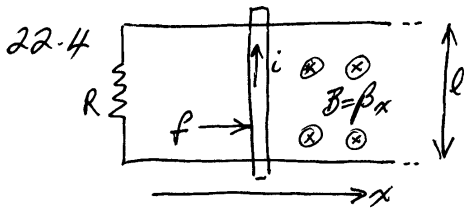$\therefore \text{Voltage Regulation} = (12,289 - 12,000)/12,000 = 2.4\%$




For bar, velocity = u
position $x = ut$

$$(a) e(t) = \frac{d\lambda}{dt} = Blu$$


$$\therefore i(t) = \frac{e(t)}{R} = \frac{Blu}{R} = \frac{(\beta x)lu}{R} = \frac{B(ut)lu}{R} = \frac{\beta u^2 l t}{R} \text{ A}$$
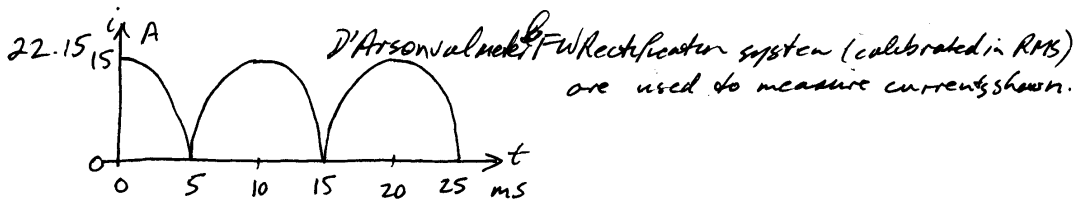
$$(b) f(t) = f_d = Bli = (\beta x) l i(t) = \beta (ut) l \frac{\beta u^2 l t}{R} = \frac{\beta^2 u^3 l^2 t^2}{R} \text{ N}$$



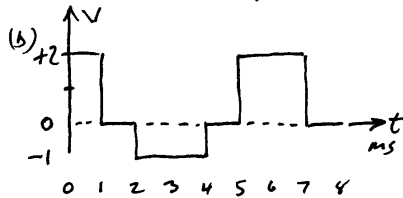(a) D'Arsonval meter reads $I_{AV} = 2 I_{PK} / \pi = 2 \times 15 / \pi = 9.55 \text{ A}$

Rectification system reads $I_{RMS} = 1.11 I_{AV} = 1.11 \times 9.55 = 10.6 \text{ A}$




D'Arsonval: $V_{AV} = \frac{2 \times 1 - 1 \times 2 + 2 \times 2}{8} = 0.5 \text{ V}$

(note: Interpretation of where the cycle ends — possibly 6 ms period
 $V_{AV} \rightarrow 2/6 = 1/3 \text{ V}$)

For rectification instrument $V_{RMS} = 1.11 V_{AV} = 1.11 \left(\frac{2 \times 1 + 1 \times 2 + 2 \times 2}{8} \right) = 1.11 \text{ V}$

(Note formula on page 731.)

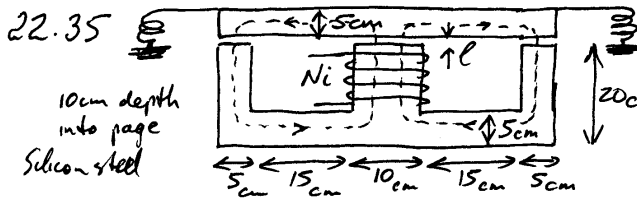

(a) Find N_i for 60 N force on bar at $l = 1$ cm. Consider 2 fluxes in parallel:

$$\begin{aligned} \text{Gap area} &= 10 \times 5 \times 10^{-4} \\ \text{for each} &= 5 \times 10^{-3} \text{ m}^2 \\ \text{Total area} &= 4 \times 5 \times 10^{-3} = 2 \times 10^{-2} \text{ m}^2 \end{aligned}$$

$$f = \frac{B^2 A}{2\mu_0} \quad (\text{eqn 22.40}) \rightarrow B = \sqrt{\frac{2f\mu_0}{A_{\text{tot}}}} = \sqrt{\frac{2 \times 60 \times 4\pi \times 10^{-7}}{2 \times 10^{-2}}} = (75.4 \times 10^{-6})^{1/2} = 8.7 \times 10^{-3} \text{ Wb/m}^2$$

assuming $\mu_{\text{air}} \gg \mu_{\text{iron}}$

Fig 20.16 $\rightarrow B = 8.7 \text{ mWb/m}^2$
 $H \approx \frac{8.7 \times 10^{-3} \times 50}{0.37} \text{ A.t./m} = 1.18 \text{ A.t./m}$

$$l_i = 2 \times (20 + 20) \times 10^{-2} \text{ for each loop} \quad \therefore F_i = H_i \cdot l_i = 0.8 \times 1.18 = 0.944 \text{ A.t.}$$

$$\& F_a = H_a l_a = \frac{B}{\mu_0} l_a = \frac{8.7 \times 10^{-3} \times 2 \times 10^{-2}}{4\pi \times 10^{-7}} = 136.5 \text{ A.t.}$$

is. 1.89 A.t. total.


$$\therefore N_i = (136.5 + 1.9) \text{ A.t. / Loop}$$

is. = $2 \times 140.4 \text{ A.t.} = 288.8 \text{ A.t. total.}$

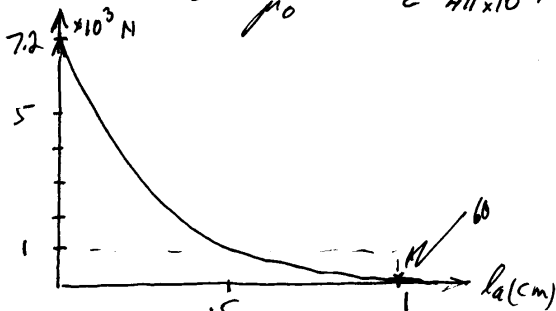(b) If $l_a \rightarrow 0$ $H_i = \frac{N_i}{l_i} = \frac{140.4}{0.8} \text{ A.t./m} = 175.5 \text{ A.t./m}$ each loop.

is. Fig 20.16 $\rightarrow B_i = 0.95 \text{ T}$


$$f = \frac{1}{2} \frac{B_i^2 A}{\mu_0} = \frac{1}{2} \frac{.95^2}{4\pi \times 10^{-7}} \times 2 \times 10^{-2} \text{ total} = 7.2 \times 10^3 \text{ N}$$



$$f \propto B^2 \propto \frac{1}{l_a^2}$$

for $l_a \gg \frac{\mu_0 N_i^2}{m}$

7.36

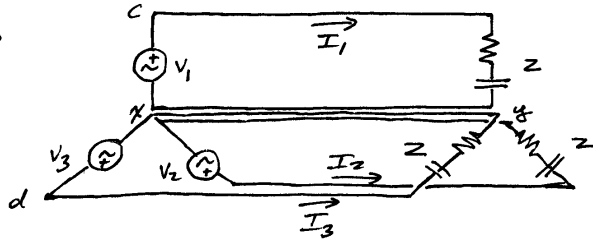

$$V_1 = 240 \angle 90^\circ \text{ V}$$

$$V_2 = 240 \angle -30^\circ \text{ V}$$

$$V_3 = 240 \angle -150^\circ \text{ V}$$

$$Z = 40 \angle -30^\circ \Omega$$

(a) I_1, I_2, I_3

$$I_1 = \frac{240 \angle 90^\circ}{40 \angle -30^\circ} = 6 \angle 120^\circ \text{ Similarly } I_2 = 6 \angle 0^\circ$$


$$I_3 = 6 \angle -120^\circ$$

(b) For x's, y's connected

$$I_{yx} = I_1 + I_2 + I_3$$

$$= 6 \angle 120^\circ + 6 \angle 0^\circ + 6 \angle -120^\circ$$

Graphically

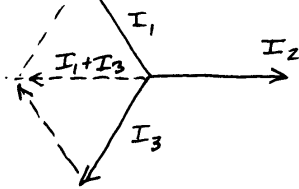

$$I_1 + I_2 = -I_3 \text{ or}$$

$$= 6 \cos 120^\circ + j 6 \sin 120^\circ$$

$$+ 6$$

$$+ 6 \cos -120^\circ + j 6 \sin -120^\circ$$

$$= \left(-\frac{6}{2} + j \frac{6\sqrt{3}}{2}\right) + 6 + \left(-\frac{6}{2} - j \frac{6\sqrt{3}}{2}\right)$$


$$= 0$$

(c) For x,x,x and y,y,y connected

$$\vec{V}_{cd} = \vec{V}_1 - \vec{V}_3 = 240 \angle 90^\circ - 240 \angle -150^\circ$$

$$= 240 \angle 90^\circ + 240 \angle 30^\circ$$

(d)

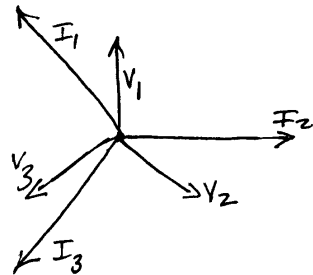


$$= 240 \times 0 + j 240 \times 1 + 240 \frac{\sqrt{3}}{2} + j 240 \frac{1}{2}$$

$$= 240 \frac{\sqrt{3}}{2} + j 240 \frac{3}{2}$$

$$= \frac{240}{2} (\sqrt{3}^2 + 3^2)^{1/2} \arctan \frac{3/2}{\sqrt{3}/2}$$

$$= 240 \sqrt{3} \angle 60^\circ = 416 \angle 60^\circ \text{ V}$$


7.40

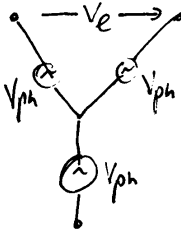

$$V_{line} = \sqrt{3} V_{phase}$$

$$\therefore V_{phase} = \frac{V_{line}}{\sqrt{3}} = \frac{208}{\sqrt{3}}$$

$$= 120.09 \text{ V}$$

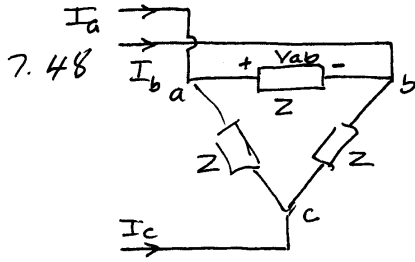

$$|V_{ab}| = 300V \quad Z \rightarrow \text{Capacitive Loads}$$

$$|I_a| = 20A$$

$$|V_{ab} \cdot I_a| = 4240W$$

Find \vec{Z} , sketch phasors

$$V_{ab} = 300 \angle 0^\circ \text{ (reference)}$$

$$I_a = 20 \angle \theta$$

$$4240 = V_{ab} I_a \cos \theta = 300 \times 20 \times \cos \theta \therefore \cos \theta = \frac{4240}{6000} = 0.707$$

$$= \frac{1}{\sqrt{2}} \therefore \theta = \pm 45^\circ$$

Phase current: Phase θ as shown for capacitive load.

$$\therefore I_a = I_{ab} + I_{ac}$$

$$= I_{ab} - I_{ca}$$

as shown

$$I_{ab} \text{ phase} = I_a \text{ phase} + 30^\circ \text{ (Eq. 7.56)}$$

$$\therefore I_a \text{ phase} = \pm 45^\circ - 30^\circ > 0 \text{ for Capacitive Load}$$

$$\therefore I_a = 20 \angle 45^\circ$$

$$I_{ab} = \frac{I_a \angle 30^\circ}{\sqrt{3}} = \frac{20}{\sqrt{3}} \angle 30^\circ + 45^\circ = 11.5 \angle 75^\circ A$$

$$\vec{Z} = \frac{\vec{V}_{ab}}{\vec{I}_{ab}} = \frac{300 \angle 0^\circ}{11.5 \angle 75^\circ} \approx 26 \angle -75^\circ$$

