
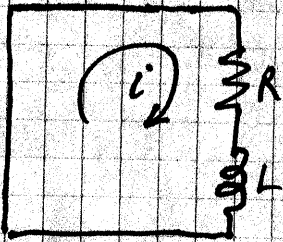


# FCE241 Lecture 10 TRANSIENTS II


(Chapter 6: Complete Response)

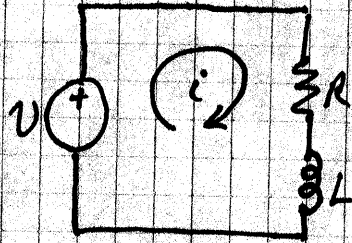

(a) Natural response (Chapter 4)



(b) Forced response (Chapter 5)

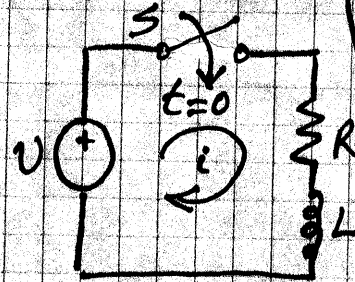

(c) Complete response (Chapter 6)

Remember (a) exponential decay from initial condition — time constant  $L/R$

(b) follows  $e^{-t/\tau}$  for exponential forcing function.


Natural response  $\rightarrow$  initially stored energy dissipates

Forced response  $\rightarrow$  energy continually supplied

Complete response  $\rightarrow$  combination:

Initial transient  $\rightarrow$  steady state

Example:

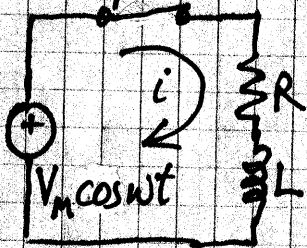

$$L \frac{di}{dt} + Ri = V_m \cos \omega t$$

Any  $i$  which satisfies eq<sup>n</sup> is a possible solution

eg.  $i_f = I_m (\cos \omega t + \phi)$  is the forced response

(see back)

where  $I_m, \phi$  found from  $\bar{Z}$

Also, natural response:  $i_n = I_n e^{-(R/L)t}$

is a solution of  $L \frac{di}{dt} + Ri = 0$

So  $i = i_f + i_n = I_m \cos(\omega t + \phi) + I_n e^{-(R/L)t}$   
is also a solution (since  $i_n$  makes LHS = 0)

$i_f \rightarrow$  "particular" solution  $i_n \rightarrow$  "complementary" solution

# PROCEDURE

Forced response :

Same "form" as forcing function  
(eg. sinusoid)

Amplitude : Forcing function  
amplitude  $\times Z$


$Z(0)$  for DC;  $Z(j\omega)$  for sinusoid

- ① Write impedance  $Z(s)$  or admittance  $Y(s)$  function for the appropriate terminals for desired :  
(open circuit) voltage, or (short circuit) current
- ② Determine forced response from forcing function and impedance or admittance ( $Z(s)$  or  $Y(s)$ ) as defined by forcing function.
- ③ Identify the natural response components from the poles or zeros of  $Z(s)$  or  $Y(s)$   
eg. for  $Z(s)$  : poles  $\rightarrow$  voltage  
zeros  $\rightarrow$  current
- ④ Add forced and natural responses, and find amplitudes from initial conditions


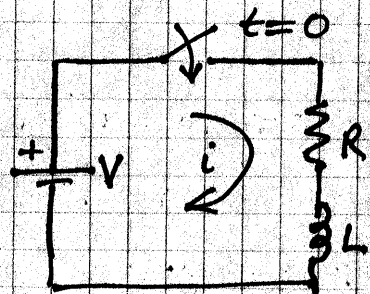
# A. FIRST ORDER CIRCUITS

① R-L step response  
(i.e. DC forcing function)



Step 1:  $Z(s) = R + sL$

Step 2: Forced response  $i_f = \frac{V}{R + sL} \xrightarrow[\text{DC}]{s=0} \frac{V}{R}$

Step 3: Natural components: Find current from zeros of  $Z(s)$   
i.e.  $R + sL = 0$  gives  $s = -R/L$   
 $\therefore i_n = A e^{-(R/L)t}$


Step 4: Evaluate undetermined constants

$$i = i_f + i_n = \frac{V}{R} + A e^{-(R/L)t}$$

At  $t = 0^+$   $i(0^+) = 0$  (since  $i(0) = 0$  &  $i$  can't change instantaneously.)

$$i(0) = 0 = \frac{V}{R} + A \quad \therefore A = -\frac{V}{R}$$

$$\& i = \frac{V}{R} (1 - e^{-(R/L)t})$$

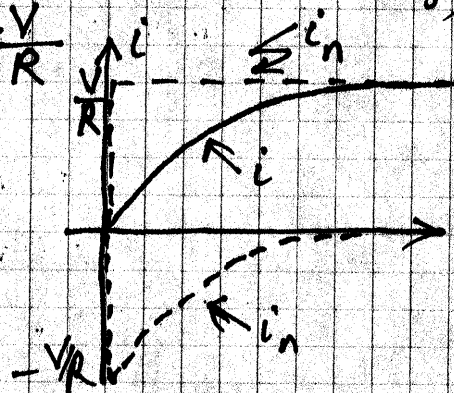

Exercise 6.1  $V = 5\text{V}$ ,  $R = 2\Omega$  above. Find  $\tau$  and sketch response

for  $L = 4\text{H}$ ,  $L = 0.4\text{H}$


$$\tau(4\text{H}) = 4\text{H}/2\Omega = 2\text{s}$$

$$\tau(0.4\text{H}) = 0.4/2 = 0.2\text{s}$$


Note  $L \frac{di}{dt} + Ri = V$

$$\therefore \frac{di}{dt} = \frac{V - Ri}{L} \quad \begin{matrix} t=0 \\ i=0 \\ \frac{V}{L} \end{matrix}$$

$$\begin{matrix} t \rightarrow \infty \\ i \rightarrow V/R \\ 0 \end{matrix}$$

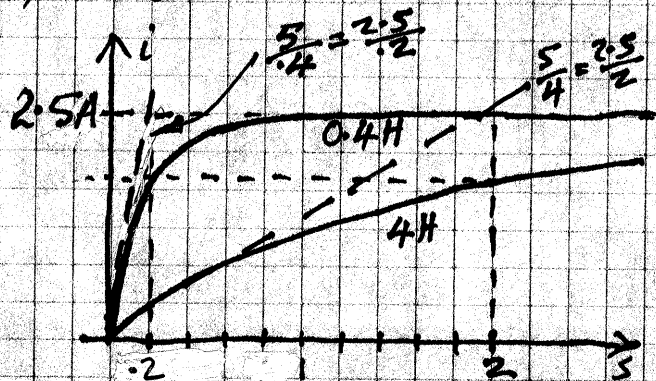

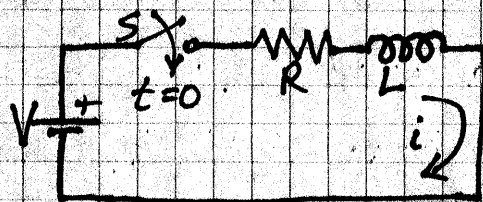Exercise 6.2. Find  $i(0)$ ,  $i(t)$ ,  $\frac{di}{dt}$  for  $t \geq 0$



This is the same circuit already solved,


$$\text{so } i(t) = \frac{V}{R}(1 - e^{-t/\tau})$$

where  $\tau = L/R$

$$i(0) = 0 \quad \text{and} \quad \frac{di}{dt} = 0 - \frac{V}{R}(e^{-t/\tau})\left(-\frac{1}{\tau}\right) = \frac{V}{R} \frac{R}{L} e^{-t/\tau} = \frac{V}{L} e^{-t/\tau}$$

② AC switching

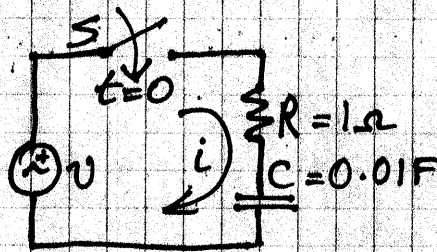eg. Exercise 6.3  $v = 10\sqrt{2} \cos 100t$  Find  $i_p$ ,  $i_n$



$$\textcircled{1} \quad Z(s) = R + 1/sC$$

② For sinusoidal forcing function

$$\begin{aligned} Z(j\omega) &= R - j\omega C \\ &= 1 - j \frac{1}{100(0.01)} = 1 - j \\ &= \sqrt{2} \arctan -1 = \sqrt{2} \angle -45^\circ \end{aligned}$$

$$\begin{aligned} \text{Hence } \vec{I} &= \frac{\vec{V}}{Z} = \frac{10}{\sqrt{2}} \frac{\angle 0^\circ}{\angle -45^\circ} \\ &= \frac{10}{\sqrt{2}} \angle 45^\circ \end{aligned}$$

$$\begin{aligned} \therefore i_p &= \frac{10}{\sqrt{2}} \sqrt{2} \cos(\omega t + 45^\circ) \\ &= 10 \cos(\omega t + 45^\circ) \text{ A} \end{aligned}$$

③ Zero of  $Z(s)$  to find natural current:  $R + \frac{1}{sC} = 0$

$$\begin{aligned} \text{at } s &= -1/RC \\ &= -\frac{1}{1(0.01)} = -100 \end{aligned}$$


$$\textcircled{4} \quad i = i_n + i_p = 10 \cos(\omega t + 45^\circ) + A e^{-100t}$$

$$\text{At } t=0 \quad i = \frac{v(0)}{R} = \frac{10\sqrt{2}}{1} = 10 \cos 45^\circ + A = \frac{10}{\sqrt{2}} + A$$

$$\therefore A = 10\sqrt{2} - \frac{10}{\sqrt{2}} = 14.14 - 7.07 = 7.07$$
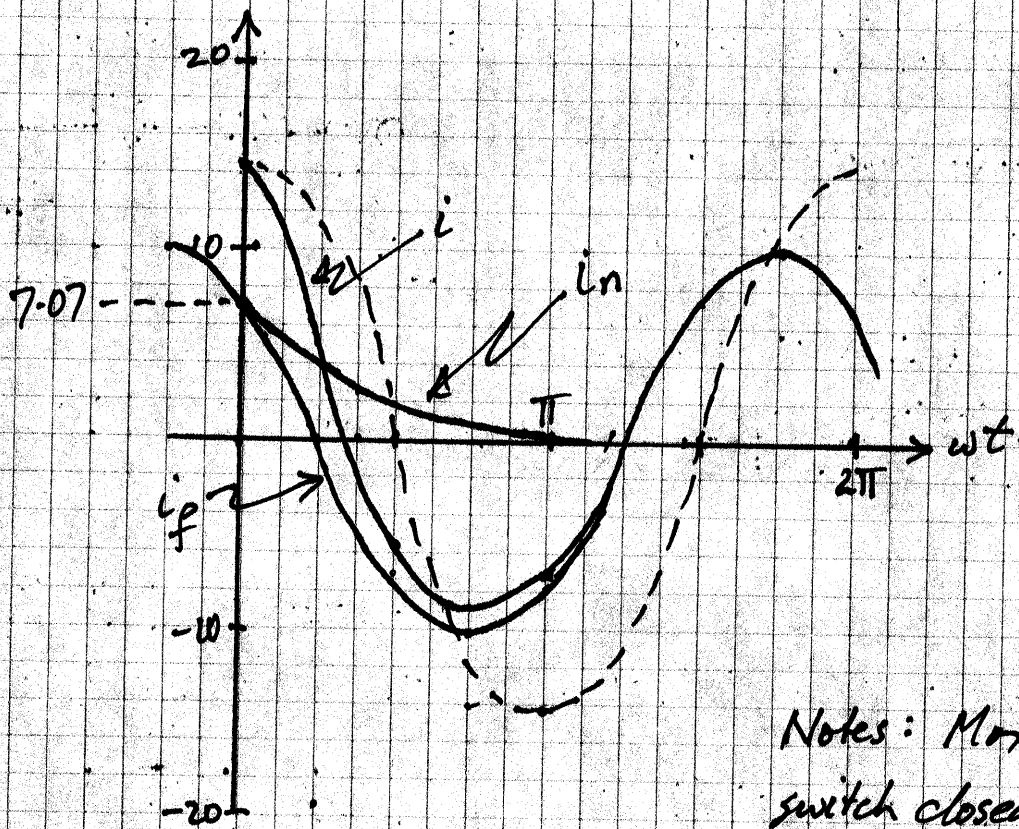
$$\text{So } i_n = 7.07 e^{-100t} \quad \text{and } i = 10 \cos(\omega t + 45^\circ) + 7.07 e^{-100t}$$





$$\omega t = 100t = 2\pi$$

When  $t = 62.84 \text{ ms}$

$$\omega t = \pi \text{ at } t = 31.84 \text{ ms}$$

$$T = 0.01 \text{ s} = 10 \text{ ms.}$$

Notes: Max transient current if switch closed at max  $v_{in}$


Also, no transient  $i_n$  if  $A=0$ , i.e. if switch closed at  $t=T$  such that  $10\sqrt{2} \cos 100T = 10 \cos(100T + 45^\circ)$

$$\cos 100T = \frac{1}{\sqrt{2}} (\cos 100T \cos 45^\circ - \sin 100T \sin 45^\circ)$$

$$= (\cos 100T - \sin 100T) / 2$$

i.e. when  $\sin 100T = -\cos 100T$   
 $\tan 100T = -1, 100T = -45^\circ$

### ③ Parallel Circuits

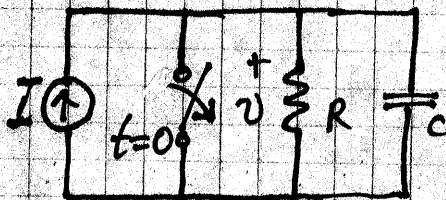

Employ duality or by inspection plus experience —

$$v_f = IR$$

$$v = IR(1 - e^{-t/RC})$$

$$\therefore v_n = -IR e^{-t/RC}$$


$$Y(s) = \frac{1}{R} + sC \quad v_f \text{ for dc, } Y(0) = 1/R : v_f = I/Y = IR$$

Zeros of  $Y(s)$  to find voltage  $\rightarrow s = -1/RC : v_n = A e^{-t/RC}$

At  $t=0^+ \quad IR + A e^{-t/RC} = 0 = IR + A \therefore A = -IR \text{ \& } v_n = -IR e^{-t/RC}$

$$\therefore v = IR(1 - e^{-t/RC})$$


### Exercise 6.4

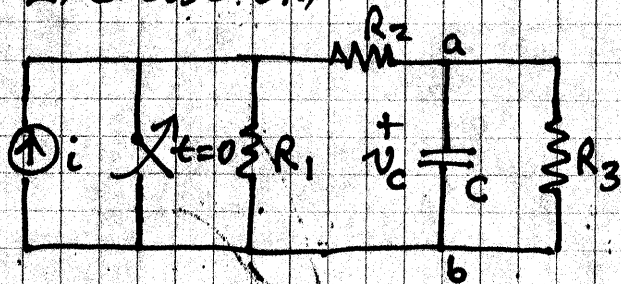

For  $v_c(t)$ :


Find natural response  $\tau$

Redraw:

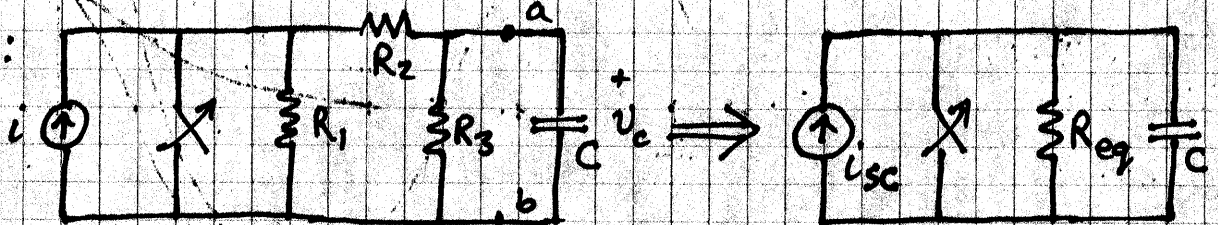

$$\tau = R_{eq} C \quad \text{where} \quad R_{eq} = R_3 \parallel (R_1 + R_2) \quad \therefore \tau = \frac{R_3(R_1 + R_2)C}{R_1 + R_2 + R_3}$$

&


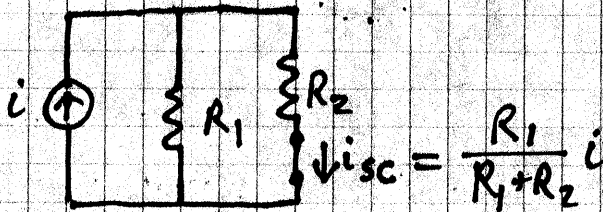


$$i_{sc} = \frac{R_1}{R_1 + R_2} i$$

Hence  $v_c(t) =$

$$\begin{aligned} & \frac{R_1}{R_1 + R_2} i R_{eq} (1 - \exp^{-t/\tau}) \\ & = \frac{R_1 R_3}{R_1 + R_2 + R_3} i (1 - \exp^{-t/\tau}) \end{aligned}$$

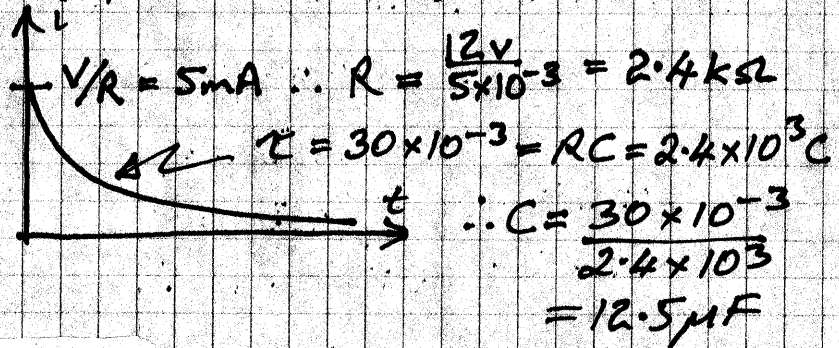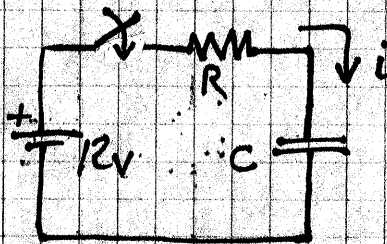
Exercise 6.5: Given 12V battery, design circuit for current in one element to jump to 5mA at  $t=0^+$  when switch closed, then decay exponentially with  $\tau=30\mu s$ .





## B. SECOND ORDER CIRCUITS

### ① Step Response

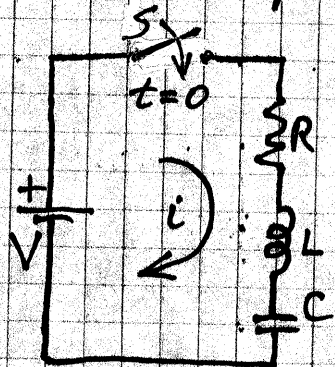

$$\textcircled{1} Z(s) = R + sL + \frac{1}{sC}$$

② Forced response

$$i_f = \frac{V}{Z(0)} \quad \text{since forcing function is DC } s=0$$

$$= \frac{V}{\infty} = 0$$

③ Natural response components from  $Z(s)=0$

$$s^2L + sR + \frac{1}{C} = 0$$

has roots  $s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm j\omega$

For roots real & distinct ( $R^2 > \frac{4L}{C}$ )  $i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

For roots real & equal ( $R^2 = \frac{4L}{C}$ )  $i_n = A_1 e^{s t} + A_2 t e^{s t}$

For roots complex ( $R^2 < \frac{4L}{C}$ )  $i_n = e^{-\alpha t} (\beta_1 \cos \omega t + \beta_2 \sin \omega t)$   
 $= A e^{-\alpha t} \sin(\omega t + \theta)$

④ In all cases, 2 constants need to be determined from initial cond.'s

For  $i(0) = 0 = i_n + i_f$  assuming as here  $i(0) = 0$


& assuming here  $v_C(0) = 0$  and  $v_R(0) = iR = 0$

then  $L \left. \frac{di}{dt} \right|_{t=0} = V$  i.e.  $\frac{di}{dt} = \frac{V}{L}$

i.e. 2 conditions from which to find the two constants.

(The details will vary for different cases.)

### Exercise 6.6 (See also Example 4)

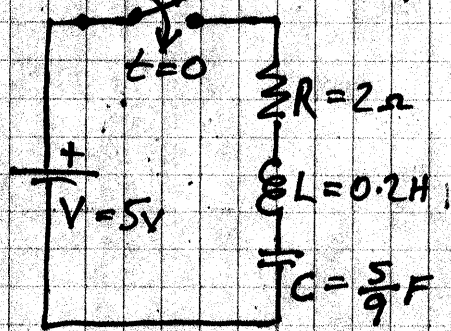

Find  $i$ ,  $v_L$ ,  $\frac{di}{dt}$  at  $t=0^+$

$$i(0^+) = 0$$

$$v_L(0^+) = 5V \quad \text{since } v_L(0) = 0 \text{ \& } Ri'(0) = 0$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{5V}{0.2H} = 25/s$$

From previous slide and for  $R^2 = 4 > \frac{4L}{C} = \frac{4 \times 0.2}{5/9} = 1.44$   
 i.e. real, distinct roots

$$i = 0 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad i(0) = A_1 + A_2 = 0$$

$$A_2 = -A_1$$

$$\left. \frac{di}{dt} \right|_{t=0} = s_1 A_1 + s_2 A_2 = 25$$

$$\begin{aligned} s_1, s_2 &= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\frac{2}{.4} \pm \sqrt{\left(\frac{2}{.4}\right)^2 - \frac{1}{2(5/9)}} \\ &= -5 \pm \sqrt{25 - 9} = -5 \pm \sqrt{16} = -5 \pm 4 \\ &= -9, -1 \end{aligned}$$


$$\therefore -9A_1 - A_2 = 25 \rightarrow -9A_1 + A_1 = 25, \quad A_1 = -25/8 \quad A_2 = +25/8$$

$$i(t) = \frac{25}{8} (e^{-t} - e^{-9t})$$



## ② AC Switching Transients (See Example 5 + Exercise 6.7)

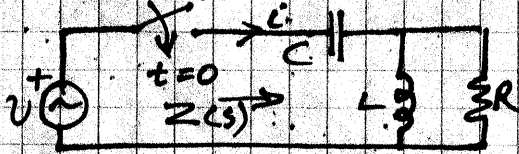Exercise 6.8  $R=1\Omega$   $C=1F$   $L=1H$   $v=\sqrt{20}\cos(t-149^\circ)V$



- (a) Find  $Z(s)$ ,  $i_p(t)$   
 (b) Find roots of  $Z(s)$  and complete response

Step ①  $Z(s) = \frac{1}{sC} + \frac{R \cdot sL}{R+sL} = \frac{(R+sL) + sRL \cdot sC}{sC(R+sL)}$   
 $= \frac{s^2 RLC + sL + R}{sC(R+sL)} = \frac{s^2 + s \frac{1}{RC} + \frac{1}{LC}}{s(s + R/L)}$   
 $= (s^2 + s + 1) / s(s+1)$

Step ② Forcing function  $i_f = \frac{V}{Z(s)}$  where  $s=j\omega$  for sinusoidal input  $v$   
 $= \frac{\sqrt{10} \angle -149^\circ}{Z(j\omega)}$  and  $\omega=1$

$Z(j\omega) = \frac{-\omega^2 + j\omega}{j\omega(j\omega + 1)} = \frac{-1^2 + 1 + j}{j(1+j)} = \frac{j}{-1+j} = j \frac{(-1-j)}{1+1}$   
 $= \frac{1}{2}(1-j) = \frac{1}{\sqrt{2}} \angle -45^\circ$   $\therefore i_f = \frac{\sqrt{10} \angle -149^\circ}{\frac{1}{\sqrt{2}} \angle -45^\circ} = \sqrt{20} \angle -104^\circ$

$\therefore i_f = \sqrt{2} \sqrt{20} \cos(t - 104^\circ) = 2\sqrt{10} \cos(t - 104^\circ)$  (Book answer incorrect)

Step ③ Zeros of  $Z(s)$  for current:  $Z(s) = s^2 + s + 1$


$s_1, s_2 = -\frac{1}{2} \pm \sqrt{(\frac{1}{2})^2 - 1} = -\frac{1}{2} \pm j\sqrt{3/4}$   
 $= -\frac{1}{2} (1 \pm j\sqrt{3}) = -\alpha \pm j\omega$

$\therefore i_n = A e^{-t/2} \sin(\frac{\sqrt{3}}{2}t + \theta)$

Step ④ Initial conditions  $i'(0) = 2\sqrt{10} \cos(-104^\circ) + A \sin \theta$   
 $= \frac{v(0)}{R} = \frac{\sqrt{20} \cos(-149^\circ)}{1}$

$\therefore A \sin \theta = \sqrt{20} \cos(-149^\circ) - 2\sqrt{10} \cos(-104^\circ) = -5.36$

Also at  $t=0^+$

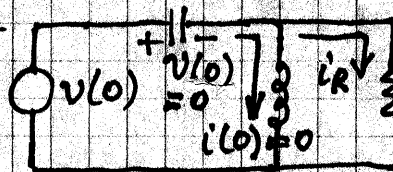


$v(0) = L \left. \frac{di_L}{dt} \right|_{t=0} = L \left. \frac{di}{dt} \right|_{t=0}$


$\left. \frac{di}{dt} \right|_{t=0} = -2\sqrt{10} \sin(-104^\circ) + A [\cos \theta + \sin \theta (-1/2)]$

$\therefore A \cos \theta = 2\sqrt{10} [\cos(-104^\circ) + \sin(-104^\circ)] + \frac{1}{2} A \sin \theta = -10.345$  Hence  $A, \theta$ .

# PULSE/IMPULSE RESPONSES

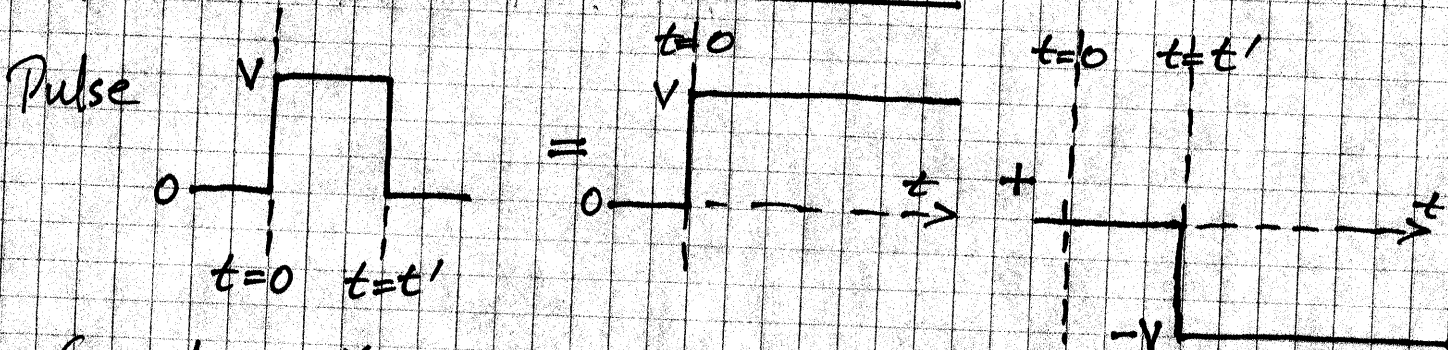

Consider as the response to 2 steps

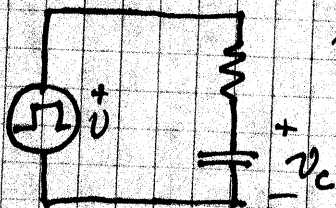

$$v_c = V(1 - e^{-t/RC})$$


$$\text{and } v_c = V(1 - e^{-t/RC}) - V(1 - e^{-(t-t')/RC})$$

$$0 < t < t'$$

$$t' < t$$

Impulse :

Current pulse  $I_0 T_p = Q_0$

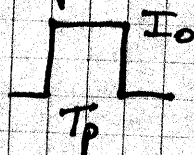


$$\text{Impulse } \left. \begin{matrix} T_p \rightarrow 0 \\ I_0 \rightarrow \infty \end{matrix} \right\} I_0 T_p = Q_0$$

$$M_p = \int i dt \text{ for arbitrary shape} = CV$$

$$M_p = \int v dt = LI$$

where  $M_p$  is impulse "magnitude." Similarly :

Exercise 6.12

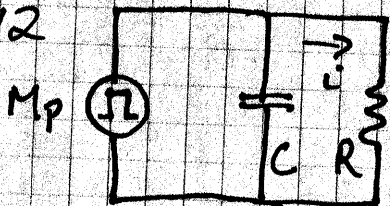

$M_p$  A.s at  $t=0$

Find  $M_p$  to establish current

$$i_R(t) = I_0 e^{-at}$$

Impulse charges capacitor with infinite current zero time

$$M_p = CV_0 = C(I_0 R)$$