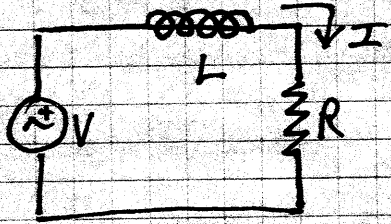


ECE241 LECTURE 12

FREQUENCY RESPONSE




$$I(\omega) = \frac{\bar{V}}{\bar{Z}} = \frac{\bar{V}}{R + j\omega L} = \frac{\bar{V}/R}{1 + j\omega \frac{L}{R}} \xrightarrow[\omega=0]{\text{DC}} \bar{I}_0 = \bar{V}/R$$

$$\begin{aligned} \frac{\bar{I}}{\bar{I}_0} &= \frac{1}{1 + j\omega \frac{L}{R}} = \frac{1 - j\omega \frac{L}{R}}{1 + (\omega \frac{L}{R})^2} = \frac{[1 + (\omega \frac{L}{R})^2]^{-1/2}}{1 + (\omega \frac{L}{R})^2} \angle \arctan -\frac{\omega L}{R} \\ &= \frac{1}{\sqrt{1 + (\omega \frac{L}{R})^2}} \angle \arctan -\frac{\omega L}{R} = \frac{\bar{I}}{\bar{I}_0} \angle \theta \end{aligned}$$


At $\omega_c = R/L$

$$\frac{\bar{I}}{\bar{I}_0} = \frac{1}{\sqrt{2}} \angle \arctan -1 = 0.707 \angle -45^\circ$$

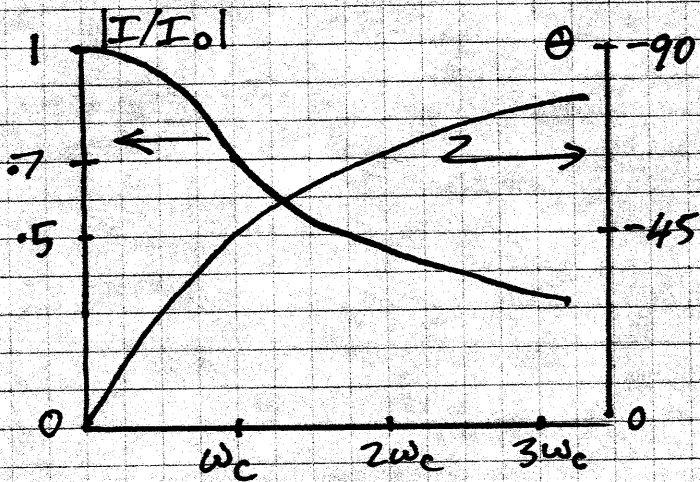$I^2 R = \frac{1}{2} I_0^2 R$ i.e. this is the "half-power" freq




Low pass filter

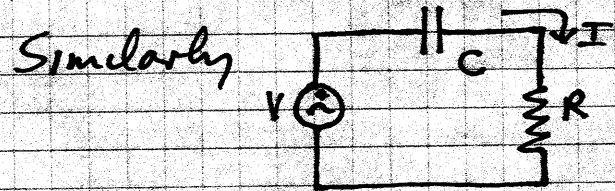


$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{\bar{V}}{R - j/\omega C} = \frac{\bar{V}/R}{1 - \frac{j}{\omega RC}} \xrightarrow[\omega \rightarrow \infty]{\text{HF}} \bar{I}_\infty = \frac{\bar{V}}{R}$$

$$\frac{\bar{I}}{\bar{I}_0} = \frac{1}{1 - j/\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle \arctan 1/\omega RC$$

At $\omega_c = 1/RC$ $\left| \frac{\bar{I}}{\bar{I}_0} \right| \rightarrow \frac{1}{\sqrt{2}}$

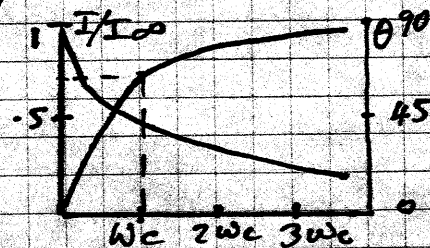


L-SECTION FILTERS

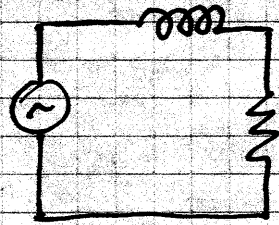


Low Pass Filter.

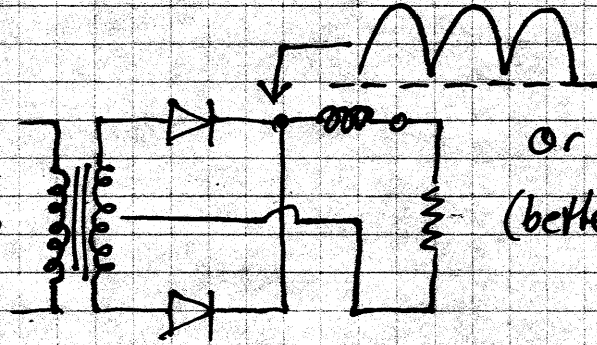Possible use
in power supply
filtering if
 $\omega L \gg R_L/3$



or
(better)

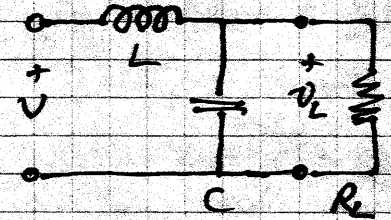


"L-section"

Full wave rectifier \rightarrow half-sine wave series of pulses


Fourier Series \rightarrow
$$V = \frac{2}{\pi} V_m \left(1 - \frac{2}{3} \cos 2\omega t - \frac{2}{15} \cos 4\omega t - \frac{2}{35} \cos 6\omega t - \dots \right)$$

DC term \uparrow
 \uparrow 2nd harmonic
 \uparrow Higher frequency harmonics

Consider L-section for DC

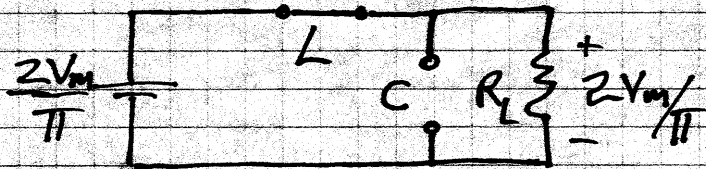

For 2nd harmonic

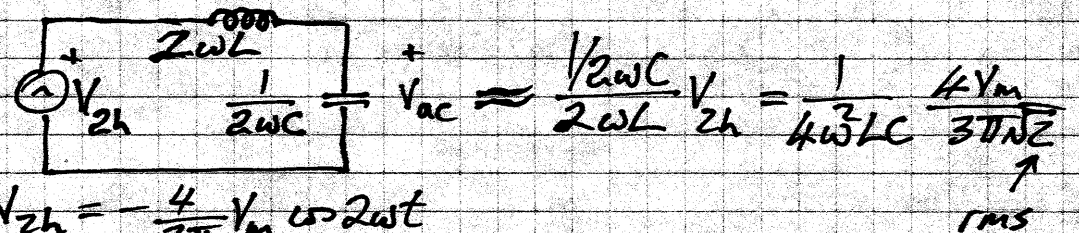

$$V_{2h} = \frac{4}{3\pi} V_m \cos 2\omega t$$

Assume $R_L \gg \frac{1}{2\omega C}$ & $2\omega L \gg \frac{1}{2\omega C}$
for effective smoothing

Ripple factor $r = \frac{I_{ac}}{I_{dc}} = \frac{V_{ac}}{V_{dc}} = \frac{\text{RMS AC amplitude}}{\text{DC amplitude}} \Rightarrow \frac{4V_m}{4\omega^2 LC 3\sqrt{2}} \frac{\pi}{2V_m} \text{ (2nd harmonic only)}$

$$= \frac{\sqrt{2}/3}{4\omega^2 LC}$$

Note: $4\omega^2$ term justifies 2nd harmonic approx!
Next terms $5 \times 16\omega^2$, $11^2/3 \times 36\omega^2$, etc

BRIDGED-T FILTERS

For loops

$$\textcircled{1} \rightarrow V_i = Z_1(I_1 - I_2) + Z_3 I_1$$

$$\textcircled{2} \rightarrow I_2 Z_4 = (I_1 - I_2) Z_1 - I_2 Z_2$$

Need $V_o = V_i - I_2 R_4 \therefore$ Eliminate $I_1 = \frac{Z_1 + Z_2 + Z_4}{Z_1} I_2$ from $\textcircled{2}$

$$\textcircled{1} \rightarrow I_2 = \frac{1}{Z_1} (Z_1 + Z_3) \frac{Z_1 + Z_2 + Z_4}{Z_1} I_2 - \frac{V_i}{Z_1}$$

$$= \frac{V_i / Z_1}{\left(1 + \frac{Z_3}{Z_1}\right) \left(1 + \frac{Z_2 + Z_4}{Z_1}\right) - 1} = \frac{V_i}{(Z_1 + Z_3)(Z_1 + Z_2 + Z_4) - Z_1^2} Z_1$$



$$= \frac{V_i Z_1}{Z_1 Z_2 + Z_1 Z_4 + Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_4}$$

$$\text{So } \frac{V_o}{V_i} = 1 - \frac{1}{\frac{Z_2}{Z_4} + 1 + \frac{Z_3}{Z_4} + \frac{Z_2 Z_3}{Z_1 Z_4} + \frac{Z_3}{Z_1}} = 1 - \frac{1}{1 + \frac{1/j\omega C_2}{R_4} + \frac{R_3}{R_4} + \frac{R_3}{1/j\omega C_1} \frac{1/j\omega C_2}{R_4}}$$

$$= 1 - \frac{1}{1 + \frac{R_3}{R_4} \left(1 + \frac{C_1}{C_2}\right) + j\omega R_3 C_1 - j \frac{1}{\omega R_4 C_2}} = 1 - \frac{1}{1 + \frac{R_3}{R_4} \left(1 + \frac{C_1}{C_2}\right) + j \frac{1}{\omega R_4 C_2} \left[\omega^2 - 1\right]}$$

$$\text{where } \frac{1}{\omega_0^2} = R_4 C_2 R_3 C_1$$



Band-reject filter.

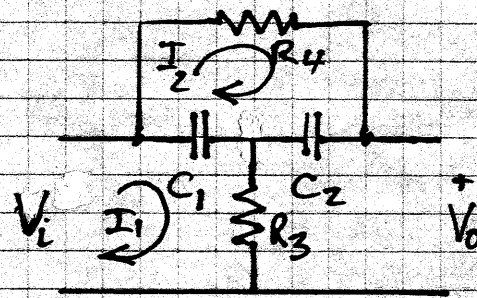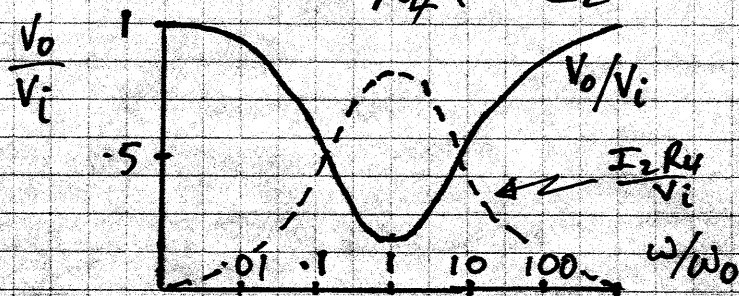

Low Freq: R_4
 C_1, C_2 O.C.

High Freq: R_4
 C_1, C_2 S.C.

RESONANCE

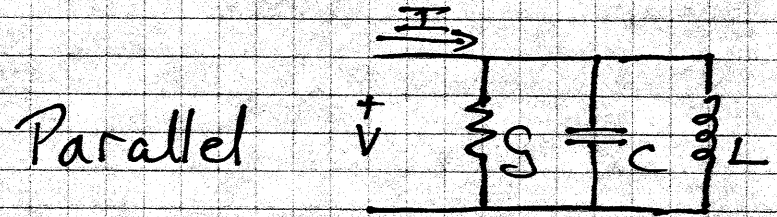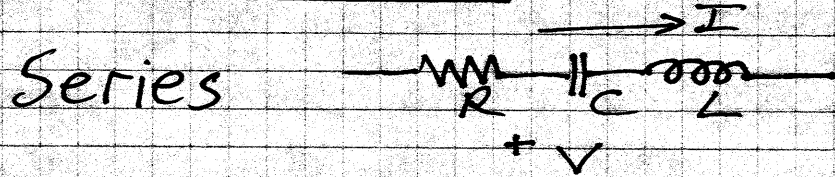

$$Z = R + j\omega L - \frac{j}{\omega C}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$= \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} / \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$

→ $R \angle 0^\circ$ when $\omega_0 L = \frac{1}{\omega_0 C}$
at $\omega = \omega_0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



$$Y = G + j\omega C - \frac{j}{\omega L}$$

$$= G + j\left(\omega C - \frac{1}{\omega L}\right)$$



$$= \sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2} / \tan^{-1} \frac{\omega C - \frac{1}{\omega L}}{G}$$

→ $G \angle 0^\circ$ when $\omega_0 L = \frac{1}{\omega_0 C}$
at $\omega = \omega_0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

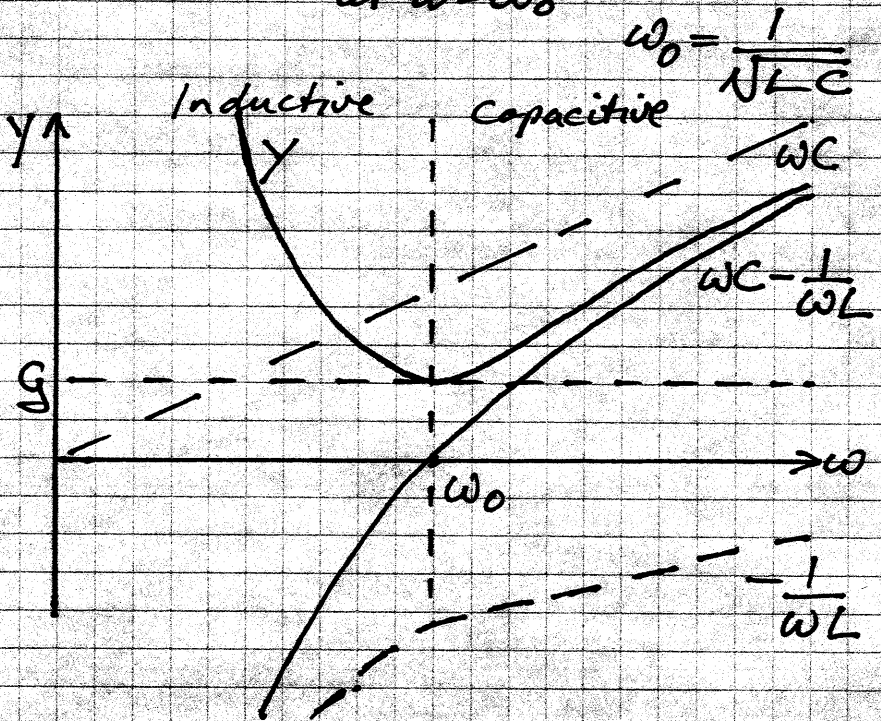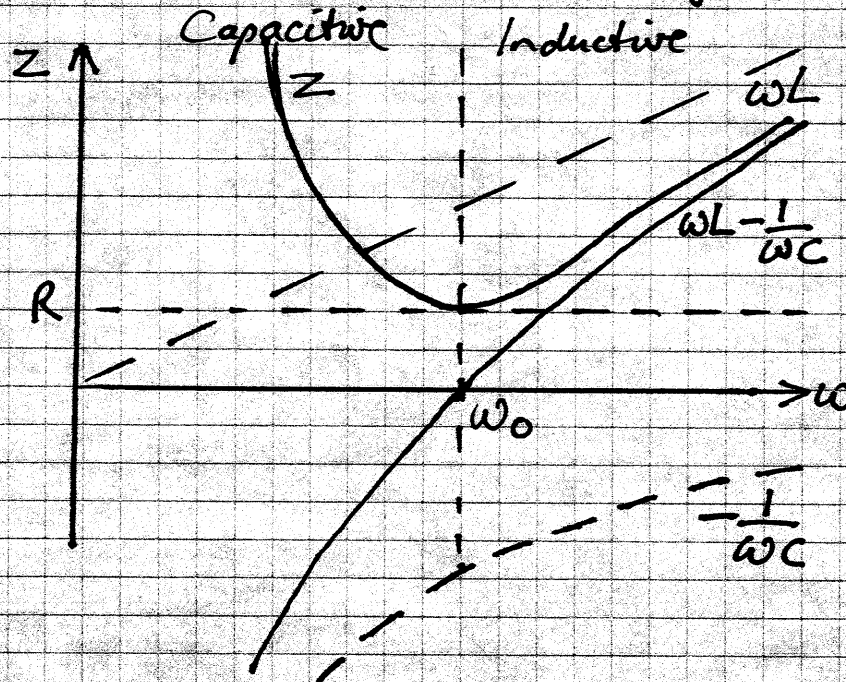

PHASOR VIEW OF RESONANCE

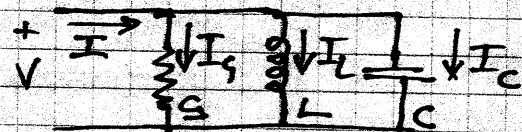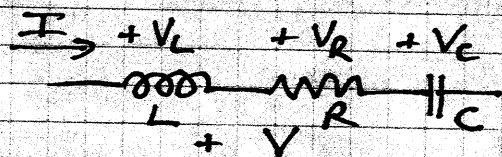

Common element: I as reference

Common element: V as reference


At resonance:

$$\omega = \omega_0$$

$$V_C + V_L = 0$$

$$|V_C| = |V_L|$$

Resistive

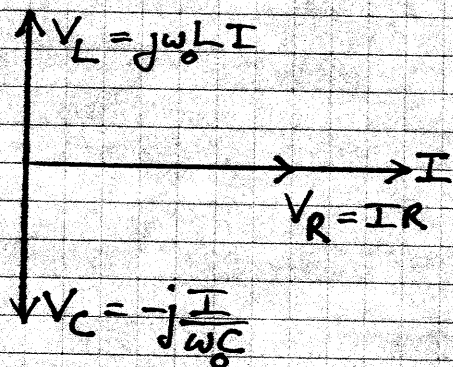


$$\omega = \omega_0$$

$$I_C + I_L = 0$$

$$|I_C| = |I_L|$$


Resistive

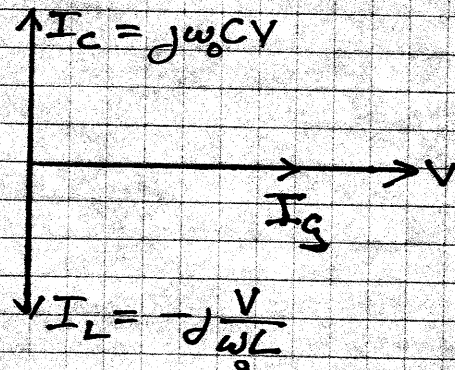

$$\omega < \omega_0$$

$$|V_C| > |V_L|$$


Capacitive

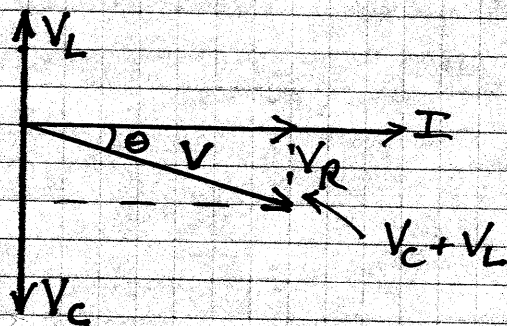

$$\omega < \omega_0$$

$$|I_L| > |I_C|$$


Inductive

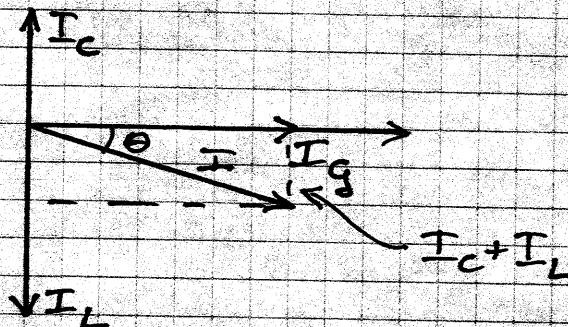

$$\omega > \omega_0$$

$$|V_L| > |V_C|$$


Inductive

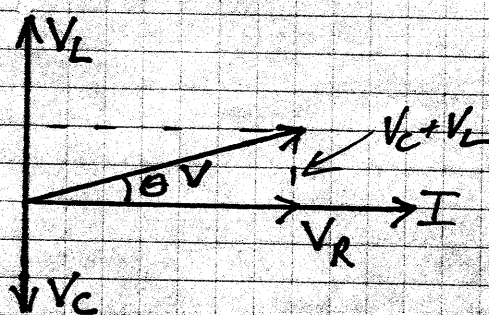

$$\omega > \omega_0$$

$$|I_C| > |I_L|$$

Capacitive

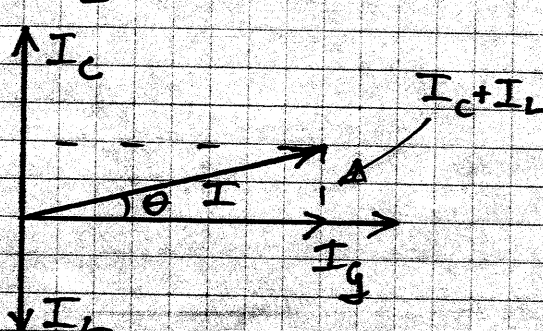

$$\text{QUALITY FACTOR, } Q = 2\pi \frac{\text{Maximum Energy Stored}}{\text{Energy Dissipated/Cycle}}$$

Series

Common element is current

$$i = \sqrt{2} I \cos \omega t$$

$$W_{\text{diss/cycle}} = P \times T_0 = \frac{I^2 R}{f_0}$$

$$\text{Max } W_{\text{stored}} = \frac{1}{2} L I_m^2 = L I^2$$

$$\therefore Q_s = 2\pi \frac{L I^2}{I^2 R / f_0} = \frac{\omega_0 L}{R}$$

Note: Substitute for $\omega_0 = \frac{1}{\sqrt{LC}}$

$$Q_s = \frac{L}{R} \frac{1}{\sqrt{LC}} = \sqrt{\frac{L}{C}} \cdot \frac{1}{R}$$

At resonance $I_0 = V/R$ and $V_L = -V_C$

$$\omega_0 L I_0 = I_0 / \omega_0 C$$

$$\omega_0 L V/R = V / \omega_0 RC \quad \left. \begin{array}{l} \omega_0 L I_0 = I_0 / \omega_0 C \\ \omega_0 L V/R = V / \omega_0 RC \end{array} \right\} Q_s = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Parallel

Common element is voltage

$$v = \sqrt{2} V \cos \omega t$$

$$W_{\text{diss/cycle}} = P \times T_0 = \frac{g V^2}{f_0}$$

$$\text{Max } W_{\text{stored}} = \frac{1}{2} C V_m^2 = C V^2$$

$$\therefore Q_p = 2\pi \frac{C V^2}{g V^2 / f_0} = \frac{\omega_0 C}{g} = \omega_0 RC$$

$$Q_p = RC \frac{1}{\sqrt{LC}} = \sqrt{\frac{C}{L}} R = \frac{1}{Q_s}$$

$V_0 = I/g$ and $I_L = -I_C$

$$V_0 / \omega_0 L = \omega_0 C V_0 \quad \left. \begin{array}{l} V_0 / \omega_0 L = \omega_0 C V_0 \\ I_0 R / \omega_0 L = \omega_0 C I_0 R \end{array} \right\} Q_p = \frac{\omega_0 RC}{R / \omega_0 L} = \omega_0 RC$$

$$I_0 R / \omega_0 L = \omega_0 C I_0 R \quad \left. \begin{array}{l} V_0 / \omega_0 L = \omega_0 C V_0 \\ I_0 R / \omega_0 L = \omega_0 C I_0 R \end{array} \right\} Q_p = \frac{\omega_0 RC}{R / \omega_0 L} = \omega_0 RC$$

NORMALIZED RESONANCE CURVES

Series:

$$Z = R + j(\omega L - \frac{1}{\omega C}) = \frac{1}{Y}$$

& at resonance $Z_0 = R = \frac{1}{Y_0}$

$$\begin{aligned} \frac{Y}{Y_0} &= \frac{Z_0}{Z} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \\ &= \frac{1}{1 + j(\frac{\omega L}{R} - \frac{1}{\omega RC})} \\ &= \frac{1}{1 + j(\frac{\omega_0 L}{R} \cdot \frac{\omega}{\omega_0} - \frac{1}{\omega_0 RC} \cdot \frac{\omega_0}{\omega})} \\ &= \frac{1}{1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} \end{aligned}$$

Parallel:

$$Y = G + j(\omega C - \frac{1}{\omega L}) = \frac{1}{Z}$$

& at resonance $Y_0 = G = \frac{1}{Z_0}$

$$\begin{aligned} \frac{Z}{Z_0} &= \frac{Y_0}{Y} = \frac{G}{G + j(\omega C - \frac{1}{\omega L})} \\ &= \frac{1}{1 + j(\frac{\omega C}{G} - \frac{1}{\omega GL})} \\ &= \frac{1}{1 + j(\omega_0 RC \frac{\omega}{\omega_0} - \frac{R}{\omega_0 L} \frac{\omega_0}{\omega})} \\ &= \frac{1}{1 + jQ_p \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} \end{aligned}$$

Series:


$$\left| \frac{Y}{Y_0} \right| = \frac{1}{\sqrt{2}} \text{ when } \frac{Y}{Y_0} = \frac{1}{1 \pm j} = \frac{1}{\sqrt{2}} \angle \pm 45^\circ$$

when $\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \pm \frac{1}{Q_s}$

ie. at $\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1} = -\frac{1}{Q_s}$ and $\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} = +\frac{1}{Q_s}$

$$\omega_1 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q_s}\right)^2} - \frac{\omega_0}{2Q_s} \quad \omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q_s}\right)^2} + \frac{\omega_0}{2Q_s}$$

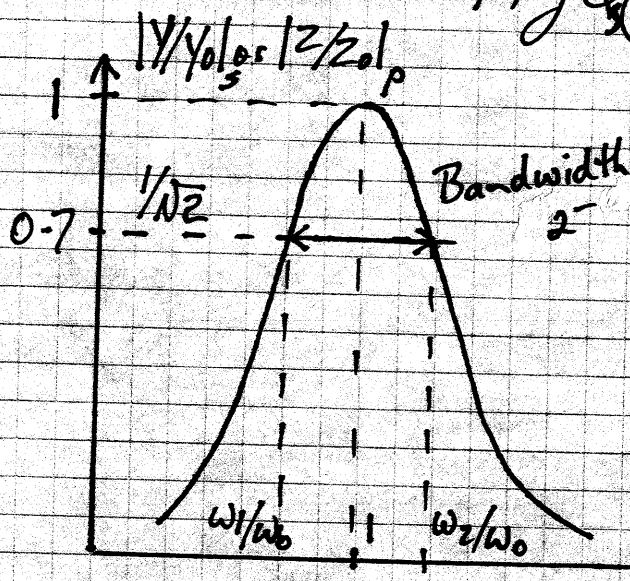Bandwidth $\omega_2 - \omega_1 = \frac{\omega_0}{Q_s} \rightarrow f_2 - f_1 = \frac{f_0}{Q_s}$



Approximation:

$$\text{If } Q_s \geq 10 \quad \sqrt{1 + \left(\frac{1}{2Q_s}\right)^2} \approx 1$$

$$\text{so } \omega_1 \approx \omega_0 - \frac{\omega_0}{2Q_s}$$

$$\omega_2 \approx \omega_0 + \frac{\omega_0}{2Q_s}$$

$$\frac{\omega_1}{\omega_0} \approx 1 - \frac{1}{2Q_s}$$

$$\frac{\omega_2}{\omega_0} \approx 1 + \frac{1}{2Q_s}$$

$$\text{and } \frac{\omega_2}{\omega_0} - \frac{\omega_1}{\omega_0} = \frac{1}{Q_s} \text{ still}$$


(no approximation)

ie. resonance curve is
approximately symmetrical
about ω_0 for high Q_s .


Parallel: All bandwidth results apply to the normalized parallel Z/Z_0 curve with Q_p substituted for Q_s .

Note: Practical resonant circuits:

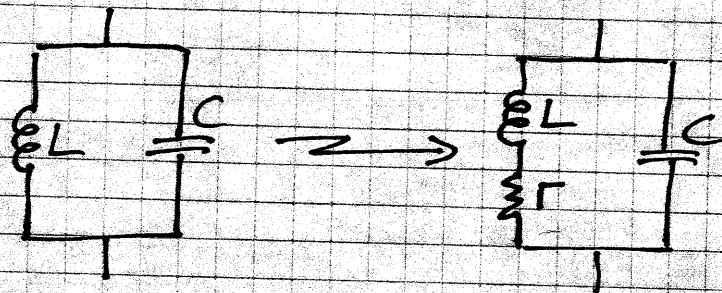Inductors typically have non-negligible series resistance
so practical L-C parallel resonant "tank" circuits look like:




EXERCISES

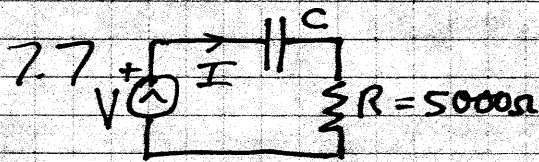

$$\omega_{co} = 500 \text{ rad/sec} \quad \text{i.e. } f_{co} = 500/2\pi = 79.58 \text{ Hz}$$
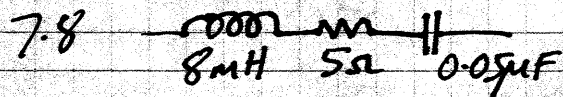
$$= \frac{1}{RC} = \frac{1}{5000C} \quad \therefore C = \frac{1}{(500)(5000)} = 0.4 \mu\text{F}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = (8 \times 10^{-3} \times 0.05 \times 10^{-6})^{-1/2} = (4 \times 10^{-10})^{-1/2} = 5 \times 10^4 \text{ rad/s}$$

At ω_0 $X_L = \omega_0 L = 5 \times 10^4 \times 8 \times 10^{-3} = 400 \Omega$, $X_C = (\omega_0 C)^{-1} = 2 \times 10^{-5} \times 20 \times 10^6 = 400 \Omega$


7.9

$$f = 5000 \text{ Hz} \quad (a) \quad 2\pi f_0 = \frac{1}{\sqrt{LC}} \quad \therefore C = \frac{1}{L(2\pi f_0)^2} = \frac{1}{2 \times 10^{-2} \times 4\pi^2 \times 25 \times 10^6} = 0.05 \mu\text{F}$$

(b) at f_0 , $|V_C| = 5 \text{ V} \quad \therefore |V_L| = 5 \text{ V}$ & $V_{tot} = V_R = IR = \frac{5 \text{ V}}{1/2\pi f_0 C} R = 5 \times 2\pi \times 5000 \times 6.28 \times 0.05 \times 10^{-6}$
 $= 4.93 \times 10^{-3} \text{ V}$

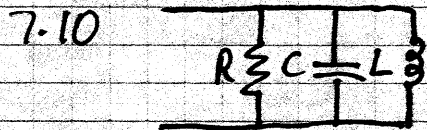(c) For $C' = 0.025 \mu\text{F}$ $f_0' = \frac{1}{2\pi \sqrt{LC'}} = f_0 \sqrt{\frac{C}{C'}} = \sqrt{2} f_0 = 1.414 \times 5000 = 7070 \text{ Hz}$

$$Q_s' = \omega_0 L / R = 2\pi \times 7070 \times 20 \times 10^{-3} / 6.28 = 14.14$$



$$Q_p = 60, Z_{max} = 10,000 \Omega$$

at 240,000

$$\therefore R = 10 \text{ K}\Omega \text{ and } f_0 = 240 \text{ kHz}$$

$\frac{1}{2}$ power frequencies ω_1, ω_2 ?

Since $Q_p = 60 > 10$, can use the approximation of symmetrical resonance

$$f_1, f_2 \approx f_0 \pm \frac{f_0}{2Q} = \left(240 \pm \frac{240}{2 \times 60} \right) \text{ kHz}$$

$$= 240 \pm 2 \text{ kHz}$$

i.e. $\omega_1 \approx 238 \text{ kHz}$ $\omega_2 \approx 242 \text{ kHz}$