

ECE 241 LECTURE 13 NETWORK THEORY

ONE-PORT NETWORKS:

Generalize earlier results for one-port resistive networks to AC.

Equivalence: 2 one-ports are equivalent if they have the same I-V characteristic.
(For ac networks, equivalence is generally only at one frequency)

Network Reduction:

$$\bar{Z}_{EQ} = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 + \dots + \bar{Z}_n$$

$$\bar{Y}_{EQ} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots + \bar{Y}_n$$

Dividers: Voltage Divider $\rightarrow V_2 = \frac{\bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \bar{V}$


Current Divider $\rightarrow \bar{I}_2 = \frac{\bar{Y}_2}{\bar{Y}_1 + \bar{Y}_2} \bar{I} = \frac{\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_2} \bar{I}$

Linearity & Superposition:

Linear $\rightarrow f(kx) = kf(x)$

$f(x_1 + x_2) = f(x_1) + f(x_2)$

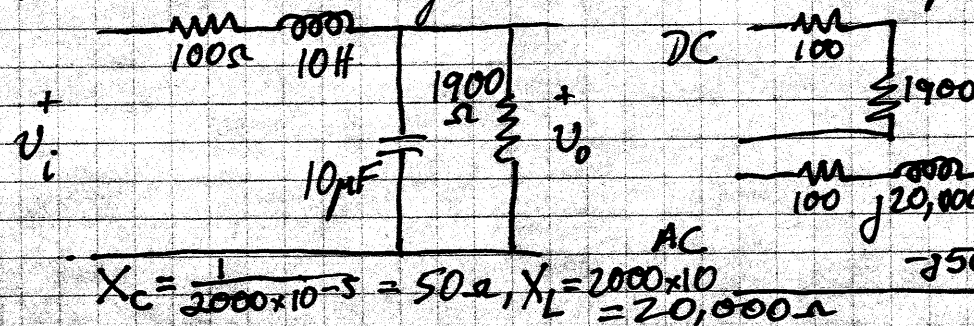Exercise 8.1 Signal 50V dc + 50V (peak) ac at 2000 rad/s at input. Predict output.



DC: $v_o)_{DC} = \frac{1900}{100 + 1900} 50V = 47.5V$

AC: Neglect R_s $100\Omega \ll |j20,000|$
 $1900 \gg | -j50 |$


$\therefore v_o)_{AC} \approx \frac{-j50}{j20,000 - j50} 50 \approx 0.125V_{pk}$
 $\therefore v_o = 47.5 - 0.125 \cos 2000t$

$X_C = \frac{1}{2000 \times 10^{-9}} = 50\Omega$, $X_L = 2000 \times 10 = 20,000\Omega$

ACTIVE NETWORKS: (Norton/Thevenin)



From the point of view of the load, any one-part network of linear elements and sources can be replaced by:

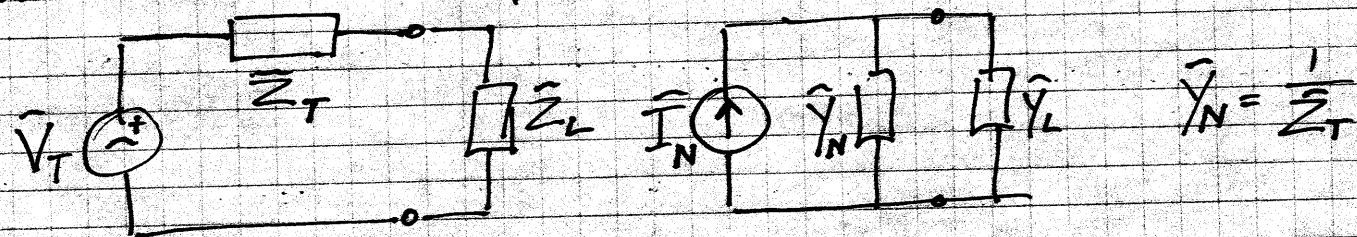Thevenin \rightarrow Either: A series combination of ideal voltage source and linear impedance
 Norton \rightarrow Or: A parallel combination of ideal current source and linear admittance.




See Example 2 (Bridge circuit)



Exercise 8.2: Find I_L

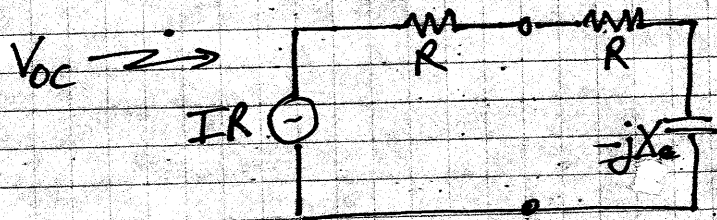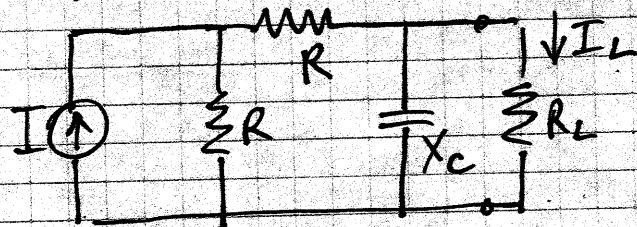

$$V_{OC} = \frac{-jX_C}{2R - jX_C} I$$

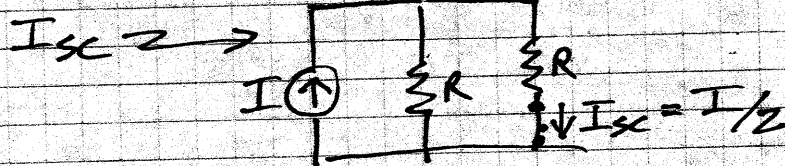

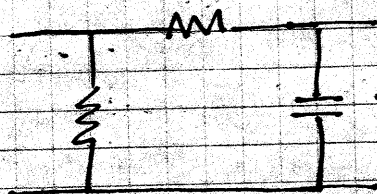
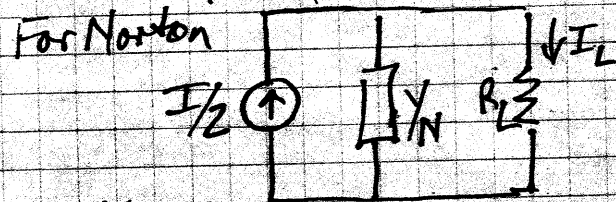
Use any 2 of V_{OC} , I_{SC} , Y_N (or Z_T)



$$Y_N = \frac{1}{Z_T} = \frac{j}{X_C} + \frac{1}{2R}$$

$$\text{Hence } I_L = \frac{1/R_L}{Y_N + 1/R_L} \cdot \frac{I}{2} = \frac{I}{2(1 + Y_N R_L)}$$

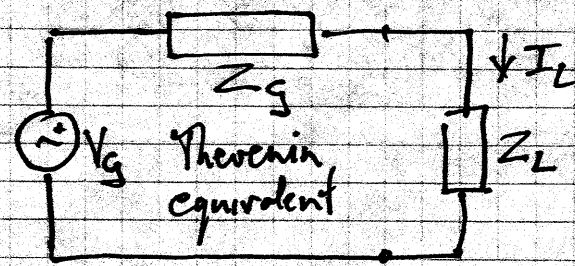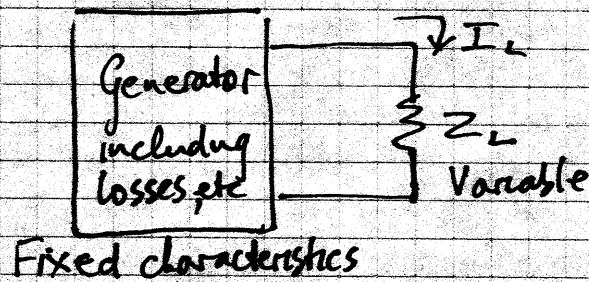MAXIMUM POWER TRANSFER (Recall P_{\max} when $R_L = R_g$ for DC)



$$I_L = \frac{V_g}{|\bar{Z}_g + \bar{Z}_L|} = \frac{V_g}{\sqrt{(R_g + R_L)^2 + (X_g + X_L)^2}}$$

$$\text{Real power transferred to load} = P_L = I_L^2 R_L = \frac{V_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2}$$

For any value of R_L (R_g, X_g, V_g fixed),

P_L is max when $X_L = -X_g$

$$\text{Hence } P_L = \frac{V_g^2 R_L}{(R_g + R_L)^2}, \quad \frac{dP_L}{dR_L} = V_g^2 \cdot \frac{(R_g + R_L)^2 - R_L(2)(R_g + R_L)}{(R_g + R_L)^4} = 0 \text{ for max}$$

$$\text{when } (R_g + R_L)^2 = 2R_L(R_g + R_L)$$


$$R_g + R_L = 2R_L$$

$$R_L = R_g$$

Hence max power transfer when $R_L = R_g$ and $X_L = -X_g$

$$\bar{Z}_L = R_L + jX_L = R_g - jX_g = \bar{Z}_g^* \text{ (complex conjugate)}$$


Exercise 8.3

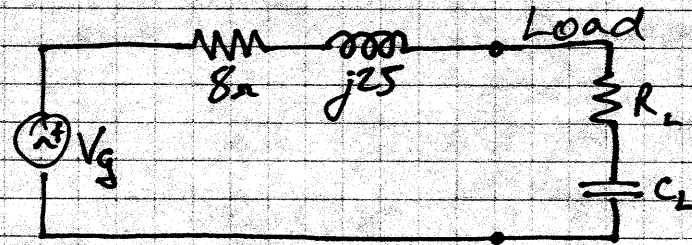


Find R_L, C_L for max power delivered to load.
 $\omega = 4000 \text{ rad/s}$

$$R_L = R_g = 8 \Omega \quad X_L = \frac{-1}{\omega C_L} = -X_g = -j25 \quad \therefore C_L = \frac{1}{25 \omega} = 10^{-5} = 10 \mu\text{F}$$

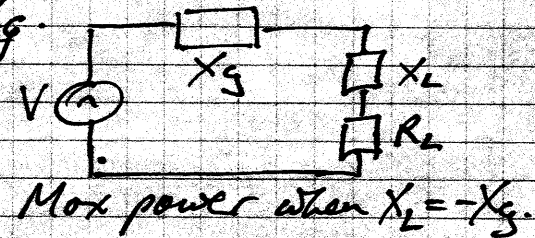Note: Max power transfer condition is NOT maximum efficiency. (50%)
 Max efficiency \rightarrow minimize losses \rightarrow minimize R_g .



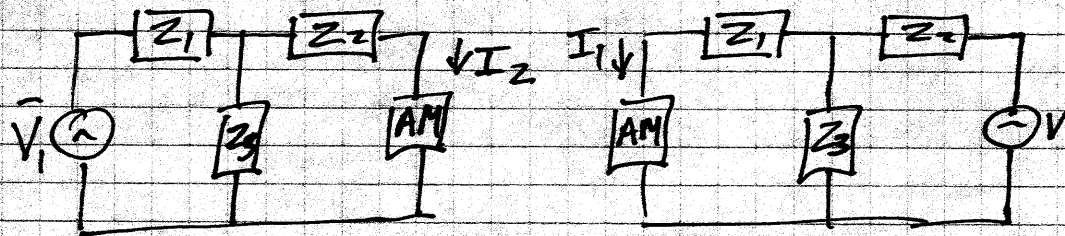RECIPROCITY THEOREM: In any passive linear network, if a voltage \bar{V} in branch 1 causes current \bar{I} in branch 2, then voltage \bar{V} in branch 2 will cause current \bar{I} in branch 1.



Define "transfer impedance"
 $\bar{Z}_{12} = \bar{V}_1 / \bar{I}_2$

In passive linear networks
 $\bar{Z}_{12} = \bar{Z}_{21}$

$$I_2 = \frac{Z_3}{Z_2 + Z_3} \cdot \frac{V_1}{Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}}$$

$$= \frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} V_1$$



$$I_1 = \frac{Z_3}{Z_2 + Z_3} \cdot \frac{V_1}{Z_2 + \frac{Z_1 Z_3}{Z_1 + Z_3}}$$

$$= \frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} V_1$$

$$= I_2$$

Exercise 8.4

$$I_1 = 4 \angle -45^\circ \text{ V}$$

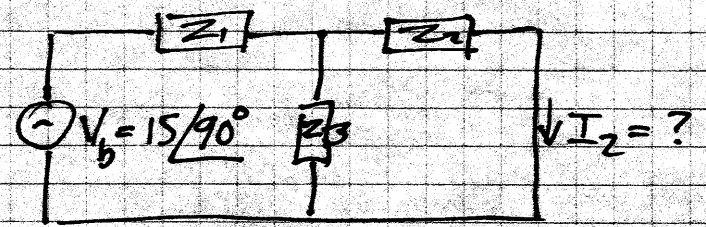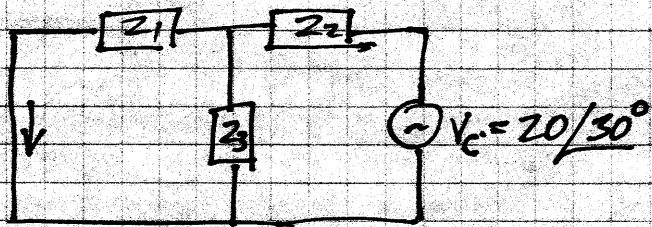


$V_b = 20 \angle 30^\circ$ would yield $I_2 = 4 \angle -45^\circ$

$V_b = 15 \angle 30^\circ$ " " $I_2 = \frac{15}{20} 4 \angle -45^\circ = 3 \angle -45^\circ$


$V_b = 15 \angle 90^\circ$ " " $I_2 = 3 \angle -45^\circ + 60^\circ = 3 \angle 15^\circ$

TWO PORT NETWORKS


Problem with finding R_{ab} by

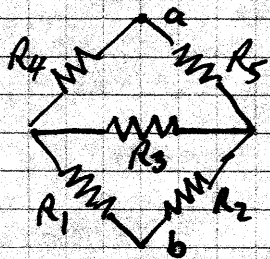

network reduction
But can transform

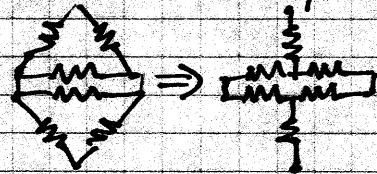

In general, for a 2-port network

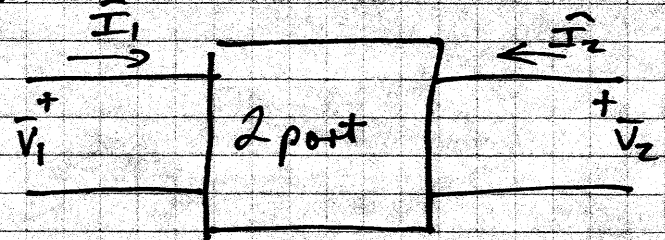


$$\begin{aligned} \bar{V}_1 &= \bar{Z}_{11} \bar{I}_1 + \bar{Z}_{12} \bar{I}_2 & \bar{I}_1 &= \bar{Y}_{11} \bar{V}_1 + \bar{Y}_{12} \bar{V}_2 \\ \bar{V}_2 &= \bar{Z}_{21} \bar{I}_1 + \bar{Z}_{22} \bar{I}_2 & \bar{I}_2 &= \bar{Y}_{21} \bar{V}_1 + \bar{Y}_{22} \bar{V}_2 \end{aligned}$$

where $\bar{Z}_{12} = \bar{Z}_{21}$ or $\bar{Y}_{12} = \bar{Y}_{21}$

by the Reciprocity Theorem.

i.e. any 2-port linear network can be characterized by 3 parameters

For the circuits shown.

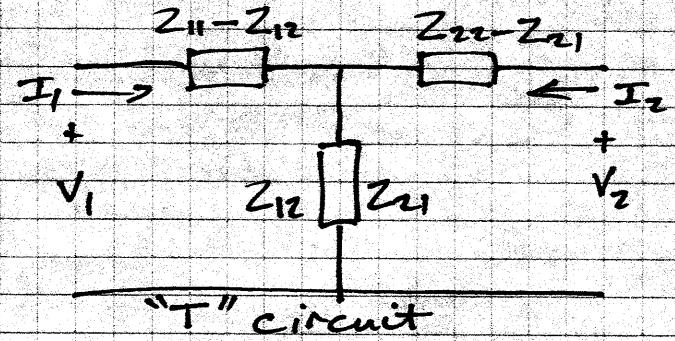


$$V_1 = (Z_{11} - Z_{12})I_1 + Z_{12}(I_1 + I_2)$$

$$= Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = (Z_{22} - Z_{21})I_2 + Z_{21}(I_1 + I_2)$$

$$= Z_{21}I_1 + Z_{22}I_2$$

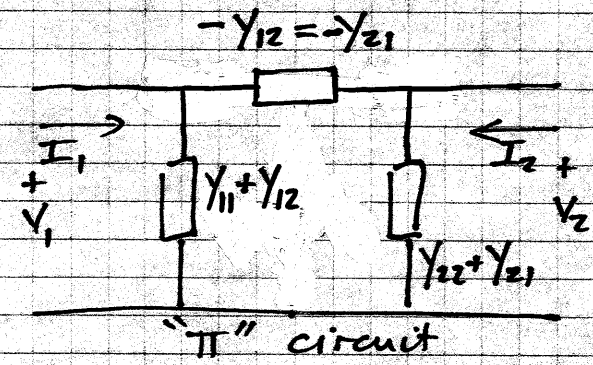

$$I_1 = (Y_{11} + Y_{12})V_1 - Y_{12}(V_1 - V_2)$$

$$= Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = (Y_{22} + Y_{21})V_2 - Y_{21}(V_2 - V_1)$$

$$= Y_{21}V_1 + Y_{22}V_2$$

T-to-Π TRANSFORMATION

(Three terminal circuits)


Equating impedances (with 3rd terminal open)

$$Z_3 + Z_1 = Z_{31} \parallel (Z_{12} + Z_{23})$$

$$Z_2 + Z_3 = Z_{23} \parallel (Z_{31} + Z_{12})$$

$$Z_1 + Z_2 = Z_{12} \parallel (Z_{23} + Z_{31})$$

Elim Z_3
Elim Z_2

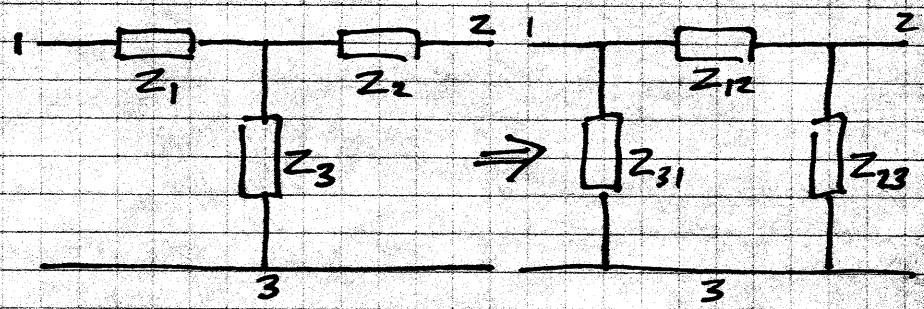

$$Z_1 - Z_2 = Z_{31} \parallel (Z_{12} + Z_{23}) - Z_{23} \parallel (Z_{31} + Z_{12})$$

$$2Z_1 = Z_{12} \parallel (Z_{23} + Z_{31}) - Z_{23} \parallel (Z_{31} + Z_{12}) + Z_{31} \parallel (Z_{12} + Z_{23})$$

$$= \frac{Z_{12}(Z_{23} + Z_{31}) - Z_{23}(Z_{31} + Z_{12}) + Z_{31}(Z_{12} + Z_{23})}{Z_{12} + Z_{23} + Z_{31}}$$

$$= \frac{Z_{12}Z_{23} + Z_{12}Z_{31} - Z_{23}Z_{31} - Z_{12}Z_{23} + Z_{31}Z_{12} + Z_{31}Z_{23}}{Z_{12} + Z_{23} + Z_{31}}$$

$$Z_2 = \frac{Z_{12}Z_{23}}{Z_{12} + Z_{23} + Z_{31}} \quad Z_3 = \frac{Z_{23}Z_{31}}{Z_{12} + Z_{23} + Z_{31}} \quad \leftarrow \text{Similarly} \quad Z_1 = \frac{Z_{31}Z_{12}}{Z_{12} + Z_{23} + Z_{31}}$$



Similarly for Π -to- T (Δ - Y delta-wye)

$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3} \text{ etc.}$$

OR

$$Y_{12} = \frac{Y_1 Y_2}{Y_1 + Y_2 + Y_3} \text{ etc.}$$

Example 4:

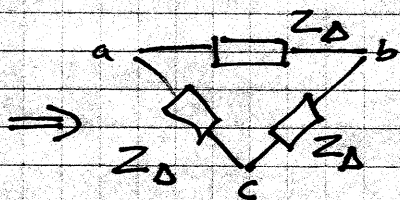
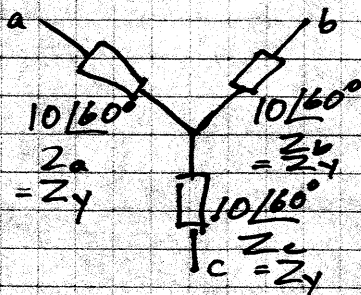


$$Z_D = Z_{ab} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$

$$= \frac{3(Z_y)^2}{Z_y} = 3Z_y = 30/60^\circ$$

This is important for 3ϕ applications.


Exercise 8.5:

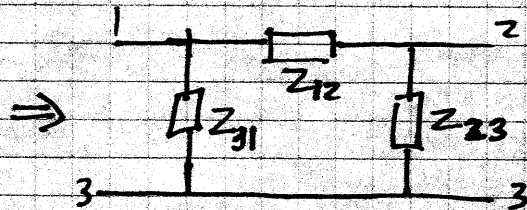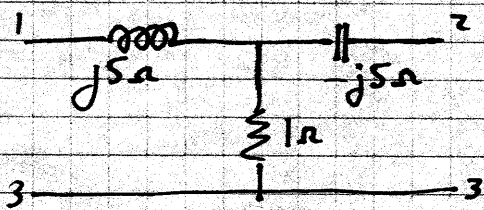


$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3} = \frac{(j5)(-j5) + (-j5)(1) + (1)(j5)}{1} = 25\Omega$$

$$Z_{23} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} = \frac{25\Omega}{j5} = -j5\Omega$$

$$Z_{31} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2} = \frac{25\Omega}{-j5} = +j5\Omega$$

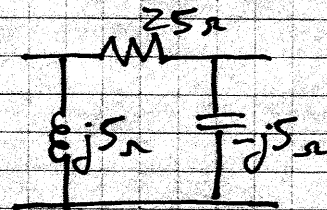


Exercise 8.6

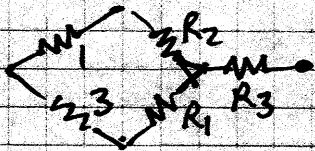

$$R_1 = \frac{12 \times 4}{6 + 4 + 10} = \frac{48}{20} = 2.4\Omega$$


$$R_2 = \frac{4 \times 12}{20} = 2.4\Omega$$
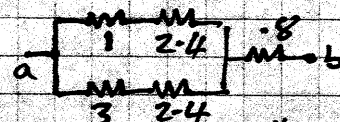
$$R_3 = \frac{4 \times 4}{20} = 0.8\Omega$$




$$R_{ab} = 0.8 + 3.4/5.4 = 2.89\Omega$$

COUPLING CIRCUITS

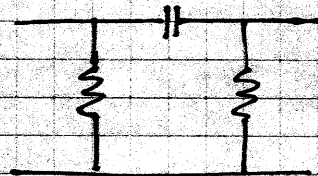


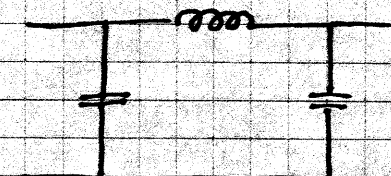eg. amplifier coupling from source or to load
blocks dc, passes signal.



eg. smoothing filter on power supply

MUTUAL INDUCTANCE

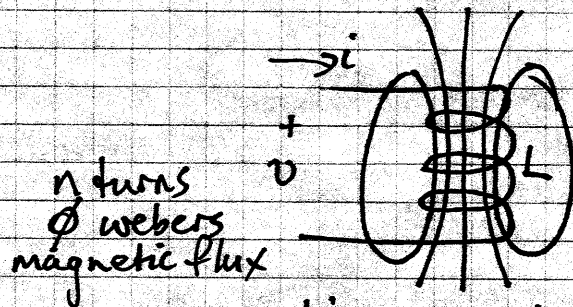

$$v = L \frac{di}{dt} = n \frac{d\phi}{dt}$$


$$= n \frac{d(kni)}{dt}$$

$$= kn^2 \frac{di}{dt}$$

$$\phi \propto ni$$


L is "self-inductance"

Exercise 8.7

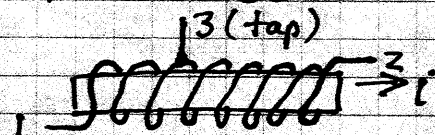


$$L_T = (L_1 + M) + (L_2 + M)$$

$$= L_1 + L_2 + 2M$$

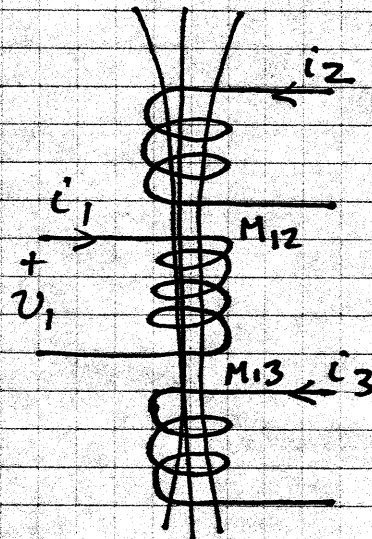

$$v_1 = v_{11} + v_{12} + v_{13}$$
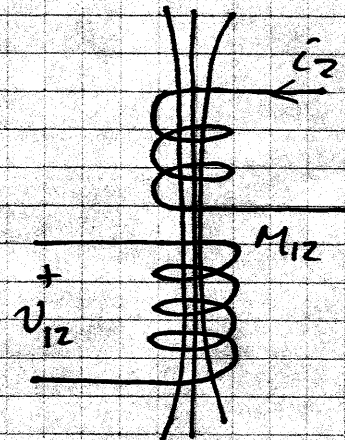
$$= L \frac{di_1}{dt} + M_{12} \frac{di_2}{dt} + M_{13} \frac{di_3}{dt}$$



$$v_{12} = M_{12} \frac{di_2}{dt}$$

Signs are important


Exercise 8.8: 2 coils $N_2 = 2N_1$
 $\therefore L_2 = 4L_1$

In series: $L_s = 8L_1$

$$= (L_1 + M) + (4L_1 + M)$$


$$\therefore 2M = 3L_1 \quad M = 1.5L_1$$

INDUCTIVE COUPLING

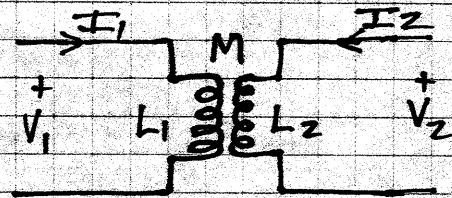

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$
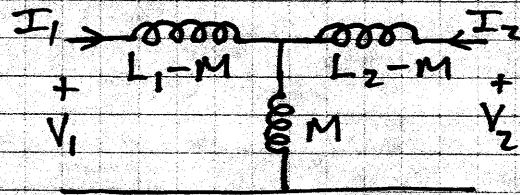
$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$



Equivalent circuits


$$V_1 = j\omega(L_1 - M)I_1 + j\omega M(I_1 + I_2)$$

$$= j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega(L_2 - M)I_2 + j\omega M(I_1 + I_2)$$

$$= j\omega M I_1 + j\omega L_2 I_2$$

TRANSFORMER COUPLING

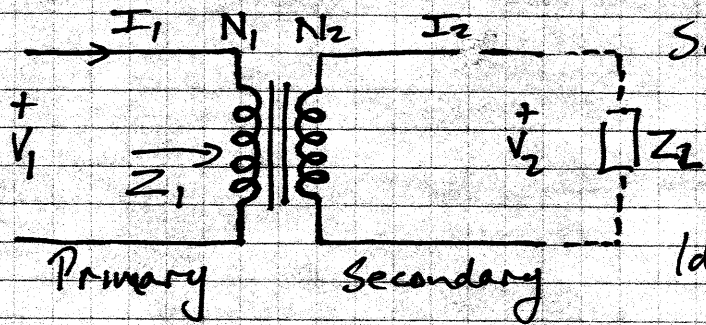

Same flux ϕ links both coils

$$V = N \frac{d\phi}{dt} \rightarrow \frac{V_2}{V_1} = \frac{N_2}{N_1}$$

Ideal transformer: No power loss $\therefore P_{in} = P_{out}$

$$V_1 I_1 = V_2 I_2$$

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

For impedance $Z_2 = \frac{V_2}{I_2}$ $Z_1 = \frac{V_1}{I_1} = \frac{V_2 (N_1/N_2)}{I_2 (N_2/N_1)} = \left(\frac{N_1}{N_2}\right)^2 Z_2$

Z_1 is the "reflected" impedance "seen" at the primary, due to the secondary load Z_2


Exercise 8.9

$N_1/N_2 = 5$	}	$\therefore I_2 = 5 \times 1 \text{ A} = 5 \text{ A}$
$Z_2 = 10 \Omega$		$\therefore V_2 = I_2 Z_2 = 50 \text{ V}$
$I_1 = 1 \text{ A}$		$\therefore V_1 = 5 \times 50 = 250 \text{ V}$

Note: Only changing flux induces voltage

∴ transformer acts on ac signals, not dc

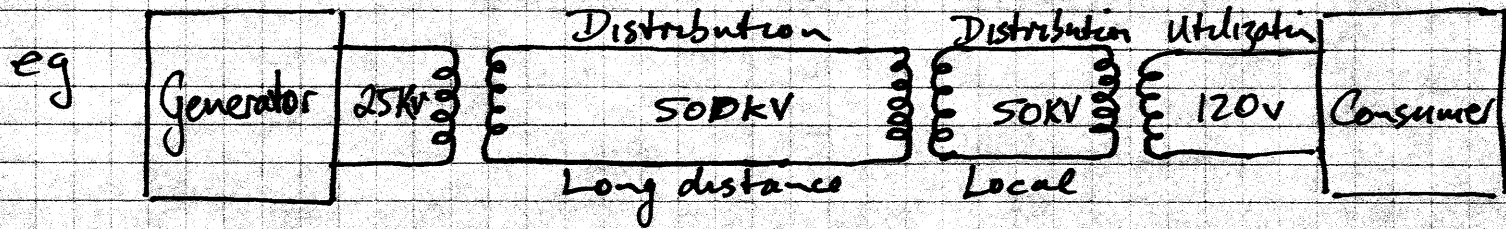
Note use of transformers in power distribution



Impedance matching:

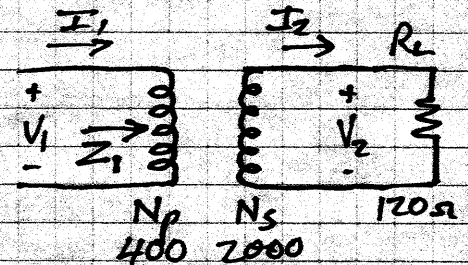Exercise 8.10

$N_p = 400$ primary
 $N_s = 2000$ secondary
 $V_1 = 120V$
 $R_L = 120\Omega$
Find V_2, I_1



$$V_2 = \frac{N_2}{N_1} V_1 = \frac{2000}{400} 120 = 600V$$

$$I_1 = \frac{N_2}{N_1} I_2 = \frac{N_2}{N_1} \frac{V_2}{R_L} = \frac{2000}{400} \frac{600}{120} = 25A$$

$$Z_1 = \frac{V_1}{I_1} = \frac{120V}{25A} = 4.8\Omega$$

Could use this transformer to couple current source to higher impedance load.

Assignment #6

P 7.16

P 7.28

P 7.33

P 8.19

P 8.23

P 8.30

AP 8.7