
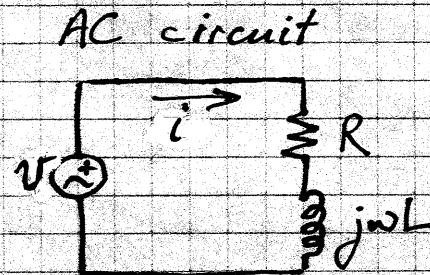
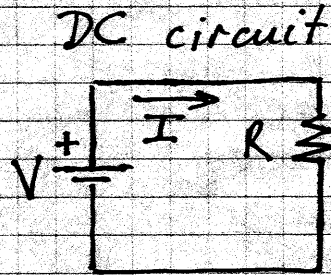


ECE 241 Lecture 15 TRANSFORMERS

MAGNETIC CIRCUITS: AC

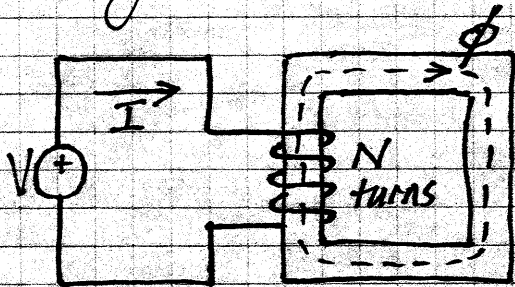

$$I = V/R \text{ (windings)}$$
$$\phi_{DC} = NI/R$$
$$= \mu NIA/l$$

(constant)

Typically $R \ll \omega L$

$$\phi_{AC} \rightarrow \text{induced voltage}$$
$$\approx v \approx j\omega L i$$

INDUCTANCE

Induced voltage in coil linked to changing field $v = N \frac{d\phi}{dt} = \frac{d\lambda}{dt}$
($\lambda =$ number of flux linkages ... weber.turns ... $N\phi$)

LENZ'S LAW: Induced voltage direction opposes the change in flux linkage that produces it.

ie. if flux ϕ is decreasing, the induced voltage direction ($v = N \frac{d\phi}{dt}$) will cause current to increase ϕ

Assuming constant μ (linear B-H curve):


For $\phi = \phi_m \sin \omega t$

Induced voltage $v = N \frac{d\phi}{dt} = N\omega \phi_m \cos \omega t$

ie. $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{N\omega \phi_m}{\sqrt{2}} = \frac{2\pi}{\sqrt{2}} Nf \phi_m = 4.44 Nf \phi_m$

$v = L \frac{di}{dt} = N \frac{d\phi}{dt} (= \frac{d\lambda}{dt})$ ie. $L = N \frac{d\phi}{di} (= \frac{d\lambda}{di})$
 Magnetic circuit & for $\phi \propto i$

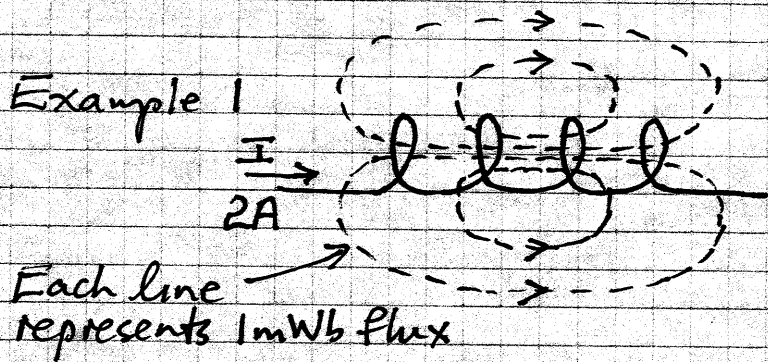$L = N \frac{\phi}{i} (= \frac{\lambda}{i})$



Find λ and L :


2 turns link 4mWb } $\therefore \lambda = 2 \times 4 \times 10^{-3}$
 other 2 turns link 2mWb } $+ 2 \times 2 \times 10^{-3}$
 $= 12 \text{ mWb.t}$

$\therefore L = \lambda/i = 12 \times 10^{-3} / 2 = 6 \text{ mH}$

Note "leakage" effect of field lines linking few turns

→ high permeability core } → high L
 → tightly wound coils }

ENERGY STORAGE

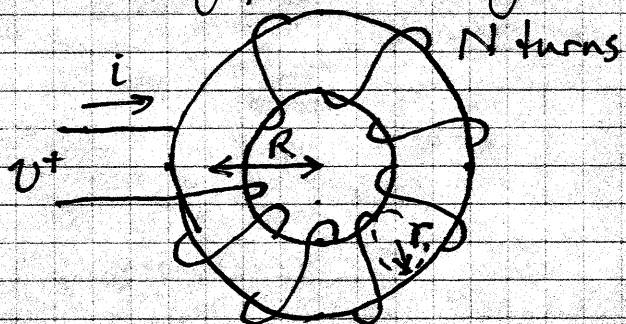

$$\mathcal{F} = Ni = Hl \quad \leftarrow 2\pi R$$

$$\phi = BA \quad \text{for } r \ll R, \text{ approx uniform } B, H$$

For initially unmagnetized core

$$W = \int_0^t v i dt = \int_0^t N \frac{d\phi}{dt} i dt$$

$$= \int_0^\phi Ni d\phi = \int_0^B (HL)(A dB)$$

$$= (lA) \int_0^B H dB$$

ie. Energy density $W_V = \frac{W}{\text{vol}} = \int_0^B H dB$

(see above for non-linear interpretation)

For linear $B = \mu H$, $W_V = \int_0^B \frac{B}{\mu} dB = \frac{1}{2} \frac{B^2}{\mu}$

$$= \int_0^H H \cdot \mu dH = \frac{1}{2} \mu H^2$$

Note also: $W = (lA) \int_0^B H dB = \frac{(lA)}{2\mu} B^2 = \frac{(lA)}{2\mu} \frac{\phi}{A} \frac{\phi}{A} = \frac{(lA)}{2\mu} \frac{\phi}{A} \cdot \frac{Ni}{A \cdot \frac{1}{\mu} \frac{l}{A}} = \frac{1}{2} N \phi i$

$$= \frac{1}{2} \frac{N \phi}{i} i^2 = \frac{1}{2} L i^2$$


Ex 21.2 Thin toroid $r \ll R$ with air gap length l_a . Toroid "length" $l_i \approx 2\pi R$
 Toroid permeability $\mu_r = 1800$ Find $\frac{l_a}{l_i}$ for $W_a = 0.9 W_i$

$$\frac{W_a}{W_i} = \frac{l_a A_a \frac{B_a^2}{\mu_0}}{l_i A_i \frac{B_i^2}{\mu_r \mu_0}} \rightarrow \mu_r \frac{l_a}{l_i} \text{ assuming negligible fringing in the gap} \\
 \& \text{ hence that } A_a = A_i, B_a = B_i$$

$$\text{So } \frac{l_a}{l_i} = \frac{1}{\mu_r} 0.9 = \frac{0.9}{1800} = 5 \times 10^{-4} \Rightarrow 0.05\%$$

PHYSICAL ENERGY LOSS MECHANISMS

(a) Hysteresis

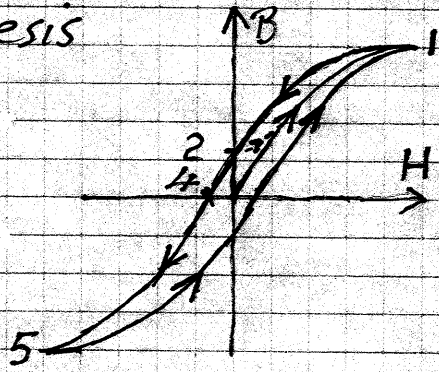


- 1: Saturation $\rightarrow dB = \mu_0 dH$
- 2: Residual magnetism

(If re-apply $H > 0$, path $2 \rightarrow 1$)

Cyclic path $1 \rightarrow 2 \rightarrow 4 \rightarrow 5 \rightarrow 1$

Area enclosed \rightarrow hysteresis loss

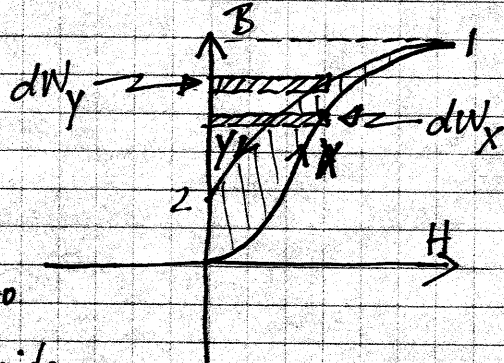
From 2, negative H (coercive force) needed for $B=0$ (pt 4)



Energy absorbed, path X $\int_0^{B_1} H_x dB_x$


Energy returned, path Y $\int_{B_1}^{B_2} H_y dB_y < \text{path X}$

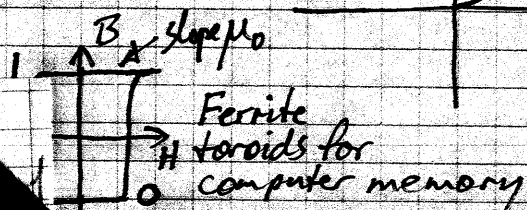Energy absorbed \rightarrow heats up, inelastic domain rotation
 $P_H = K_H f B_m^n$ (n typ 1.6) etc



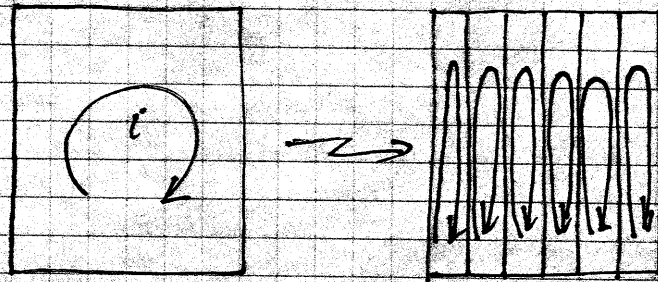(b) Eddy currents

Conductive core material (eg. iron), changing ϕ induces V in core
 $V_{\text{core}} \rightarrow i_{\text{core}}^2 R$ losses \rightarrow Joule heating.



Solid core

Laminated
(eg. varnish)


Laminations reduce induced V_{core}
and increase path resistance.

Losses (Joule heating) $P_E = K_E f^2 B_m^2$

$V_{\text{induced}} \propto f B_m$, $P \propto V_{\text{induced}}^2$

(c) Copper losses — winding resistances.



TRANSFORMER

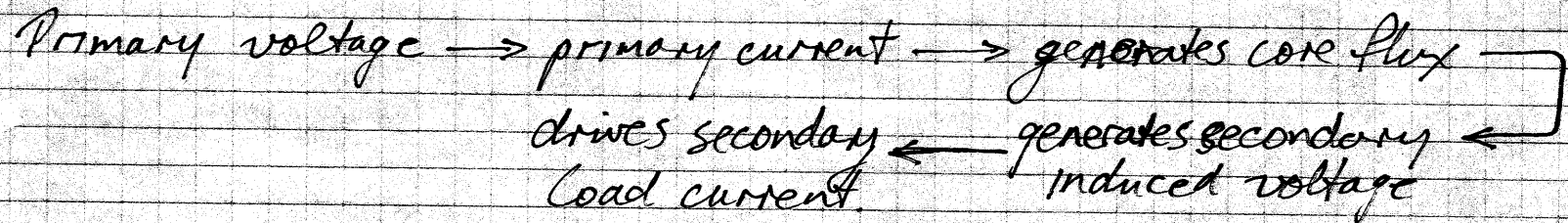

See Fig 2.19 for construction examples. (Also toroid, etc)

VOLTAGE & CURRENT RELATIONS

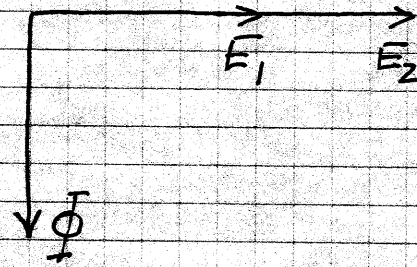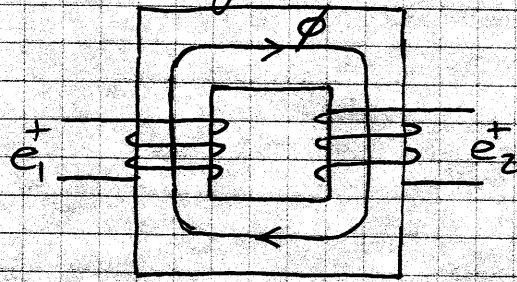Assuming negligible flux leakage, tight coupling \rightarrow i.e. both coils link same flux
 Voltage induced \rightarrow electromotive force (emf)



For $\phi = \Phi_m \sin \omega t$

$$e_1 = N_1 \frac{d\phi}{dt} = N_1 \omega \Phi_m \cos \omega t = \sqrt{2} E_1 \cos \omega t$$

$$e_2 = N_2 \frac{d\phi}{dt} = N_2 \omega \Phi_m \cos \omega t = \sqrt{2} E_2 \cos \omega t$$

$$e_2/e_1 = E_2/E_1 = N_2/N_1$$

$$\sin \omega t = \cos(\omega t - 90^\circ)$$

\therefore Flux phasors lags the emf phasors by $\pi/2$


Terminal voltages \neq emfs

EXCITING CURRENT

Open circuit secondary \rightarrow v_2 at terminals 2 = e_2 = induced emf₂


Ideally $I_1 = 0$ if $I_2 = 0$, but in practice current must flow to generate ϕ

so $I_1 \Big|_{I_2=0} = I_E$ (exciting current) = I_m (magnetizing current) + I_c (core loss current)

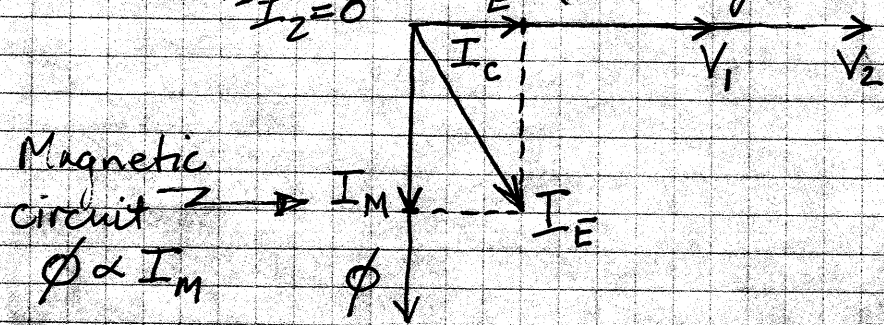

Hysteresis/eddy currents
 (typically/ideally small $\ll I_m$)

PRIMARY & SECONDARY CURRENTS WITH LOAD

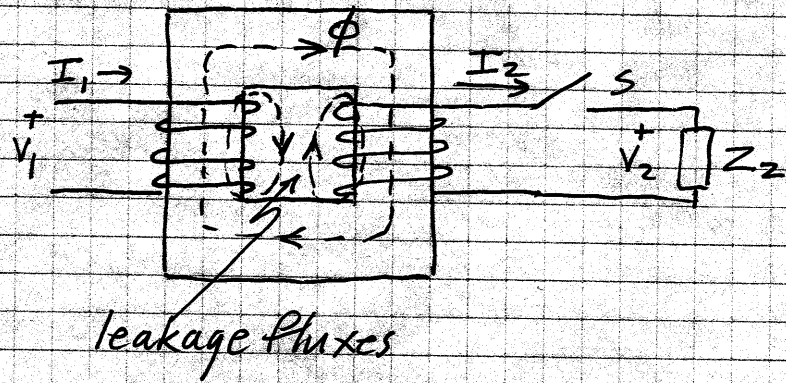

Assume $V_2 = E_2$ $V_1 = E_1$ $I_c = 0$
 so $I_E = I_m$

With S closed $I_2 = V_2/Z_2$ flows

$I_2 \rightarrow$ mmf $N_2 I_2$ which

Opposes ϕ (check by RH Rule as drawn)


Additional I_1 current must flow to offset the potential reduction in ϕ .

New net mmf = mmf due to I_m (no load)

$$N_1 I_m - N_2 I_2 + N_1 I_1' = N_1 I_m$$

\uparrow added primary current for finite Z_2, I_2

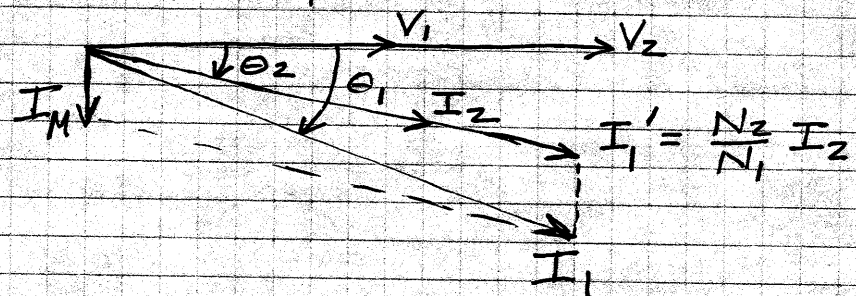
$$\therefore I_1' = \frac{N_2}{N_1} I_2$$



I_2 phase θ_2 depends on Z_2

$$P_{IN} = I_1 V_1 \cos \theta_1$$

Exercise 2.1.5

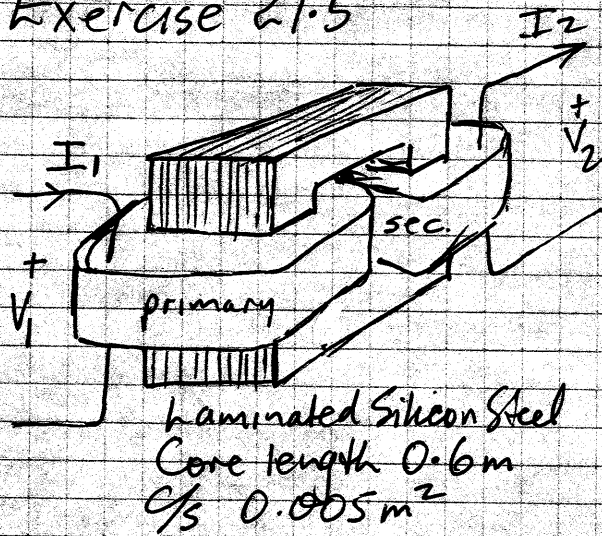

$N_1 = 200$ $N_2 = 800$ Find I_1 for (a) OC secondary
 $V_1 = 200V_{rms}$ at 60Hz (b) Secondary load = 200Ω

(a) Magnetizing flux $= \Phi_m = \frac{\sqrt{2} E_1}{N_1 \omega} = \frac{\sqrt{2} 200}{200 \times 2\pi \times 60}$

$= 3.75 \times 10^{-3} \text{ Wb}$
 $B_m = \Phi_m / A = 3.75 \times 10^{-3} / 5 \times 10^{-3} = 0.75 \text{ T}$

For Si steel $B_m = 0.75 \text{ T} \Rightarrow H = 130 \text{ A.t/m}$


Magnetizing current $I_m = \frac{1}{\sqrt{2}} \frac{F}{N_1} = \frac{Hl}{\sqrt{2} N_1} = \frac{130 \times 0.6}{\sqrt{2} \times 200}$
 $= 0.276 \text{ A} = 276 \text{ mA}$

(b) Assuming $V_2 = \frac{N_2}{N_1} V_1 = \frac{800}{200} 200 = 800 \text{ V}$

With $R_L = 200 \Omega$ connected $I_2 = V_2 / R_2 = 800 / 200 = 4 \text{ A}$

$\therefore I_1' = \frac{N_2}{N_1} I_2 = \frac{800}{200} \times 4 = 16 \text{ A}$

LINEAR MODELS

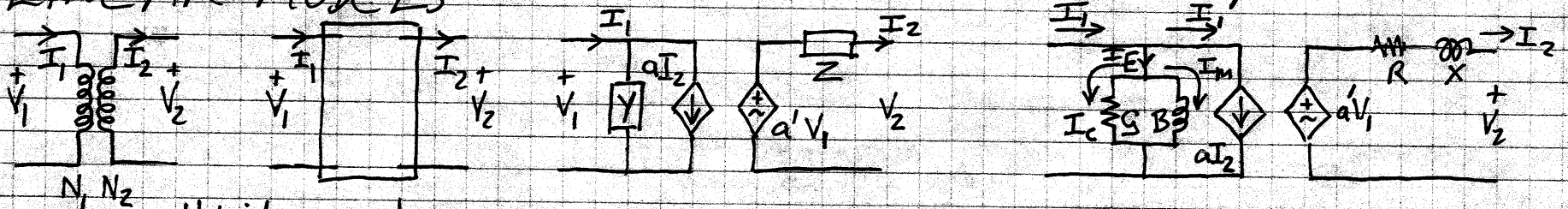


Hybrid parameters $I_1 = YV_1 + aI_2$
 $V_2 = a'V_1 - ZI_2$

$I_2 = 0 \rightarrow I_1 = I_E \therefore Y = I_E / V_1 = \frac{I_C}{V_1} - j \frac{I_M}{V_1}$
 $= G + jB$
 $a' = N_2 / N_1$

$I_2 \neq 0$ $I_1' = \frac{N_2}{N_1} I_2$ added to I_1 . $\therefore a = \frac{N_2}{N_1} = a'$
 $R \rightarrow$ losses in both windings, $L \rightarrow$ leakage inductance

OPEN & SHORT-CIRCUIT TESTING

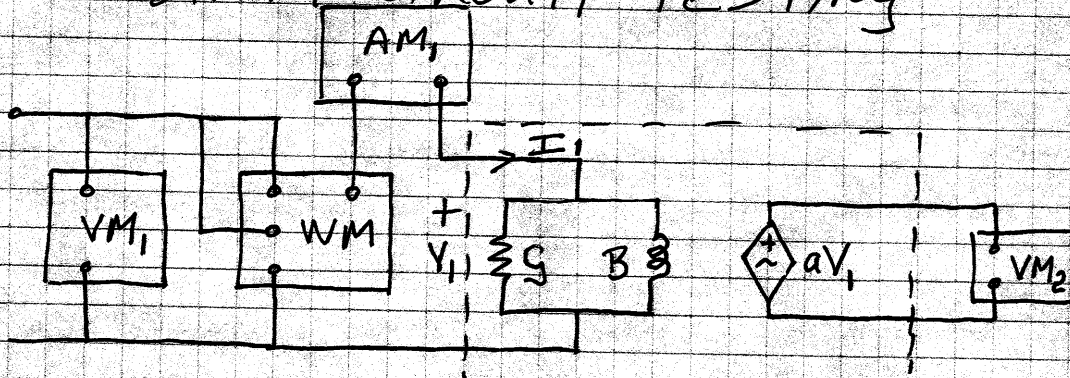


Open circuit — R, X in secondary no effect

$$I_1' = aI_2 = 0$$

$$I_1 = I_E$$

core loss
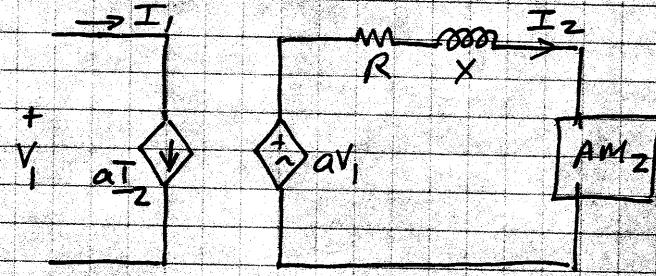
$$a = \frac{V_{20}}{V_{10}}, \quad G = \frac{P_{oc}}{V_{10}^2} \quad \& \quad Y = \frac{I_{10}}{V_{10}} \therefore B = -\sqrt{Y^2 - G^2}$$



Short circuit

V_1 very small $\therefore Y$ negligible

Copper loss

$$P_{sc} = I_{2s}^2 R = \left(\frac{I_{1s}}{a}\right)^2 R$$

$$\therefore R = a^2 \frac{P_{sc}}{I_{1s}^2}$$

$$Z = \frac{aV_{1s}}{I_{2s}} = a^2 \frac{V_{1s}}{I_{1s}} \quad \& \quad X = \sqrt{Z^2 - R^2}$$

(AM2 unnecessary, but useful check)

Exercise 2.1.6

Open circuit: $V_1 = 1000V, V_2 = 250V, I_1 = 0.3A, P = 20W$
 Short circuit: $I_2 = 40A, V_1 = 128V, P = 100W$

$$OC \begin{cases} a = V_{20}/V_{10} = 250/1000 = 1/4 \\ Y = I_{10}/V_{10} = 0.3/1000 = 0.3 \text{ ms} \\ \quad = 300 \mu\text{s} \end{cases}$$

$$G = \frac{P_{oc}}{V_{10}^2} = \frac{20}{1000^2} = 20 \mu\text{s}$$

$$B = -\sqrt{Y^2 - G^2} = -\sqrt{300^2 - 20^2} \cdot 10^{-6} \approx -300 \mu\text{s}$$

$$R = a^2 P_{sc} / I_{1s}^2 = \frac{1}{16} \frac{100}{(40 \times \frac{1}{4})^2} = \frac{1}{16} \Omega$$

$$X = \sqrt{Z^2 - R^2} = \sqrt{\left(a^2 \frac{V_{1s}}{I_{1s}}\right)^2 - R^2} = \sqrt{\left(\frac{1}{16} \cdot \frac{128}{10}\right)^2 - \left(\frac{1}{16}\right)^2}$$

$$= 0.8 \Omega$$

TRANSFORMER MISCELLANEOUS


(a) Ratings e.g. 4400:220V 60Hz 10KVA

Turns ratio $\approx 20:1$ Either side primary

10KVA rated "full" load \rightarrow heating due to currents
 \therefore KVA rated rather than power KW

At 60Hz, specified voltages bring magnetization up to knee of magnetization curve, but losses not excessive

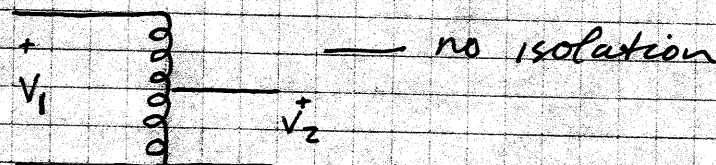(b) Autotransformer — some turns carry both primary & secondary currents



$$(c) \text{ Efficiency} = \frac{\text{output power}}{\text{input power}} = \frac{\text{output}}{\text{output} + \text{losses}} = 1 - \frac{\text{losses}}{\text{input}}$$

$$(d) \text{ Voltage regulation} = \frac{\text{No-load} - \text{full-load voltages}}{\text{full load voltage}}$$

ASSIGNMENT #8

Part A

Problems 21.5, 21.16, 21.35