
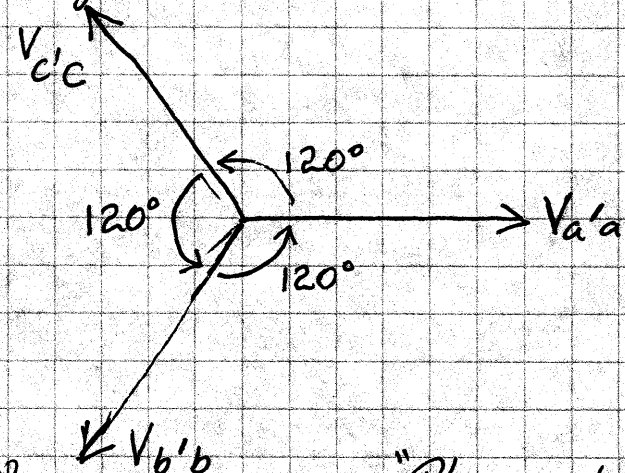


ECE 241 Lecture 17 THREE PHASE CIRCUITS

3- ϕ Generation Figs 7.25/26

3 windings on armature 120° apart.

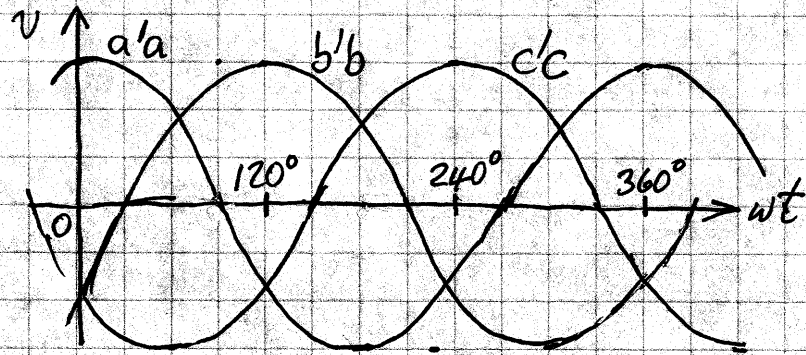

$$V_{a'a} = \sqrt{2} V \cos \omega t$$

$$V_{b'b} = \sqrt{2} V \cos (\omega t - 120^\circ)$$



$$V_{c'c} = \sqrt{2} V \cos (\omega t - 240^\circ)$$

$$V_{a'a} = V \angle 0^\circ$$

$$V_{b'b} = V \angle -120^\circ$$



$$V_{c'c} = V \angle -240^\circ$$

"Phase rotation" is abc

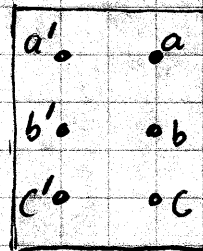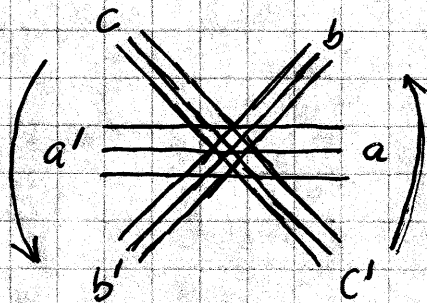

One can connect single-phase 120V loads across each phase a'a, etc. But needs 6 wires to supply multiple loads. Y & Δ connections help with 3 wires.

DELTA CONNECTION

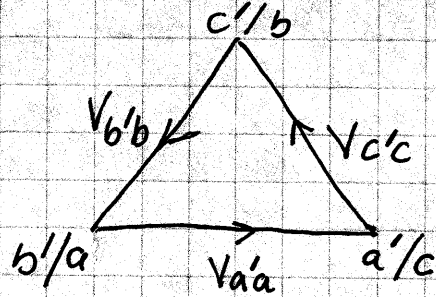
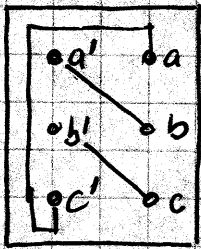


eg. $V_{a'b} = V_{a'a} + V_{c'c} + V_{b'b}$
 $= V_{a'a} + V_{b'b} + V_{c'c} = 0$

as expected since $V_{a'b} = 0$



3 single- ϕ wires; lab weightings

Alternative

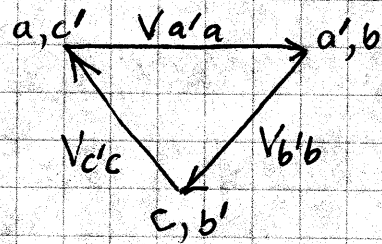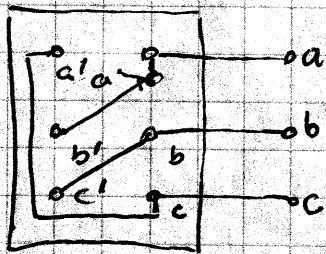

△ Typically used in residential areas


WYE CONNECTION

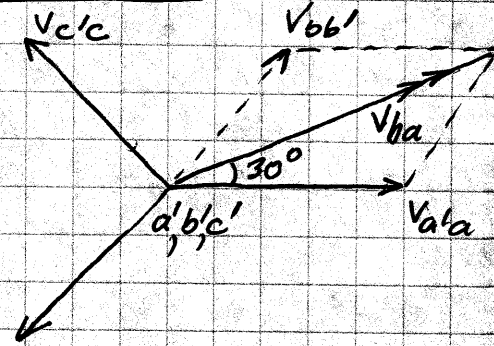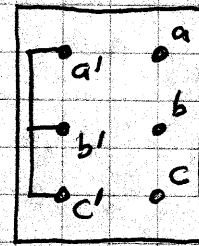

Line-to-line voltages: $V_{b'b}$
 $\hat{V}_{ba} = \hat{V}_{a'a} - V_{b'b} = V_{a'a} + V_{b'b'}$
 $= 2V_{a'a} \cos 30^\circ$
 $= \sqrt{3} V_{a'a} \angle 30^\circ$

In general, $V_{line} = \sqrt{3} V_{phase} \angle 30^\circ$

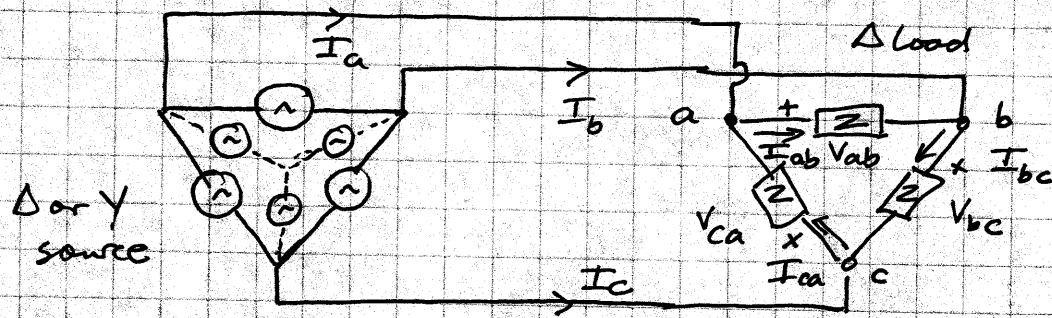DELTA CIRCUITS : Delta Load, Delta source



Balanced load

Take \tilde{V}_{ab} as phase reference

Δ "phase" voltages V_{ab}, V_{bc}, V_{ca} = "line" voltages

Phase currents
$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{V \angle 0^\circ}{Z \angle \theta_2} = \frac{V}{Z} \angle -\theta_2$$

$$I_{bc} = \frac{V_{bc}}{Z_{bc}} = \frac{V \angle -120^\circ}{Z \angle \theta_2} = \frac{V}{Z} \angle -120^\circ - \theta_2$$

$$I_{ca} = \frac{V_{ca}}{Z_{ca}} = \frac{V \angle -240^\circ}{Z \angle \theta_2} = \frac{V}{Z} \angle -240^\circ - \theta_2$$

Line currents \neq Phase currents


$$I_a = I_{ab} + I_{ac} = I_{ab} - I_{ca} \quad (\text{See fig.})$$

$$I_{ac} = -I_{ca}$$

$$\therefore I_a = 2I_{ab} \cos 30^\circ \angle -\theta_2 - 30^\circ$$

$$= \sqrt{3} I_{ab} \angle -30^\circ \quad \& \parallel I_b, I_c$$

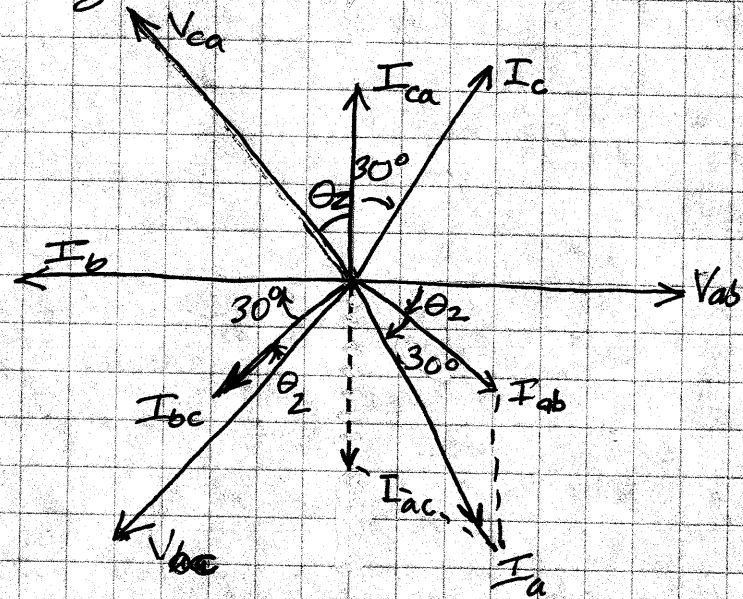So
$$I_{\text{line}} = \sqrt{3} I_{\text{phase}} \angle -30^\circ$$



3 ϕ POWER

Total power = Σ 3 equal phase powers

$$P_{\text{total}} = 3P_p = 3 \underbrace{V_p I_p}_{\substack{\text{Phase voltages and currents} \\ \uparrow}} \cos \theta \quad \uparrow \text{power factor of load}$$

Easier to measure ϕ line voltage, power, etc, rather than phase voltages

Note: θ is not the angle between line voltage and line current.

For Δ load, $V_l = V_p$ & $I_l = \sqrt{3} I_p$


$$\therefore P_{\Delta} = 3 V_p I_p \cos \theta = 3 V_l \frac{I_l}{\sqrt{3}} \cos \theta = \sqrt{3} V_l I_l \cos \theta$$

For Y load: $V_l = \sqrt{3} V_p$ & $I_l = I_p$

$$\text{So } P_Y = 3 V_p I_p \cos \theta = 3 \frac{V_l}{\sqrt{3}} I_l \cos \theta = \sqrt{3} V_l I_l \cos \theta$$

Power Measurement

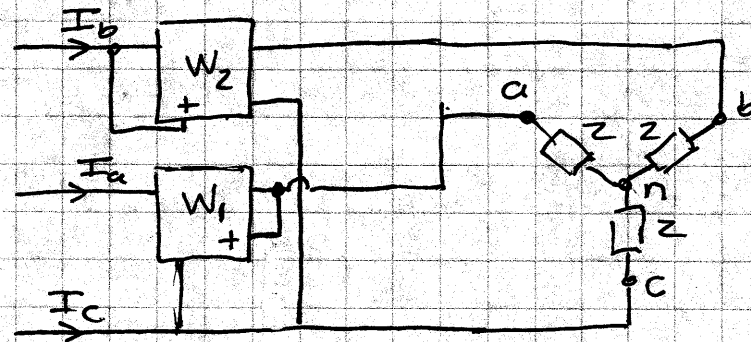Connect 3 wattmeters:
But define line C as reference $\therefore W_3$ wattmeter measures potential difference.



$$W_1 = I_a V_{ac} \cos \theta_1$$

$$W_2 = I_b V_{bc} \cos \theta_2$$

For numbers in Example 11
where $P_{\text{tot}} = 3420 \text{ W}$
 $W_1 + W_2 = 3420 \text{ W}$.

Hence, eliminate W_3 since senses zero voltage to ref.

Assignment 8 (c) P7.36 P7.40 P7.48