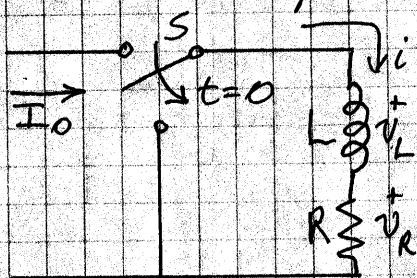


E241 Lecture 8 TRANSIENTS I (Chapter 4)

First Order Systems




Initially, I_0 in L, R
 $i(0) = I_0$

For $t > 0$

$$v_L + v_R = 0$$

$$L \frac{di}{dt} + iR = 0$$

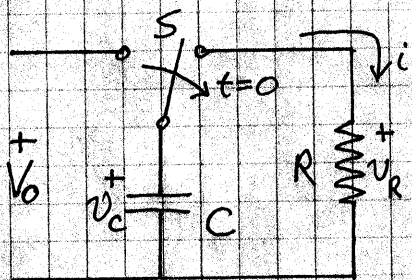


Initially V_0 across R, C
 $v_C(0) = v_R(0) = V_0$

For $t > 0$

$$v_C = -v_R$$

$$V_0 - \frac{1}{C} \int_0^t i dt = iR$$

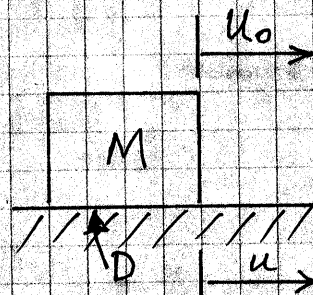

Initially, velocity u_0
 Remove force at $t=0$

For $t > 0$

$$M \frac{du}{dt} = -Du$$

Solutions:-

$$L \frac{di}{dt} + iR = 0$$

$$R \frac{di}{dt} + \frac{i}{C} = 0$$

$$M \frac{du}{dt} + Du = 0$$

Separate variables:

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\frac{di}{i} = -\frac{1}{RC} dt$$

$$\frac{du}{u} = -\frac{D}{M} dt$$

$$\int_{I_0}^i \frac{di}{i} = -\frac{R}{L} \int_0^t dt$$

$$\int_{V_0/R}^i \frac{di}{i} = -\frac{1}{RC} \int_0^t dt$$

$$\int_{u_0}^u \frac{du}{u} = -\frac{D}{M} \int_0^t dt$$

$$\ln i \Big|_{I_0}^i = -\frac{t}{(L/R)}$$

$$\ln i \Big|_{V_0/R}^i = -\frac{t}{RC}$$

$$\ln u \Big|_{u_0}^u = -\frac{t}{(M/D)}$$

$$i/I_0 = \exp\left(-\frac{t}{(L/R)}\right)$$

$$i/(V_0/R) = \exp\left(-\frac{t}{RC}\right)$$

$$u/u_0 = \exp\left(-\frac{t}{(M/D)}\right)$$

$$i(t) = I_0 \exp\left(-t/(L/R)\right)$$

$$i(t) = \frac{V_0}{R} \exp\left(-\frac{t}{RC}\right)$$

$$u(t) = u_0 \exp\left(-\frac{t}{(M/D)}\right)$$

Note text method — assumes solution of the form Ae^{st}

so for $L \frac{di}{dt} + Ri = 0$ & $i = Ae^{st}$

$$sL Ae^{st} + R Ae^{st} = 0$$

$$(R + sL) Ae^{st} = 0$$

so for $Ae^{st} \neq 0$, $s = -R/L$


and $i = Ae^{-\frac{R}{L}t}$

When $t = 0^+$ $i(0) = I_0 = A$

$$\therefore i(t) = I_0 \exp\left(-\frac{t}{L/R}\right)$$

(See text for RC example)

Exercise H.1

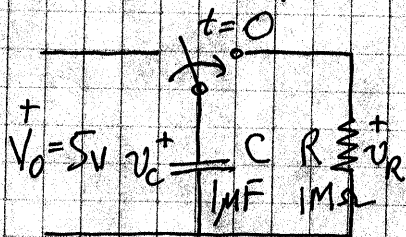

(a) Voltage $v_R(0^+) = V_0 = 5V$

(b) Hence $v_R(t) = V_0 \exp\left(-\frac{t}{RC}\right) = 5 \exp^{-t}$


$v_R(t) = \frac{V_0}{2}$ when $\exp^{-t} = 0.5$

i.e. at $t = \ln 2 = 0.693s$

Current $i(0.693) = \frac{V_0/2}{R} = \frac{2.5V}{1M\Omega} = 2.5\mu A$

[Energy stored in C dissipated in R.]

Exercise H.2

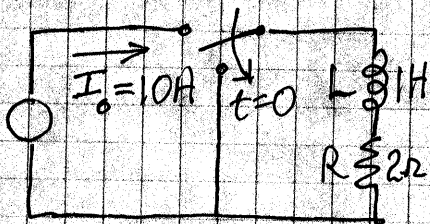

$$i(t) = I_0 \exp\left(-\frac{t}{L/R}\right) = 10 \exp^{-2t}$$

At $t = 1s$, $i(1) = 10 \exp^{-2} = 1.35A$

At $t = 10s$, $i(10) = 10 \exp^{-20} = 20.6 \times 10^{-9} A = 20.6 nA$

Procedure for solution:

1. Write governing equation (Kirchoff)
2. Convert to homogeneous differential equation
3. Assume a general exponential solution
4. Find exponents from homogeneous equation
5. Find coefficients from initial conditions.

Note: $\exp -\lambda$ where λ is a constant.


So — solutions $\exp -\frac{t}{RC}$, $\exp -\frac{t}{(L/R)}$, $\exp -\frac{t}{(M/D)}$

are of the form $\exp -\frac{t}{\tau}$

where τ is the "time constant"

e.g. $[RC] = [R][C] = \frac{[V]}{[I]} \cdot \frac{[I]}{[V]/[T]} = [T]$

Second Order Systems (RLC)

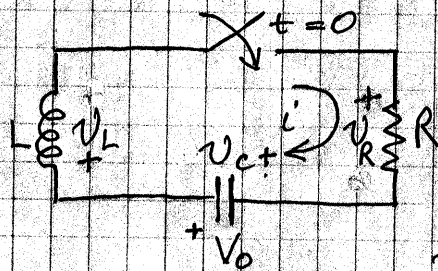

$$\begin{aligned}\sum v &= 0 = v_R + v_C + v_L \\ &= iR + \frac{1}{C} \int_0^t i dt - V_0 + L \frac{di}{dt}\end{aligned}$$

Differentiate: —

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

Assume a solution of the form $i = Ae^{st}$

$$\therefore s^2 LAe^{st} + sRAe^{st} + \frac{1}{C} Ae^{st} = 0$$

which is (for $Ae^{st} \neq 0$) the Characteristic Equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$


with roots $s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$

Note that if both $i_1 = A_1 e^{s_1 t}$ and $i_2 = A_2 e^{s_2 t}$ satisfy the differential equation, then so does

$$i = i_1 + i_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

where s_1, s_2 found as above, A_1, A_2 from initial conditions.

Case 1: Roots s_1, s_2 real & distinct $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$

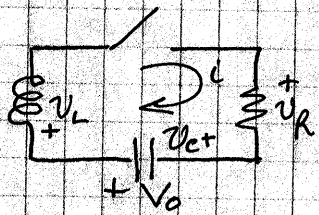

Exercise 4-5: $L=1H$ $C=10F$ $R=4\Omega$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\frac{4}{2 \times 1} \pm \sqrt{\left(\frac{4}{2 \times 1}\right)^2 - \frac{1}{1 \times 10}}$$

$$= -2 \pm \sqrt{3.9} = -2 \pm 1.975$$

$$= -3.975, -0.025$$

$$\therefore i = A_1 e^{-3.975t} + A_2 e^{-0.025t}$$

At $t=0^+$, $i=0 \quad \therefore A_1 + A_2 = 0$


and if $i=0$, $v_R=0 \quad \therefore v_L = -v_c = -(-V_0)$

$$\therefore v_L(0) = L \left. \frac{di}{dt} \right|_{t=0} = L(-3.975A_1 - 0.025A_2) = V_0$$

$$\therefore A_2 + 59A_1 = -V_0/L$$

$$A_2 = -A_1 \quad \rightarrow \quad 58A_1 = -V_0/L \quad A_1 = -V_0/58$$
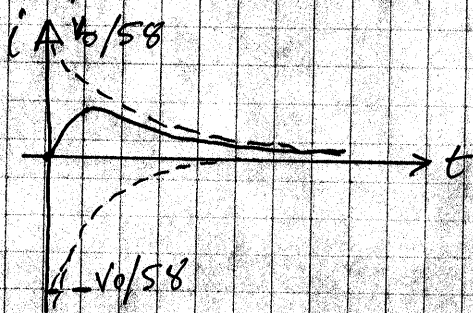
$$A_1 = -A_2 \quad \rightarrow \quad -58A_2 = -V_0/L \quad A_2 = +V_0/58$$



Roots real & distinct when $2\frac{L}{R} < \frac{RC}{2}$

— always negative
(decaying exponentials)

Over-damped system $R^2 > 4\frac{L}{C}$

Case 2: Roots s_1, s_2 complex when $R^2 < 4\frac{L}{C}$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Write $s_1, s_2 = -\alpha \pm j\omega$ where $\alpha = R/2L$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{4L^2} = \omega_n^2 - \alpha^2$$

so $i = A_1 e^{(\alpha + j\omega)t} + A_2 e^{(-\alpha - j\omega)t}$

$$= e^{-\alpha t} (A_1 e^{j\omega t} + A_2 e^{-j\omega t})$$

where $\omega_n^2 = 1/LC$

$$= e^{-\alpha t} (A_1 [\cos \omega t + j \sin \omega t] + A_2 [\cos \omega t - j \sin \omega t])$$

$$= e^{-\alpha t} [(A_1 + A_2) \cos \omega t + j(A_1 - A_2) \sin \omega t]$$

$(A_1 + A_2)$ and $j(A_1 - A_2)$ must be real for real currents,

so write $A_1 + A_2 = B_1$, $j(A_1 - A_2) = B_2$, for

$$i = e^{-\alpha t} (B_1 \cos \omega t + B_2 \sin \omega t)$$

$$= A e^{-\alpha t} \sin(\omega t + \theta)$$

Damped sinusoid


Examples 3 & 4: $L=1H, C=1/17F, R=2\Omega$

$$s_1, s_2 = -\frac{2}{2 \times 1} \pm \sqrt{\left(\frac{2}{2 \times 1}\right)^2 - \frac{1}{1 \times 1/17}} = -1 \pm \sqrt{1 - 17} = -1 \pm \sqrt{-16}$$

$$= -1 \pm j4$$

\therefore Response is $e^{-t} (A_1 e^{j4t} + A_2 e^{-j4t})$

$$= A e^{-t} \sin(\omega t + \theta)$$

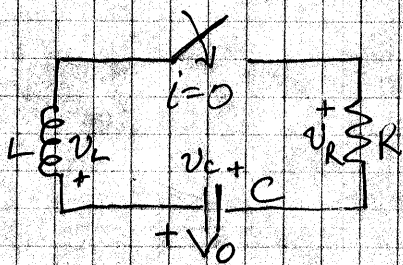

At $t=0^+$ $i=0 = A \sin \theta$

$\therefore \sin \theta = 0, \theta = 0$ if $A \neq 0$

$L \frac{di}{dt} = V_0 \therefore V_0 = A e^{-t} \omega \cos(\omega t + \theta) - A e^{-t} \sin(\omega t + \theta)$

$= 4A \therefore A = V_0/4$

$i = \frac{V_0}{4} e^{-t} \sin 4t$ with $T = \frac{1}{f} = \frac{2\pi}{\omega} = \frac{2\pi}{4} = \frac{\pi}{2} = 1.57 \text{ sec.}$

Case 3: Roots real and equal $s_1, s_2 = -\frac{R}{2L}$ when $R = \frac{4}{LC}$
 $= S$

$$i = A_1 e^{st} + A_2 t \cdot e^{st}$$

Exercise 4.7 $R = 2\Omega$ $L = 0.5H$ $C = 0.5F$

$$(a) s_1, s_2 = -\frac{2}{2 \times 0.5} \pm \sqrt{\left(\frac{2}{2 \times 0.5}\right)^2 - \frac{1}{0.5 \times 0.5}} = -2$$

$$(b) \therefore i = (A_1 + A_2 t) e^{-2t}$$

$$(c) \text{ At } t = 0^+ \quad i(0^+) = 0 = A_1$$


$$L \frac{di}{dt} = V_0 = L \left[A_2 t e^{-2t} (-2) + A_2 e^{-2t} \right]$$

$$\underset{t=0}{=} L A_2 \quad \therefore A_2 = V_0 / L$$


$$\therefore i = 2V_0 t e^{-2t}$$

Roots in the complex plane

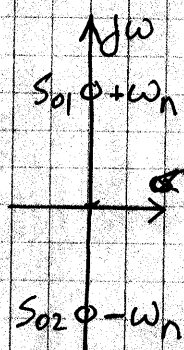
$$R=0 \quad \therefore s_1, s_2 = \pm \sqrt{-1/LC} = \pm j\omega_n$$




$R=0$
Roots imag.

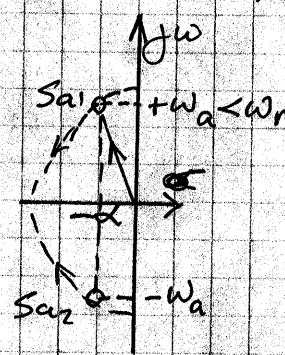

$R=R_a$
Roots complex

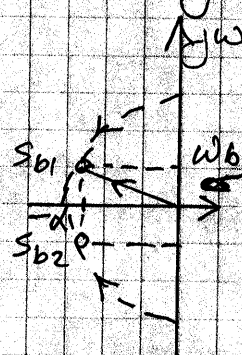

$R=R_b > R_a$
Roots complex

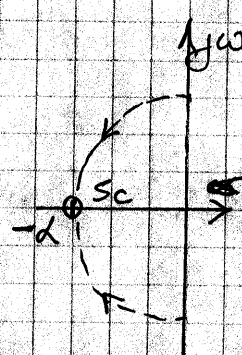


$R=R_c$
Roots equal

$$\text{Arc radius} = (\alpha^2 + \omega^2)^{1/2}$$


$$= \left[\left(-\frac{R}{2L}\right)^2 + \left(\frac{1}{LC} - \frac{R^2}{4L^2}\right) \right]^{1/2}$$

$$= \frac{1}{\omega_n LC} = \omega_n$$

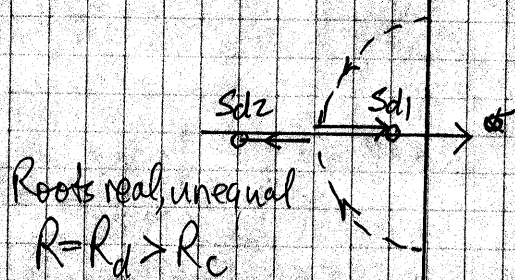

Roots real, unequal
 $R=R_d > R_c$

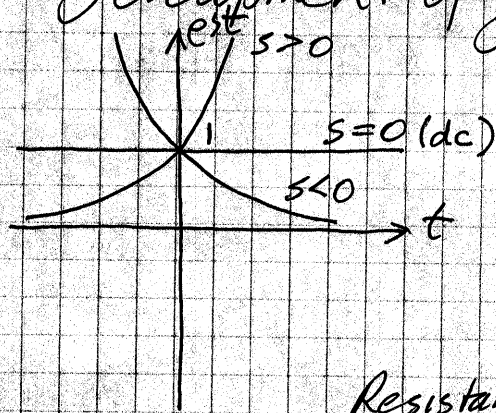Development of generalized impedance concepts



If $i = I_0 e^{st}$ $\frac{di}{dt} = s I_0 e^{st} = si$


$v = V_0 e^{st}$ $\frac{dv}{dt} = s V_0 e^{st} = sv$

Resistance: Define $Z_R = \frac{v}{i} = \frac{iR}{i} = R$ ohms

Inductance: $v = L \frac{di}{dt} = sLi$ $Z_L = \frac{v}{i} = \frac{sLi}{i} = sL$ ohms

Capacitance: $i = C \frac{dv}{dt}$ $Z_C = \frac{v}{i} = \frac{v}{sCv} = \frac{1}{sC}$ ohms

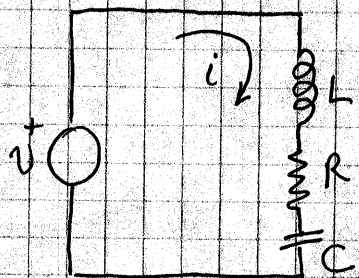Works for waveforms expressible as exponentials, eg. sinusoids



$$v = L \frac{di}{dt} + iR + \frac{1}{C} \int i dt$$


For $i = I_0 e^{st}$

$$v = sLi + Ri + \frac{1}{sC} i$$

$$\& Z = \frac{v}{i} = sL + R + \frac{1}{sC} = Z_L + Z_R + Z_C$$

See Examples 5, 6, & 7

Exercise 4.9

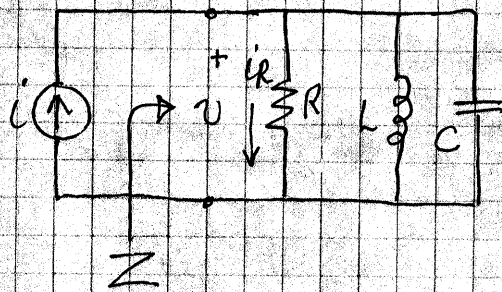

$i = e^{-5t} A$ $L = 1H$ $C = 1F$ $R = 1\Omega$


Find Z , v , i_R

$$Z_R = R \quad Z_L = sL = s = -5 \quad Z_C = \frac{1}{sC} = \frac{1}{s} = \frac{-1}{5}$$

$$Z = \left(\frac{1}{R} + \frac{1}{s} + s \right)^{-1} = [1 + (-0.2) + (-5)]^{-1} = \frac{1}{-4.2} = -0.238 \Omega$$

$\therefore v = iZ = -0.238 e^{-5t} V$ & $i_R = v/R = -0.238 e^{-5t} A$

Exercise 4.10

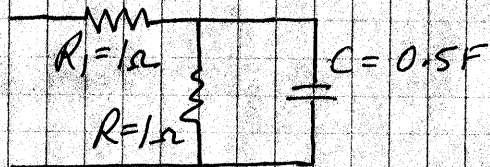

Plot $Z(s)$ for real s

$$Z(s) = R_1 + R \parallel \frac{1}{sC} = R_1 + \frac{R \frac{1}{sC}}{R + \frac{1}{sC}} = R_1 + \frac{R}{1 + sRC}$$


$$= \frac{R_1(1 + sRC) + R}{1 + sRC} = \frac{(R + R_1) + sRR_1C}{1 + sRC}$$

$$= (R + R_1) \frac{1 + sR_p C}{1 + sRC} \quad \text{where } R_p = \frac{R R_1}{R + R_1} = R \parallel R_1 = 0.5 \Omega$$

When $s = 0$ $Z(0) = R + R_1 = 2$

$$Z(s) = 0 \quad 1 + sR_p C = 0 \quad s = -\frac{1}{R_p C} = -\frac{1}{(0.5)(0.5)} = -4$$

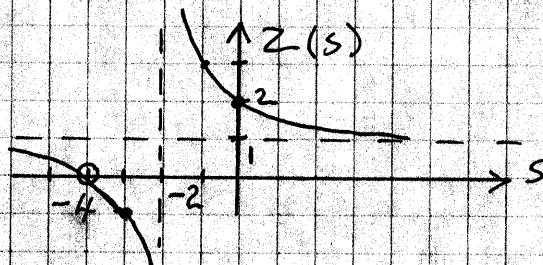As $s \rightarrow \pm \infty$ $Z(s) \rightarrow \frac{(R + R_1) s R_p C}{sRC} = \frac{(R + R_1) R_1 R}{R(R_1 + R)} = R_1 = 1$



$$Z(s) \rightarrow \infty \text{ at } s = -\frac{1}{RC} = -2$$

For $s = -1$ $Z(-1) = 2 \frac{1 + 0.25(-1)}{1 + 0.5(-1)} = 2 \frac{1 - 0.25}{1 - 0.5} = 3$

For $s = -3$ $Z(-3) = 2 \frac{1 - 0.75}{1 - 1.5} = -1$

Exercise 4.11 (a) Plot $Z(s)$ for imaginary $s = \pm j\omega$
 (b) Plot the pole-zero diagram


$$Z(s) = 2 \frac{1 + s/4}{1 + s/2} = \frac{4 + s}{2 + s}$$

$$\begin{matrix} s=0 & \rightarrow & 2 \\ s \rightarrow \infty & \rightarrow & 1 \end{matrix}$$


$$\begin{matrix} \pm j & \rightarrow & \frac{4 \pm j}{2 \pm j} & |Z| = 1.844 \end{matrix}$$

$$\begin{matrix} \pm 2j & \rightarrow & \frac{2 \pm j}{1 \pm j} & |Z| = 1.58 \end{matrix}$$

$$\begin{matrix} \pm 3j & \rightarrow & \frac{4 \pm 3j}{2 \pm 3j} & |Z| = 1.154 \end{matrix}$$

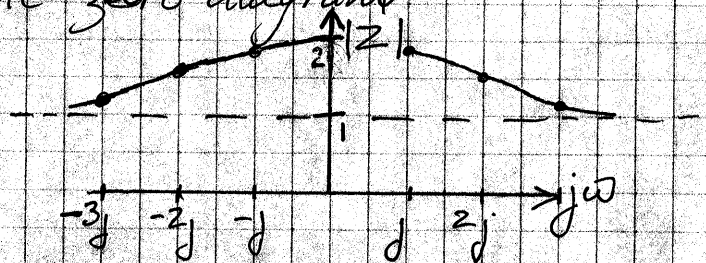


For complex s
 see Fig 4.16 (c) p 129

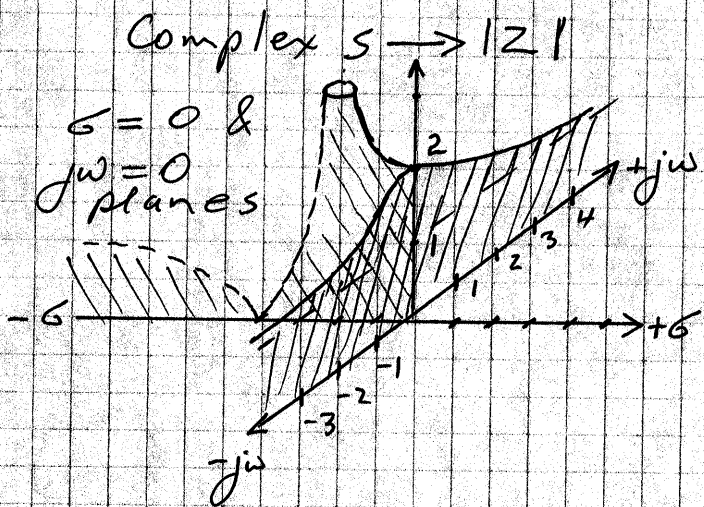

3-D surface for complex s
Hard to draw/visualize


Pole-zero diagram
on Complex plane.
Show where $|Z| \rightarrow \infty$
 $|Z| \rightarrow 0$

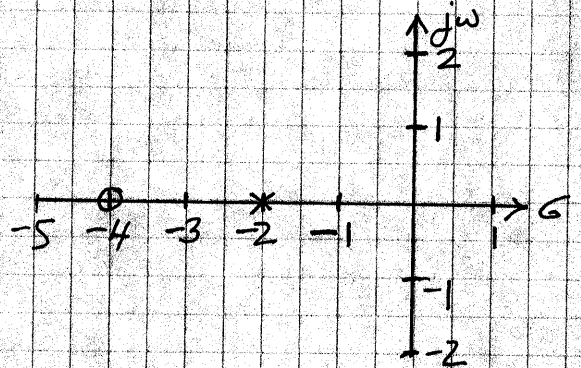

In this case: Pole at $\sigma = -2$
Zero at $\sigma = -4$

Exercise 4.12.

$v_c(0) = V_0$ Find $i_c(t)$ for $t > 0$

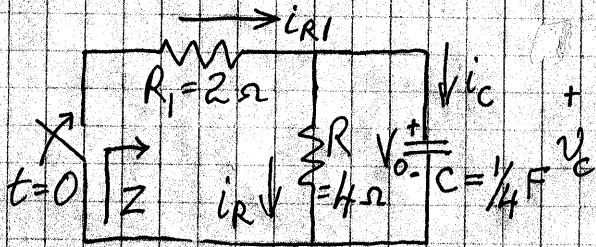


$$Z(s) = R_1 + \frac{R \frac{1}{sC}}{R + \frac{1}{sC}} = R_s \frac{1 + sR_p C}{1 + sRC}$$

where $R_s = R_1 + R = 6 \Omega$
 $R_p = R_1 \parallel R = \frac{4}{3} \Omega$

$$\therefore Z(s) = 6 \frac{1 + s/3}{1 + s} = 2 \frac{3 + s}{1 + s}$$

Pole when $|Z| \rightarrow \infty$
ie. when $s = -1$

Zero when $|Z| \rightarrow 0$
ie. when $s = -3$

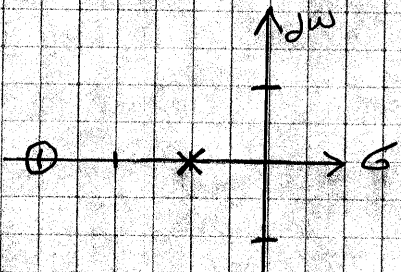

Concept of a zero where $|Z| = 0$

Can have current with no forcing voltage \rightarrow natural current response (roots of characteristic equation)

\therefore natural response defined by $s = -3$

$$i_{R1} = I_1 e^{-3t} \text{ \& at } t = 0^+, I_1 = \frac{V_0}{R_1}$$

Hence $i_{R1} = -\frac{V_0}{R_1} e^{-3t}$

Current divider: $i_c = \frac{R}{R + 1/sC} i_{R1} = \frac{4}{4 + 1/(1/4)} i_{R1} = \frac{3}{2} i_{R1}$

$$\therefore i_c = -\frac{3}{2} \frac{V_0}{2} e^{-3t} = -0.75 V_0 e^{-3t}, v_c = -v_{R1} = -i_{R1} R_1 = +V_0 e^{-3t}$$

In general, any network impedance can be reduced to the form:

$$Z(s) = K \frac{s^N + \dots + k_2 s^2 + k_1 s + k_0}{s^M + \dots + b_2 s^2 + b_1 s + b_0}$$

$$= K \frac{(s-s_1)(s-s_2)\dots(s-s_n)}{(s-s_a)(s-s_b)\dots(s-s_m)}$$

where $s = s_1, s_2, \dots, s_n$ are zeros

$s = s_a, s_b, \dots, s_m$ are poles

If we have the network, $Z(s)$ can be found and poles/zeros identified.

If we have the poles & zeros, a network can be found (except K undefined)

Exercise 4.14 $Z(s) = \frac{(s^2 + 4s + 8)(s+1)}{s^2 + 2s + 5}$

$$s_1, s_2 = \frac{-4 \pm \sqrt{4^2 - 4 \times 8}}{2} = -2 \pm j2$$

$$s_a, s_b = \frac{-2 \pm \sqrt{2^2 - 4 \times 5}}{2} = -1 \pm j2$$

Zeros: $-1, -2+j2, -2-j2$ Poles: $-1+j2, -1-j2$


Note: All complex poles/zeros appear as conjugate pairs

Admittance: $Y = \frac{i}{v} = \frac{1}{Z}$

$$Y_R = \frac{1}{R} = G$$

$$Y_L = \frac{1}{sL}$$

$$Y_C = sC$$

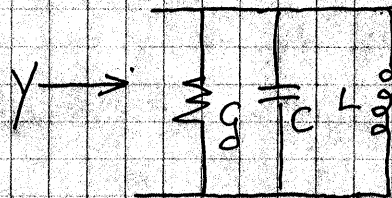

$$Y(s) = G + sC + \frac{1}{sL}$$

In general:

$$Y(s) = \frac{1}{Z(s)} = \frac{1}{K} \frac{(s-s_a)(s-s_b)\dots(s-s_m)}{(s-s_1)(s-s_2)\dots(s-s_n)}$$

Using poles/zeros: ① Find poles & zeros from $Z(s)$ or $Y(s)$; plot pole/zero diag.
 Natural behavior:
 ② For SC terminals, $i = I_1 e^{s_1 t} + I_2 e^{s_2 t} + \dots + I_n e^{s_n t}$ s_1, s_2, \dots, s_n Z zeros
 For OC terminals, $v = V_1 e^{s_a t} + V_2 e^{s_b t} + \dots + V_m e^{s_m t}$ s_a, s_b, \dots, s_m Y poles
 ③ Coeffs from initial conditions