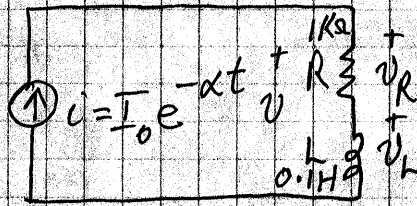


ECE 241 Lecture 9 Chapter 5 Forced Response

Response to exponential forcing function:

Exercise 5.1



(a) Circuit time constant $\tau = L/R = 0.1/10^3 = 0.1\text{ms}$

(b) v for $i = 2 e^{-5000t}$ A $v = iR + L \frac{di}{dt}$
 $v = 10^3 2 e^{-5000t} + 0.1 (2 e^{-5000t}) (-5000)$
 $= 1000 e^{-5000t}$

(c) v for $i = 2 e^{-20,000t} \rightarrow v = 10^3 2 e^{-20,000t} + 0.1 (2 e^{-20,000t}) (-20,000)$
 $= -2000 e^{-20,000t}$

DC Response

$s = 0 \quad i = I_0 e^{0t} = I_0 \leftarrow \text{cap's} \rightarrow \text{DC}$

$Z_R(0) = R$


$Z_L(0) = 0$
(= sL)

$Z_C(0) = \infty$
(= 1/sC)

s.c. at DC


o.c. at DC

Exponential Forcing Function

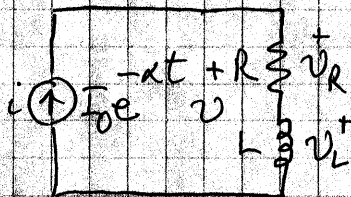

$v = v_R + v_L = (R - \alpha L) I_0 e^{-\alpha t}$

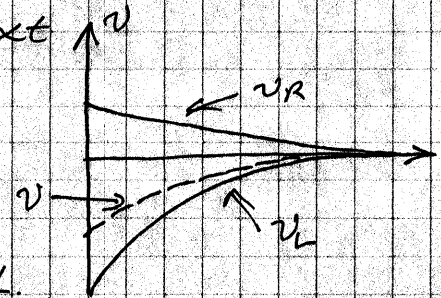
Voltage response also exponential of time constant (shape) as the forcing function



Note: +ve $i \rightarrow$ -ve v due to inductance L . (opposes change in current)

Note: if $\alpha = R/L$ i.e. forcing time constant = circuit time constant then $v = 0$

Exercise 5.2

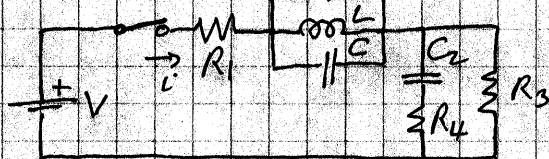

$V = 5\text{V} \quad R_1 = R_2 = 1\text{k}\Omega$

$R_3 = R_4 = 4\text{k}\Omega$

$L = 1\text{mH}$

$C_1 = C_2 = 10\mu\text{F}$

S closed for long time

(a) $i = V / (R_1 + R_3) = 5\text{V} / 5\text{k}\Omega = 1\text{mA}$

(b) Voltage across resistors:

$v_{R1} = i \times 1\text{k} = 1\text{V}$

$v_{R2} = 0$ (L is s.c.)

$v_{R3} = i \times 4\text{k} = 4\text{V}$


$v_{R4} = 0$ (C is o.c.)

SINUSOIDS: PHASOR REPRESENTATION

A. $\mathbf{W} = a + jb$
 = $M(\cos\theta + j\sin\theta)$
 = $M e^{j\theta}$ (Euler's theorem)
 = $M \angle \theta$

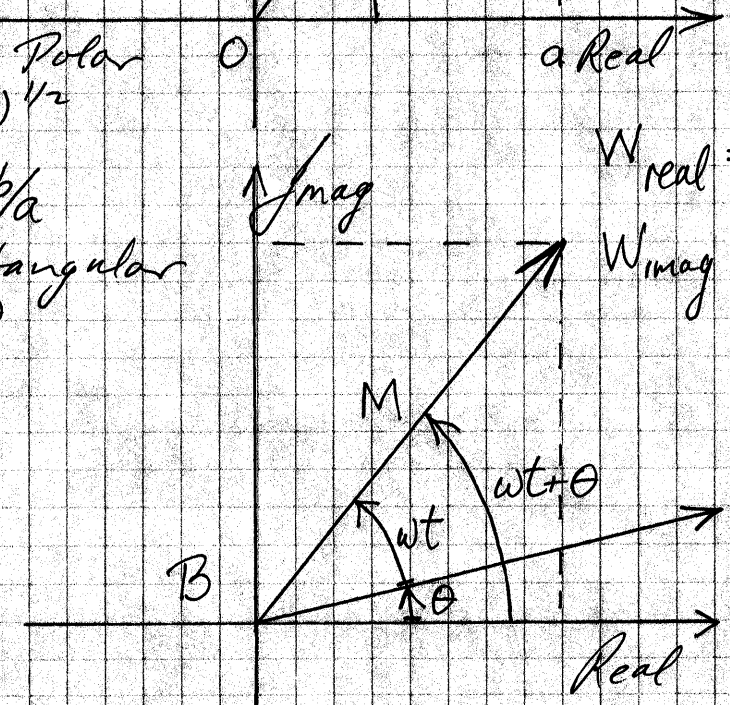B. Rotating vector
 angular velocity ω
 ie. $\theta \rightarrow \omega t + \theta$
 $W(t) = M e^{j(\omega t + \theta)}$

Rectangular \rightarrow Polar
 $M = (a^2 + b^2)^{1/2}$
 $\theta = \arctan b/a$
 Polar \rightarrow Rectangular
 $a = M \cos \theta$
 $b = M \sin \theta$



$W_{real} = M \cos(\omega t + \theta)$
 $W_{imag} = M \sin(\omega t + \theta)$

Represent sinusoids by W_{real} (or W_{imag})

Exercise 5.4

(a) $W_1 = 5 + j5$ $W_2 = 5 - j5$ convert to polar
 $M_1 = (5^2 + 5^2)^{1/2} = 5\sqrt{2}$ $M_2 = (5^2 + (-5)^2)^{1/2} = 5\sqrt{2}$
 $\theta_1 = \arctan 5/5 = \pi/4$ $\theta_2 = \arctan \frac{-5}{5} = -\pi/4$
 $\therefore W_1 = 5\sqrt{2} e^{j\pi/4}$ $W_2 = 5\sqrt{2} e^{-j\pi/4}$

(b) Convert $W_3 = e^{j\pi/3}$ $W_4 = e^{j4\pi/3}$ to rectangular
 $a_3 = 1 \cos \pi/3 = 0.5$ $a_4 = 1 \cos \frac{4\pi}{3} = -\cos \pi/3 = -0.5$
 $b_3 = 1 \sin \pi/3 = \sqrt{3}/2$ $b_4 = 1 \sin \frac{4\pi}{3} = -\sin \pi/3 = -0.866$
 $\therefore W_3 = 0.5 + j0.866$ $\therefore W_4 = -0.5 - j0.866$

For $v(t) = V_m \cos(\omega t + \theta) = \sqrt{2} V \cos(\omega t + \theta)$

\swarrow peak \swarrow rms

$$= \operatorname{Re} \{ V_m e^{j(\omega t + \theta)} \} = \operatorname{Re} \{ \sqrt{2} (V e^{j\theta}) e^{j\omega t} \}$$

\swarrow "Phasor" $V = V e^{j\theta}$
 \swarrow vector

V is a "transform" of $v(t)$
 $e^{j\omega t}$ is common to all terms
 and can be removed for calculation
 with the understanding that it can be restored later.

Exercise 5.5: For $v_1(t) = \operatorname{Re} \{ 5 e^{j(100\pi t + \pi/4)} \}$ & $v_2(t) = \operatorname{Re} \{ 10 e^{j(100\pi t + \pi/2)} \}$

(a) Effective values: $V_{eff1} = \frac{5}{\sqrt{2}} = 3.54 \text{ V}$ $V_{eff2} = \frac{10}{\sqrt{2}} = 7.07 \text{ V}$

(b) Rectangular forms of phasors $V e^{j\theta}$

$$V_1 = 3.54 \cos \pi/4 + j 3.54 \sin \pi/4 = 2.5 + j 2.5$$

$$V_2 = 7.07 \cos 1/2 + j 7.07 \sin 1/2 = 2.5 + j 6.6$$

Exercise 5.6: Represent $i = 5 \sin(100t + 120^\circ)$ as a phasor

$$I = \frac{5}{\sqrt{2}} \angle 30^\circ = 3.54 \angle 30^\circ = 3.54 e^{j\pi/6}$$

$$= 5 \cos(100t + 120^\circ - 90^\circ) = 5 \cos(100t + 30^\circ)$$


Exercise 5.7:

$$v_1 = 150 \sqrt{2} \cos(377t - \pi/6)$$

$$\therefore V_1 = 130 - j 75$$

$$V_2 = 200 \angle 130.5^\circ = 200(\cos 130.5^\circ + j \sin 130.5^\circ)$$

$$= -130 + j 152$$

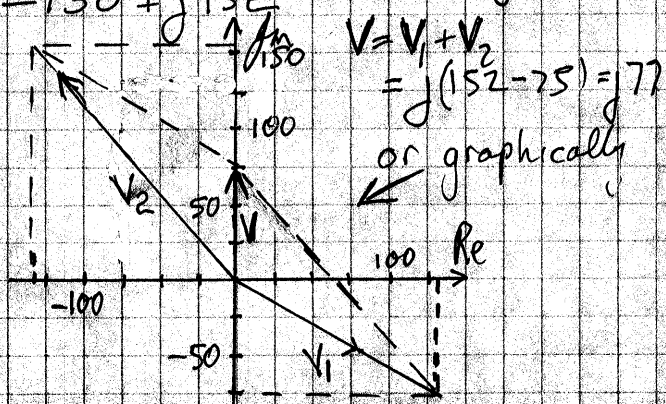

Exercise 5.8: $\begin{cases} i_1 = 10\sqrt{2} \cos(\omega t + 135^\circ) \\ i_2 = 6\sqrt{2} \cos(\omega t - 60^\circ) \end{cases}$

(a) As phasors $I_1 = 10 \angle 135^\circ$ $I_2 = 6 \angle -60^\circ$

(b) $I_1 + I_2$ graphically


(c) $I_1 + I_2$

$$= 10 \cos 135^\circ + j \sin 135^\circ + 6 \cos -60^\circ + j \sin -60^\circ$$

$$= -7.07 + j 7.07 + 3 - j 5.2$$

$$= -4.07 + j 1.87$$

$$= 4.48 \angle 155.3^\circ$$

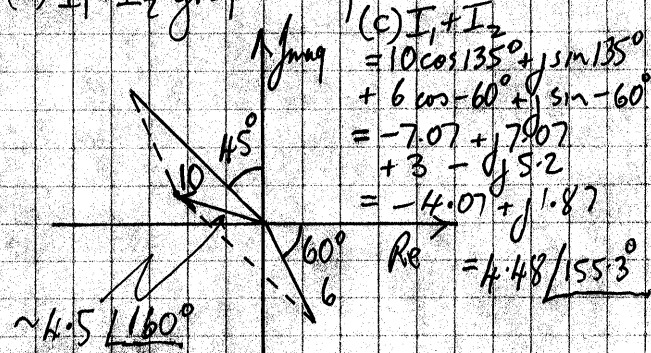

AC CIRCUIT ANALYSIS

Assume "AC" is sinusoidal, unless stated otherwise.

Sinusoidal \leftrightarrow exponential \leftrightarrow phasor representations

Current $i = \sqrt{2} I \cos \omega t = I \angle 0^\circ$ in R

$$v_R = iR = \sqrt{2} IR \cos \omega t = \sqrt{2} V_R \cos \omega t = V_R \angle 0^\circ$$

$$\text{Impedance } \frac{V_R \angle 0^\circ}{I \angle 0^\circ} = \frac{R I \angle 0^\circ}{I \angle 0^\circ} = R \angle 0^\circ \leftarrow \text{Num} \angle - \text{Denom}$$

Current $i = \sqrt{2} I \cos \omega t = I \angle 0^\circ$ in L

$$v_L = L \frac{di}{dt} = \sqrt{2} \omega L I (-\sin \omega t) = \sqrt{2} \omega L I \cos(\omega t + 90^\circ)$$

$$\text{Impedance } \frac{V_L \angle 90^\circ}{I \angle 0^\circ} = \frac{\omega L I \angle 90^\circ}{I \angle 0^\circ} = \omega L \angle 90^\circ = j\omega L$$

\uparrow implies 90° anticlockwise rotation

Voltage $v = \sqrt{2} V \cos \omega t = V \angle 0^\circ$ across C

$$i_C = C \frac{dv}{dt} = \sqrt{2} \omega C V (-\sin \omega t) = \sqrt{2} \omega C V \cos(\omega t + 90^\circ)$$

$$\text{Impedance } \frac{V \angle 0^\circ}{\omega C V \angle 90^\circ} = \frac{1}{\omega C} \angle -90^\circ = \frac{-j}{\omega C}$$

\downarrow clockwise rotation 90°


$$\text{Resistance } Z_R = Z_R(j\omega) = R = R \angle 0^\circ$$

$$\text{Inductance } Z_L = Z_L(j\omega) = j\omega L = \omega L \angle 90^\circ$$

$$\text{Capacitance } Z_C = Z_C(j\omega) = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$


$$\text{General term Impedance } Z = R + jX$$

Reactance

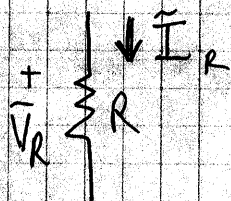


$$\hat{V}_R = \hat{I}_R R$$
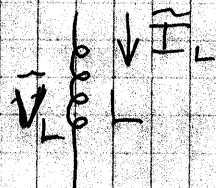
$$\hat{I}_R = \frac{1}{R} \hat{V}_R = \underset{\substack{\uparrow \\ \text{Conductance}}}{\tilde{G}} \hat{V}_R$$



$$\hat{V}_L = j\omega L \hat{I}_L$$
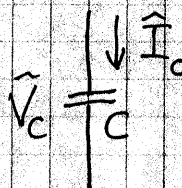
$$\hat{I}_L = \frac{1}{j\omega L} \hat{V}_L$$




$$\hat{V}_C = \frac{1}{j\omega C} \hat{I}_C$$


$$\hat{I}_C = j\omega C \hat{V}_C$$

Susceptance

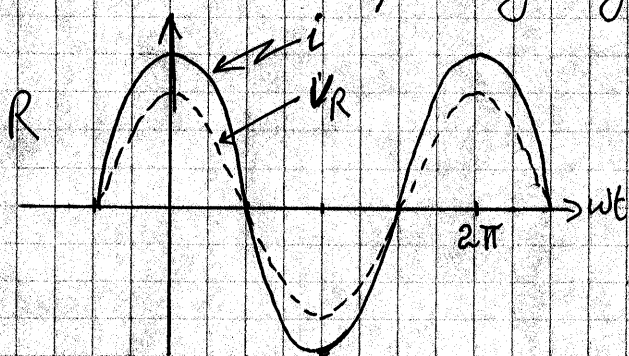
Admittance $\tilde{Y} = \tilde{G} + j\tilde{B}$





voltage in phase with current

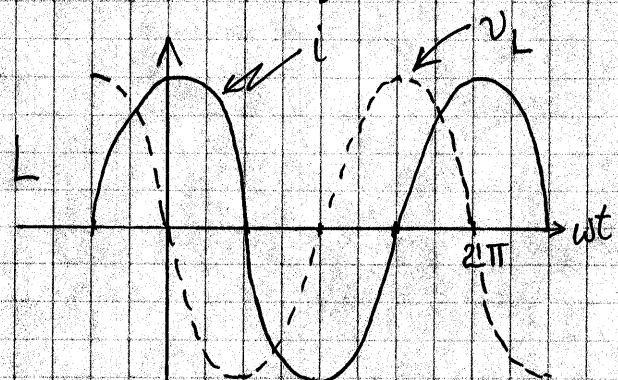

Voltage LEADS current by $\pi/2$

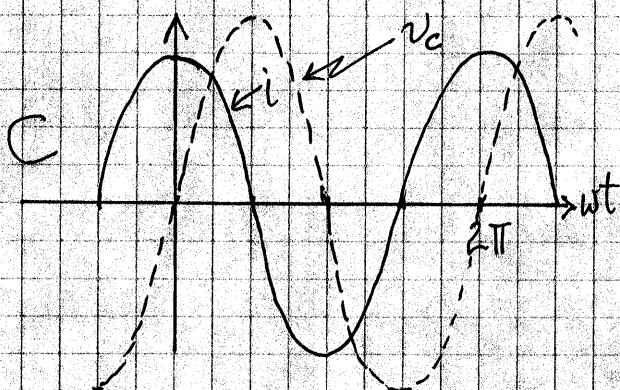

Voltage LAGS current by $\pi/2$

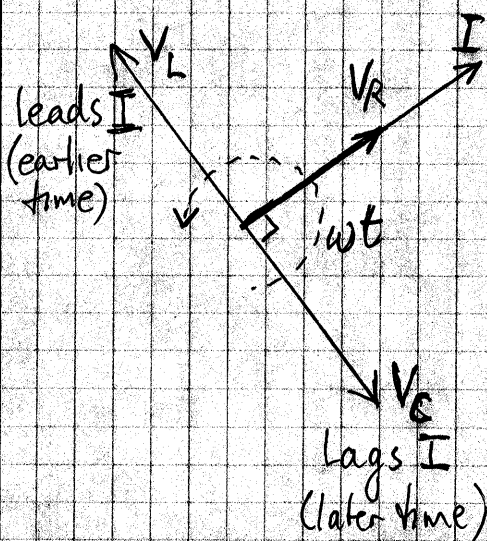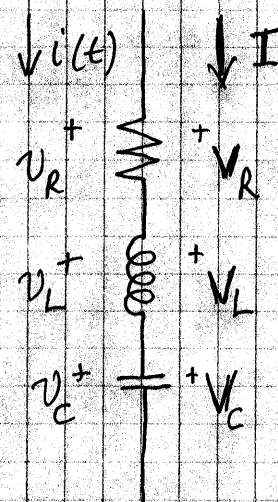

KIRCHHOFF'S LAWS hold for phasors


$$\sum V = 0 = V_1 + V_2 + V_3 + \dots + V_n$$

around any loop

$$\sum I = 0 = I_1 + I_2 + I_3 + \dots + I_n$$

into any node

Exercise 5.9

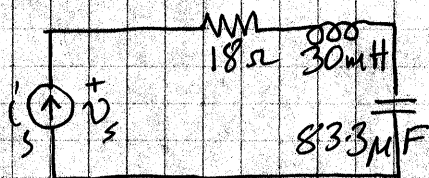

$i_s = 120\sqrt{2} \cos(1000t + 90^\circ)$. Find v_s

$$Z = 18 + j\omega 30 \times 10^{-3} + \frac{1}{j\omega 83.3 \times 10^{-6}}$$

$$\omega = 10^3 \quad 18 + j30 - j \frac{10^3}{83.3}$$

$$= 18 + j30 - j12 = 18 + j18 = 18\sqrt{2} \angle 45^\circ$$

$$I_s = 120 \angle 90^\circ, \text{ so } V_s = I_s Z = 120 \times 18\sqrt{2} \angle 90^\circ + 45^\circ$$

$$= 3054 \angle 135^\circ$$

$$\therefore v(t) = 3054\sqrt{2} \cos(1000t + 135^\circ) \text{ volts.}$$

In General — impedance Z is complex, and $V = ZI$

where $Z = Z \angle \phi_z = R + jX$

where $Z = \sqrt{R^2 + X^2}$ $\phi_z = \arctan X/R$

Z complex but not a phasor, not varying with time.

Exercise 5.10

(a) Find impedance of 100mH coil of resistance 400Ω at 2000Hz.

$$Z = 400 + j 2000 \times 2\pi \times 10^{-1} = 400 + j1257 = (400^2 + 1257^2)^{1/2} \angle \arctan \frac{1257}{400}$$

$$= 1319 \angle 72.3^\circ$$

(b) Find C in RC series ckt for $Z = 100 \angle -80^\circ$ at 5KHz.

$$Z = 100 \angle -80^\circ = 100 \cos 80^\circ - j 100 \sin 80^\circ$$


$$Z_{RC} = R - j \frac{1}{2\pi 5000 C} \quad \therefore \frac{1}{\pi 10^4 C} = 100 \times 0.985 \text{ ie. } C = \frac{1}{10^6 \pi (0.985)} \approx 0.32 \mu\text{F}$$

(c) Find freq for $R = 200\Omega$ in series with $L = 10\text{mH}$ to have 45° phase angle

$$Z = R + j\omega L = 200 + j 2\pi f 10^{-2} \text{ ie. } \frac{2\pi f 10^{-2}}{200} = \tan 45^\circ = 1 \quad \therefore f = \frac{20000}{2\pi} = 3.183 \text{ KHz}$$

Exercise 5.11

$i = 10\sqrt{2} \cos(1000t + 45^\circ)$

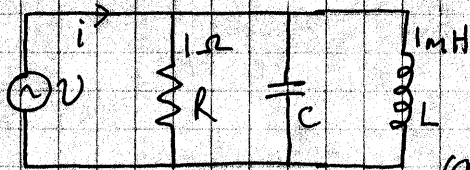

Find Z_{eq} , R_{eq} , X_{eq} for (a) $C=0.5 \mu F$
(b) $C=2 \mu F$


(a) $Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{1 - \frac{j}{10^{-3} \cdot 10^3} + j \frac{10^{-3}}{2} \cdot 10^3}$
 $= \frac{1}{1 - j0.5} = \frac{1}{1.1 \angle -26.6^\circ} = 0.9 \angle 26.6^\circ = 0.82 + j0.365$
 (Note: $1.1 = (1+0.25)^{1/2}$, $\arctan 0.5$)

(b) $Z_{eq} = \frac{1}{1 - j + j10^3 \cdot 2 \cdot 10^{-3}} = \frac{1}{1 + j} = \frac{1-j}{2-j} = \frac{\sqrt{2}}{2} \angle \arctan -1 = \frac{1}{\sqrt{2}} \angle -45^\circ$
 $= \frac{1}{\sqrt{2}} \cos -45 + j \frac{1}{\sqrt{2}} \sin -45 = 0.5 - j0.5$

So (a) $\rightarrow R_{eq} = 0.82 \Omega$ $X_{eq} = 0.365 \Omega$
 (b) $\rightarrow R_{eq} = 0.5 \Omega$ $X_{eq} = -0.5 \Omega$

Exercise 5.12

$v = 12\sqrt{2} \cos 5000t$

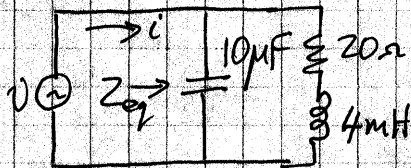

Find Z_C , Z_L , Z_R , Z_{eq} , i

$Z_R = 20 + j0 = 20 \angle 0^\circ$

$Z_L = 0 + j5000 \cdot 4 \cdot 10^{-3} = 0 + j20 = 20 \angle 90^\circ$

$Z_C = 0 - j \frac{1}{5 \cdot 10^3 \cdot 10^{-6}} = 0 - j20 = 20 \angle -90^\circ$


$Z_{RL} = Z_R + Z_L = 20 + j0 + 0 + j20 = 20 + j20 = 20\sqrt{2} \angle 45^\circ = 28.3 \angle 45^\circ$

$\therefore Z_{eq} = \frac{Z_{RL} Z_C}{Z_{RL} + Z_C} = \frac{28.3 \times 20 \angle 45^\circ - 90^\circ}{20 + j20 - j20} = 28.3 \angle -45^\circ = 20.01 - j20.01$

$\therefore I = \frac{V}{Z_{eq}} = \frac{12 \angle 0^\circ}{28.3 \angle -45^\circ} = 0.424 \angle 45^\circ = 0.424\sqrt{2} \cos(5000t + 45^\circ) = 0.60 \cos(5000t + 45^\circ)$

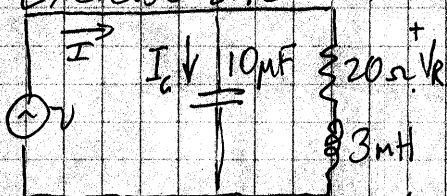Exercise 5.13

Find I_C , V_R From Example 5 $Z_R = 20$ $Z_C = -j20$ $Z_L = j15$



$I_C = \frac{Z_{LR}}{Z_{LR} + Z_C} I = \frac{20 + j15}{20 + j15 - j20} \cdot 4.9 \angle 39^\circ = \frac{4 + j3}{4 - j5} \cdot 4.9 \angle 39^\circ = \frac{5 \angle 36.9^\circ}{4.12 \angle -14.0^\circ} \cdot 0.49 \angle 39^\circ = 0.6 \angle 89.9^\circ$

$V_R = \frac{Z_R}{Z_R + Z_L} V = \left[\frac{20}{20 + j15} \right] 12 \angle 0^\circ = \frac{4}{5 \angle 36.9^\circ} \cdot 12 = 9.6 \angle -36.9^\circ$

ADMITTANCE

$$Y = \frac{I}{V} = \frac{1}{Z}$$

$$Y_R = \frac{1}{R \angle 0^\circ} = g \angle 0^\circ$$

$$Y_L = \frac{1}{j\omega L} = \frac{1}{\omega L} \angle -90^\circ$$

$$Y_C = j\omega C = \omega C \angle +90^\circ$$

$$Y = Y \angle \phi_Y = g + jB$$


$$Y = (g^2 + B^2)^{1/2}$$

$$\phi_Y = \arctan \frac{B}{g}$$

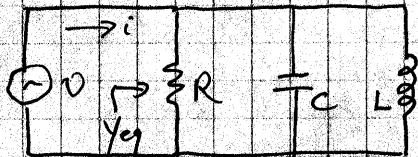Exercise 5.14

$$v = 120\sqrt{2} \cos(1000t + 90^\circ)$$

$$R = 15 \Omega \quad C = 83.3 \mu\text{F} \quad L = 30 \text{mH}$$



Find Y_R , Y_L , Y_C , Y_{eq} , I

$$Y_L = \frac{1}{1000 \cdot 30 \cdot 10^{-3}} \angle -90^\circ$$

$$= \frac{1}{30} \angle -90^\circ \text{ S}$$

$$Y_R = \frac{1}{15} \text{ S} \quad Y_C = 1000 \cdot 83.3 \cdot 10^{-6} \angle +90^\circ \text{ S}$$

$$= 0.0833 \angle +90^\circ \text{ S} = \frac{1}{12} \angle +90^\circ \text{ S}$$

$$\therefore Y = Y_R + Y_C + Y_L = \frac{1}{15} + \frac{1}{12} \angle +90^\circ + \frac{1}{30} \angle -90^\circ$$


$$= 0.067 + (\frac{1}{12} \times 0) + j \cdot 0.083 + (\frac{1}{30} \times 0) - j \cdot 0.033$$

$$= 0.067 + j \cdot 0.05 = 0.084 \angle 36.9^\circ$$

$$\text{So } I = I_V = 120 \angle 90^\circ \cdot (0.084) \angle 36.9^\circ = 10.08 \angle 126.9^\circ \approx 10 \angle 127^\circ \text{ A}$$

Exercise 5.15

$$v_g = 100 \cos 1000t$$

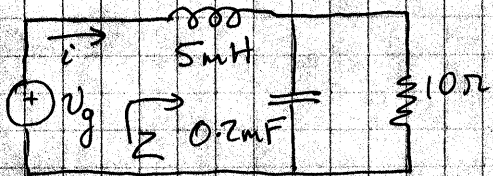

$$(a) Z = j\omega L + \frac{1}{\frac{1}{R} + j\omega C} = j10^3 \cdot 5 \times 10^{-3} + \frac{1}{\frac{1}{10} + j10^3 \cdot 0.2 \cdot 10^{-6}}$$

$$= 5j + \frac{10}{1 + 2j} = 5j + \frac{10(1 - 2j)}{1 + 4}$$

$$= 5j + 2(1 - 2j) = 2 + j \quad (\text{incorrect in text})$$

$$(b) \therefore I = \frac{V}{Z} = \frac{100/\sqrt{2} \angle 0^\circ}{2.24 \angle 26.56^\circ}$$

$$= 31.6 \angle -26.56^\circ$$

$$= \sqrt{5} \arctan 1/2$$

$$= 2.24 \angle 26.56^\circ$$

$$(c) i(t) = 31.6 \sqrt{2} \cos(1000t - 26.56^\circ)$$

↑ 44.7 A

See Section 5.4 Analogs & Duals