

Chapter 3 Inductance and Capacitance

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

Chapter 3 Inductance and Capacitance

1. Find the current (voltage) for a capacitance or inductance given the voltage (current) as a function of time.
2. Compute the capacitances of parallel-plate capacitors.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

3. Compute the stored energies in capacitances or inductances.
4. Describe typical physical construction of capacitors and inductors and identify parasitic effects.
5. Find the voltages across mutually coupled inductances in terms of the currents.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

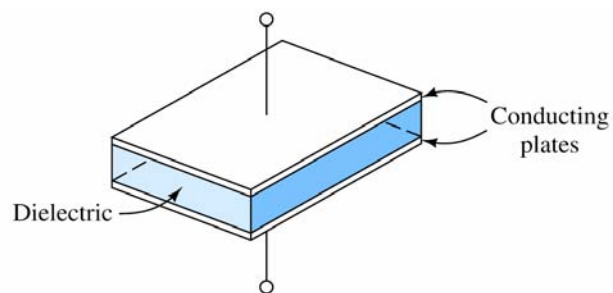


Figure 3.1 A parallel-plate capacitor consists of two conductive plates separated by a dielectric layer.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

CAPACITANCE


$$q = Cv$$

$$q(t) = \int_{t_0}^t i(t)dt + q(t_0)$$


$$i = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t)dt + v(t_0)$$

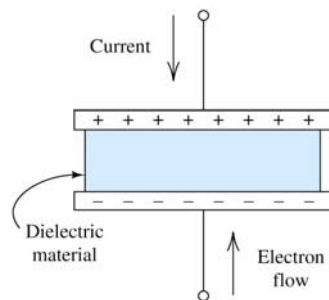ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




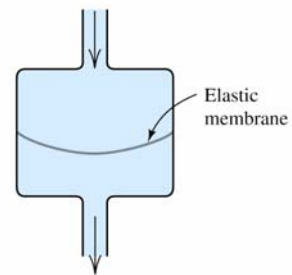
(a) As current flows through a capacitor, charges of opposite sign collect on the respective plates







(b) Fluid-flow analogy for capacitance


Figure 3.2 A capacitor and its fluid-flow analogy.

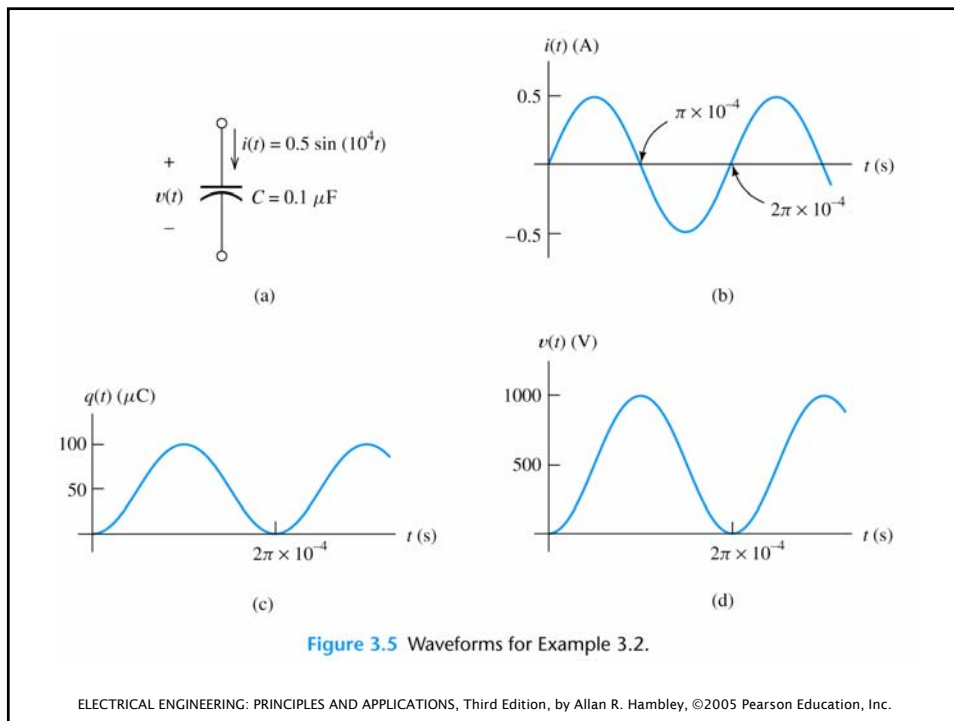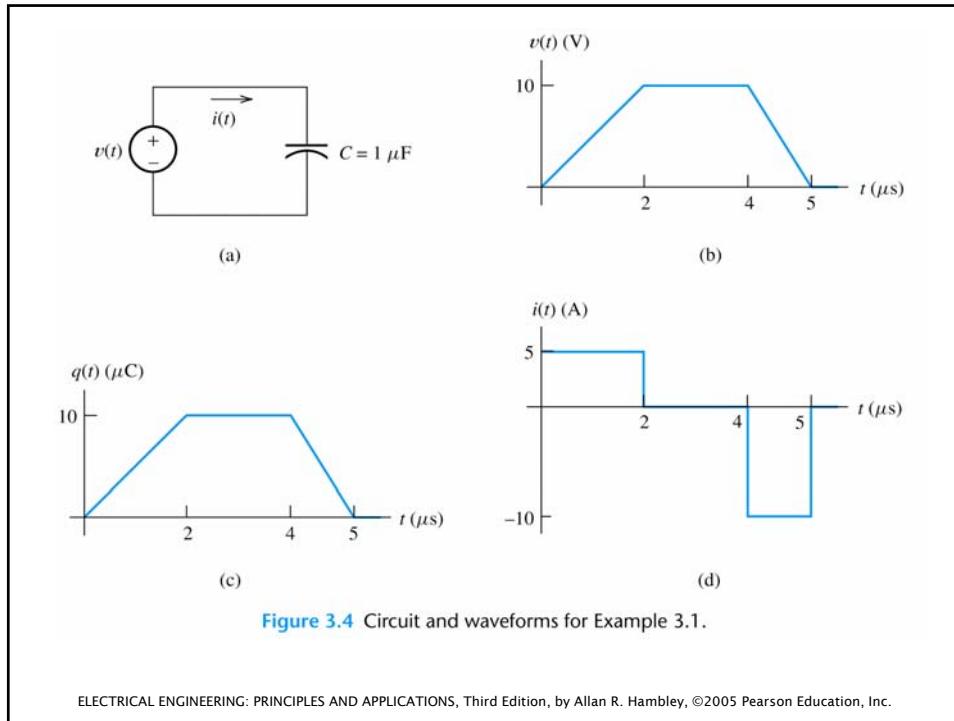ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



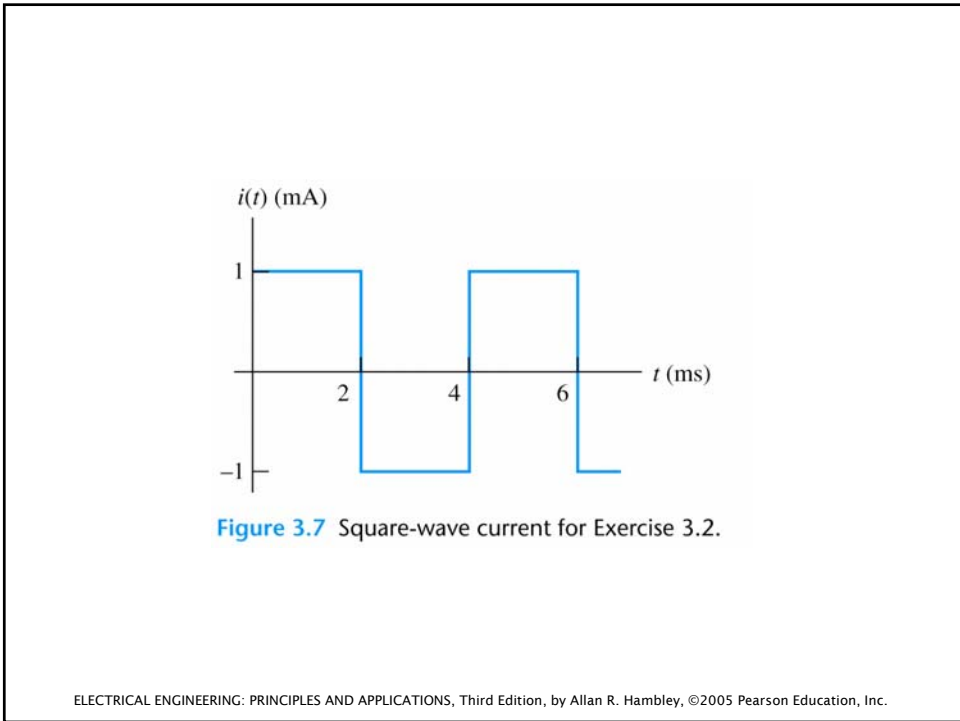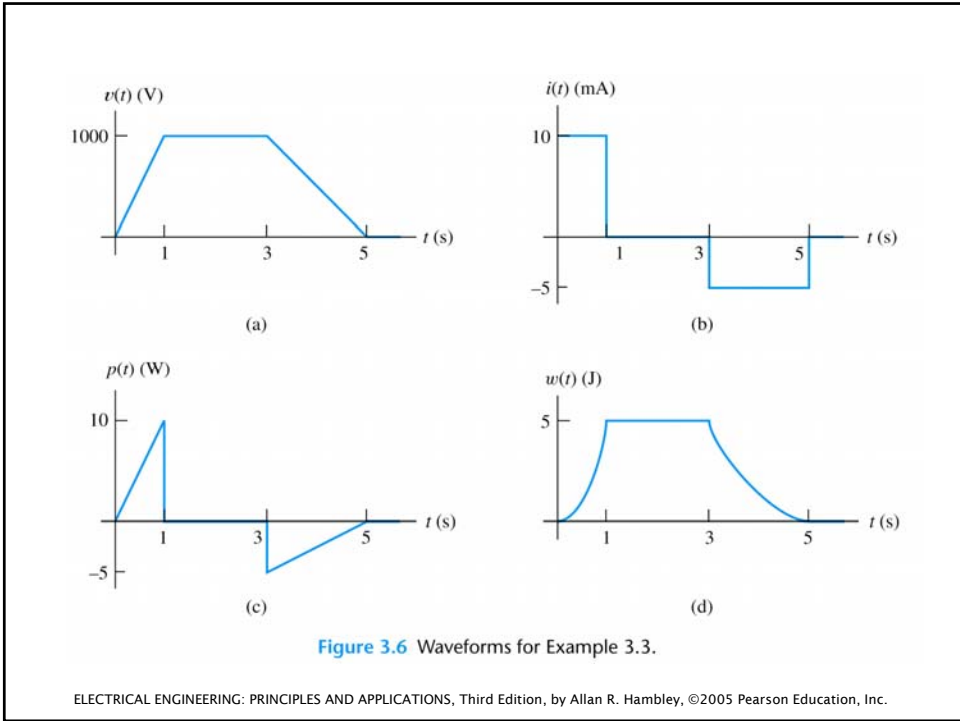

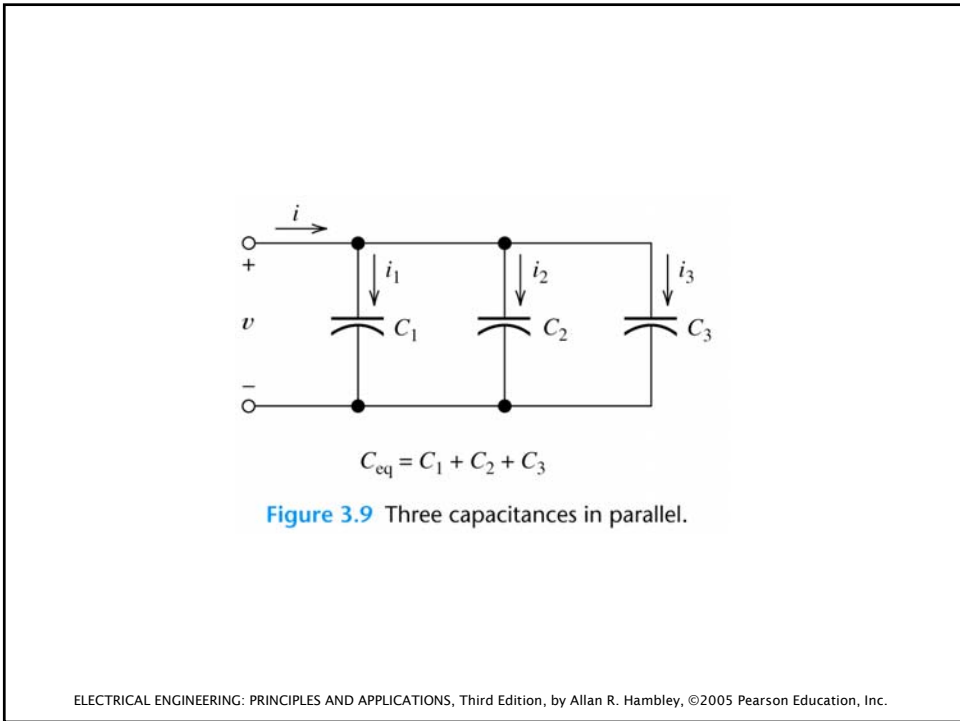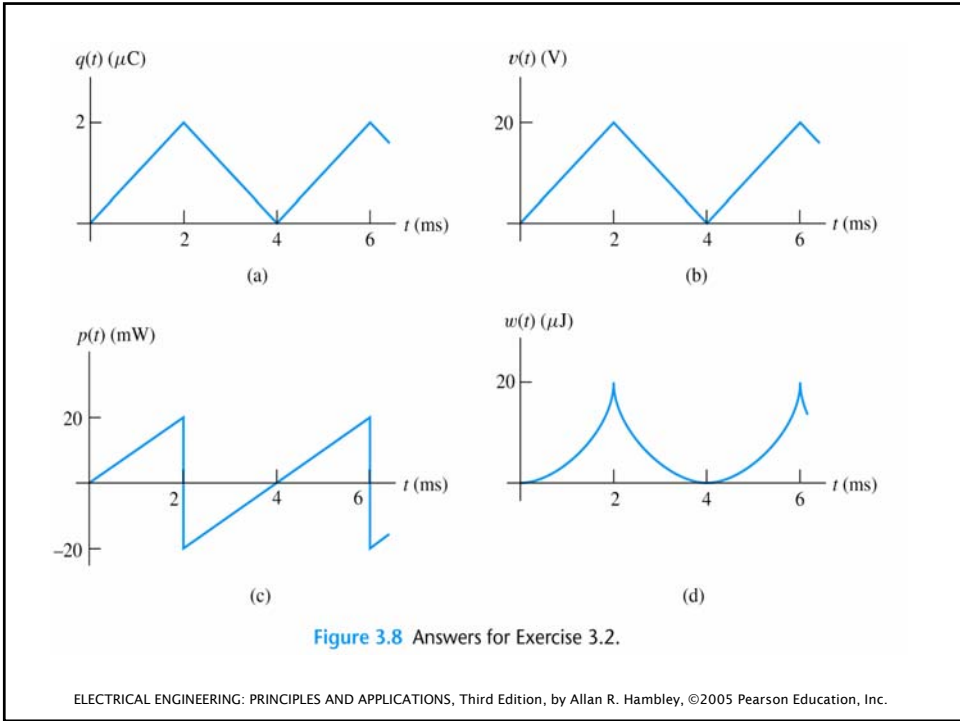

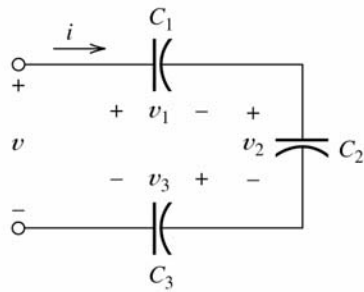

$$C_{eq} = \frac{1}{1/C_1 + 1/C_2 + 1/C_3}$$

Figure 3.10 Three capacitances in series.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


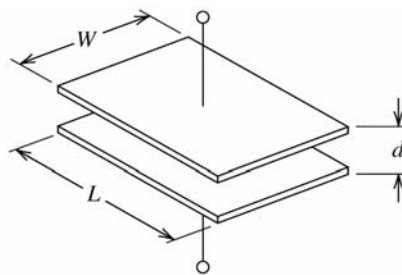


Figure 3.11 A parallel-plate capacitor including dimensions.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

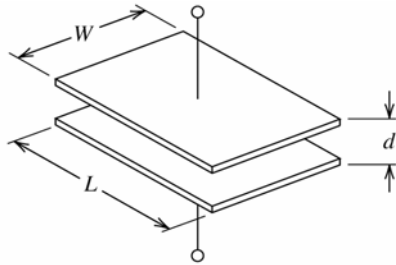Capacitance of the Parallel-Plate Capacitor



$$C = \frac{\epsilon A}{d} \quad A = WL$$

$$\epsilon_0 \cong 8.85 \times 10^{-12} \text{ F/m}$$

$$\epsilon = \epsilon_r \epsilon_0$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

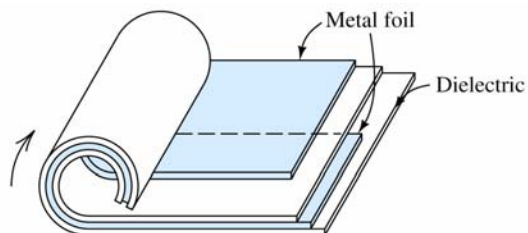


Figure 3.12 Practical capacitors can be constructed by interleaving the plates with two dielectric layers and rolling them up. By staggering the plates, connection can be made to one plate at each end of the roll.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

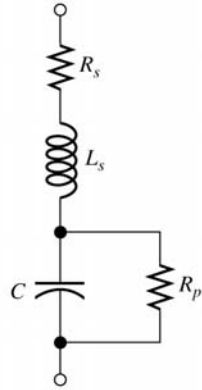


Figure 3.13 The circuit model for a capacitor including the parasitic elements R_s , L_s , and R_p .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

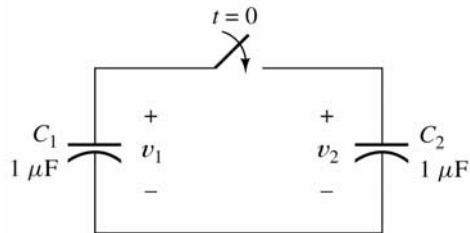


Figure 3.14 See Example 3.5.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

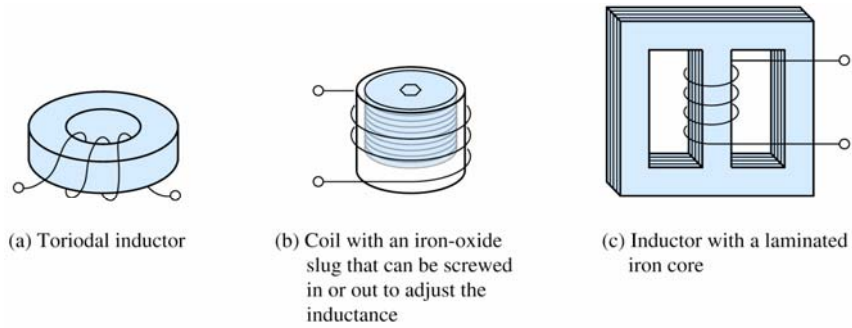


Figure 3.15 An inductor is constructed by coiling a wire around some type of form.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


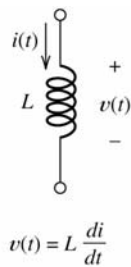


Figure 3.16 Circuit symbol and the $v - i$ relationship for inductance.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

INDUCTANCE

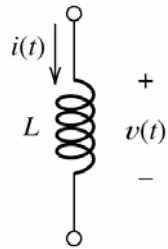


$$v(t) = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$


$$v(t) = L \frac{di}{dt}$$

$$w(t) = \frac{1}{2} Li^2(t)$$

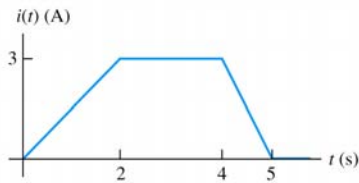
ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




(a)

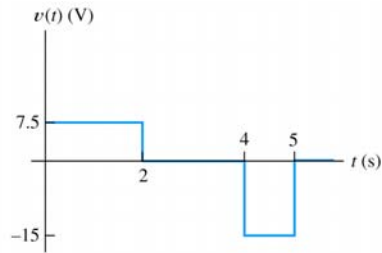

(b)

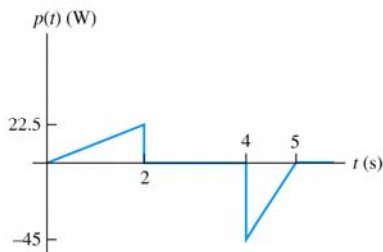



(c)


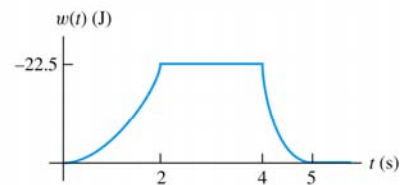


(d)

Figure 3.17 Waveforms for Example 3.6.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

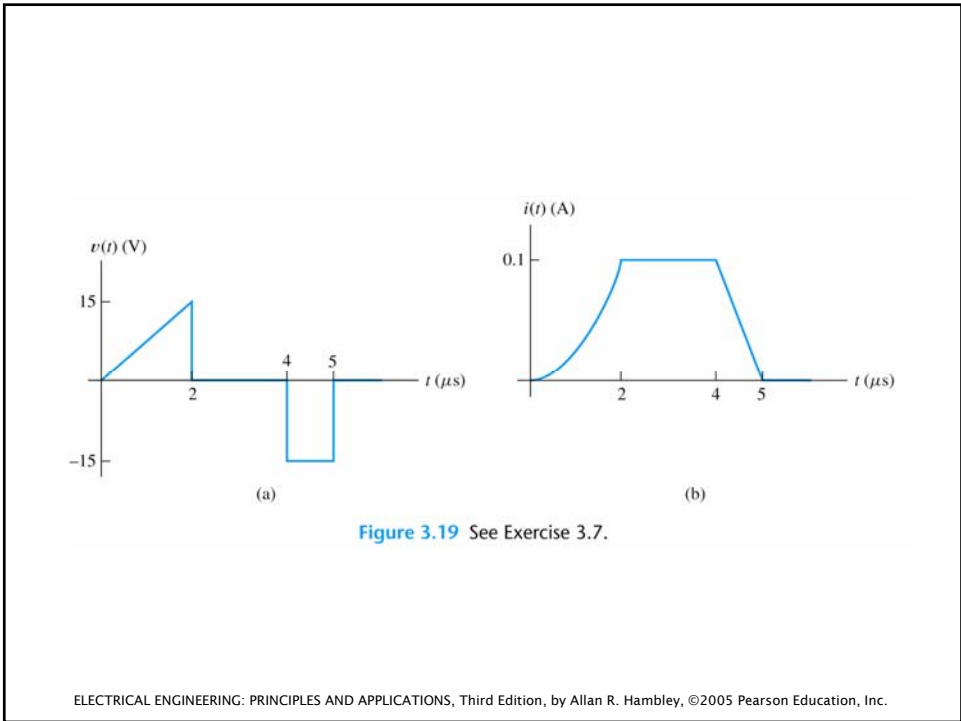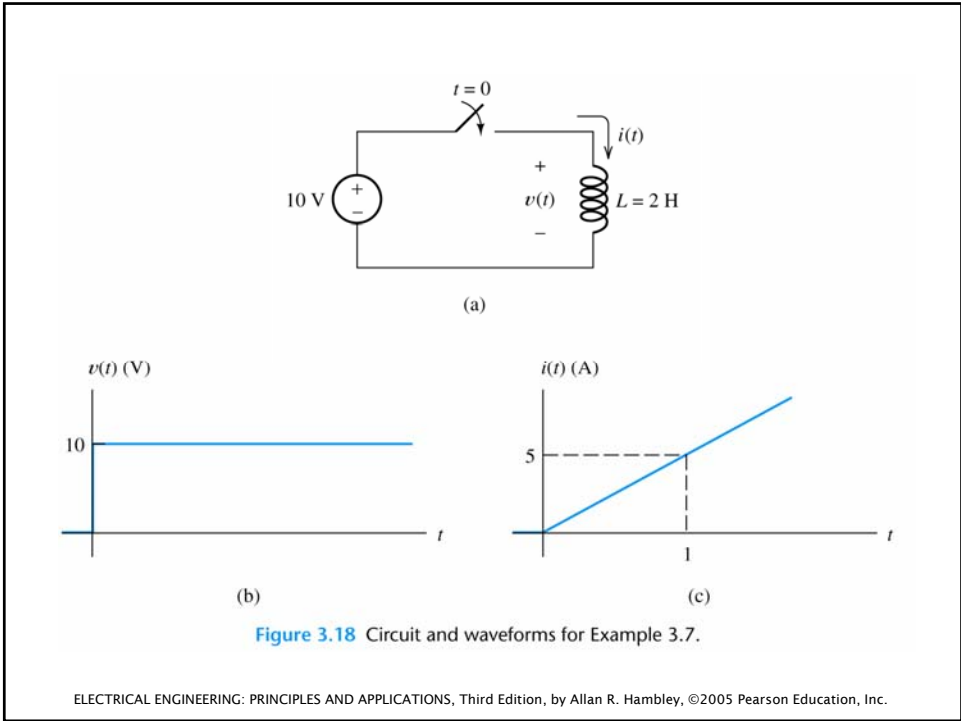

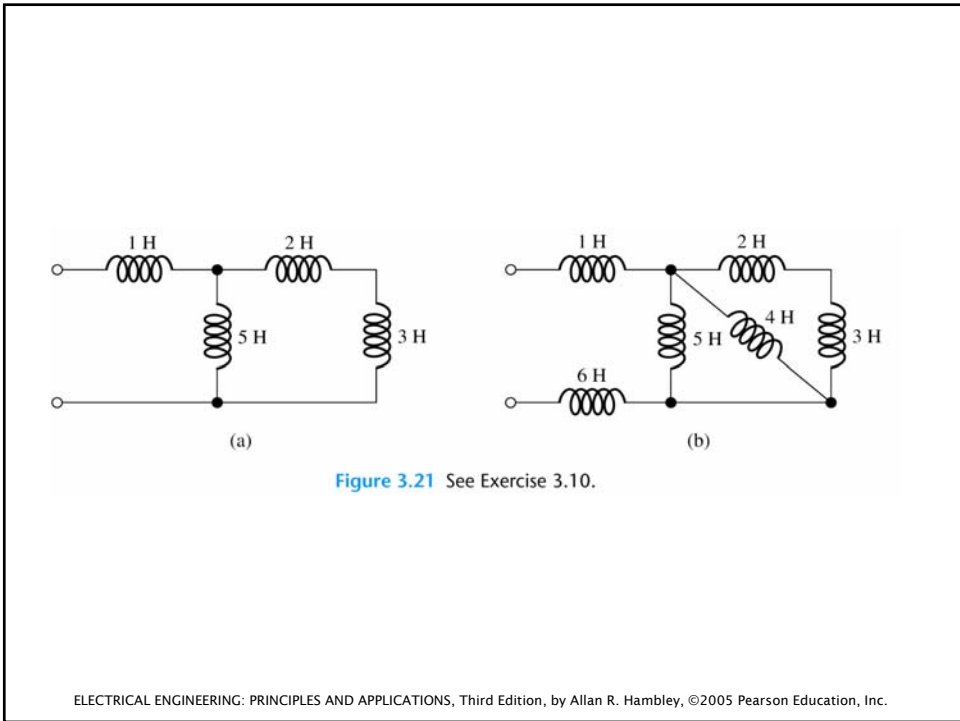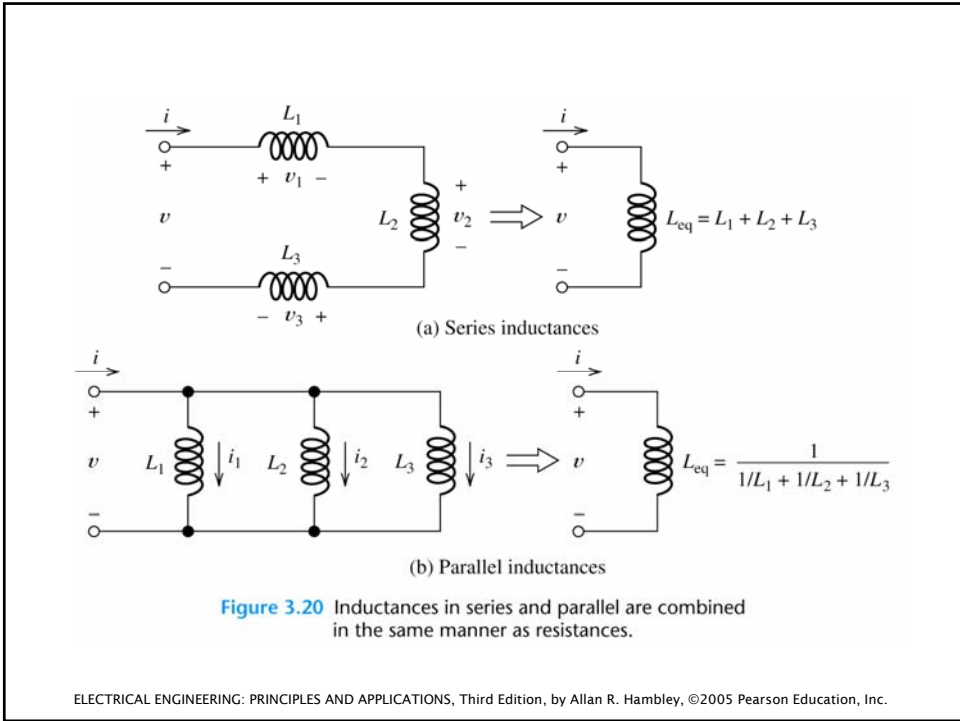

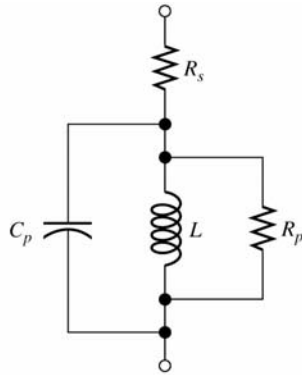


Figure 3.22 Circuit model for real inductors including several parasitic elements.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

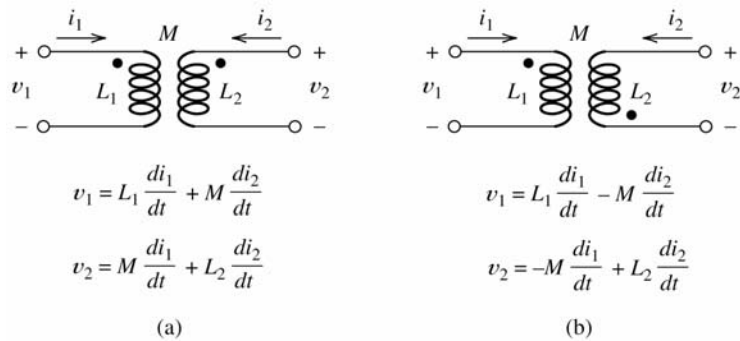


Figure 3.23 Circuit symbols and $v - i$ relationships for mutually coupled inductances.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

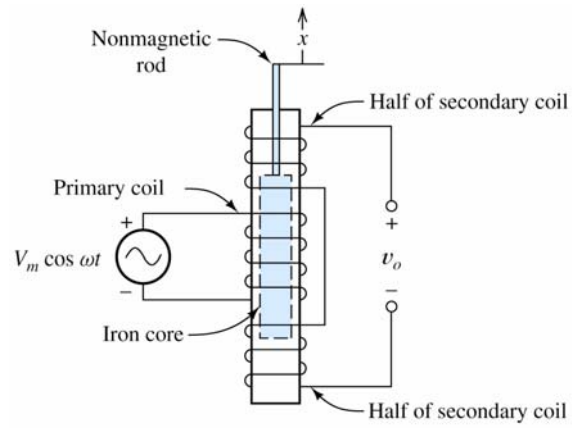


Figure 3.24 A linear variable differential transformer used as a position transducer.