

## Chapter 4 Transients

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Chapter 4 Transients

1. Solve first-order  $RC$  or  $RL$  circuits.
2. Understand the concepts of transient response and steady-state response.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


3. Relate the transient response of first-order circuits to the time constant.
4. Solve *RLC* circuits in dc steady-state conditions.
5. Solve second-order circuits.
6. Relate the step response of a second-order system to its natural frequency and damping ratio.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.
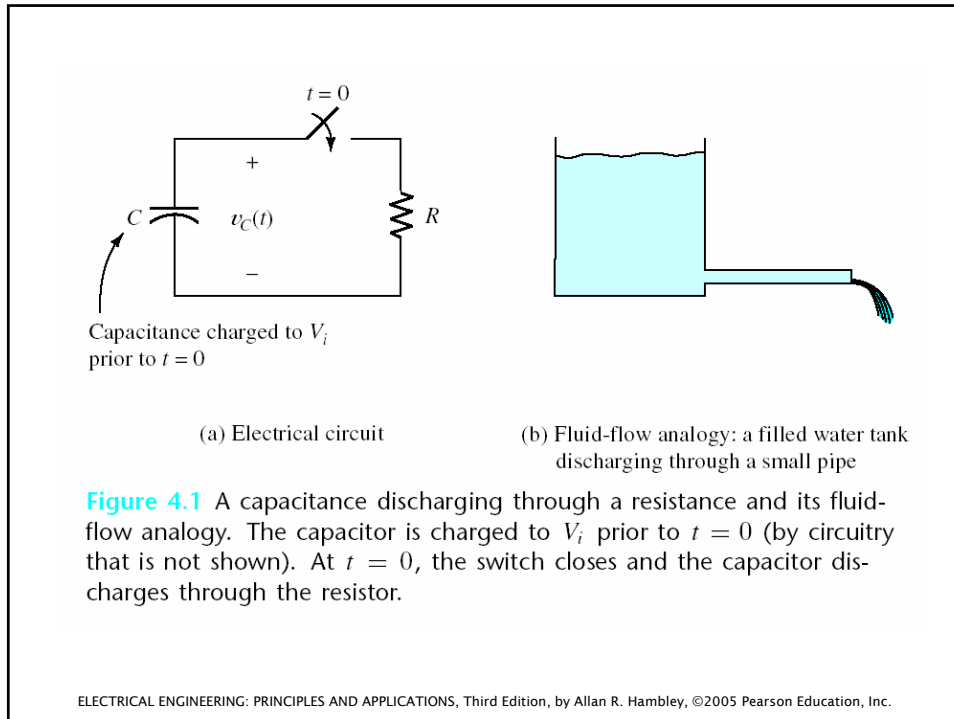
## Transients

The time-varying currents and voltages resulting from the sudden application of sources, usually due to switching, are called **transients**. By writing circuit equations, we obtain integrodifferential equations.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



## Discharge of a Capacitance through a Resistance

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0 \qquad v_C(t) = Ke^{st}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0 \qquad RCKse^{st} + Ke^{st} = 0$$


$$s = \frac{-1}{RC}$$

$$v_C(0+) = V_i$$

$$v_C(t) = Ke^{-t/RC}$$

$$v_C(t) = V_i e^{-t/RC}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

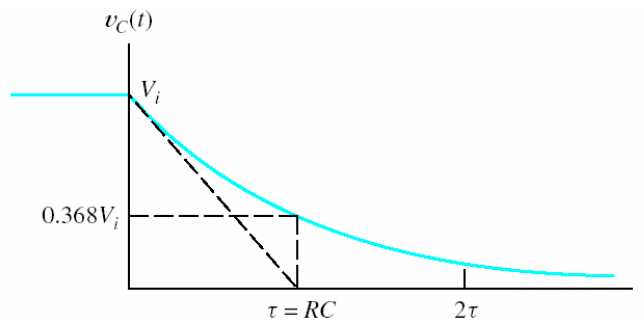

**Figure 4.2** Voltage versus time for the circuit of Figure 4.1(a). When the switch is closed, the voltage across the capacitor decays exponentially to zero. At one time constant, the voltage is equal to 36.8 percent of its initial value.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

The time interval  $\tau = RC$  is called the time constant of the circuit.


$$v_C(t) = V_s - V_s e^{-t/\tau}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

**Figure 4.3** Capacitance charging through a resistance. The switch closes at  $t = 0$ , connecting the dc source  $V_s$  to the circuit.

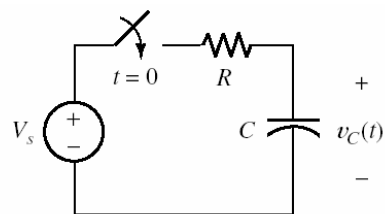

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

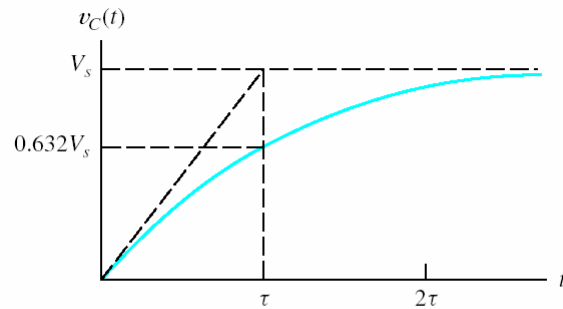

**Figure 4.4** The charging transient for the  $RC$  circuit of Figure 4.3.



ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## DC STEADY STATE

The steps in determining the forced response for  $RLC$  circuits with dc sources are:

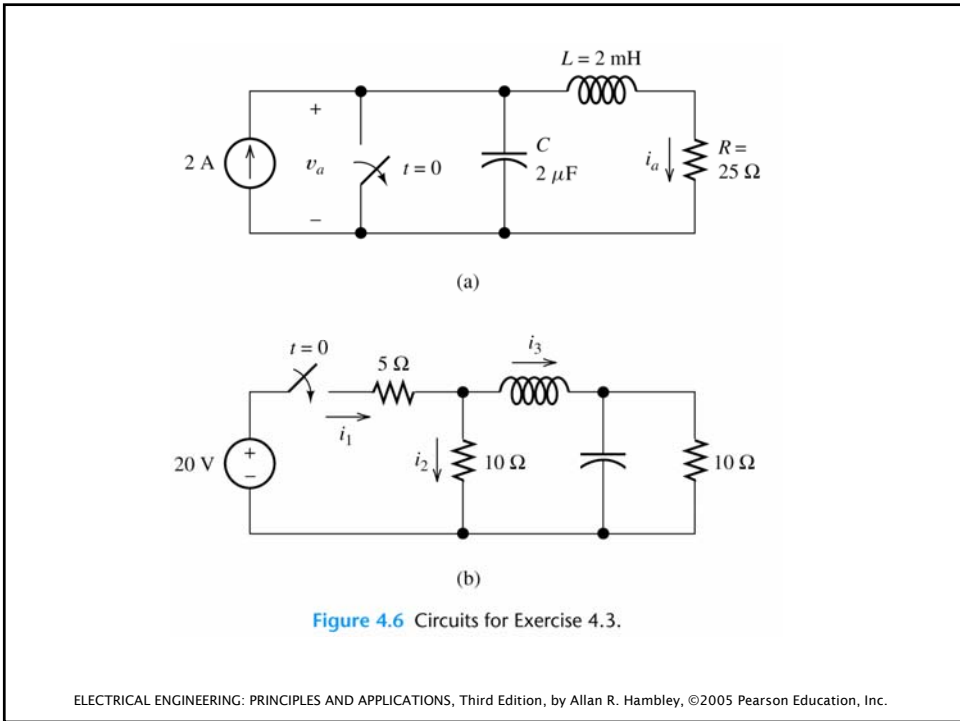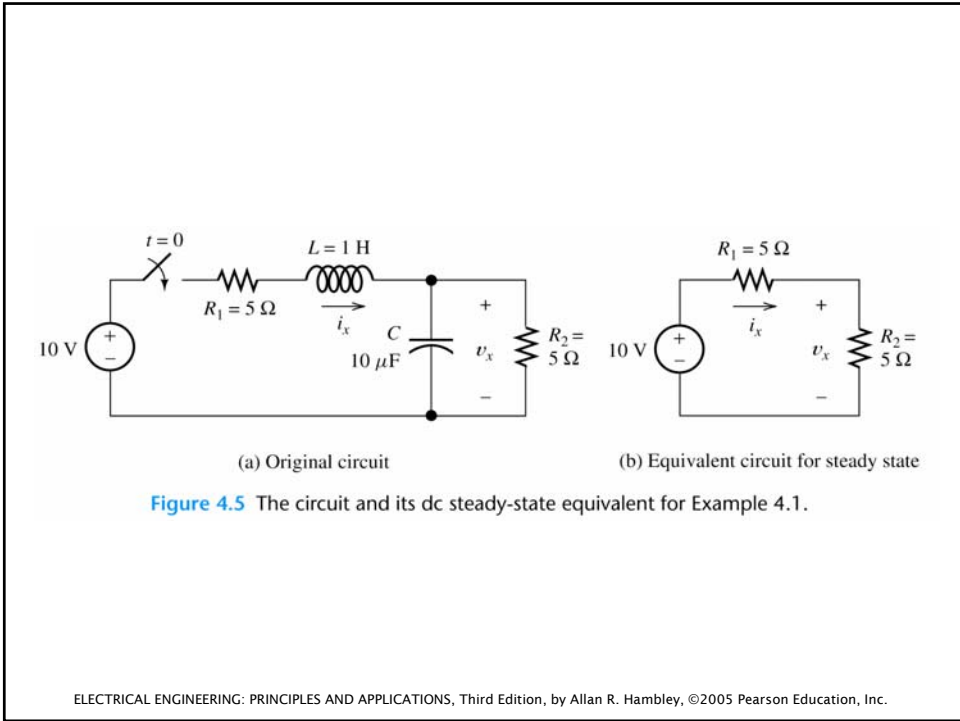1. Replace capacitances with open circuits.
2. Replace inductances with short circuits.
3. Solve the remaining circuit.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



## ***RL* CIRCUITS**

The steps involved in solving simple circuits containing dc sources, resistances, and one energy-storage element (inductance or capacitance) are:

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

- 1.** Apply Kirchhoff's current and voltage laws to write the circuit equation.
- 2.** If the equation contains integrals, differentiate each term in the equation to produce a pure differential equation.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

- 3.** Assume a solution of the form  $K_1$



4. Substitute the solution into the differential equation to determine the values of  $K_1$  and  $s$ . (Alternatively, we can determine  $K_1$  by solving the circuit in steady state as discussed in Section 4.2.)

5. Use the initial conditions to determine

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

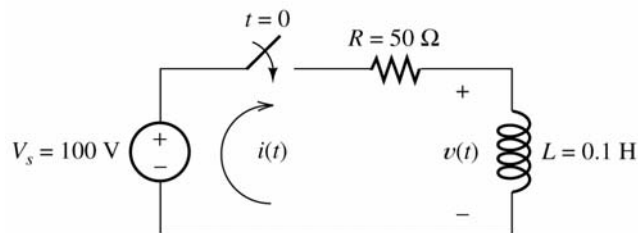


Figure 4.7 The circuit analyzed in Example 4.2.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

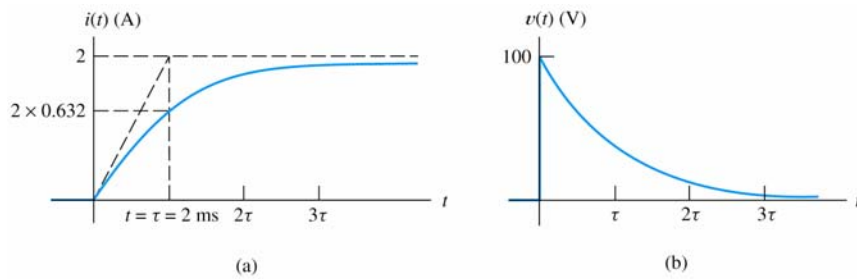


Figure 4.8 Current and voltage versus time for the circuit of Figure 4.7.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


## RL Transient Analysis

$$i(t) = 2 + K_2 e^{-tR/L}$$

Time constant is


$$\tau = \frac{L}{R}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

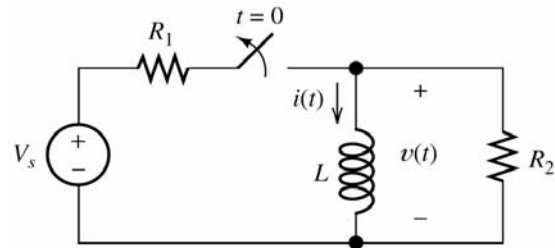

**Figure 4.9** The circuit analyzed in Example 4.3.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

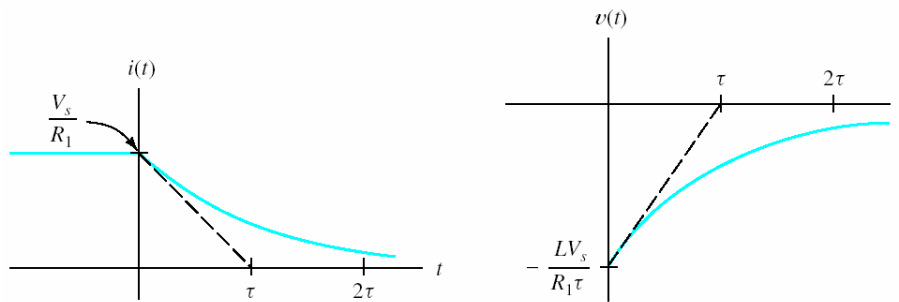

**Figure 4.10** The current and voltage for the circuit of Figure 4.9.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

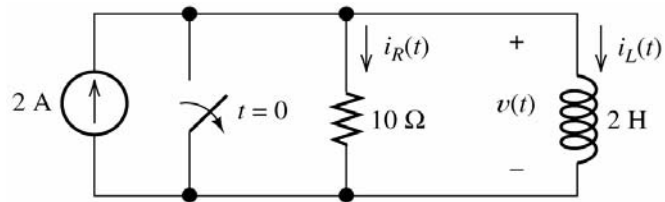


Figure 4.11 The circuit for Exercise 4.5.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


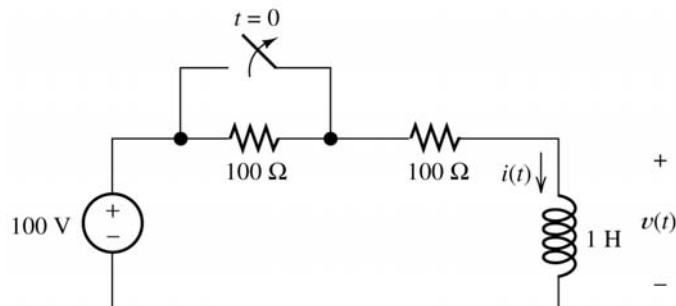


Figure 4.12 The circuit for Exercise 4.6.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

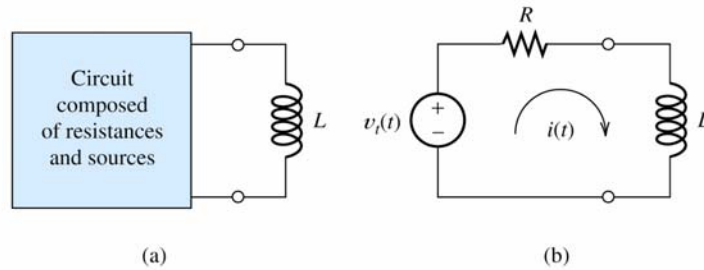

**Figure 4.13** A circuit consisting of sources, resistances, and one inductance has an equivalent circuit consisting of a voltage source and a resistance in series with the inductance.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## **RC AND RL CIRCUITS WITH GENERAL SOURCES**

The general solution consists of two parts.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

The particular solution (also called the forced response) is any expression that satisfies the equation.

In order to have a solution that satisfies the initial conditions, we must add the complementary solution to the particular solution.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

The homogeneous equation is obtained by setting the forcing function to zero.

The complementary solution (also called the natural response) is obtained by solving the homogeneous equation.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Step-by-Step Solution

Circuits containing a resistance, a source, and an inductance (or a capacitance)


1. Write the circuit equation and reduce it to a first-order differential equation.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

2. Find a particular solution. The details of this step depend on the form of the forcing function. We illustrate several types of forcing functions in examples, exercises, and problems.


3. Obtain the complete solution by adding the particular solution to the complementary solution given by Equation 4.44, which contains the arbitrary constant  $K$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

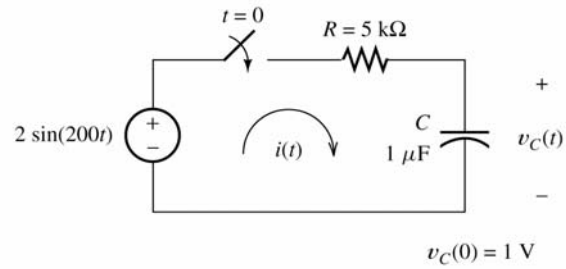

**Figure 4.14** A first-order  $RC$  circuit with a sinusoidal source. See Example 4.4.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

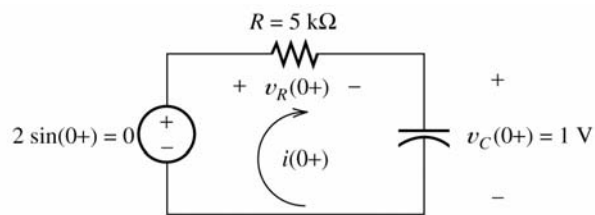

**Figure 4.15** The voltages and currents for the circuit of Figure 4.14 immediately after the switch closes.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



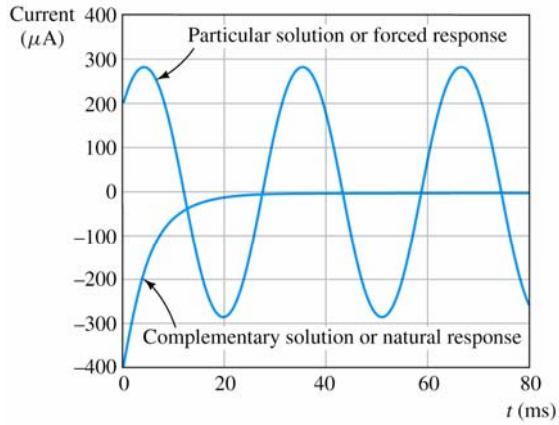


**Figure 4.16** The complementary solution and the particular solution for Example 4.4.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

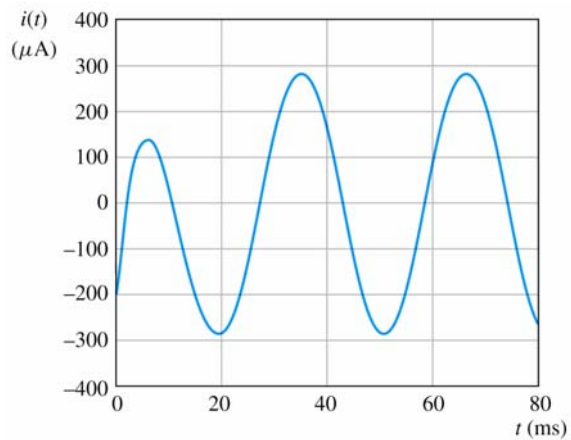


**Figure 4.17** The complete solution for Example 4.4.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

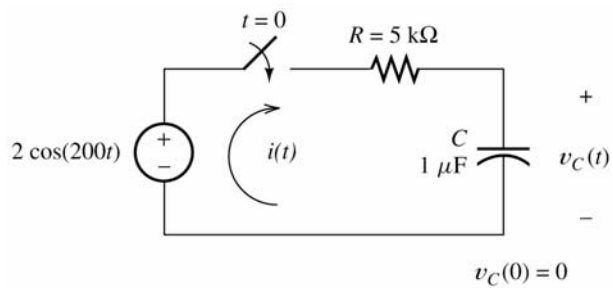


**Figure 4.18** The circuit for Exercise 4.7.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

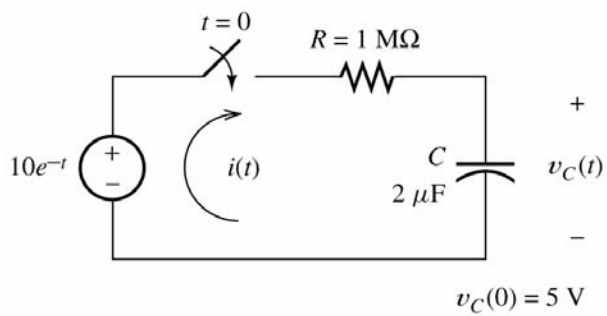

**Figure 4.19** The circuit for Exercise 4.8.

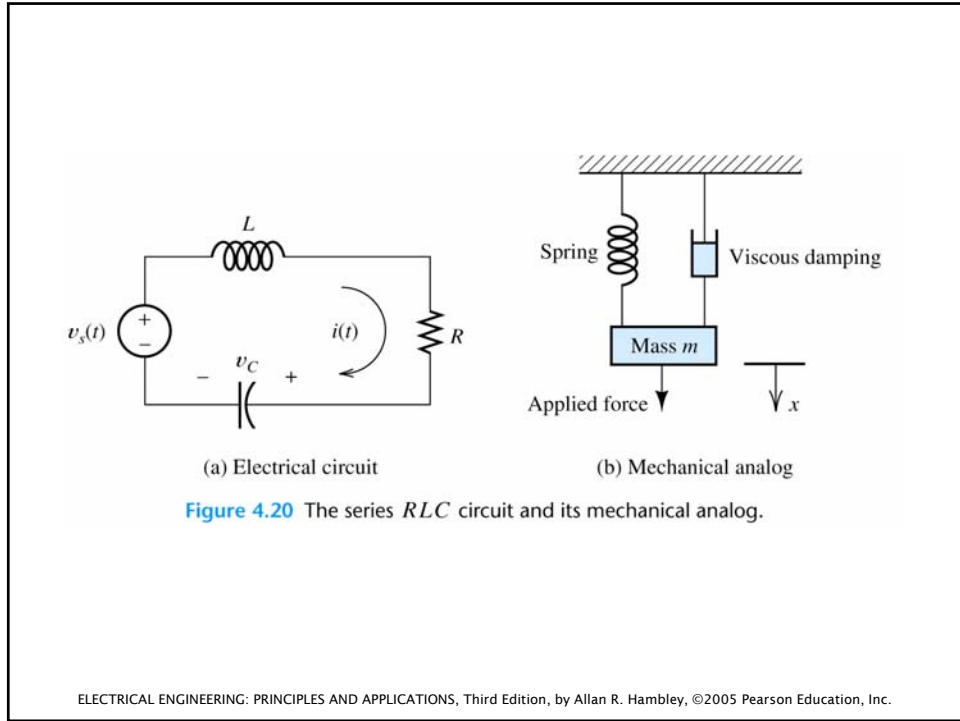ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




## SECOND-ORDER CIRCUITS

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(t) dt + v_C(0) = v_s(t)$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
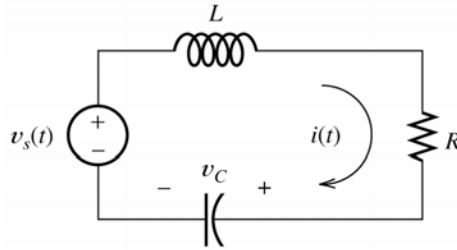
$$\frac{d^2 i(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$



(a) Electrical circuit

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

$$\zeta = \frac{\alpha}{\omega_0}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

1. *Overdamped case* ( $\zeta > 1$ ). If  $\zeta > 1$  (or equivalently, if  $\alpha > \omega_0$ ), the roots of the characteristic equation are real and distinct.

Then the complementary solution is

$$x_c(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

In this case, we say that the circuit is **overdamped**.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

2. *Critically damped case* ( $\zeta = 1$ ). If  $\zeta = 1$  (or equivalently, if  $\alpha = \omega_0$ ), the roots are real

and equal. Then the complementary solution  $x_c(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$  is

In this case, we say that the circuit is **critically damped**.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

3. *Underdamped case* ( $\zeta < 1$ ). Finally, if  $\zeta < 1$

(or equivalently, if  $\alpha < \omega_0$ ), the roots are complex. (By the term *complex*, we mean that

the roots involve the square root of  $-1$ .) In  $s_1 = -\alpha + j\omega_n$  and  $s_2 = -\alpha - j\omega_n$  other words, the roots are of the form in which  $j$  is the square root of  $-1$  and the

**natural frequency** is given by

$$\omega_n = \sqrt{\omega_0^2 - \alpha^2}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


In electrical engineering, we use  $j$  rather than  $i$  to stand for square root of  $-1$ , because we use  $i$  for current.

For complex roots, the complementary solution is of the form

$$x_c(t) = K_1 e^{-\alpha t} \cos(\omega_n t) + K_2 e^{-\alpha t} \sin(\omega_n t)$$


In this case, we say that the circuit is **underdamped**.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

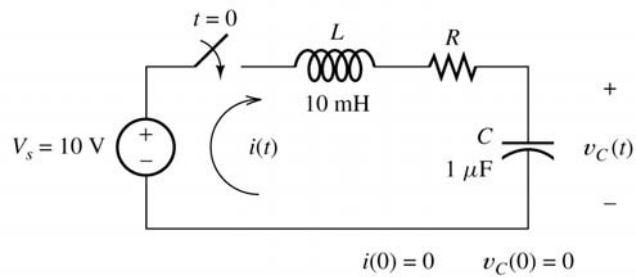

**Figure 4.21** The circuit for Example 4.5.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

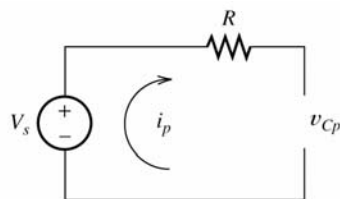

**Figure 4.22** The equivalent circuit for Figure 4.21 under steady-state conditions. The inductor has been replaced by a short circuit and the capacitor by an open circuit.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

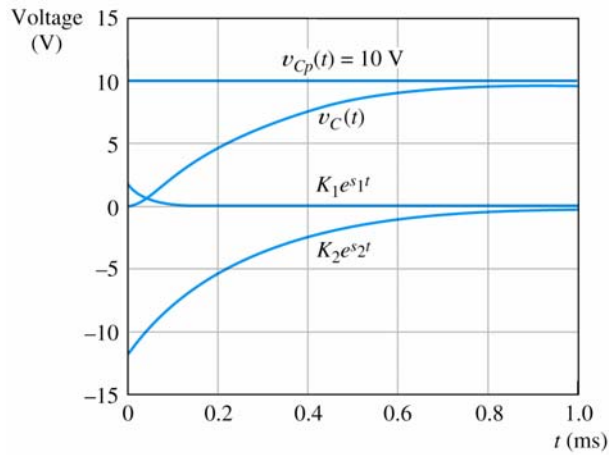


Figure 4.23 Solution for  $R = 300 \Omega$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

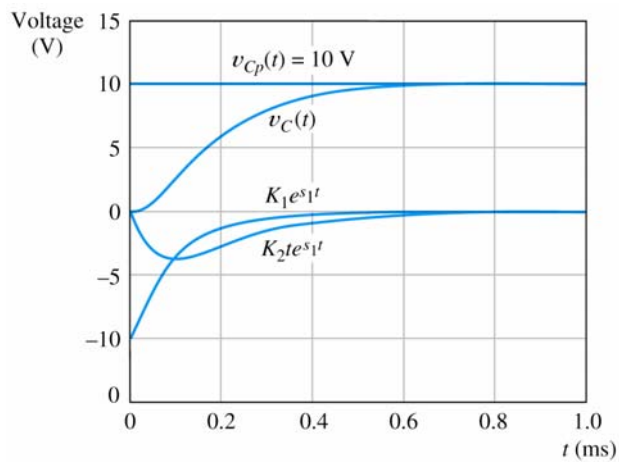


Figure 4.24 Solution for  $R = 200 \Omega$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



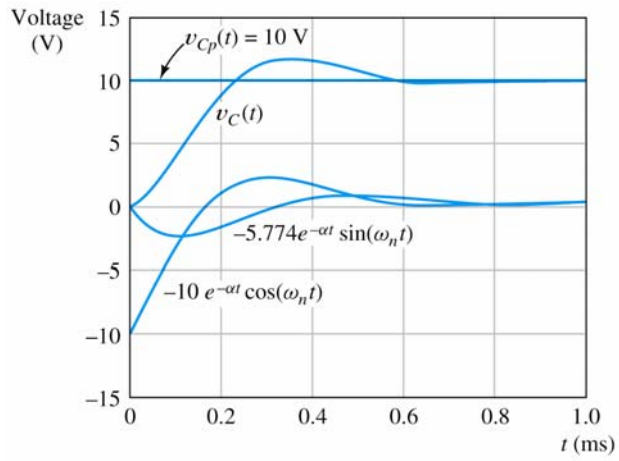


Figure 4.25 Solution for  $R = 100 \Omega$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


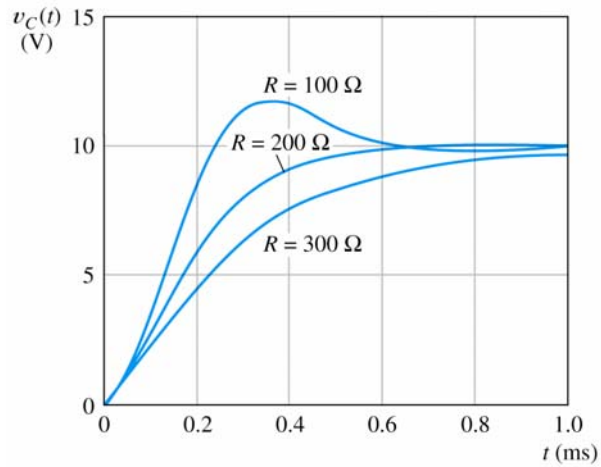



Figure 4.26 Solutions for all three resistances.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

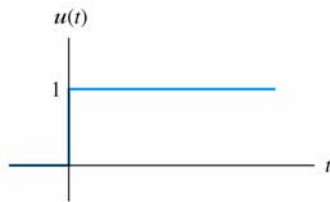


**Figure 4.27** A unit step function  $u(t)$ . For  $t < 0$ ,  $u(t) = 0$ . For  $t \geq 0$ ,  $u(t) = 1$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

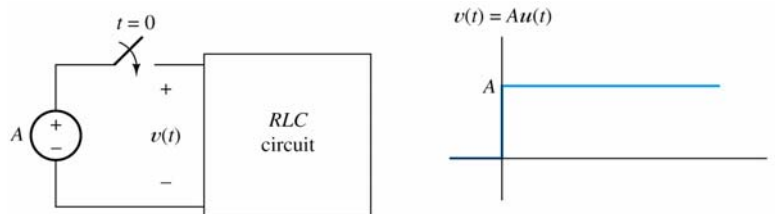


**Figure 4.28** Applying a dc voltage by closing a switch results in a forcing function that is a step function.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

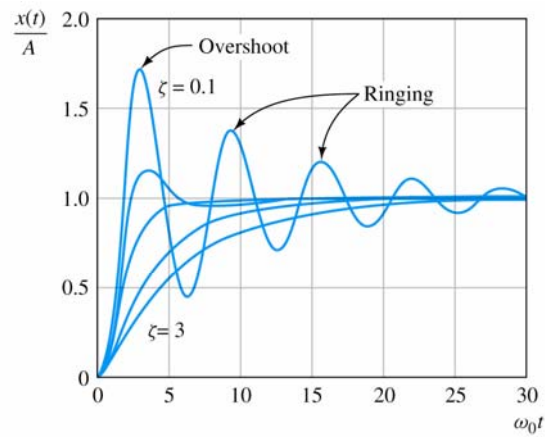


**Figure 4.29** Normalized step responses for second-order systems described by Equation 4.99 with damping ratios of  $\zeta = 0.1, 0.5, 1, 2,$  and  $3$ . The initial conditions are assumed to be  $x(0) = 0$  and  $x'(0) = 0$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

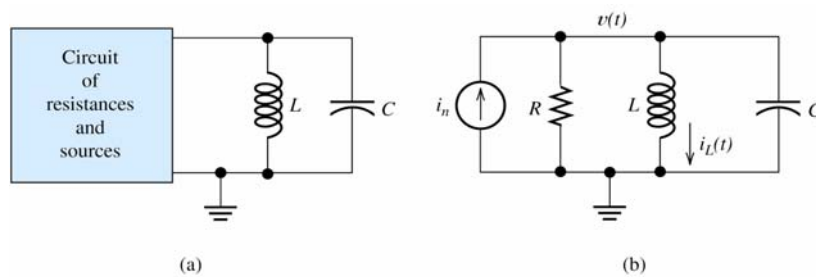

**Figure 4.30** Any circuit consisting of sources, resistances, and a parallel  $LC$  combination can be reduced to the equivalent circuit shown in (b).

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

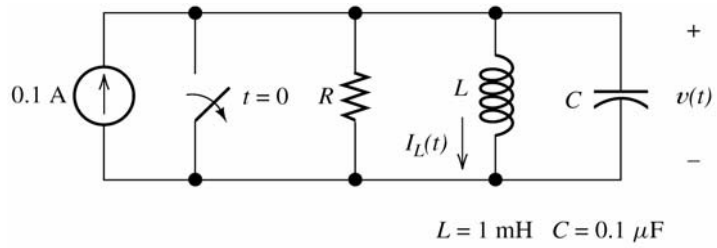

**Figure 4.31** Circuit for Exercises 4.9, 4.10, and 4.11.