

## **CHAPTER 6**

# **Frequency Response, Bode**

# **Plots, and Resonance**

1. State the fundamental concepts of Fourier analysis.
2. Determine the output of a filter for a given input consisting of sinusoidal components using the filter's transfer function.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

3. Use circuit analysis to determine the transfer functions of simple circuits.

4. Draw first-order lowpass or highpass filter circuits and sketch their transfer functions.

5. Understand decibels, logarithmic frequency

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

6. Draw the Bode plots for transfer functions of first-order filters.

7. Use software to produce Bode plots for more complex *RLC* filters.


8. Calculate parameters for series and parallel resonant circuits.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

9. Select and design simple filter circuits.

10. Design simple digital signal-processing systems.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

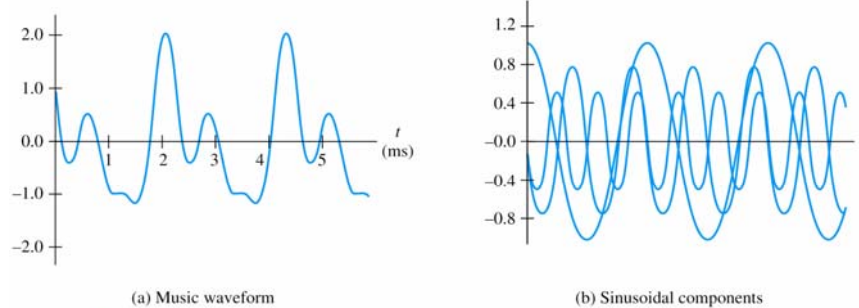


**Figure 6.1** The short segment of a music waveform shown in (a) is the sum of the sinusoidal components shown in (b).

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

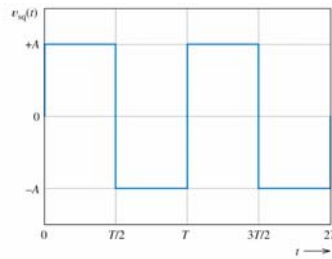
# Fourier Analysis

All real-world signals are sums of sinusoidal components having various frequencies, amplitudes, and phases.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



(a) Periodic square wave

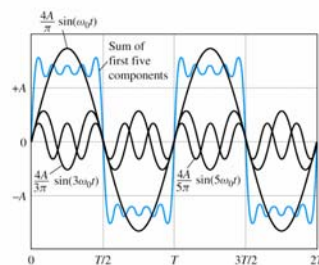

(b) Several of the sinusoidal components and the sum of the first five components


Figure 6.2 A square wave and some of its components.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

**Table 6.1. Frequency Ranges of Selected Signals**

Electrocardiogram	0.05 to 100 Hz
Audible sounds	20 Hz to 15 kHz
AM radio broadcasting	540 to 1600 kHz
Video signals (U.S. standards)	Dc to 4.2 MHz
Channel 6 television	82 to 88 MHz
FM radio broadcasting	88 to 108 MHz
Cellular radio	824 to 891.5 MHz
Satellite television downlinks (C-band)	3.7 to 4.2 GHz
Digital satellite television	12.2 to 12.7 GHz

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

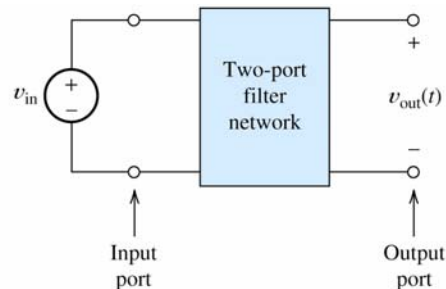

**Figure 6.3** When an input signal  $v_{in}(t)$  is applied to the input port of a filter, some components are passed to the output port while others are not, depending on their frequencies. Thus,  $v_{out}(t)$  contains some of the components of  $v_{in}(t)$  but not others. Usually, the amplitudes and phases of the components are altered in passing through the filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Filters

Filters process the sinusoid components of an input signal differently depending of the frequency of each component. Often, the goal of the filter is to retain the components in certain frequency ranges and to reject components in other ranges.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Transfer Functions

The **transfer function**  $H(f)$  of the two-port filter is defined to be the ratio of the phasor output voltage to the phasor input voltage as a function of frequency:

$$H(f) = \frac{V_{\text{out}}}{V_{\text{in}}}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

The magnitude of the transfer function shows how the amplitude of each frequency component is affected by the filter. Similarly, the phase of the transfer function shows how the phase of each frequency component is affected by the filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

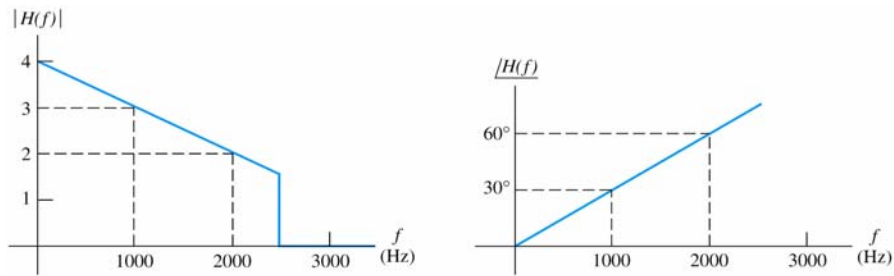


Figure 6.4 The transfer function of a filter. See Examples 6.1 and 6.2.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## **Determining the output of a filter for an input with multiple components:**


- 1.** Determine the frequency and phasor representation for each input component.
- 2.** Determine the (complex) value of the transfer function for each component.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

- 3.** Obtain the phasor for each output component by multiplying the phasor for each input component by the corresponding transfer-function value.
- 4.** Convert the phasors for the output components into time functions of various frequencies. Add these time functions to produce the output.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



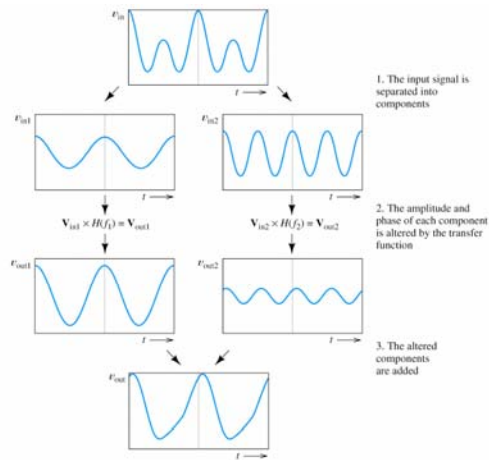


**Figure 6.5** Filters behave as if they separate the input into components, modify the amplitudes and phases of the components, and add the altered components to produce the output.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Linear circuits behave as if they:


1. Separate the input signal into components having various frequencies.
2. Alter the amplitude and phase of each component depending on its frequency.
3. Add the altered components to produce the output signal.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

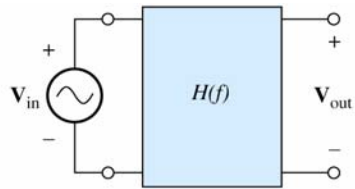

**Figure 6.6** To measure the transfer function, we apply a sinusoidal input signal, measure the amplitudes and phases of input and output in steady state, and then divide the phasor output by the phasor input. The procedure is repeated for each frequency of interest.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

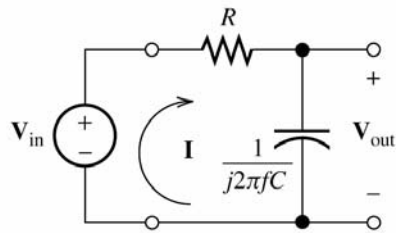


**Figure 6.7** A first-order lowpass filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

# FIRST-ORDER LOWPASS FILTERS

$$f_B = \frac{1}{2\pi RC} \quad |H(f)| = \frac{1}{\sqrt{1 + (f/f_B)^2}}$$
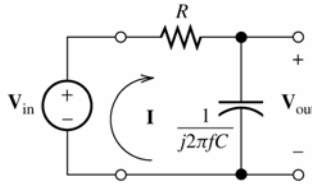
$$H(f) = \frac{1}{1 + j(f/f_B)} \quad \angle H(f) = -\arctan\left(\frac{f}{f_B}\right)$$



ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


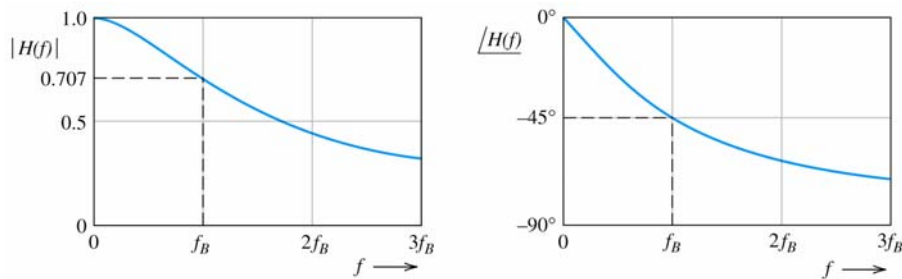



Figure 6.8 Magnitude and phase of the first-order lowpass transfer function versus frequency.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

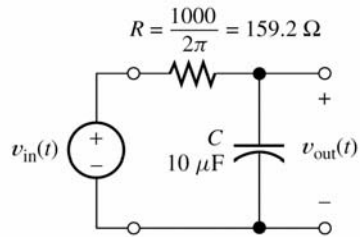


**Figure 6.9** Circuit of Example 6.3. The resistance has been picked so the break frequency turns out to be a convenient value.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

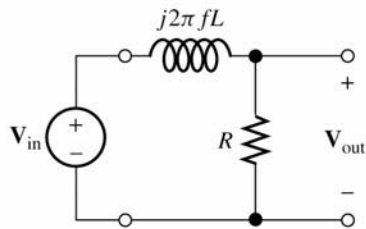

**Figure 6.10** Another first-order lowpass filter; see Exercise 6.4.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

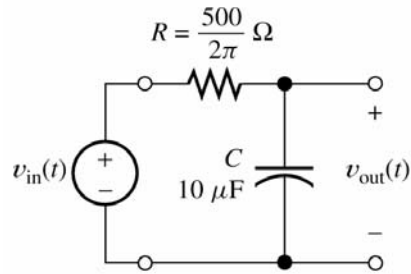

**Figure 6.11** Circuit for Exercise 6.5.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## DECIBELS, THE CASCADE CONNECTION, AND LOGARITHMIC FREQUENCY SCALES


$$|H(f)|_{\text{dB}} = 20 \log |H(f)|$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

**Table 6.2. Transfer-Function Magnitudes and Their Decibel Equivalents**

$ H(f) $	$ H(f) _{\text{dB}}$
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
1/2	-6
0.1	-20
0.01	-40

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

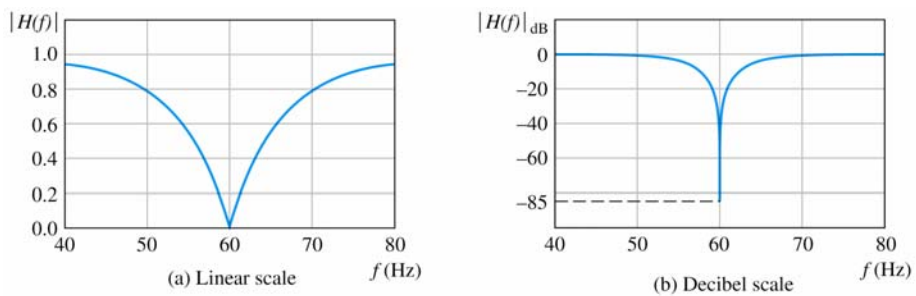

**Figure 6.12** Transfer-function magnitude of a notch filter used to reduce hum in audio signals.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

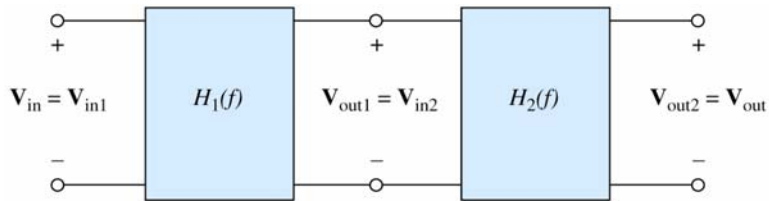



Figure 6.13 Cascade connection of two two-port circuits.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Cascaded Two-Port Networks

$$H(f) = H_1(f) \times H_2(f)$$

$$|H(f)|_{\text{dB}} = |H_1(f)|_{\text{dB}} + |H_2(f)|_{\text{dB}}$$

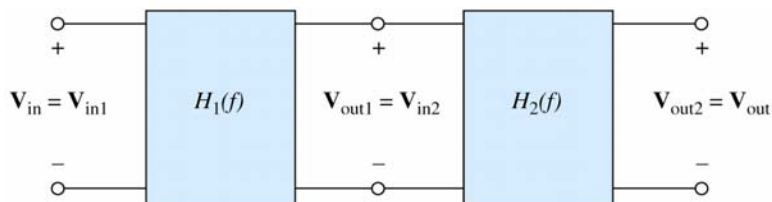

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

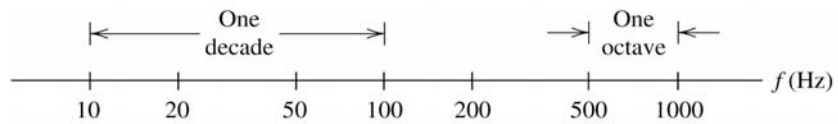


Figure 6.14 Logarithmic frequency scale.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Logarithmic Frequency Scales

On a logarithmic scale, the variable is multiplied by a given factor for equal increments of length along the

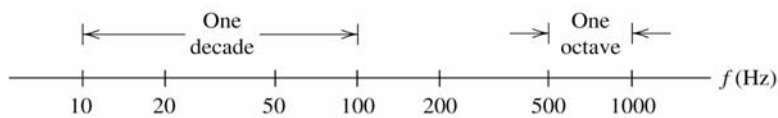


Figure 6.14 Logarithmic frequency scale.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




A **decade** is a range of frequencies for which the ratio of the highest frequency to the lowest is 10.

$$\text{number of decades} = \log\left(\frac{f_2}{f_1}\right)$$

An **octave** is a two-to-one change in frequency

$$\text{number of octaves} = \log_2\left(\frac{f_2}{f_1}\right) = \left(\frac{\log(f_2/f_1)}{\log(2)}\right)$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

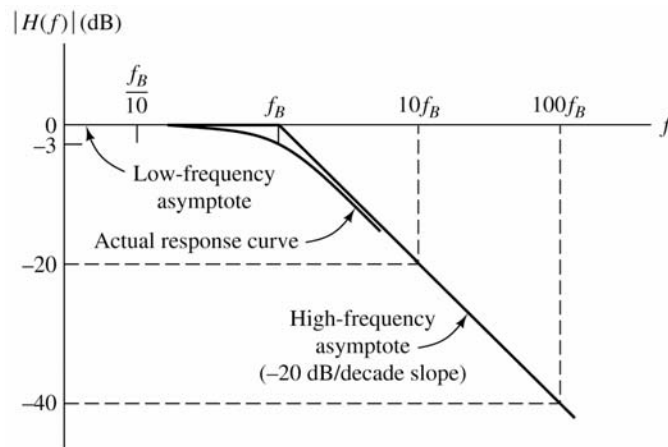

**Figure 6.15** Magnitude Bode plot for the first-order lowpass filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

# BODE PLOTS

A Bode plot shows the magnitude of a network function in decibels versus frequency using a logarithmic scale for frequency.

$$H(f) = \frac{1}{1 + j(f/f_B)}$$

$$|H(f)|_{\text{dB}} = -10 \log \left[ 1 + \left( \frac{f}{f_B} \right)^2 \right]$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


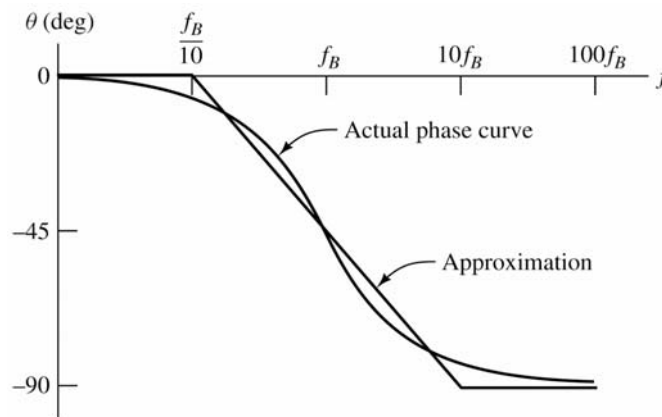



Figure 6.16 Phase Bode plot for the first-order lowpass filter.

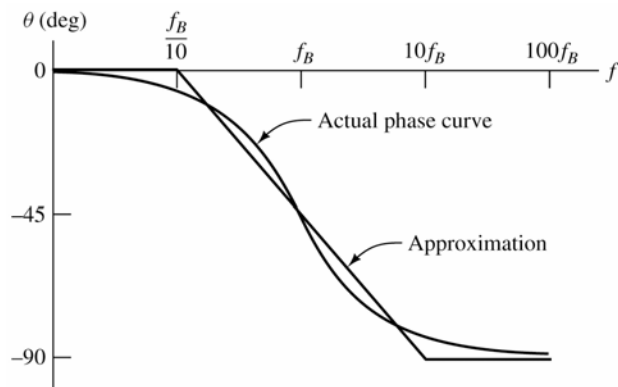ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



1. A horizontal line at zero for  $f < f_B/10$ .
2. A sloping line from zero phase at  $f_B/10$  to  $-90^\circ$  at  $10f_B$ .
3. A horizontal line at  $-90^\circ$  for  $f > 10f_B$ .

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

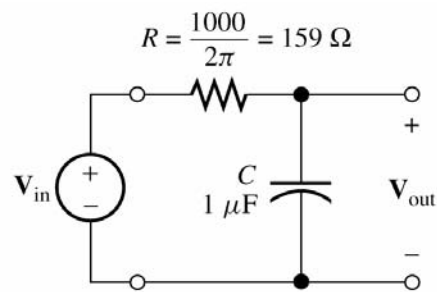

**Figure 6.17** Circuit for Exercise 6.11.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

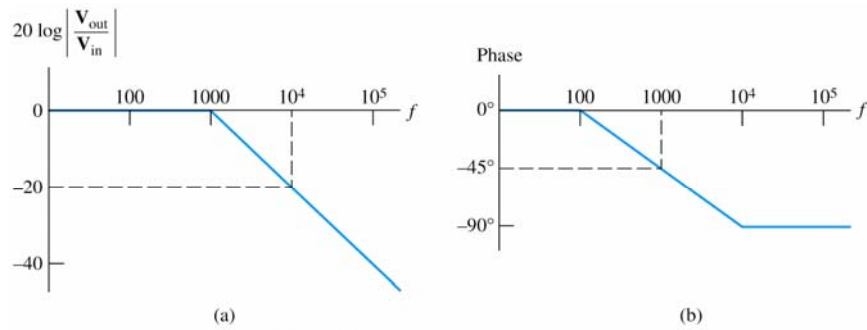


Figure 6.18 Answers for Exercise 6.11.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

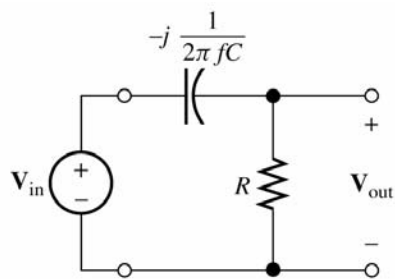



Figure 6.19 First-order highpass filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

# FIRST-ORDER HIGHPASS FILTERS

$$H(f) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j(f/f_B)}{1 + j(f/f_B)}$$

$$f_B = \frac{1}{2\pi RC}$$

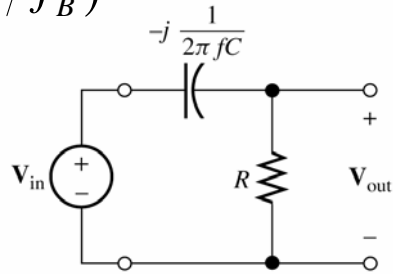

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


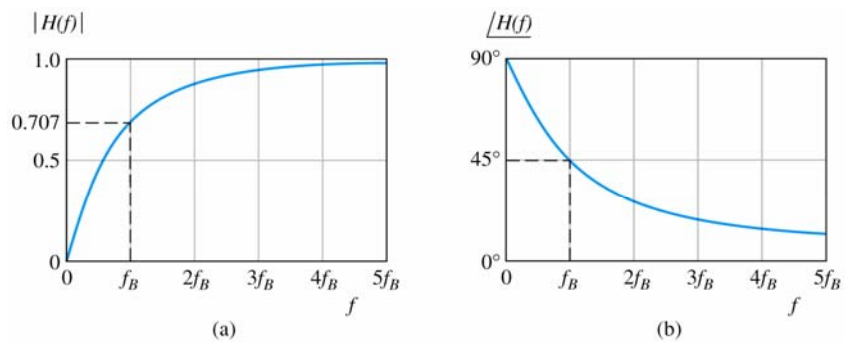



Figure 6.20 Magnitude and phase for the first-order highpass transfer function.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

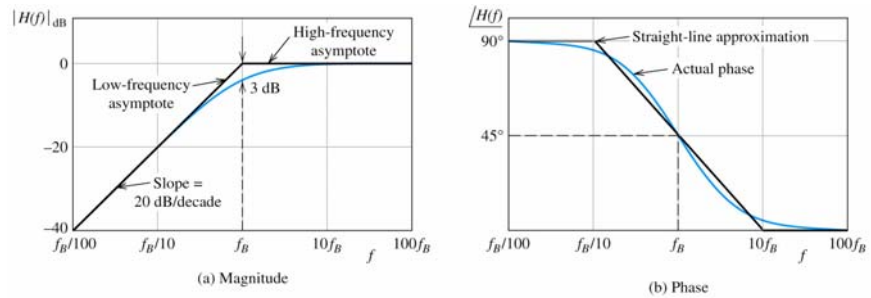

**Figure 6.21** Bode plots for the first-order highpass filter.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

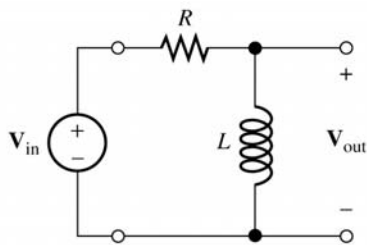

**Figure 6.22** Circuit for Exercise 6.13.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Computer-Generated Bode Plot

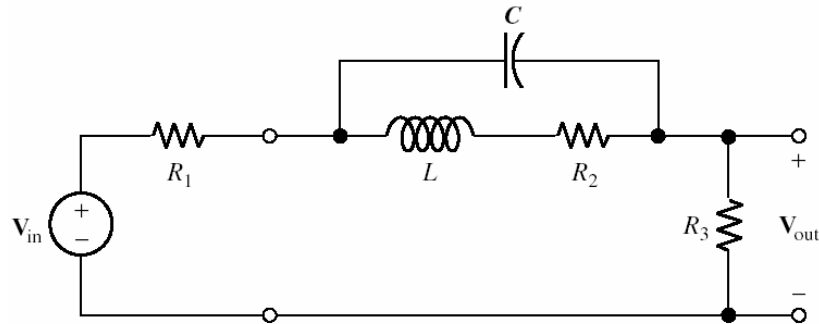

$$R_1 = 90 \Omega$$

$$L = 100 \text{ mH}$$

$$R_2 = 10 \Omega$$

$$C = 0.1 \mu\text{F}$$

$$R_3 = 100 \Omega$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

$$H(0) = \frac{R_3}{R_1 + R_2 + R_3} = 0.5$$

$$H_{\text{dB}}(0) = 20 \log(0.5) = -6 \text{ dB}$$

$$H(\infty) = \frac{R_3}{R_1 + R_3} = 0.5263$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

$$H_{\text{dB}}(\infty) = 20 \log(0.5263) = -5.575 \text{ dB}$$

$$H(f) = \frac{R_3}{R_1 + R_3 + 1/[j\omega C + 1/(R_2 + j\omega L)]}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


```

R1 = 90
R2 = 10
R3 = 100
L = 0.1
C = 1e-7
logf = 1:0.001:5;
f = 10.^logf;
w = 2*pi*f;
H = R3./(R1+R3+1./(j*w*C + 1./(R2 + j*w*L)));
semilogx(f,20*log10(abs(H)))


```

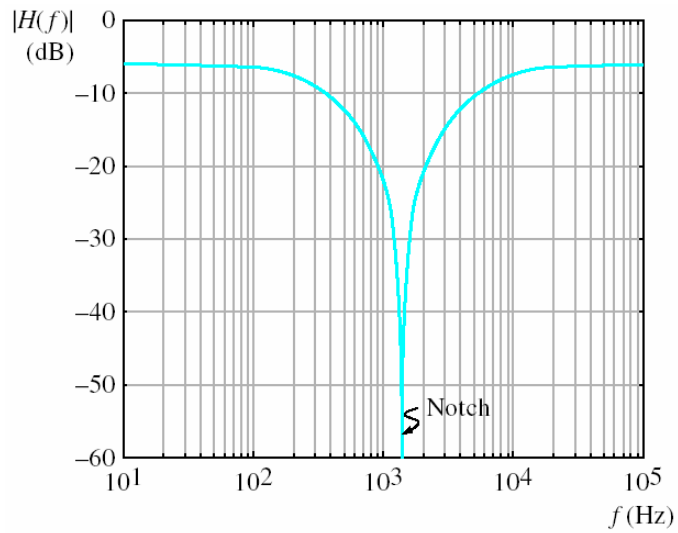ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.





ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

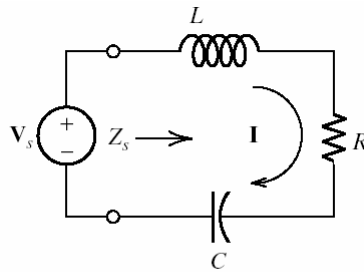

**Figure 6.25** The series resonant circuit.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

# SERIES RESONANCE

Resonance is a phenomenon that can be observed in mechanical systems and electrical circuits.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$$Q_s = \frac{1}{2\pi f_0 CR}$$

$$Q_s = \frac{2\pi f_0 L}{R}$$
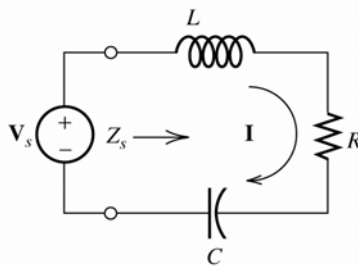
$$Z_s(f) = R \left[ 1 + jQ_s \left( \frac{f}{f_0} - \frac{f_0}{f} \right) \right]$$




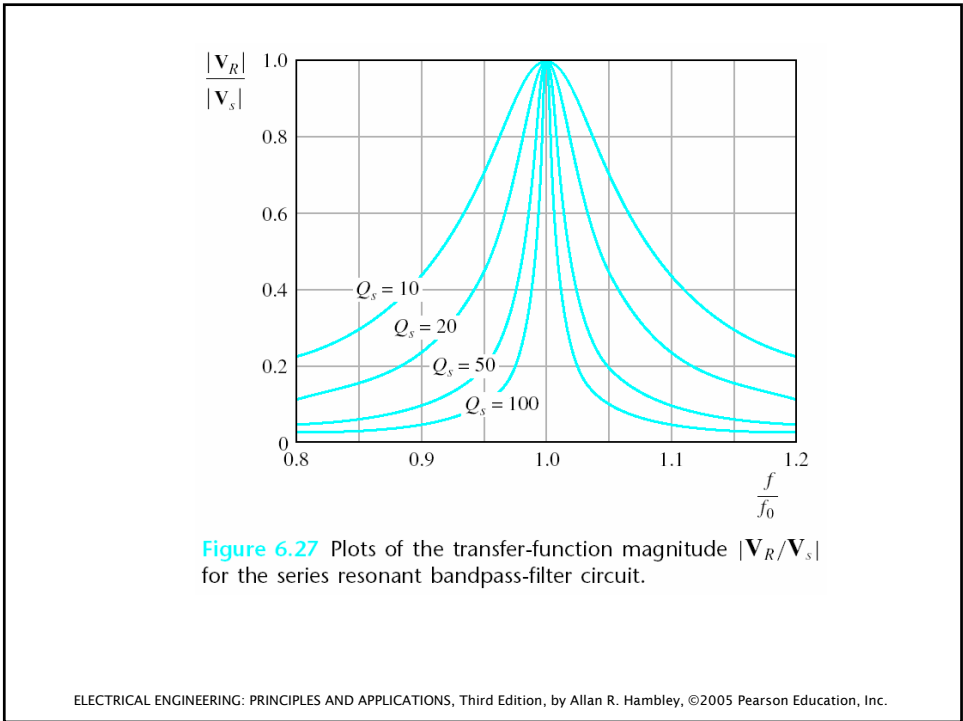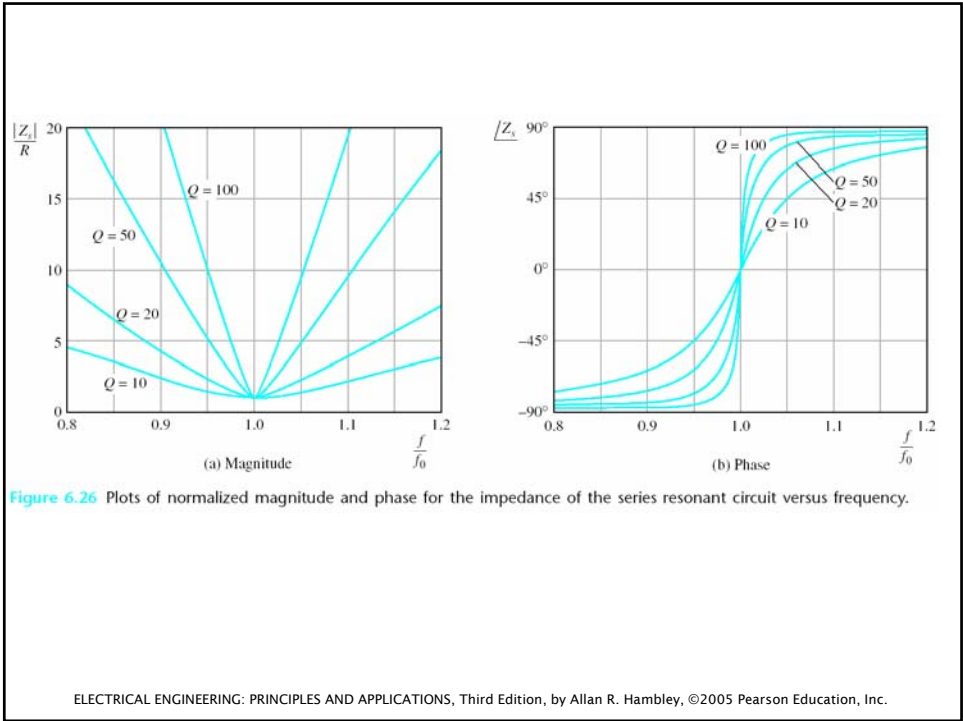ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



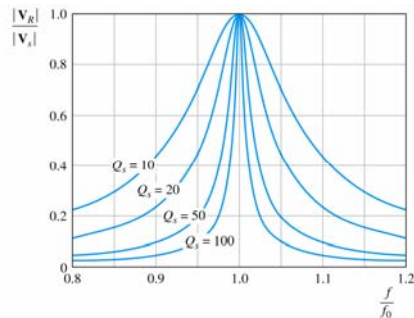
## Series Resonant Circuit as a Bandpass Filter

$$\frac{\mathbf{V}_R}{\mathbf{V}_s} = \frac{1}{1 + jQ_s(f/f_0 - f_0/f)}$$



ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

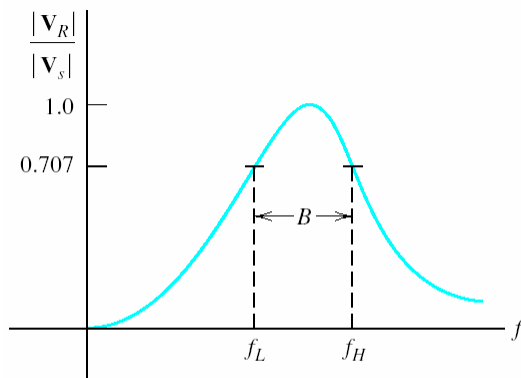


**Figure 6.28** The bandwidth  $B$  is equal to the difference between the half-power frequencies.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

$$B = f_H - f_L \qquad f_H \cong f_0 + \frac{B}{2}$$

$$B = \frac{f_0}{Q_s} \qquad f_L \cong f_0 - \frac{B}{2}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

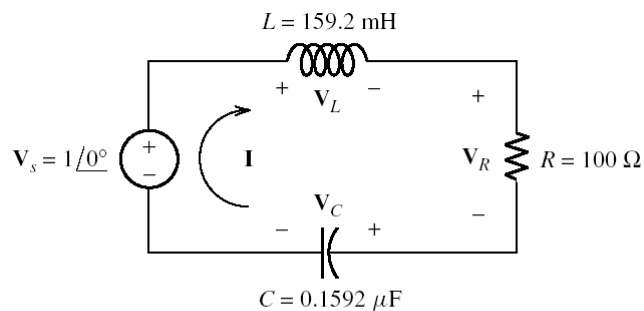

**Figure 6.29** Series resonant circuit of Example 6.6. (The component values have been selected so the resonant frequency and  $Q_s$  turn out to be round numbers.)

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

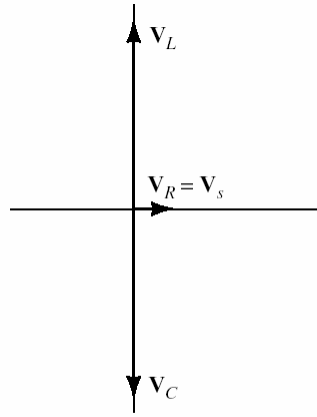


Figure 6.30 Phasor diagram for Example 6.6.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

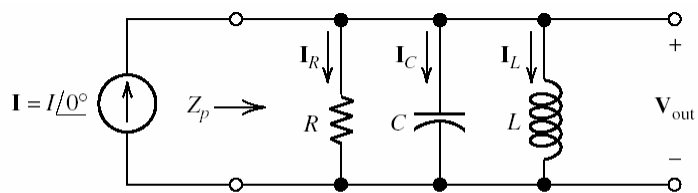


Figure 6.31 The parallel resonant circuit.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

# PARALLEL RESONANCE


$$Z_p = \frac{1}{(1/R) + j2\pi fC - j(1/2\pi fL)}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


$$Q_p = \frac{R}{2\pi f_0 L}$$

$$Q_p = 2\pi f_0 CR$$
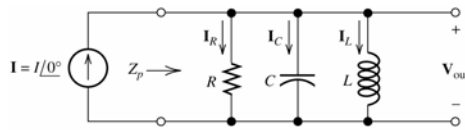
$$Z_p = \frac{R}{1 + jQ_p(f/f_0 - f_0/f)}$$



ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

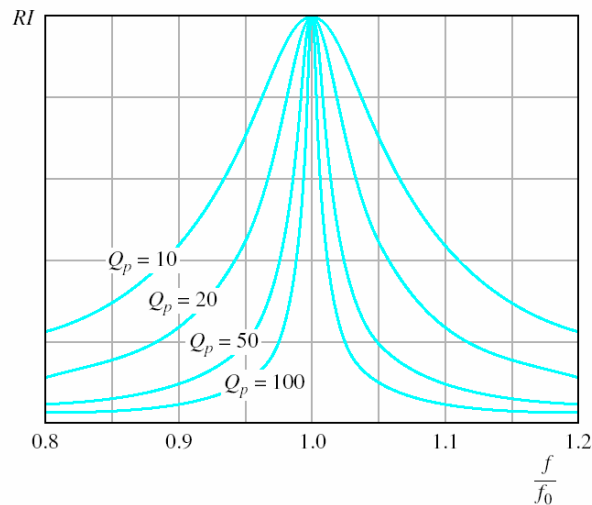

**Figure 6.32** Voltage across the parallel resonant circuit for a constant-amplitude variable-frequency current source.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.



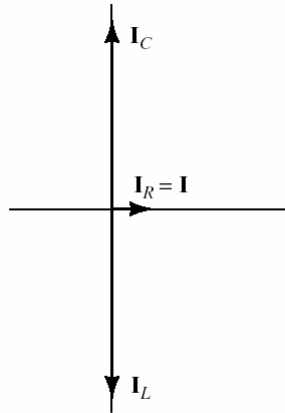


Figure 6.33 Phasor diagram for Example 6.7.

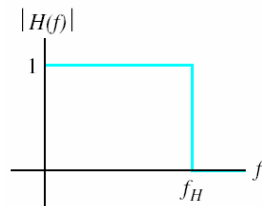
ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




(a) Lowpass

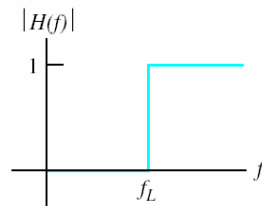

(b) Highpass

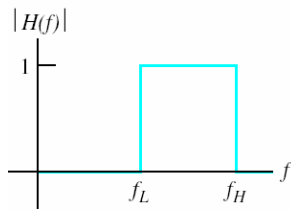

(c) Bandpass

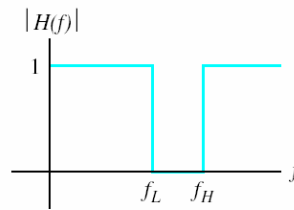


(d) Band reject

Figure 6.34 Transfer functions of ideal filters.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




# Ideal Filters

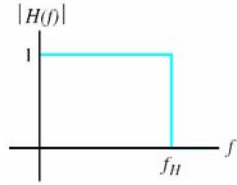


(a) Lowpass

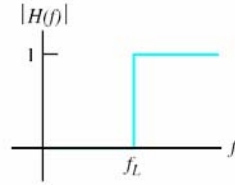

(b) Highpass

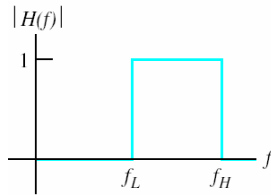

(c) Bandpass

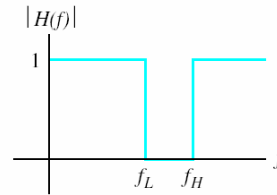

(d) Band reject

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

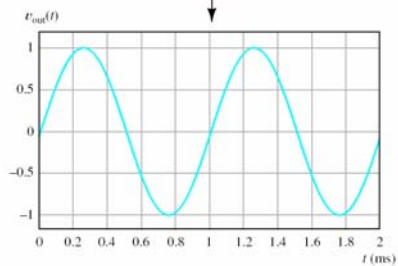
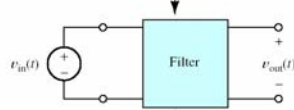
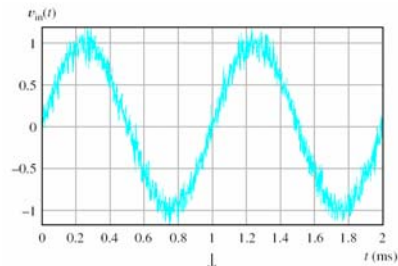


Figure 6.35 The input signal  $v_{in}$  consists of a 1-kHz sine wave plus high-frequency noise. By passing  $v_{in}$  through an ideal lowpass filter with the proper cutoff frequency, the sine wave is passed and the noise is rejected, resulting in a clean output signal.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

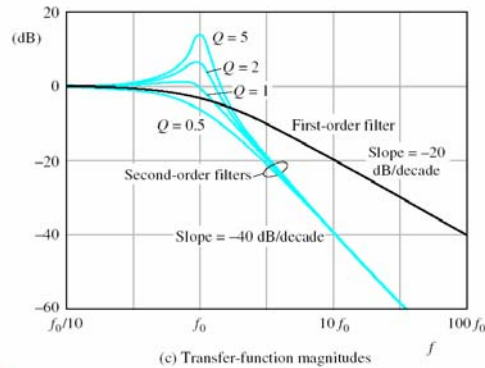
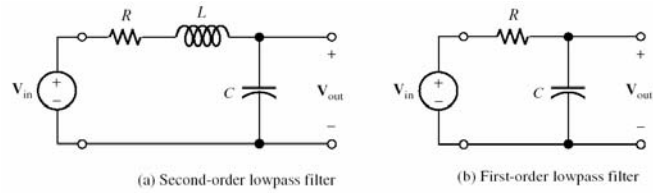




Figure 6.36 Lowpass filter circuits and their transfer-function magnitudes versus frequency.



ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## Second-Order Lowpass Filter

$$H(f) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-jQ_s(f_0/f)}{1 + jQ_s(f/f_0 - f_0/f)}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

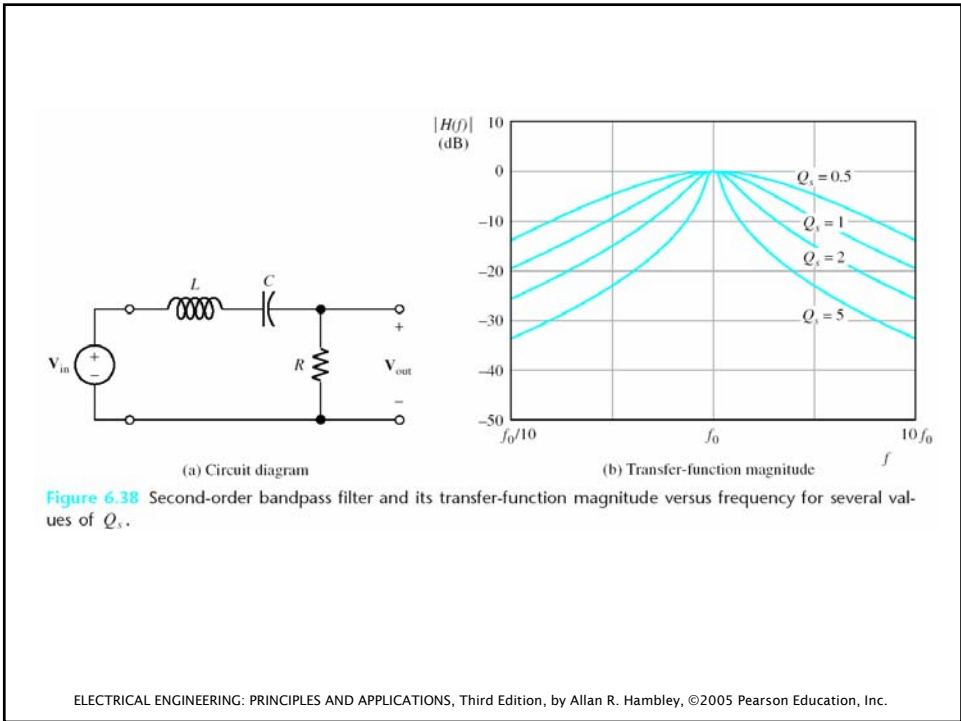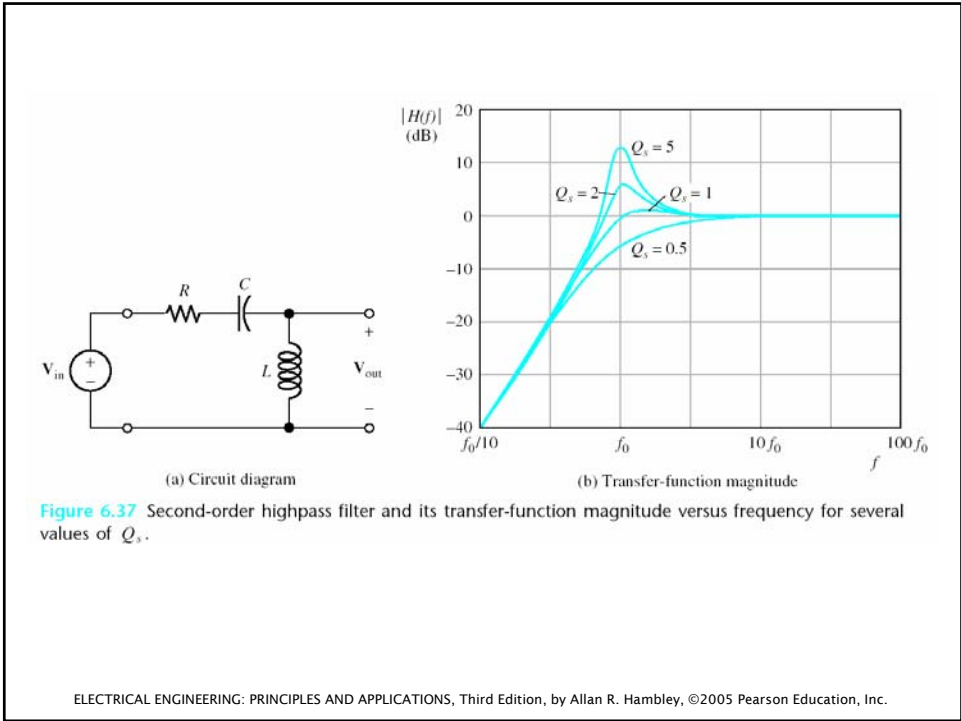

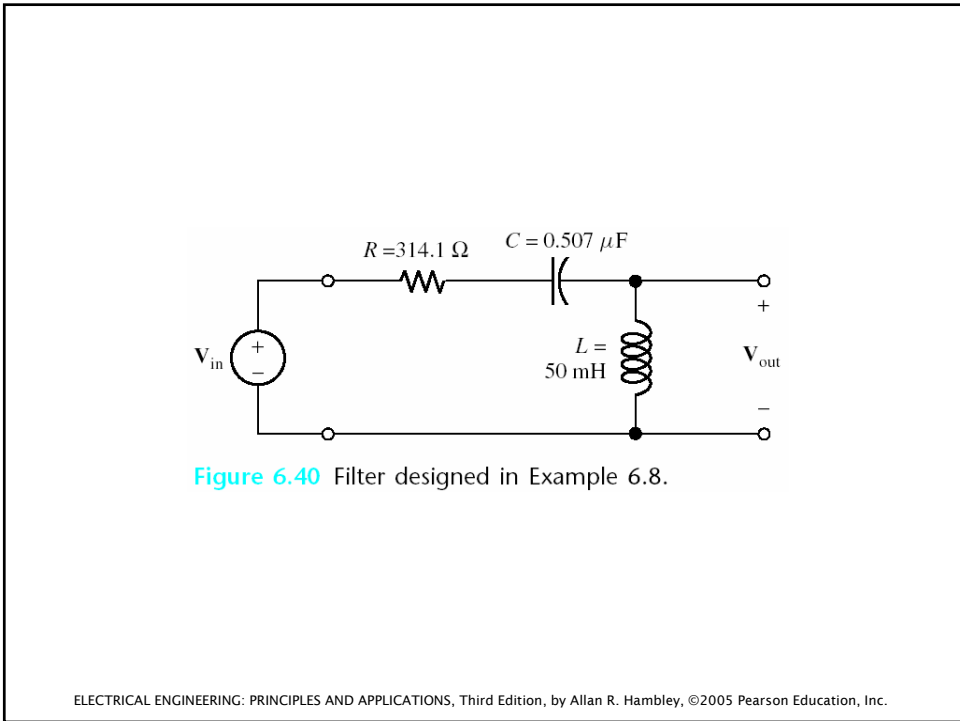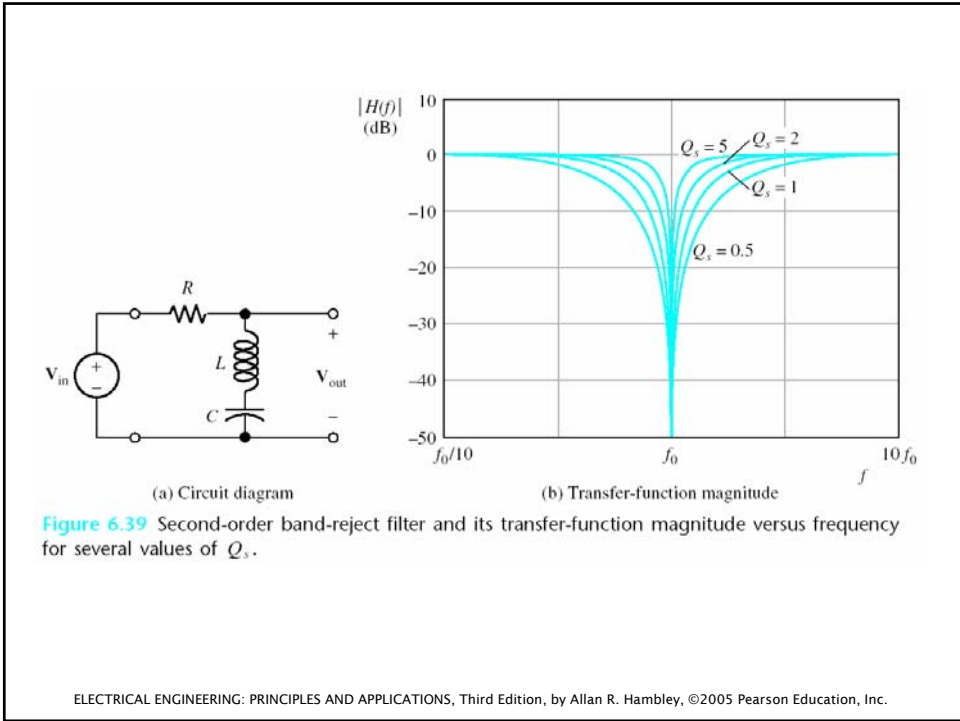

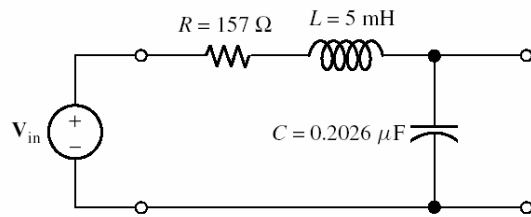


Figure 6.41 Answer for Exercise 6.20.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

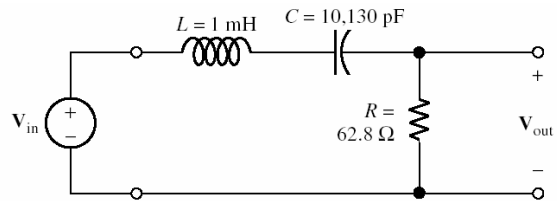


Figure 6.42 Answer for Exercise 6.21.


ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.




**Figure 6.43** Generic block diagram of a digital signal-processing (DSP) system.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

## DIGITAL SIGNAL PROCESSING


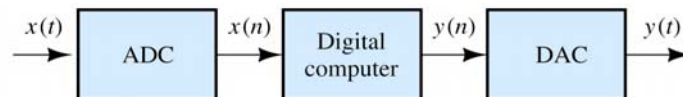


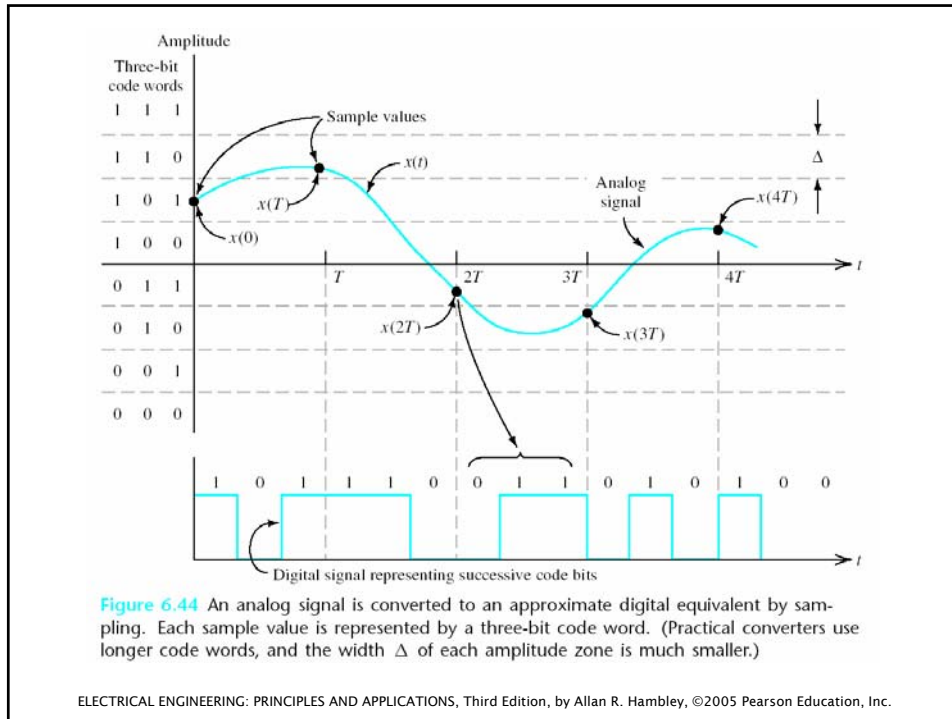ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


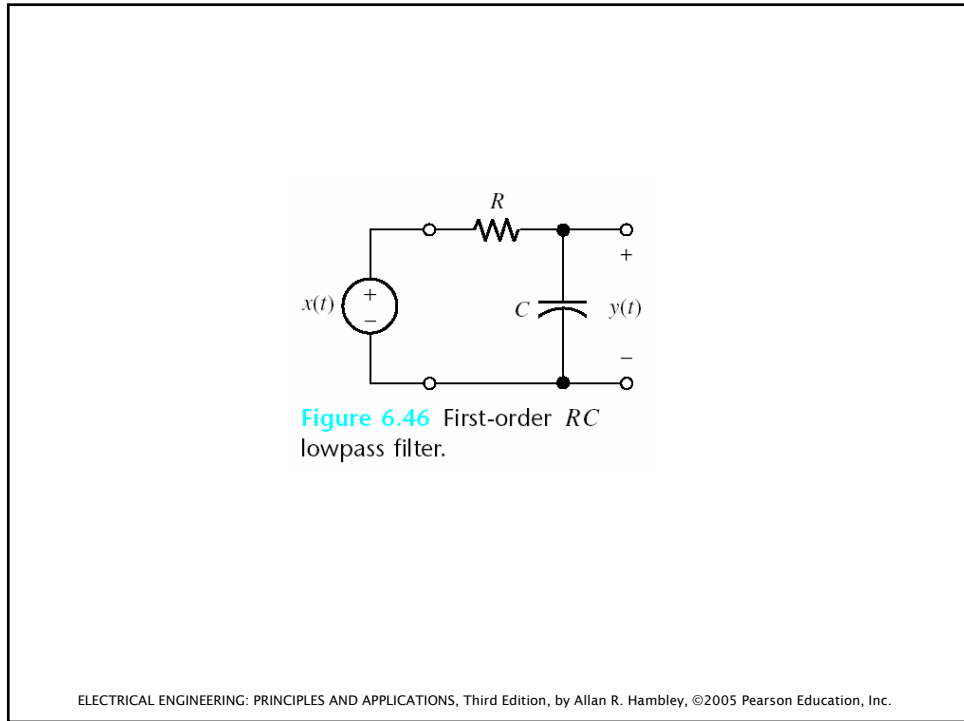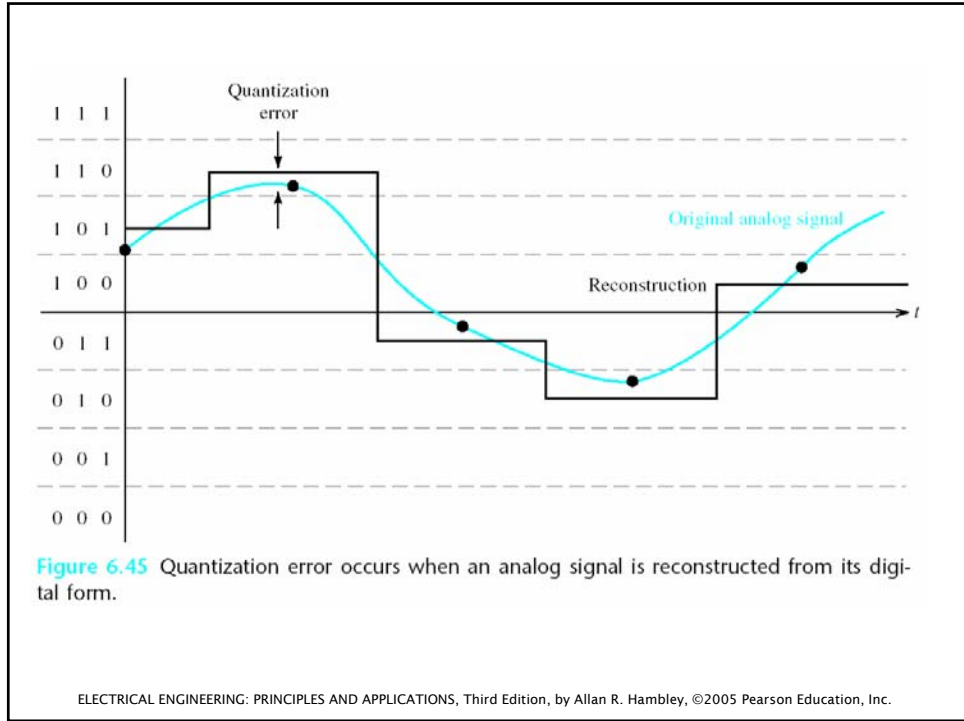
## Conversion of Signals from Analog to Digital Form

If a signal contains no components with frequencies higher than  $f_H$ , the signal can be exactly reconstructed from its samples, provided that the sampling rate  $f_s$  is selected to be more than twice  $f_H$ .





# Digital Lowpass Filter

$$y(n] = ay(n - 1) + (1 - a)x(n)$$

$$a = \frac{\tau/T}{1 + \tau/T}$$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.


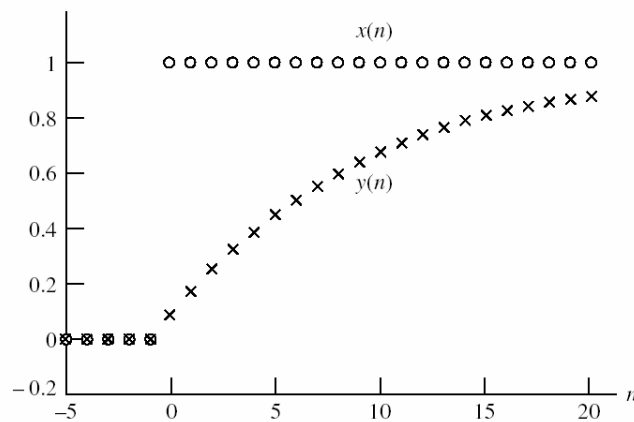



Figure 6.47 Step input and corresponding output of a first-order digital lowpass filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

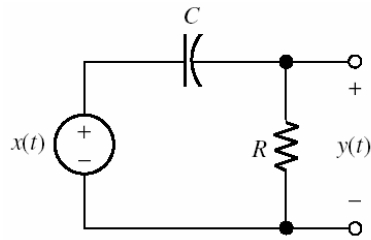

**Figure 6.48** RC highpass filter. See Exercise 6.23.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

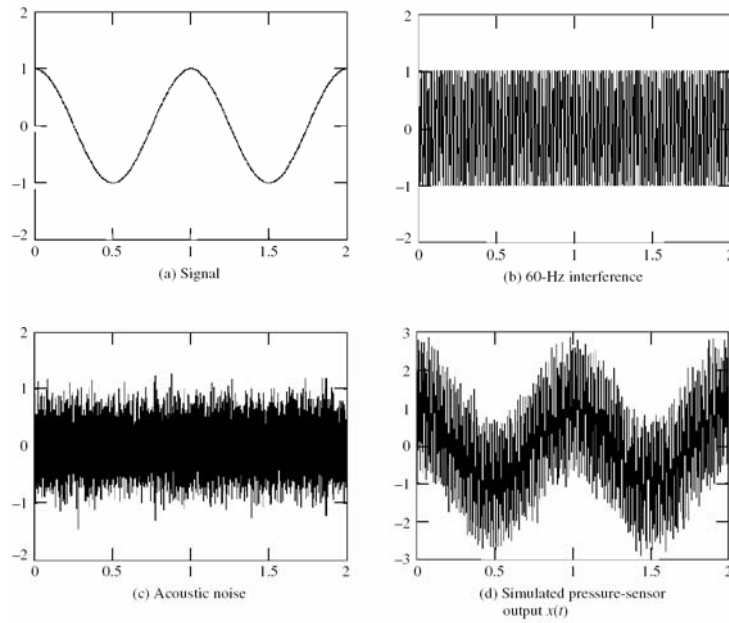

**Figure 6.49** Simulated pressure-sensor output and its components.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

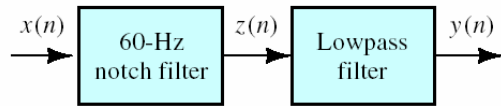


Figure 6.50 Digital filter.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.

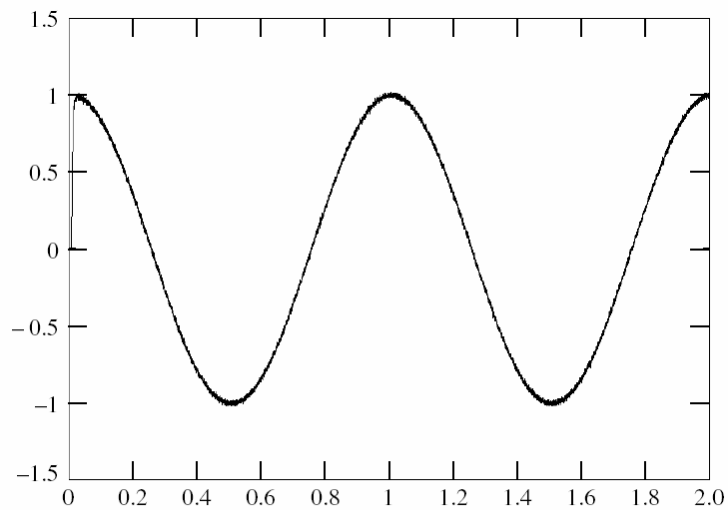


Figure 6.51 Output signal.

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Third Edition, by Allan R. Hambley, ©2005 Pearson Education, Inc.