

Electrical Package Design

TKK 2009 Lecture 2

James E. Morris
Dept of Electrical & Computer Engineering
Portland State University



Electrical Package Design

- Lecture topics A: Introduction
 - CMOS; R, L, & C
- Lecture topics B: Transmission lines
 - Z_0 , velocity, lossless lines, lossy lines
- Lecture topics C: Transmission lines
 - Transmission line reflections
- Lecture topics D: Transmission lines
 - Crosstalk
- Lecture topics E: Electromagnetism & Modeling
- Lecture topics F: Electromagnetic Compatibility

Lecture topics A: Introduction CMOS; R, L, & C

1. Interconnect modeling
2. Resistance, inductance, & capacitance
 - R, L, & C
3. Skin effect
4. Ground planes
5. MOS devices and CMOS
6. Delta-I (ΔI) switching noise

3

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

1. Interconnect modeling

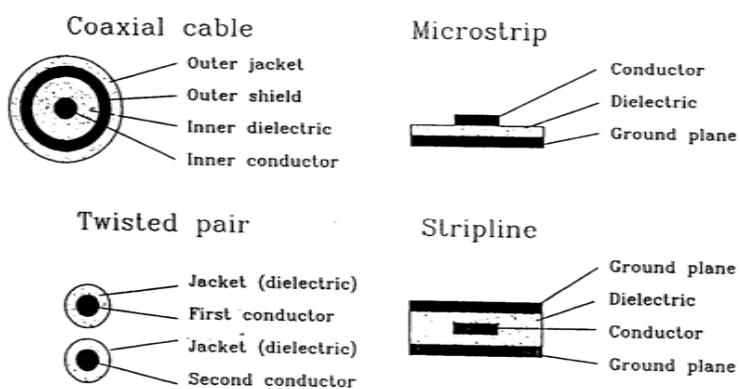


Figure 4.4 Cross sections of popular transmission line geometries.


4.2.1 Ideal Distortionless, Lossless Transmission Line

4

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Three modeling approaches:

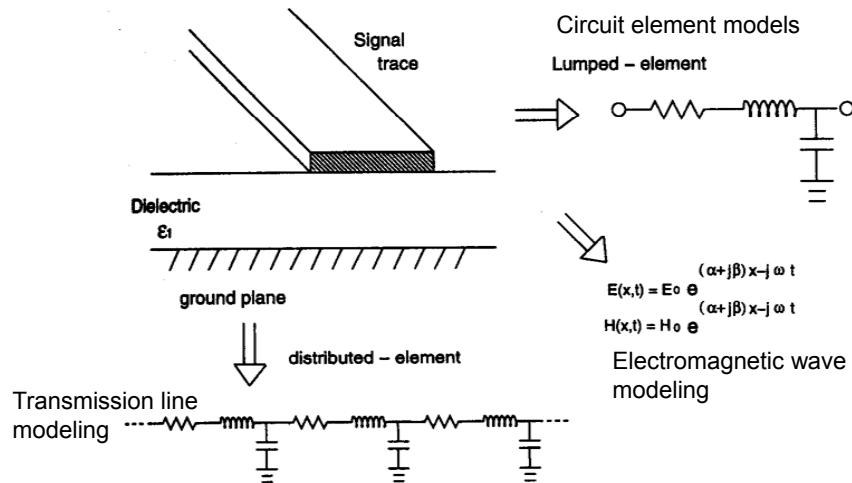

5

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

(a) $\omega L \gg R$, (b) $R \gg \omega L$, (c) $R \approx 0$

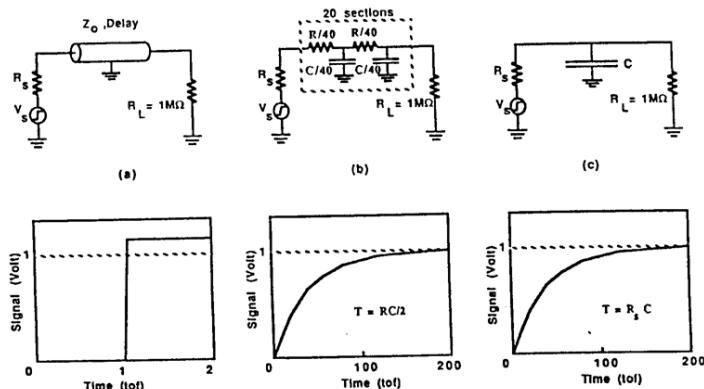


Figure 5-7 Simplified SPICE circuits & signal load responses for limiting propagation regimes. (a)Time-of-flight ($R_s < Z_0$) (b)lossy-line diffusion (c) R_s -limited; time scales are in units of time-of-flights


6

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

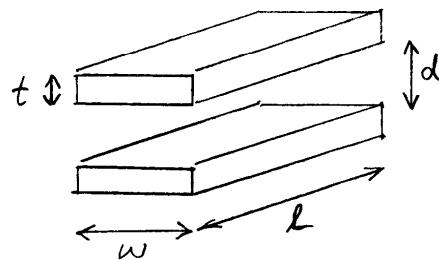2. R, G, L, and C

- Conductor:
- $R = \rho L/A = \rho L/wt$
- $R/L = \rho/wt$
- Dielectric:
- $G = \sigma A/d = \sigma Lw/d$
- $G/L = \sigma w/d$
- $C = \epsilon A/d = \epsilon Lw/d$
- $C/L = \epsilon w/d$



- Note: L=length in this slide; used for inductance later


7

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Capacitance/unit length: Generalized geometries

- (a) "Visual" approximations

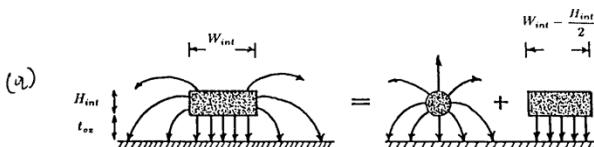

- (b) Method of images

- (c) Graphical approximations

- (d) Experimental field plotting

- (e) Numerical techniques
(mesh/iteration)

- (f) Analytical: $V=\sum V_i$
for charges Q_i

FIGURE 4.2 Modeling of the contribution of fringing fields to interconnection capacitance. Total wire capacitance can be thought of having two components: a parallel plate capacitance determined by the perpendicular field lines between the wire and the ground plane and a fringing field component, which can be approximated by the capacitance of a cylindrical wire with a diameter equal to interconnection thickness [4.3]. Reprinted by permission of Addison-Wesley Publishing Co.

reduced by $H_{int}/2$ to account for some second-order effects [4.4]. This yields the interconnection capacitance per unit length C_{int} as

$$C_{int} = \epsilon_{ox} \left\{ \frac{W_{int}}{t_{ox}} - \frac{H_{int}}{2t_{ox}} + \frac{2\pi}{\ln \left[1 + \frac{2t_{ox}}{H_{int}} \left(1 + \sqrt{1 + \frac{H_{int}}{t_{ox}}} \right) \right]} \right\}. \quad (4.5)$$

8

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

(g) Method of Moments: Example

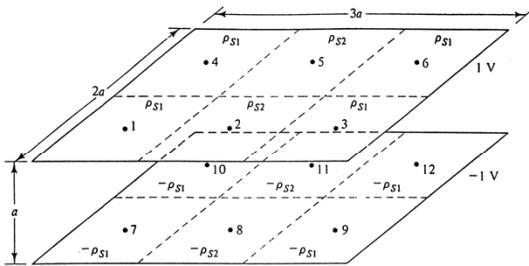


Figure 5.10. For finding the capacitance of a parallel-plate capacitor by the method of moments.

$$\text{For point 2 } \frac{\rho_{S2}a}{\pi\epsilon_0} \ln(1 + \sqrt{2}) + \frac{\rho_{S1}a^2}{4\pi\epsilon_0} \left(\frac{2}{a} + \frac{2}{\sqrt{2}a} - \frac{2}{\sqrt{2}a} - \frac{2}{\sqrt{3}a} \right) + \frac{\rho_{S2}a^2}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{a} - \frac{1}{\sqrt{2}a} \right) = 1 \quad (5.31b)$$

or

$$2.9101\rho_{S1} + 0.4226\rho_{S2} = \frac{4\pi\epsilon_0}{a} \quad (5.32a)$$

$$0.8453\rho_{S1} + 2.8184\rho_{S2} = \frac{4\pi\epsilon_0}{a} \quad (5.32b)$$

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

9

Method of Moments Example

PARALLEL PLATE CAPACITOR

$$C = \epsilon \frac{A}{d}$$

Field curvature \Rightarrow non-uniform surface charge distribution ρ_s

e.g. $3a \times 2a \times a$ capacitor. Charges ρ_{S1}, ρ_{S2} by symmetry. Assume charges at center of L's.

Potential at point 1 due to ρ_{S1} at point 4

$$\rightarrow \frac{(\rho_{S1} \times a^2)}{4\pi\epsilon a} \text{ at } z = \text{distance}$$

Potential at point 1 due to distributed charge $\rho_{S1}a^2$ on square #1 = $\frac{(\rho_{S1} \times a^2)}{\pi\epsilon a} \ln(1 + \sqrt{2})$

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

10

\therefore For fixed plate potentials $V_1, -V_2$


$$\text{Square #1: } V_1 = \frac{\rho_{S1}a}{4\pi\epsilon} \ln(1+\sqrt{2}) + \frac{\rho_{S1}a}{4\pi\epsilon} \left(\frac{1}{2} + 1 + \frac{1}{\sqrt{5}} - 1 - \frac{1}{\sqrt{5}} - \frac{1}{\sqrt{2}} \right) \\ + \frac{\rho_{S2}a}{4\pi\epsilon} \left(\frac{1}{2} + \frac{1}{\sqrt{2}} - \frac{1}{\sqrt{2}} - \frac{1}{\sqrt{3}} \right) = V_1$$

$$\text{Square #2: } V_2 = \frac{\rho_{S2}a}{4\pi\epsilon} \ln(1+\sqrt{2}) + \frac{\rho_{S1}a}{4\pi\epsilon} \left(2 + \frac{2}{\sqrt{2}} - \frac{2}{\sqrt{2}} - \frac{2}{\sqrt{3}} \right) \\ + \frac{\rho_{S2}a}{4\pi\epsilon} \left(1 - 1 - \frac{1}{\sqrt{2}} \right) = V_2$$

$$\text{Solve: } \rho_{S1} = 3.8378 \epsilon/a \quad \rho_{S2} = 3.3075 \epsilon/a$$

$$\therefore \text{Total } C = 21.9662 \epsilon a \quad kC = Q/a = 10.983 \epsilon, \text{ of } 6\epsilon.$$

Inductance of a Straight Wire

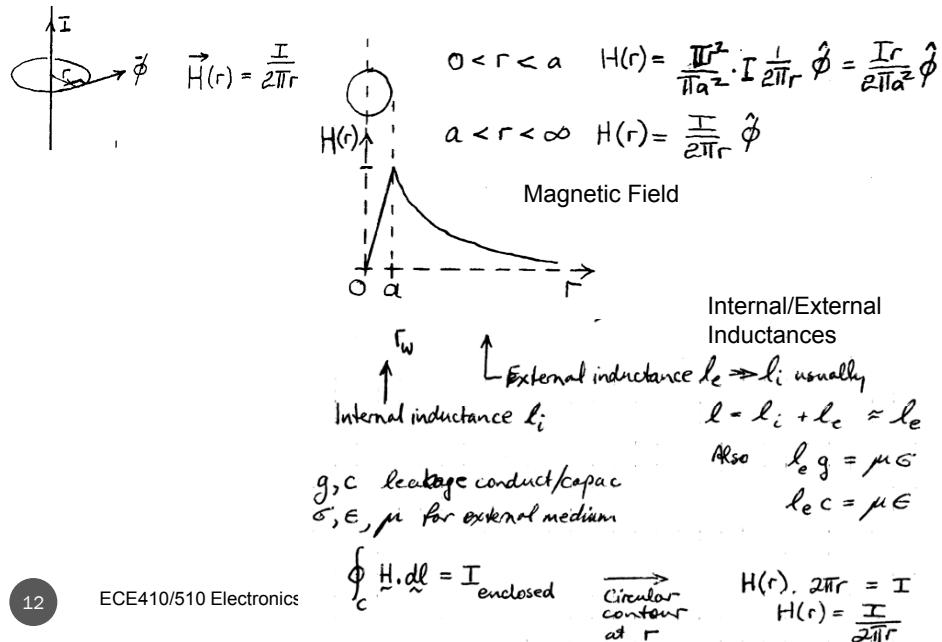

Internal Inductance

low freq — uniform current.


$$I_{\text{encl},i} = \pi r^2 \left(\frac{I}{\pi r_w^2} \right) = I \left(\frac{r}{r_w} \right)^2$$

$$\therefore H(r) \cdot 2\pi r = I \left(\frac{r}{r_w} \right)^2 \Rightarrow H(r) = \frac{I}{2\pi r_w^2} \cdot r$$

&

$$\Psi_i = \int_s B(r) \cdot ds \Rightarrow \Psi_i \times L = \mu_0 \int_{r_w}^{r_w} \frac{I}{2\pi r_w^2} r \cdot \cancel{L} dr$$

per unit length

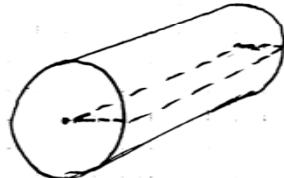

$$\Psi_i = \frac{\mu_0 I}{4\pi}$$


$$l_i = \frac{\mu_0}{4\pi} H/m$$

13

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

External Inductance: Basic formula

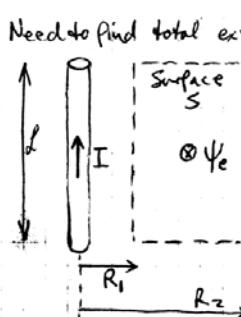

$$\begin{aligned} \text{Need to find total external flux} \quad \Psi_e &= \int_s B(r) \cdot ds \\ &= \int_{R_1}^{R_2} \mu_0 \frac{I}{2\pi r} dr \\ &= \frac{\mu_0 I}{2\pi} \ln \left(\frac{R_2}{R_1} \right) \end{aligned}$$


Note: To find $l_e = \frac{\Psi_e}{I} = \frac{\mu_0}{2\pi} \ln \left(\frac{R_2}{R_1} \right)$
over all space ($\frac{R_2}{R_1} \rightarrow \infty$)
requires assumption of specific geometries

14

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Compare:-

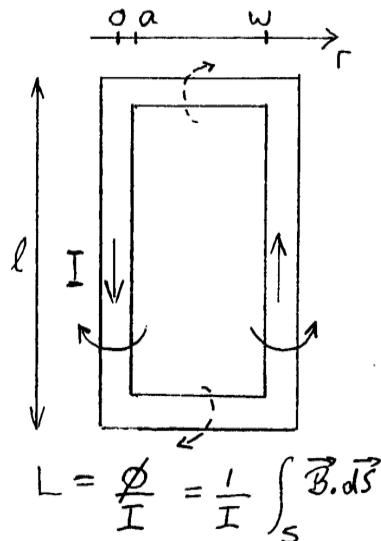

$$= \frac{\mu}{I} \int H \cdot d\vec{s}$$

$$\approx 2\frac{\mu l}{I} \left[\int_0^a \frac{I r}{2\pi a^2} dr + \int_a^w \frac{I}{2\pi r} dr \right]$$

$$L/l = 2 \left[\frac{\mu}{4\pi} \left(1 + 2 \ln \frac{w}{a} \right) \right]$$

Hence "partial" inductance

$$L = \frac{\mu_0}{4\pi} + \frac{\mu_0}{2\pi} \ln \frac{w}{a}$$

$$= L_i + L_e \approx L_e$$

15

ECE410/510 Electronics Packaging Fall 2005

4/16/2009


External Inductance: 2-wire line

(a) 2-wire line

Total flux between wires

$$l_e = \frac{\Phi_e}{I} = \frac{\mu_0 I}{2\pi} \left[\ln \left(\frac{s+r_{w1}}{r_{w1}} \right) + \ln \left(\frac{s+r_{w2}}{r_{w2}} \right) \right]$$
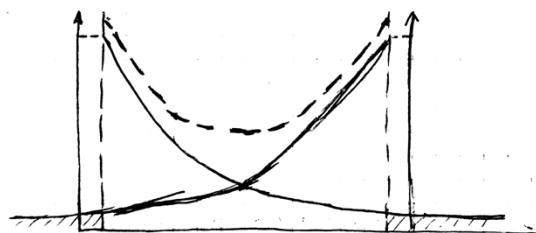
$$s \gg r_{w1} + r_{w2} = r_w \quad \frac{\mu_0}{2\pi} \ln \frac{s^2}{r_w^2} = \frac{\mu_0}{\pi} \ln \frac{s}{r_w}$$




16

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Straight Wire: Radial Electric Field

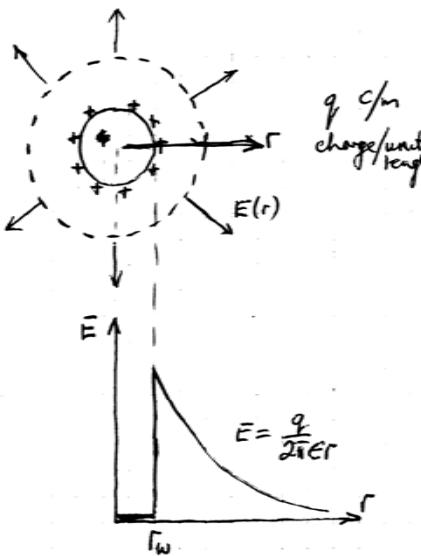

$$\oint_S \vec{E} \cdot d\vec{s} = Q_{\text{enc}}.$$

$$\epsilon E (2\pi r \times L) = q \times L$$

$$\therefore E(r) = \frac{q}{2\pi r \epsilon}$$

$$\& V = - \int_C \vec{E} \cdot d\vec{l}$$

$$= - \int_{R_1}^{R_2} \frac{q}{2\pi r \epsilon} dr$$

$$= \frac{q}{2\pi \epsilon} \ln \left(\frac{R_2}{R_1} \right)$$


17

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Magnetic and Electric Fields:
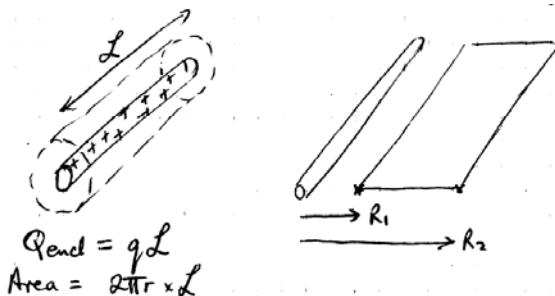
$$(2\pi)^{-1} \ln(R_2/R_1) = \epsilon V/q \text{ (electric)} = \psi_e / I \mu_0$$



$$Q_{\text{enc}} = qL$$

$$\text{Area} = 2\pi r \times L$$

$$\& \text{note } \frac{V \epsilon}{q} = \frac{\psi_e}{\mu_0 I}$$

$$l_e = \frac{\psi_e}{I} = \mu_0 \epsilon \frac{V}{q} = \mu_0 \epsilon C^{-1}$$


$$\text{i.e. } L_e \cdot C = \text{constant} = \mu_0 \epsilon$$

18

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Lead inductances

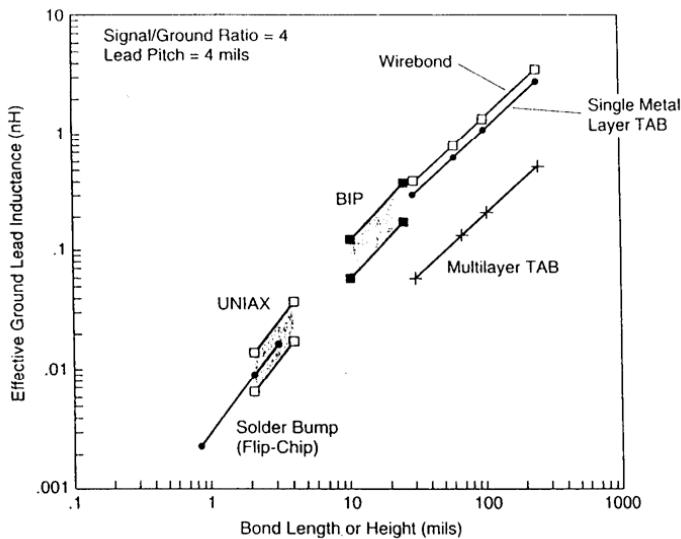

19

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

3. Skin Effect

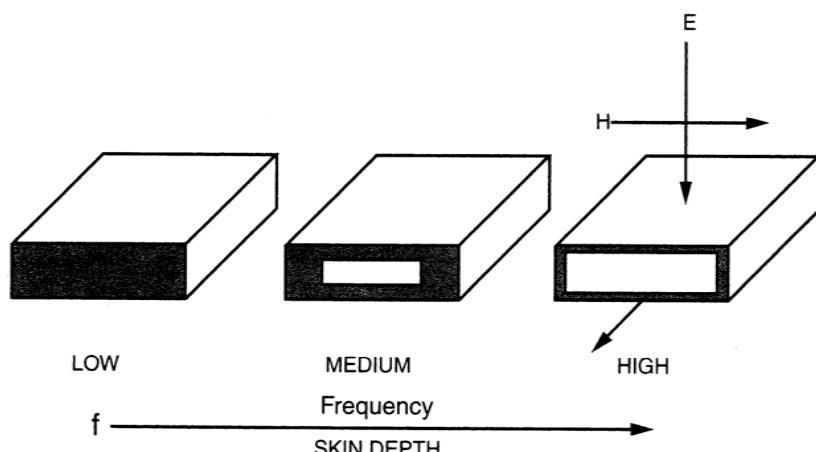



FIGURE 13.19 Effect of frequency on conductor cross section.

20

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

8. SKIN EFFECT

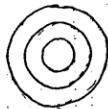

Consider wire to consist of concentric cylinders

Inductance of outer rings < Inductance of center rings

At high frequency, current path seeks lower inductance \rightarrow outer "skin"

$$\text{SKIN DEPTH } \delta = \left(\frac{2\rho}{\omega \mu} \right)^{1/2}$$

As current area decreases, resistance increases
($R = \rho \frac{l}{A}$)

$$R \propto \frac{1}{\delta} \propto \text{freq}^{1/2}$$

$$\text{and } L_{\text{skin}} \propto \text{freq}^{-1/2}$$

$$\text{Skin Resistance } \omega L_{\text{skin}} \propto \text{freq}^{1/2}$$

$$(L_{\text{internal}} \ll L_{\text{external}})$$

21

ECE410/510

16/2009

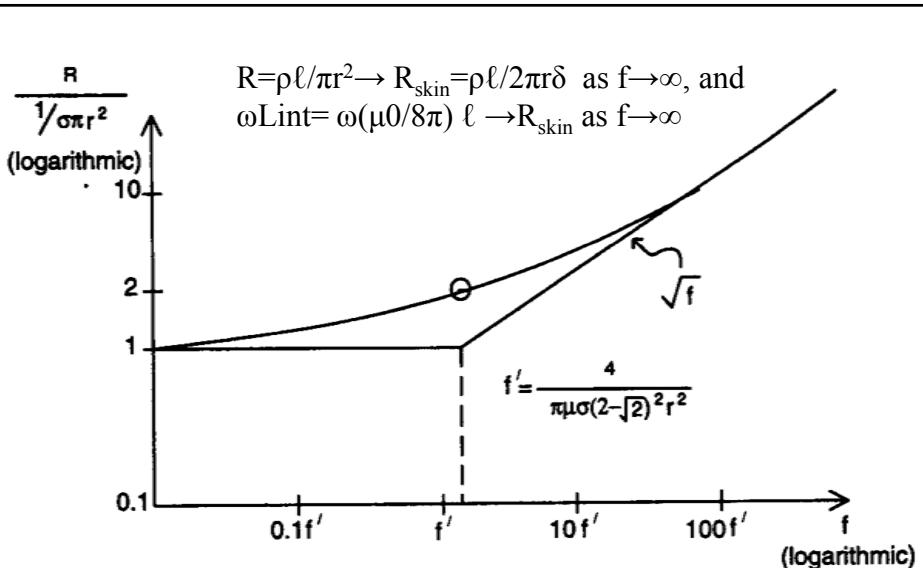



Figure 2.25 $R(f)$ for a wire of circular cross section, radius r .

22

ECE410/510 Electronics Packaging Fall 2005

4/16/2009


8. Skin Effect.

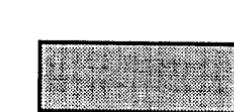

Current Distribution in the conductor at low frequencies.



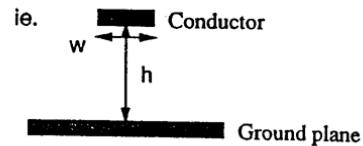Current distribution in the conductor at high frequencies (skin effect.) when $w/h \rightarrow 0$



Current distribution in the conductor at high frequencies (skin effect.) when $w/h \rightarrow \infty$



23

Figure 7.5 The skin effect.

4. Ground planes

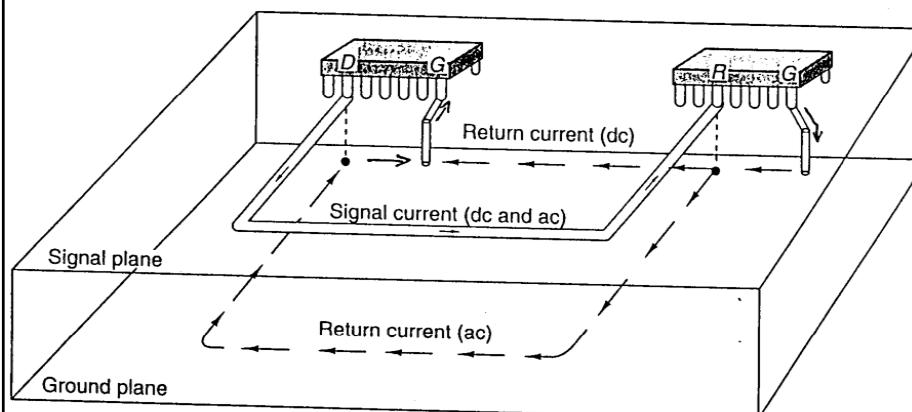


Figure 8.16 Paths for dc and ac ground returns on a multilayer board.

24

Loss of coupled return → inductance, EMI

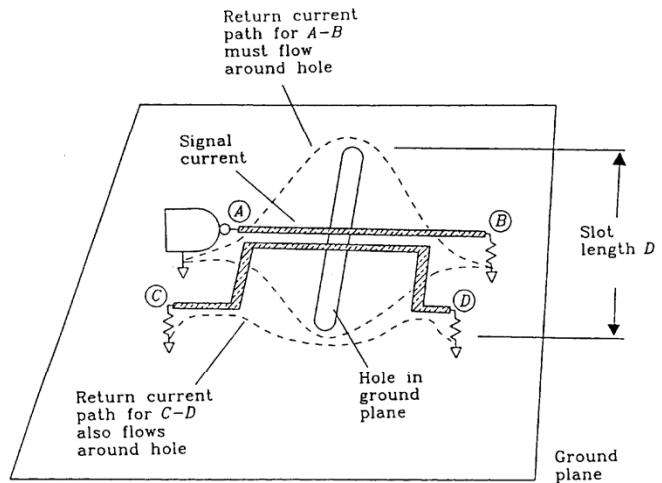



Figure 5.8 Crosstalk in a slotted ground plane.

25

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

5. MOS devices and CMOS

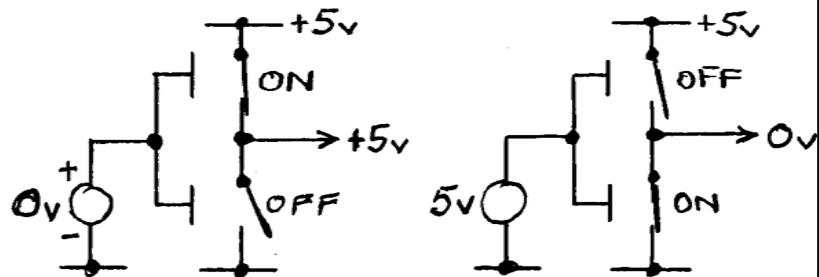

26

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Derivation of MOSFET characteristic equations

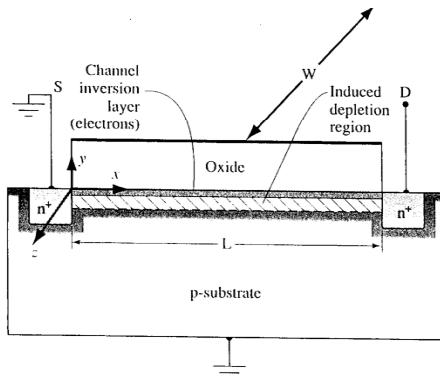


Figure 10.42 Geometry of a MOSFET for I_D versus V_{DS} derivation

Now set $(\mu W/2L)C_{ox} = k \rightarrow$

ECE410/510 Electronics Packaging Fall 2005

27

$$I(x) = \int \int J(x) dy dz$$

$$= W \cdot \mu \int_y \sigma(x) \frac{dV(x)}{dx} dy$$

$$I(x) dx = \mu W g(x) dV(x)$$

$$\text{and } g(x) = \frac{C_{ox}}{C_{ox}} [V_g - V(x)] \\ = C_{ox} [(V_g - V_T) - V(x)]$$

$$I_{DS} \int_0^L dx = \mu W C_{ox} \int_0^L [(V_g - V_T) - V(x)] dV$$

$$I_{DS} \cdot L = \mu W C_{ox} [(V_g - V_T)V_{DS} - V_{DS}^2/2]$$


$$I_{DS} = \frac{\mu}{2} \frac{W}{L} C_{ox} [2(V_g - V_T) - V_{DS}] V_{DS}$$

$$\frac{\partial I_{DS}}{\partial V_{DS}} = \mu \frac{W}{L} C_{ox} [(V_g - V_T) - V_{DS}]$$

$\rightarrow 0$ when $V_{DS} = V_g - V_T$

$$\text{Substitute: } I_{DS,\text{SAT}} = \frac{\mu}{2} \frac{W}{L} C_{ox} (V_g - V_T)^2 \\ = \frac{\mu}{2} \frac{W}{L} C_{ox} V_{DS}^2$$

CMOS dynamic characteristics (part 1)

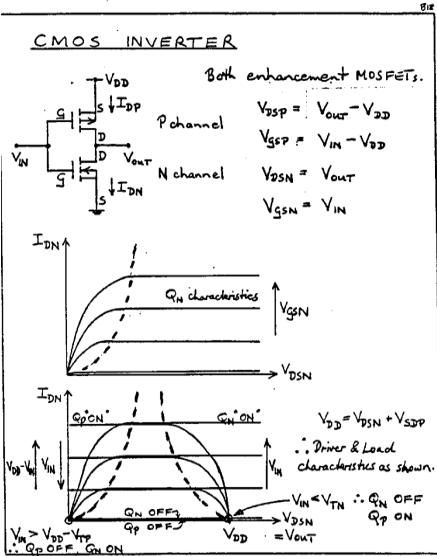

CMOS INVERTER (cont)

As V_{IN} increases from 0 results :-

(i) For $V_{IN} < V_{TN}$, Q_N OFF $\therefore I = 0$

$$\therefore V_{SSP} = V_{IN} - V_{DD} = -V_{DD}, Q_P$$
 not saturated.

$$V_{OUT} = V_{DD} \text{ see diagram.}$$

(ii) For $V_{IN} > V_{TN}$, Q_N begins to turn ON

(For $V_{IN} < V_{DSN} + V_{TN}$) Q_P not saturated - see diagram

$$\therefore I_{DN} = I_{DP}$$

$$\text{gives } k_N (V_{IN} - V_{TN})^2 = k_P [2(V_{SSP} - V_{TP})V_{DSP} - V_{DSP}^2] \\ \Rightarrow k_P [2(V_{SSP} + V_{TP})V_{SDP} - V_{SDP}^2]$$

$$k_N (V_{IN} - V_{TN})^2 = k_P [2(V_{DD} - V_{IN} + V_{TP})(V_{DD} - V_{OUT}) \\ - (V_{DD} - V_{OUT})^2]$$

$$\therefore V_{OUT} = V_{DD} + (V_{DD} - V_{IN} + V_{TP}) - [(V_{DD} - V_{IN} + V_{TP})^2 - \frac{k_N}{k_P}(V_{IN} - V_{TN})^2]$$

N.B. $V_{TN} > 0$ } for enhancement
 $V_{TP} < 0$ }

28

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

CMOS dynamic characteristics (part 2)

CMOS INVERTER (cont.)

(iii) Middle region, Q_N & Q_P both saturated.

Q_P saturates when $V_{SSP} = V_{SDP} - V_{TP}$
ie. when $V_{DD} - V_{THN} = V_{DD} - V_{OUT} - V_{TP}$

$V_{IN} = V_{OUT} + V_{TP}$
 Q_N goes out of saturation when $V_{SSN} = V_{DSN} + V_{TN}$
ie when $V_{IN} = V_{OUT} + V_{TN}$

In region (iii) with both transistors saturated $I_{PP} = I_{DN}$

$$k_p(V_{SSP} + V_{TP})^2 = k_n(V_{SSN} + V_{TN})^2$$

$$k_p(V_{DD} - V_{IN} + V_{TP})^2 = k_n(V_{IN} - V_{TN})^2$$

$$V_{IN} = \frac{V_{DD} + V_{TP} + (k_n/k_p)^{1/2} V_{TN}}{1 + (k_n/k_p)^{1/2}}$$

N.B. only V_{IN} defined, V_{OUT} changes abruptly.

N.B. Need this transition at $V_{IN} = V_{DD}/2$ for symmetry ie. need:

- $k_N = k_P \Leftrightarrow$ Since $\mu_N \neq \mu_P$, need different geometries

& $V_{TP} = -V_{TN}$ (P channel area > N channel area)


CMOS INVERTER (cont.)

(iv) Q_N goes out of saturation
 Q_P still saturated

Complement of region (iii). Following same sequence:

$$V_{OUT} = (V_{IN} - V_{TN}) - \left[(V_{IN} - V_{TN})^2 - \left(\frac{k_p}{k_n} \right) (V_{DD} - V_{IN} + V_{TP})^2 \right]^{1/2}$$

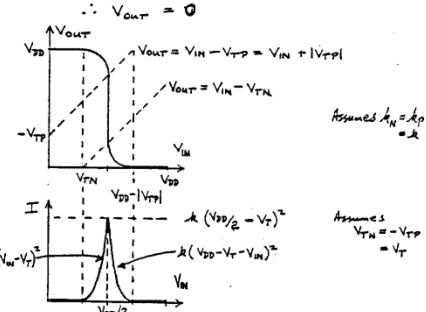(v) When $V_{IN} > V_{DD} - V_{TP}$, Q_P turned off




29

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Switching current (1)

CMOS TRANSIENTS

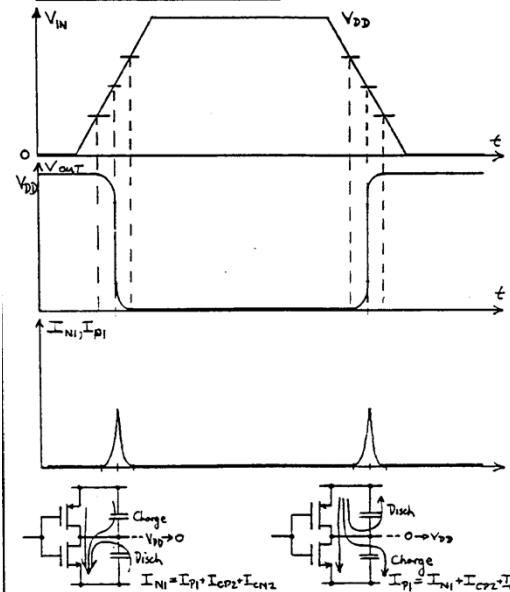

30

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Switching current (2)

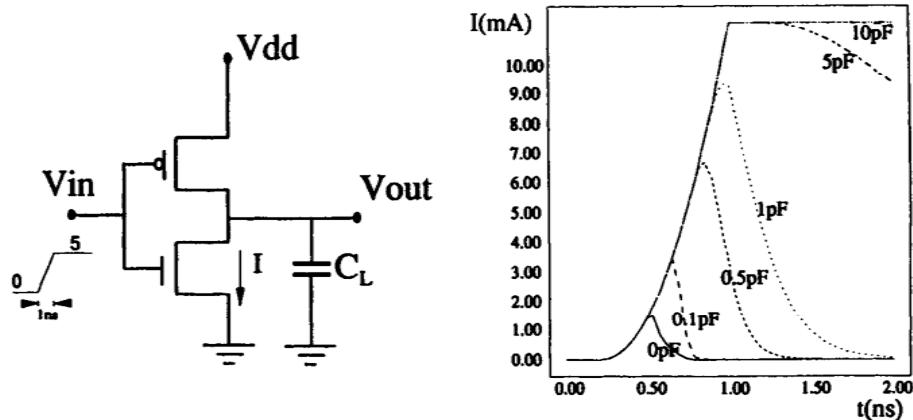


Figure 2.75 N-channel MOSFET current for various sizes of C_L .

31

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

6. Delta-I (ΔI) switching noise


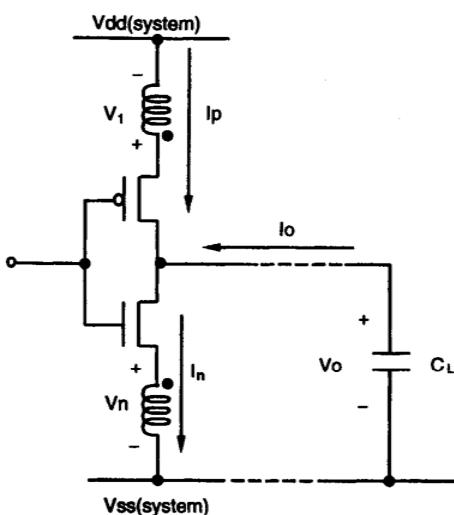


Figure 2.83 Driver circuit for the calculation of the mutual effect between L_{vss} and L_{vdd} on V_n .

32

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

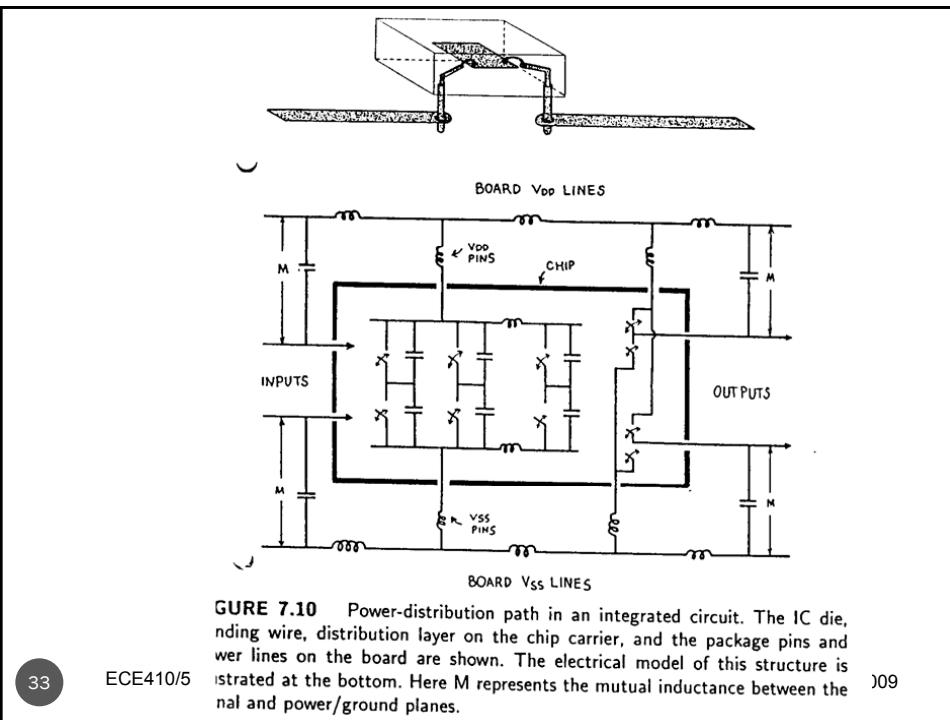

33

ECE410/5

109

Example to show typical values

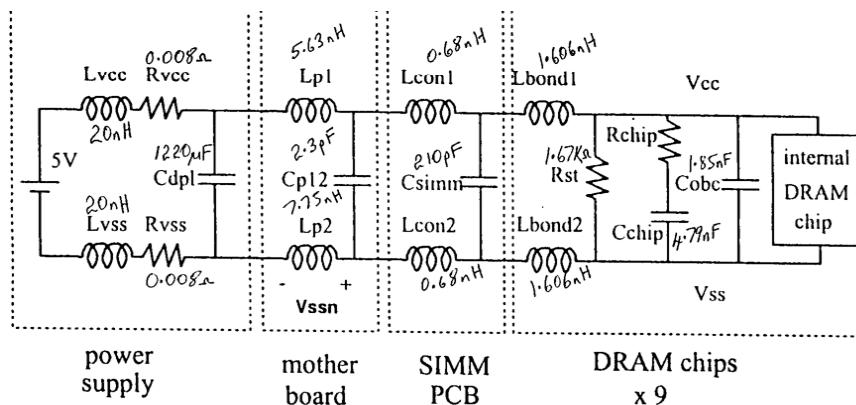


Fig. 15. Simplified equivalent circuit of the test setup shown in Fig. 14.

34

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

B/C/D. Transmission line effects

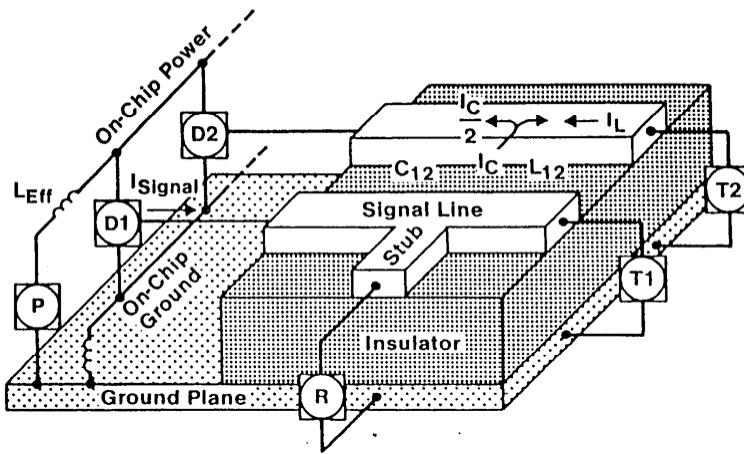


Figure 1-12. Causes of Reflected, Coupled, and Switching (ΔI) Noises.

35

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

Lecture topics B: Transmission lines

(Z_0 , velocity, lossless, lossy)


1. Transmission line theory
 - Characteristic impedance Z_0
 - Attenuation, dispersion, velocity
2. Z_0 calculations
3. Lossless line
 - Distortionless transmission
 - Shape factor
4. Z_0 for practical geometries
5. Effects of loss
 - Distortion

36

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

1. Transmission line theory

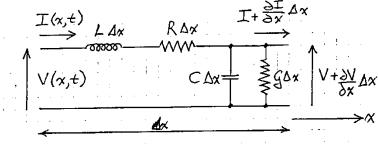

$$V - \left(V + \frac{\partial V}{\partial x} \Delta x \right) = R \Delta x I + L \Delta x \frac{dI}{dt}$$

$$\text{i.e. } -\frac{\partial V}{\partial x} = R I + L \frac{dI}{dt}$$

$$\text{Assume } V(x,t) = V(x) e^{j\omega t}$$

$$I(x,t) = I(x) e^{j\omega t}$$

$$\text{then } -\frac{\partial V(x)}{\partial x} = (R + j\omega L) I(x)$$

And similarly

$$I - \left(I + \frac{\partial I}{\partial x} \Delta x \right) = G \Delta x V + C \Delta x \frac{\partial V}{\partial t}$$

$$\text{gives } -\frac{dI(x)}{dx} = (G + j\omega C) V(x)$$

These give

$$\frac{d^2 V(x)}{dx^2} = (R + j\omega L)(G + j\omega C)V(x)$$

$$\& \frac{d^2 I(x)}{dx^2} = (G + j\omega C)(R + j\omega L)I(x)$$

2nd order differential equation has solution:

$$V(x) = A e^{-\lambda x} + B e^{+\lambda x}$$

$$\text{where } \lambda = [(R + j\omega L)(G + j\omega C)]^{1/2}$$

$$\text{i.e. } V(x,t) = V(x) e^{j\omega t} = A e^{j\omega t - \lambda x} + B e^{j\omega t + \lambda x}$$

$$\begin{array}{c} \xrightarrow{\text{Forward wave}} \quad \xleftarrow{\text{Reverse wave}} \\ (\text{damped } \lambda) \quad (\text{damped } \lambda) \end{array}$$

$$\begin{aligned} \text{Similarly } I(x) &= -(R + j\omega L)^{-1} \frac{dV(x)}{dx} \\ &= -\frac{[-A e^{-\lambda x} + B e^{+\lambda x}] \lambda}{(R + j\omega L)} \\ &= \frac{A e^{-\lambda x} - B e^{+\lambda x} (G + j\omega C)^{1/2}}{(R + j\omega L)^{1/2}} \\ &= \frac{A e^{-\lambda x} - B e^{+\lambda x}}{Z_0} \end{aligned}$$

where the Characteristic Impedance is

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$


Note: units Ω

37

ECE410/510 Electronics Packaging Fall 2005

Summary

TRANSMISSION LINE THEORY

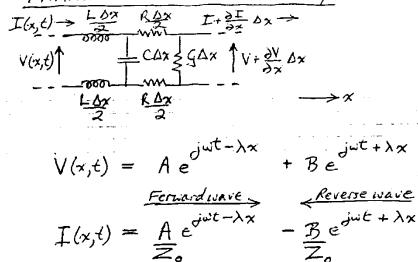

$$\text{where } Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\text{units } \Omega)$$

Characteristic Impedance

$$\begin{aligned} \& \lambda = \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \alpha + j\beta \\ & \text{Attenuation} \quad \text{Dispersion} \end{aligned}$$

$$\text{wave velocity } v = \omega/\beta$$

Attenuation, dispersion, velocity :-

$$\lambda = [(R + j\omega L)(G + j\omega C)]^{1/2}$$

$$\text{write } \lambda = \alpha + j\beta$$

Real part α is attenuation

Imag. part β is dispersion

$$\lambda^2 = \alpha^2 - \beta^2 + 2j\beta\alpha = (RG - \omega^2 LC) + j\omega(RC + GL)$$

$$\therefore \alpha^2 - \beta^2 = RG - \omega^2 LC$$

$$2\alpha\beta = \omega(RC + GL)$$

$$\text{Substitute for } \beta = \frac{1}{2} \frac{\omega}{\alpha} (RC + GL)$$

$$\lambda^2 - \frac{\omega^2}{4\alpha^2} (RC + GL)^2 = (RG - \omega^2 LC)$$

$$(\lambda^2)^2 - (\alpha^2)^2 (RG - \omega^2 LC) - \frac{\omega^2}{4} (RC + GL)^2 = 0$$

$$\lambda^2 = \frac{1}{2} \sqrt{RG - \omega^2 LC} \pm \sqrt{[(RG - \omega^2 LC)^2 + \omega^2 (RC + GL)^2]}^{1/2}$$

$$\& \beta^2 = \alpha^2 - (RG - \omega^2 LC)$$

$$= \frac{1}{2} \sqrt{[(RG - \omega^2 LC)^2 + \omega^2 (RC + GL)^2]}^{1/2}$$

By comparison with standard wave equations:

$$V(x,t) = A e^{j\omega t - \lambda x} = A e^{j\omega t - (\alpha + j\beta)x}$$

$$= A e^{-\alpha x} e^{j\omega t - \beta x}$$

$$\text{i.e. velocity } v = \omega/\beta$$

38

ECE410/510 Electronics Packaging Fall

2. Z_0 calculations

- Need L, C
- Also gives β , v
- Easiest geometry is coaxial line
 - (radial symmetry)

(b) Leakage conductance:
G/unit length

(b) FOR LEAKAGE CONDUCTANCE: G/unit length



Current density $J = \sigma E$

$$\text{& using } E, V_o \text{ from above } E = \frac{1}{l} \frac{V_o}{\ln(b/a)}$$

$$\text{Conductance } G = \frac{J}{V_o} = \frac{J(r) 2\pi r \cdot l}{V_o} / l \\ = \frac{\sigma}{V_o} 2\pi r \frac{l}{\ln(b/a)} \\ = 2\pi \sigma / \ln(b/a)$$

Note: for $G \ll \omega C$ need $\sigma \ll \omega C$
or $\omega \gg \sigma/E$

(a) Dielectric: C/unit length

$$\text{GAUSS'S LAW } \oint E \cdot dS = \epsilon_0 q_i \\ \text{Diagram shows a cylindrical Gaussian pillbox of radius } r \text{ and height } l. \text{ The volume charge density is } \rho. \\ \therefore E = \frac{q_i}{2\pi\epsilon_0 r} \\ \therefore V_o = - \int_b^a E \cdot dr = \frac{q_i}{2\pi\epsilon_0} \ln \frac{b}{a}$$

$$\text{Capacitance } C = \frac{q_i}{V_o} = \frac{2\pi\epsilon_0}{l} \ln \left(\frac{b}{a} \right)$$

(c) Inductance: L/unit length

$$(c) \text{ FOR INDUCTANCE : } L / \text{unit length} \\ \text{Diagram shows a cylindrical loop of radius } r \text{ and height } l. \\ B = \mu_0 H = \mu_0 \frac{I}{2\pi r} \quad \Phi = \int B dA = \mu_0 \frac{I}{2\pi} \ln \left(\frac{b}{a} \right) \\ \text{Magnetic flux } \Phi = \int_B^a B dA = \mu_0 \frac{I}{2\pi} \ln \left(\frac{b}{a} \right) \\ L = \frac{d\Phi}{dI} = \frac{\mu_0}{2\pi} \ln \left(\frac{b}{a} \right) / \text{unit length.}$$

3. Lossless lines

In practice: $G \ll \omega C$ in practical systems
ie. set $G \approx 0$

$$Z_0 \Rightarrow \sqrt{\frac{L}{C} + \frac{(R/G)^2}{G^2}}$$

$$\alpha^2 \Rightarrow \frac{1}{2} \omega^2 LC \left\{ \left[1 + \left(\frac{R}{\omega L} \right)^2 \right]^{1/2} - 1 \right\}$$

$$\beta^2 \Rightarrow \frac{1}{2} \omega^2 LC \left\{ \left[1 + \left(\frac{R}{\omega L} \right)^2 \right]^{1/2} + 1 \right\}$$

In practice $G \ll \omega C$ ie. set $G \approx 0$

Also usually assume $R \ll \omega L$ for simplicity
(not always a valid assumption)

i.e. set $R \approx 0$

Then:

$$Z_0 \Rightarrow \sqrt{L/C} \quad \text{Real, but non-dissipative}$$

$$\alpha \Rightarrow 0 \quad \text{i.e. lossless}$$

$$\beta \Rightarrow \omega \sqrt{LC}$$

$$\text{and } v \Rightarrow \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

e.g. Coaxial line



$$L = \frac{\mu_0}{2\pi} \ln \left(\frac{b}{a} \right) \text{ H/m}$$

$$C = 2\pi\epsilon_0 / \ln \left(\frac{b}{a} \right) \text{ F/m}$$

$$\therefore Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0} \frac{\ln(b/a)}{2\pi}}$$

$$= \sqrt{\frac{\mu_0}{\epsilon_0}} \times \text{Shape factor}$$

$$= \sqrt{\frac{\mu_0}{\epsilon_0}} \times \frac{\text{Shape factor}}{\sqrt{\epsilon_r}}$$

$$= 376.7 \Omega \left(\frac{\text{S.F.}}{\sqrt{\epsilon_r}} \right)^{1/2}$$

TABLE 5.2 CONDUCTANCE, CAPACITANCE, AND INDUCTANCE PER UNIT LENGTH FOR SOME STRUCTURES CONSISTING OF INFINITELY LONG CONDUCTORS HAVING THE CROSS SECTIONS SHOWN IN FIG. 5.12

Description	Capacitance per unit length, ϵ	Conductance per unit length, G	Inductance per unit length, L
Parallel-plane conductors, Fig. 5.12(a)	$\frac{\epsilon w}{d}$	$\frac{\sigma w}{d}$	$\mu \frac{d}{w}$
Coaxial cylindrical conductors, Fig. 5.12(b)	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\mu}{2\pi} \ln \frac{b}{a}$
Parallel cylindrical wires, Fig. 5.12(c)	$\frac{\pi\epsilon}{\cosh^{-1}(d/a)}$	$\frac{\pi\sigma}{\cosh^{-1}(d/a)}$	$\frac{\mu}{\pi} \cosh^{-1} \frac{d}{a}$
Eccentric inner conductor, Fig. 5.12(d)	$\frac{2\pi\epsilon}{\cosh^{-1} \left(\frac{a^2+b^2-d^2}{2ab} \right)}$	$\frac{2\pi\sigma}{\cosh^{-1} \left(\frac{a^2+b^2-d^2}{2ab} \right)}$	$\frac{\mu}{2\pi} \cosh^{-1} \frac{a^2+b^2-d^2}{2ab}$
Shielded parallel cylindrical wires, Fig. 5.12(e)	$\frac{\pi\epsilon}{\ln \frac{d(b^2-d^2/4)}{a(b^2+d^2/4)}}$	$\frac{\pi\sigma}{\ln \frac{d(b^2-d^2/4)}{a(b^2+d^2/4)}}$	$\frac{\mu}{\pi} \ln \frac{d(b^2-d^2/4)}{a(b^2+d^2/4)}$

41

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

4. Practical Z_0

For $Z_0 = [376.7/\sqrt{\epsilon_r}] \times s.f.$ \rightarrow

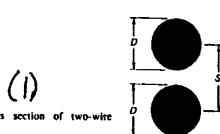


Figure E-2 Cross section of two-wire transmission line

The shape factor of the transmission line, $s.f.$, depends only on the shapes, sizes, and positions of the conductors. Two-wire transmission line (Figure E-2) has shape factor

$$s.f. = \frac{1}{\pi} \ln \left[\frac{S}{D} + \left(\frac{S^2}{D^2} - 1 \right)^{1/2} \right]$$

when both wires have diameter D . When the wires have diameters D_1 and D_2 , the shape factor becomes

$$s.f. = \frac{1}{2\pi} \ln \{x + (x^2 - 1)^{1/2}\}$$

where

$$x = \frac{4S^2 - D_1^2 - D_2^2}{2D_1 D_2}$$

(2) Twisting a two-wire transmission line to form a twisted-pair increases the average relative permittivity ϵ_r' . For hard insulation with relative permittivity ϵ_r ,

$$\epsilon_r' = 1 + (0.25 + 0.0004\Theta^2)(\epsilon_r - 1),$$

and for soft insulation (Teflon, polyvinyl chloride)

$$\epsilon_r' = 1 + (0.25 + 0.001\Theta^2)(\epsilon_r - 1),$$

$$\Theta = \arctan(\pi Sn) \text{ degrees},$$

and n is the number of twists per meter.

(3) A wire near a ground plane (Figure E-3) has shape factor

$$s.f. = \frac{1}{2\pi} \ln \left[\frac{2S}{D} + \left(\frac{4S^2}{D^2} + 1 \right)^{1/2} \right].$$

(4) A laminar bus (Figure E-4) has shape factor

$$s.f. \approx \frac{1}{\pi} \ln \left(\frac{4S}{W} + \frac{W}{2S} \right) \text{ for } W \leq \frac{S}{2}, T \ll W,$$

$$s.f. \approx \frac{2}{\frac{2W}{S} + 2.42 - \frac{0.22S}{W} + \left(1 - \frac{S}{2W} \right)^6} \text{ for } W > \frac{S}{2}, T \ll W.$$

If an insulator separates the conductors (Figure E-1(c)),

$$\epsilon_r' \approx \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{\left(4 + 20 \frac{S}{W} \right)^{1/2}}.$$

42

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

(5) Microstrip (Figure E-5) has shape factor

$$sf \approx \frac{1}{2\pi} \ln \left(\frac{8S}{W} + \frac{W}{4S} \right) \quad \text{for } W \ll S, T \ll W,$$

$$sf \approx \frac{1}{\frac{W}{S} + 2.42 - \frac{0.44S}{W} + \left(1 - \frac{S}{W} \right)^2} \quad \text{for } W > S, T.$$

If an insulator separates the conductors (Figure E-1(c)),

$$\epsilon_r \approx \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{\left(4 + 40 \frac{S}{W} \right)^{1/2}}.$$

(6) Coplanar lines (Figure E-6) have shape factor

$$sf \approx \frac{1}{\pi} \ln \left[2 \frac{\left(\frac{2W}{S} + 1 \right)^{1/2} + 1}{\left(\frac{2W}{S} + 1 \right)^{1/2} - 1} \right] \quad \text{for } W \leq 2.414S, T \ll$$

$$sf \approx \frac{\pi}{4 \ln \left[2 \left(\frac{2W}{S} + 1 \right)^{1/2} \right]} \quad \text{for } W > 2.414S, T \ll W.$$

If the lines are supported by an insulator on one side,

$$1 < \epsilon_r < \frac{\epsilon_r + 1}{2}.$$

(7) Triplate stripline (Figure E-7) has shape factor

$$sf \approx \frac{1}{2\pi} \ln \left[\frac{\exp \left(\frac{\pi W}{4S} \right) + 1}{2 - \frac{\exp \left(\frac{\pi W}{4S} \right) - 1}{\exp \left(\frac{\pi W}{4S} \right) + 1}} \right] \quad \text{for } W \leq 1.117S, T \ll S,$$

$$sf \approx \frac{1}{1.765 + \frac{2W}{S}} \quad \text{for } W > 1.117S, T \ll S.$$

(8) Coaxial cable (Figure E-8) has shape factor

$$sf = \frac{1}{2\pi} \ln \left(\frac{B}{D} \right).$$

(9) Shielded twisted-pair (Figure E-9) has shape factor

$$sf = \frac{1}{\pi} \ln \left(\frac{2S B^2 - S^2}{D B^2 + S^2} \right).$$

4/16/2009

Figure E-3 Cross section of wire near a groundplane

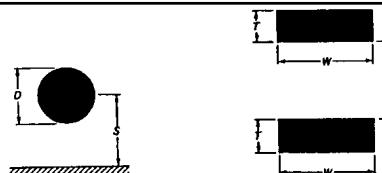


Figure E-4 Cross section of a laminar bus

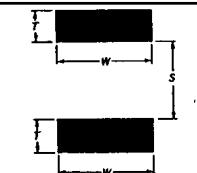


Figure E-7 Cross section of triplate stripline

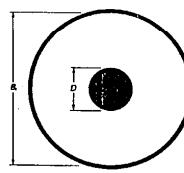


Figure E-8 Cross section of coaxial cable

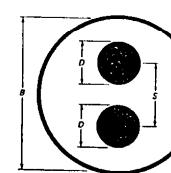


Figure E-9 Cross section of shielded twisted-pair

Figure E-5 Cross section of microstrip


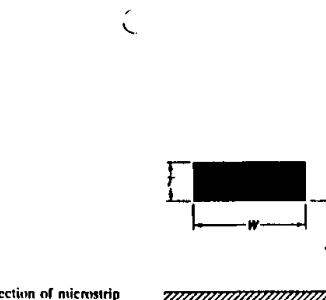


Figure E-6 Cross section of coplanar lines

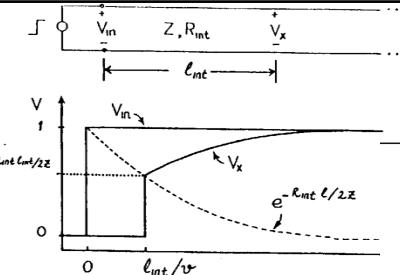

4/16/2009



5. Lossy lines

LOSSY TRANSMISSION LINES 247

FIGURE 6.10 Waveforms in a lossy transmission line

The response of this line to a unit step input at a distance x from the beginning of the line is [6.1]:

$$V(x, t) = \left\{ e^{-Rx/2Z_0} + \frac{Rx}{2Z_0} \int_{t=x\sqrt{LC}}^t \left[\frac{e^{-R(t-t')/2LC}}{\sqrt{t^2 - x\sqrt{LC}}} \frac{I_1 R}{2LC} \sqrt{t^2 - x\sqrt{LC}} \right] dt \right\} x u(t - x\sqrt{LC}).$$

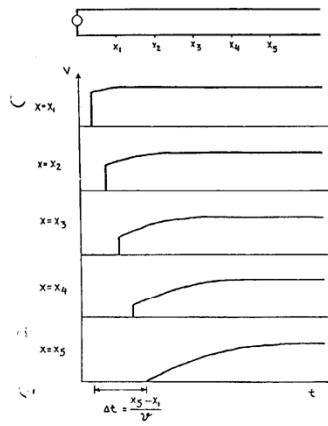


FIGURE 6.11 Waveform propagating along a lossy transmission line. The input to the transmission line is a unit voltage step, and the response is captured at successive points along the line. The size of the step is attenuated as the waveform travels down the line, and at a point far enough from the source, the response is like that of a distributed RC line.

45

ECE410/510 Electronics Packaging Fall 2005

Lecture topics C: Transmission lines

Transmission line reflections


1. Reflection coefficients
2. Basic cases:
 - Matched and open circuit
3. Generalized mismatches
 - Source and load
4. Bounce chart/lattice diagram
5. Reflections from discontinuities

46

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

1. Reflection Coefficient

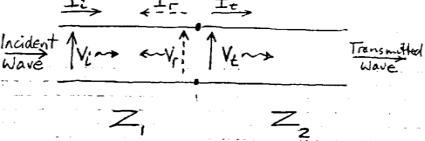

At discontinuity $Z_1 \rightarrow Z_2$

and the relationships of the incident wave $V_i = I_i Z_1$
cannot be maintained in the transmitted wave $V_t = I_t Z_2$
without changes in V , I . Solution requires
reflected wave $V_r = I_r Z_1$

Boundary conditions $V_i + V_r = V_t$

$$I_i - I_r = I_t$$

Gives $V_r = \frac{Z_2 - Z_1}{Z_2 + Z_1} V_i$ $T_v = \Gamma_v V_i$


& $I_r = \frac{\Gamma_v}{1 + \Gamma_v} I_i = -\frac{\Gamma_v}{1 + \Gamma_v} I_i$ (Voltage) Reflection Coefficient

(Current) Reflection Coefficient

Voltage transmission coefficient $V_t/V_i = 1 + \Gamma_v$

Voltage reflection at Load $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow 0$ for $Z_L = Z_0 = R_0$

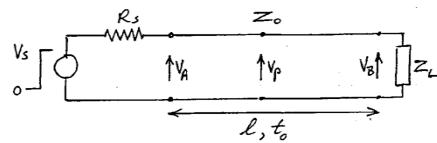" SOURCE $\Gamma_{VS} = \frac{R_S - Z_0}{R_S + Z_0} \rightarrow 0$ for $R_S = Z_0$



At source end: $V_A = \frac{Z_0}{R_S + Z_0} V_S$

Along line: $V_p = \frac{Z_0}{Z_0 + Z_0} 2V_i = V_i$

V_i is propagating Need equivalent 2V source signal

At load end: $V_B = \frac{Z_L}{Z_0 + Z_L} 2V_i$

V : if $Z_L = Z_0$

2. 3 significant cases:

$$\Gamma_{VL} = (R_L - Z_0) / (R_L + Z_0)$$

- Load $R_L = Z_0$ (above) $\Gamma_{VL} = 0$
- Open circuit load:
 - $R_S = Z_0$ ($\Gamma_{VL} = 1$)
 - $R_S = 0$ ($\Gamma_{VS} = -1$)
- Short circuit load $R_L = 0$, $\Gamma_{VL} = -1$

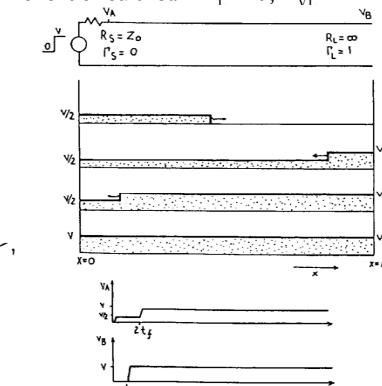


FIGURE 6.18 Termination at the source end: $R_S = Z_0$, $R_L = \infty$

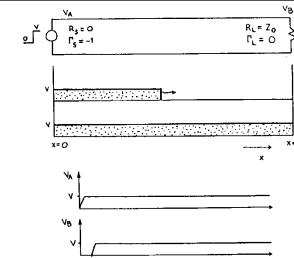


FIGURE 6.17 Termination at the receiving end: $R_S = 0$, $R_L = Z_0$

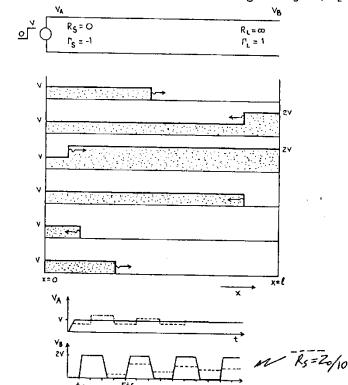


FIGURE 6.16 No termination: $R_S = 0$, $R_L = \infty$

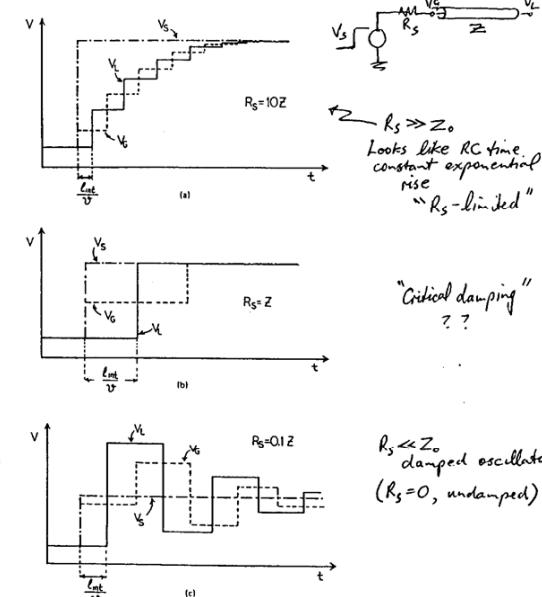


FIGURE 6.8 Waveforms for various R_s and Z_0 combinations in the circuit in Fig. 6.7. As can be seen by the t_{int}/v markers, the time axes of the plots are not drawn at the same scale for clarity. The top plot $R_s = 10Z_0$ has the longest delay.

49

ECE410/51

4/16/2009

3. Mismatched load &/or source

- 1 volt pulse, $Z_0 = 78\Omega$
- Consider $R_L = 78\Omega$ cases first, then vary R_L for
 - (a) $R_s = Z_0$
 - (b) $R_s \ll Z_0$
 - (c) $R_s \gg Z_0$

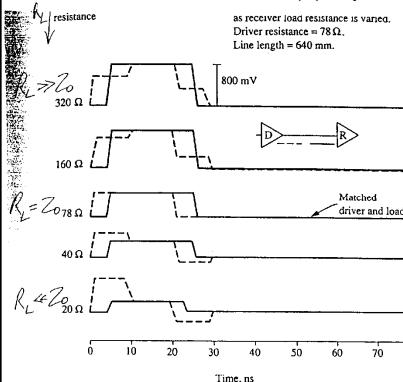


FIGURE 3-10
 Same as Figure 3-9, but driver resistance is 78Ω . $R_s = Z_0$

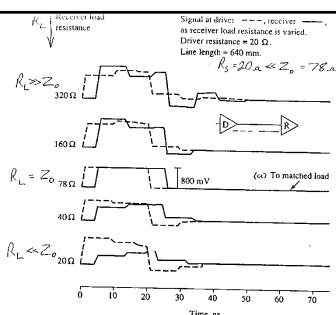


FIGURE 3-9
 Multiple reflections on a transmission line. Signal at driver and receiver, driver resistances 20Ω , R_s is varied from low to high values. Characteristic impedance Z_0 of line is 78Ω . waveform is a 20-ns wide trapezoidal pulse with 1 ns rise and fall times and 1 V p-p into an open circuit.

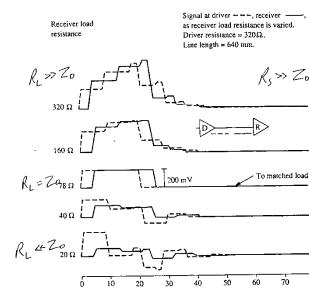


FIGURE 3-11
 Same as Figure 3-9, but driver resistance is 78Ω .

4. Bounce chart (lattice diagram)

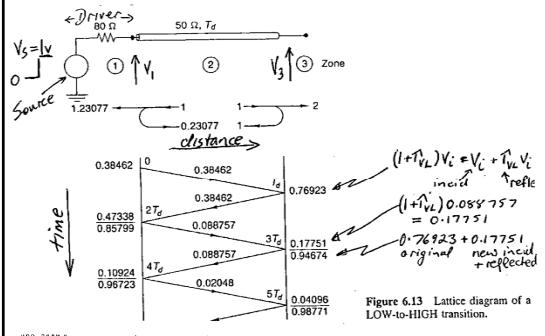


Figure 6.13 Lattice diagram of a LOW-to-HIGH transition.

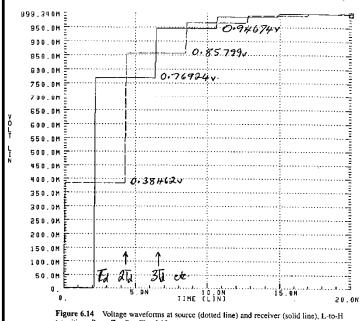


Figure 6.14 Voltage waveforms at source (dotted line) and receiver (solid line). L-to-H transition, $R_s > Z_0$. See Fig. 6.13.

- Calculate reflection coefficients
- Distance / time diagram
- Transfer data to waveform plots
- Example: Open circuit line

"BOUNCE" CHART / LATTICE DIAGRAM

$$(1) R_s = 80 \Omega \quad Z_0 = 50 \Omega \quad R_L = \infty$$

$$\therefore T_{V_s} = \frac{80 - 50}{80 + 50} = \frac{3}{13} \quad \Gamma_{VL} = \frac{80 - 50}{80 + 50} = 1 = 0.23077$$

$$At t=0: V_i = \frac{50}{50+80} V_s = \frac{5}{13} V_s = 0.38462V$$

$$t=T_d: Load \quad V_i = 0.38462V \quad V_f = \Gamma_{VL} V_i = 0.38462V$$

$$t=2T_d: Drive \quad Reflected wave \quad V_f = T_{V_s} \times 0.38462V = 0.088757V$$

$$V_3 = 0.38462V + 0.38462V + 0.088757V \\ \text{original pulse} \quad \text{reflected wave} \quad \text{reflection back to load} \\ = 0.85799V$$

$$t=3T_d: Load \quad Reflected wave = T_{VL} \times 0.85799V = 0.058757V$$

$$V_3 = 0.76924 + 0.088757 + 0.058757 \\ \text{Previous value} \quad (1+\Gamma_{VL})V_i = 0.17751 \\ \text{incident reflection} + \text{next refl. back to load} \\ = 0.94674V$$

$$t=4T_d: Driver \quad Reflected wave = T_{VL} \times 0.088757V = 0.02048V$$

$$V_i = 0.85799V + (0.088757 + 0.02048)V = 0.96723V$$

5. Discontinuities


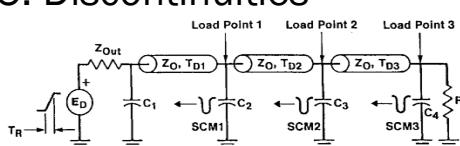
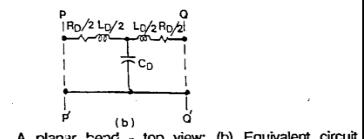
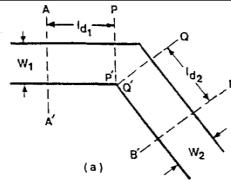
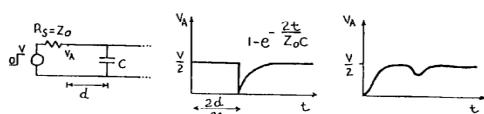


Figure 3-9. Discrete or Distributed Net Configurations. Note reflections from discontinuities.

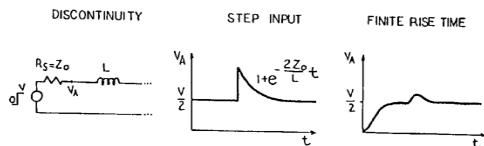

A planar bend - top view; (b) Equivalent circuit

FIGURE 6.6 Inductive and capacitive discontinuities. The transmission line is driven by a signal generator with $R_s = Z_0$, and the reflected waveforms are observed at the source end. The line is either infinitely long or is terminated with $R_L = Z_0$ at the far end. Two types of reflected waveforms are plotted for each discontinuity: one assuming a step input (left) and another assuming a finite-rise-time input (right).

4/16/2009


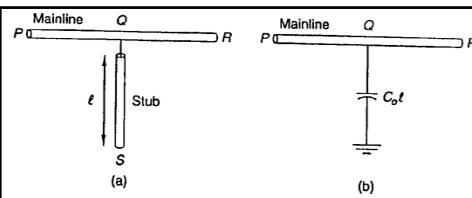


Figure 6.3 A short stub (a) reflects as a capacitor (b).

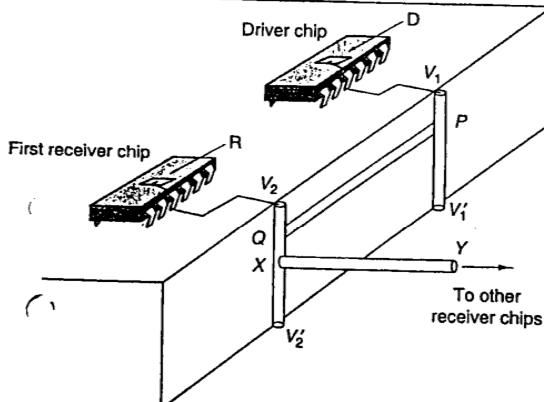

*Best to drive multiple loads from branch at matched source
avoids multiple reflection times from stubs.*

Figure 6.4 DV_1, RV_2 are metallizations on the board surface.
 PQ, XY are board internal traces.
 $V_1V'_1, V_2V'_2$ are through vias. The path DV_1PQXY is the mainline, while RV_2Q, PV'_1 and XV'_2 are stubs.

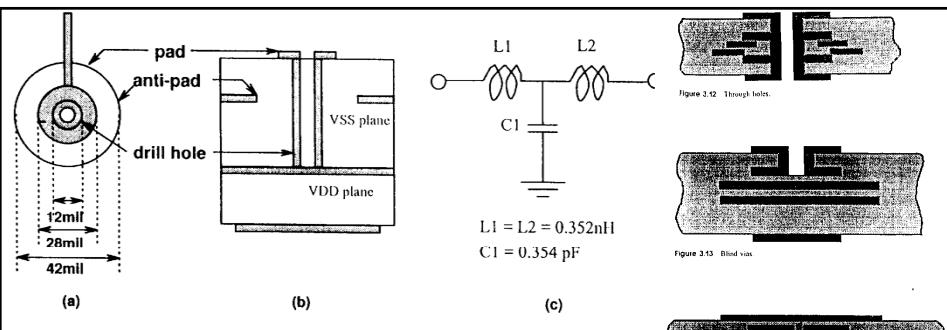


Fig. 10. A via hole (a) top view (b) cross-sectional view (c) equivalent circuit model

Figure 3.12 Through holes.



Figure 3.13 Blind via.

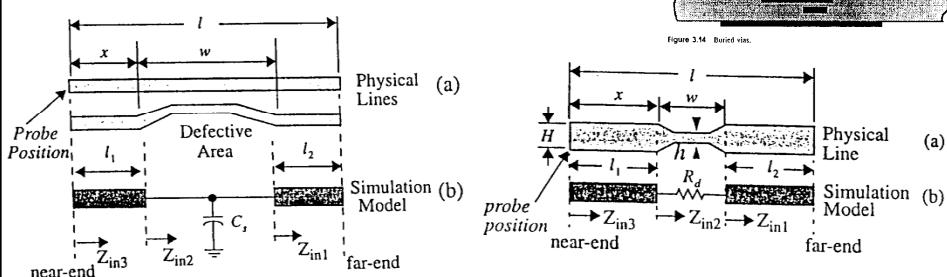


Figure 7. Simulation Model for an Interconnect with Near-Short Defect.

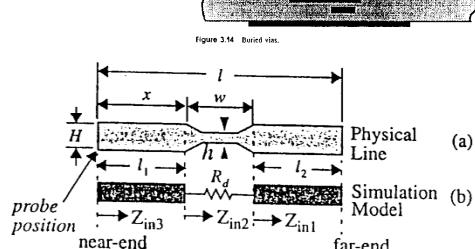


Figure 6. Simulation Model for an Interconnect with Near-Open Defect.

Summary

Waveform	Transmission line effect	Description/environment	Sectior
(1)		Propagation delay T_d Risetime degradation ($T_{r,r} > T_{r,s}$)	Line is distributed if $2T_d \geq T_r$ 9.1.4
(2)		Ohmic drop (frequency-independent)	Steady-state attenuation 5.2
(3)		Skin effect (frequency dependent)	Slow dribble-up at transition 10.4
(4)		Reflection from lumped loads: (a) capacitor (b) inductor	Glitch accompanies every transition 6.2.2
(5)		Undershoot on (a) short line (b) long line	Parallel-terminated line: (at receiver): $R_s < Z_0$ 6.4
(6)		Overshoot on (a) short line (b) long line	Series-terminated line: (at source): $R_s > Z_0$ Parallel-terminated line: (at receiver): $R_s > Z_0$ Series-terminated line: (at source): $R_s > Z_0$ 6.4
(7)		Spurious noises: • cross talk • switching • oscillations • others	Non-deterministic association with every transition Chap. 7, 8

3/2009

55

ECE410/510 Elect

Lecture topics D: Transmission lines Crosstalk

1. Inductive and capacitive coupling
2. Forward and backward noise
3. Far end and near end noise
4. Incremental model and formulae
5. Crosstalk examples
6. Capacitive crosstalk systems
7. No ground plane


56

ECE410/510 Electronics Packaging Fall 2005


4/16/2009

1. Inductive and capacitive coupling

Incremental line model

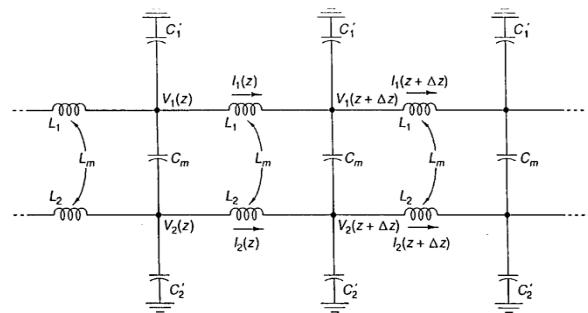


Crosstalk polarities

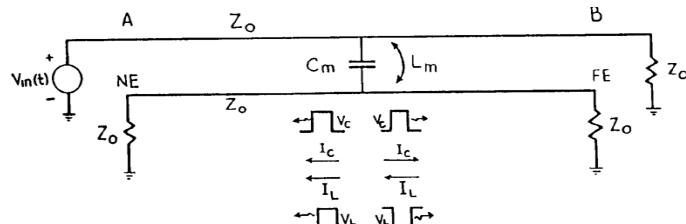


57

4/16/2009

2. Forward & backward noise

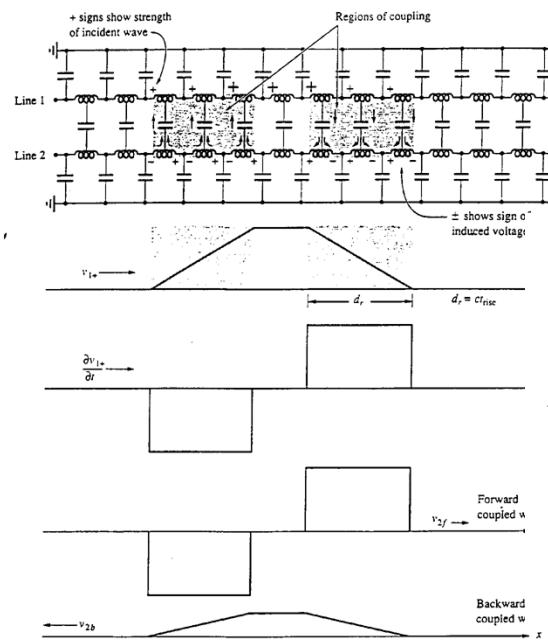


3. Near end & far end

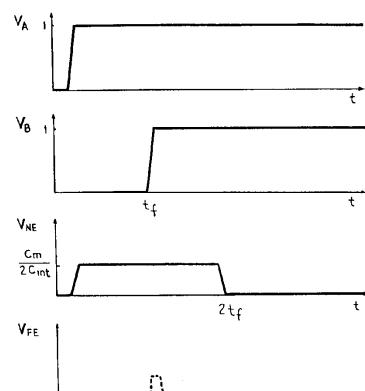


4. Theory: line segment

(a) Capacitive

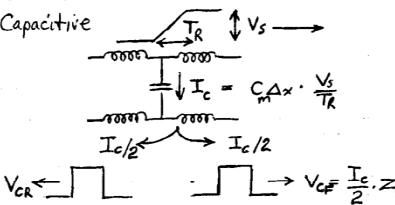


Consider line elements of length Δx

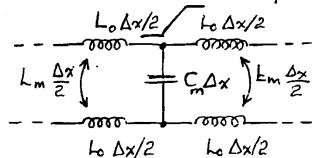

$$I = \frac{V_s}{Z_0} \downarrow \rightarrow T_R = \frac{C_m Z_0}{2} \cdot \frac{V_s}{T_R} \cdot \Delta x$$


(b) Inductive

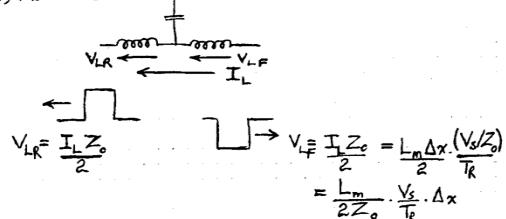


59

Far end overview

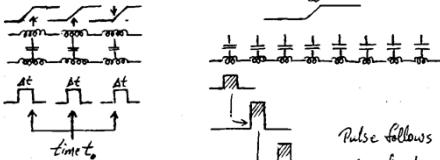For forward coupled wave. $t_0 \rightarrow$



At far end (FE):

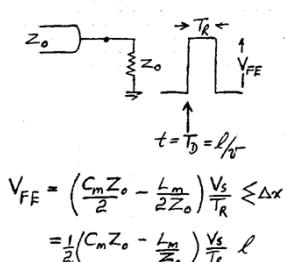


This is so if medium is "homogeneous"
Apprx true for most MCM "strip-line" structures, etc. $\mu_r = \mu_0$ homogeneous
 E_r constant

60

Backward wave model


For reverse coupled wave

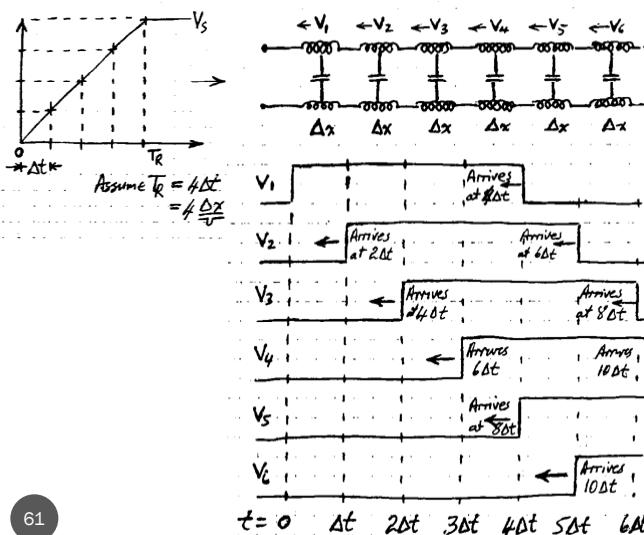Consider the near end (NE) as pulse starts:-



Each pulse

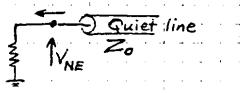
$$\Delta V = \left(\frac{C_m Z_0 + L_m}{2Z_0} \right) \frac{V_s}{T_R} \Delta x$$



61


4/16/2009

Near end pulse shape

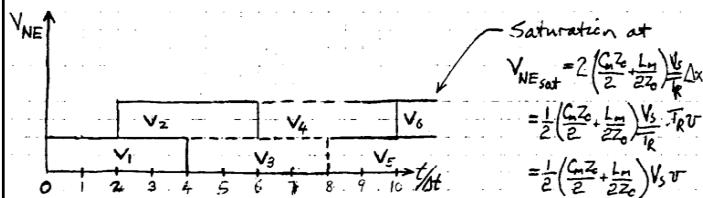

Note: Independent of T_R !!

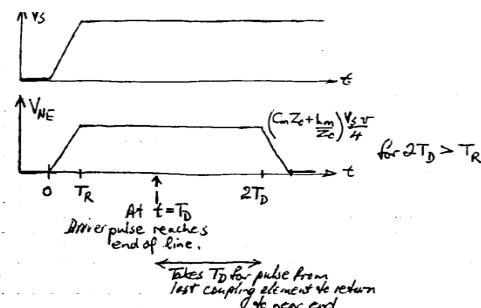
Also independent of ϵ_r : $C_m Z_0 \sqrt{\epsilon_r} \propto \epsilon_r \epsilon_r^{-1/2} \epsilon_r^{-1/2}$
 $V/Z_0 \propto \epsilon_r^{-1/2} (\epsilon_r^{-1/2})^{-1}$



ECE410/510 Electronics Packaging Fall 2

62

Near End Saturation

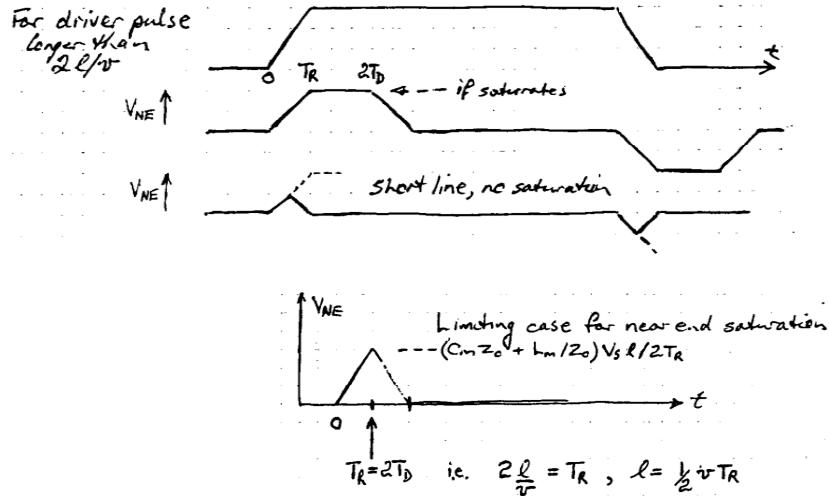


63

ECE410/510 Electroni

I need to reduce $V_{NE,max}$, need to increase T_R & / or decrease l
 (i.e. decrease l/T_R) so cannot saturate.

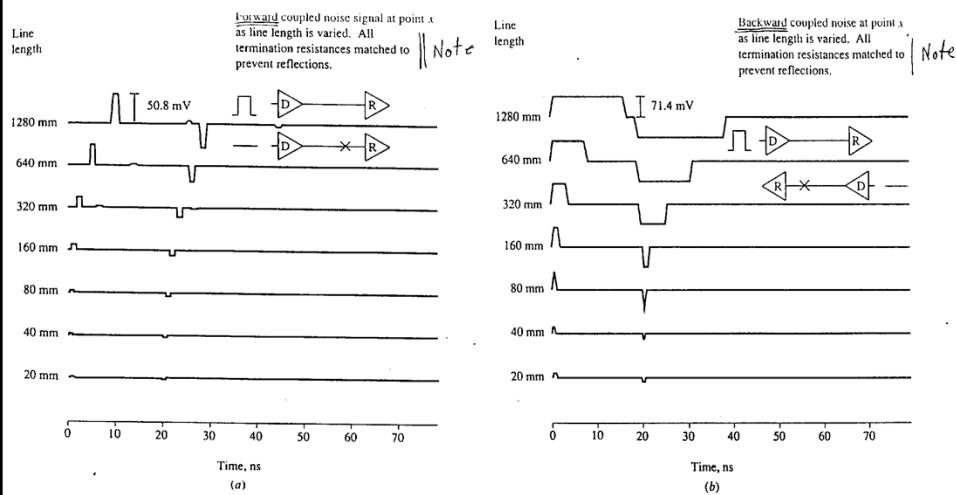5. Pulse crosstalk noise examples

Drive pulse: 0.5 volt, $t_{width}=20\text{ns}$, $t_{rise}=t_{fall}=1\text{ns}$




Forward noise: matched

Backward: matched

Not matched

Forward(Far end)

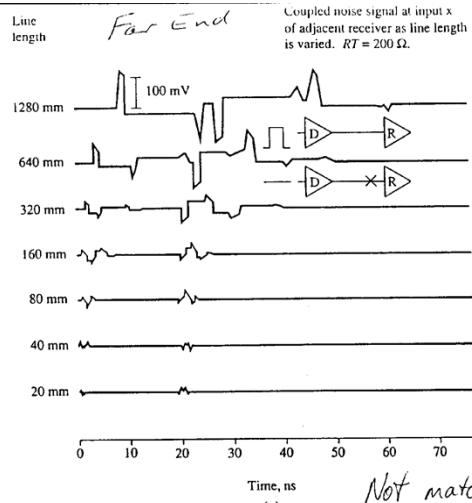

Backward (Near end)

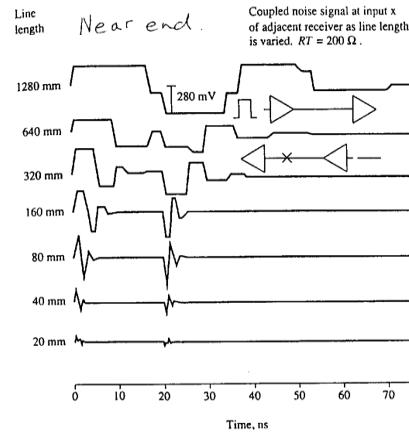


FIGURE 3-15
(continued)

Not matched

6. Ground coupled crosstalk

$$\text{Crosstalk} \approx \frac{K}{1 + (D/H)^2}$$

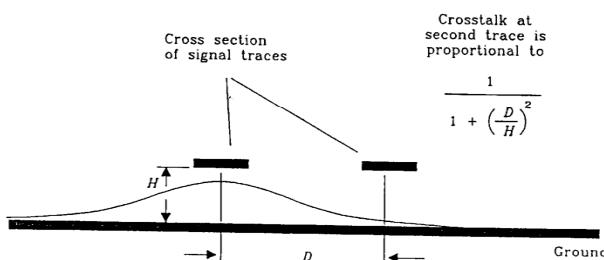


Figure 5.4 Cross section of two traces

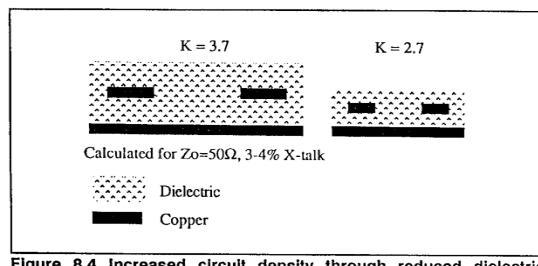


Figure 8.4 Increased circuit density through reduced dielectric constant.

7. Mutual capacitances


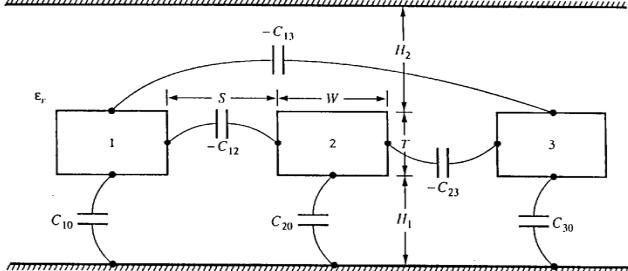


FIGURE 4-3
Cross section of three coupled lines in a homogeneous medium.

Even/odd modes

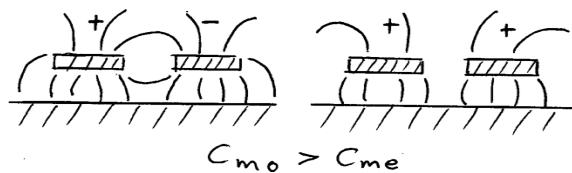


67

4/16/2009

Lecture topics E: Electromagnetic Modeling

Microstrip

Transmission line

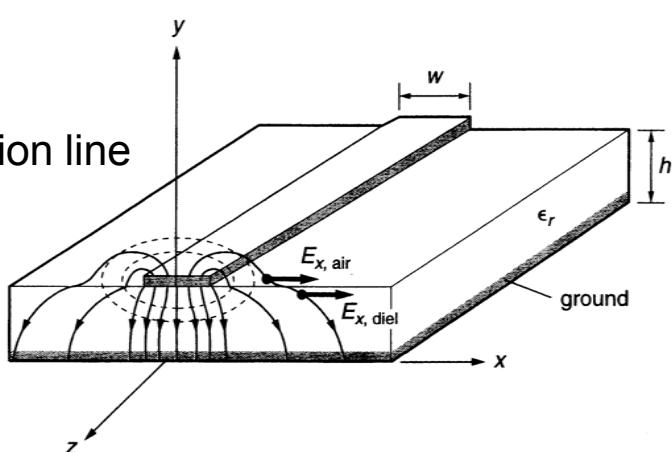


68

Figure 23.8 Sketch of a microstrip line. The electric field lines are sketched in solid line, and the magnetic field lines in dashed line.

3. Electromagnetic Modeling (Fang)

Finite element mesh

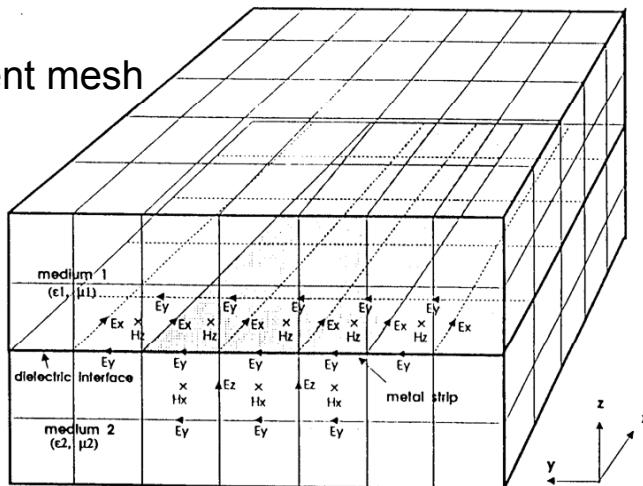


69

ECE410/510 Electronics Packaging Fall 2005

4/16/2009


a. Current pulse excitation of line

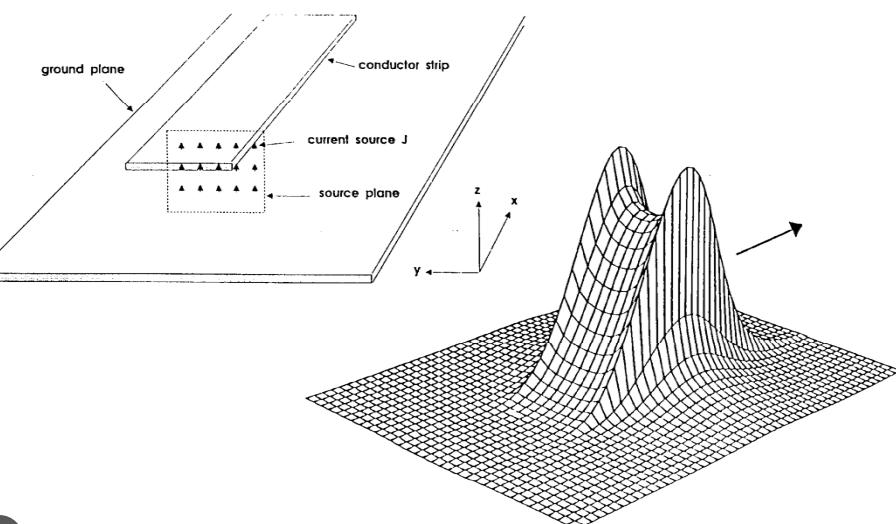

70


Electric field distribution on line

b. Chamfered right angle bend

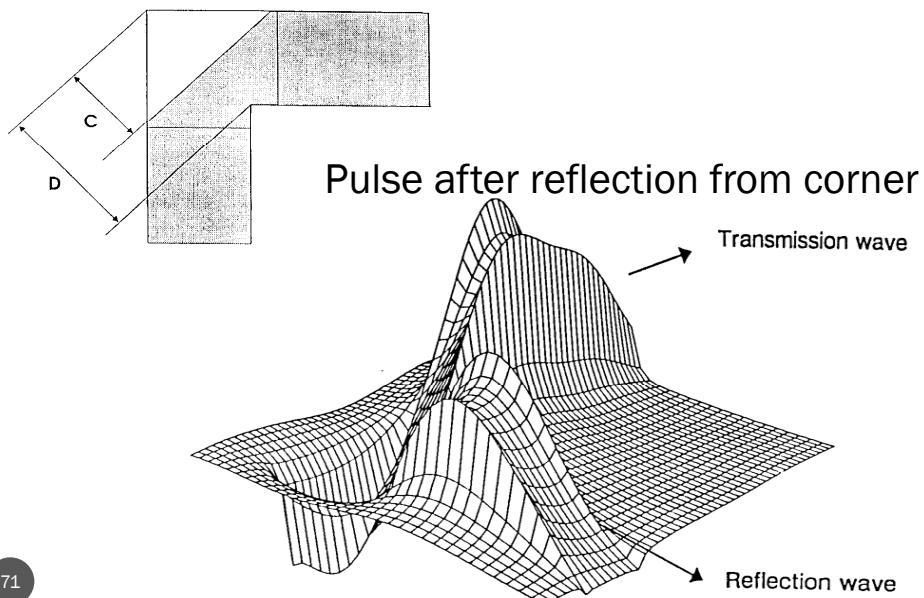

71

c. Orthogonal line crosstalk

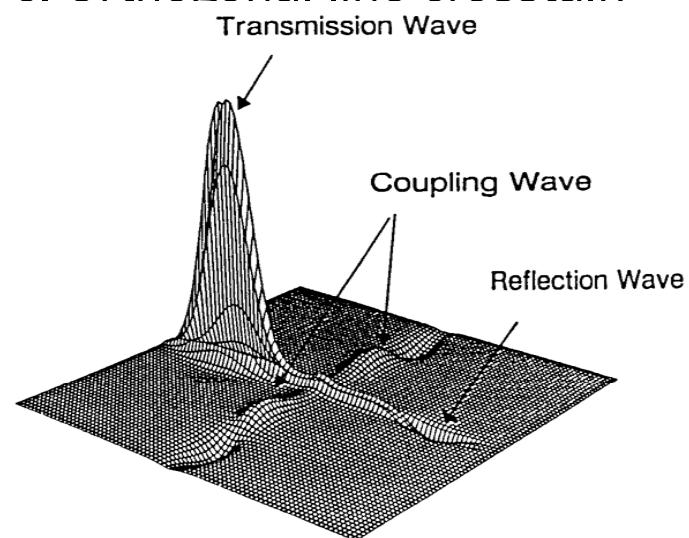

72

Lecture topics F: Electromagnetic Compatibility


1. Antennas
2. Emissions
3. Susceptibility

73

ECE410/510 Electronics Packaging Fall 2005

4/16/2009


1. EMI/EMC Models: Loop/Dipole Antennas

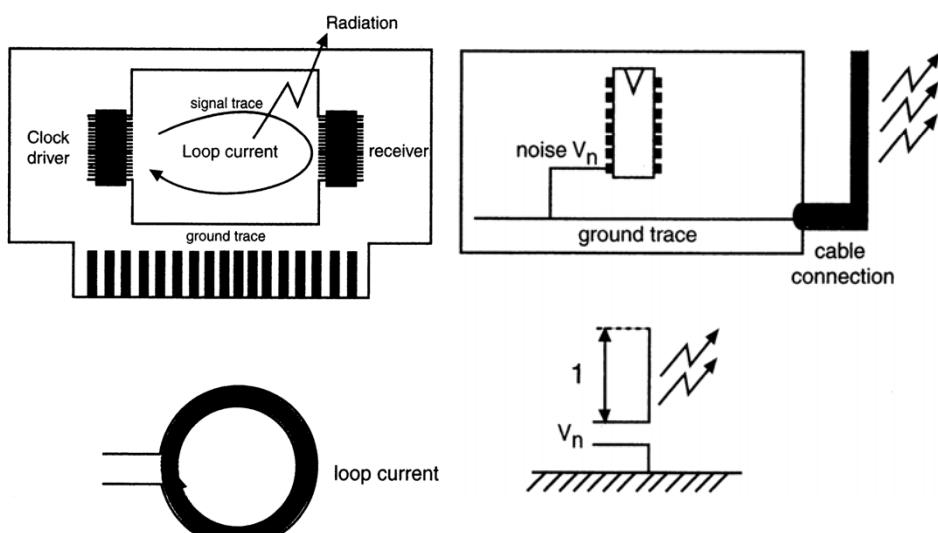

74

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

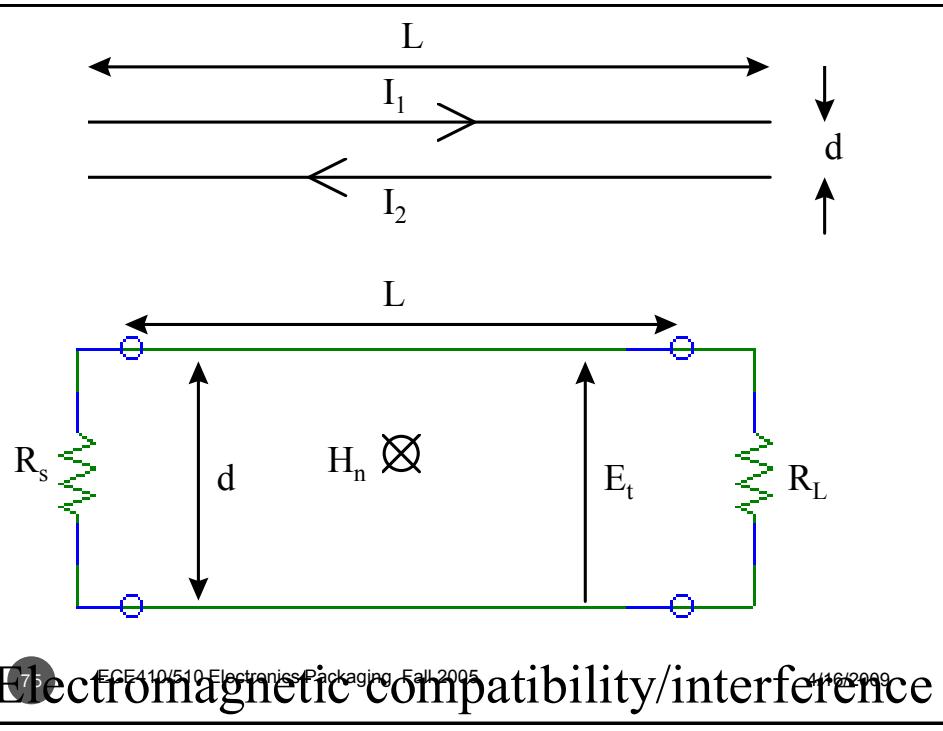


1. Electromagnetic compatibility/interference

2. EMI/EMC Models: Emissions

- At “far field” distance $r (\geq \lambda = c/f)$ from the line of length L and area $A = L.d$, the radiated electric field strength is
 - $E = E_D + E_{CM}$
- where E_D due to the differential current I_D is
 - $E_D = 131.6 \times 10^{-16} f^2 A I_D / r \text{ V/m}$
- and E_{CM} due to the common mode current I_{CM} is (for $L \leq \lambda$)
 - $E_{CM} = 4\pi \times 10^{-7} f^2 L I_{CM} / r \text{ V/m}$
- where $I_D = (I_1 + I_2)/2$ and $I_{CM} = (I_1 - I_2)/2$. Common mode currents are ideally zero, but small values can lead to CM dominance over differential. For the differential current, the maximum value can be taken to be the supply current, but the user must specify a non-ideal common mode estimate. For digital systems, use $f = 2\pi/t_r$. For other geometries, other expressions for A are valid.
- There are many different standards for EM radiation limits, but for guidance the EU limit is $E \leq 100 \mu\text{V/m}$ at $r = 10\text{m}$ (class A) or 3m (class B).

EMI/EMC Models: Susceptibility

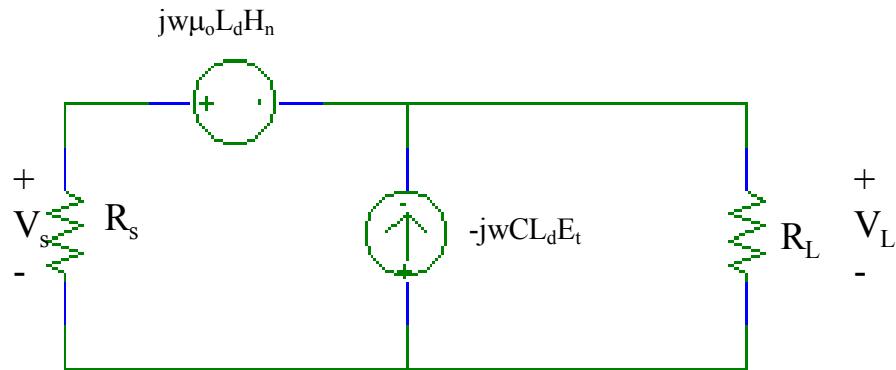

models

77

ECE410/510 Electronics Packaging Fall 2005

4/16/2009

3. Susceptibility

- For the line shown, with capacitance C per unit length,
e.g.
- $C = \pi \epsilon_r \epsilon_0 / \ln(d/r_w)$
- for parallel wires, the induced voltages are
 - $V_s = -j\omega [R_L R_S / (R_L + R_S)] [Ld] [C - (\mu_0 / \eta_0) / R_L]$
 - $V_L = -j\omega [R_L R_S / (R_L + R_S)] [Ld] [C + (\mu_0 / \eta_0) / R_S]$
- where $E = E_t = \eta_0 H_n$, and $\eta_0 = 120\pi = 377\Omega$.
- As an example of an EU standard, the device must function in a field of $E = 3V/m$.

78

ECE410/510 Electronics Packaging Fall 2005

4/16/2009