

ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 10
26th October, 2006

CHAPTER 4

MOS Field-Effect Transistors (MOSFETs)

~~4.5~~ — ~~Biasing~~

4.6 Small-Signal


4.7 *Single Stage Amp's*

DC BIAS POINT

Assume saturation

ie. $V_D > V_{gs} - V_t$
(then confirm)

Assume $\lambda = 0$ for simplicity

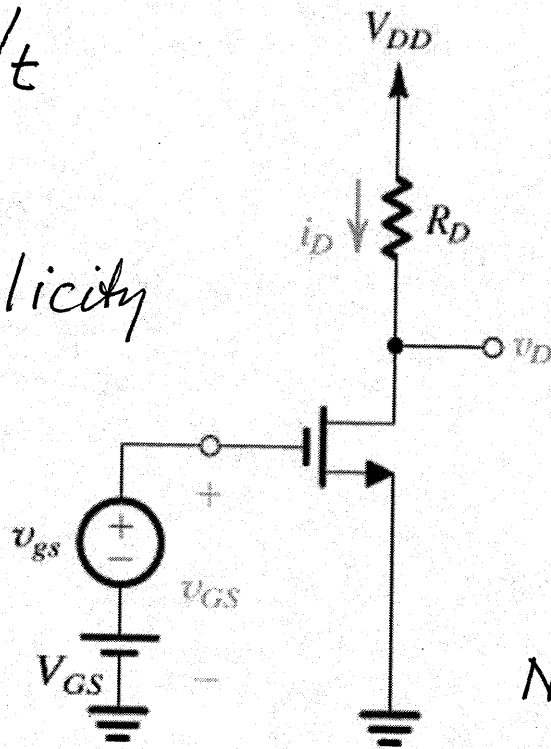

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{gs} - V_t)^2$$
$$= \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2$$

$$V_D = V_{DD} - I_D R_D$$

Note: As amplifier,

need $V_D > V_{gs} - V_t$ for all

$$v_{gs} = V_{gs} + v_{gs}$$

$$\text{ie. } v_D)_{\min} > v_{gs})_{\max} - V_t$$

Figure 4.34 Conceptual circuit utilized to study the operation of the MOSFET as a small-signal amplifier.

SMALL SIGNAL:

$$v_{gs} = V_{gs} + v_{gs} \rightarrow i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{gs} + v_{gs} - V_t)^2$$

$$= \frac{1}{2} k_n' \frac{W}{L} \left([V_{gs} - V_t]^2 + 2[V_{gs} - V_t]v_{gs} + v_{gs}^2 \right)$$

DC bias term

Small signal; linear in v_{gs}

Non linear term

Make $v_{gs} \ll 2(V_{gs} - V_t) \rightarrow i_D = I_D + i_d$

where $i_d = k_n' \frac{W}{L} (V_{gs} - V_t) v_{gs}$

$$g_m = \frac{i_d}{v_{gs}} = k_n' \frac{W}{L} (V_{gs} - V_t)$$

$$(V_{gs} - V_t)^2 = \frac{2I_D}{k_n' \frac{W}{L}}$$

$$\sqrt{2k_n' \frac{W}{L} I_D}$$

$$k_n' \frac{W}{L} = \frac{2I_D}{(V_{gs} - V_t)^2}$$

$$\frac{2I_D}{V_{gs} - V_t} = \frac{2I_D}{V_{ov}}$$

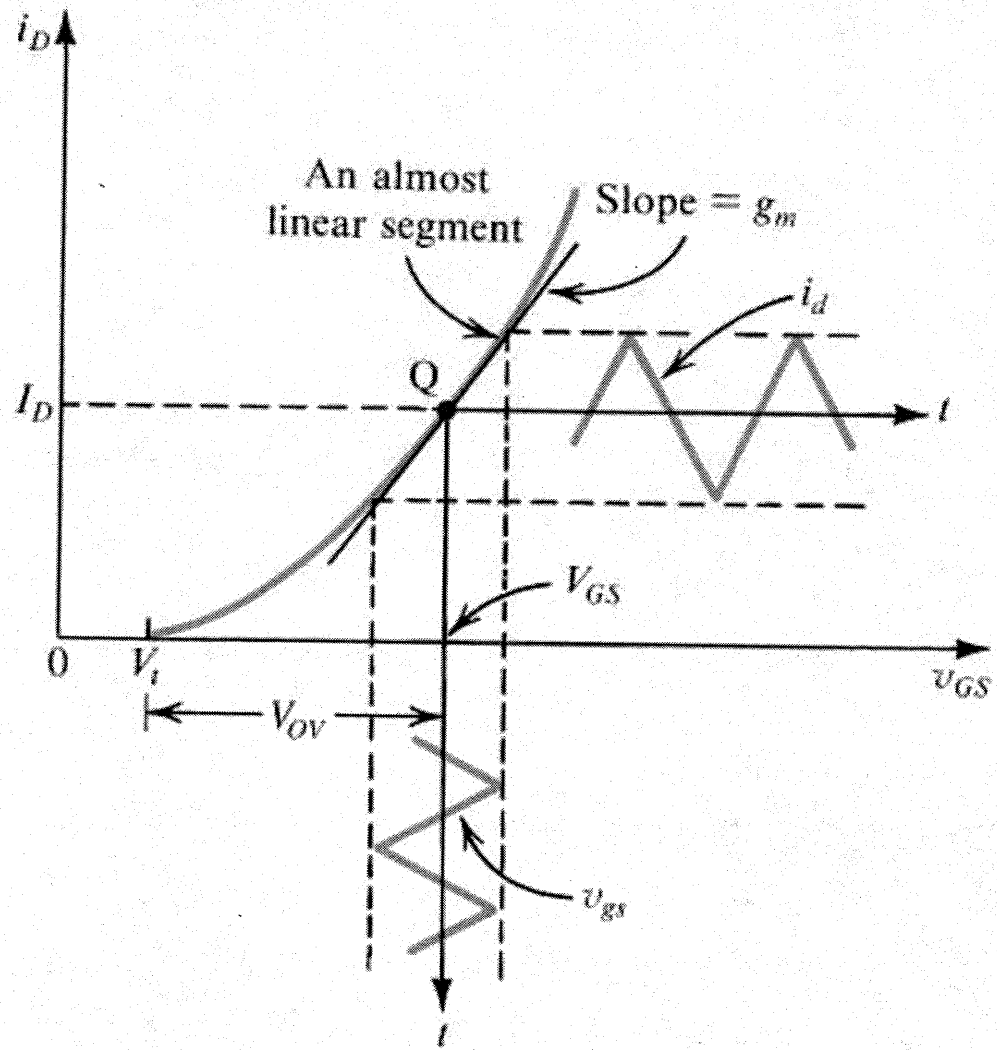


Figure 4.35 Small-signal operation of the enhancement MOSFET amplifier.

$$v_D = V_{DD} - i_D R_D = V_{DD} - R_D (I_D + i_d) = V_D + v_d$$

$$\therefore v_d = -i_d R_D$$

$$= -g_m v_{gs} R_D$$

$$\therefore A_V = \frac{v_d}{v_{gs}} = -g_m R_D$$


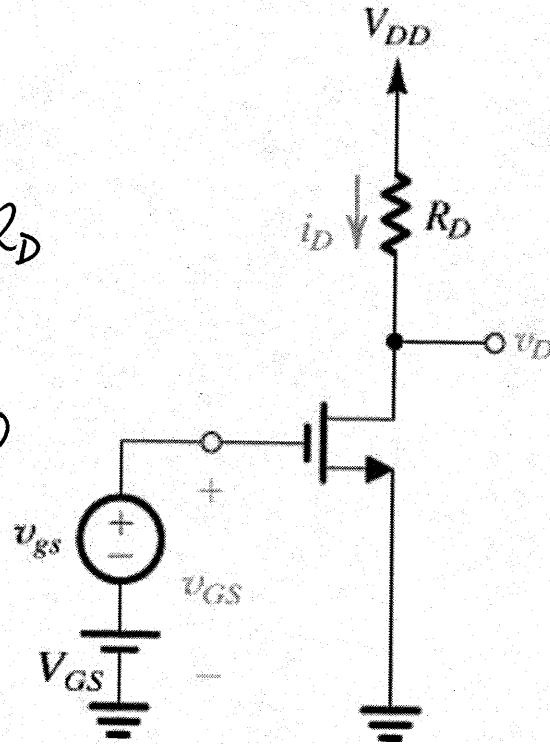



Figure 4.34 Conceptual circuit utilized to study the operation of the MOSFET as a small-signal amplifier.

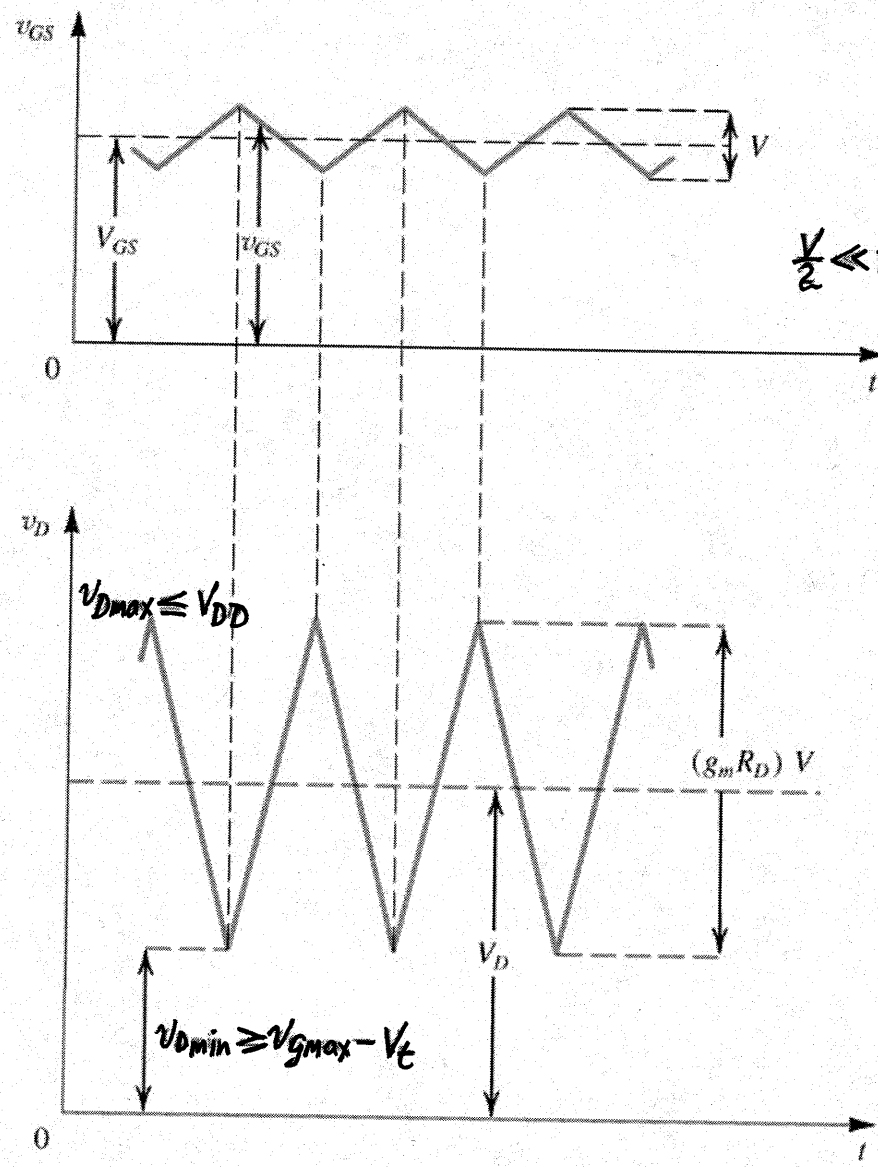


approx!
 $\frac{V}{2} \ll 2(V_{GS} - V_t)$ for λ linearity

Figure 4.36 Total instantaneous voltages v_{GS} and v_D for the circuit in Fig. 4.34.

SMALL SIGNAL EQUIVALENT CIRCUIT

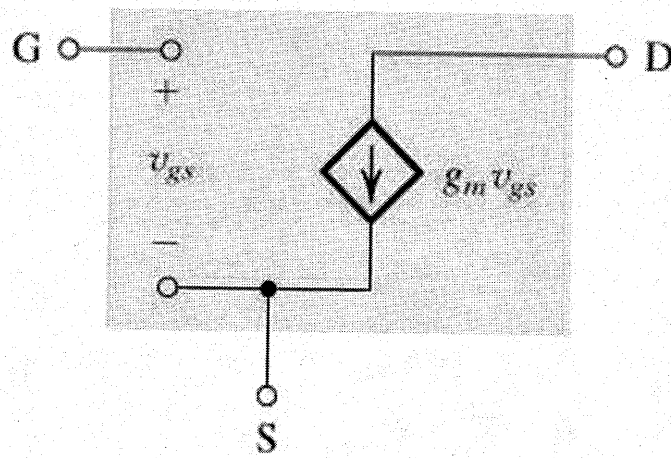

(a)

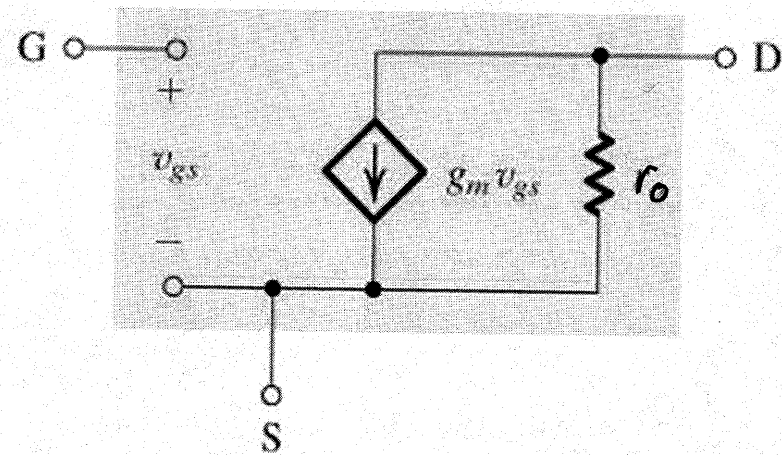

(b)


$$r_o = \frac{|V_A|}{I_D}$$

$$A_v \rightarrow -g_m (r_o \parallel R_D)$$


Figure 4.37 Small-signal models for the MOSFET: (a) neglecting the dependence of i_D on v_{DS} in saturation (the channel-length modulation effect); and (b) including the effect of channel-length modulation, modeled by output resistance $r_o = |V_A|/I_D$.

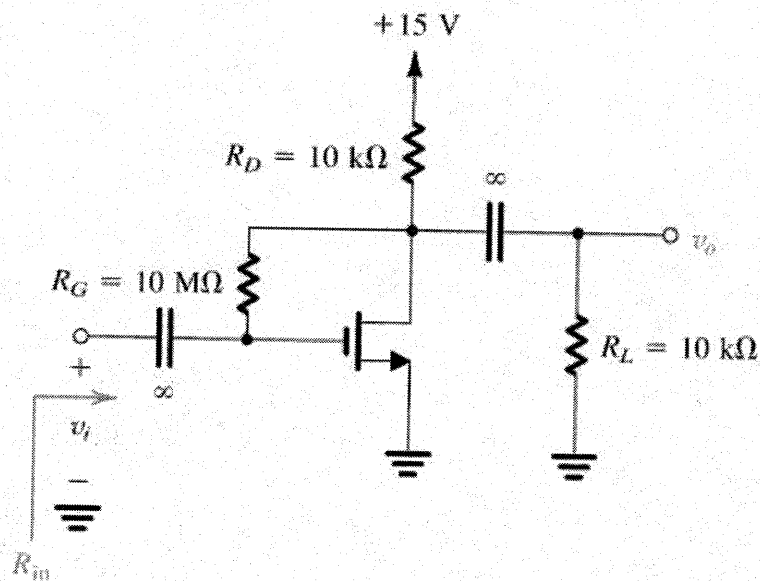Example 4.10 — Feedback R_G

- ① Find DC operating point to verify saturation and calculate V_{GS} , I_D (assuming $\lambda = 0$)



(a)

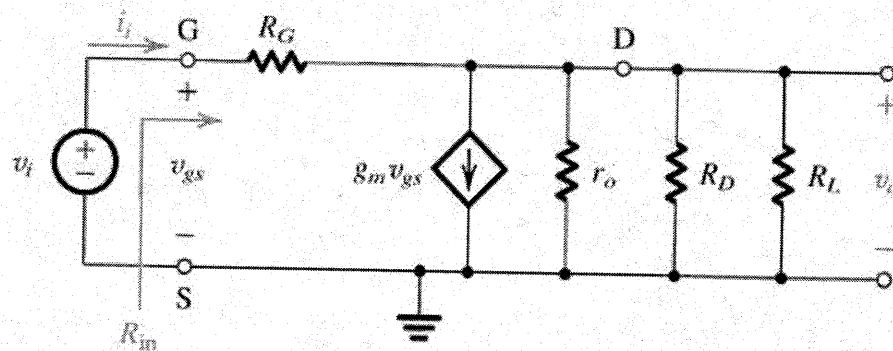

(b)

- ② Calculate g_m , r_o [Note: r_o calculation uses approximate DC bias]

Gain calculation neglects R_G (negligible current from D to G)
 But R_{in} is due to R_G \therefore must include R_G in R_{in} calculation

Figure 4.38 Example 4.10: (a) amplifier circuit; (b) equivalent-circuit model.

Hybrid- π to T-Model

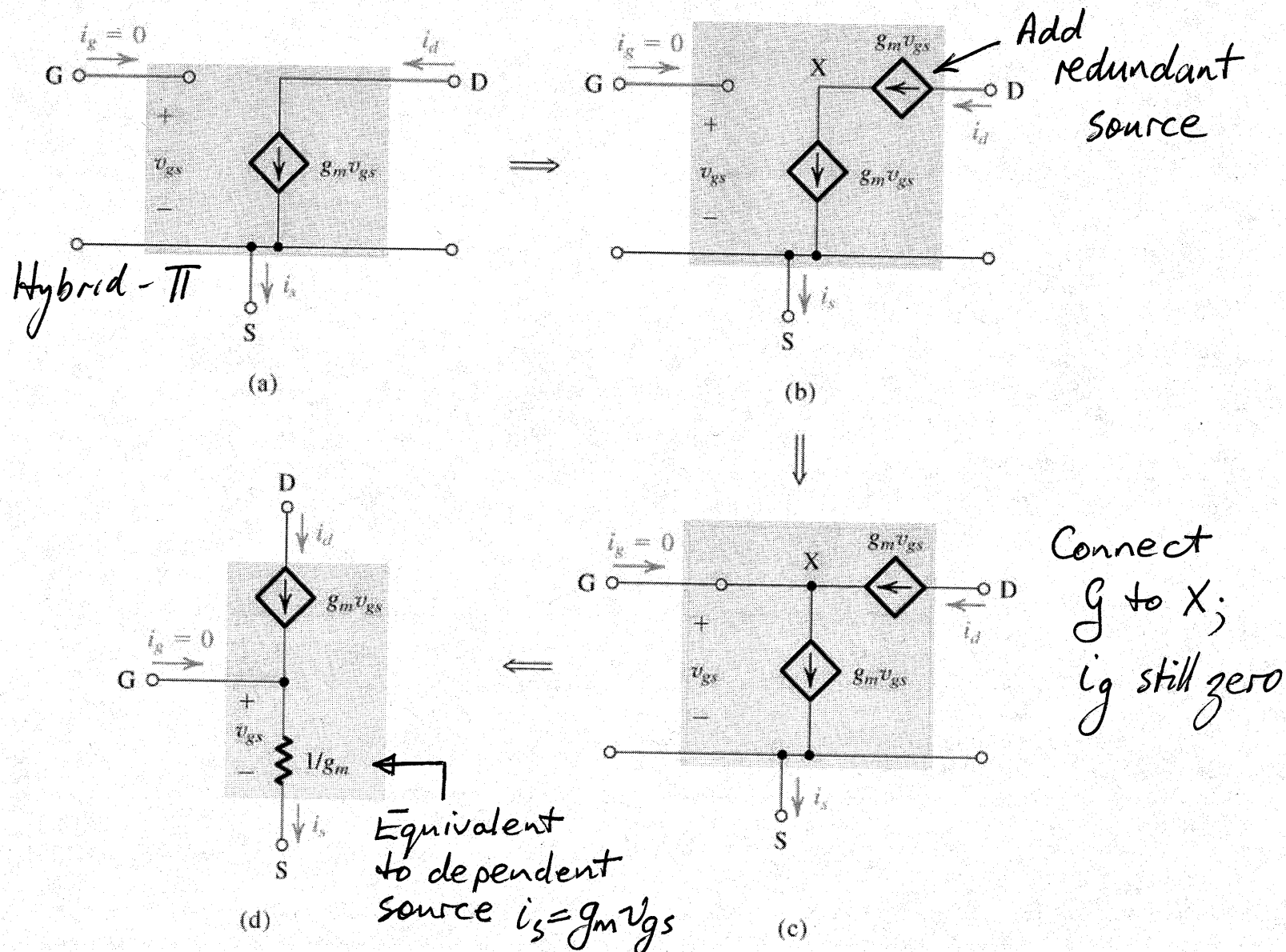


Figure 4.39 Development of the T equivalent-circuit model for the MOSFET. For simplicity, r_o has been omitted but can be added between D and S in the T model of (d).

Channel-length Modulation $\rightarrow r_o$

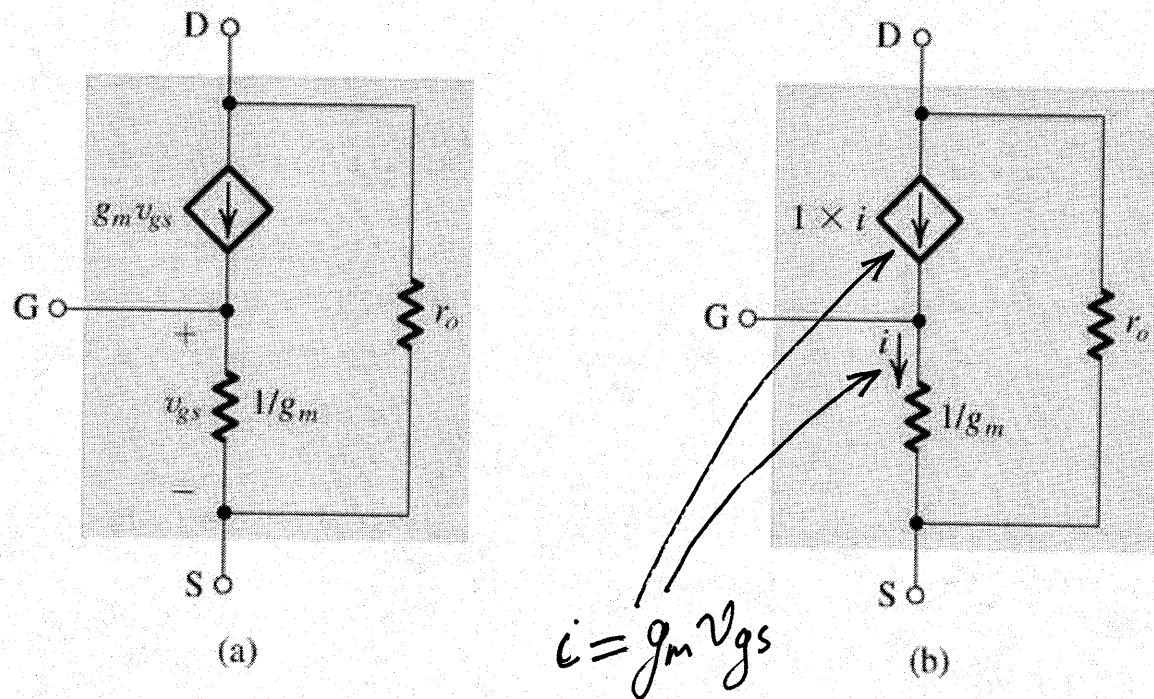


Figure 4.40 (a) The T model of the MOSFET augmented with the drain-to-source resistance r_o . (b) An alternative representation of the T model.

BODY EFFECT



See Section #4.2.5 Eqⁿ 4.33

$$V_t = V_{t0} + \gamma \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$\gamma = \frac{\sqrt{2q N_A E_s}}{C_{ox}}, \quad 2\phi_f \sim 0.6 \text{ V typ.}$$

For N-channel,

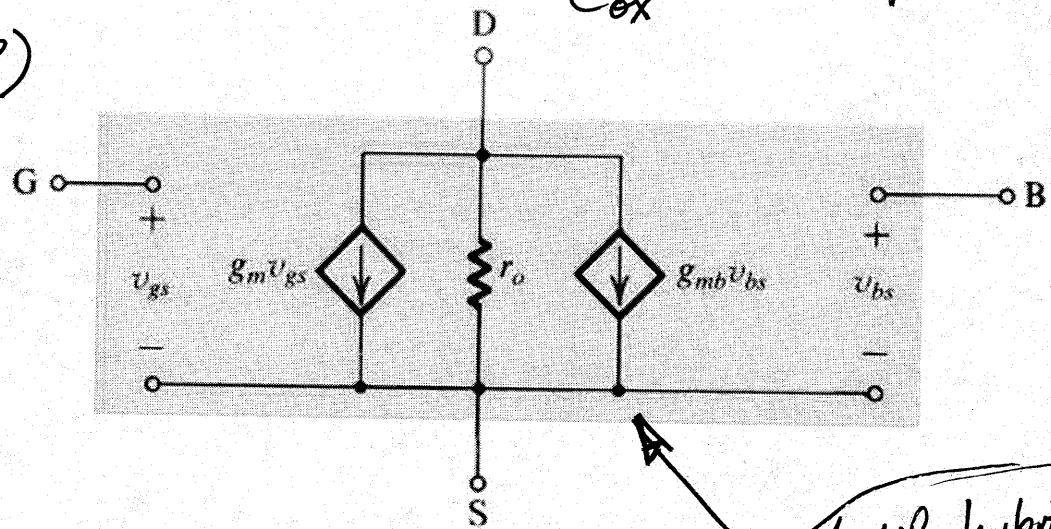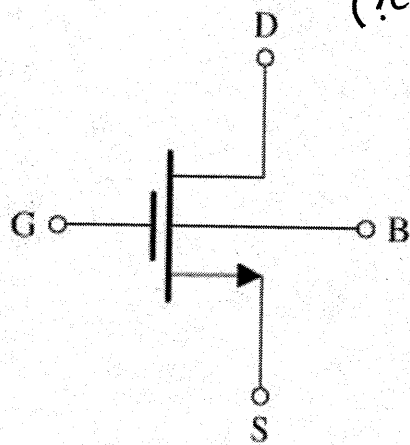Connect B (substrate) to most negative point (ie. ground?)



Modify hybrid- π

Often, S connected to ground/most negative point

If not, get $v_{bs} \neq 0 \rightarrow$ "back gate" $\rightarrow i_{ds2} = -g_{mb} v_{bs}$

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{v_{GS} \text{ constant}, v_{DS} \text{ constant}} = \chi g_m, \quad \text{where } \chi = \frac{\partial V_t}{\partial V_{SB}} = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}}$$

Figure 4.41 Small-signal equivalent-circuit model of a MOSFET in which the source is not connected to the body.

SUMMARY

NMOS

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov}$$




$$= \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$= 2 I_D / V_{ov}$$


$$r_o = V_A / I_D = 1 / \lambda I_D$$

Table 4.2

T-Models

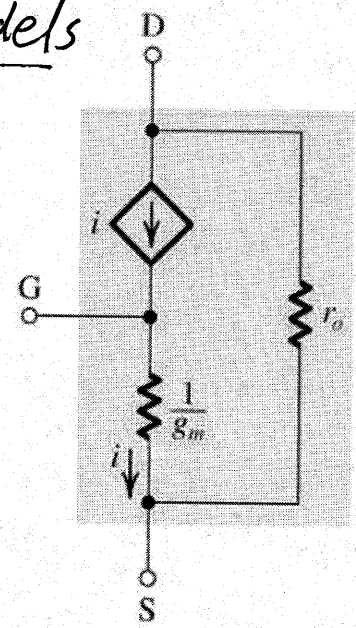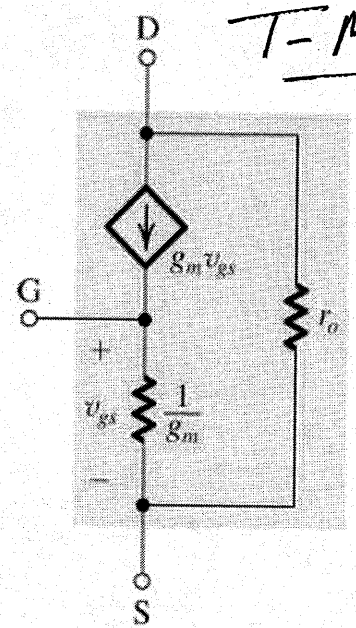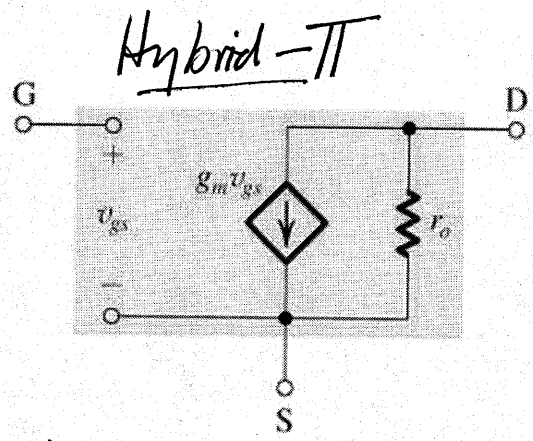

Body Effect

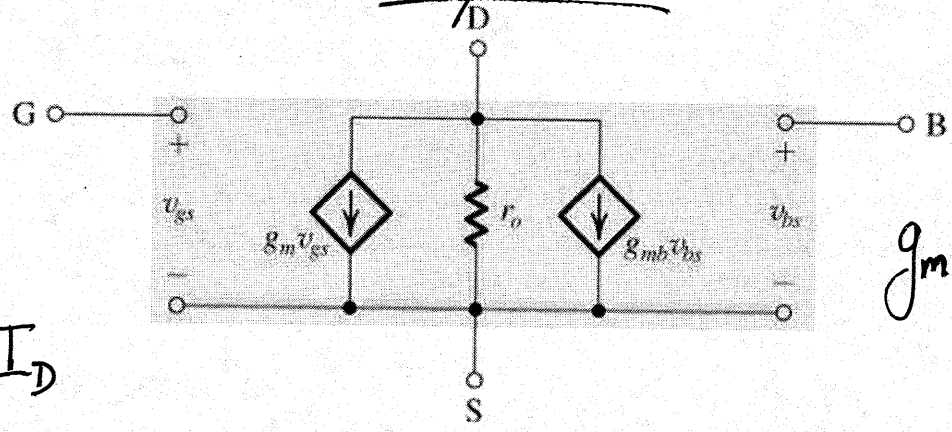

$$g_{mb} = \chi g_m$$

$$= \frac{\gamma}{2 \sqrt{2 \phi_F + V_{SB}}} g_m$$

Exercises:

4.23 For the amplifier of Fig 4.34: $V_{DD} = 5V$, $R_D = 10k\Omega$, $V_t = 1V$, $k_n' = 20\mu A/V^2$, $\frac{W}{L} = 20$, $V_{GS} = 2V$, $\lambda = 0$
 (a) Find I_D , V_D (b) Find g_m (c) Find voltage gain (d) For $v_{gs} = 0.2 \sin \omega t$ volts, find v_d assuming the small signal approximation; what are min/max values of v_D ? (e) Use eq. 4.57 to determine components of i_D . Using $\sin^2 \omega t = \frac{1}{2} - \frac{1}{2} \cos 2\omega t$, show there is a slight shift in I_D . (How much?) and a second harmonic.

4.24 An NMOS transistor has $\mu_n C_{ox} = 60\mu A/V^2$, $W/L = 40$, $V_t = 1V$, $V_A = 15V$. Find g_m , r_o when
 (a) $V_{GS} = 1.5V$, and (b) $I_D = 0.5mA$

4.25 MOSFET operates at $I_D = 0.1mA$ and needs $g_m = 1mA/V$. If $k_n' = 50\mu A/V^2$ find W/L and V_{ov} .


4.26 For process giving $\mu_p \approx 0.4\mu_n$, find W_p/W_n for equal g_m at equal bias. ($L_1 = L_2$)

4.27 NMOS transistor. $2\phi_F = 0.6V$, $\gamma = 0.5V^{1/2}$, $V_{SB} = 4V$. Find $\chi = g_{mb}/g_m$

4.28 PMOS transistor $V_t = -1V$, $k_p' = 60\mu A/V^2$, $W/L = 16\mu m/0.8\mu m$. Find I_D , g_m for $V_{GS} = -1.6V$.
 Also r_o if λ (at $L = 1\mu m$) = $-0.04V^{-1}$

4.29 Derive an expression for $g_m r_o$ in terms of V_A , V_{ov} . Evaluate $g_m r_o$ for $0.8\mu m$ CMOS process, $V_A' = 12.5V/\mu m$ channel length, with min. channel length and $V_{ov} = 0.2V$

PROBLEM PH.5H

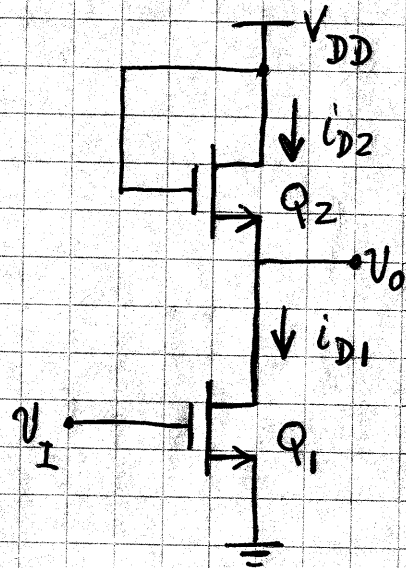

CS amplifier with load resistor R_D replaced by Q_2
 "Saturated load" or "enhancement load" NMOS

Q_2 in saturation, since $v_{DG} = 0$

$$i_{D1} = i_{D2}$$

For Q_1 in saturation i.e. $v_{DS1} > v_{GS1} - V_{t1}$ & $v_{GS1} > V_{t1}$

for $v_O + V_{t1} > v_I > V_{t1}$

$$\frac{1}{2} k_n' \left(\frac{W}{L}\right)_1 (v_{GS1} - V_{t1})^2 = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_2 (v_{GS2} - V_{t2})^2 \quad v_{GS1} = v_I \text{ \& } v_{GS2} = V_{DD} - v_O$$

$$\therefore \left(\frac{W}{L}\right)_1 (v_I - V_{t1})^2 = \left(\frac{W}{L}\right)_2 (V_{DD} - v_O - V_{t2})^2$$

$$\left[\frac{(W/L)_1}{(W/L)_2}\right]^{1/2} (v_I - V_{t1}) = (V_{DD} - v_O - V_{t2})$$

$$v_O = V_{DD} - \left[\frac{(W/L)_1}{(W/L)_2}\right]^{1/2} v_I + \left[\frac{(W/L)_1}{(W/L)_2}\right]^{1/2} V_{t1} - V_{t2}$$


$$= V_{DD} - A v_I + (A-1)V_t \quad \text{for } V_{t1} = V_{t2} = V_t \text{ \& } A = \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

For $v_I < V_t$, $i_{D1,2} = 0$ & $v_O \leq V_{DD}$ (v_{DS2} undefined)

For $v_I > v_O + V_t$, Q_1 in triode \Rightarrow

$$2 \left(\frac{W}{L}\right)_1 [(v_I - V_t)v_O - v_O^2/2] = \left(\frac{W}{L}\right)_2 (V_{DD} - v_O - V_t)^2$$

until $v_I > \frac{V_{DD} + AV_t}{1+A}$

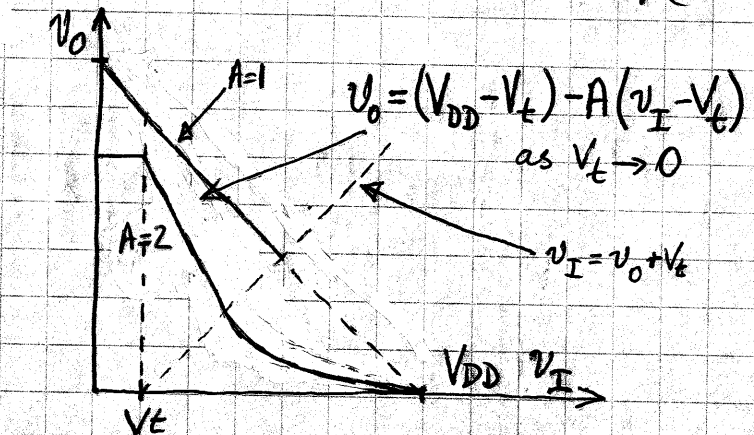

SINGLE-STAGE MOS Amplifiers (Assume $\lambda = 0$ for simplicity)

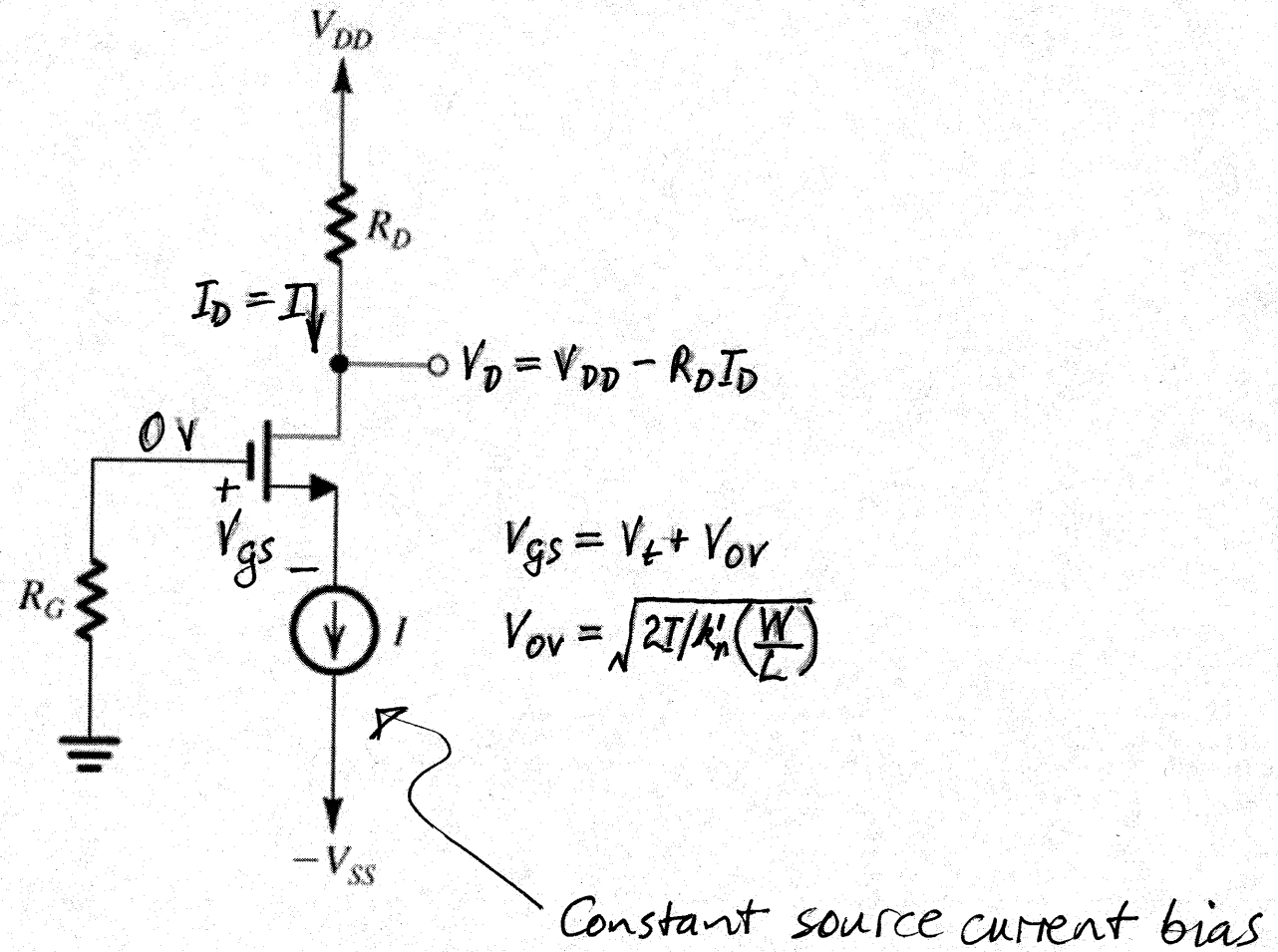


Figure 4.42 Basic structure of the circuit used to realize single-stage discrete-circuit MOS amplifier configurations.

Exercise 4.30

CS Amplifier


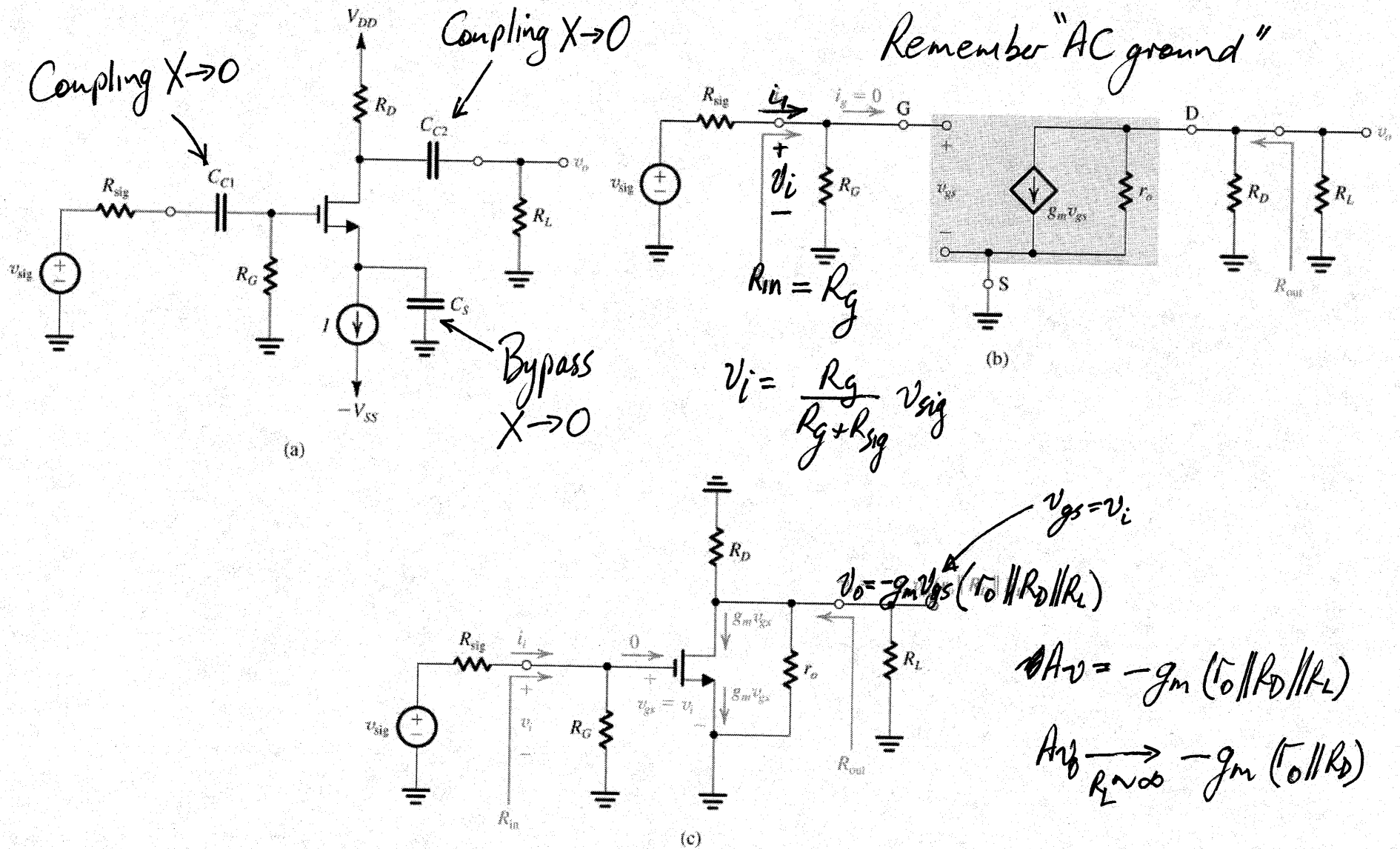


Figure 4.43 (a) Common-source amplifier based on the circuit of Fig. 4.42. (b) Equivalent circuit of the amplifier for small-signal analysis. (c) Small-signal analysis performed directly on the amplifier circuit with the MOSFET model implicitly utilized.

CS Amplifier with Source Resistor R_S

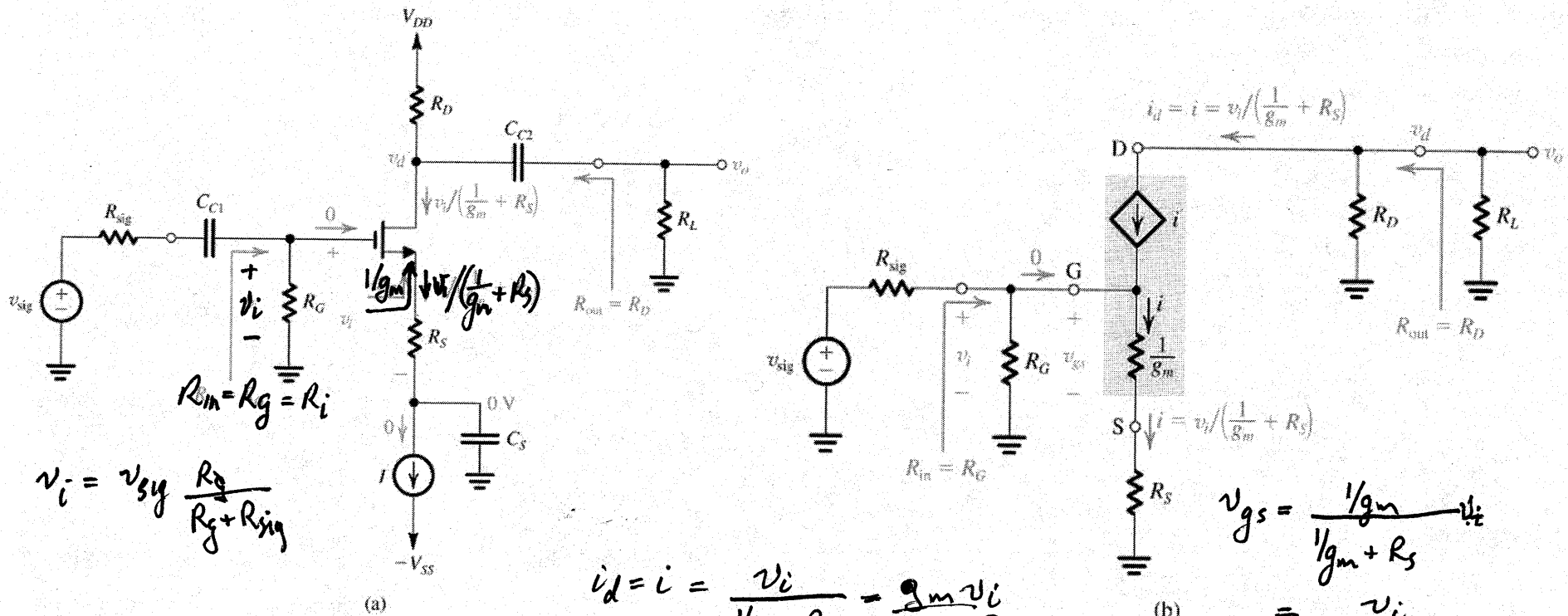(Neglect $r_o \rightarrow$ major complication)



$$v_i = v_{sig} \frac{R_G}{R_G + R_{sig}}$$

$$R_{in} = R_G = R_i$$

$$i_d = i = \frac{v_i}{\frac{1}{g_m} + R_S} = \frac{g_m v_i}{1 + g_m R_S}$$

$$v_{gs} = \frac{\frac{1}{g_m} v_i}{\frac{1}{g_m} + R_S} = \frac{v_i}{1 + g_m R_S}$$


$$v_o = -i_d (R_D || R_L) = -\frac{g_m (R_D || R_L) v_i}{1 + g_m R_S}$$

$$\therefore A_V = -\frac{g_m}{1 + g_m R_S} (R_D || R_L) \xrightarrow{R_S = \infty} A_{V0} = -\frac{g_m R_D}{1 + g_m R_S}$$

Figure 4.44 (a) Common-source amplifier with a resistance R_S in the source lead. (b) Small-signal equivalent circuit with r_o neglected.

$$G_V = -\frac{R_G}{R_G + R_{sig}} \cdot \frac{g_m}{1 + g_m R_S} (R_D || R_L)$$

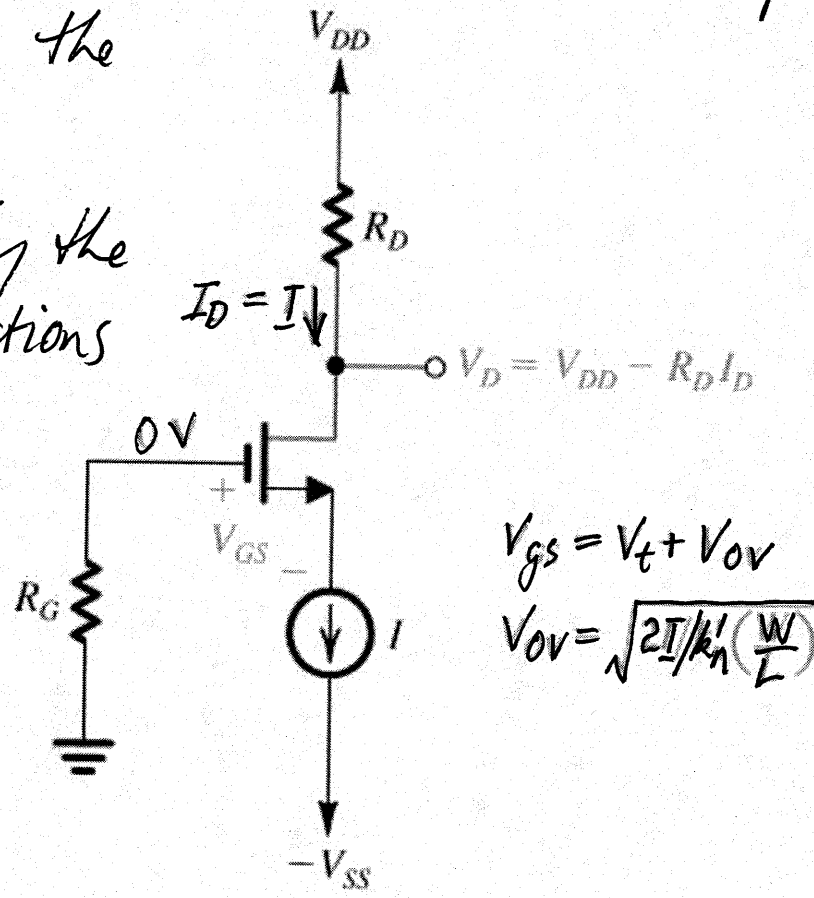The Common Gate & Common Drain amplifiers use the same bias circuit as the Common Source amplifier. Only the AC signal connections change.



$$V_{GS} = V_t + V_{OV}$$


$$V_{OV} = \sqrt{2I/k'_n \left(\frac{W}{L}\right)}$$

Assume saturation

Figure 4.42 Basic structure of the circuit used to realize single-stage discrete-circuit MOS amplifier configurations.

Fig 4.42 from last lecture

Common Gate (CG) Amplifier

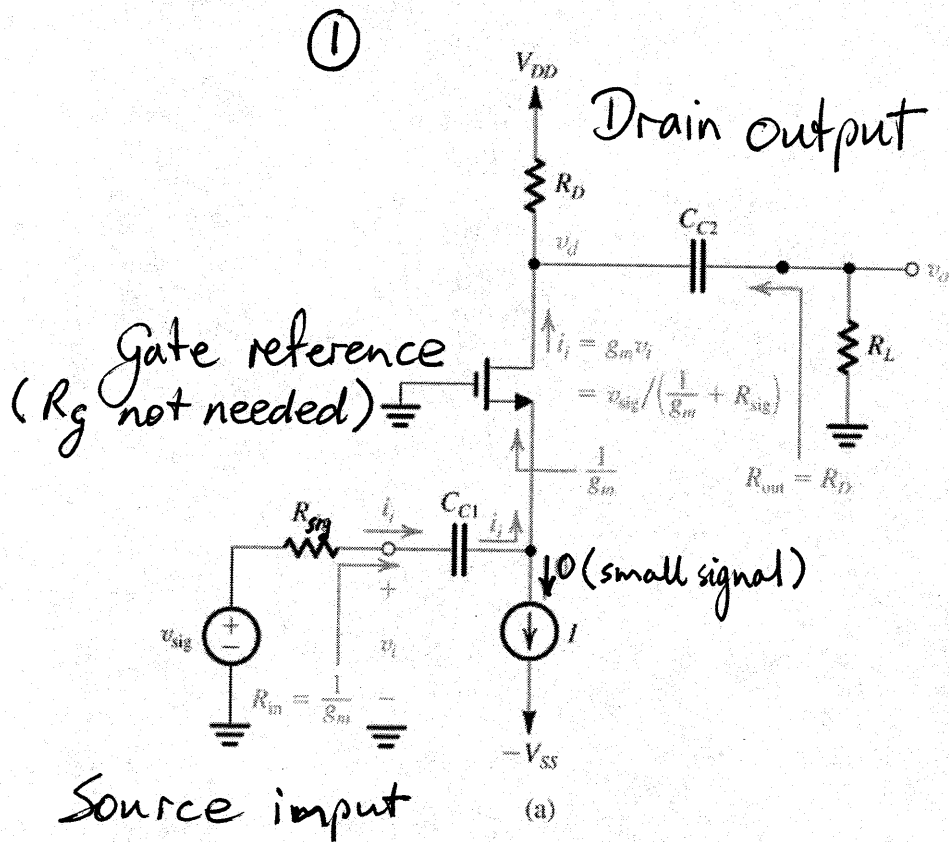

Note: r_o excluded; would connect input to output — complications!

② T-model circuit

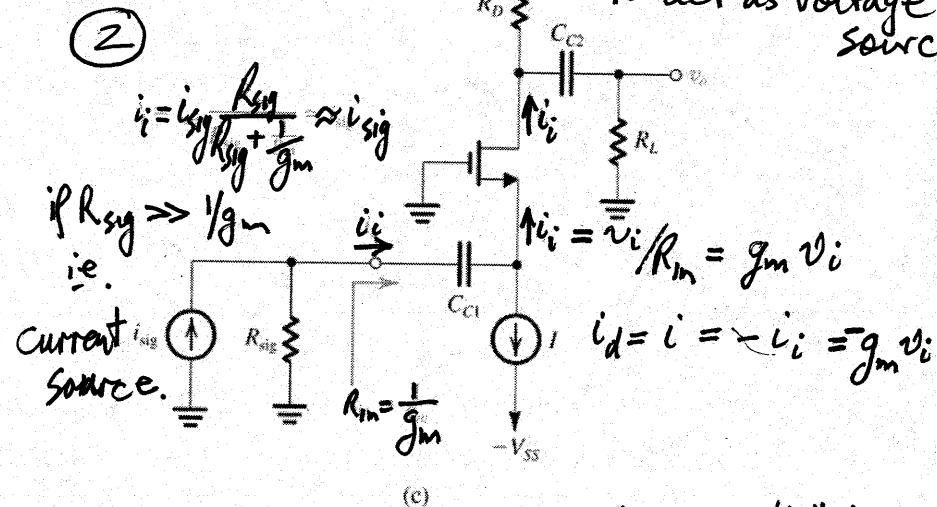
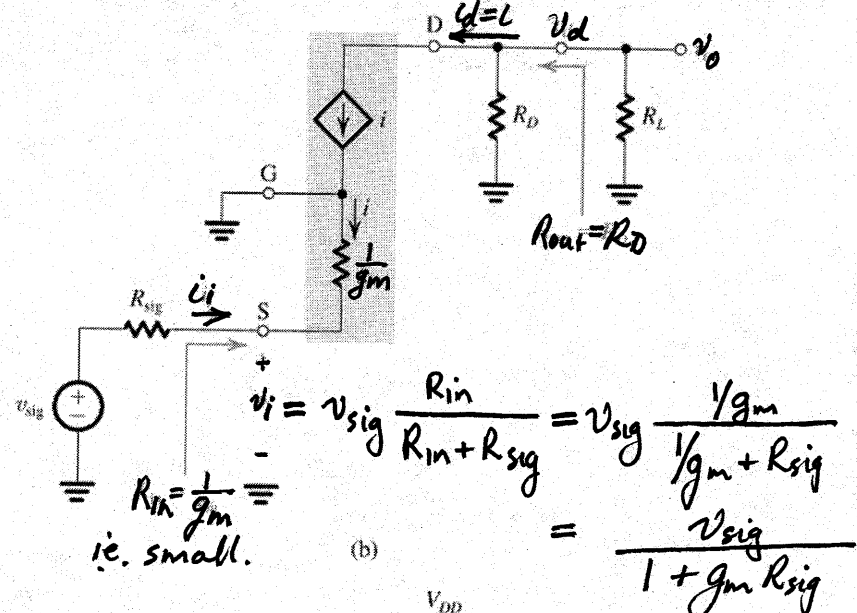


Figure 4.45 (a) A common-gate amplifier based on the circuit of Fig. 4.42. (b) A small-signal equivalent circuit of the amplifier in (a). (c) The common-gate amplifier fed with a current-signal input.

$$G_v = \frac{v_o}{v_i} \frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} \cdot g_m (R_D || R_L) = \frac{g_m}{1 + g_m R_{sig}} (R_D || R_L)$$





$R_{in} = 1/g_m$ relatively small \therefore current input \rightarrow unity gain current amp.

$$A_v = \frac{v_o}{v_i} = -i_d (R_D || R_L) / v_i = +g_m \frac{v_i}{v_i} (R_D || R_D)$$

$$\therefore A_{v0} = +g_m R_D$$

Common Drain (CD) Amplifier

T-model circuit

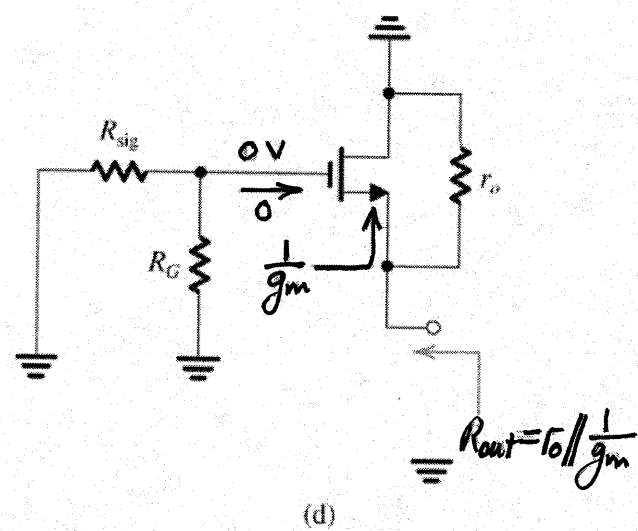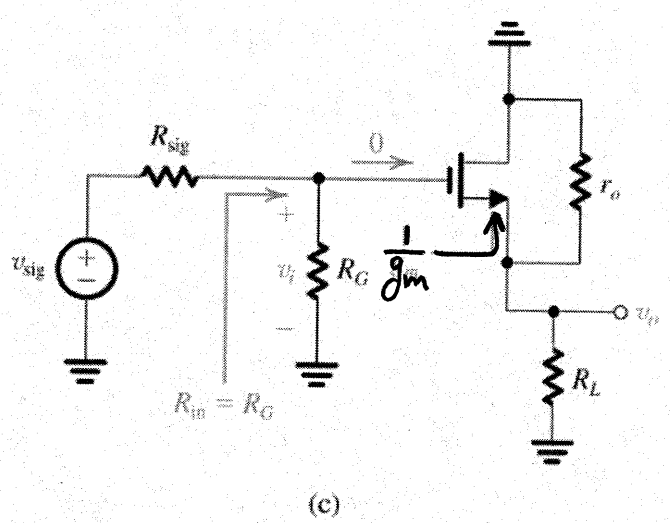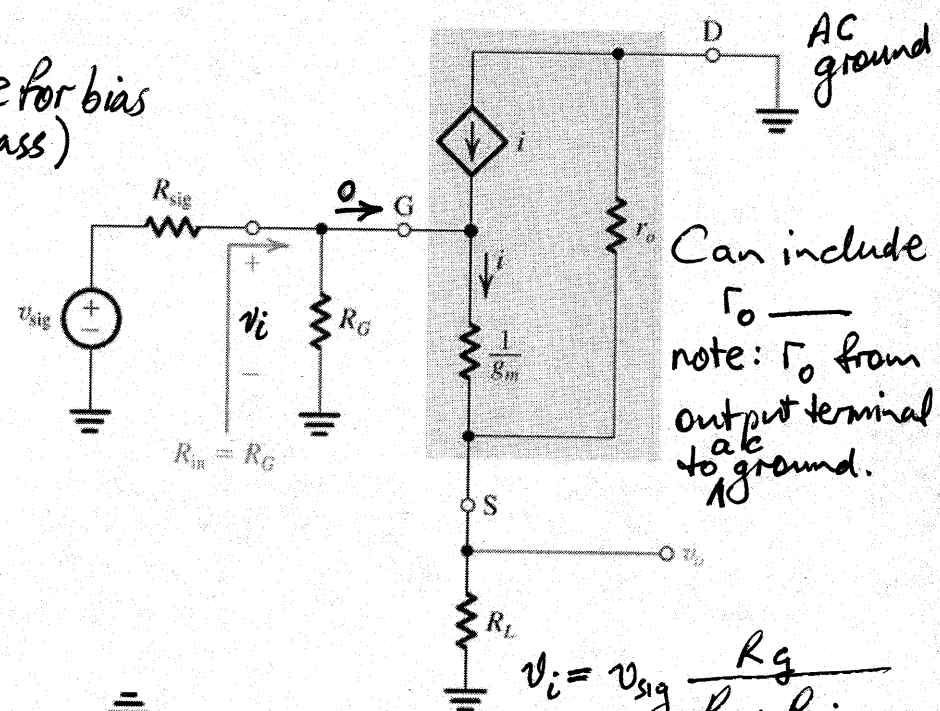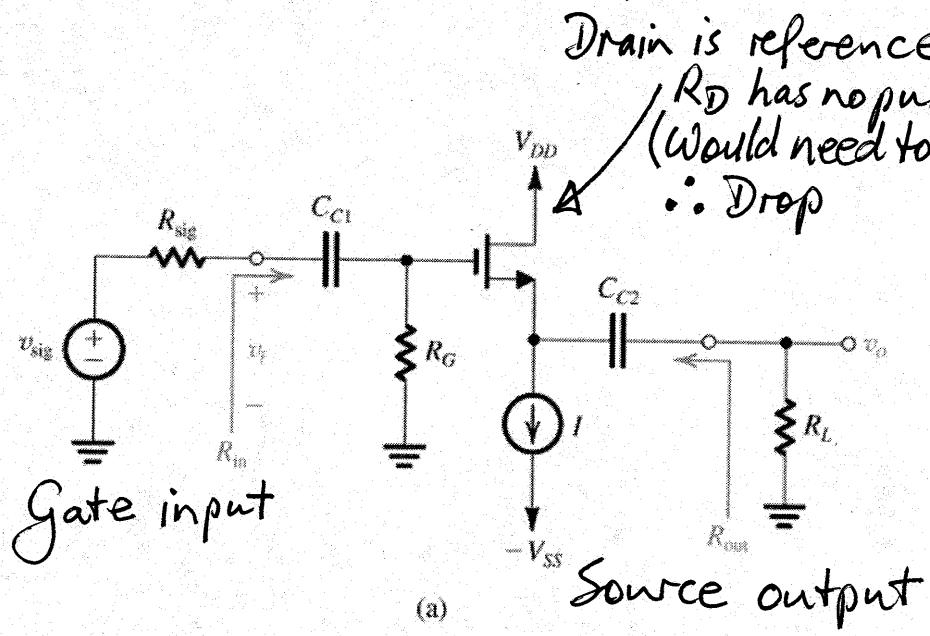

$$v_i = v_{sig} \frac{R_g}{R_g + R_{sig}}$$

$$\approx v_{sig} \text{ if } R_g \gg R_{sig}$$

$$\frac{v_o}{v_i} = \frac{(R_L \parallel r_o)}{1/g_m + (R_L \parallel r_o)}$$

$$A_v = \frac{g_m (R_L \parallel r_o)}{1 + g_m (R_L \parallel r_o)}$$

$$\approx 1$$

$$A_{vo} = \frac{g_m r_o}{1 + g_m r_o} \approx 1$$

Figure 4.46 (a) A common-drain or source-follower amplifier. (b) Small-signal equivalent-circuit model. (c) Small-signal analysis performed directly on the circuit. (d) Circuit for determining the output resistance R_{out} of the source follower.


$$G_v = \frac{R_g}{R_g + R_{sig}} \cdot \frac{g_m (R_L \parallel r_o)}{1 + g_m (R_L \parallel r_o)} \approx 1$$

$$R_{out} = r_o \parallel 1/g_m \approx 1/g_m$$

Unity gain voltage amplifier \rightarrow Source follower

SUMMARY


CS
Voltage amplifier

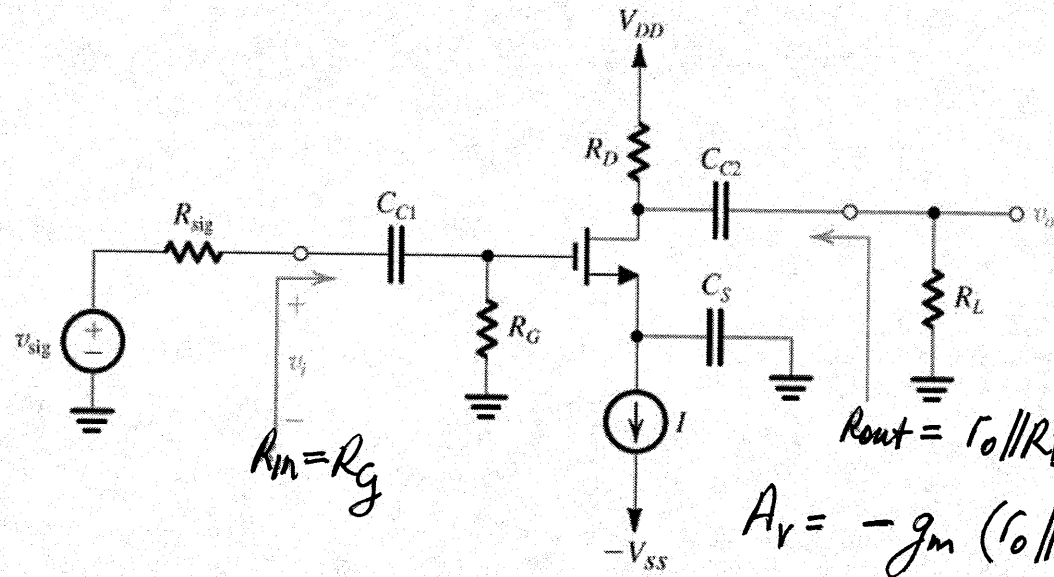

$$A_v = -g_m (r_o || R_D || R_L)$$

$$G_v = -\frac{R_g}{R_g + R_{sig}} g_m (r_o || R_D || R_L)$$

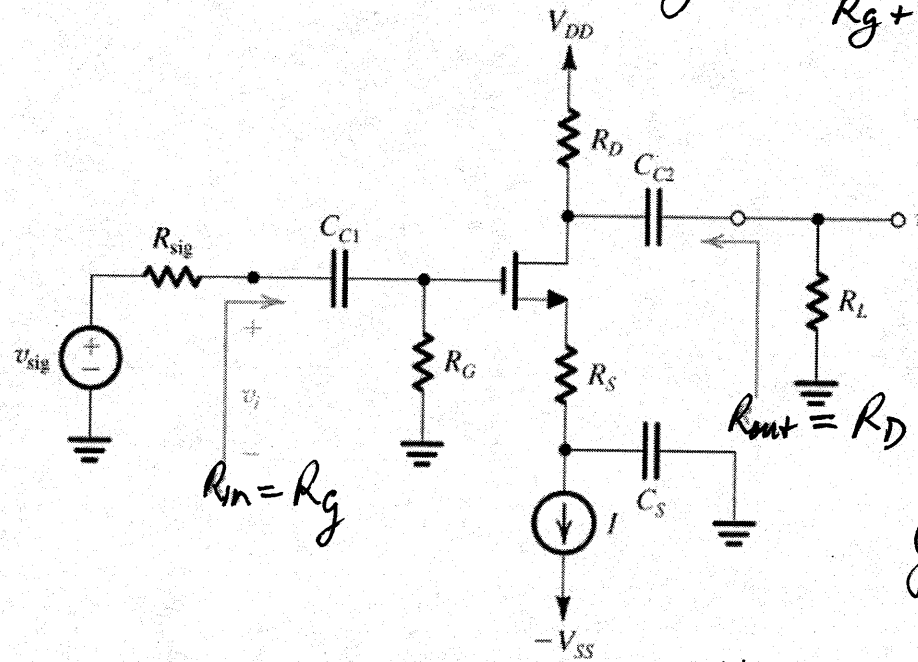CS with R_s
Reduced gain
Voltage amplifier



Note: r_o neglected here.

$$A_v = \frac{-g_m (R_L || R_D)}{1 + g_m R_s}$$


$$G_v = \frac{R_g g_m (R_o || R_L)}{R_g + R_{sig} (1 + g_m R_s)}$$

Note: $v_{gs} = \frac{v_i}{1 + g_m R_s}$

Table 4.4

(CG)

Note: Neglecting r_o

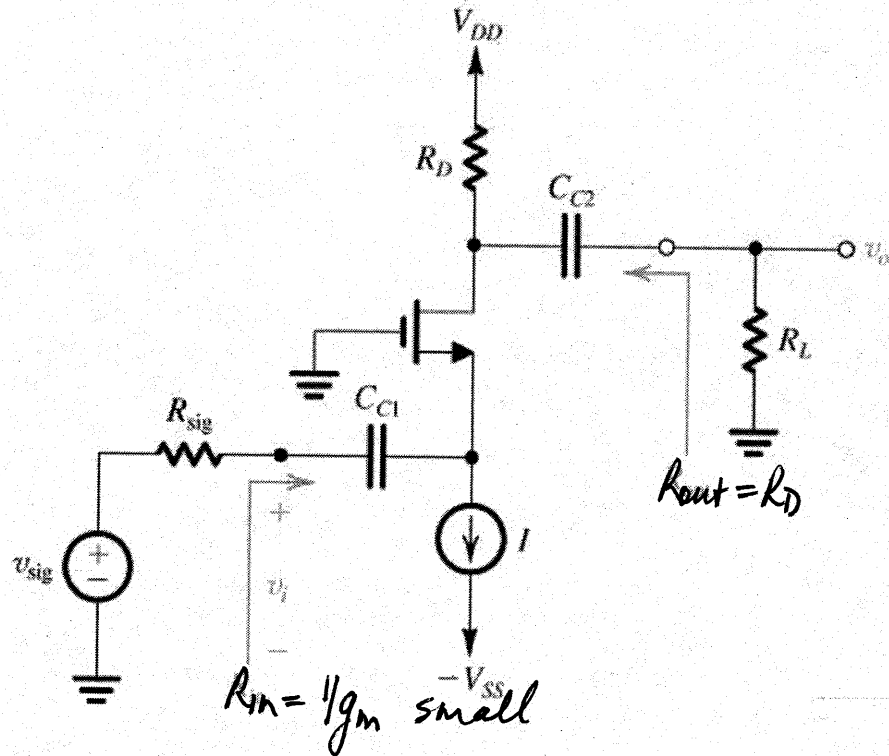


$$A_v = g_m (R_D \parallel R_L)$$

$$G_v = \frac{g_m (R_D \parallel R_L)}{1 + g_m R_{sig}}$$

Table 4.4 (Continued)

Current follower \rightarrow Cascode circuit

(CD)

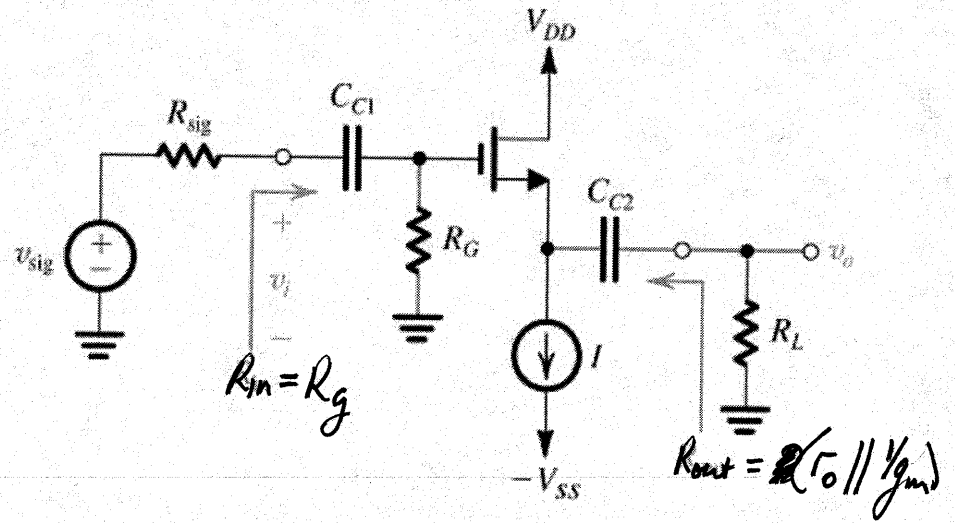

$$A_v = \frac{g_m (r_o \parallel R_L)}{1 + g_m (r_o \parallel R_L)}$$

$$G_v = \frac{R_g}{R_g + R_{sig}} \frac{r_o \parallel R_L}{(r_o \parallel R_L) + \frac{1}{g_m}}$$

Voltage follower

Assignment #5

Problems:

D4.36

D4.37



D4.56

4.74

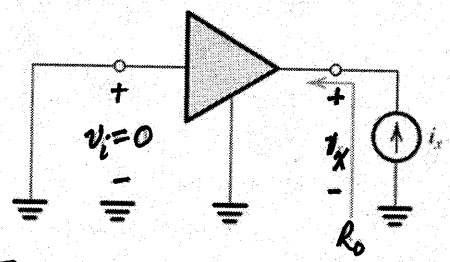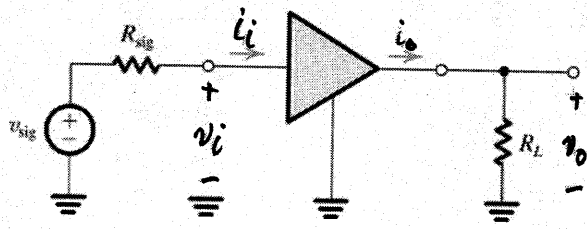4.75

Generalized Amplifiers

- ① Basic amplifier: R_i R_o A_{vo} A_{is} G_m
- ② Generalized \rightarrow R_{in} R_{out} A_v A_i G_{vo} G_v
 May depend on R_{sig}, R_L $R_i = R_{in} \Big]_{R_L = \infty}$ $R_o = R_{out} \Big]_{R_{sig} = 0}$
- ③ Unilateral amplifiers (no internal feedback) $R_i = R_{in}$ $R_o = R_{out}$
 Non-unilateral amplifiers (with feedback) $R_{in} \neq R_i$ $R_{out} \neq R_o$
 in general
- ④ $G_v = v_o/v_{sig}$ Overall voltage gain
 $G_{vo} = \frac{v_o}{v_{sig}} \Big]_{R_L = \infty} = G_v \Big]_{R_L = \infty}$ Open circuit overall voltage gain



Compare


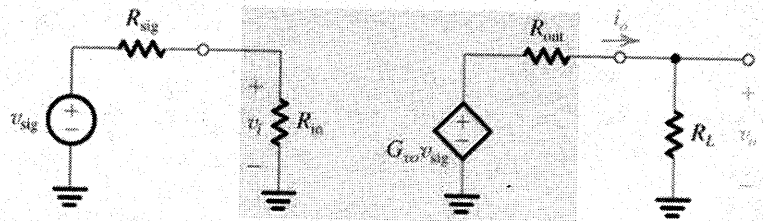
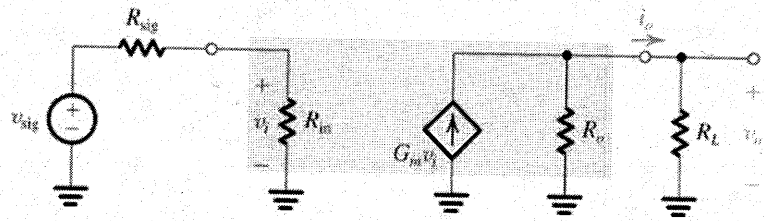
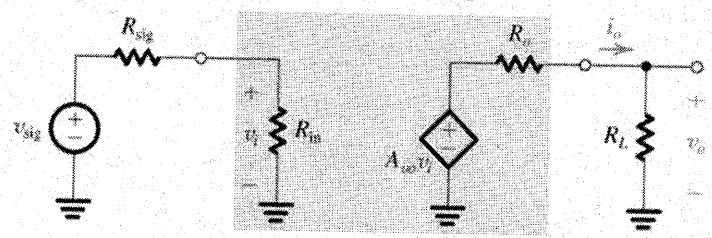
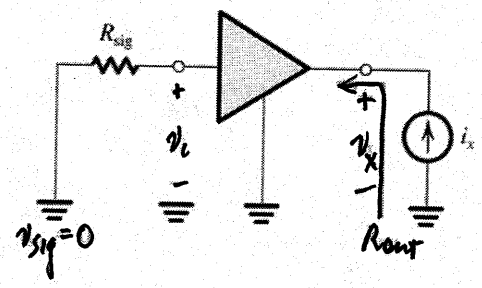


Table 4.3

Amplifier characteristics

Circuit

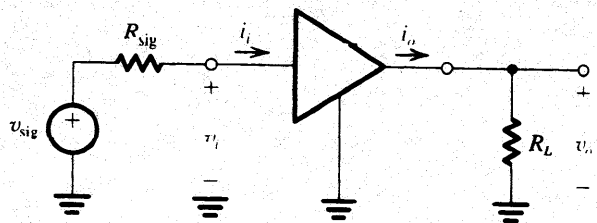

Definitions

- Input resistance with no load:

$$R_i \equiv \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$$

- Input resistance:

$$R_{in} \equiv \frac{v_i}{i_i}$$

- Open-circuit voltage gain:

$$A_{vo} \equiv \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$$

- Voltage gain:

$$A_v \equiv \frac{v_o}{v_i}$$

- Short-circuit current gain:

$$A_{is} \equiv \left. \frac{i_o}{i_i} \right|_{R_L = 0}$$

- Current gain:

$$A_i \equiv \frac{i_o}{i_i}$$

- Short-circuit transconductance:


$$G_m \equiv \left. \frac{i_o}{v_i} \right|_{R_L = 0}$$

- Output resistance of amplifier proper:

$$R_o \equiv \left. \frac{v_x}{i_x} \right|_{v_i = 0}$$

- Output resistance:

$$R_{out} \equiv \left. \frac{v_x}{i_x} \right|_{v_{sig} = 0}$$

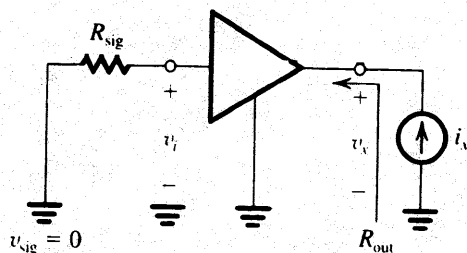


- Open-circuit overall voltage gain:

$$G_{vo} \equiv \left. \frac{v_o}{v_{sig}} \right|_{R_L = \infty}$$


- Overall voltage gain:

$$G_v \equiv \frac{v_o}{v_{sig}}$$

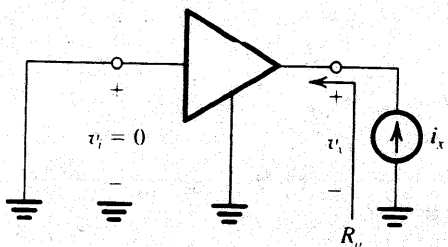


Equivalent Circuits


- A:

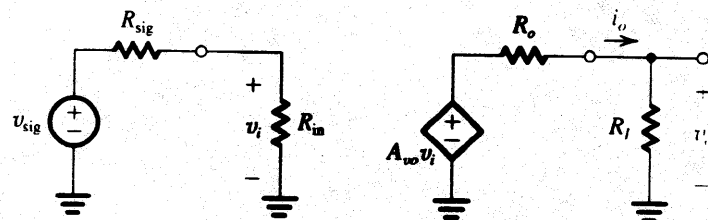

- B:

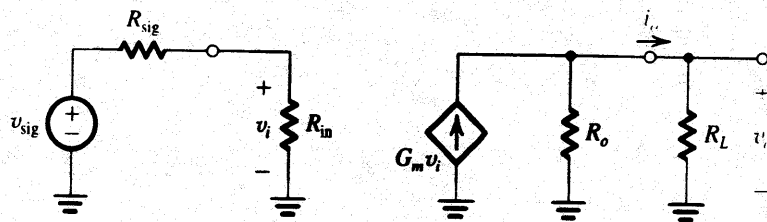

- C:

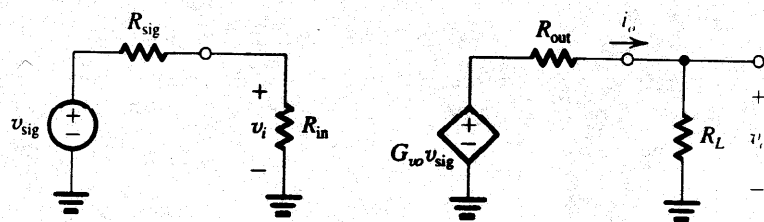

Relationships

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}$$

$$A_v = A_{vo} \frac{R_L}{R_L + R_o}$$

$$A_{vo} = G_m R_o$$

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o}$$

$$G_{vo} = \frac{R_i}{R_i + R_{sig}} A_{vo}$$

$$G_v = G_{vo} \frac{R_L}{R_L + R_{out}}$$

Exercise 4.31 (include Example 4.11)

Exercise 4.32

Exercise 4.33

Ex 4.30 See Fig 4.42. $V_{DD} = V_{SS} = 10V$, $I = 0.5mA$, $R_g = 4.7M\Omega$, $R_D = 15K\Omega$, $V_t = 1.5V$
 $k_n' W/L = 1mA/V^2$, Find V_{ov} , V_{GS} , V_G , V_S , V_D , g_m , f_0 for $V_A = 75V$
 Max signal swing at drain to remain saturated?


4.31 (a) For Example 4.11, if R_{sig} is doubled, find R_{in} , G_v , R_{out}
 (b) Repeat for R_{sig} same, R_L doubled
 (c) " " both R_L & R_{sig} doubled

4.32 CS amplifier, based on Fig 4.30: Find R_{in} , A_{vo} , R_{out} with & without C_s .
 Calculate G_v (incl C_s) for $R_{sig} = 100K\Omega$, $R_L = 15K\Omega$. Output for $V_{sig} = 0.4V$ p-p.

4.33 Ex 4.32 (cont'd) $\cdot 4V \xrightarrow{p-p} 2.8V$ Incr input $\rightarrow 1.2V$ p-p. Find R_g for same A_v output.

Example 4.11 → Ex. 4.31

Example 4.11

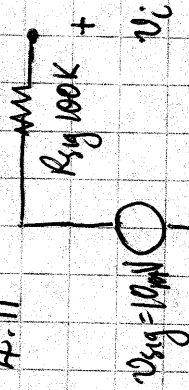

$R_L = \infty$	v_o
$R_L = 10K$	90mV
	70mV

No R_L : $A_{v0} = 90/9 = 10$

$G_{v0} = 90/10 = 9 = \frac{R_i}{R_i + R_{sig}}$

$A_{v0} \rightarrow 9 = 10 \frac{R_i}{R_i + 100K}$
 $\therefore R_i = 900K$

$R_L = 10K$: $A_v = 70/8 = 8.75$

$G_v = 70/10 = 7$

$A_v = \frac{R_L}{R_L + R_o} A_{v0} \rightarrow \frac{70}{8} = \frac{10}{10 + R_o}$

$\therefore R_o = \frac{800 - 700}{7} = 1.43K$

Similarly

$G_v = G_{v0} \frac{R_L}{R_L + R_{out}} \rightarrow 7 = 9 \frac{10}{10 + R_{out}}$

$\therefore R_{out} = \frac{90 - 70}{7} = 2.86K$


$\frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} \rightarrow \frac{8}{10} = \frac{R_{in}}{R_{in} + 100}$

$\therefore R_{in} = \frac{800}{2} = 400K$

$G_m = A_{v0}/R_o = 10/1.43K = 7mA/V$

$A_i = \frac{v_o/R_L}{v_i/R_{in}} = \frac{v_o}{v_i} \frac{R_{in}}{R_L} = \frac{70}{8} \frac{400}{10} = \frac{28}{8} \cdot 100 = 350$

$A_{is} =$

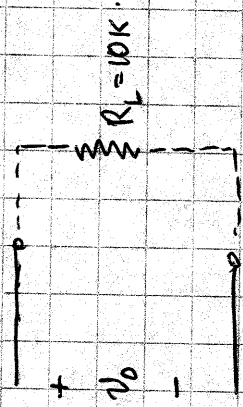

Ex 4.31

Want R_{in} , G_v , R_{out} for


R_L	R_{sig}
(a) 10K	100K
(b) 20K	200K
(c) 20K	200K

← Example 4.11

$$R_{in} \Rightarrow \frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}$$

$$G_v \Rightarrow \frac{v_o}{v_i} \cdot \frac{v_i}{v_{sig}}$$
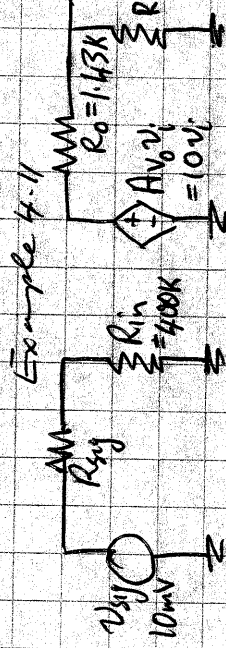
$$R_{out} \Rightarrow G_v = G_{vo} \frac{R_L}{R_L + R_{out}}$$



(a) R_{in} indep of $R_{sig} \rightarrow 400K$.

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{400}{400 + 200} \cdot 8.75 = 5.83$$

$$G_{vo} = \frac{R_L}{R_L + R_{sig}} A_{vo} = \frac{900}{900 + 200} \cdot 10 = 8.18$$

$$G_v = G_{vo} \frac{R_L}{R_L + R_{out}} \rightarrow 5.83 = 8.18 \frac{10}{10 + R_{out}} \rightarrow R_{out} = \frac{81.8 - 5.83}{5.83} = 12.03K$$

← E4.11 unchanged indep of R_{sig}

(b)

R_{sig} same $\rightarrow R_o$, R_{out} as for E4.11 $R_{out} = 2.86K$

G_{vo} is for $R_L = \infty$ \therefore Same $\rightarrow G_{vo} = 9$

$$\therefore G_v = G_{vo} \frac{R_L}{R_L + R_{out}} = 9 \frac{20}{20 + 2.86} = 7.87$$

$$\& G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o} \rightarrow 7.87 = \frac{R_{in}}{R_{in} + 100} \cdot 10 \cdot \frac{20}{20 + 1.43} \Rightarrow R_{in} = 538K$$


(c) R_{in} as for (b) $\rightarrow 538K$

R_{out} indep of R_L \therefore Same as (a) $R_{out} = 4.03K$ from E4.11

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o} = \frac{538}{538 + 100} \cdot 10 \cdot \frac{20}{20 + 1.43} = 6.8$$

Ex 4.30

Fig 4.42

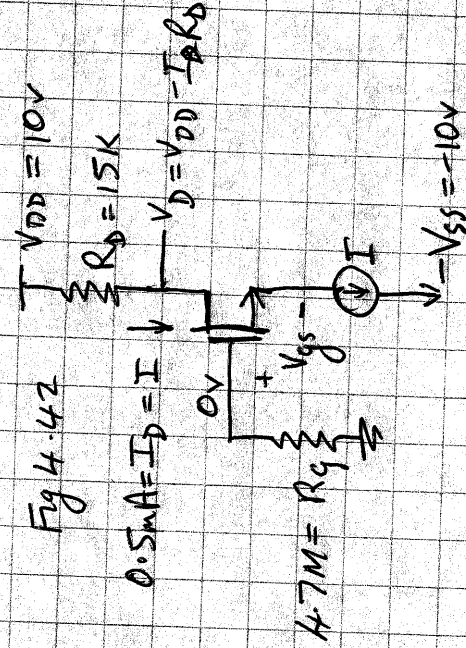

$$V_{ov} = V_{gs} - V_t$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{ov})^2$$

$$\therefore V_{ov} = \left(\frac{2 \times 0.5 \text{mA}}{1 \text{mA}} \right)^{1/2} = 1 \text{V}$$

$$\therefore V_{gs} = V_{ov} + V_t = 2.5 \text{V}$$

$$V_g = 0 \text{V}$$

$$\therefore V_s = -2.5 \text{V}$$

$$V_D = 10 - 15 \times 10^3 \times 0.5 \times 10^{-3} = 2.5 \text{V}$$

$$g_m = 2I_D/V_{ov} = 1 \text{mA/V} \quad r_o = 150 \text{K}$$

$$r_o = V_A/I_D = 75 \text{V}/0.5 \text{mA} = 150 \text{K}$$

Ex 4.30

$$V_t = 1.5 \text{V}$$

$$k_n' \frac{W}{L} = 1 \text{mA/V}^2$$

$$0.5 \text{mA} = I_D = I$$

$$4.7 \text{M} = R_g$$

$$-V_{SS} = -10 \text{V}$$

Ex 4.31

(incl 4.11)

Ex 4.32

For Ex 4.30 figure & values. $g_m = 1 \text{mA/V}$ $r_o = 150 \text{K}$
 $R_{in} = R_g = 4.7 \text{M}\Omega$ (with or without r_o)

$$A_{vo} |_{r_o = \infty} = -g_m R_D = -10^{-3} \times 15 \times 10^3 = -15$$

$$A_{vo} |_{r_o = 150 \text{K}} = -g_m (R_D || r_o) = -10^{-3} \frac{15 \times 150}{165} 10^3 = -13.64$$

$$R_{out} |_{r_o = \infty} = R_D = 15 \text{K}$$

$$R_{out} |_{r_o = 150 \text{K}} = R_D || r_o = \frac{15 \times 150}{165} \text{K} = 13.64 \text{K}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} \cdot A_{vo} \cdot \frac{R_L}{R_L + R_{out}} \xrightarrow{\text{incl } r_o} \frac{-4.07}{4.7 + 0.1} \cdot \frac{13.64}{15 + 13.64} \cdot \frac{15}{15 + 13.64} = -6.995$$

\therefore for $v_{sig} = 0.4 \text{V p-p}$ $\therefore v_o \approx 2.8 \text{V p-p}$

Bias $V_D = 2.5 \text{V} \therefore v_D \rightarrow 1.1 \text{V} \rightarrow 3.9 \text{V}$

$$v_D |_{\text{min}} = 1.1 \text{V} > V_G - V_t = -1.5 \text{V}$$

$$v_D |_{\text{max}} < V_{DD}$$

4.33

incl v_i $3 \times R_s$ for same output?

$$1 + g_m R_s = 3 \quad \therefore R_s = 2/g_m = 2 \text{K}$$

(20.15K in text incorrect)

Exercise 4.34

Exercise 4.35

EX 4.34/35 ~~Amplifiers~~ Amplifiers designed with circuit of Fig 4.42 (bias) analyzed in Fig E4.30. Note $g_m = 1 \text{ mA/volt}$.

4.34

CG Amplifier: $R_D = 15 \text{ k}\Omega$, $R_L = 15 \text{ k}\Omega$ ($R_{sig} = 50 \Omega$)

Find R_{in} , R_{out} , A_{vo} , A_v , G_v & overall voltage gain
for $R_{sig} \Rightarrow 1 \text{ k}\Omega, 10 \text{ k}\Omega, 100 \text{ k}\Omega$


4.35

CD (source follower) Amplifier: $r_o = 150 \text{ k}\Omega$ ($R_{sig} = 1 \text{ M}\Omega$) $R_L = 15 \text{ k}\Omega$

Find R_{in} , A_{vo} , A_v , R_{out} with and without r_o

Find G_v with r_o

EX 4.34

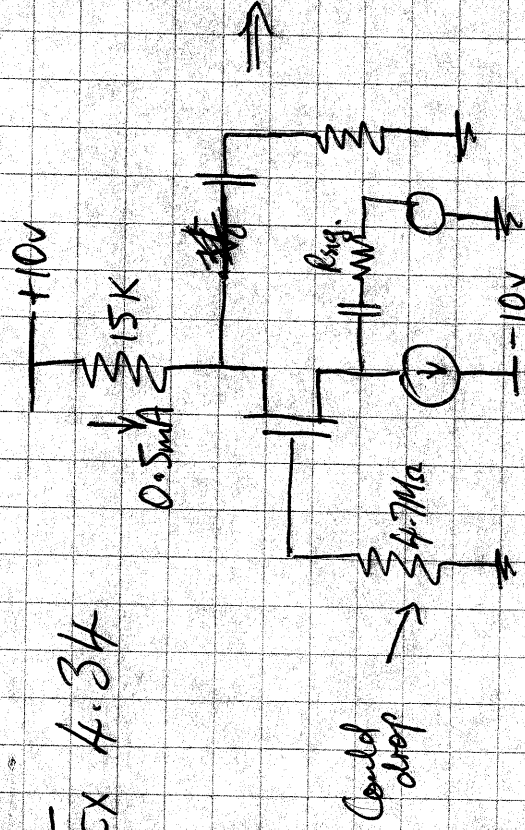

$$R_{in} = 1/g_m = 1K$$

$$R_{out} = R_D = 15K$$

$$A_{v0} = g_m R_D = 10^{-3} \times 15 \times 10^3 = 15$$


$$A_v = g_m R_D R_L = 10^{-3} \times 7.5 \times 10^3 = 7.5$$

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{1K}{1K + 0.5K} \cdot 7.5 = \frac{1}{1.5} \cdot 7.5 = 5$$


$$R_{sig} = 1K \quad G_v = \frac{1}{1+1} \cdot 7.5 = 3.75$$

$$10K \quad \frac{1}{11} \cdot 7.5 = 0.68$$

$$100K \quad \frac{1}{101} \cdot 7.5 = 0.07$$

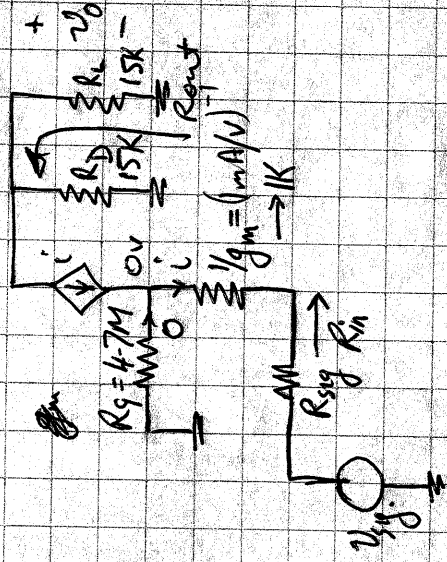

EX 4-35

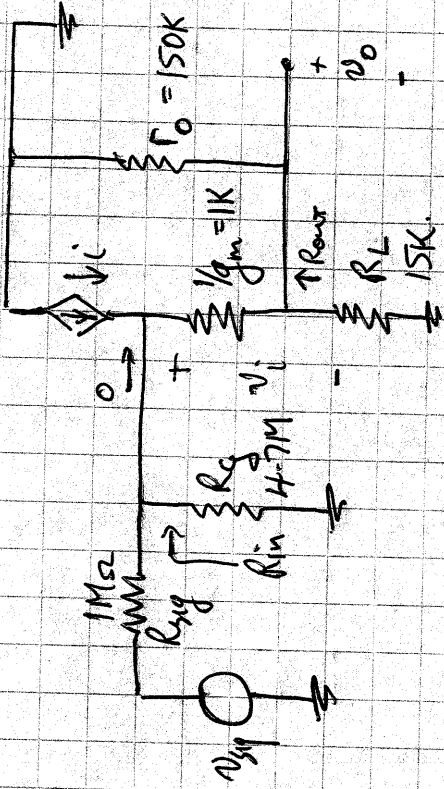

$$R_{in} = R_g = 4.7M\Omega \quad \text{indep of } r_o.$$


$$N_o R_L \rightarrow A_{v0} = \frac{r_o}{r_o + 1/g_m} = \frac{150}{151} = 0.993 \rightarrow 1 \text{ for } r_o \rightarrow \infty$$

$$A_v = \frac{R_L \parallel r_o}{R_L \parallel r_o + 1/g_m} = 0.932 \rightarrow 0.938 \text{ for } r_o \rightarrow \infty$$



$$R_{out} = 1/g_m \parallel r_o = \frac{1.150}{151} = 0.993k\Omega \rightarrow 1k \text{ for } r_o \rightarrow \infty$$

$$G_v = \frac{R_g}{R_g + R_{sig}} \cdot \frac{R_L \parallel r_o}{R_L \parallel r_o + 1/g_m} = \frac{4.7}{5.7} \cdot \frac{15 \parallel 150}{15 \parallel 150 + 1} = 0.768$$

Ex 4.34 uses Ex 4.30

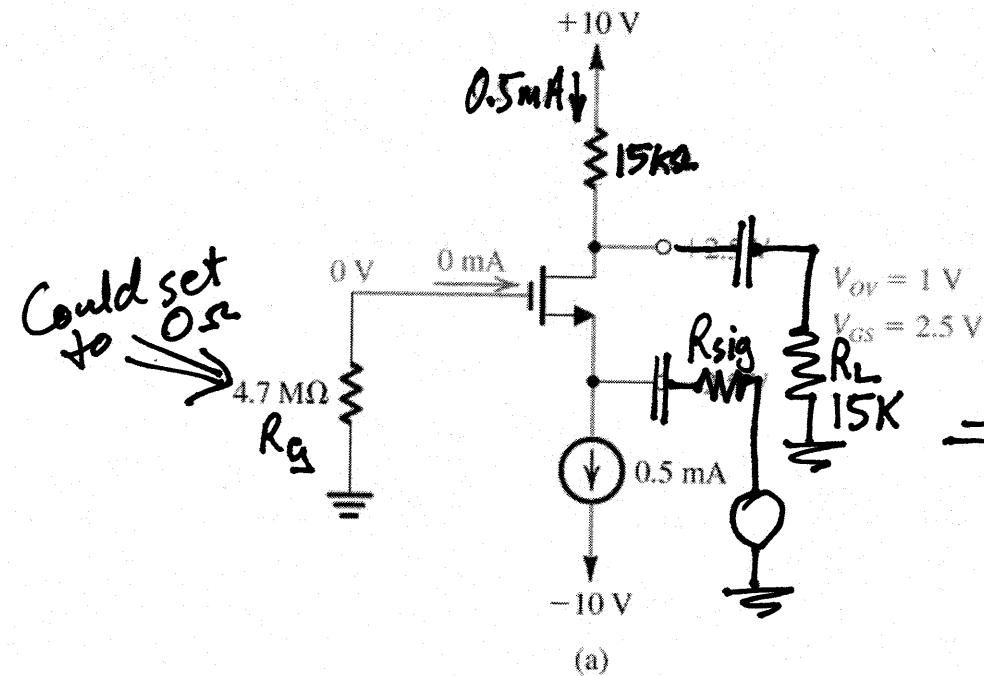


$R_{sig} = 50\Omega$

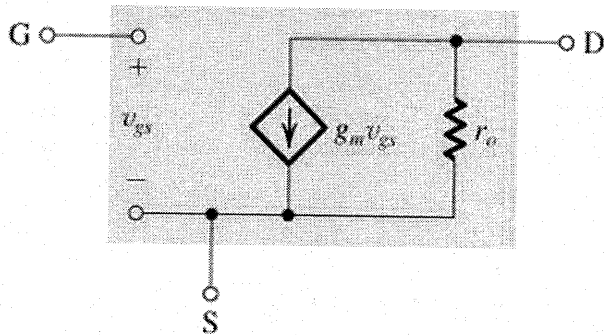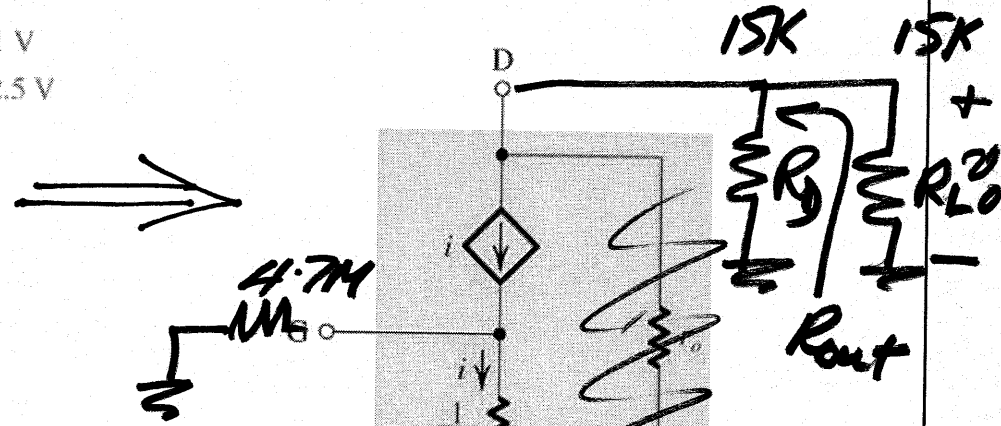

$g_m = 1\text{ mA/V}$

$r_o = 150\text{ k}\Omega$

$1/g_m = 1\text{ k}\Omega$

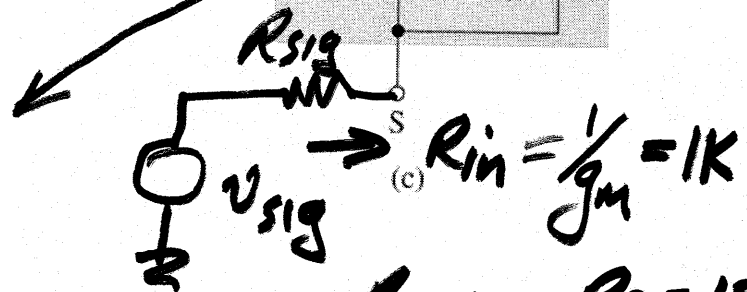

$R_{out} = R_D = 15\text{ k}$

$A_{v0} = g_m R_D = 10^{-3} \times 15 \times 10^3 = 15$

$A_v = g_m (R_D || R_L) = 7.5$

$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{1\text{ k}}{1\text{ k} + 0.05\text{ k}} \times 7.5 = 7.14$

$R_{sig} = 1\text{ k}$ $G_v = \frac{1}{1+1} \times 7.5 = 3.75$


Figure E4.30

10 k $\frac{1}{11} \times 7.5 = 0.68$

100 k


$\frac{1}{101} \times 7.5 = 0.07$

Ex 4.35 uses Ex. 4.30

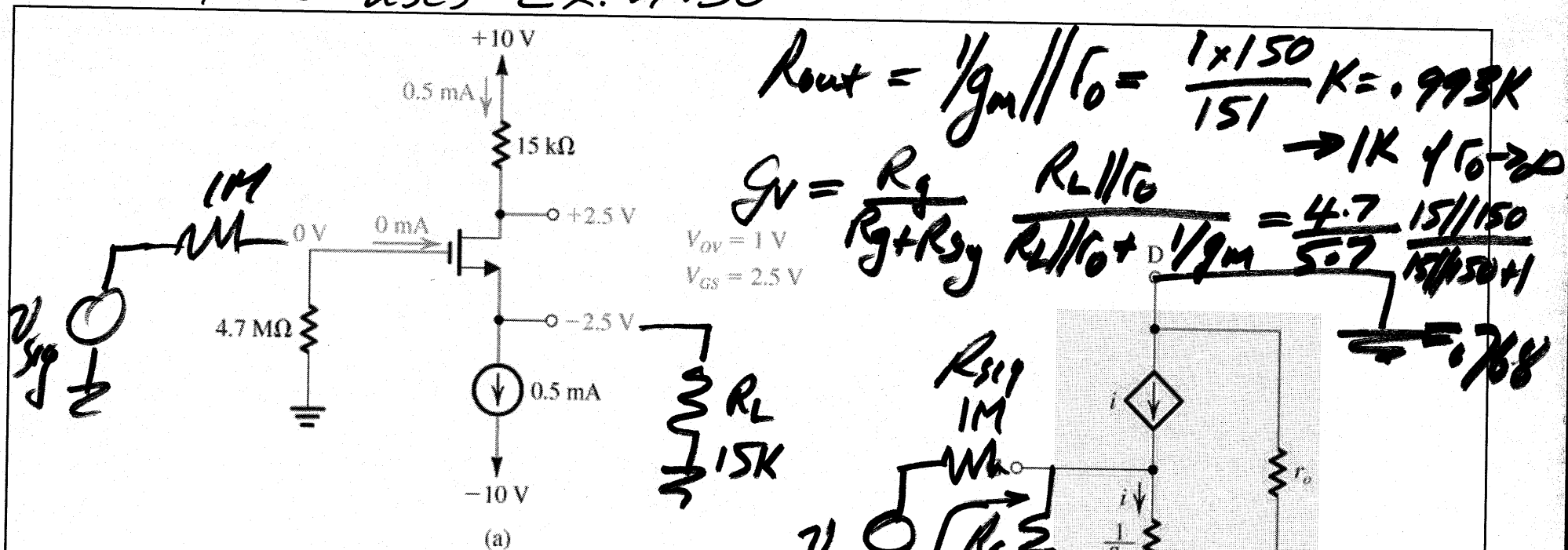


$$R_{out} = 1/g_m \parallel r_o = \frac{1 \times 150}{151} \text{ k} = 0.993 \text{ k} \rightarrow 1 \text{ k} \text{ if } r_o \rightarrow \infty$$
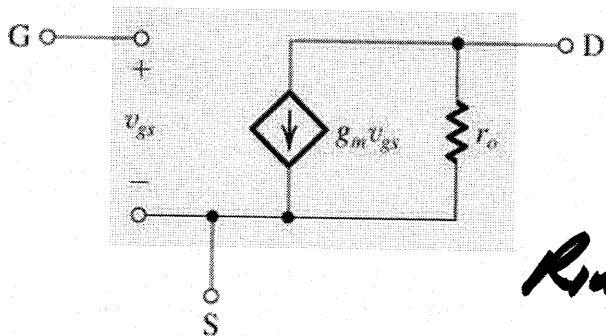
$$G_V = \frac{R_g}{R_g + R_{sig}} \frac{R_L \parallel r_o}{R_L \parallel r_o + 1/g_m} = \frac{4.7}{5.7} \frac{15 \parallel 150}{15 \parallel 150 + 1} = 0.768$$



$g_m = 1 \text{ mA/V}$
 $r_o = 150 \text{ k}\Omega$
 $1/g_m = 1 \text{ k}\Omega$

$R_{in} = 4.7 \text{ M}$


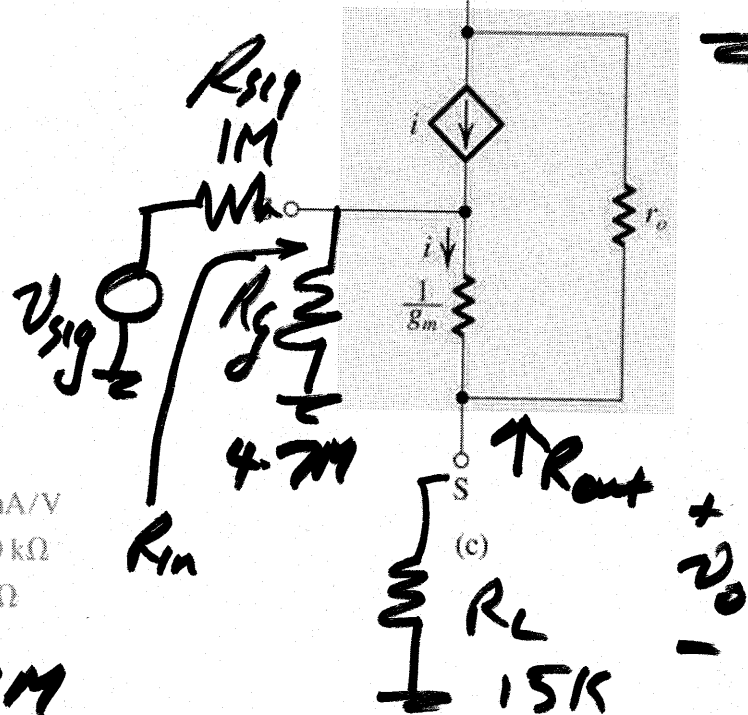


$$A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \frac{r_o}{r_o + 1/g_m} = \frac{150}{151} = 0.993 \rightarrow 1 \text{ if } r_o \rightarrow \infty$$

$$A_v = \frac{R_L \parallel r_o}{R_L \parallel r_o + 1/g_m} = \frac{15 \parallel 150}{15 \parallel 150 + 1} = 0.932 \rightarrow 0.938 \text{ if } r_o \rightarrow \infty$$

Figure E4.30

Ex 4.32 follows from Ex 4.30

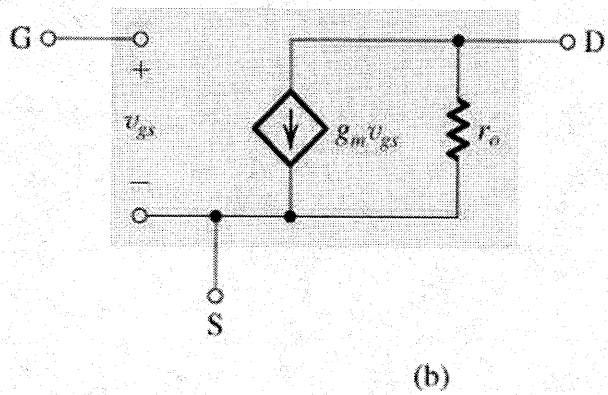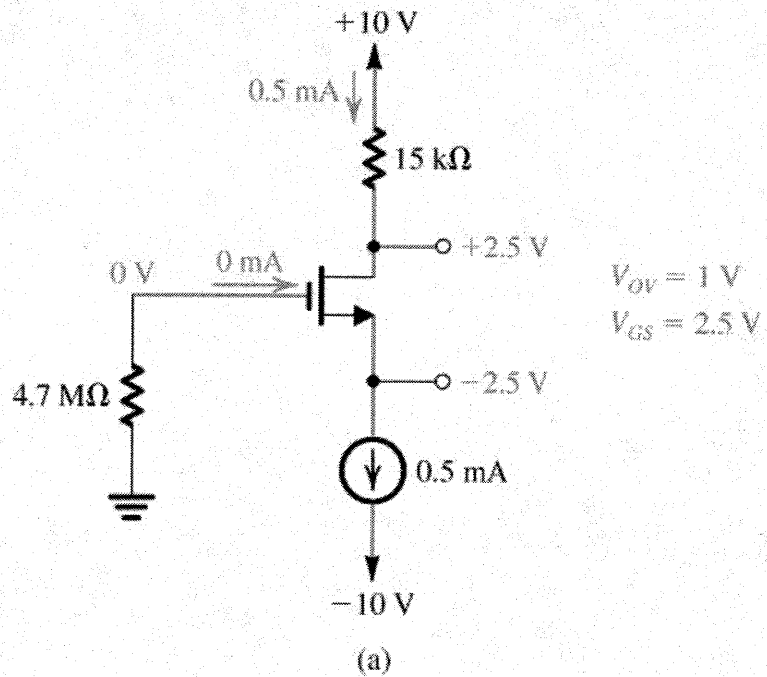

$$g_m = 1\text{ mA/V}$$

$$r_o = 150\text{ k}\Omega$$

$$1/g_m = 1\text{ k}\Omega$$


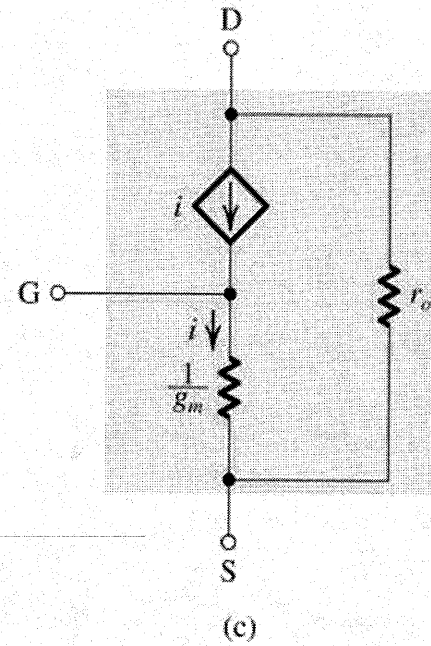


Figure E4.30

Ex H.23 ① Draw diagram — Fig 4.34

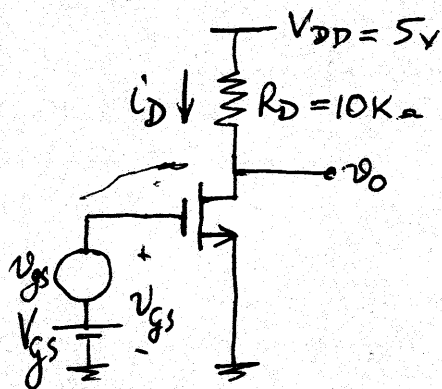

$V_{DD} = 5V$ $V_t = 1V$ $k_n' = 20 \mu A/V^2$ $W/L = 20$ $V_{GS} = 2V$ $\lambda = 0$

② $I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$ if sat'd
 $= \frac{1}{2} 20 \times 10^{-6} \times 20 (1)^2 = 0.2 \text{ mA}$

$V_D = V_{DD} - I_D R_D = 5 - 0.2 \times 10^{-3} \times 10 \times 10^3 = 3V$

③ $g_m = k_n' \frac{W}{L} (V_{GS} - V_t) = 20 \times 10^{-6} \times 20 \times 1 = 0.4 \text{ mA/V}$
OR $\frac{2I_D}{V_{GS} - V_t} \rightarrow \frac{0.4 \times 10^{-3}}{1}$

④ Voltage gain $\frac{v_o}{v_{gs}} = -g_m R_D = -0.4 \times 10^3 \times 10 \times 10^{-3} = -4$

⑤ $v_{gs} = 0.2 \sin \omega t$ small sig $\rightarrow v_d = -0.8 \sin \omega t$

Min $v_D \rightarrow V_D - |v_d| = 2.2V$
 Max $v_D \rightarrow \dots = 3.8V$ } Check $V_{GS} - V_t = 1V$
 \therefore Sat'd

⑥ Eqn 4.57 $i_D = \frac{1}{2} k_n' \frac{W}{L} \left[(V_{GS} - V_t)^2 + 2(V_{GS} - V_t)v_{gs} + v_{gs}^2 \right]$
 $= \dots \left[(V_{GS} - V_t)^2 + 2(V_{GS} - V_t)v_{gs} + v_{gs}^2 \right]$
 $= 200 \times 10^{-6} \left[1 + 0.4 \sin \omega t + 0.04 - \frac{0.04}{2} \cos 2\omega t \right]$
 $= 204 + 80 \sin \omega t - 4 \cos 2\omega t \mu A$

$\therefore I_D$ incr $\frac{4}{200} 100\% = 2\%$
 2nd harmonic $\frac{4}{200} 100\% = 5\%$

Ex 4.24 $\mu_n C_{ox} = 60 \mu\text{A}/\text{V}^2 \frac{W}{L} = 40$ $V_t = 1\text{V}$ $V_A = 15\text{V}$

$$g_m = \frac{2I_D}{V_{ov}} \quad \& \quad r_o = \frac{V_A}{I_D}$$

(a) $V_{GS} = 1.5\text{V} \quad \therefore I_D = \frac{1}{2} 60 \times 10^{-6} 40 (1.5 - 1)^2 = 300 \mu\text{A}$
 $\therefore g_m = \frac{2 \times 300 \times 10^{-6}}{0.5} = 1.2 \text{ mA/V}$

$$r_o = 15 / 300 \times 10^{-6} = 50 \text{ K}\Omega$$

(b) $I_D = 0.5 \text{ mA}$ $g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 60 \times 10^{-6} \times 40 \times 0.5 \times 10^{-3}}$
 $= \sqrt{2.4} \text{ mA/V} = 1.55 \text{ mA/V}$
 $r_o = V_A / I_D = 15\text{V} / 0.5 \times 10^{-3} = 30 \text{ K}\Omega.$

Ex 4.25 $g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.1 \text{ mA}}{V_{ov}} = 1 \text{ mA/V} \quad \therefore V_{ov} = \frac{0.2 \text{ mA}}{1 \text{ mA/V}} = 0.2 \text{ V}$

$$\therefore I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{ov})^2 = 0.1 \text{ mA} = \frac{1}{2} 50 \mu\text{A}/\text{V}^2 \frac{W}{L} (0.2)^2$$

$$\therefore W/L = \frac{10^{-4} \times 2}{50 \times 10^{-6} \times 4 \times 10^{-2}} = \frac{10^4}{100} = 100$$

• 4.26 $\mu_p = 0.4 \mu_n$ Equal $g_m = \frac{2I_D}{V_{ov}}$ ← same
 $\mu_p W_p = \mu_n W_n$ $0.4 W_p = W_n$ $W_p = 2.5 W_n$

• 4.27 $\chi = \frac{g_{mb}}{g_m} = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} = \frac{0.5}{2\sqrt{0.6 + 4}} = 0.1166$

• 4.28 PMOS $V_t = -1V$ $k_p' = 60 \mu A/V^2$ $w/L = 16/0.8 \mu m$ $V_{gs} = -1.6V$
 $I_D = \frac{1}{2} 60 \mu A 20 (0.6)^2 = 624 \mu A$ $\therefore g_m = \frac{2I_D}{V_{ov}} = \frac{432 \mu A}{0.6} = 0.720 mA/V$

$V_A \propto L \rightarrow r_o = \frac{V_A \times L}{I_D} = \frac{(V_A/L)L}{I_D} = \frac{25 \times (0.8)}{216 \times 10^{-6}} = 92.6 K\Omega$

• 4.29 $g_m r_o = \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} = 2 \frac{V_A}{V_{ov}} = A_0$ intrinsic gain
 $L = 0.8 \mu m \therefore V_A = 0.8 \times 12.5V = 10V$ $\therefore g_m r_o = 2 \frac{10}{0.2} = 100$

Ex H. 30 Find V_{ov} , V_{gs} , V_g , V_s , V_D & g_m, r_o for $V_A = 75V$; max V_D swing for Q to remain sat'd

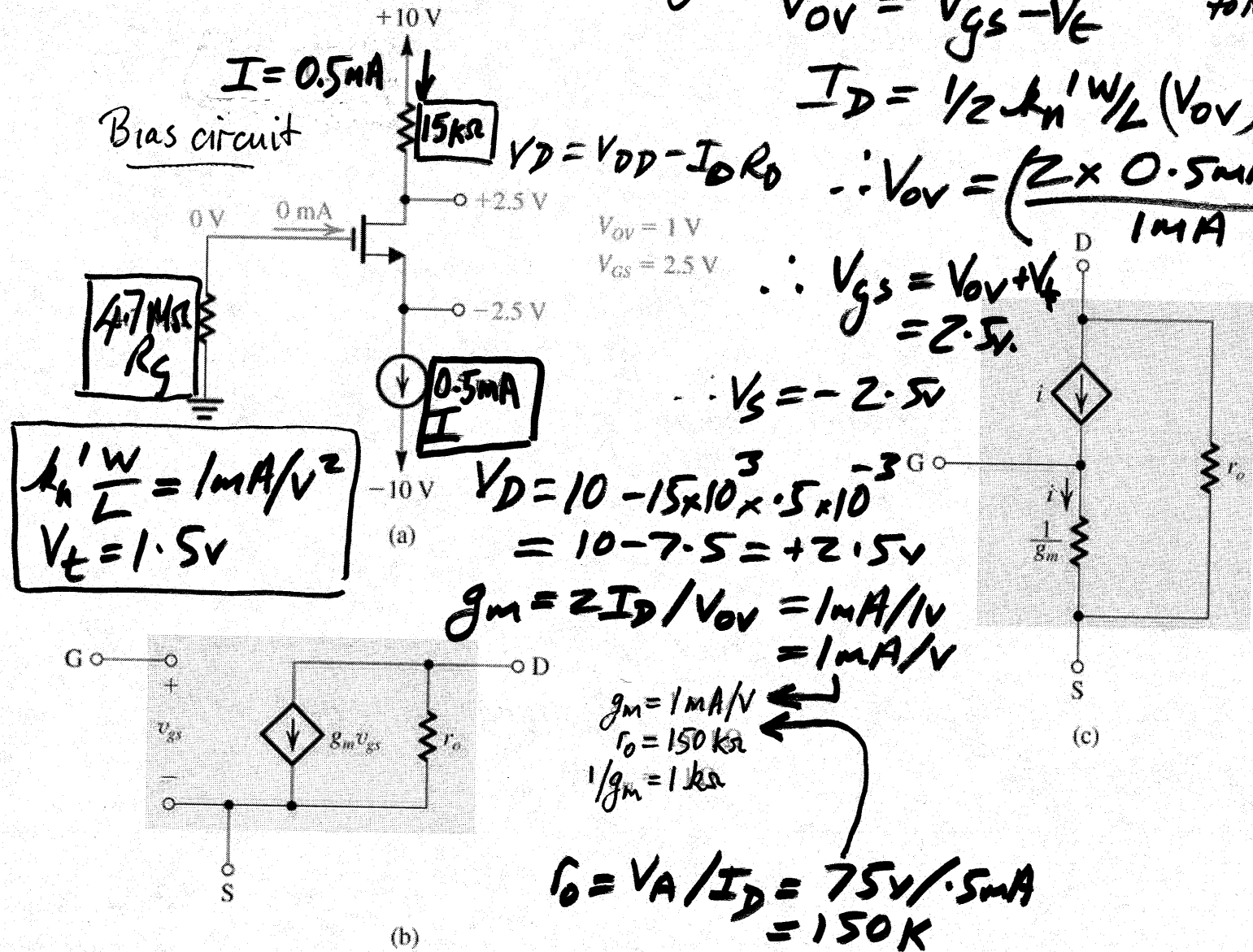


Figure E4.30 Max swing: Onset of saturation when $V_{gs} - V_t \leq V_{ds}$
 ie. $V_g - V_s - V_t \leq V_D - V_s \Rightarrow V_{gd} \leq V_t$ ie. $0 - V_D \leq 1.5V$
 when $V_D \geq -1.5V$ ie. max swing $+2.5V \rightarrow -1.5V = 4V$ peak

Ex. 4.30



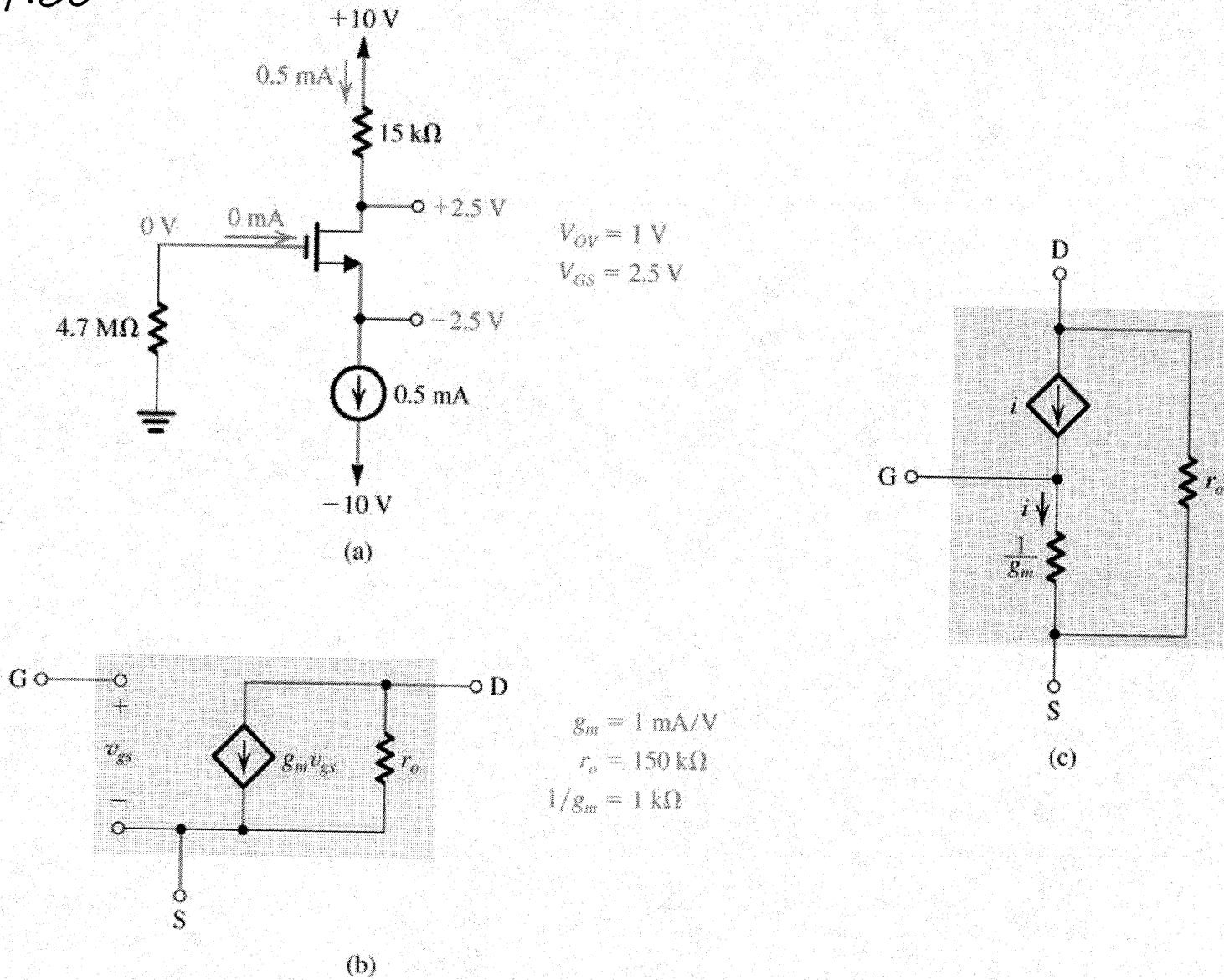
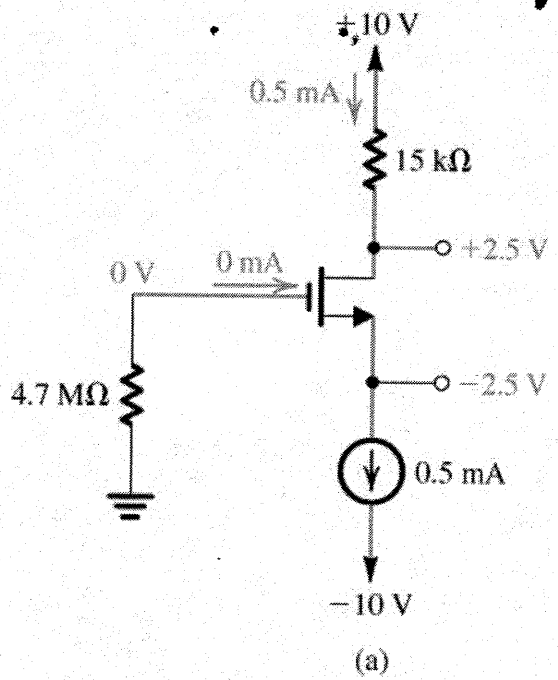


Figure E4.30

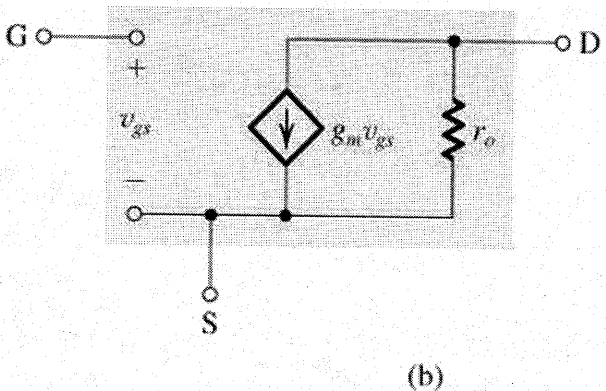

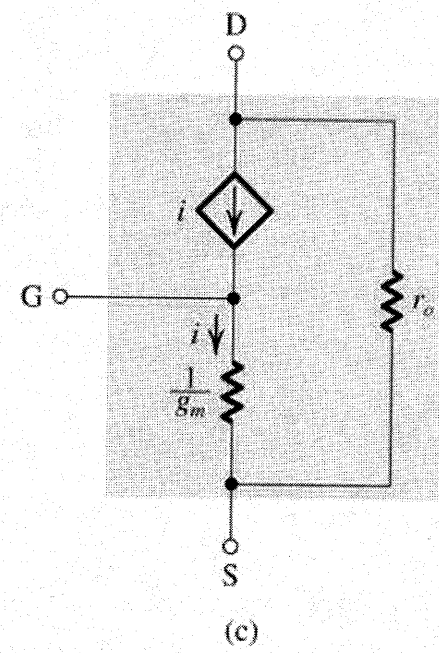$V_{OV} = 1\text{ V}$
 $V_{GS} = 2.5\text{ V}$



$g_m = 1\text{ mA/V}$
 $r_o = 150\text{ k}\Omega$
 $1/g_m = 1\text{ k}\Omega$

Figure E4.30