

# **ECE321 ELECTRONICS I**

## **FALL 2006**

**PROFESSOR JAMES E. MORRIS**

**Lecture 11**  
**31<sup>st</sup> October, 2006**


## CHAPTER 5

# Bipolar Junction Transistors (BJTs)

5.1 Device Structure & Physics

5.2 I – V Characteristics ← Convert 5.1 info  
to circuit applications


# NPN BJT

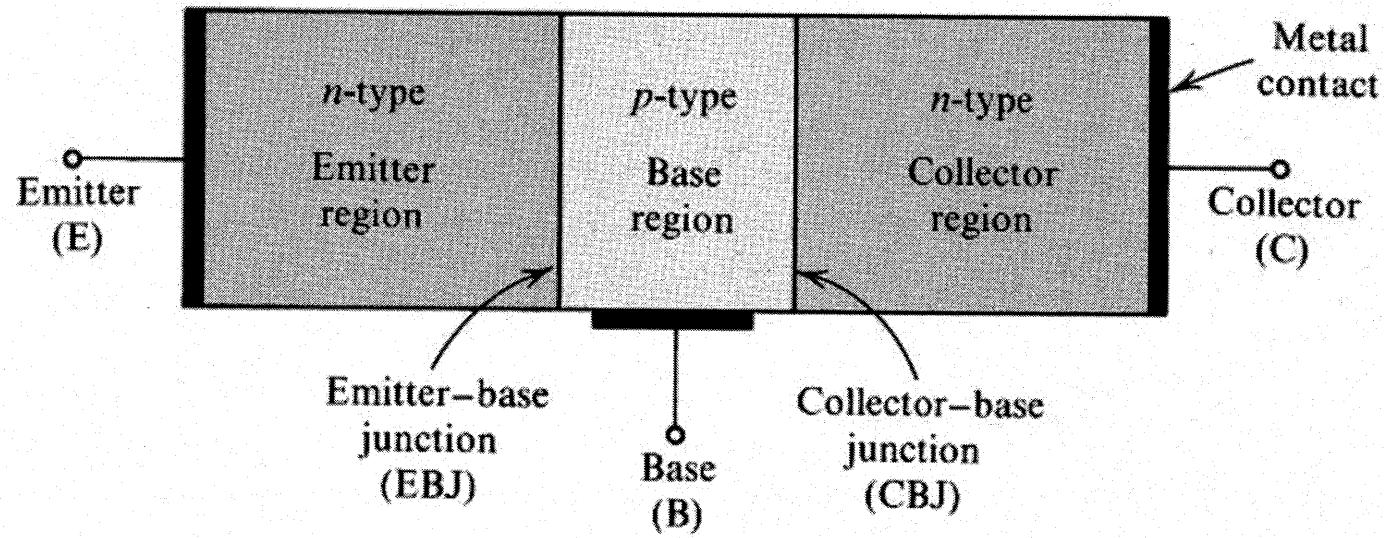

Emitter      Base      Collector

Figure 5.1 A simplified structure of the *npn* transistor.

# *PNP BJT*

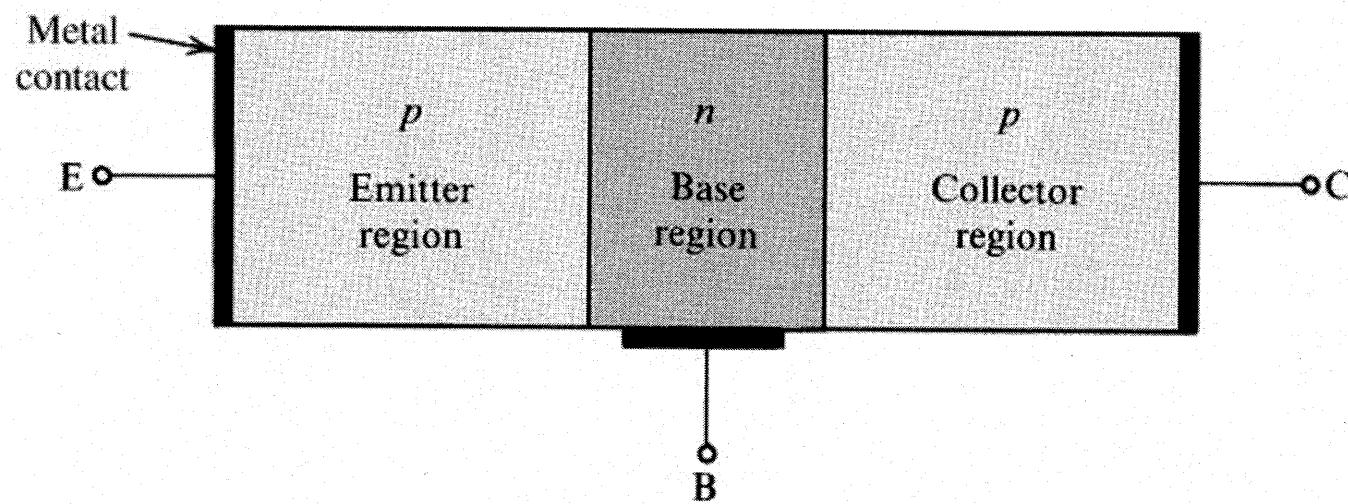

**Figure 5.2** A simplified structure of the *pnp* transistor.


# Table 5.1 BJT Operation Modes

Mode	Emitter-Base Junction Bias	Collector-Base Junction Bias
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Reverse Active	Reverse	Forward
Saturation	Forward	Forward

Linear amplification — Active

Digital/switching — Cutoff & Saturation
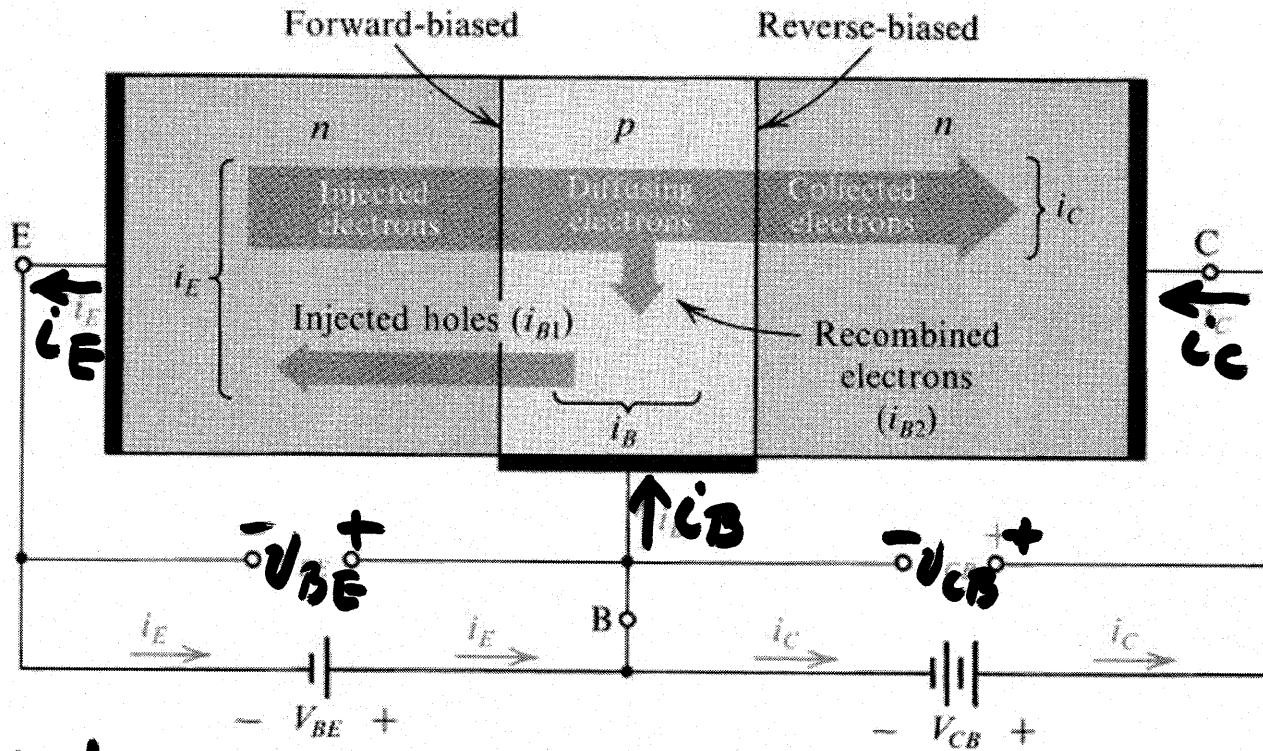
# NPN Active Mode : BE Fwd Bias CB Rev Bias



BE diode  $\sim 0.7\text{v}$


Electrons are minority carriers in base

Figure 5.3 Current flow in an *npn* transistor biased to operate in the active mode. (Reverse current components due to drift of thermally generated minority carriers are not shown.)

Emitter doping >> Base doping  
 $N_{DE} \gg N_{AB}$   
 $\therefore I_E \approx I_{nE}$

Key point: Base very thin, so electrons from emitter reach C-B junction before many lost to recombination.  
 But electrons accelerated across C-B junction into collector

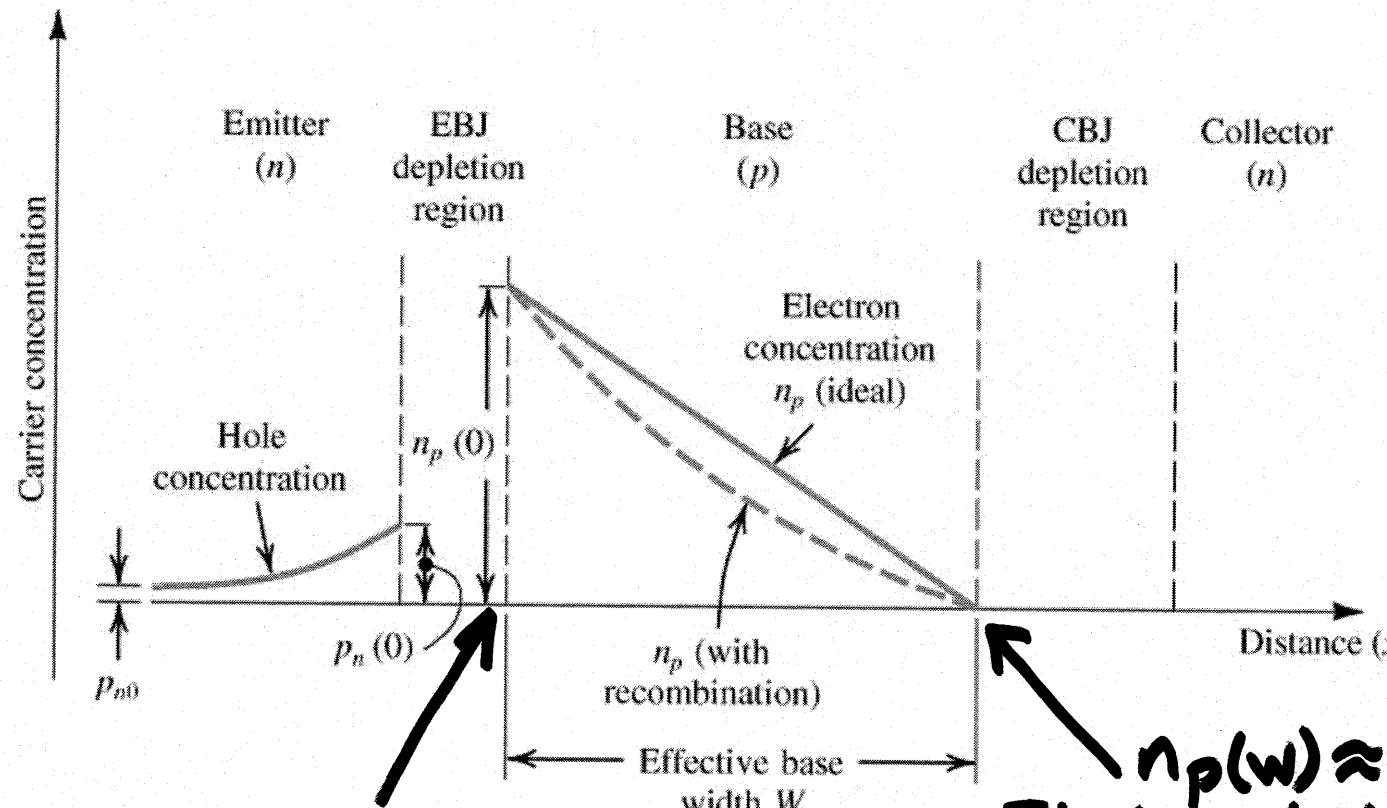$E-B$  junction as a diode (forward bias)  
Then consider recombination in base



$$n_p(0) = n_{p0} \exp V_{BE}/V_T$$

$n_p(0) \approx 0$   
Electrons here are  
accelerated across the  
 $C-B$  junction

Figure 5.4 Profiles of minority-carrier concentrations in the base and in the emitter of an  $npn$  transistor operating in the active mode:  $V_{BE} > 0$  and  $V_{CB} \geq 0$ .

$$(i_n)_{base} = A_E q D_n \frac{dn_p(x)}{dx} = A_E q D_n \left(-\frac{n_p(0)}{W}\right)$$

$$i_C = I_s \exp(V_{BE}/V_T) \text{ where } I_s = A_E q D_n n_i^2 / N_A W$$

and note  $i_C = A_E q D_n \frac{n_i^2}{N_A W} \exp \frac{V_{BE}}{V_T}$

is (ideally) independent of  $V_{CB}$

Base Current:  $i_B = i_{B1} + i_{B2}$

where  $i_{B1}$  = hole current  $I_p$  base  $\rightarrow$  emitter  
 $= A_E q \frac{D_p n_i^2}{L_p N_D} \exp \frac{V_{BE}}{V_T}$


and  $i_{B2} \rightarrow$  hole current to replace base holes lost to recombination with electrons from emitter

Minority carrier lifetime in base =  $\tau_b$

i.e.  $Q_n$  electron charge in base recombines with holes in  $\tau_b$

$$\therefore i_{B2} = \frac{Q_n}{\tau_b} = A_E q \cdot \frac{1}{2} n_p(0) W / \tau_b$$
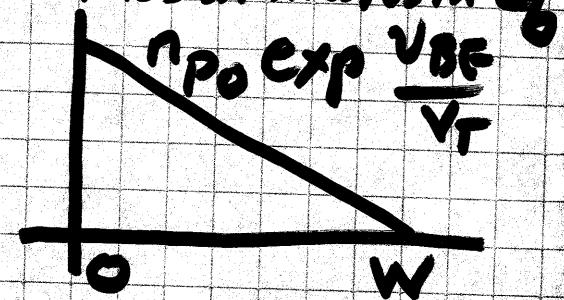
$$= \frac{A_E q W n_i^2}{2 N_A \tau_b} \exp \frac{V_{BE}}{V_T}$$



$$\therefore \dot{I}_B = \dot{I}_{B1} + \dot{I}_{B2} = I_s \left( \frac{D_p}{D_n} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_n \tau_b} \right) \exp \frac{V_{BE}}{V_T}$$

where  $I_s = A_E q D_n n_i^2 / W N_A$

Rewrite  $\dot{I}_B = \left( \frac{D_p}{D_n} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_n \tau_b} \right) \dot{I}_C = \dot{I}_C / \beta$

$$\therefore CE \text{ current gain } \beta = ( )^{-1}$$

$\beta$  high  $\rightarrow W \ll L_p, N_A \ll N_D$

Common emitter (CE) :  $\dot{I}_B$  input,  $\dot{I}_C$  output

$$\dot{I}_E = \dot{I}_C + \dot{I}_B = \dot{I}_C \left( 1 + \frac{1}{\beta} \right) = \frac{1+\beta}{\beta} \dot{I}_C$$


OR  $\dot{I}_C = \frac{\beta}{1+\beta} \dot{I}_E = \alpha \dot{I}_E$  where  $\alpha \approx 1$

Common base (CB) :  $\dot{I}_E$  input,  $\dot{I}_C$  output

$$\alpha = \frac{\beta}{1+\beta} \quad \& \quad \beta = \frac{\alpha}{1-\alpha}$$

$\alpha \rightarrow \alpha_F$  (Forward) also  $\alpha_R$  (Reverse)  
 $\beta \rightarrow \beta_F$  (active) also  $\beta_R$  (active)
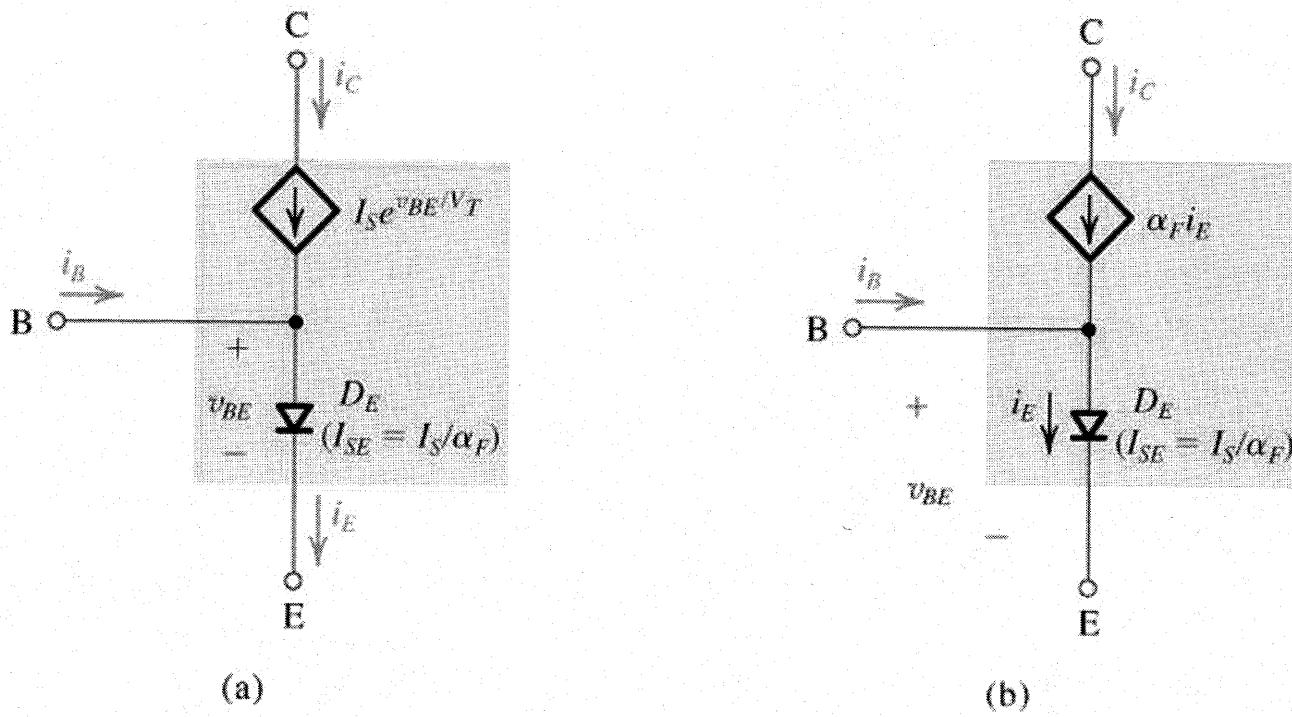
# Large Signal BJT Models: Forward Active Mode



$i_C$  voltage controlled  
(i.e. by  $v_{BE}$ )

$i_C$  current controlled  
(i.e. by  $i_E$ )

Figure 5.5 Large-signal equivalent-circuit models of the *npn* BJT operating in the forward active mode.

# Exercises

- 5.1
  - NPN  $v_{BE}=0.7V$  at  $i_C=1mA$ .  
Find  $v_{BE}$  at  $i_C=0.1mA, 10mA$
- 5.2
  - Find  $\alpha$  range for  $\beta=50$  to  $150$ .
- 5.3
  - NPN  $I_B=14.46\mu A$  for  $I_E=1.460mA$ , and  $V_{BE}=0.7V$ .  
Find  $\alpha$ ,  $\beta$ , and  $I_S$
- 5.4
  - $I_C=10mA$ . Find  $\beta$  and  $I_B$  for  $\alpha = 0.99, 0.98$ .

icculus:

## BJT Structure

Collector junction surrounds emitter  
 $\rightarrow \alpha_F \sim 1$

Not symmetrical  $\therefore \alpha_F, \beta_F \neq \alpha_R, \beta_R \ll \alpha_F, \beta_F$


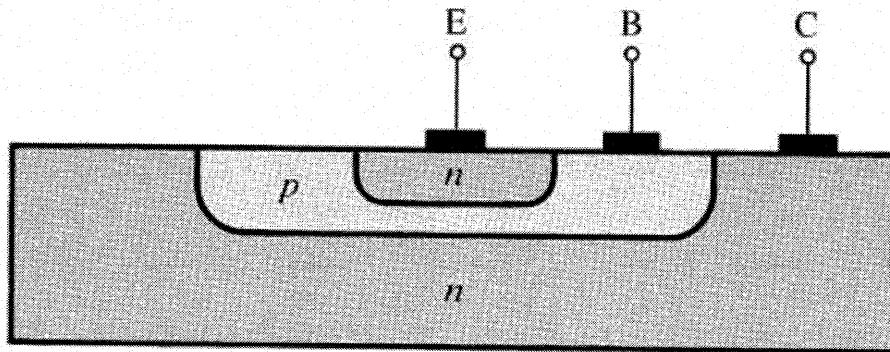


Figure 5.6 Cross-section of an *n*p*n* BJT.

Reverse Active Model : CB forward bias  
 EB reverse bias

As for Active Mode, except  $\alpha_F \rightarrow \alpha_R$

$BE \leftrightarrow CB$

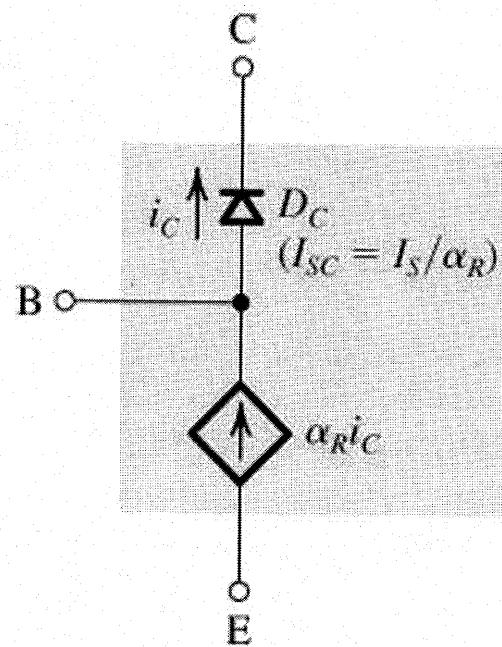

$$\alpha_F I_{SE} = I_S = \alpha_R I_{SC}$$

$$\alpha_R \ll \alpha_F$$

$$I_{SC} \gg I_{SE}$$

Figure 5.7 Model for the  $npn$  transistor when operated in the Reverse active mode (i.e. with the CBJ forward biased and the EBJ reverse biased).

OR: for same currents  $I$ ,  $(V_{CB})_{fwd} \ll (V_{EB})_{fwd}$   
 bias bias

# Ebers-Moll Model

Combines  
Forward Active  
& Reverse Active  
models

Covers all possible  
modes.

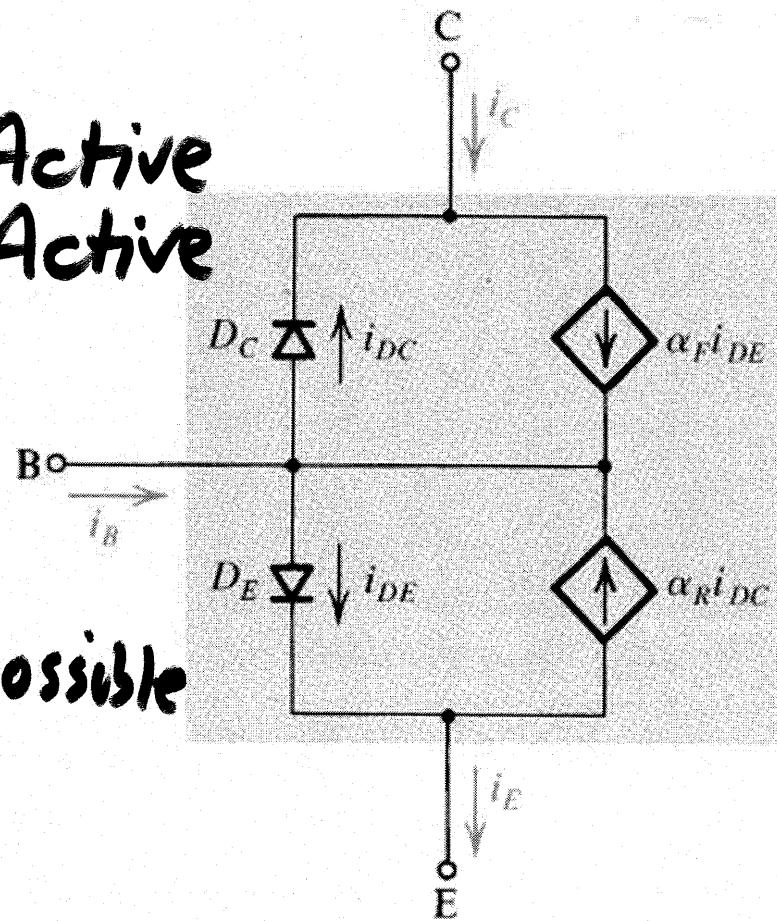


Figure 5.8 The Ebers-Moll (EM) model of the *npn* transistor.

See text p388 — from the Ebers-Moll circuit model:

$$\left. \begin{aligned} i_E &= i_{DE} - \alpha_R i_{DC} \\ i_C &= -i_{DC} + \alpha_F i_{DE} \\ i_B &= (1 - \alpha_F) i_{DE} + (1 - \alpha_R) i_{DC} \end{aligned} \right\} \text{where}$$

$$i_{DE} = I_{SE} \left( \exp \frac{V_{BE}}{V_T} - 1 \right)$$

$$i_{DC} = I_{SC} \left( \exp \frac{V_{BC}}{V_T} - 1 \right)$$

Substitute ↓ &  $I_{SE} = I_S / \alpha_F$   
for  $i_{DE}$ ,  $i_{DC}$        $I_{SC} = I_S / \alpha_R$

Gives :  $i_E = \left( \frac{I_S}{\alpha_F} \right) \left( \exp \frac{V_{BE}}{V_T} - 1 \right) - I_S \left( \exp \frac{V_{BC}}{V_T} - 1 \right)$

$$i_C = I_S \left( \exp \frac{V_{BC}}{V_T} - 1 \right) - \left( \frac{I_S}{\alpha_R} \right) \left( \exp \frac{V_{BC}}{V_T} - 1 \right)$$

$$\& \quad i_B = \left( \frac{I_S}{\beta_F} \right) \left( \exp \frac{V_{BE}}{V_T} - 1 \right) + \left( \frac{I_S}{\beta_R} \right) \left( \exp \frac{V_{BC}}{V_T} - 1 \right)$$

In active mode, for  $V_{BE} \sim 0.6$  to  $0.8$  v &  $V_{BC} < 0$

$$\exp \frac{V_{BC}}{V_T} \approx 0, \text{ so}$$

$$i_E \approx \left( I_S / \alpha_F \right) \exp \frac{V_{BE}}{V_T} + I_S (1 - 1/\alpha_F)$$


$$i_C \approx I_S \exp \frac{V_{BC}}{V_T} + I_S (1/\alpha_R - 1)$$

$$i_B \approx \left( I_S / \beta_F \right) \exp \frac{V_{BE}}{V_T} - I_S (1/\beta_F + 1/\beta_R)$$

# Exercise

- 5.6
  - BJT  $\alpha_F=0.99$ ,  $\alpha_R=0.02$ ,  $I_S=10^{-15}A$ :
  - Calculate second term on RHS of equations 5.31, 5.32, 5.33, and verify they can be neglected.
  - Calculate  $i_E$ ,  $i_C$ , and  $i_B$  for  $v_{BE}=0.7V$ .


# Start considering saturation mode:

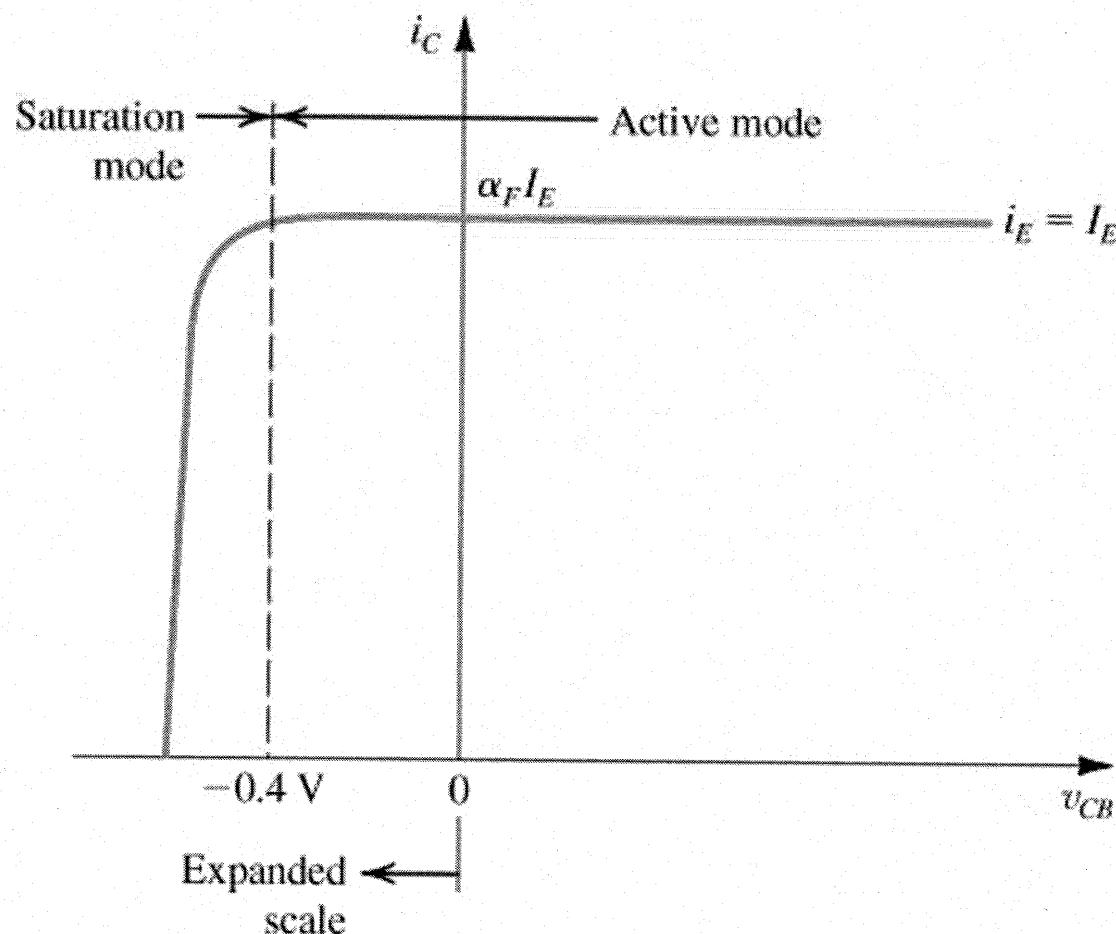

C-B junction not effectively forward biased  
until  $v_{CB} \leq -0.5\text{V}$

Figure 5.9 The  $i_C-v_{CB}$  characteristic of an *npn* transistor fed with a constant emitter current  $I_E$ . The transistor enters the saturation mode of operation for  $v_{CB} < -0.4$  V, and the collector current diminishes.

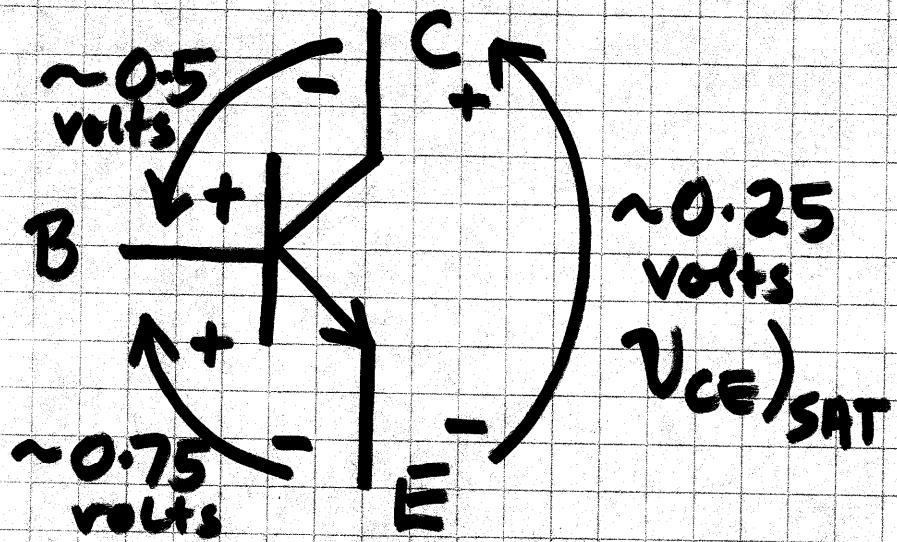Hence forward active mode until saturation  
at  $v_{CB} \leq -0.4\text{V}$




Typical saturation

$$i_C = I_S \exp \frac{V_{BE}}{V_T} - \frac{I_S}{\alpha_R} \exp \frac{V_{BC}}{V_T}$$

Forward bias EB      Forward bias CB  
 $\rightarrow 0$  as  $V_{BC} \rightarrow -\infty \sim -0.5 \text{ volts}$

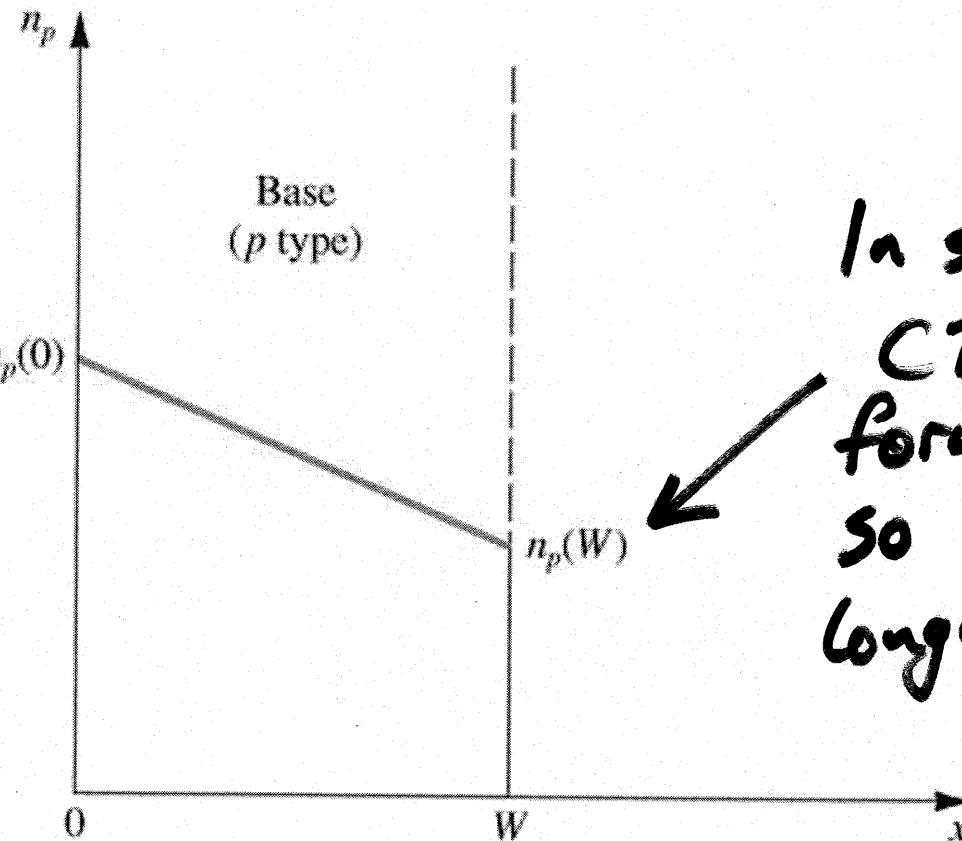$E \bar{B}$   
forward  
biased  
as for  
active



In saturation  
 $C \bar{B}$  now  
forward biased,  
so  $n_p(W)$  no  
longer zero

Figure 5.10 Concentration profile of the minority carriers (electrons) in the base of an  $npn$  transistor operating in the saturation mode.

# PNP BJT

All similar, but  
 $e^- \leftrightarrow$  holes  
 polarities, etc  
 reversed

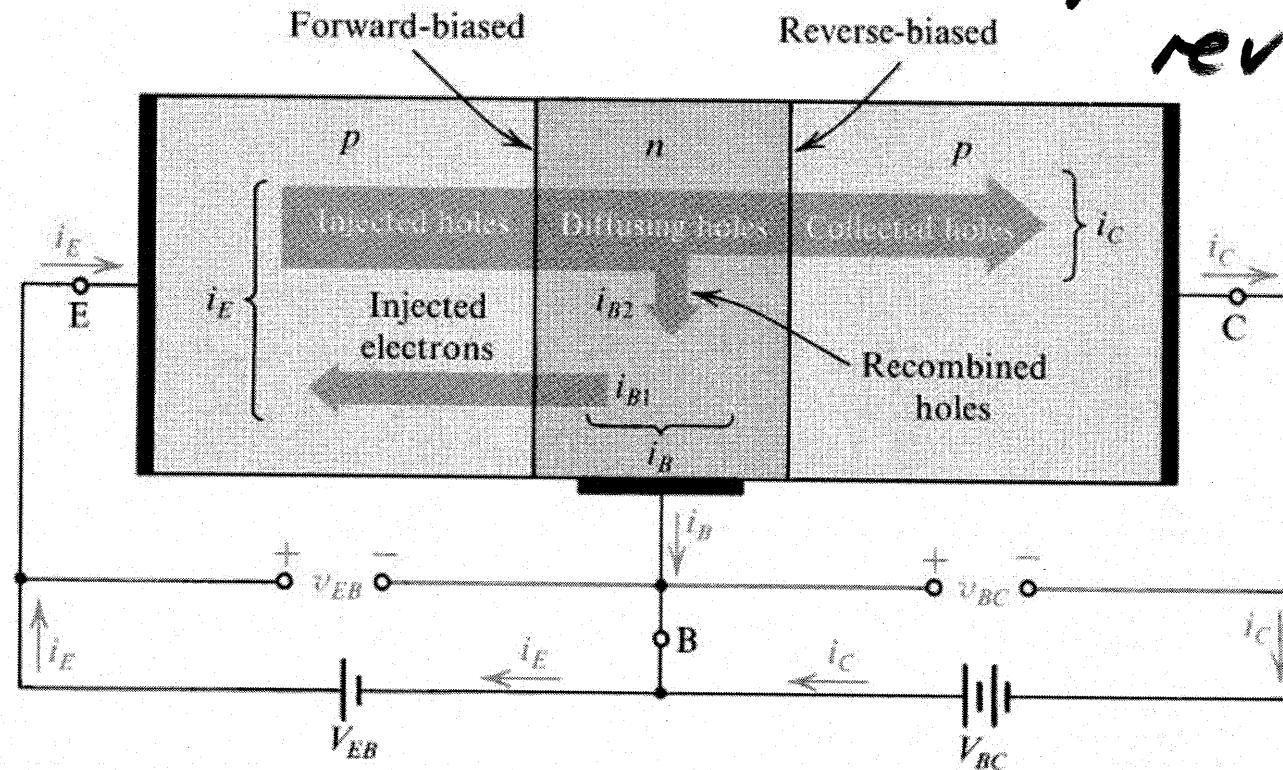


Figure 5.11 Current flow in a *pnp* transistor biased to operate in the active mode.

# PNP Large Signal Model

Forward Active  
Mode


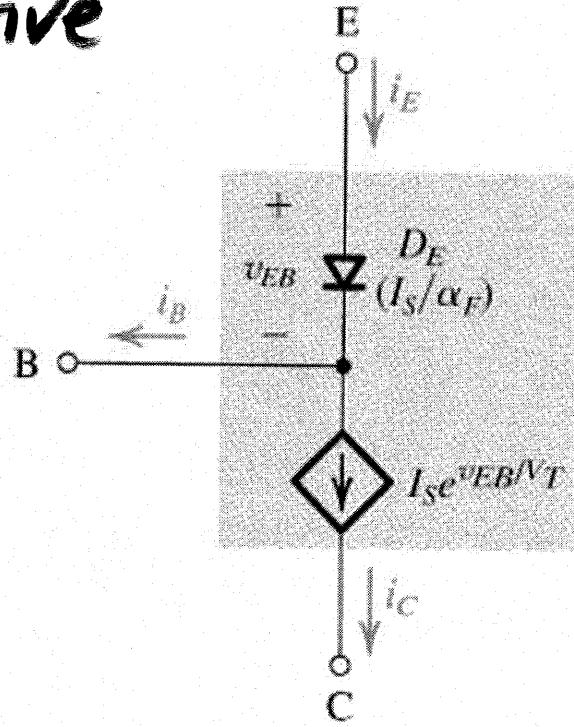


Figure 5.12 Large-signal model for the *pnp* transistor operating in the active mode.

*NPN      PNP*

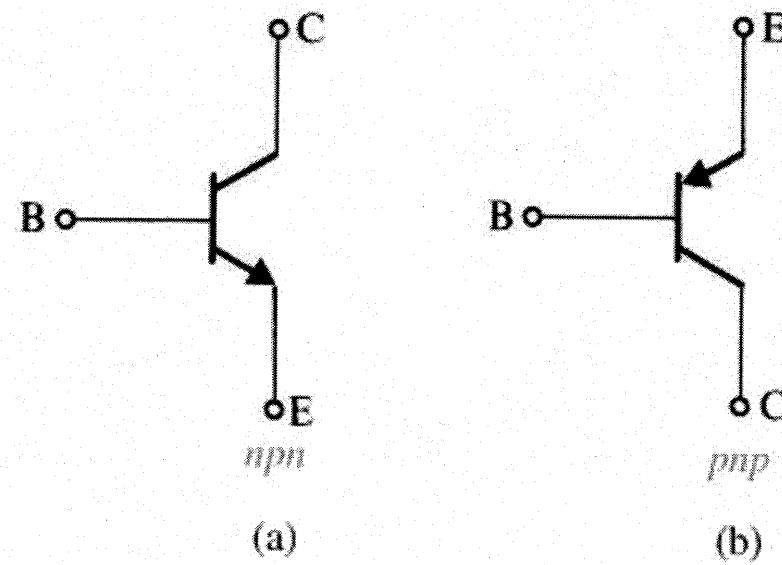

*Emitter arrow*

Figure 5.13 Circuit symbols for BJTs.

# Forward Active Bias Systems



See also Table 5-2:

$$i_c = I_s \exp \frac{V_{BE}}{V_T}$$

$$i_B = i_c / \beta, i_E = i_c / \alpha$$

$$\text{so } i_c = \alpha i_E = \beta i_B, i_E = (1 + \beta) i_B, i_B = (1 - \alpha) i_E$$

$$= \frac{i_E}{1 + \beta}$$

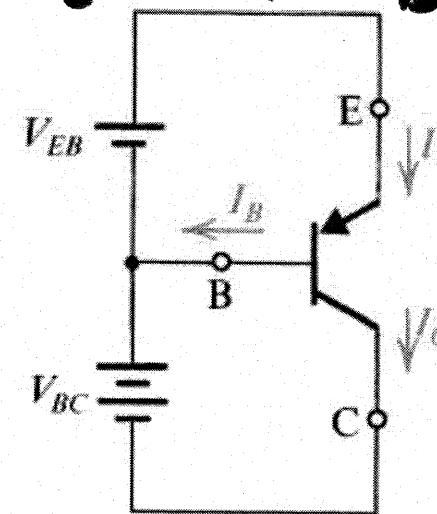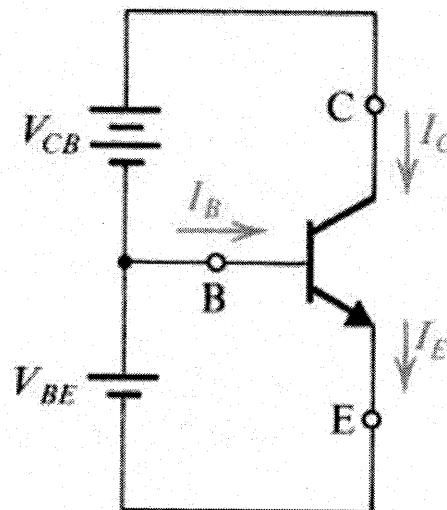

Note also:  $\alpha = 1$

Reverse leakage:  $I_c = \beta I_B + (1 + \beta) I_{cbo}$

where  $I_{cbo} = I_s + \text{leakage currents}$

Figure 5.14 Voltage polarities and current flow in transistors biased in the active mode.

Temperature dependent, doubles ~ every 5°C rise

# Exercises


- 5.10
- 5.11

## $i_C - v_{BE}$ characteristic

Note  $i_E - v_{BE}$  is forward bias diode

$$i_C = I_s \exp^{v_{BE}/V_T}$$
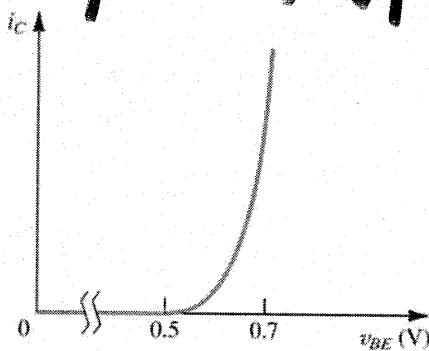
$$i_E = \frac{I_s}{2} \exp^{v_{BE}/V_T}$$



$$i_B = \frac{I_s}{\beta} \exp^{v_{BE}/V_T}$$

All follow same basic shape with current scale factor

Figure 5.16 The  $i_C - v_{BE}$  characteristic for an *npn* transistor.

# B-E Diode temperature dependence


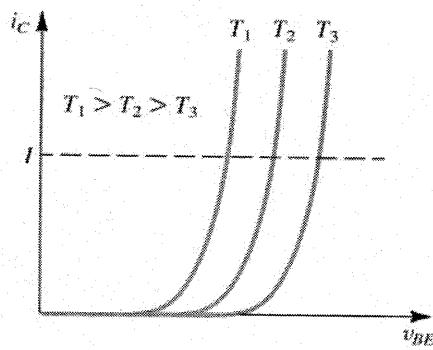


Figure 5.17 Effect of temperature on the  $i_C$ - $v_{BE}$  characteristic. At a constant emitter current (broken line),  $v_{BE}$  changes by  $-2 \text{ mV}^{\circ}\text{C}$ .


# Common Base Characteristics

$|i_C \text{ vs } v_{CB}|$

const  $I_E$

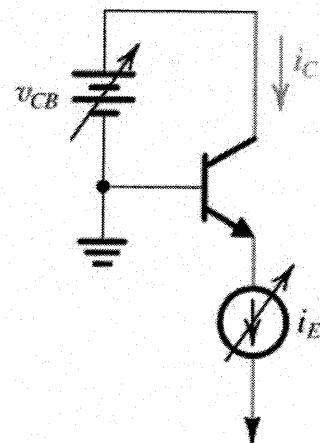

(a)

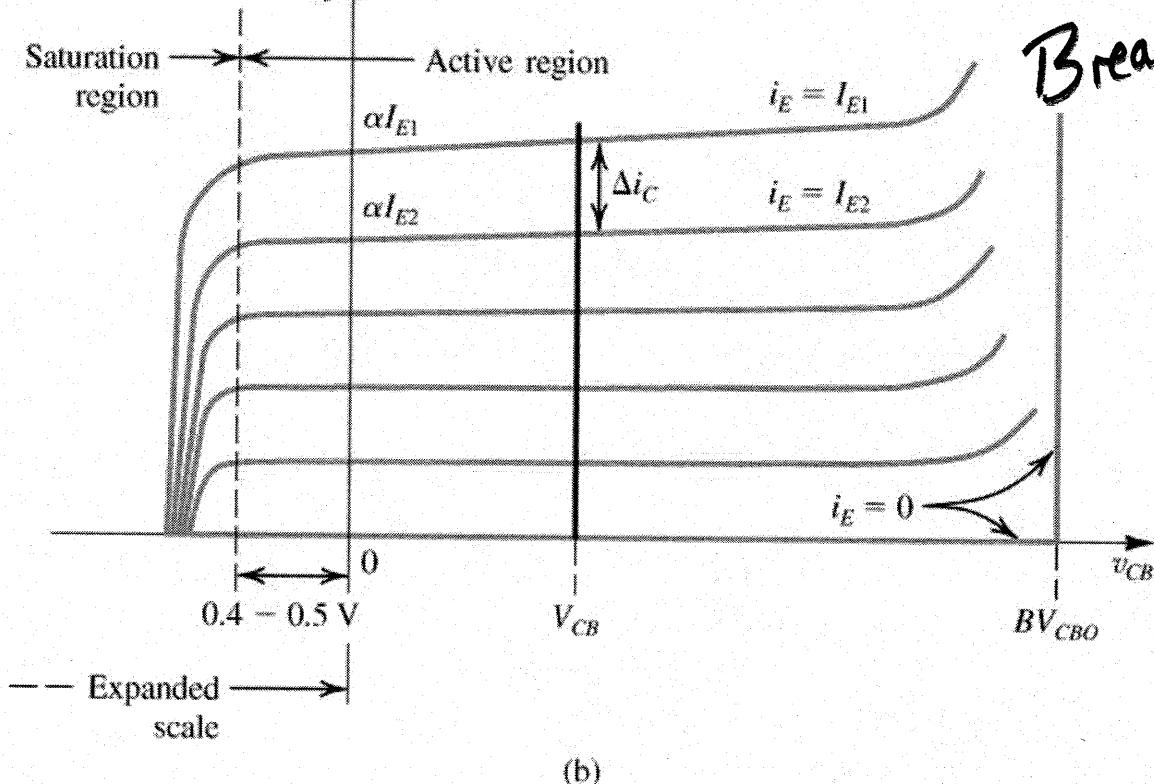

(b)

$V_B$  constant  $\rightarrow$  CB


Note  $i_C$  not constant  
for constant  $i_E$

Figure 5.18 The  $i_C-v_{CB}$  characteristics of an *npn* transistor.

Small signal  $\alpha = \frac{\Delta i_C}{\Delta i_E} \approx \text{large signal } \alpha$
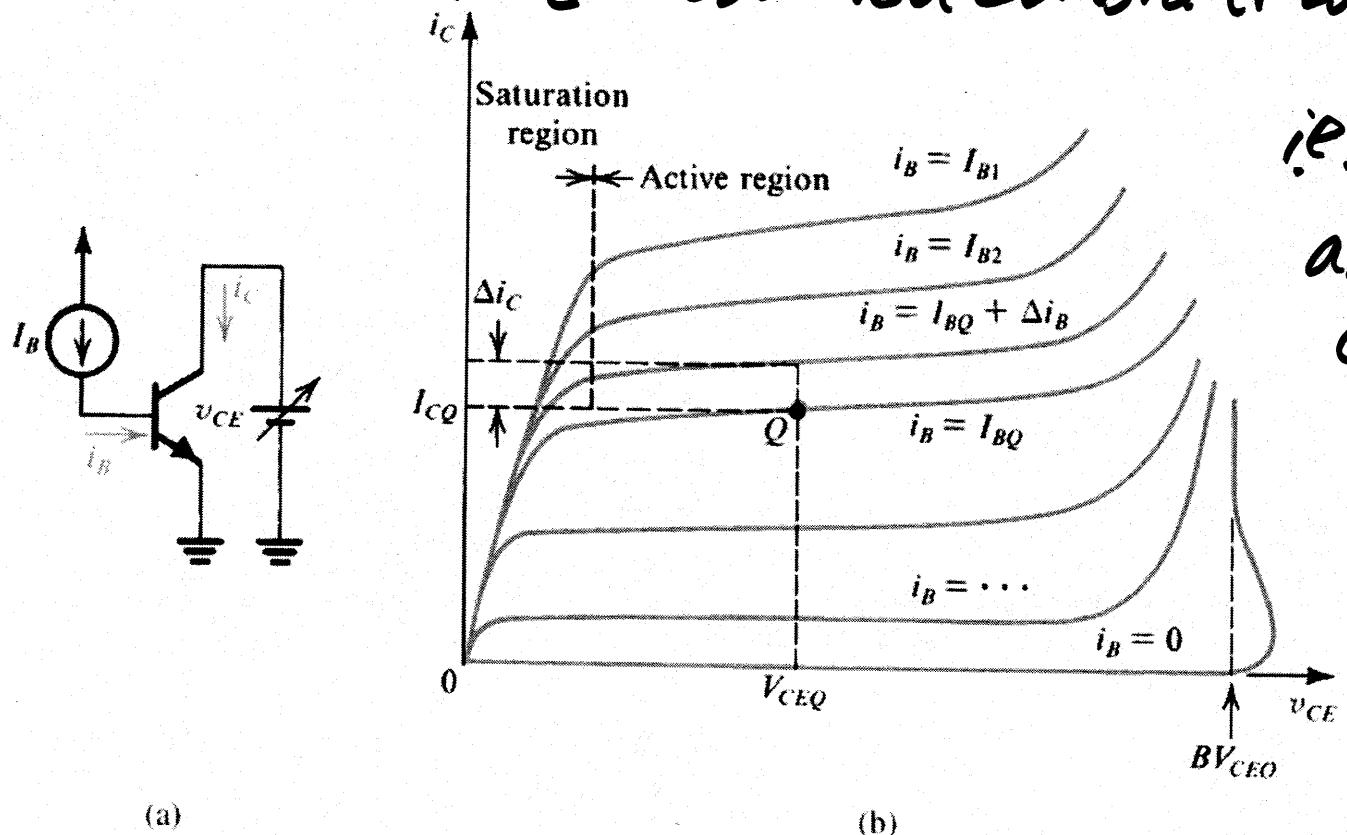
# Common Emitter Characteristics

Note slope of characteristics  
Until now,  $i_C$  assumed constant with  $v_{BE}$  or  $i_B$




i.e.  $\beta = \beta_T =$   
assumed  
constant

Figure 5.21 Common-emitter characteristics. Note that the horizontal scale is expanded around the origin to show the saturation region in some detail.
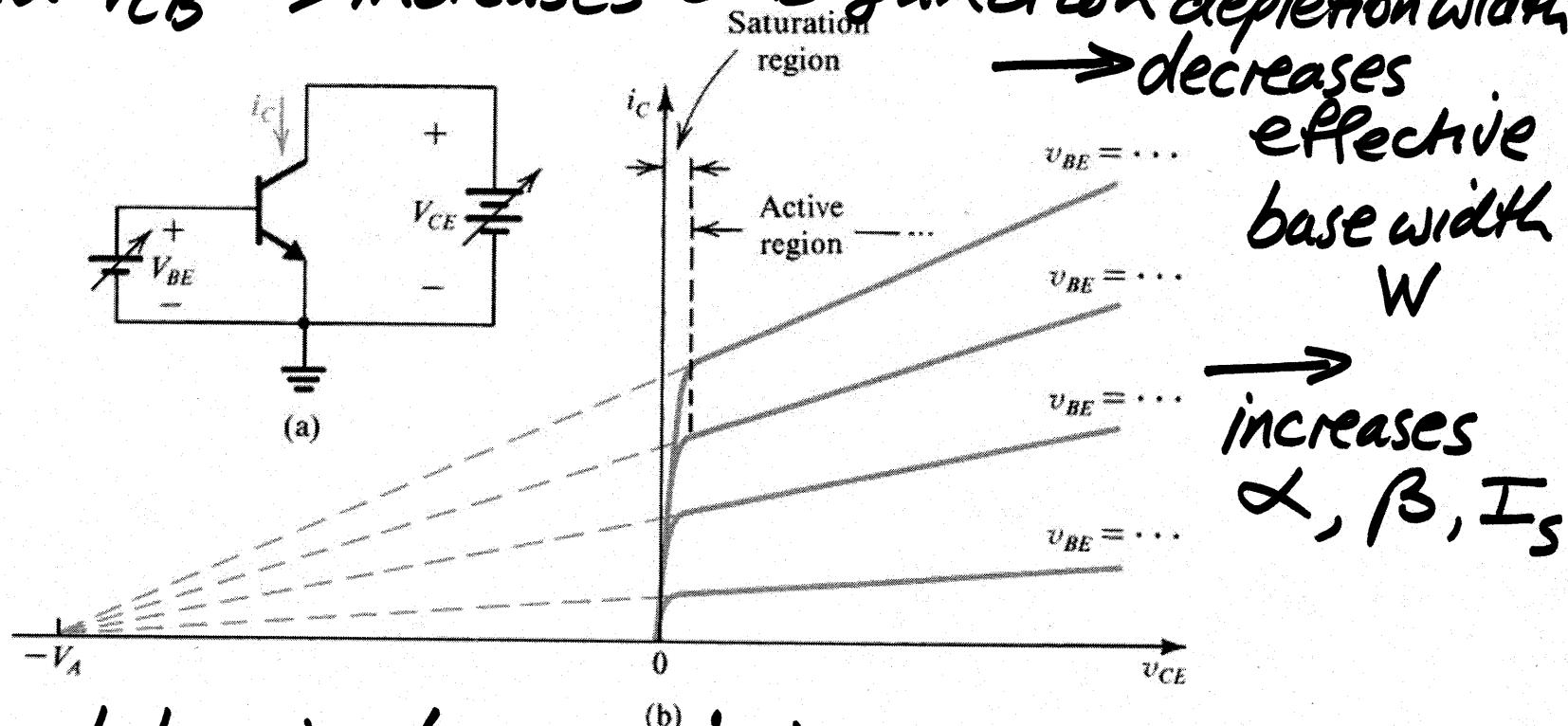
# Early Voltage

Increase  $V_{CE}$  increases  $V_{CB} = V_{CE} - V_{BE}$   
 Increased  $V_{CB} \rightarrow$  increases C-B junction depletion width




Represent by  $i_C = (I_s \exp \frac{v_{BE}}{V_T}) \cdot (1 + v_{CE}/V_A)$

$$r_o = \left\{ \frac{\partial i_C}{\partial v_{CE}} \Big|_{v_{BE}} \right\}^{-1} = \frac{V_A}{(I_s \exp \frac{v_{BE}}{V_T})} \\ = \frac{V_A}{[I_c / (1 + \frac{v_{CE}}{V_A})]} = \frac{V_A + V_{CE}}{I_c}$$

Figure 5.19 (a) Conceptual circuit for measuring the  $i_C - v_{CE}$  characteristics of the BJT. (b) The  $i_C - v_{CE}$  characteristics of a practical BJT.
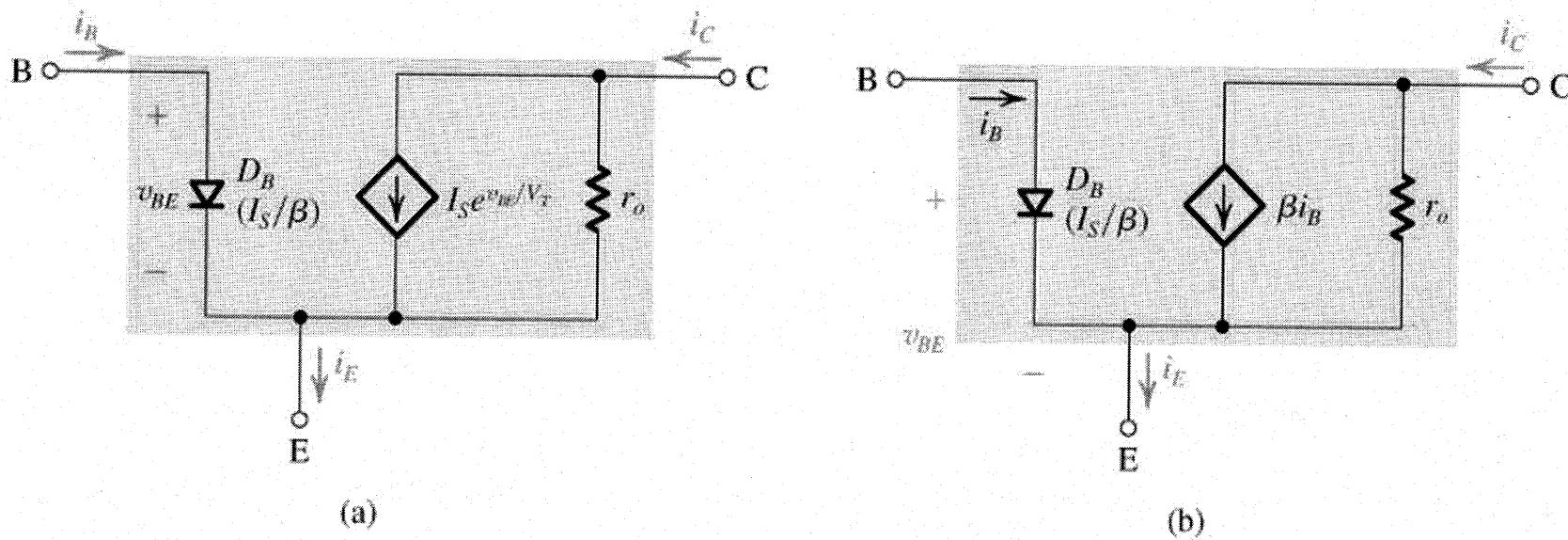
# Equivalent Circuit Model

Modify forward active model to include  $r_o$





$v_{BE}$  controls  $i_C \longleftrightarrow i_B$  controls  $i_C$   
equivalent

Figure 5.20 Large-signal equivalent-circuit models of an *n*p*n* BJT operating in the active mode in the common-emitter configuration.

# Common Emitter Characteristics

Bias point Q

$I_{CQ}$ ,  $I_{BQ}$ ,  $V_{CEQ}$

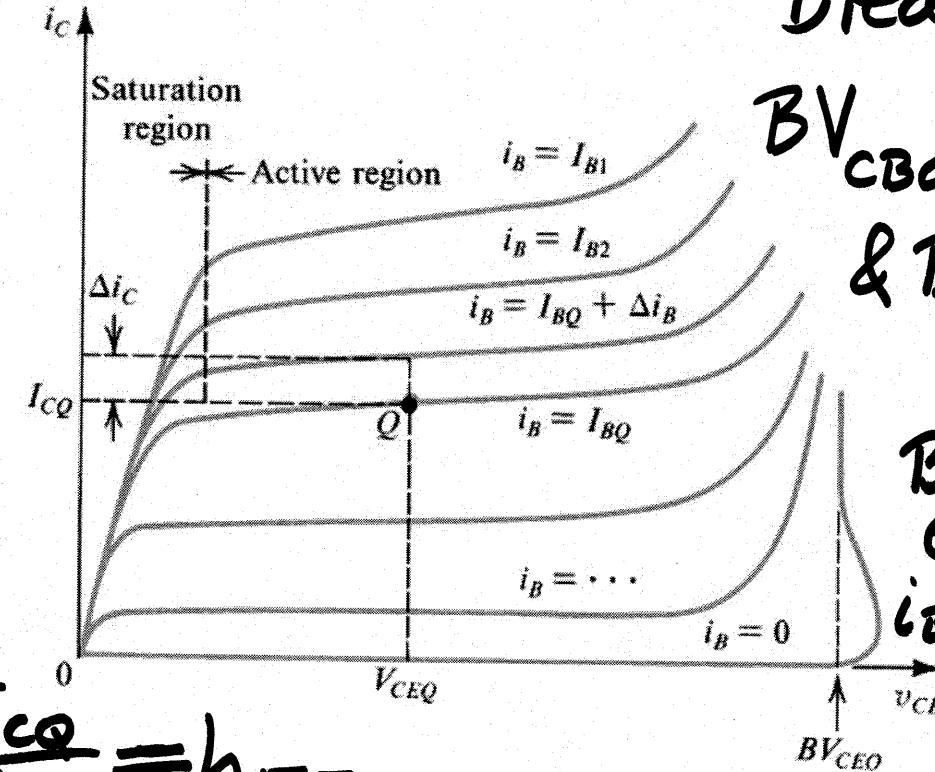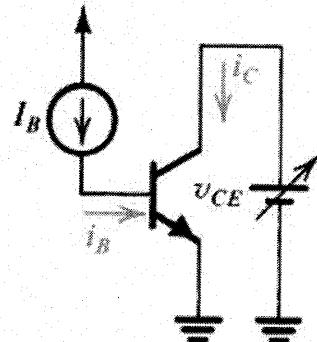

$$\text{Large signal } \beta_{DC} = \frac{I_{CQ}}{I_{BQ}} = h_{FE}$$

$$\text{Small signal } \beta_{ac} = \left| \frac{\Delta I_C}{\Delta I_B} \right| = h_{fe}$$

(Incremental / a.c.)

Typically  $BV_{CBO} \sim 50V$   
 &  $BV_{EBO} \sim 6 \text{ to } 8V$

$V_{CE}$  constant, i.e.  $\bar{v}_{ce} = 0$ , no signal  
 Hence "short circuit" current gain

$\beta_{DC} \& \beta_{ac} \sim 10\text{-}20\%$   
 different

Breakdown

$$BV_{CBO} \rightarrow BV_{CEO}$$


$$\& BV_{CEO} \sim \frac{1}{2} BV_{CBO}$$

Base O.C.  
 $i_B = 0$

Emitter O.C.  
 $i_E = 0$


Figure 5.21 Common-emitter characteristics. Note that the horizontal scale is expanded around the origin to show the saturation region in some detail.

## $\beta_{DC}$ variations

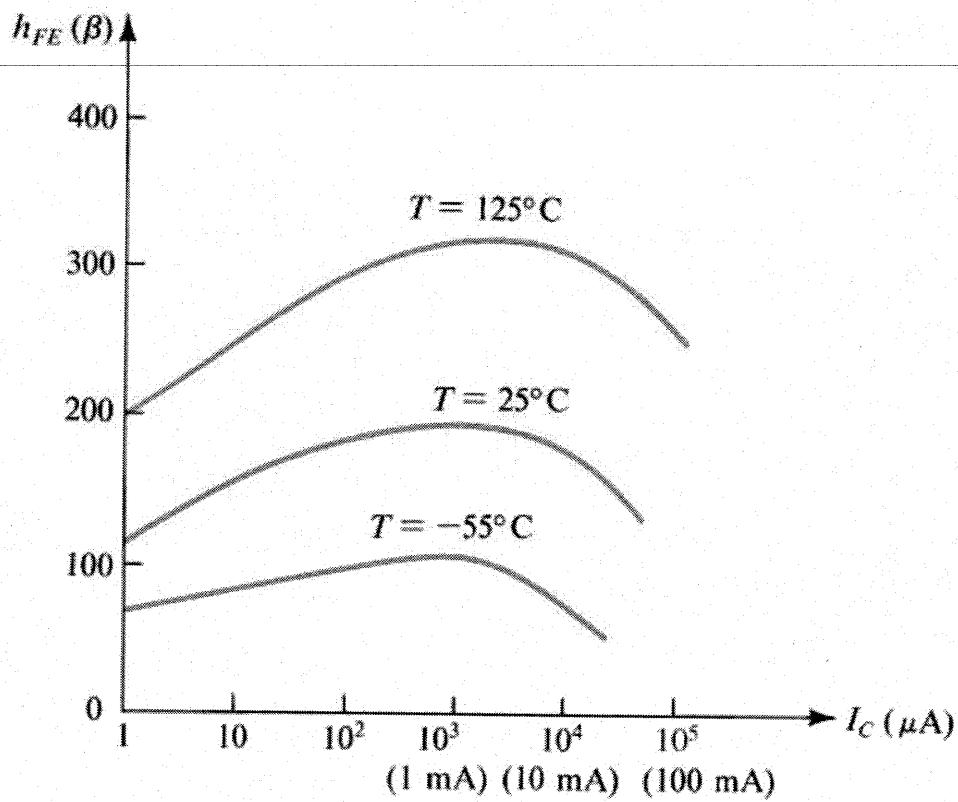

**Figure 5.22** Typical dependence of  $\beta$  on  $I_C$  and on temperature in a modern integrated-circuit *npn* silicon transistor intended for operation around 1 mA.

# Saturation

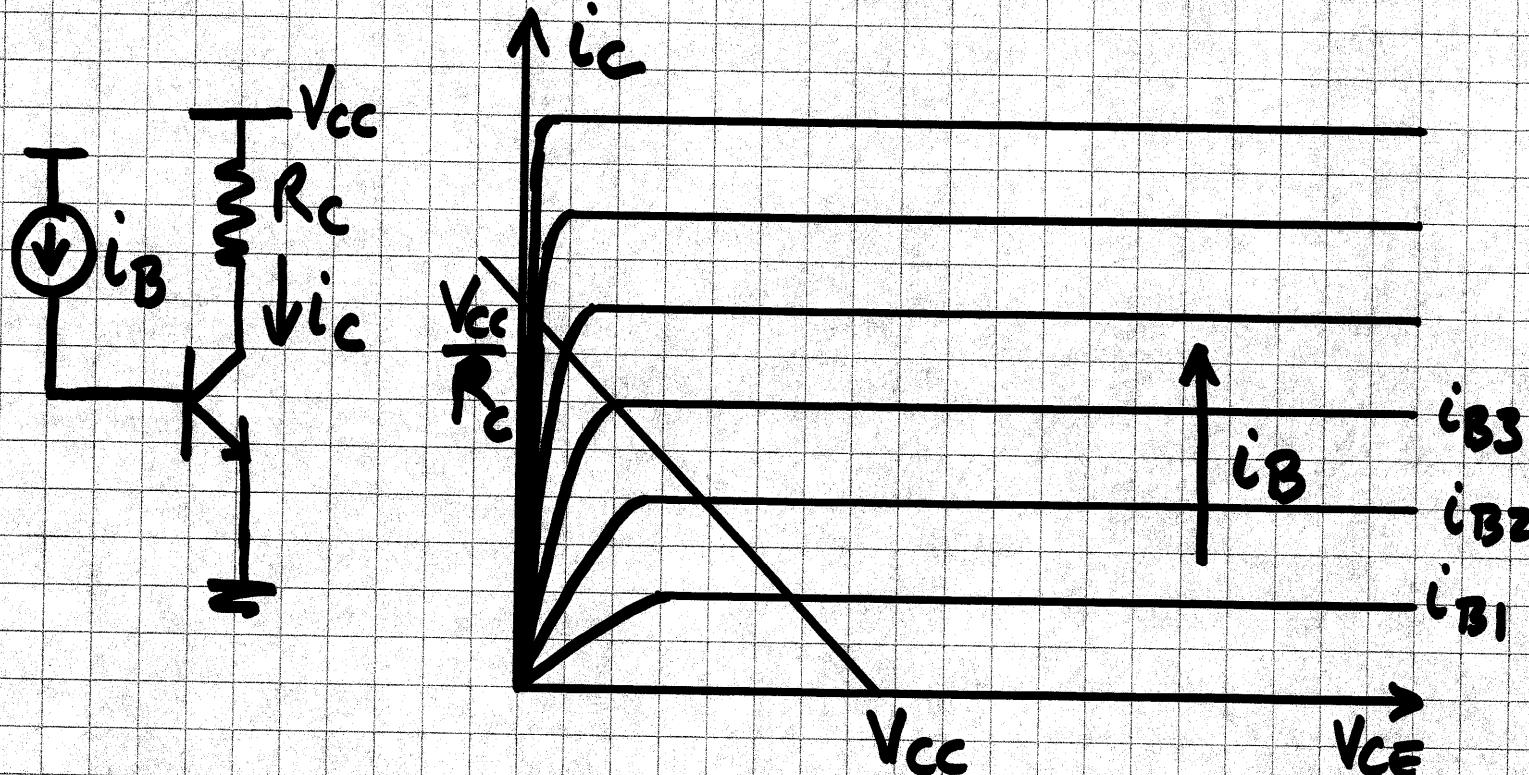

Increasing  $I_B \rightarrow I_C = \beta I_B$  &  $V_{CE} = V_{CC} - I_C R_C$

Works until  $i_{B3}$  here, then  $\rightarrow$  saturation

$I_C \rightarrow V_{CC}/R_C$  max as  $V_{CE} \rightarrow 0$

In practice  $\frac{V_{CC} - V_{CE})_{SAT}}{R_C}$  &  $V_{(CE)_{SAT}}$

# Saturation Region, e.g. at X

$$\beta_{\text{sat}} < \beta_{\text{active}} \quad I_{C\text{SAT}} < \beta I_B$$

Overdrive factor

$$= \frac{\beta_F}{(I_c/I_B)_{\text{SAT}}}$$

$$= \beta_F \left( \frac{I_B}{I_c} \right)_{\text{SAT}}$$

$$\rightarrow \frac{(I_B)_{\text{SAT}}}{I_c/\beta_F}$$

$$= \frac{\beta_F}{\beta_{\text{forced}}}$$


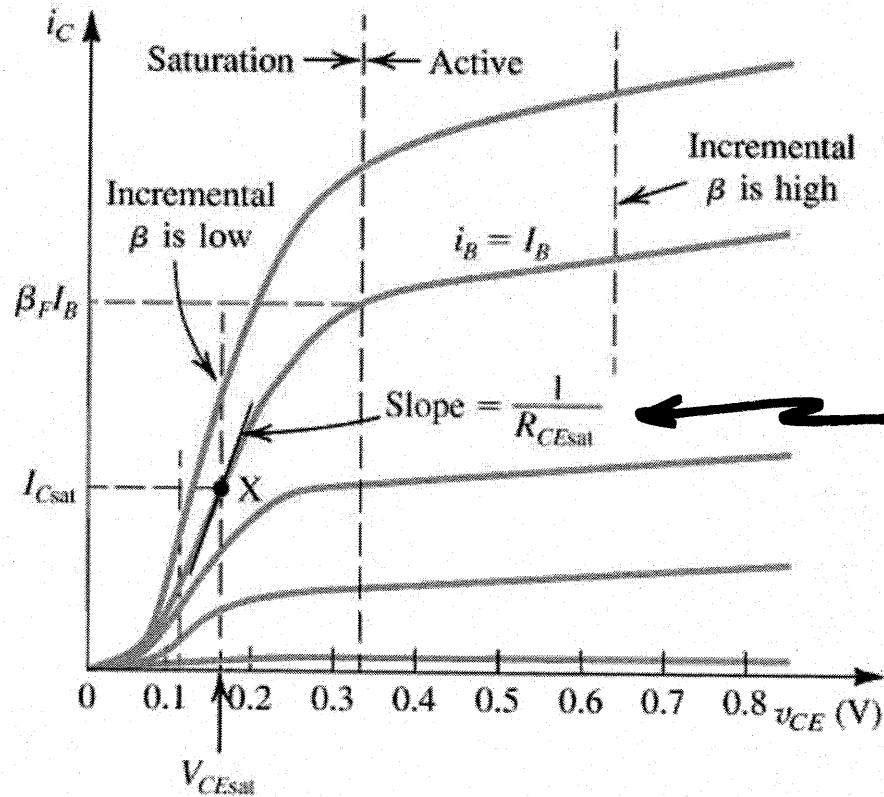



Figure 5.23 An expanded view of the common-emitter characteristics in the saturation region.

→ 1 in active region


# Saturation Mode models

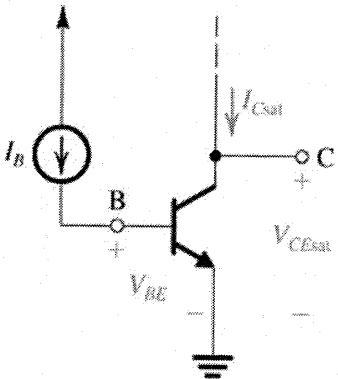


(a)

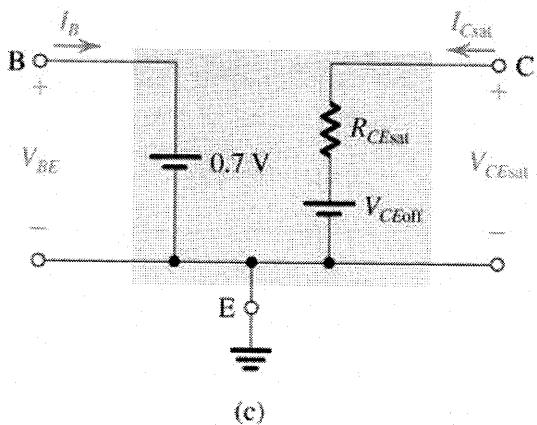

(c)

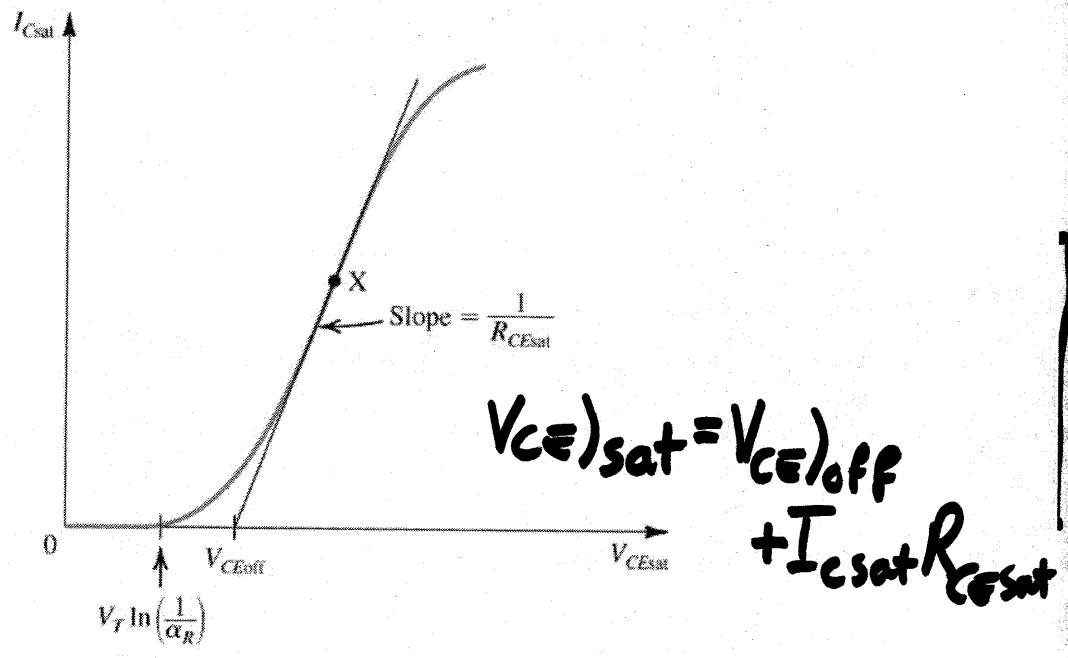

(b)

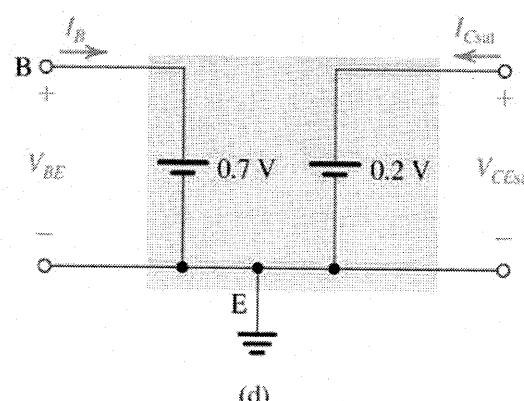


(d)

$$V_{CE} \text{ (sat)} = V_{CE} \text{ (off)} + I_{C \text{ sat}} R_{C \text{ sat}}$$

**Figure 5.24** (a) An *npn* transistor operated in saturation mode with a constant base current  $I_B$ . (b) The  $i_C$ - $v_{CE}$  characteristic curve corresponding to  $i_b = I_B$ . The curve can be approximated by a straight line of slope  $1/R_{CE\text{sat}}$ . (c) Equivalent-circuit representation of the saturated transistor. (d) A simplified equivalent-circuit model of the saturated transistor.


**Ex. 5.18:  $BV_{CBO}=70V$ . Find  $V_o$**

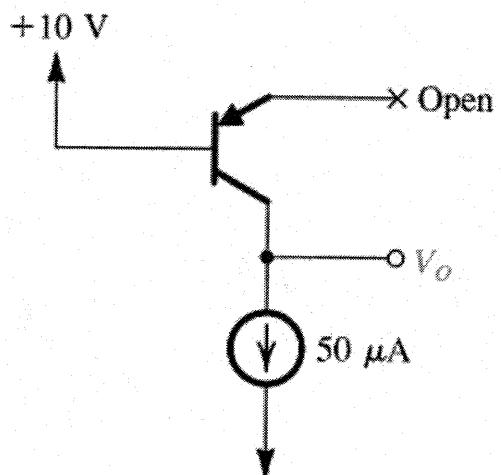


**Figure E5.18**

# Summary of BJT models

## NPN

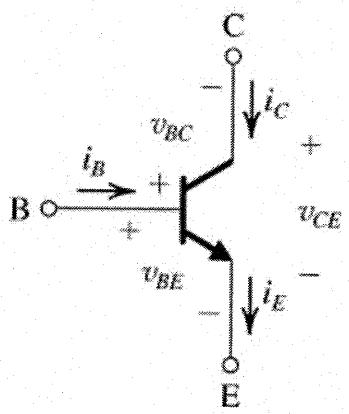

## PNP

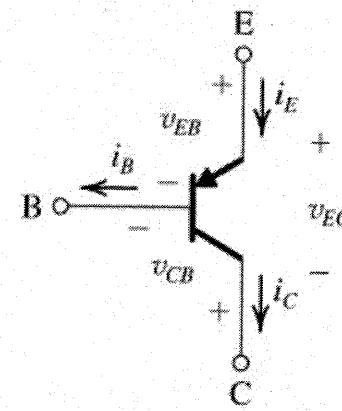

Large signal equivalent circuits (including Early Effect)


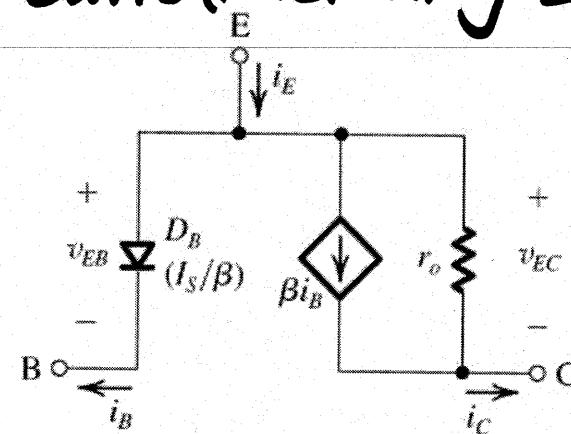
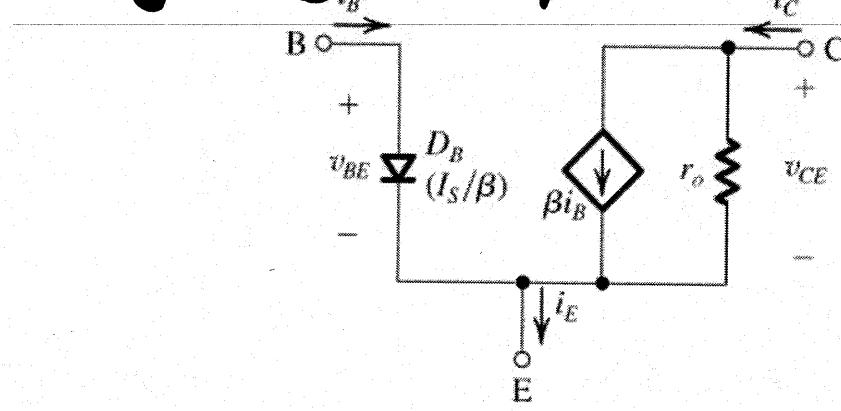


Table 5.3

# BJT Models continued

## Ebers-Moll Models

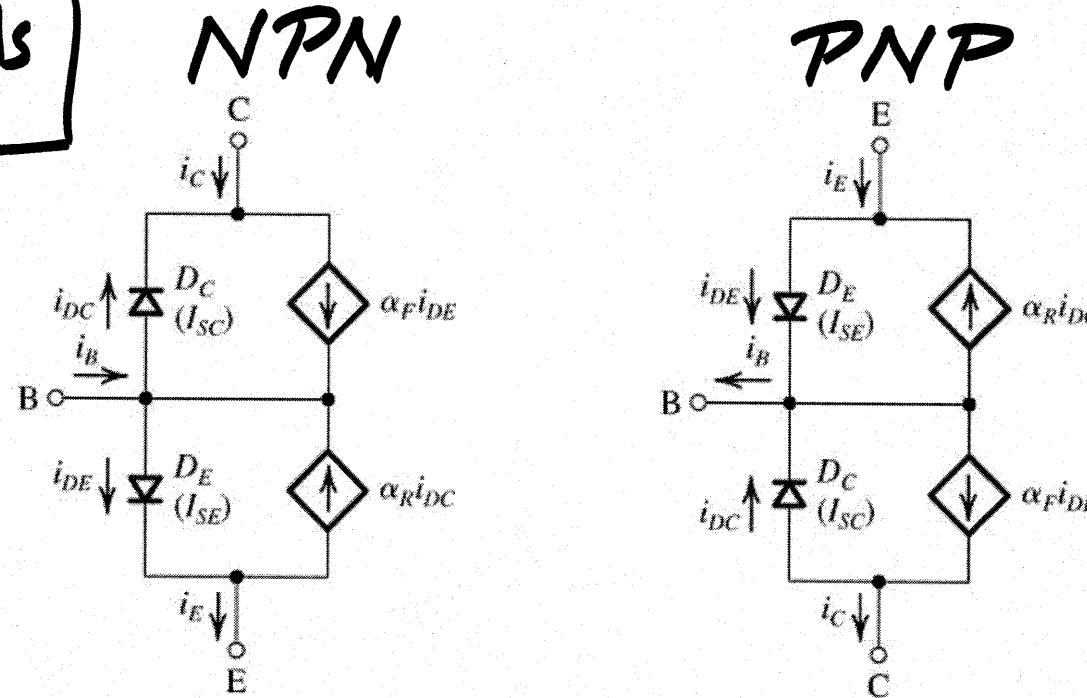

## Saturation mode

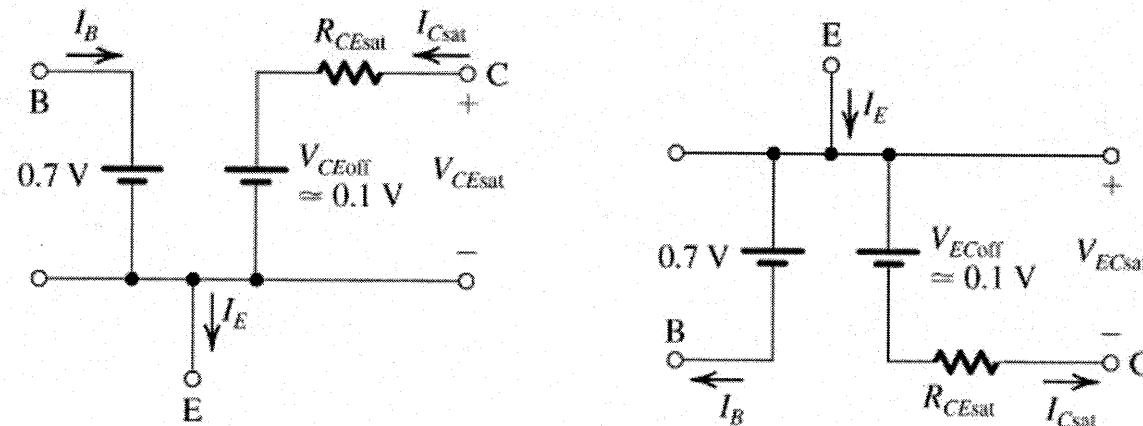


Table 5.3 (Continued)

# Exercises

- 5.1
  - NPN  $v_{BE}=0.7V$  at  $i_C=1mA$ .  
Find  $v_{BE}$  at  $i_C=0.1mA, 10mA$
- 5.2
  - Find  $\alpha$  range for  $\beta=50$  to  $150$ .
- 5.3
  - NPN  $I_B=14.46\mu A$  for  $I_E=1.460mA$ , and  $V_{BE}=0.7V$ .  
Find  $\alpha$ ,  $\beta$ , and  $I_S$
- 5.4
  - $I_C=10mA$ . Find  $\beta$  and  $I_B$  for  $\alpha = 0.99, 0.98$ .

Ex 5.1 NPN with  $V_{BE} = 0.7V$  at  $i_C = 1mA$

Find  $V_{BE}$  for  $i_C = 0.1mA, 10mA$

( $i_C$  controlled by  $V_{BE}$  — hence same as earlier diode examples)

Method 1:  $i_C = I_S \exp(V_{BE}/V_T)$  Solve for  $I_S$  & substitute back.

Method 2:  $V_{BE} = V_T \ln(i_C/I_S) \rightarrow V_{BE}' = 0.7V + V_T \ln \frac{i_C'}{1mA}$   
 $= 0.7V + 2.3 \times 25mV \ln \frac{i_C'}{1mA}$

$$i_C' = 0.1mA$$

$$V_{BE}' = 0.7 - 2.3 \times 25mV = 0.64V$$

$$i_C' = 10mA$$

$$V_{BE}' = 0.7 + 2.3 \times 25mV = 0.76V$$

Ex 5.2  $\beta = 50$  to  $150$ , find  $\alpha$  range

$$\alpha = \frac{50}{51} \text{ to } \frac{150}{151} = 0.982 \text{ to } 0.993$$

Ex 5.3  $i_B = 14.46 \mu A$   $i_E = 1.446 mA$   $V_{BE} = 0.7V$   
 Calculate  $\alpha$ ,  $\beta$ ,  $I_S$

$$\beta = \frac{i_C}{i_B} = \frac{i_E - i_B}{i_B} = \frac{1.446 mA}{14.46 \mu A} = 100$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} = 0.99 \quad \text{OR} \quad \frac{i_C}{i_E} = \frac{1.446 mA}{1.460 mA}$$

$$I_S = i_C \exp - \frac{V_{BE}}{V_T} = 1.446 mA \exp - \frac{0.7}{25 \times 10^{-3}} = 9.998 \times 10^{-16} A \\ \approx 10^{-15} A \approx 1 fA$$

Ex 5.4  $i_C = 10 mA$

$$(a) \text{ For } \alpha = 0.99 \quad i_B = i_C/\beta = i_C \frac{1-\alpha}{\alpha} = \frac{0.01}{0.99} 10 mA \\ \beta = \frac{0.99}{0.01} = 99 \quad \approx 0.1 mA$$

$$(b) \text{ For } \alpha = 0.98 \quad i_B = \frac{0.02}{0.98} 10 mA \approx 0.2 mA \\ \beta = \frac{0.98}{0.02} = 49$$

# Exercise

- 5.6
  - BJT  $\alpha_F=0.99$ ,  $\alpha_R=0.02$ ,  $I_S=10^{-15}A$ :
  - Calculate second term on RHS of equations 5.31, 5.32, 5.33, and verify they can be neglected.
  - Calculate  $i_E$ ,  $i_C$ , and  $i_B$  for  $v_{BE}=0.7V$ .

Ex 5.6  $\alpha_F = 0.99$   $\alpha_R = 0.02$   $I_S = 10^{-15} A$  &  $V_{BE} = 7V$   
 Repeat previous equations for convenience:

$$i_E = (I_S / \alpha_F) \exp \frac{V_{BE}}{V_T} + I_S (1 - 1/\alpha_F)$$

$$i_C = I_S \exp \frac{V_{BE}}{V_T} + I_S (1/\alpha_R - 1)$$

$$i_B = (I_S / \beta_F) \exp \frac{V_{BE}}{V_T} - I_S (1/\beta_F + 1/\beta_R)$$

$$\beta_F = \frac{.99}{.01} = 99$$

$$\exp \frac{.7V}{.025V} = 1.446 \times 10^{12}$$

$$\beta_R = \frac{.02}{.98} \approx .02$$

$$\therefore I_S \exp \frac{.7}{.025} = 1.446 \text{ mA}$$

Show these terms  
negligible


$$\therefore i_E \approx 1.446 \text{ mA} = 10^{-17} A$$

$$i_C \approx 1.446 \text{ mA} + 4.9 \times 10^{-14} A$$

$$i_B \approx 14.5 \mu A = 3 \times 10^{-17} A$$

negligible

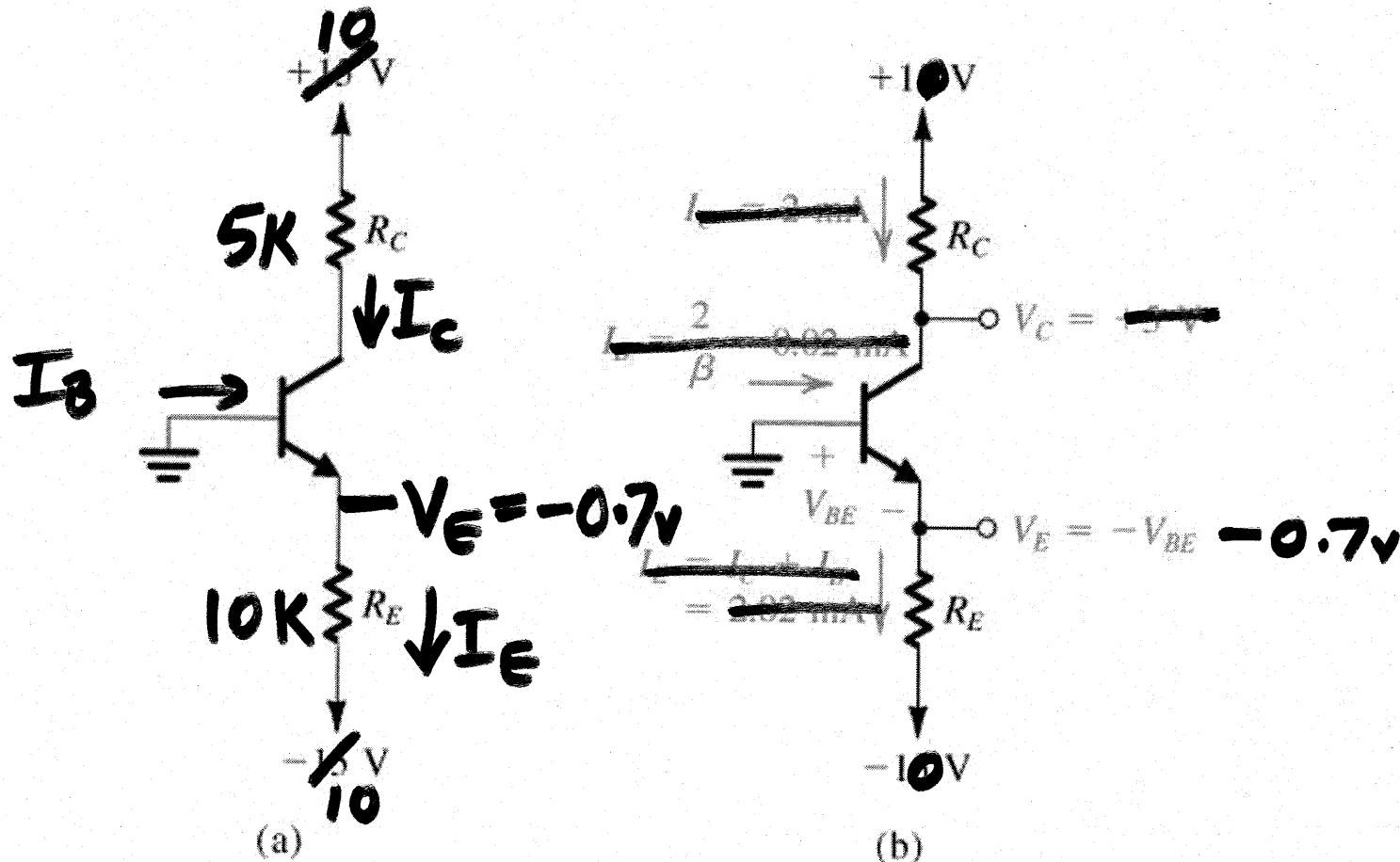Ex 5.10  $\beta = 50$ .  $I_E, I_B, I_C, V_C$ ?



$$I_E = \frac{-0.7 - (-10)}{10k} = 0.93\text{mA}, I_B = \frac{I_E}{1+\beta} = \frac{0.93}{51} = 18.24\mu\text{A}$$


Figure 5.15 Circuit for Example 5.1.

$$I_C = \frac{\beta}{1+\beta} I_E = \frac{50}{51} 0.93\text{mA} = 0.912\text{mA} \quad (\text{Check } I_C + I_B = I_E)$$

$$V_C = 10\text{v} - 5\text{K} \times 0.912\text{mA} = 5.44\text{volts}$$

Ex 5.11 Find  $\alpha, \beta, V_C$ .  $V_B = 1V$   $V_E = 1.7V$
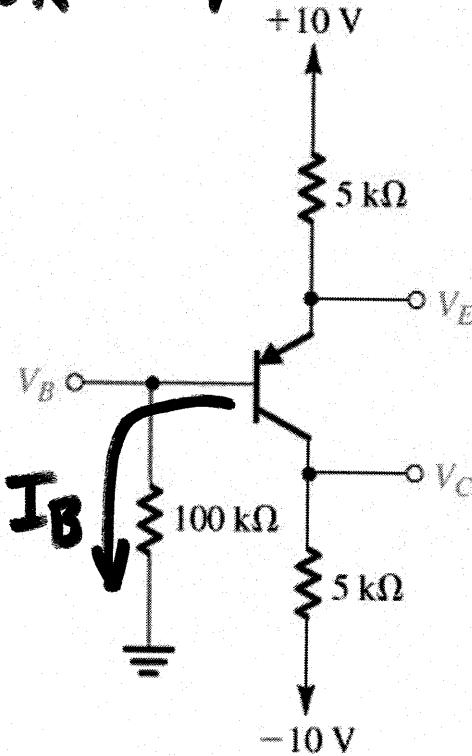
$$V_B = 1V \therefore I_B = \frac{1V}{100k\Omega} = 10\mu A$$



$$\begin{aligned} V_E &= 1.7V \therefore I_E &= \frac{10 - 1.7V}{5k\Omega} \\ &= 8.3V/5k\Omega \\ &= 1.66mA \end{aligned}$$

$$\therefore I_C = I_E - I_B = 1.66 - 0.01mA = 1.65mA$$

$$\therefore V_C = -10V + 5k\Omega \times 1.65mA = -10V + 8.25V = -1.75V$$

Figure E5.11

$$\alpha = I_C/I_E = 1.65/1.66 = 1 - \frac{0.01}{1.66} = 1 - \frac{0.01}{10} = 0.994$$

$$\beta = I_C/I_B = 1.65/0.01 = 165$$

Ex 5.18 Find  $V_o = V_c$  if  $BV_{BCEO} = 70V$

Note : Emitter open circuit




$I_E = 0 \therefore I_B, I_C = 0$  if BJT in active region  
Also, not saturation

$\therefore C-B$  breakdown

for finite

$I_C \& \therefore I_B$

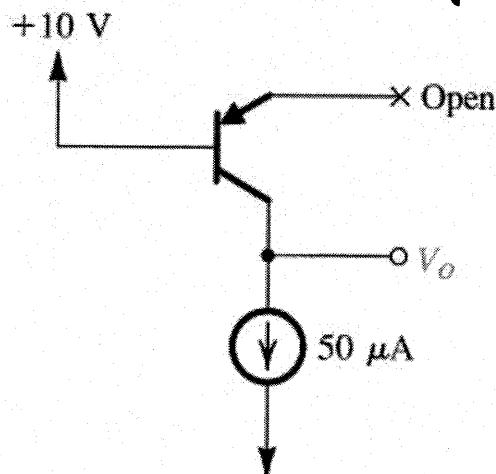

$$\therefore V_B - V_C = BV_{BCEO} = 70V$$

$$\begin{aligned} & \& V_C &= +10V - 70V \\ & & &= -60V \end{aligned}$$

Figure E5.18