

ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 13

9th November, 2006



CHAPTER 5

Bipolar Junction Transistors (BJTs)

5.5 Biasing


← DC analysis/design

5.6 Small Signal

← AC analysis/design

Two simple bias schemes


Set V_{BE}

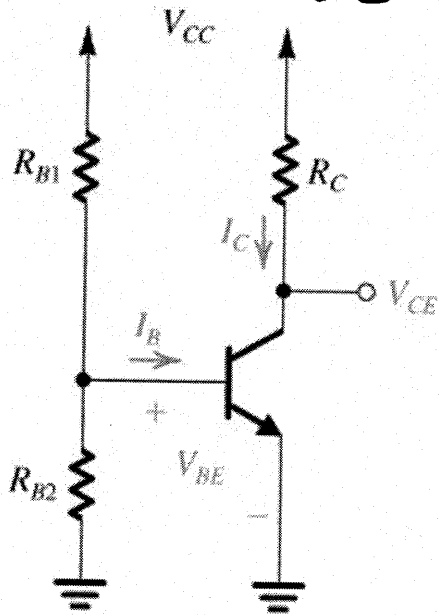

(a)

$$I_C = I_S \exp \frac{V_{BE}}{V_T}$$

Set I_B

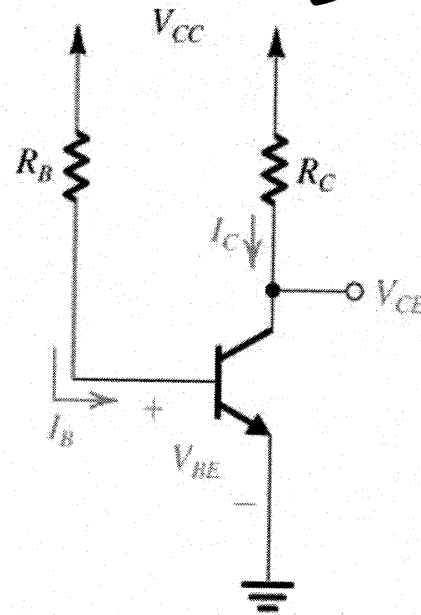

(b)

$$I_C = \beta I_B$$

Figure 5.43 Two obvious schemes for biasing the BJT: (a) by fixing V_{BE} ; (b) by fixing I_B . Both result in wide variations in I_C and hence in V_{CE} and therefore are considered to be "bad." Neither scheme is recommended.

Small variations in V_{BE}
due to R_1, R_2 tolerances

β variations

→ exp → large I_C variations ←

S & S: "Classical" bias } R_E negative feedback
 Self-bias } \rightarrow defines I_E
 Auto-bias }

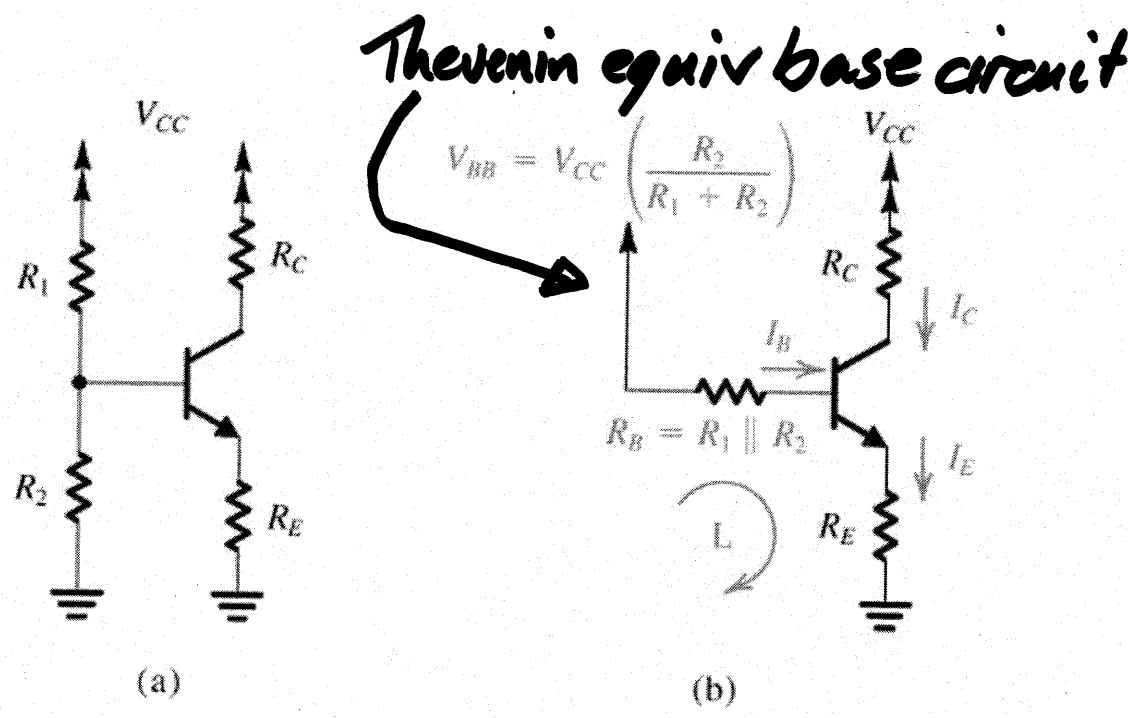


Figure 5.44 Classical biasing for BJTs using a single power supply: (a) circuit; (b) circuit with the voltage divider supplying the base replaced with its Thévenin equivalent.

$$I_B = \frac{V_{BB} - V_{BE} - I_E R_E}{R_B}$$

$$= \frac{V_{BB} - V_{BE} - (1+\beta)I_B R_E}{R_B}$$

$$= \frac{(V_{BB} - V_{BE})/R_B}{1 + (1+\beta)R_E/R_B} = \frac{V_{BB} - V_{BE}}{R_B + (1+\beta)R_E}$$

But we actually want to control $I_E \approx I_C$, not I_B

$$I_E = (1+\beta)I_B = \frac{(1+\beta)(V_{BB} - V_{BE})}{R_B + (1+\beta)R_E}$$

$$= \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{1+\beta}} \approx \frac{V_{BB}}{R_E} \quad \text{if } V_{BB} \gg V_{BE} \text{ \& } R_B \ll (1+\beta)R_E$$

$V_{BB} \gg V_{BE}$ minimizes effects of V_{BE} variation with β and thermal effects

$R_B \ll (1+\beta)R_E$ minimizes effects of β variations

Typically:

(a) make $V_{BB} \sim \frac{1}{3}V_{CC}$

(b) make $\frac{V_{CC}}{R_1+R_2} \sim (0.1 \text{ to } 1) \times I_E$

(c) include $V_{BE} \sim 0.7$ in formula, rather than completely neglected.


(b) \rightarrow Say $I_E \sim 10\text{mA}$, $\beta = 100 \rightarrow I_B \sim 0.1\text{mA}$

If "standing current" $V_{CC}/(R_1+R_2) = 10\text{mA}$

Base current "drawn off" = $I_B \sim 0.2\text{mA}$ to 0.05mA
as $\beta = 50$ to 200

i.e. minimizes variation in $I_B R_B$ with β

Negative feedback effect with R_E

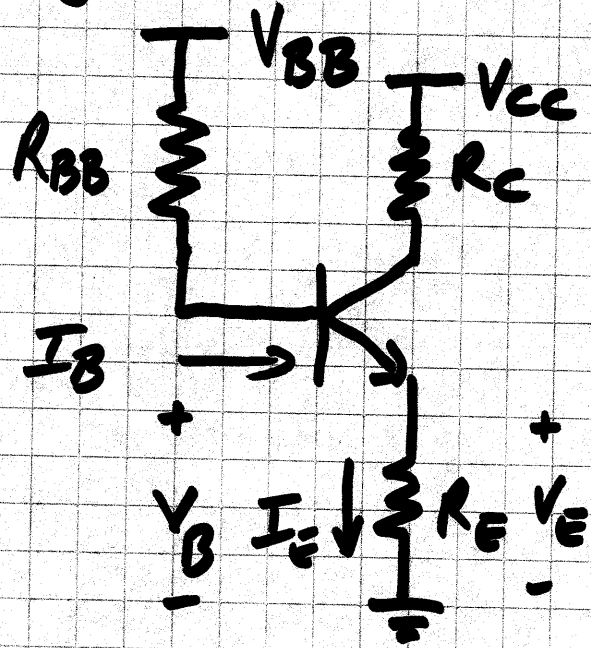

Assume ideal design for nominal β .

If β increases (due to temperature or different transistor)

I_E tends to increase

$\therefore V_E$ increases

and for $V_{BE} \sim \text{constant}$, V_B increases

$$\therefore I_B = \frac{V_{BB} - V_B}{R_B}$$

decreases, decreasing I_E
back towards design value

Exercise 5.32
(refers to Example 5.13)


2 Supply voltage bias (+, -, and ground)

$$I_E = (1 + \beta) I_B = \frac{1 + \beta}{R_B} (0 - V_{BE} - I_E R_E - (-V_{EE}))$$

$$= \frac{(V_{EE} - V_{BE}) \frac{1 + \beta}{R_B}}{1 + (1 + \beta) R_E / R_B}$$

$$= \frac{V_{EE} - V_{BE}}{R_E + \frac{R_B}{1 + \beta}}$$
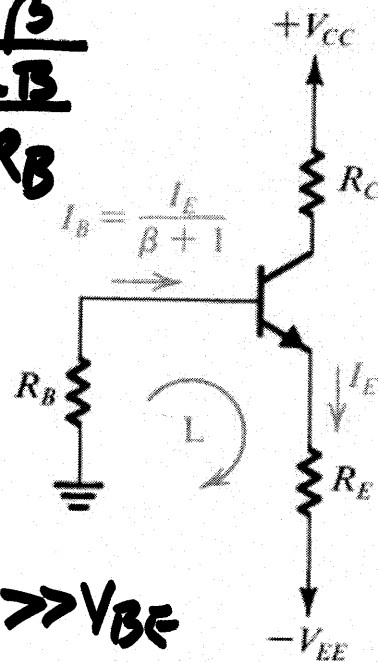
$$\Rightarrow \frac{V_{EE}}{R_E} \text{ for } V_{EE} \gg V_{BE} \\ R_E \gg \frac{R_B}{1 + \beta}$$



Introduces the idea of constant current source emitter bias.

Figure 5.45 Biasing the BJT using two power supplies. Resistor R_B is needed only if the signal is to be capacitively coupled to the base. Otherwise, the base can be connected directly to ground, or to a grounded signal source, resulting in almost total β -independence of the bias current.


Exercise D5.33

Collector-Base Feedback Bias


$$V_{CC} = I_E R_C + \frac{I_E}{1+\beta} R_B + V_{BE}$$

$$\therefore I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{1+\beta}} \approx \frac{V_{CC}}{R_C} \text{ for } V_{CC} \gg V_{BE}$$

$$R_C \gg \frac{R_B}{1+\beta}$$

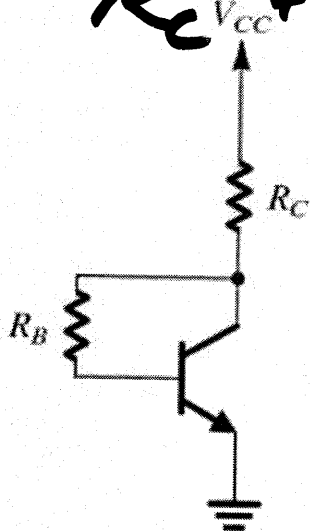

(a)

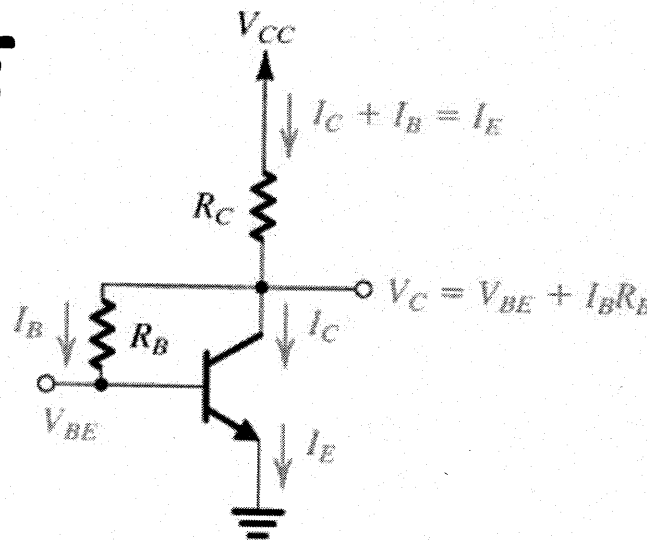

(b)

Ex 5.34 $V_{CC} = 10\text{V}$ $\beta = 100$ $I_E = 1\text{mA}$ $\pm 2\text{V}$ swing at V_C
 i.e. $V_{CE} = 2.3\text{V}$

$$I_C \approx I_E = 1\text{mA}$$

$$\therefore R_C = \frac{(10 - 2.3\text{V})}{1\text{mA}} = 7.7\text{K}$$

$$R_B = \frac{(2.3 - 0.7\text{V})}{1\text{mA}/100} = 160\text{K}$$

for $V_{CESAT} \sim 0.3\text{V}$
 OR $R_C \rightarrow \frac{(10 - 0.3)}{1\text{mA}} \sim 9.7\text{K}$
 $R_B \rightarrow \frac{2.3 - 0.6}{1\text{mA}/101} \sim 162\text{K}$


Figure 5.46 (a) A common-emitter transistor amplifier biased by a feedback resistor R_B . (b) Analysis of the circuit in (a).

Constant Current Source Bias


$$I_{REF} = \frac{V_{CC} - V_{BE} - (-V_{EE})}{R}$$

$$\approx \frac{V_{CC} + V_{EE}}{R}$$

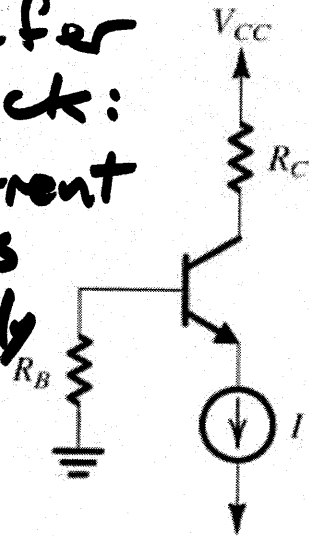Refer back:
Constant current emitter bias from 2-supply bias circuit.



(a)

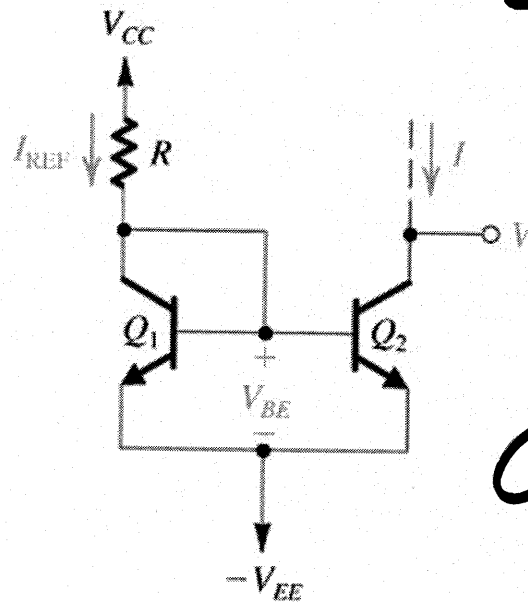

(b)

& $V_{BE1} = V_{BE2}$
 $\therefore I_{E1} = I_{E2}$
 $I = I_{REF}$
Current Mirror

Note $V_{CE1} = V_{BE} > V_{CE(SAT)}$
 \therefore Forward Active

Ex 5.35 (a) $V_{CC} = 10V$, $I = 1mA$, $R_B = 100K$, $R_C = 7.5K$
Find V_B, V_E, V_C for $\beta = 100$

Figure 5.47 (a) A BJT biased using a constant-current source I . (b) Circuit for implementing the current source I .

$$I = 1mA = I_E \therefore I_C = 0.99mA \text{ \& } V_C = 10 - (0.99)7.5 = 2.575V$$


$$I_B = 1mA/101 \therefore V_B = -100K \times 1mA/101 = -0.99V \text{ \& } V_E = -1.69V$$

$$(b) \text{ Find } R \text{ for } I = 1mA \text{ (} V_{EE} = 10V \text{)} \therefore R = (20V - 0.7V)/1mA = 19.3K\Omega$$


Small Signal (ac) Operation/Models

Complete circuit & signals
e.g. $v_{BE} = V_{BE} + v_{be}$

DC bias only

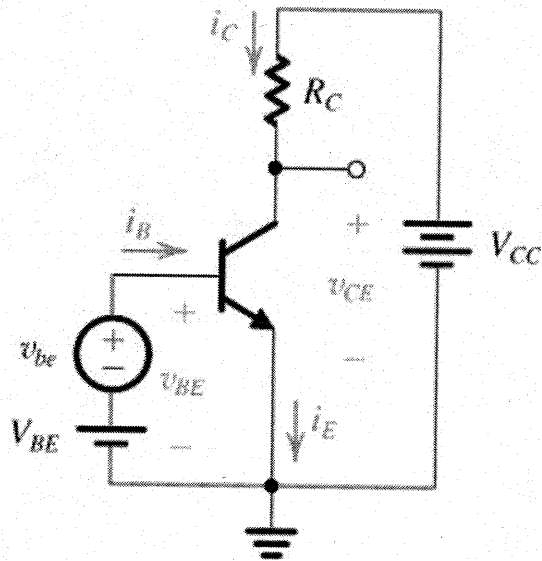

(a)

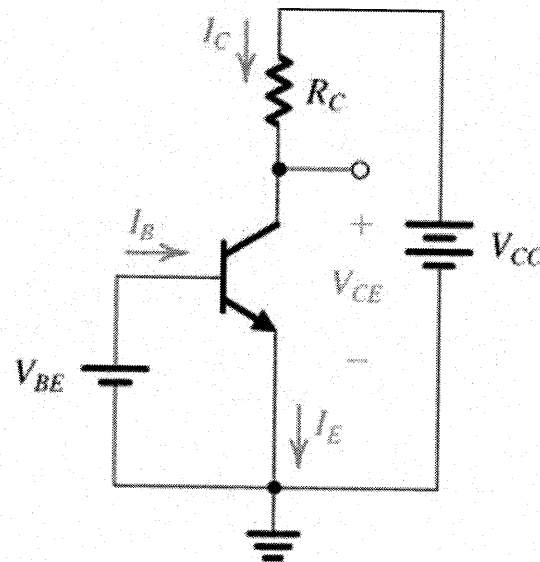

(b)

$$i_C = I_C + i_c = I_S \exp(V_{BE} + v_{be}) / V_T = I_C \exp \frac{v_{be}}{V_T} \approx I_C \left(1 + \frac{v_{be}}{V_T} \right)$$


if $v_{be} \ll V_T$

Figure 5.48 (a) Conceptual circuit to illustrate the operation of the transistor as an amplifier. (b) The circuit of (a) with the signal source v_{be} eliminated for dc (bias) analysis.

So $i_c \approx I_C \frac{v_{be}}{V_T} \Rightarrow g_m v_{be}$ where $g_m = I_C / V_T$ "Small signal approximation"

"Transconductance"

i_c vs v_{BE} characteristics

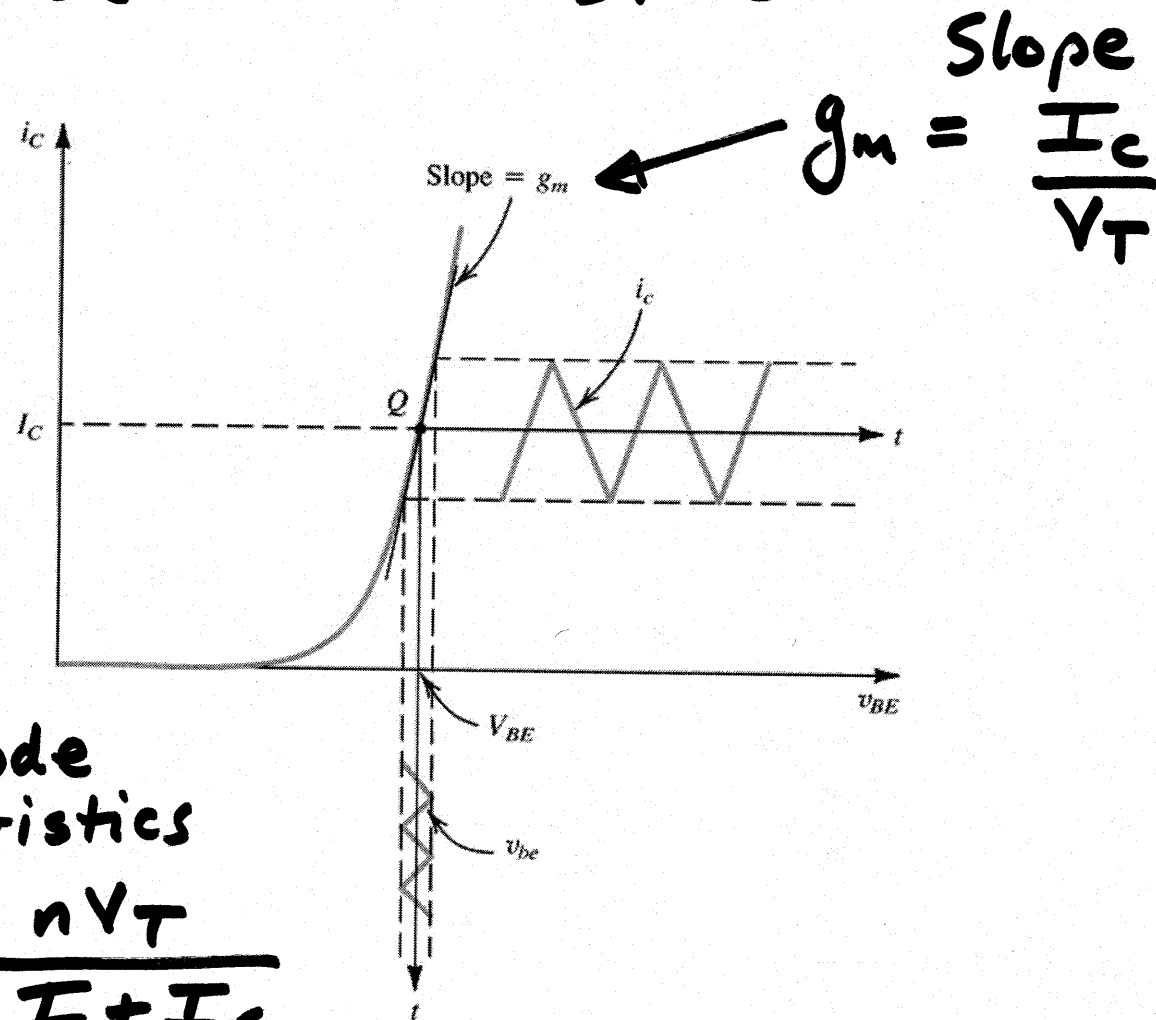

Remember diode characteristics

$$r_D = \frac{1}{\text{slope}} = \frac{nV_T}{I + I_s} \approx \frac{nV_T}{I}$$

Figure 5.49 Linear operation of the transistor under the small-signal condition: A small signal v_{be} with a triangular waveform is superimposed on the dc voltage V_{BE} . It gives rise to a collector signal current i_c , also of triangular waveform, superimposed on the dc current I_C . Here, $i_c = g_m v_{be}$, where g_m is the slope of the i_c - v_{BE} curve at the bias point Q .

Small Signal Input Resistance

$$i_B = \frac{i_C}{\beta} \approx \frac{I_C}{\beta} + \frac{I_C}{\beta} \cdot \frac{v_{be}}{V_T} \quad \& \quad i_b = \frac{I_C}{\beta} \frac{v_{be}}{V_T}$$


(small signal approximation)

$$= \frac{g_m}{\beta} v_{be}$$

Define $r_{\pi} = \frac{v_{be}}{i_b} = \frac{\beta}{g_m}$

$$= \beta \frac{V_T}{I_C}$$

$$= \frac{V_T}{I_B}$$

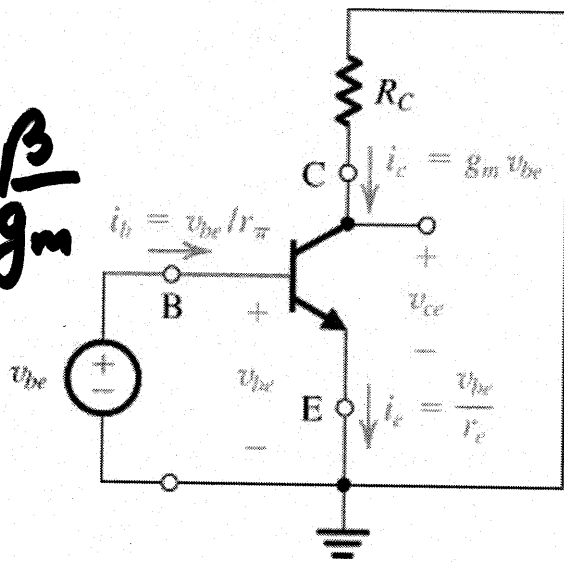

Define r_e (emitter resistance)

$$= v_{be} / i_e$$

$$= v_{be} / (i_c / \alpha)$$

$$= v_{be} / (I_C v_{be} / \alpha V_T)$$

$$= v_{be} / (I_E v_{be} / V_T)$$

$$= V_T / I_E$$

$$= \alpha V_T / I_C = \alpha / g_m$$

$$\approx 1 / g_m$$

$$v_{be} = i_b r_{\pi} = i_e r_e \quad \therefore r_{\pi} = \frac{i_e}{i_b} r_e = (1 + \beta) r_e$$


Figure 5.50 The amplifier circuit of Fig. 5.48(a) with the dc sources (V_{BE} and V_{CC}) eliminated (short circuited). Thus only the signal components are present. Note that this is a representation of the signal operation of the BJT and not an actual amplifier circuit.

Exercise 5.37

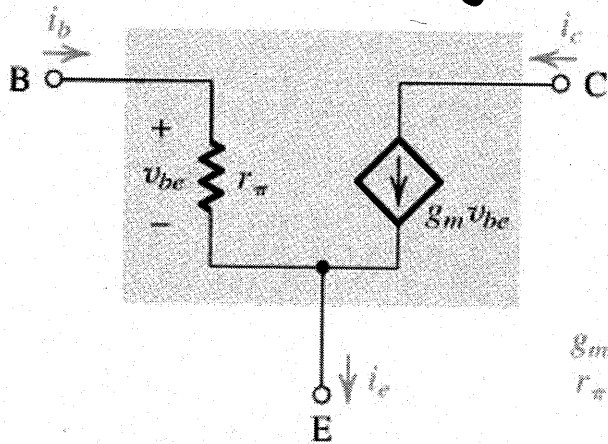Exercise 5.38


Hybrid π Small Signal Model

$$\begin{aligned}
 i_e &= i_b + i_c \\
 &= \frac{v_{be}}{r_\pi} + g_m v_{be} \\
 &= v_{be} (g_m + 1/r_\pi) \\
 &= \frac{v_{be}}{r_\pi} (1 + g_m r_\pi) \\
 &= \frac{v_{be}}{r_\pi} (1 + \beta) = v_{be} / \left(\frac{r_\pi}{1 + \beta} \right) \\
 &= v_{be} / r_e
 \end{aligned}$$



(a)
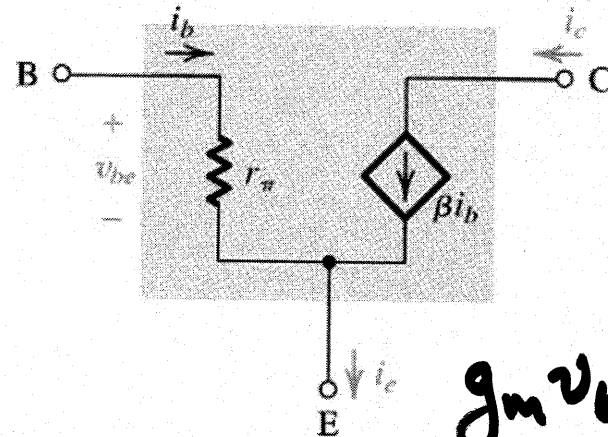
$$\begin{aligned}
 g_m &= I_C / V_T \\
 r_\pi &= \beta / g_m
 \end{aligned}$$




(b)

$$\begin{aligned}
 g_m v_{be} &= g_m i_b r_\pi \\
 &= \beta i_b
 \end{aligned}$$

Same circuits
Use whichever suits
(Given values, personal preference)


Figure 5.51 Two slightly different versions of the simplified hybrid- π model for the small-signal operation of the BJT. The equivalent circuit in (a) represents the BJT as a voltage-controlled current source (a transconductance amplifier), and that in (b) represents the BJT as a current-controlled current source (a current amplifier).

T-model : Uses r_e instead of r_{π}

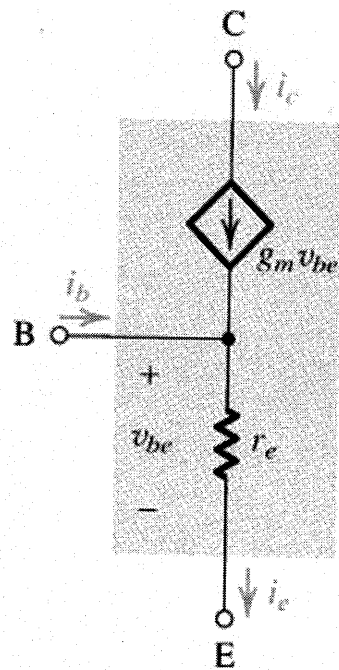

$$g_m = I_C / V_T$$
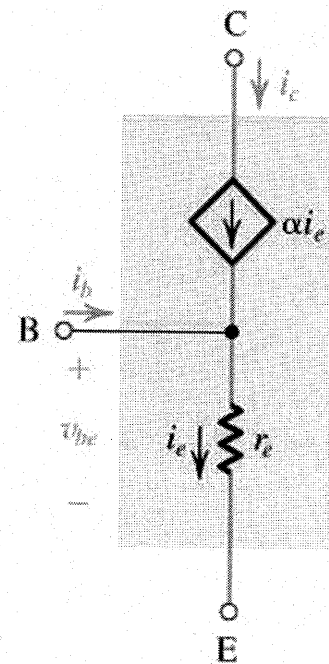
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$





(a)
Voltage controlled

(b)
Current controlled

Figure 5.52 Two slightly different versions of what is known as the *T model* of the BJT. The circuit in (a) is a voltage-controlled current source representation and that in (b) is a current-controlled current source representation. These models explicitly show the emitter resistance r_e rather than the base resistance r_{π} featured in the hybrid- π model.

Example 5.14

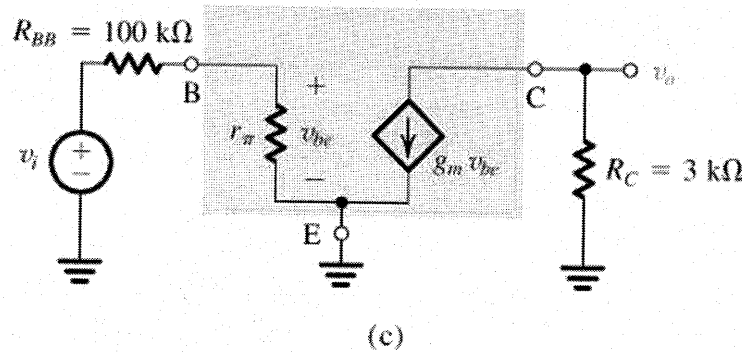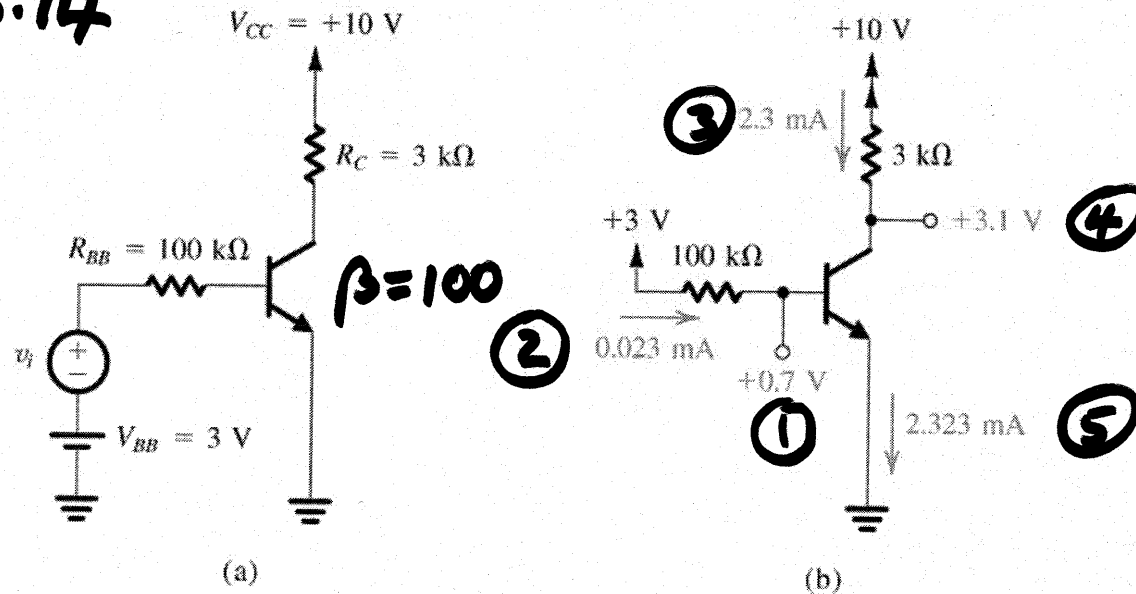

Hence

$$g_m = \frac{I_C}{V_T} = \frac{2.3\text{ mA}}{25\text{ mV}} = 92\text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{92\text{ mA}} = 1.09\text{ k}\Omega$$

$$v_{be} = \frac{1.09}{100 + 1.09} v_i$$

$$\text{So } v_o = -3\text{ k}\Omega \times 92\text{ mA} \cdot \frac{1.09}{101.09} v_i \approx -3.04 v_i$$

Figure 5.53 Example 5.14: (a) circuit; (b) dc analysis; (c) small-signal model.

Example 5.15 (Waveforms for Example 5.14)


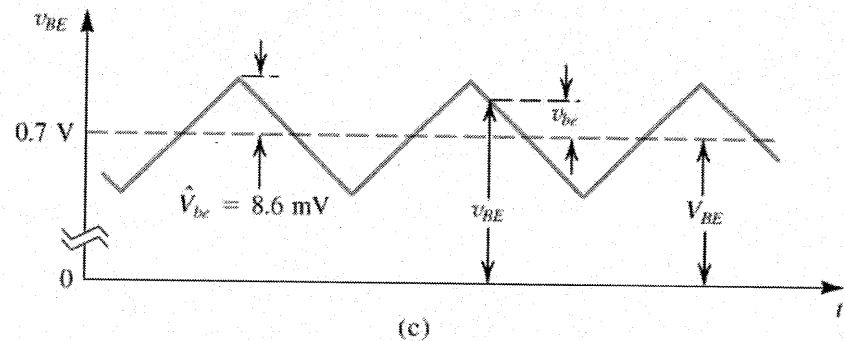
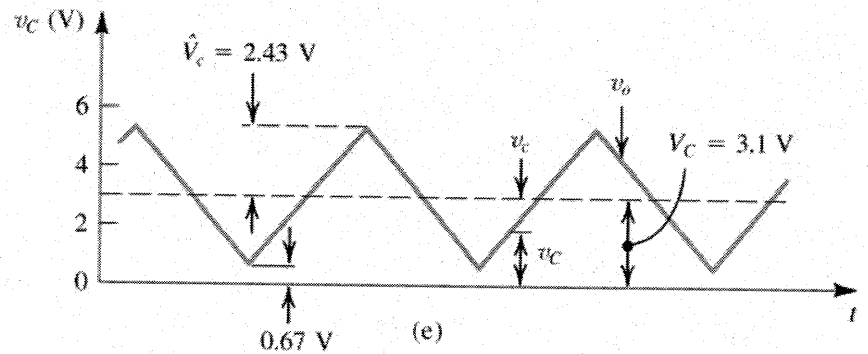
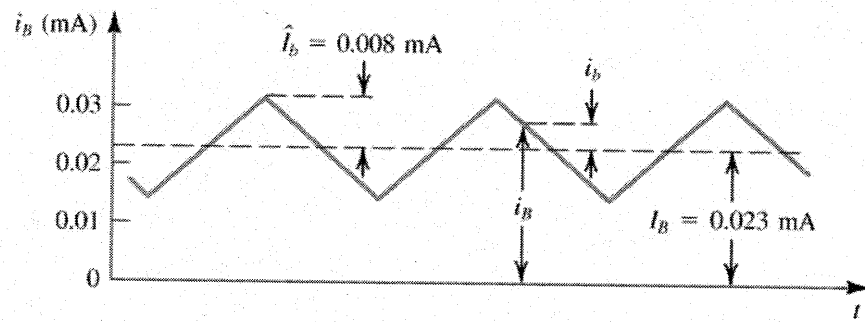
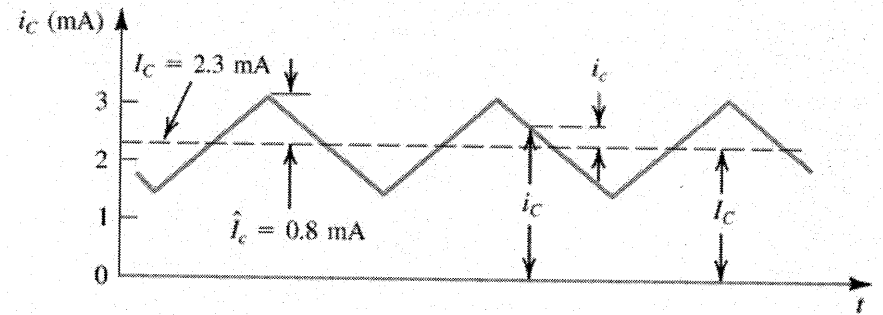
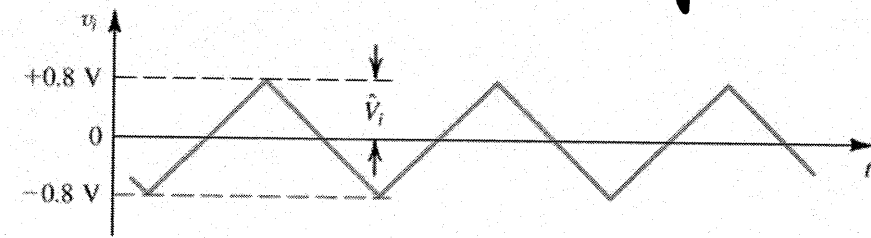
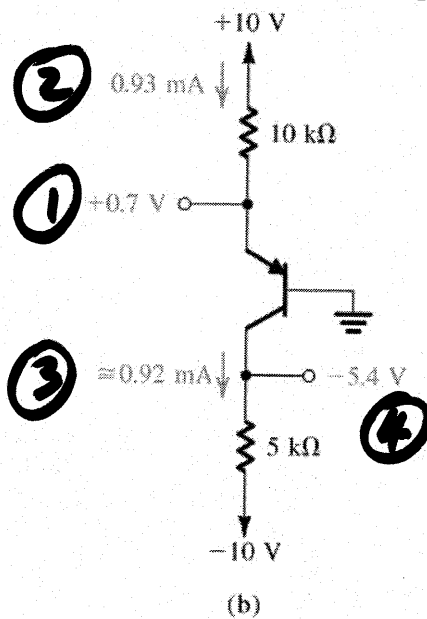


Figure 5.54 Signal waveforms in the circuit of Fig. 5.53.

PNP Common-Base


Input to E
Output from C.

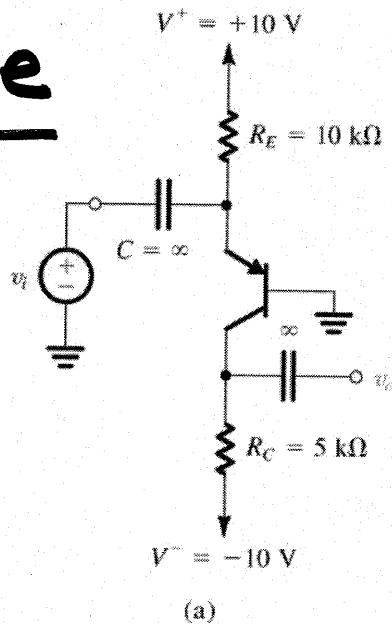

Small signal models :-

1. $X_C \rightarrow 0$
short circuit.


2. Concept of "AC ground"

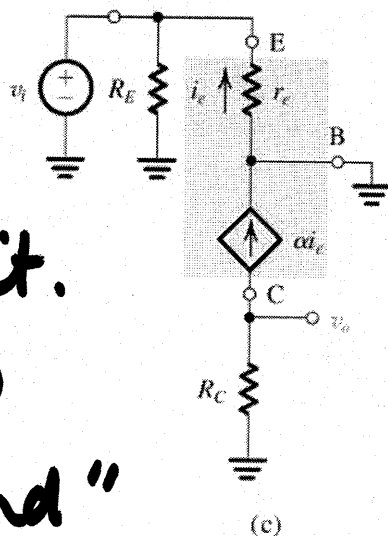

$$i_e = -\frac{v_i}{r_e}$$

$$v_o = -\alpha i_e R_C$$

$$= \frac{\alpha R_C}{r_e} v_i$$

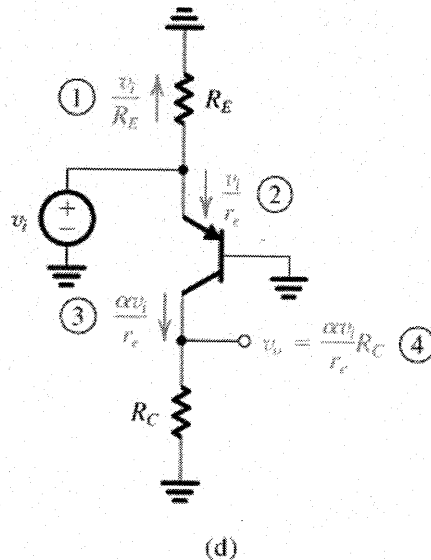

Example 5.16

Coupling capacitors

$$X_{DC} \rightarrow \infty$$

$$X_{AC} \rightarrow 0$$

Small signal analysis without/bypassing the small signal model.

Note:
Capacitors still S.C. &
 $V^+, V^- \rightarrow$ AC ground

Figure 5.55 Example 5.16: (a) circuit; (b) dc analysis; (c) small-signal model; (d) small-signal analysis performed directly on the circuit.


(a) Fixed DC \therefore AC signal = 0
(b) Power supply outputs:
Actually large C to ground.

Small signal model

Use to estimate large signal swing limitations etc!

BUT — clearly exceeding the limits of the small signal approximation, i.e. ignores device

Example 5.16

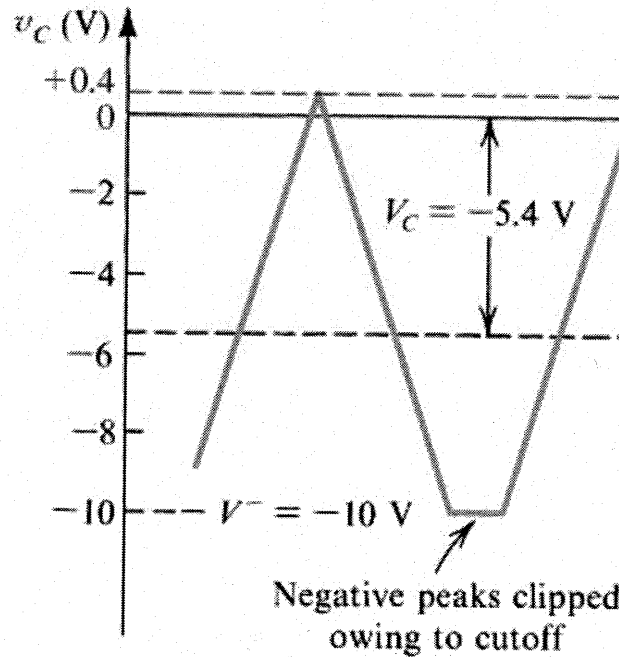

non-linearities

$$-5.4 \text{ V} = V_c$$

Max +ve swing
 $-5.4 \rightarrow +0.4$
 i.e. 5.8 V


But $-5.4 \text{ V} - 5.8 \text{ V} = -11.2 \text{ V}$

$$< V^- = -10 \text{ V}$$

\therefore Exceeds negative swing limit.

Figure 5.56 Distortion in output signal due to transistor cutoff. Note that it is assumed that no distortion due to the transistor nonlinear characteristics is occurring.

Example 5.46
Continued

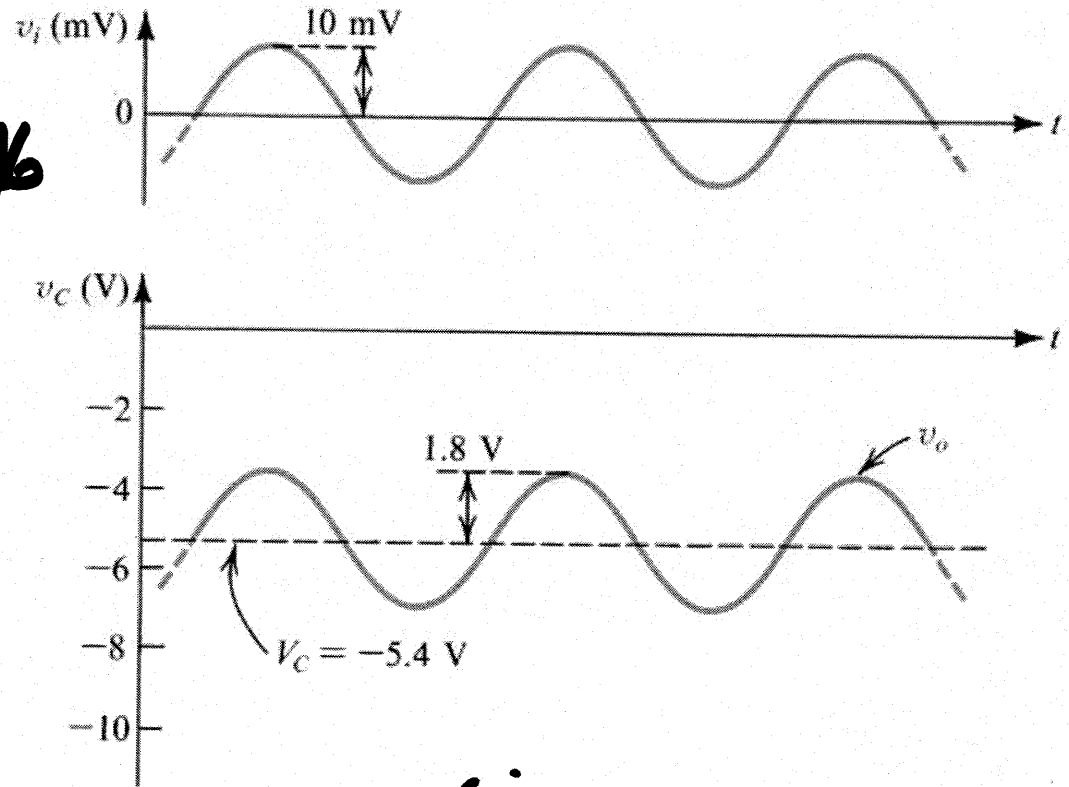

CB \rightarrow As $\left\{ \begin{matrix} v_i \\ v_{be} \end{matrix} \right\}$ incr, $\left\{ \begin{matrix} v_c \\ v_e \end{matrix} \right\}$ incr $\therefore \left\{ \begin{matrix} v_o \\ v_e \end{matrix} \right\}$ incr

Figure 5.57 Input and output waveforms for the circuit of Fig. 5.55. Observe that this amplifier is noninverting, a property of the common-base configuration.

\therefore output in phase with input

Add Early Effect to the Hybrid- π Model.
 $\longrightarrow r_o$

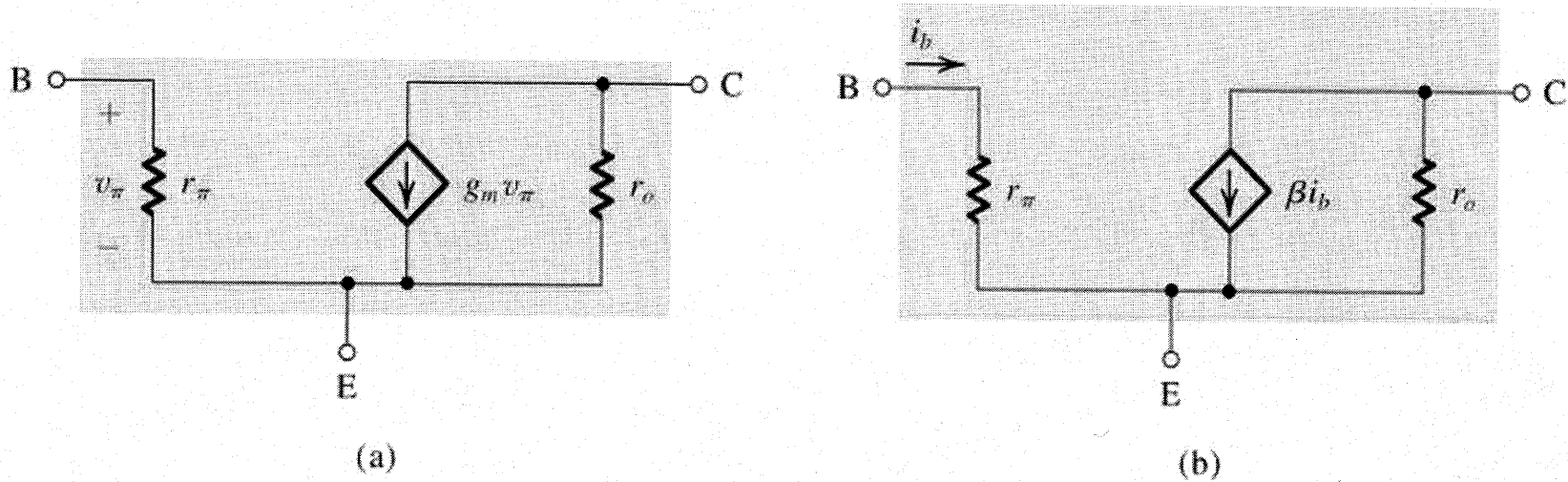


Figure 5.58 The hybrid- π small-signal model, in its two versions, with the resistance r_o included.

Exercise 5.40

$$g_m = \frac{I_c}{V_T}$$

$$r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_c} = \frac{\alpha}{g_m}$$

$$r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_c} = \frac{\beta}{g_m}$$

$$= (1 + \beta) r_e$$





&

$$\frac{1}{r_e} = \frac{1}{r_\pi} + g_m$$

Table 5.4

Small Signal Model Summary
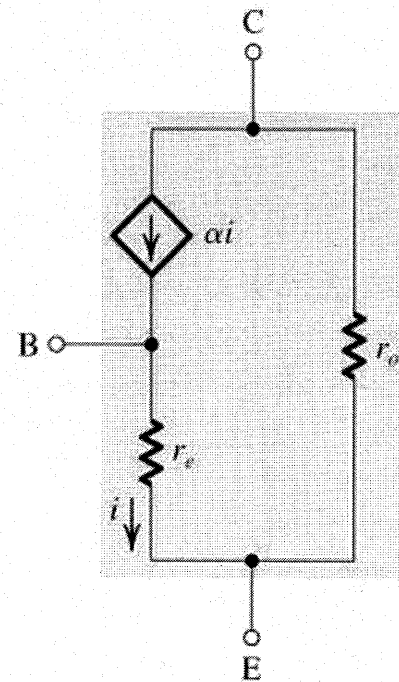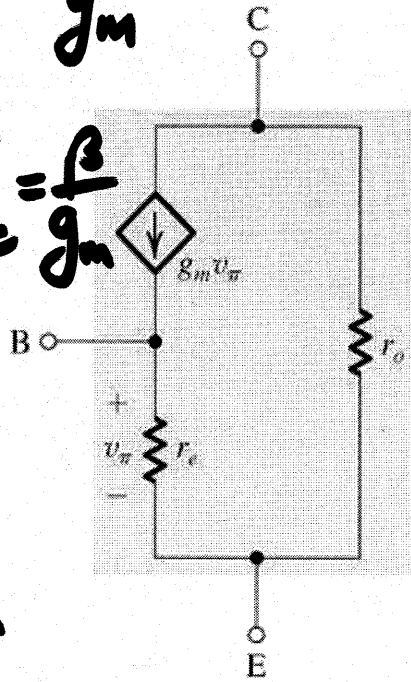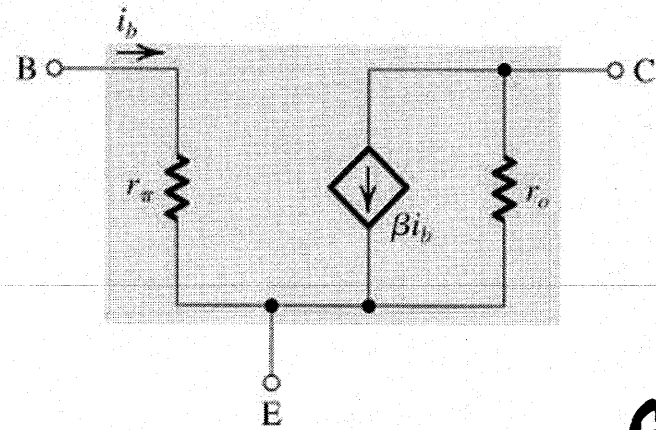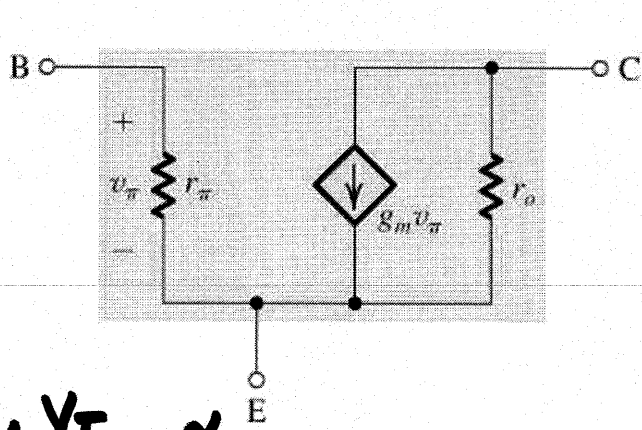
$$\frac{I_E}{V_T} = \frac{I_B}{V_T} + \frac{I_c}{V_T}$$



$$\beta = \frac{\alpha}{1 - \alpha}$$


$$\alpha = \frac{\beta}{1 + \beta}$$

$$1 + \beta = \frac{1}{1 - \alpha}$$

$$r_o \approx \frac{|V_A|}{I_c}$$

Ex 5.32 Refers to Example 5.13

Design sets $V_B = V_{CC}/3 = 4V$, so
 (neglecting V_{BE}) $V_{CE} \sim 1/3 V_{CC} \rightarrow 1/3 V_{CC} - V_{BE}$
 $V_{CC} - V_C \sim 1/3 V_{CC}$
 and $V_{CE} \sim 1/3 V_{CC}$ for signal swing

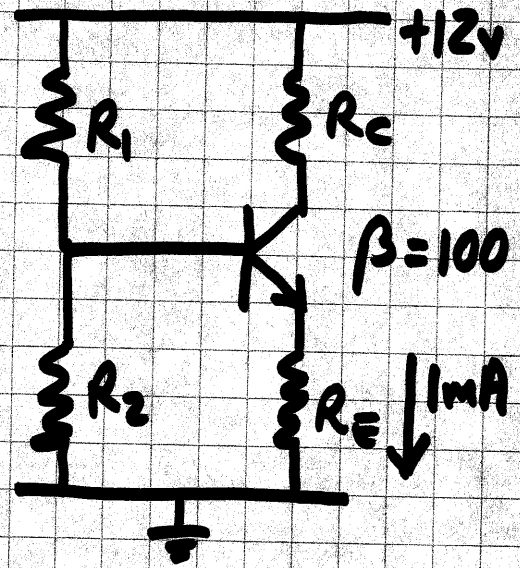

Example 5.13 \rightarrow Design 1

$$V_E = 4 - 0.7 = 3.3V$$

$$\therefore R_E = \frac{3.3V}{1mA} = 3.3K$$

$$\frac{V_{CC}}{R_1 + R_2} = 0.1 I_E = 0.1mA$$

$$\therefore R_1 + R_2 = \frac{12V}{0.1mA} = 120K$$

$$\& \frac{R_2}{R_1 + R_2} \approx \frac{4}{12} \text{ for } I_B \approx 0$$

$$R_1 = 80K \quad R_2 = 40K$$

Check on I_E :

$$\frac{4 - 0.7}{3.3K + \frac{(80||40)K}{101}} = 0.93mA \quad \text{Too low!}$$


So try Design 2

$$\frac{V_{CC}}{R_1 + R_2} = 1 \times I_E = 1mA \quad R_1 = 8K \quad R_2 = 4K$$

Check I_E :

$$\frac{4 - 0.7}{3.3K + \frac{(8||4)K}{101}} = 0.99mA \quad \text{OK!}$$

Ex 5.32 Check effect of β variation $100 \pm 50 = 50 \rightarrow 150$ on I_E as % I_{nom} for both designs.

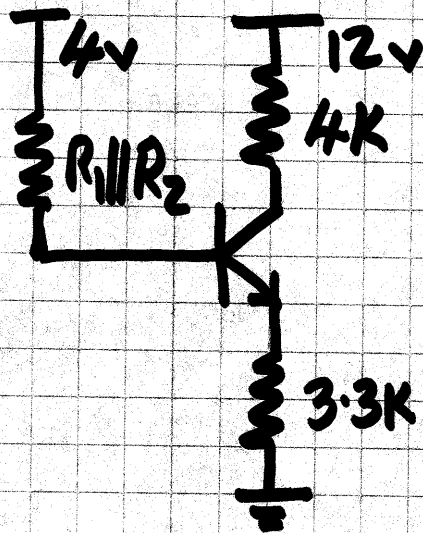

Design 1: $R_B = 40K // 80K = \frac{40 \times 80}{120} K = \frac{80K}{3}$

Design 2: $R_B = 4K // 8K = \frac{8K}{3}$


$I_E = ?$ formula or first principles

$$I_B = \frac{4 - 0.7 - 3.3K \times (1 + \beta) I_B}{R_B} = \frac{3.3 / R_B}{1 + \frac{3.3K(1 + \beta)}{R_B}}$$

$$\therefore I_E = (1 + \beta) I_B = \frac{3.3(1 + \beta)}{R_B + (1 + \beta)3.3K} = 3.3 / \left(3.3K + \frac{R_B}{1 + \beta} \right)$$

$\therefore I_E$	for $R_B = \frac{80K}{3}$, $\beta = 50 \rightarrow 0.86mA$	} Text answers for R_E changed to $3K$.
"	"	" $\beta = 100 \rightarrow 0.93mA$	
"	"	" $\beta = 150 \rightarrow 0.95mA$	
"	"	" $R_B = \frac{8K}{3}$	
"	"	" $\beta = 50 \rightarrow 0.98mA$	
"	"	" $\beta = 100 \rightarrow 0.995mA$	
"	"	" $\beta = 150 \rightarrow 0.995mA$	

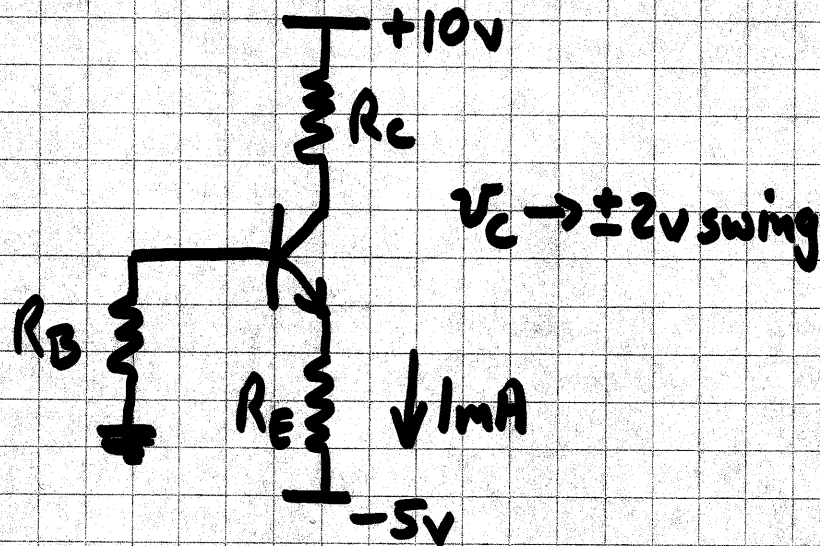Ex D.5.33 Design for max Common-Base gain
 & max collector signal swing $\pm 2\text{V}$.



CB \therefore base common
 & can use $R_B = 0$

$$\therefore V_E \approx -0.7\text{V}$$

$$\& R_E = \frac{-0.7\text{V} - (-5\text{V})}{1\text{mA}} = 4.3\text{K}$$

& for $I_C \approx I_E = 1\text{mA}$

$$\& V_C \text{ min value} = -0.7\text{V} + V_{CE(\text{SAT})} \leftarrow \text{onset} \approx -0.4\text{V}$$

$$2\text{V swing} \rightarrow V_C = -0.4 + 2\text{V} = 1.6\text{V}$$

$$\therefore R_C = \frac{10 - 1.6\text{V}}{1\text{mA}} = 8.4\text{K}$$

Ex 5.37 Typical values: Find g_m , r_e , r_{π} at bias $I_C = 1\text{mA}$
 ($\beta = 100$)

$$g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 40\text{mA/V}$$

$$r_e = \alpha/g_m \text{ or } V_T/I_E = \frac{0.99}{40\text{mA/V}} = 0.99(25\Omega) \approx 25\Omega$$

$$r_{\pi} = \beta/g_m \text{ or } V_T/I_B = \frac{100}{40\text{mA/V}} = 2.5\text{K}\Omega$$

Small Signal Voltage Gain

$$A_v = \frac{v_c}{v_{be}} = -g_m R_c$$

$$= -\frac{I_C}{V_T} R_c$$


$$v_c = V_{CC} - i_c R_c$$

$$= V_{CC} - (I_C + i_c) R_c$$

$$= v_c - i_c R_c$$

$$v_c = -i_c R_c = -(g_m v_{be}) R_c$$

Ex 5.38

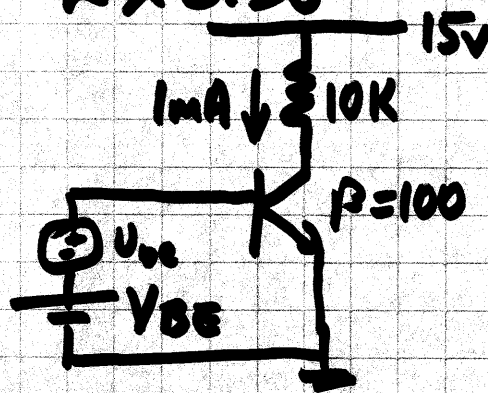

$$\frac{v_c}{v_{be}} = -\frac{1\text{mA}}{25\text{mV}} 10\text{K} = -400$$

$$v_{be} = 0.005 \sin \omega t \rightarrow v_c(t) = (15 - 1\text{mA} \times 10\text{K})\text{V} - 400 \times 0.005 \sin \omega t$$

$$= 5\text{V} - 2\text{V} \sin \omega t$$

$$i_B(t) = \frac{I_C}{\beta} + \frac{v_{be}}{r_{\pi}} = \frac{1\text{mA}}{100} + \frac{0.005 \sin \omega t}{100 / (1\text{mA} / 25\text{mV})} = 10 + 2 \sin \omega t \mu\text{A}$$

Ex 5.40 Transistor Early Voltage $V_A = 100V$

(a) Find V_B, V_E, V_C (b) Find g_m, r_π, r_o

(a) $I_B = \frac{I_E}{1+\beta} = \frac{1mA}{101} \therefore V_B = 0 - \frac{1mA}{101} 10K \approx -0.1V$

$\therefore V_E = -0.1V - 0.7V = -0.8V$

$V_C = 10 - 8K \times I_E \approx 10 - 8 \times 1$
 $\frac{2}{2} = 2V$

(b) $g_m = \frac{I_C}{V_T} \approx \frac{1mA}{25mV} = 40mA/V$

$r_\pi = \beta/g_m = \frac{100}{40 \times 10^{-3}} = 2.5K$

$r_o = \frac{102.8V}{1mA} = 102.8K\Omega \approx 100K\Omega$



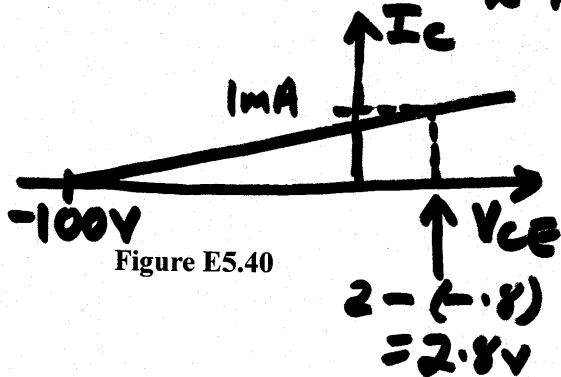


Figure E5.40

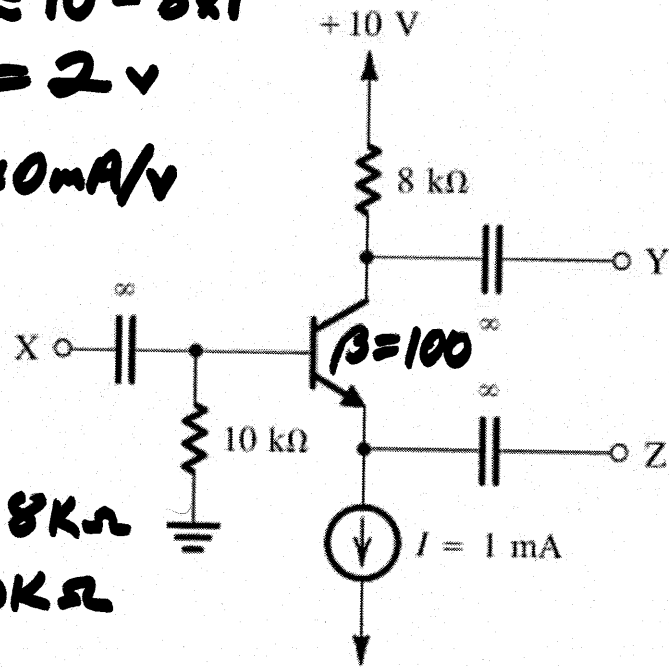

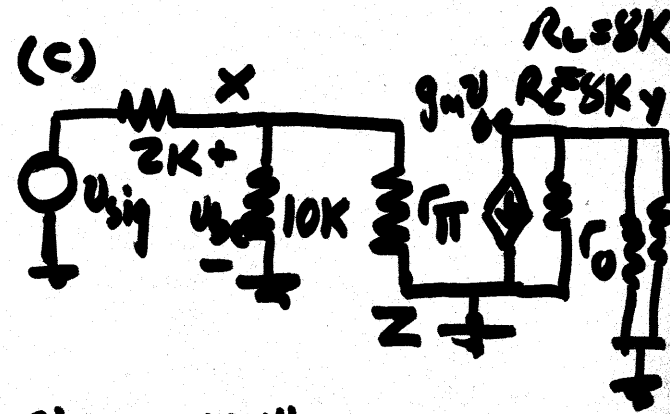(c) Z grounded, i.e. CE
 Input X: $v_{sig}, R_{sig} = 2K$
 Output Y: $R_L = 8K$. Find $\frac{v_y}{v_{sig}}$
 (d) Error if neglect r_o ?



$v_{be} = \frac{10K \parallel r_\pi}{2K + 10K \parallel r_\pi} v_{sig}$
 $(10K \parallel 2.5K = \frac{2.5 \times 10}{12.5} K = 2K)$

$\therefore v_{be} = v_{sig}/2$

$\therefore v_y = -g_m v_{be} (r_o \parallel R_L \parallel R_C)$
 $\frac{v_y}{v_{sig}} = -\frac{40 \times 10^{-3}}{2} \frac{400 \times 10^3}{104} = 76.9$

(d) Neglect $r_o \rightarrow \frac{40 \times 10^{-3}}{2} 4 \times 10^3 = 80, \sim 3.9\% \text{ error}$