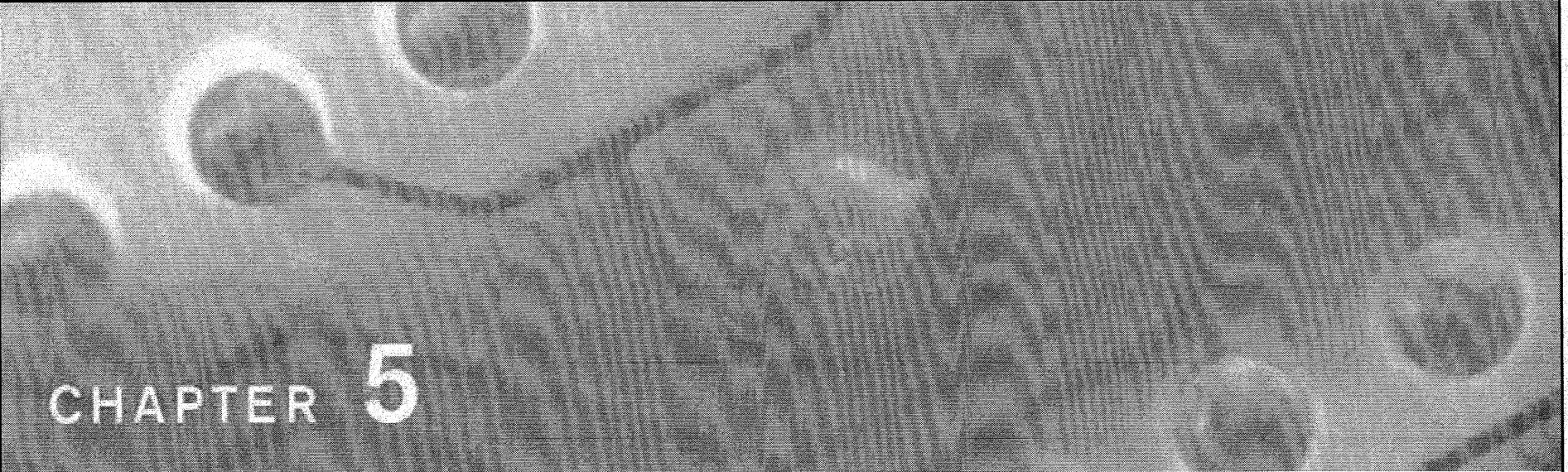


ECE321 ELECTRONICS I

FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 14
14th November, 2006




CHAPTER 5

Bipolar Junction Transistors (BJTs)

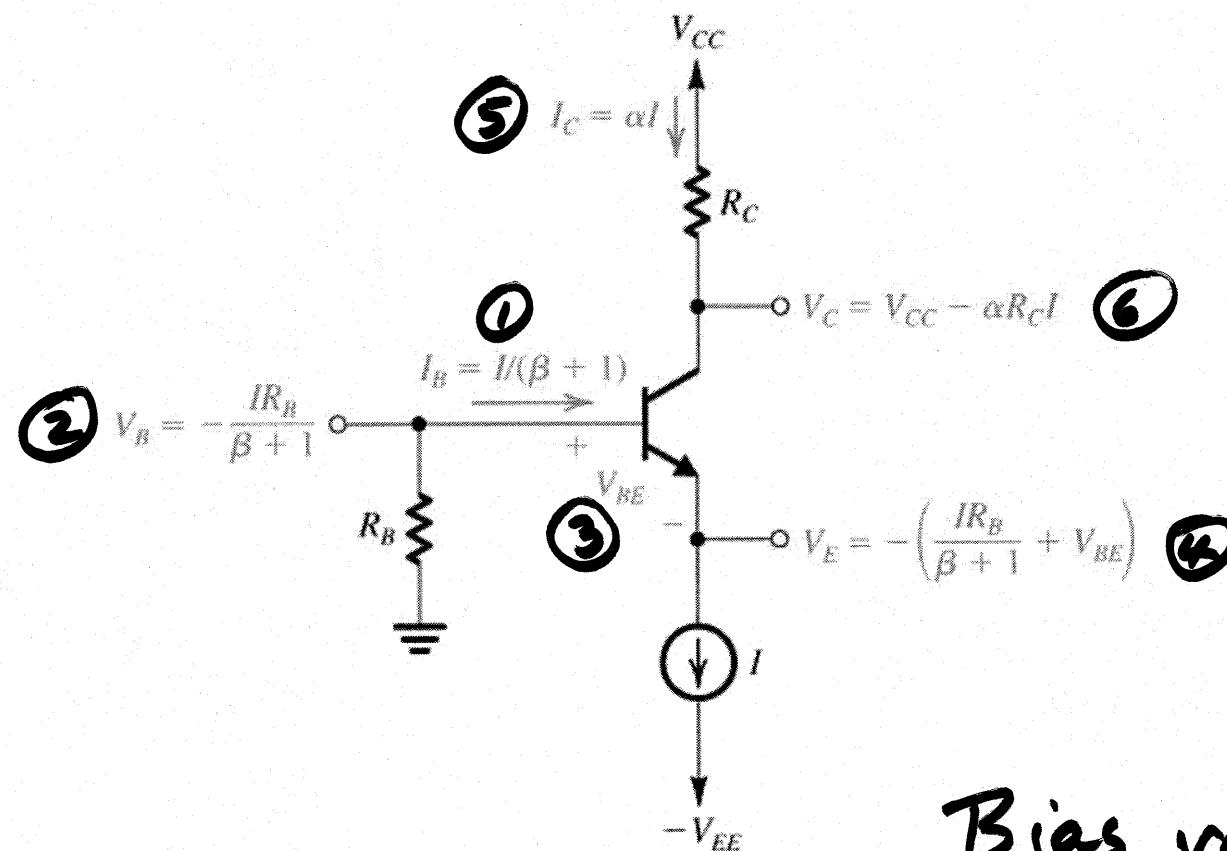5.7 Single Stage Amplifiers: CE, CB, & CC

Assume :-
2 supplies + ground
Emitter current source




Bias values

Figure 5.59 Basic structure of the circuit used to realize single-stage, discrete-circuit BJT amplifier configurations.


Exercise 5.41

Table 5.5 Compare Section 1.5 Unilateral amplifiers, extend to "non-unilateral amplifiers"


General circuit

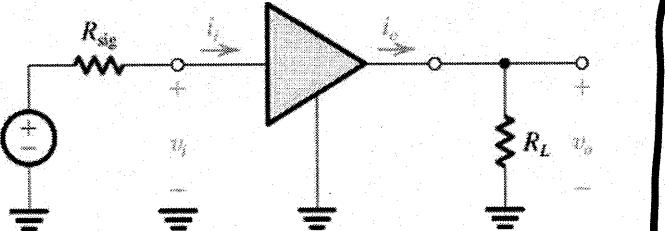




Compare

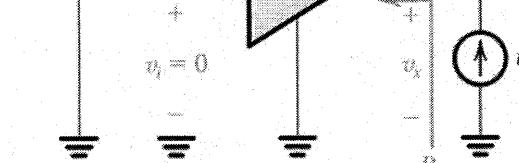
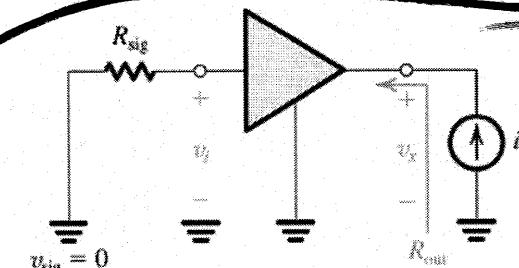
$$R_o = \frac{v_x}{i_x} \mid v_i=0 \quad \text{for "amplifier proper"}$$


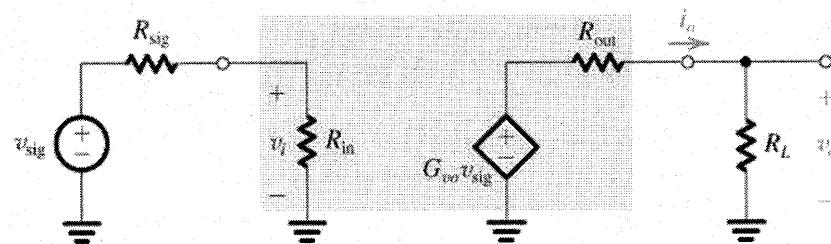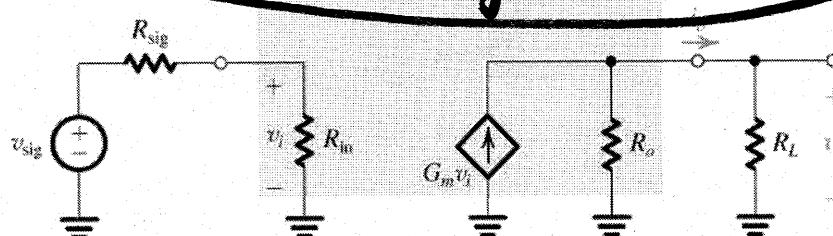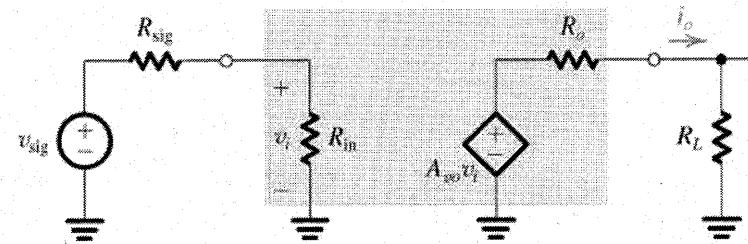
$$R_{out} = \frac{v_x}{i_x} \mid v_{sig}=0 \quad \text{includes } R_{sig}$$



Define : $R_i = v_i/i_i$, $A_v = v_o/v_i$, $A_i = i_o/i_i$
 "Overall" voltage gain $\mathcal{G}_v = v_o/v_{sig}$

Table 5.5

Unilateral $\rightarrow R_i, A_v, R_o$ fixed (R_i, R_o for "amplifier proper")


Non-unilateral $\rightarrow R_{in}, R_{out}, A_v$ may depend on R_s, R_L etc due to internal f.b.
 (R_{in}, R_{out} "actual" values, including R_s, R_L)

	Amplifier Proper	General	No-load Open Circuit g/p	Short Circuit Output
Input Resistance	$R_i = \frac{V_i}{i_i} \Big _{R_L \rightarrow \infty}$	$R_m = \frac{V_i}{i_i} \Big _{R_L \rightarrow \infty}$	$R_i = \frac{V_i}{i_i} \Big _{R_L = 0}$	
Voltage Gain	$A_v = \frac{V_o}{V_i} \Big _{i_o = 0}$	$A_v = \frac{V_o}{V_i} \Big _{i_o = 0}$	$A_{v0} = \frac{V_o}{V_i} \Big _{R_L \rightarrow \infty}$	N/A
Current Gain	$A_i = \frac{i_o}{i_i} \Big _{V_o = 0}$	$A_i = \frac{i_o}{i_i} \Big _{V_o = 0}$	N/A	$A_{is} = \frac{i_o}{i_i} \Big _{R_L \rightarrow \infty}$
Output Resistance	$R_o = \frac{V_x}{i_x} \Big _{V_i = 0}$	$R_{out} = \frac{V_x}{i_x} \Big _{V_{sig} = 0}$		
Overall Voltage Gain	N/A	$*G_v = \frac{V_o}{V_{sig}} \Big _{i_o = 0}$	$*G_{v0} = \frac{V_o}{V_{sig}} \Big _{R_L \rightarrow \infty}$	N/A
Transconductance			$G_m = \frac{i_o}{V_i} \Big _{R_L \rightarrow \infty}$	

* Note: G here is a voltage gain, not conductance units.

Small signal: $\frac{V_i}{V_{sig}} = R_{in}/(R_{in} + R_{sig})$

$$A_{v0} = G_m R_o$$

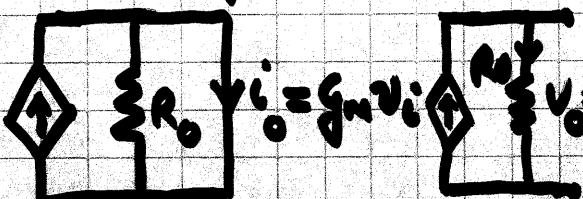


$$A_v = A_{v0} R_o / (R_o + R_d)$$

$$G_v = G_{v0} R_d / (R_d + R_{out})$$

$$G_{v0} = A_{v0} R_i / (R_i + R_{sig})$$

Exercise 5.42

CE Amplifier

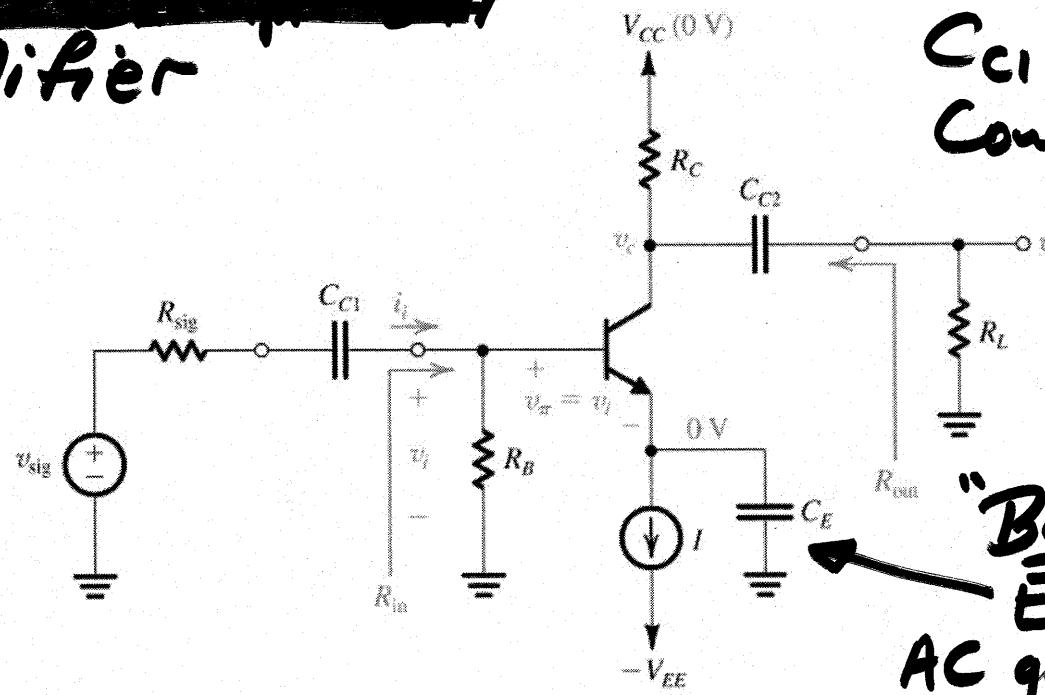

C_{C1}, C_{C2}
Coupling capacitors

"Bypass" capacitor
Establishes
AC ground for Emitter

Hybrid- π equivalent Circuit.

(a)

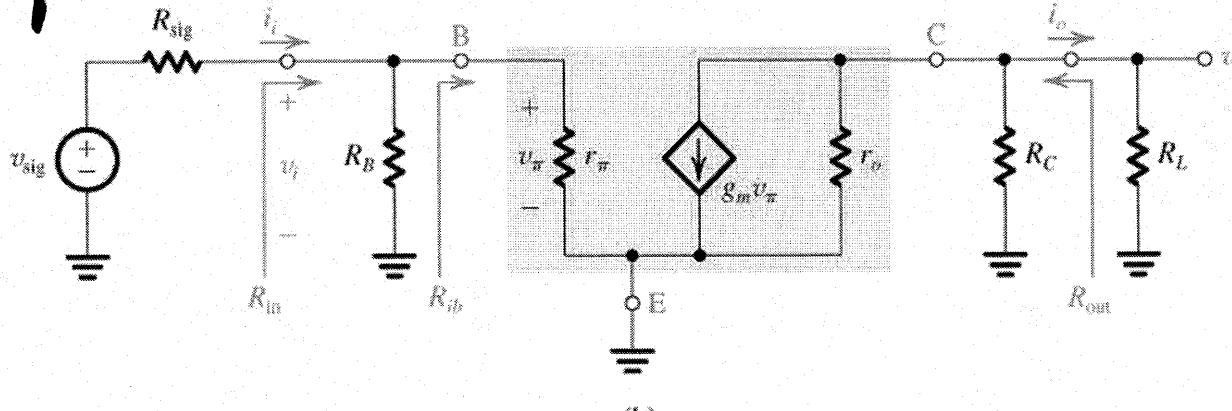


Figure 5.60 (a) A common-emitter amplifier using the structure of Fig. 5.59. (b) Equivalent circuit obtained by replacing the transistor with its hybrid- π model.

$$R_{in} = V_i / i_i = R_B \parallel R_{i'b} = R_B \parallel r_\pi \approx r_\pi \text{ for } R_B \gg r_\pi$$

$$\& V_i = V_{sig} \frac{R_{in}}{R_m + R_{sig}} = \frac{R_B \parallel r_\pi}{\cancel{R_B \parallel r_\pi} + R_{sig}} \approx \frac{r_\pi}{r_\pi + R_{sig}}$$

Text mis-print

$$= V_\pi$$

$$V_o = -g_m r_\pi (r_0 \parallel R_C \parallel R_L) \quad \therefore A_v = -g_m (r_0 \parallel R_C \parallel R_L)$$

$$\text{and } A_{v_o} \xrightarrow{R_L = \infty} -g_m (r_0 \parallel R_C)$$

Typically $r_0 \gg R_C$, so $A_{v_o} \rightarrow -g_m R_C$ & $A_v \rightarrow -g_m (R_C \parallel r_\pi)$

For R_{out} , set $V_{sig} = 0$, $\therefore V_\pi = 0$ $\therefore R_{out} = R_C \parallel r_0 \approx R_C$
 & $r_0 = R_{out}$ here

Note $A_v = A_{v_o} \frac{R_L}{R_L + R_0} = -g_m R_0 \frac{R_L}{R_L + R_0} = -g_m (R_L \parallel R_0) = -g_m (R_L \parallel R_C \parallel r_\pi)$

Checks with direct result above.

Overall source \rightarrow load $G_v = \frac{V_i}{V_{sig}} A_v = \frac{-R_B \parallel r_\pi}{R_{sig} + R_B \parallel r_\pi} g_m (r_0 \parallel R_C \parallel R_L)$

$\xrightarrow{R_B \gg r_\pi} -\frac{r_\pi}{R_{sig} + r_\pi} g_m (r_0 \parallel R_C \parallel R_L) \xrightarrow{R_{sig} \ll r_\pi} -g_m (r_0 \parallel R_C \parallel R_L)$

(Cont'd)

Note $G_V \approx \frac{-g_m r_\pi}{r_\pi + R_{sig}} (\rho_0 || R_L || R_C) \approx -\beta \frac{(R_L || R_C || r_0)}{r_\pi + R_{sig}}$


$\xrightarrow{R_{sig} \gg r_\pi} -\beta \frac{(R_L || R_C || r_0)}{R_{sig}}$ Very dependent on β

Signal source
looks like a
current source;
defines i_b

Voltage source
and $v_\pi \approx v_{sig}$

$\xrightarrow{R_{sig} \ll r_\pi} -\beta \frac{(R_L || R_C || r_0)}{r_\pi} = -g_m (R_L || R_C || r_0)$


Short circuit current gain

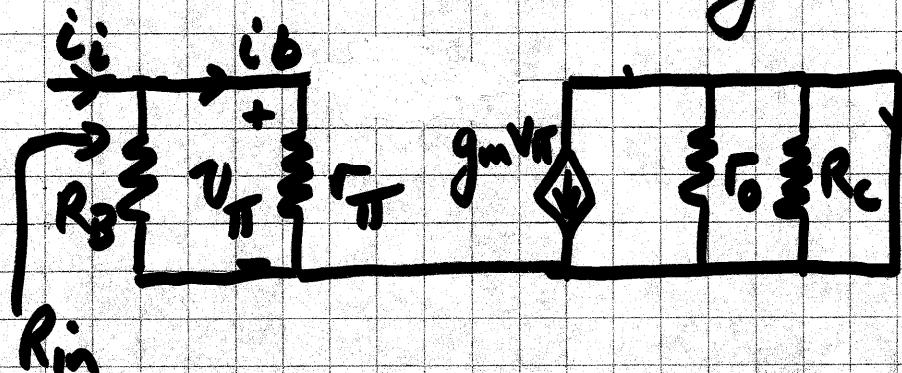


$$\begin{aligned} i_{osc} &= -g_m v_\pi = -g_m r_\pi i_o = -g_m R_{in} i_o \\ \therefore A_{i_o} &= \frac{i_{osc}}{i_o} = -g_m (R_B || r_\pi) \\ &\approx -g_m r_\pi \quad \text{for } r_\pi \gg R_B \\ &= -\beta \end{aligned}$$

CE Amplifier with R_E (Emitter "degenerated")

Example of
use of T-equivalent
circuit

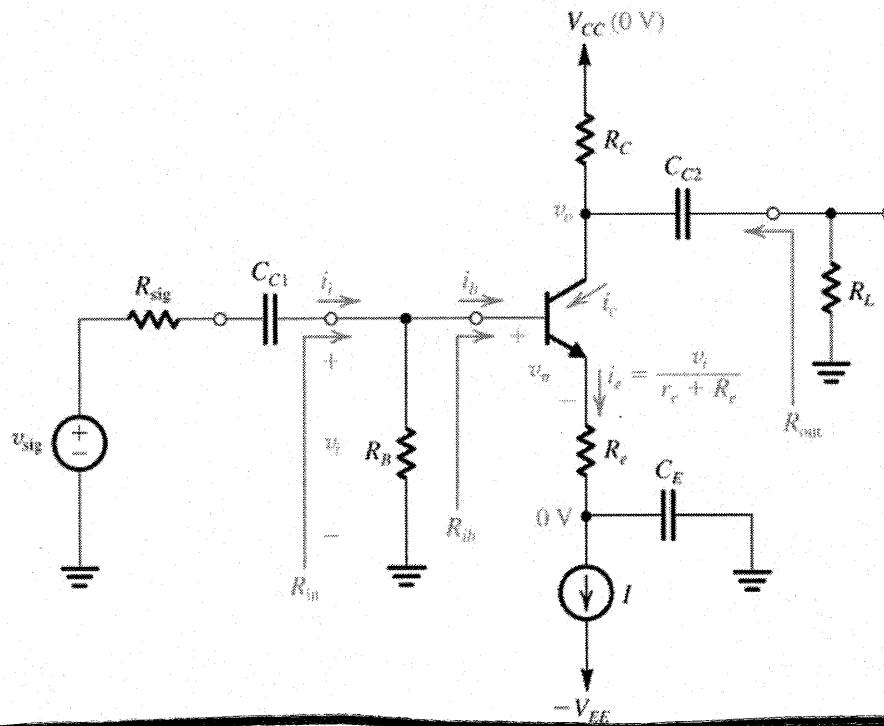
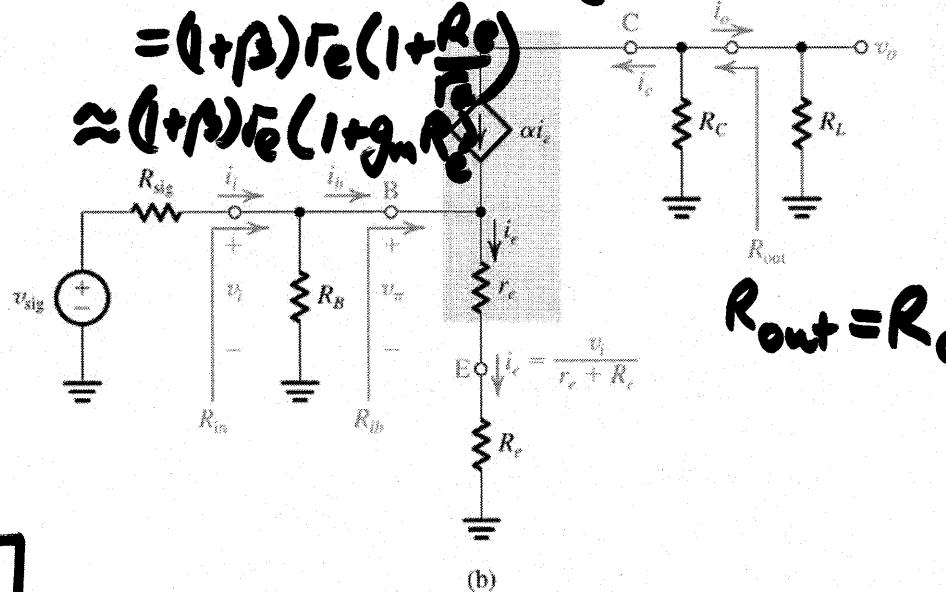
$$\begin{aligned} R_{ib} &= V_b / i_b = \frac{i_e (r_e + R_E)}{i_b} \\ &= (1 + \beta) (r_e + R_E) \\ &= (1 + \beta) r_e (1 + \frac{R_E}{r_e}) \\ &\approx (1 + \beta) r_e (1 + g_m R_E) \end{aligned}$$



$$R_{out} = R_C$$

R_{in} incr $\propto (1 + g_m R_E)$
 A_{V1} reduced $\propto (1 + g_m R_E)^{-1}$
 A_{V2} " " "
Av less dependent on β

Figure 5.61 (a) A common-emitter amplifier with an emitter resistance R_E . (b) Equivalent circuit obtained by replacing the transistor with its T model.

Improved frequency response (see later)

Gains decr $(1 + \frac{R_E}{r_e}) \approx 1 + g_m R_E$

$$\begin{aligned} A_V &= V_o / V_i = -i_c (R_C \parallel R_L) / V_i \\ &= -\alpha i_e (R_C \parallel R_L) \approx -\frac{R_C \parallel R_L}{i_e (r_e + R_E)} \approx \frac{R_C \parallel R_L}{r_e + R_E} \end{aligned}$$


$$A_{V0} \xrightarrow{R_L = \infty} -R_C / (r_e + R_E)$$

$$\& \frac{V_{II}}{V_i} = \frac{r_e}{r_e + R_E} = \frac{1}{1 + R_E/r_e} \approx \frac{1}{1 + g_m R_E}$$

Exercise 5.43

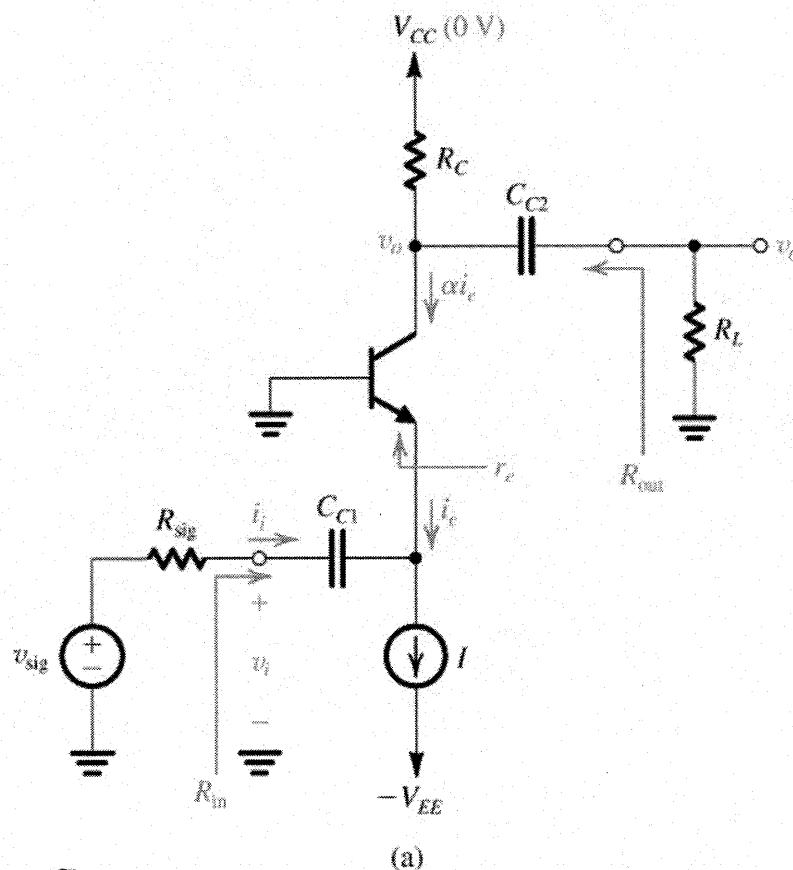Exercise 5.44

CB Amplifier → Input to Emitter
Output from Collector
Base grounded as common/
reference terminal




$$\textcircled{3} \quad A_{iS} = \frac{-\alpha i_e}{r_e} = \alpha$$

$$\textcircled{4} \quad \frac{v_i}{v_{sig}} = \frac{R_i}{R_i + R_{sig}}$$

Figure 5.62 (a) A common-base amplifier using the structure of Fig. 5.59. (b) Equivalent circuit obtained by replacing the transistor with its T model.
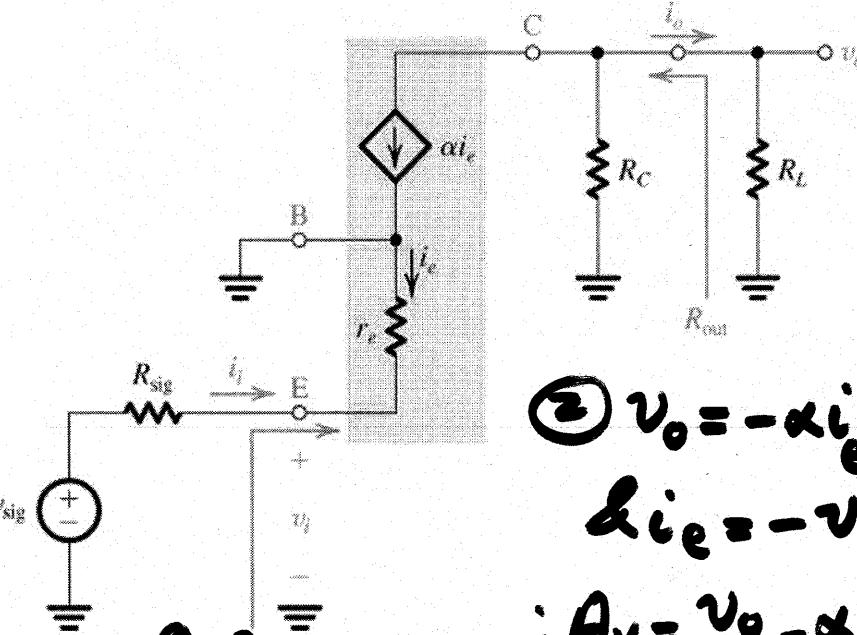
$$= \frac{r_e}{r_e + R_{sig}} \approx \frac{r_e}{R_{sig}} ??$$



$$\textcircled{2} \quad v_o = -\alpha i_e (R_C // R_L)$$

$$\alpha i_e = -v_i / r_e$$

$$\therefore A_v = \frac{v_o}{v_i} = \frac{\alpha}{r_e} (R_C // R_L)$$

$$= g_m (R_C // R_L)$$

Gives $A_v \xrightarrow{R_L = \infty} g_m R_C$



Also $R_{out} = R_C$

Small too, 50 or 75Ω if coax cable

Exercise 5.45

Exercise 5.46

Common Collector (CC) Amplifier

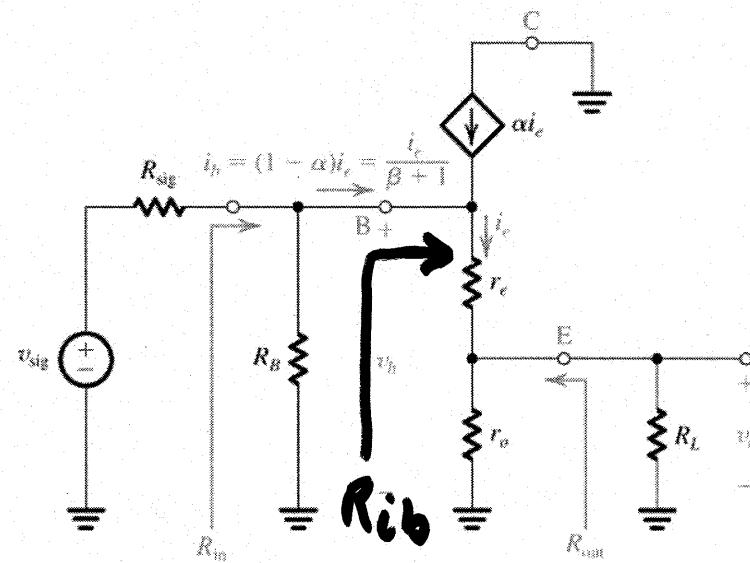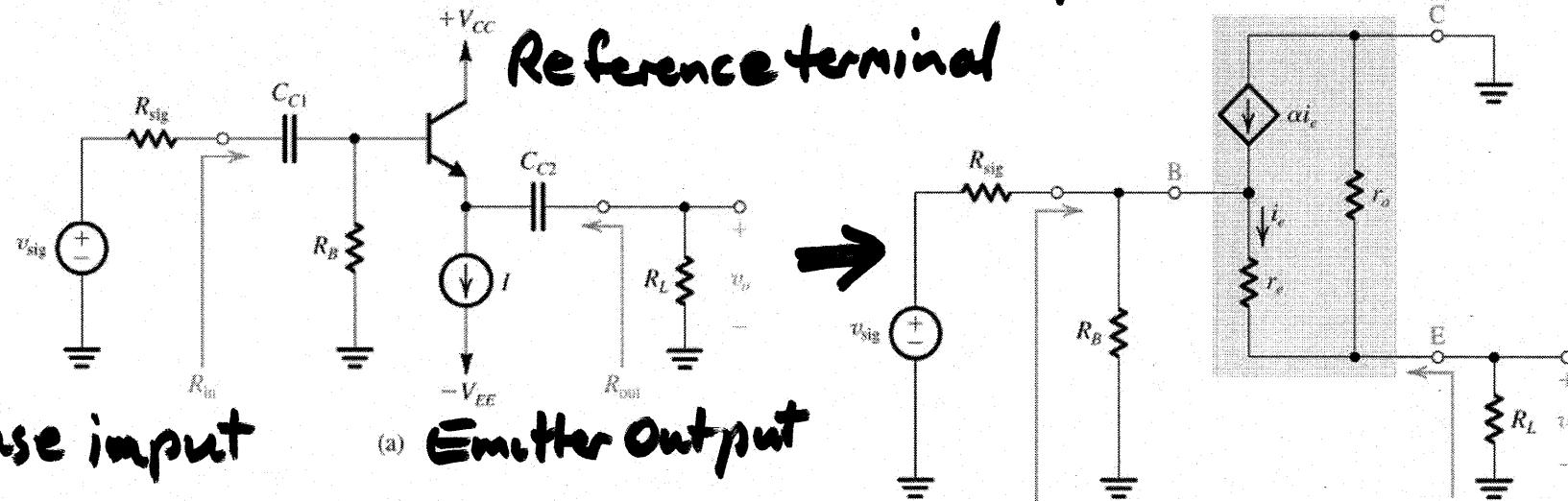


$$\begin{aligned}
 R_{ib} &= \frac{v_b}{i_b} \\
 &= \frac{i_e (\tau_e + \tau_0 || R_L)}{i_e / (1 + \beta)} \\
 &= (1 + \beta)(\tau_e + \tau_0 || R_L)
 \end{aligned}$$

Re-draw equivalent circuit ($\tau_0 || R_L$)

Figure 5.63 (a) An emitter-follower circuit based on the structure of Fig. 5.59. (b) Small-signal equivalent circuit of the emitter follower with the transistor replaced by its T model augmented with r_o . (c) The circuit in (b) redrawn to emphasize that r_o is in parallel with R_L . This simplifies the analysis considerably.

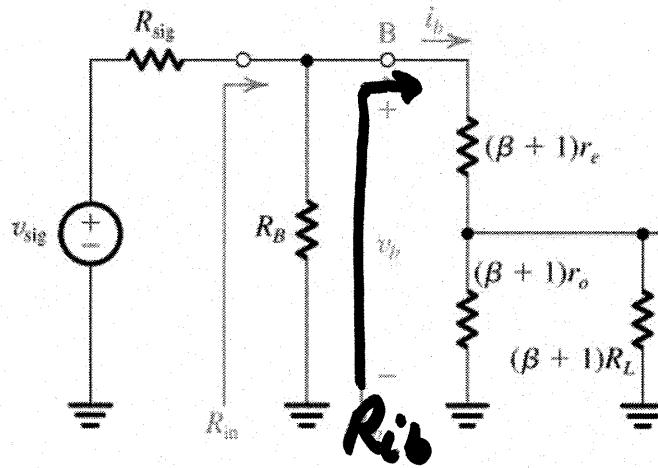
"Reflect" emitter resistances
to base circuit



$$R_{in} = R_B / ((\beta + 1)[r_e + (r_o / R_L)])$$

$$R_{in} = R_B / R_{ib}$$

Thevenin at B

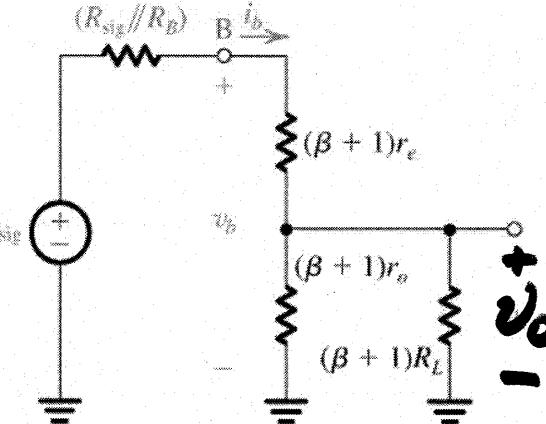


$$G_v = \frac{v_o}{v_{sig}} = \frac{R_B}{R_{sig} + R_B} \cdot \frac{(\beta + 1)(r_o / R_L)}{(R_{sig} / R_B) + (\beta + 1)[r_e + (r_o / R_L)]}$$

(a)
 $R_{in} = R_B / R_{ib}$
(b)
For $R_B \gg R_{sig}$
& $(1+\beta)(r_e + r_o / R_L) \gg (R_{sig} / R_B)$
 $G_v \rightarrow (r_o / R_L) / (r_e + r_o / R_L)$

Figure 5.64 (a) An equivalent circuit of the emitter follower obtained from the circuit in Fig. 5.63(c) by reflecting all resistances in the emitter to the base side. (b) The circuit in (a) after application of Thévenin theorem to the input circuit composed of v_{sig} , R_{sig} , and R_B .

"Emitter Follower"
(Compare Voltage follower) $\approx \frac{R_L}{r_e + R_L}$
 ≈ 1

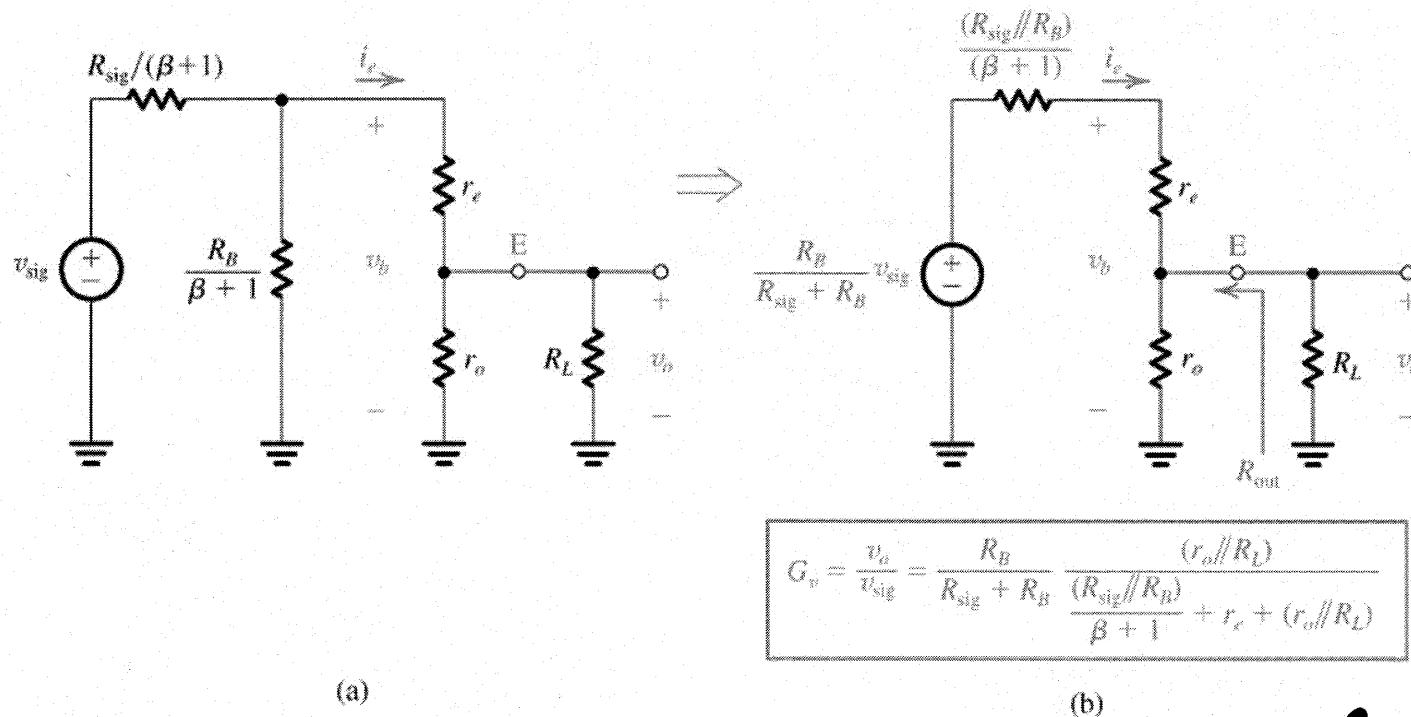Reflect Base resistances to Emitter circuit




$$G_v = \frac{v_o}{v_{sig}} = \frac{R_B}{R_{sig} + R_B} \frac{(r_o/R_L)}{\frac{(R_{sig}/R_B)}{\beta+1} + r_e + (r_o/R_L)}$$

$$R_{out} = r_o \parallel \left(r_e + \frac{R_{sig}/R_B}{1+\beta} \right)$$

Figure 5.65 (a) An alternate equivalent circuit of the emitter follower obtained by reflecting all base-circuit resistances to the emitter side. (b) The circuit in (a) after application of Thévenin theorem to the input circuit composed of v_{sig} , $R_{sig} / (\beta + 1)$, and $R_B / (\beta + 1)$.

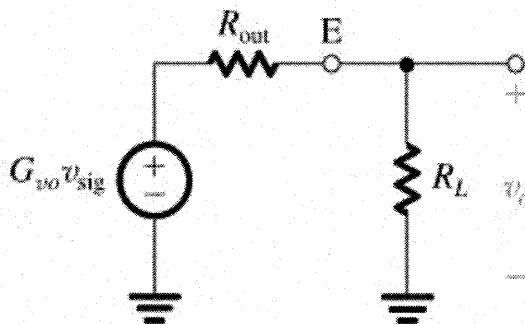Equivalent emitter follower (cc) output circuit




$$G_{vo} = \frac{R_B}{R_{sig} + R_B} \frac{r_o}{(R_{sig}/R_B) + r_e + r_o / (\beta + 1)}$$

$$R_{out} = r_o / \left(r_e + \frac{R_{sig}/R_B}{\beta + 1} \right)$$


Figure 5.66 Thévenin equivalent circuit of the output of the emitter follower of Fig. 5.63(a). This circuit can be used to find v_o and hence the overall voltage gain v_o/v_{sig} for any desired R_L .

Exercise 5.47


CE

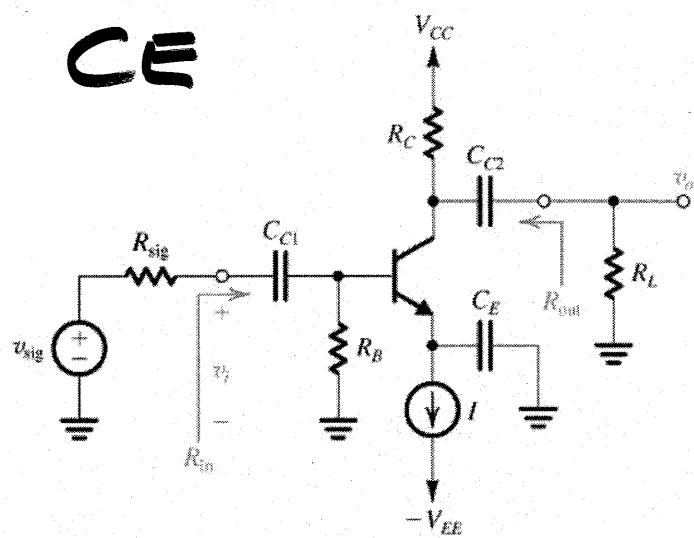

CE with R_E

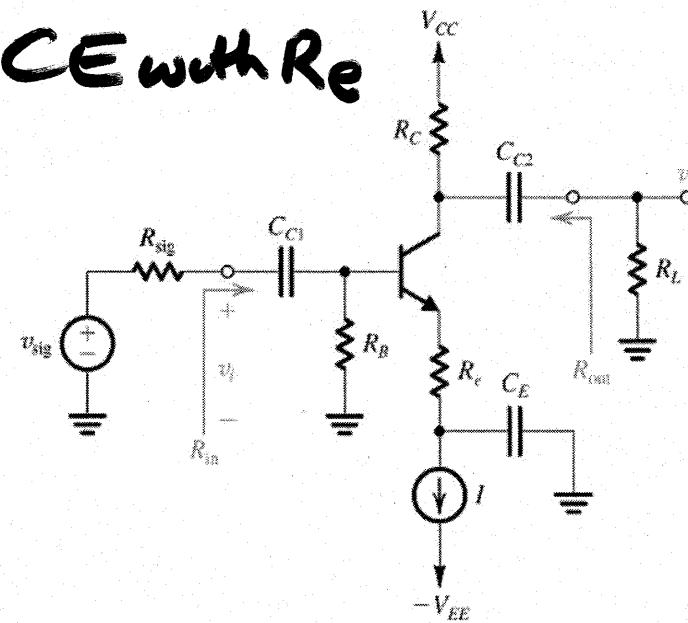

CB

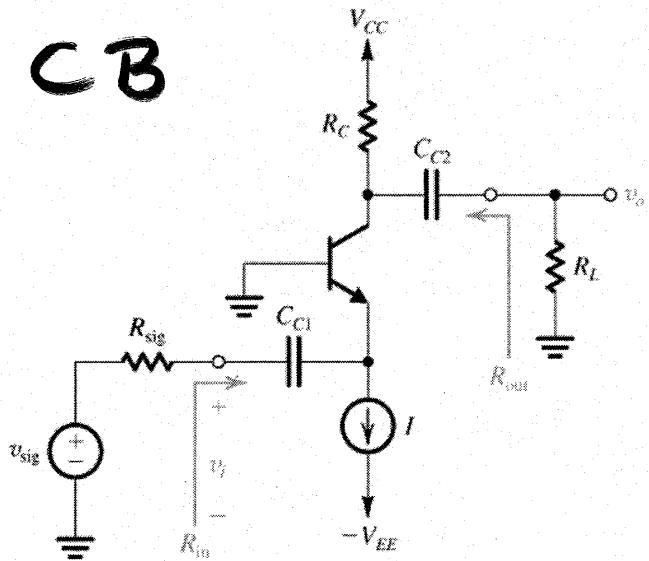

CC


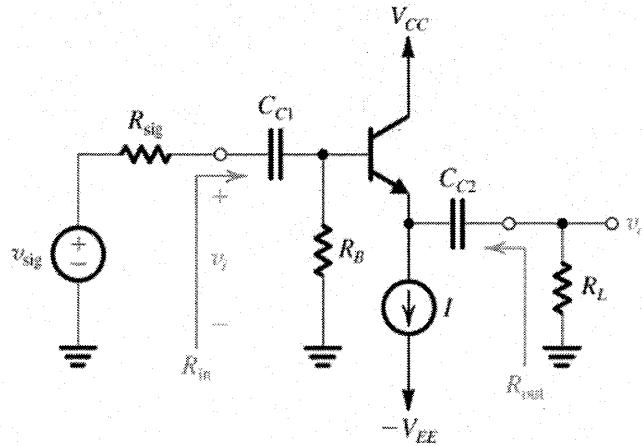
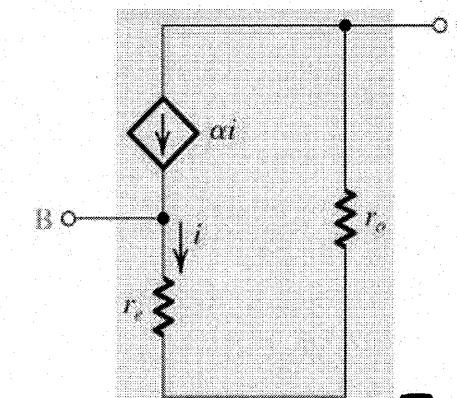
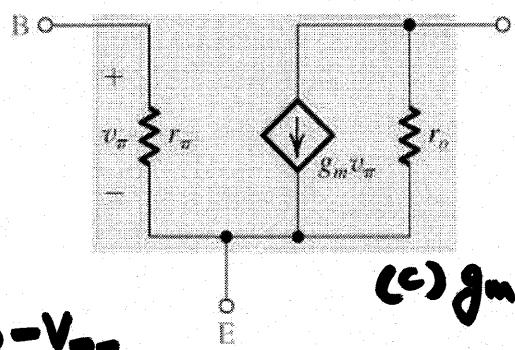


Table 5.6

Ex 5.41

(a) DC bias values

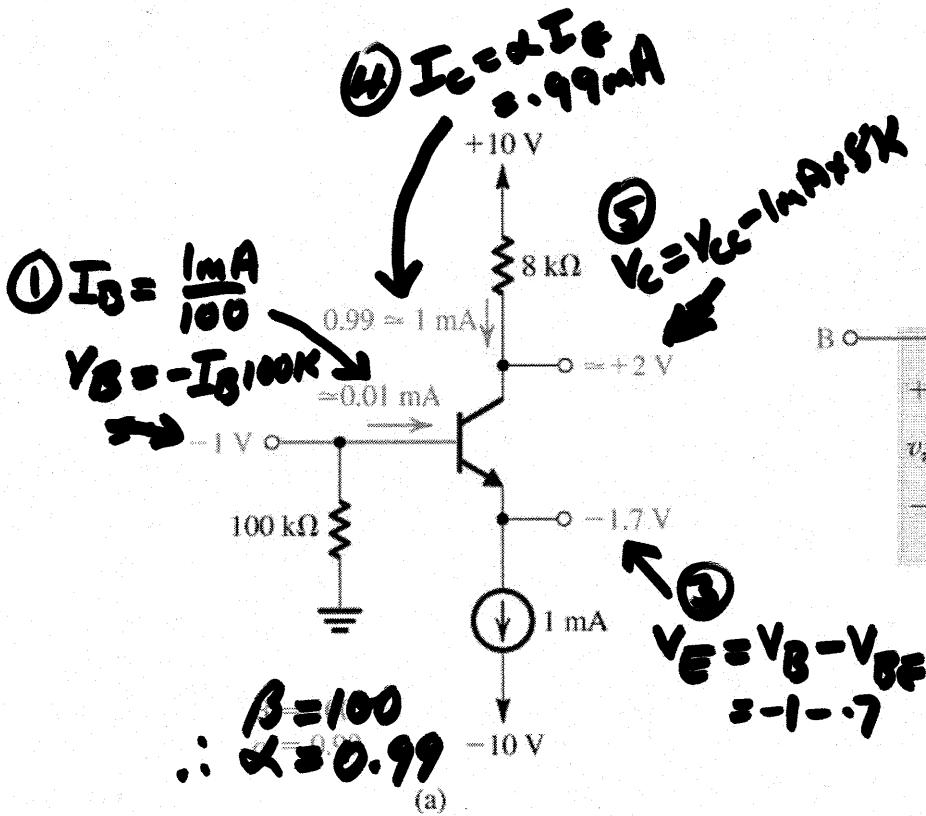

$$(c) g_m = \frac{I_m A}{25 \text{ mV}} = \frac{I_C / V_T}{I_C / V_T}$$

given as
100V

Early Voltage

$$V_A = 100 \text{ V}$$

$$g_m = 40 \text{ mA/V}$$

$$r_o = 100 \text{ kΩ}$$

$$r_e = 25 \text{ Ω}$$

$$r_e = 2.5 \text{ kΩ}$$

$$\begin{aligned} r_T &= \frac{\beta}{g_m} = \frac{100}{1 \text{ mA}/25 \text{ mV}} = \frac{V_T}{I_C} \\ r_e &= \frac{V_T}{I_C} \\ &= \frac{25 \text{ mA}}{1 \text{ mA}} \end{aligned}$$



Note: +ve swing same
+8V to Vce

(b) V_C can swing $+2 \text{ V}$ $+8 \text{ V}$ to 10 V
& $+2 \text{ V}$ -3.4 V to -1.4 V

$$\begin{aligned} \text{If } \beta \rightarrow 50 \quad I_B &= 0.02 \text{ mA} \quad V_B = -2 \text{ V} \quad V_E = -2.7 \text{ V} \quad V_C \text{ swing } +2 \text{ to } -2.4 \text{ V} = 4.4 \text{ V} \\ \beta \rightarrow 200 \quad I_B &= 0.005 \text{ mA} \quad -1.7 + V_{CE})_{SAT} \quad -0.5 \quad -1.2 \text{ V} \quad +2 \text{ to } -0.8 \text{ V} = -2.8 \text{ V} \end{aligned}$$

Figure E5.41

Ex 5.42 (See also Example 5.17)

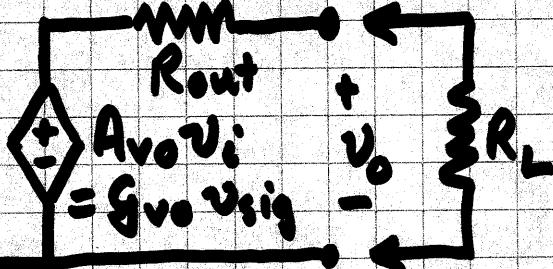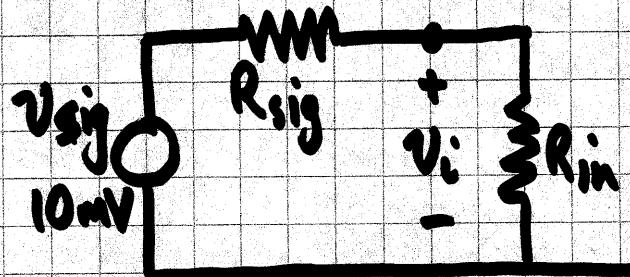

Find R_{in} , G_v , R_{out} for

$$(a) \quad R_{sig} = 200K \quad R_L = 10K$$

$$(b) \quad 100K \quad 20K$$

$$(c) \quad 200K \quad 20K$$

Example 5.17:

Measured for

	V_i	V_o
$R_L = \infty$	9mV	90mV
$R_L = 10K$	8mV	70mV
		$R_{sig} = 100K$

Use Example 5.17 measurement data to find :

$$R_L = \infty \quad \left\{ \begin{array}{l} A_{vo} = [V_o/V_i]_{R_L=\infty} = 90mV/9mV = 10 \quad \text{indep of } R_{sig}, R_L \\ G_{vo} = [V_o/V_{sig}]_{R_L=\infty} = 90mV/10mV = 9 \quad \text{depends on } R_{sig} \end{array} \right.$$

$$\left(R_i = R_{in} \right)_{R_L=\infty} \Rightarrow G_{vo} = \frac{R_i}{R_i + R_{sig}} A_{vo} \quad \therefore R_i = R_{sig} \left(\frac{A_{vo}}{G_{vo}} - 1 \right)^{-1}$$

$$= 100K \left(\frac{10}{9} - 1 \right)^{-1} \\ = 900K$$

independ of R_{sig}, R_L

Ex 5.42 (contd.)

$$R_L = 10K\Omega \left\{ \begin{array}{l} A_v = 70mV/8mV = 8.75 \\ g_v = 70mV/10mV = 7 \end{array} \right.$$

And $A_v = A_{vo} \frac{R_L}{R_L + R_o}$ gives $R_o = R_L (A_{vo} - A_v) / A_v$

$$\begin{aligned} &= R_L (A_{vo}/A_v - 1) \\ &= 10K (10/8.75 - 1) \\ &= 1.43 K\Omega \end{aligned}$$

& $R_o = [v_x/i_x]_{v_i=0}$ is independent of R_{sig}

$$g_v = g_{vo} \frac{R_L}{R_L + R_{out}}$$

gives $R_{out} = R_L (g_{vo}/g_v - 1) = 10K (9/7 - 1) = 2.86 K\Omega$

$$\& R_{out} = [v_x/i_x]_{v_{sig}=0}$$

Also

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}$$
 i.e. for $R_{sig} = 100K$ $\frac{8mV}{10mV} = \frac{R_{in}}{R_{in} + 100K}$
 $R_L = 10K$

gives $R_{in} = \frac{0.8 \times 100K}{10K} = 400K$

Ex 5.42 (cont'd.)

(a) $R_{sig} = 200K$ $R_L = 10K$ (b) $R_{sig} = 100K$ $R_L = 20K$ (c) $R_{sig} = 200K$ $R_L = 20K$

R_{in} independent of R_{sig}
 $\therefore R_m = 400K$, as for
 5.17

$$G_V = \frac{R_{in}}{R_{in} + R_{sig}} \cdot A_{vo} \cdot \frac{R_L}{R_L + R_0}$$

$$= \frac{400}{400+200} \cdot 10 \cdot \frac{10}{10+1.43}$$

$$= 5.83$$

$$\& G_{vo} = \frac{R_i}{R_i + R_{in}} A_{vo}$$

$$= \frac{900}{900+200} \cdot 10 = 8.18$$

$$R_{out} = R_L (G_{vo}/G_V - 1)$$

$$= 10K (8.18/5.83 - 1)$$

$$= 4.03K\Omega$$

R_{out} independent of R_L
 $\therefore R_{out} = 2.86K\Omega$
 as for 5.17

$$G_{vo} = G_{vo} \frac{R_L}{R_L + R_{out}}$$

$$= 9 \frac{20}{20+2.86} = 7.87$$

$$G_V = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_0}$$

$$7.87 = \frac{R_{in}}{R_{in} + 100K} 10 \frac{20}{20+1.43}$$

$$\text{gives } R_{in} = 538K\Omega$$

$R_{in} = 538K\Omega$ as
 for (b)

$R_{out} = 4.03K\Omega$ as
 for (a)


$$G_{vo} = 8.18 \text{ as for (a)}$$

$$\therefore G_V = G_{vo} \frac{R_L}{R_L + R_{out}}$$

$$= 8.18 \frac{20}{20+4.03}$$

$$= 6.8$$

Ex 5.43

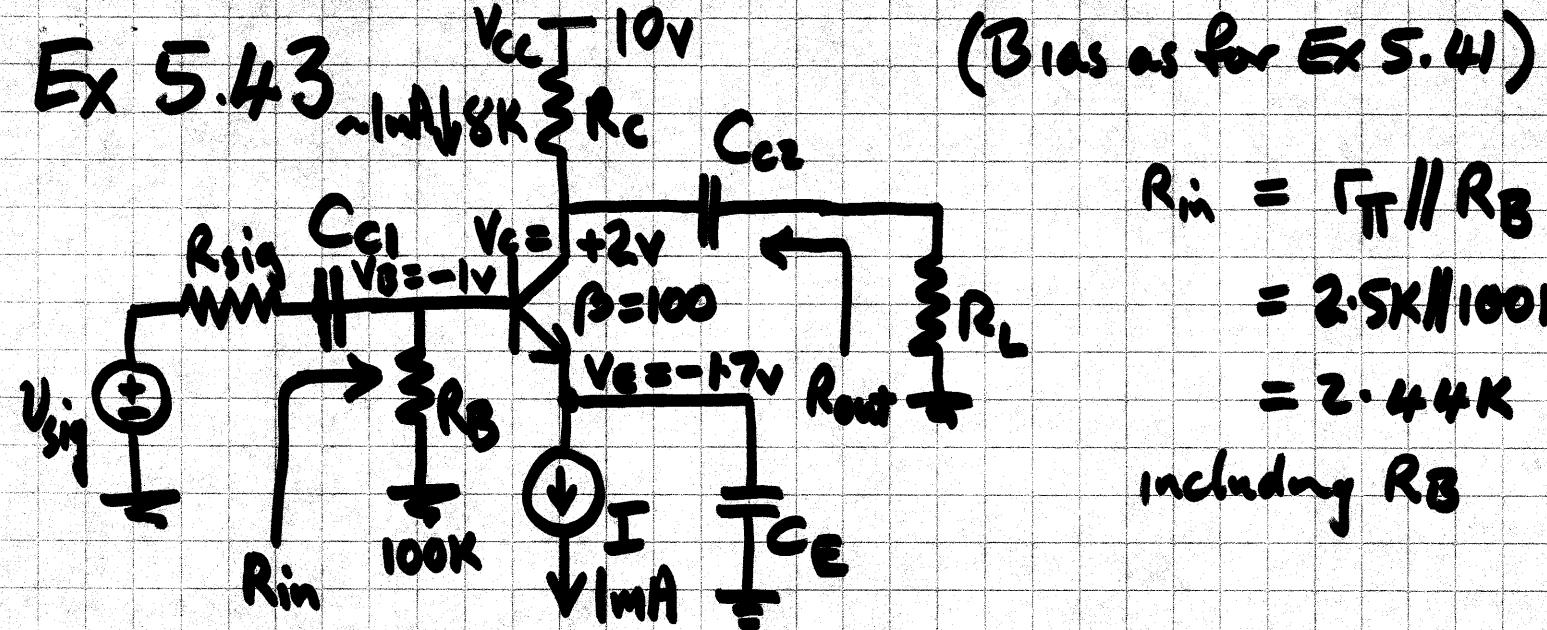

(Bias as for Ex 5.41)

$$\begin{aligned}
 R_{in} &= r_\pi \parallel R_B \approx r_\pi \\
 &= 2.5k \parallel 100k = \frac{V_T}{I_B} \\
 &= 2.44k \\
 \text{including } R_B &= \frac{25mV}{1mA \times 10} \\
 &\approx 2.5k \Omega \\
 \text{neglecting } R_B &
 \end{aligned}$$

$$\begin{aligned}
 A_{VO} &= \frac{V_O}{V_{sig}} = \frac{g_m R_C}{r_\pi} = \frac{I_c}{V_T} \cdot \frac{1mA}{25mV} = 40 \times 10^{-3} \text{ A/V} \\
 &\therefore A_{VO} = -g_m R_C = -40 \times 10^{-3} \times 8 \times 10^3 = -320 \\
 \text{Or with } r_o & A_{VO} \rightarrow -g_m (R_C \parallel r_o) \quad \left\{ \begin{array}{l} \text{Ex 5.41} \\ V_A = 100V \end{array} \right. \\
 &= 296 \quad \left\{ \begin{array}{l} r_o = 100k \\ V_A = 100V \end{array} \right.
 \end{aligned}$$


$$\begin{aligned}
 A_{IS} &= \frac{-g_m V_T}{V_T / (r_\pi \parallel R_B)} = -g_m (r_\pi \parallel R_B) \approx -g_m r_\pi = -40 \times 10^{-3} \times 2.5k \quad \left\{ \begin{array}{l} r_\pi = 100k \\ R_B = 100k \end{array} \right. \\
 &= -40 \times 10^{-3} \times \frac{2.5 \times 10^3}{102.5k} = -100 \\
 &= -97.5
 \end{aligned}$$

$$\text{For } R_L = 5k \quad A_V = \frac{5k}{5k + 7.4k} (-296) = -119.4$$

$$\begin{aligned}
 R_{out} &= r_o \parallel R_C \approx R_C = 8k \\
 &= \frac{800k}{108} = 7.4k
 \end{aligned}$$

$$\text{For } R_{sig} = 5k \quad G_V = \frac{5k}{5k + 2.44k} (-119.4) = 37.15$$

Ex 5.44

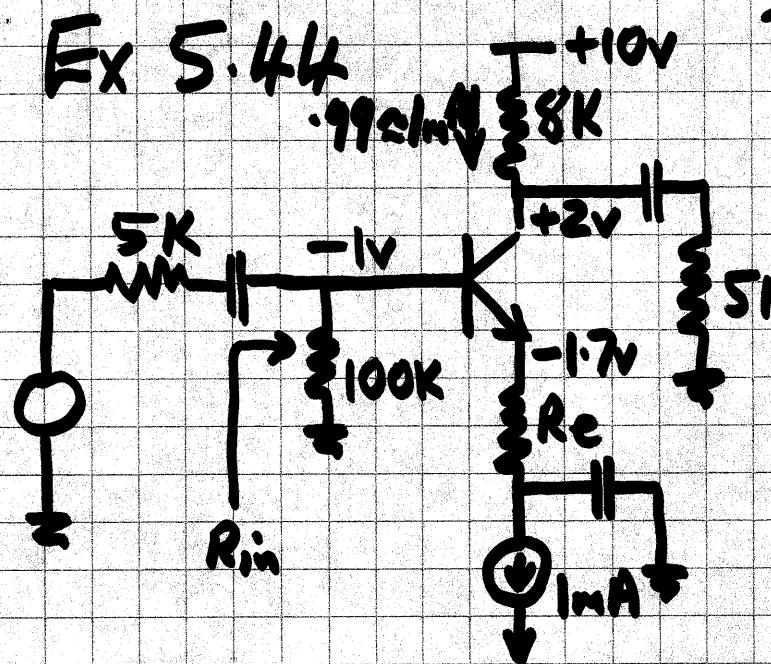

BJT: $\beta = 100$ $V_A = 100V$

Find R_C for $R_{in} = 20k$

$$R_{in} = 100k \parallel (1+\beta)(r_e + R_C) = 20k$$

$$\therefore (1+\beta)(R_C + r_e) = 25k$$

$$R_C + r_e \approx 250$$

$$r_e = \frac{V_T}{I_C} = 25\Omega \quad \therefore R_C = 225\Omega$$

$$A_{vo} = -\frac{8k}{250\Omega} = -32$$

$$R_{out} = R_C = 8k$$



$$A_v = -\frac{R_L \parallel R_C}{R_C + r_e} = -\frac{8k \parallel 5k}{250} = -\frac{-3.077k}{250} = -12.308$$

$$S_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{-20}{20+5} 12.31 = -9.84$$

$$A_{cs} = -\alpha \frac{R_B \parallel R_{ib}}{r_e + R_C} \approx -0.99 \frac{20k}{250\Omega} = -0.99 \times 80 = -79.2$$

$$\text{For max } V_T = 5mV \quad \text{Max } V_{sig} = \frac{5k + 20k}{20k} 5mV \frac{250}{25} = 62.5mV$$
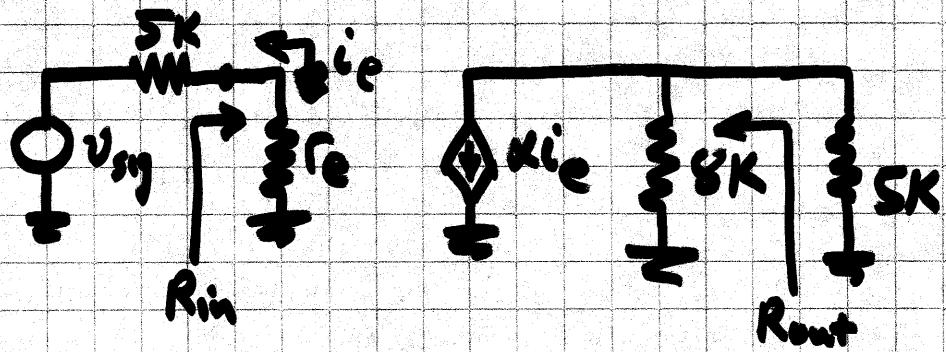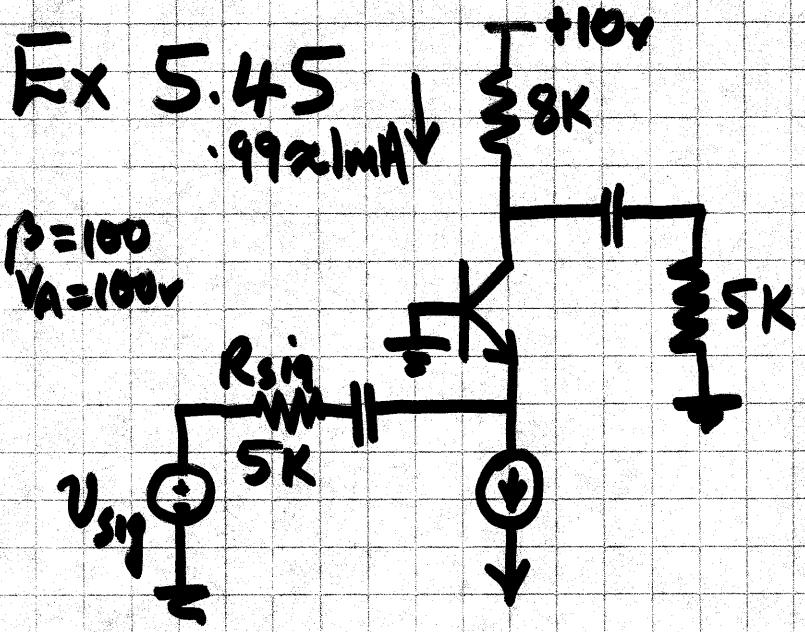
$$\Rightarrow \frac{5k + 2.5k}{2.5k} 5mV = 15mV \text{ without } R_C$$



$$R_{in} = r_e = \frac{V_T}{I_E} = \frac{25mV}{1mA} = 25\Omega$$

$$A_{v0} = -\frac{\alpha i_c 8k}{i_c r_e} = +0.99 \frac{8k}{25}$$

$$\approx 320$$

$$R_o = 8k$$

$$A_V = -\frac{\alpha i_c (8k || 5k)}{i_c r_e} \approx \frac{3.077k}{25} = 123.08$$

$$\frac{v_i}{v_s} = \frac{25}{5k + 25} \approx 5 \times 10^{-3}$$

$$g_v = 5 \times 10^{-3} A_V = .6155$$

For $g_v \rightarrow 39$, need $123 \times \frac{25}{R_s + 25} = 39$ i.e. $R_s = 53.8\Omega$

D5.46 Design CB amplifier for $R_S = 50\Omega$ (coax)
 $G_V = 100$

For matching, need $r_e = 50\Omega$


$$\therefore \frac{V_T}{I_E} = 50\Omega, I_E = \frac{25mV}{50\Omega} = 0.5mA$$

$$\therefore G_V = \frac{50}{50+50} \frac{R_C}{50} = 100 (\alpha \approx 1)$$

$$\therefore R_C = 100 \times 100\Omega = 10k\Omega$$

Ex 5.47

CC - Emitter Follower

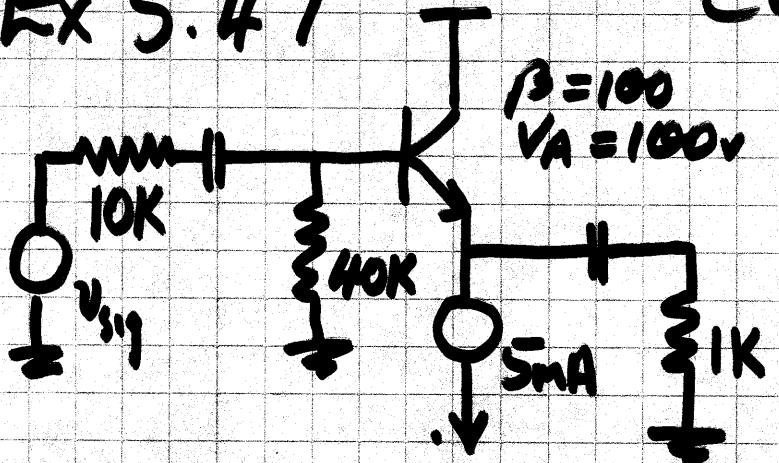

$$R_{i'b} = (1 + \beta)(r_e + R_L // 5) \quad r_e = \frac{V_T}{I_C} = \frac{25mV}{5mA} = 5\Omega$$

$$= 100 \times 95\Omega$$

$$= 96.5k\Omega$$

$$R_{in} = \frac{40k \times 96.5k}{136.5k}$$

$$= 2.83k\Omega$$

$$r_o = \frac{100V}{5mA}$$

$$= 20k\Omega$$


$$20k//1k$$

$$= \frac{20 \times 1}{21} k$$

$$= 0.95k\Omega$$

$$G_V = \frac{R_{AB}}{R_B + R_S} \frac{r_o // R_L}{r_e + r_o // R_L}$$
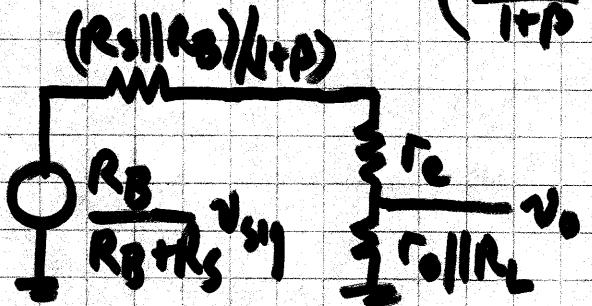
$$+ \left(\frac{R_S // R_B}{1 + \beta} \right)$$



$$= 0.8 \frac{0.95k}{\frac{8k}{101} + 5 + 0.95k}$$

$$= 0.8 \frac{950}{955 + 80} = \frac{760.0}{1035}$$

$$= 0.734$$

$$G_{VO} = -8 \frac{20k}{5\Omega + 20k} \approx 0.8$$

$$R_{out} = r_e + \frac{10k // 40k}{101} = 5\Omega + \frac{8k}{101} = 80\Omega - 8\Omega + 5\Omega = 84.2\Omega$$

Ex 5.47 continued

Max v_o before cutoff?

$$5\text{mA} \times 1\text{K} // r_0 = 4.75\text{V}$$
$$\approx 5\text{V}$$

If $v_{be} = 10\text{mV pk} \rightarrow v_o =$

$$= (1\text{K} // r_0) \frac{10\text{mV}}{r_e} = \frac{950}{5} \times 10\text{mV}$$

$$= 1.9\text{ V}$$

$$\text{If } R_L \rightarrow 2\text{K}, \quad g_v \rightarrow g_{vo} \quad \frac{2\text{K}}{2\text{K} + R_{out}} = 0.8 \quad \frac{2000}{2084}$$
$$= 0.77$$

$$\text{If } R_L \rightarrow 500, \quad g_v \rightarrow 0.8 \quad \frac{500}{584} = 0.685$$

Assignment #7

****D5.99**

5.112

5.116

***5.135**

5.143