

ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 15
16th November, 2006

CHAPTER 5

Bipolar Junction Transistors (BJTs)

5.8 High Frequency Effects

C_{π} (fwd bias BE) & C_{μ} (rev bias CB)

5.9 CE Frequency Response

Low freq effects: coupling & bypass C

Base-Emitter junction

Active (or saturated) mode \implies B-E is forward biased

$$\therefore \text{Stored charge } Q_n \text{ (electrons for NPN)} = \frac{W^2}{2D_n} i_c = \tau_F i_c$$

where $\tau_F = \frac{W^2}{2D_n} =$ "forward bias base-transit time"

The small signal capacitance due to changes in stored charge:

$$\begin{aligned} \text{Small signal } \underline{\text{diffusion}} \text{ capacitance } C_{de} &= \frac{dQ_n}{dV_{BE}} = \tau_F \frac{di_c}{dV_{BE}} \\ &= \tau_F g_m = \tau_F \frac{I_c}{V_T} \end{aligned}$$

ALSO: B-E junction/transition capacitance

BUT — formula doesn't work well for forward bias, so usually use a ROUGH approximation $C_{je} \sim 2 C_{je0}$

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{OE}}\right)^m}$$

$m \sim 0.5, V_{OE} \sim 0.9V$

Collector-Base junction

Active mode — reverse biased

Depletion capacitance


$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{0C}}\right)^m}$$

$$m \sim 0.2 \rightarrow 0.5$$

$$V_{0C} \sim 0.75\text{V}$$

HIGH FREQUENCY HYBRID- π MODEL

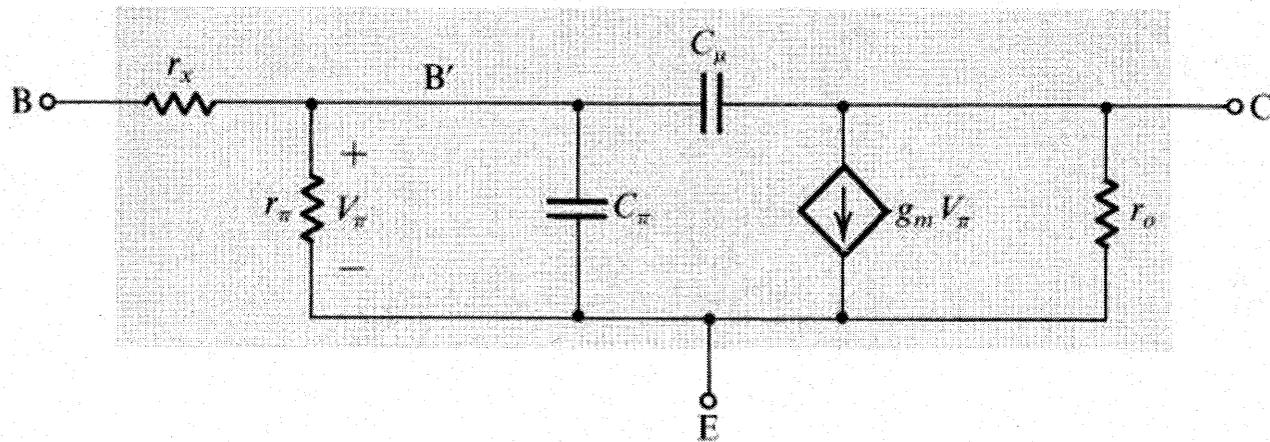$C_{\pi} \rightarrow$ (BE junction) $C_{de} + C_{je}$ Typically 10's of pF
 $C_{\mu} \rightarrow$ (C-B junction) Typically fractions of a pF



$r_x \rightarrow$ bulk "spreading resistance" of the base silicon
 $r_x = r_{bb'} \sim 10's \text{ of ohms} \ll r_{\pi}$

Figure 5.67 The high-frequency hybrid- π model.


Note r_x defines an internal B' node. Actually "distributed" parameters — use "lumped" approximation.

C_{π} and C_{μ} lead to high frequency effects that can be represented by a frequency-dependent β \leftarrow SHORT-CIRCUIT current gain Also known as h_{fe}

$$I_c = g_m V_{\pi} - s C_{\mu} V_{\pi}$$

$$V_{\pi} = I_b (r_{\pi} \parallel C_{\mu} \parallel C_{\pi})$$
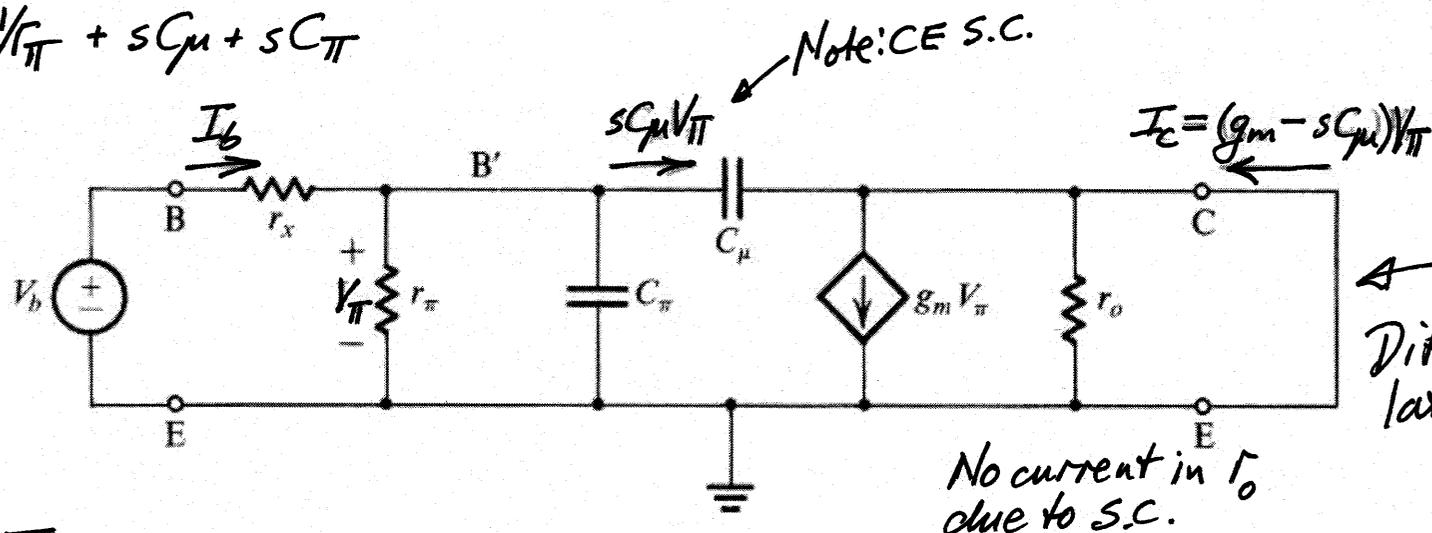
$$= \frac{I_b}{1/r_{\pi} + s C_{\mu} + s C_{\pi}}$$



Note Short circuit (sc) Differs from later treatments.

No current in r_o due to S.C.

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_{\mu}}{1/r_{\pi} + s C_{\mu} + s C_{\pi}} \approx \frac{g_m}{1/r_{\pi} + s(C_{\mu} + C_{\pi})} = \frac{g_m r_{\pi}}{1 + s r_{\pi} (C_{\mu} + C_{\pi})} = \frac{\beta_0}{1 + j(\omega/\omega_{\beta})}$$

where $\omega_{\beta} = \frac{1}{r_{\pi} (C_{\mu} + C_{\pi})}$

Figure 5.68 Circuit for deriving an expression for $h_{fe}(s)$; I_c/I_b .

Note approximation that C_{μ} current $\ll g_m V_{\pi}$. So C_{μ} current is included in the denominator, not in numerator.

Frequency dependence of h_{fe} & summary:

$$g_m = \frac{I_C}{V_T}$$

$$\Gamma_0 \approx \frac{|V_A|}{I_C}$$


$$\Gamma_{\pi} = \frac{\beta}{g_m}$$

$$C_{\pi} = C_{de} + C_{je}$$

$$C_{\mu} = \frac{C_{jco}}{\left(1 + \frac{V_{CB}}{V_{CO}}\right)^m}$$

$$C_{de} = \tau_F g_m \quad C_{je} \sim 2C_{jeo}$$
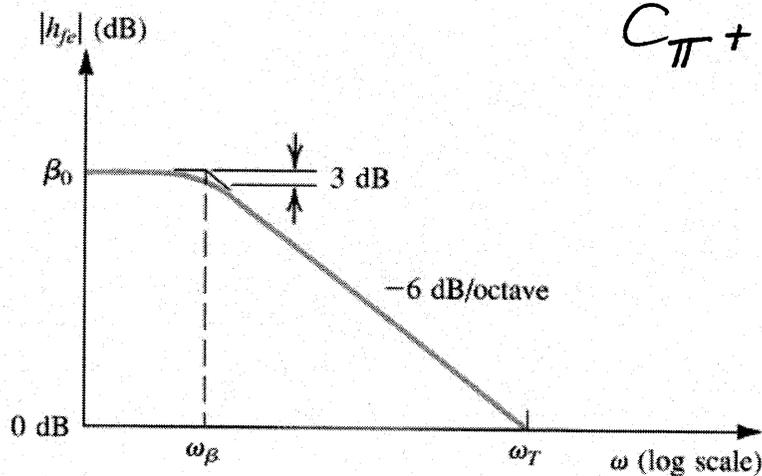
$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_T}$$



Unity gain bandwidth:

$$|h_{fe}| = \frac{\beta_0}{\left[1 + (\omega/\omega_{\beta})^2\right]^{1/2}} \rightarrow 1 \text{ when } \omega = \omega_T$$

$$\text{i.e. } \beta_0^2 = 1 + (\omega_T/\omega_{\beta})^2$$

$$\omega_T \approx \beta_0 \omega_{\beta}$$

Unity gain bandwidth (BW)

Figure 5.69 Bode plot for h_{fe} .

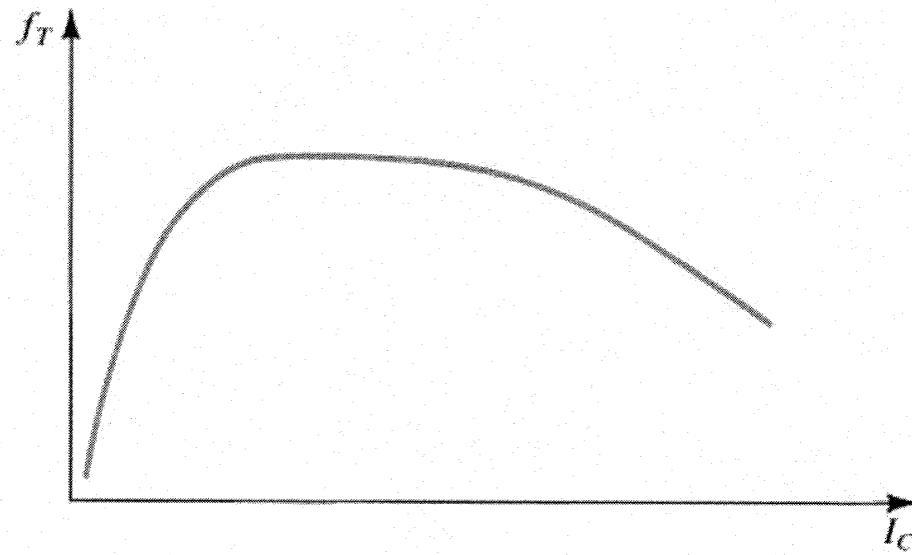


Figure 5.70 Variation of f_T with I_C .

High Frequency Hybrid- π including r_o

See back (Fig 5.69) for relationship summary.

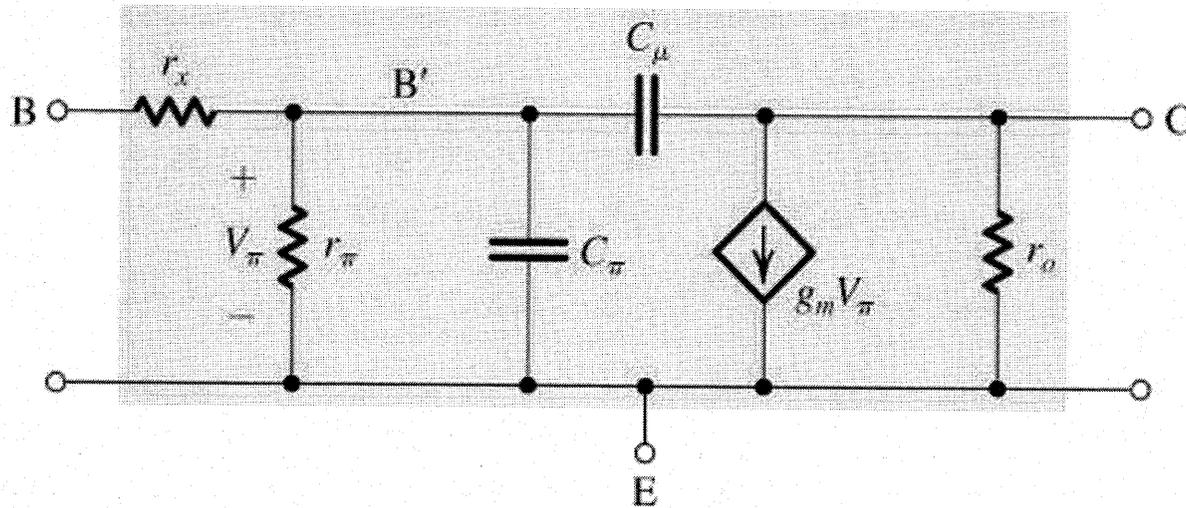


Table 5.7

Exercise 5.48

Exercise 5.49

Exercise 5.50


C_{c1}, C_{c2} coupling capacitors ——— $X_c \sim 0$ at "mid-band" frequencies

DC block
AC short

Mid-band gain:


$$A_{MB} = -g_m \left[r_o \parallel R_c \parallel R_L \right] \left[\frac{R_B \parallel r_{\pi}}{R_{sig} + R_B \parallel r_{\pi}} \right]$$

CE amp

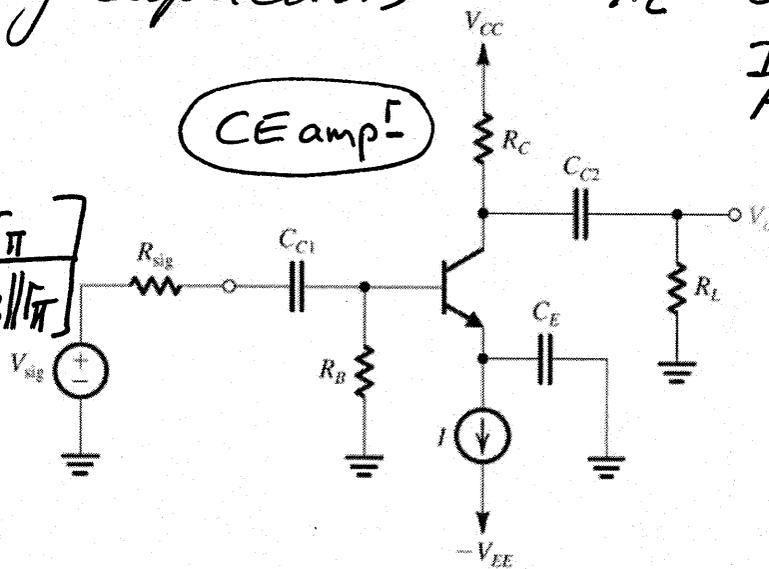

But at lower frequencies, $X_c \neq 0$

(a)

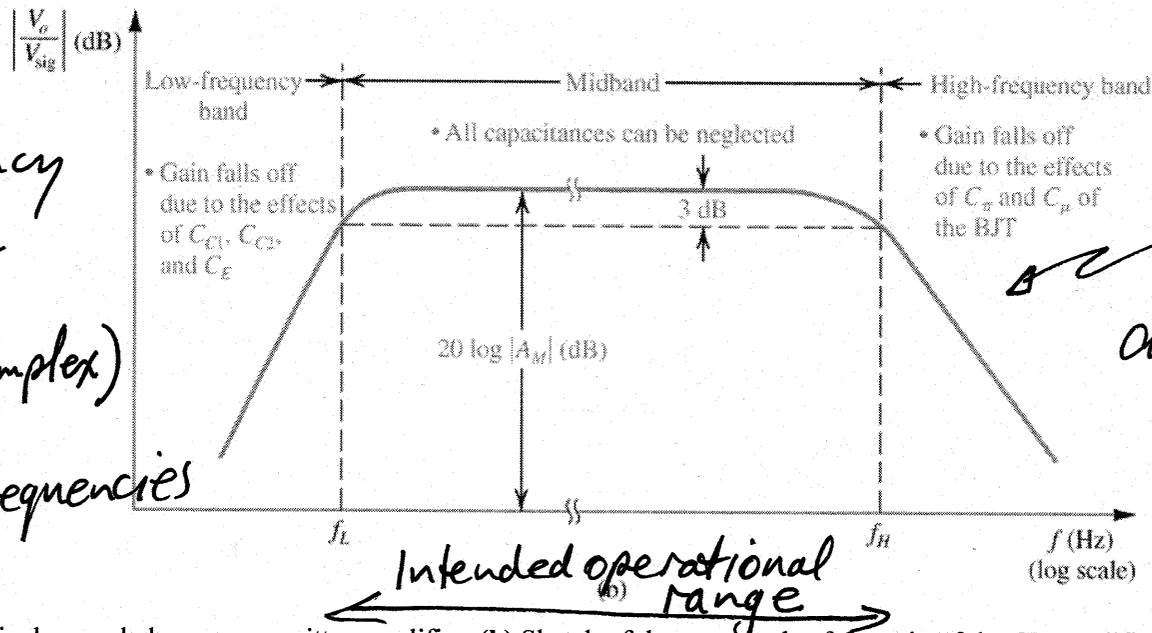

Low frequency roll-off due to C_{c1}, C_{c2} — and C_E (more complex)

High frequency roll-off due to C_{π}, C_{μ} .

Usually corner frequencies staggered.


$C_{\mu} \ll C_{\pi}$, but C_{μ} dominant due to "Miller Effect"

Intended operational range

Figure 5.71 (a) Capacitively coupled common-emitter amplifier. (b) Sketch of the magnitude of the gain of the CE amplifier versus frequency. The graph delineates the three frequency bands relevant to frequency-response determination.


$$\text{Bandwidth} = f_H - f_L \approx f_H$$

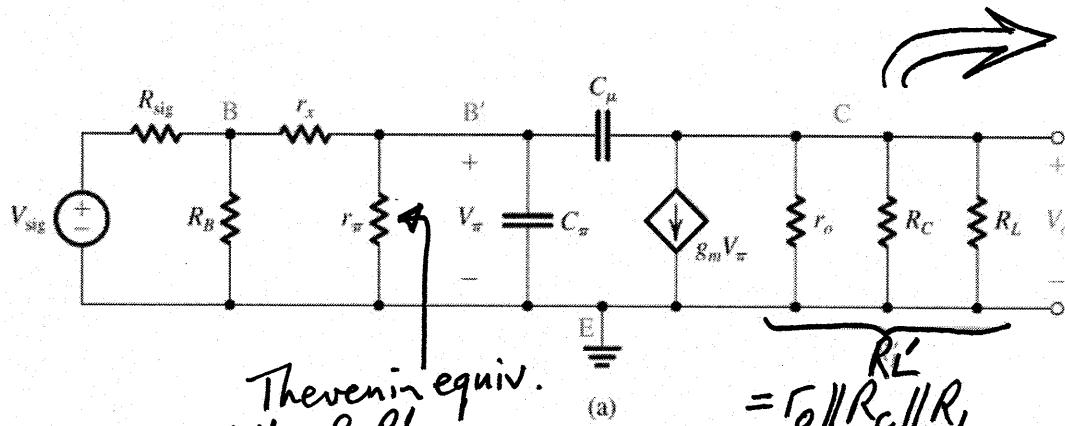Amplifier equivalent circuit: High frequencies — X_{C1}, X_{C2}, X_{CE} all s.c.
 Note: output no longer shorted.



Thevenin equiv.
 V'_{sig} & R'_{sig}
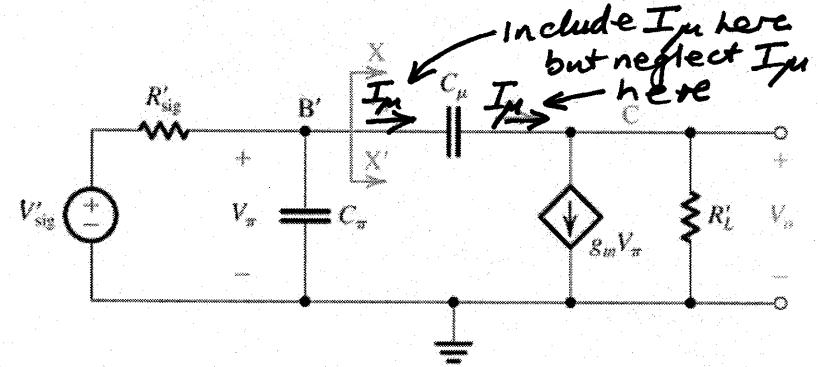
$$R'_L = r_o \parallel R_C \parallel R_L$$



$$V'_{sig} = V_{sig} \frac{R_B}{R_B + R_{sig}} \frac{r_{\pi}}{r_x + r_{\pi} + (R_{sig} \parallel R_B)}$$


$$R'_{sig} = r_o \parallel (r_x + (R_B \parallel R_{sig}))$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$I_{\mu} = sC_{\mu}(V_{\pi} - V_o)$$

$$= sC_{\mu}(V_{\pi} - (-g_m V_{\pi} R'_L))$$

$$= sC_{\mu}(1 + g_m R'_L)V_{\pi}$$

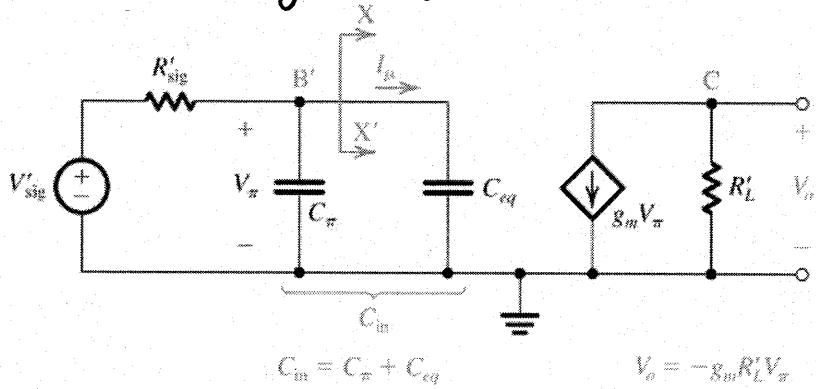


$$C_{in} = C_{\pi} + C_{eq}$$

$$= C_{\pi} + C_{\mu}(1 + g_m R'_L)$$

$$V_o = -g_m R'_L V_{\pi}$$

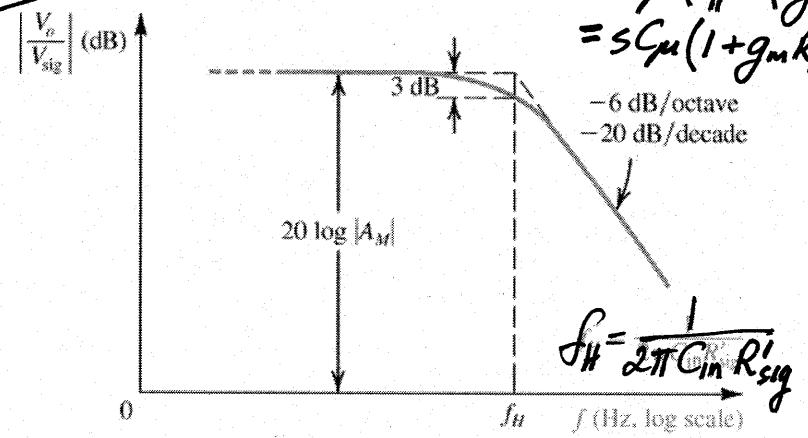$\therefore C_{eq} = C_{\mu}(1 + g_m R'_L)$
 so $I_{\mu} = sC_{eq} \cdot V_{\pi}$



$$f_H = \frac{1}{2\pi C_{in} R'_{sig}}$$

Figure 5.72 Determining the high-frequency response of the CE amplifier: (a) equivalent circuit; (b) the circuit of (a) simplified at both the input side and the output side; (c) equivalent circuit with C_{μ} replaced at the input side with the equivalent capacitance C_{eq} ; (d) sketch of the frequency-response plot, which is that of a low-pass STC circuit.

This treatment misses the second corner frequency due to the I_{μ} flowing to the output circuit.

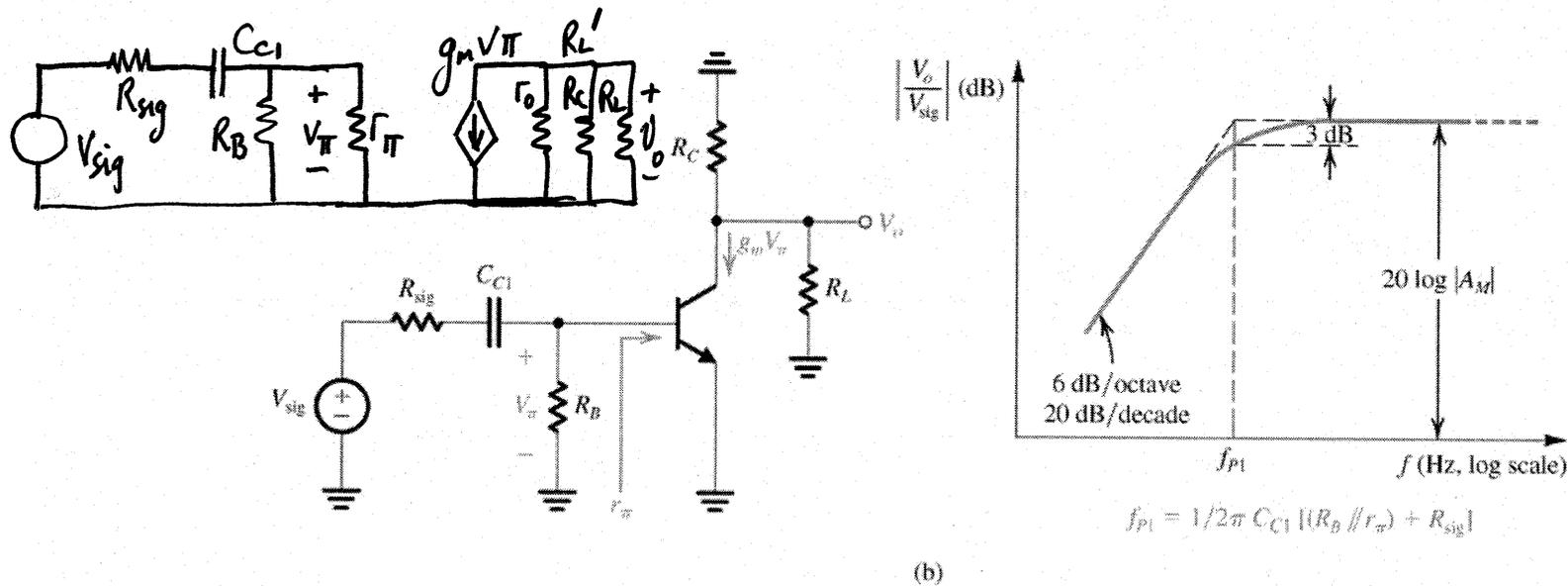
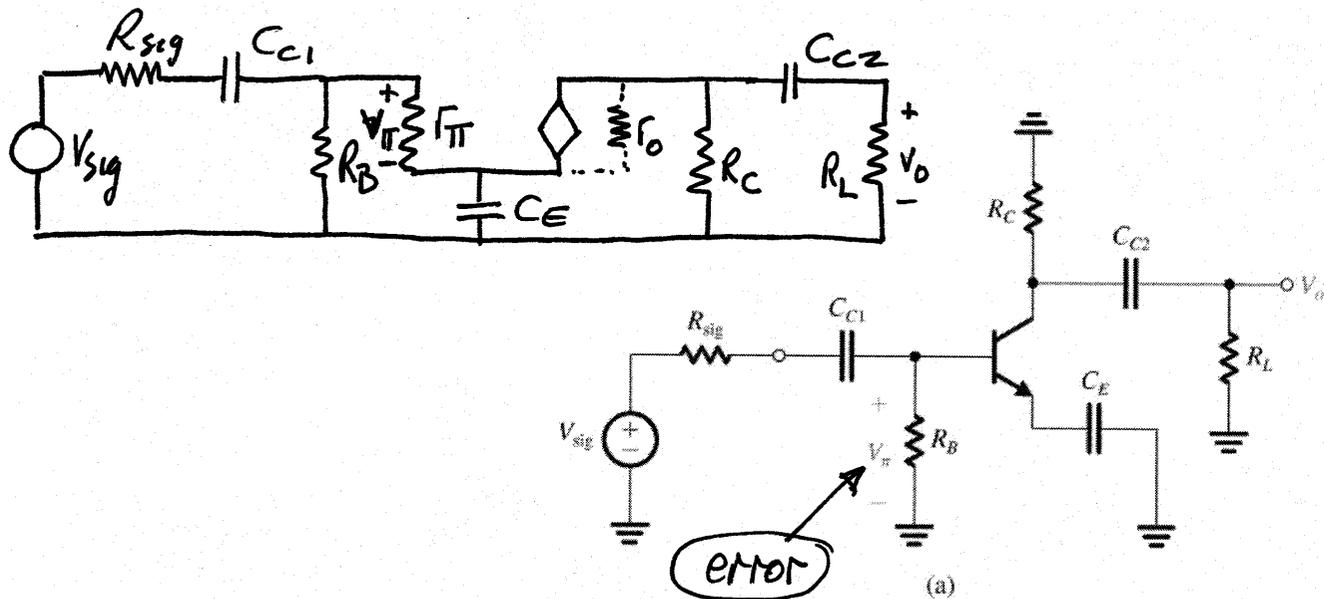




Figure 5.73 Analysis of the low-frequency response of the CE amplifier: (a) amplifier circuit with dc sources removed; (b) the effect of C_{C1} is determined with C_E and C_{C2} assumed to be acting as perfect short circuits;

$$\frac{V_o}{V_{sig}} = -g_m R_L' V_{\pi} = -g_m R_L' \frac{r_{\pi} \parallel R_B}{(r_{\pi} \parallel R_B) + R_{sig} + 1/s C_{C1}} = A_{MB} \frac{s R_S' C_{C1}}{1 + s R_S' C_{C1}}$$


$$= -g_m R_L' \frac{r_{\pi} \parallel R_B}{r_{\pi} \parallel R_B + R_{sig}} \frac{1}{1 + 1/s C_{C1} (r_{\pi} \parallel R_B + R_{sig})}$$

where $R_S' = R_{sig} + (r_{\pi} \parallel R_B)$
 $\& A_{MB} = -g_m R_L' \cdot \frac{r_{\pi} \parallel R_B}{R_S'}$


Next page

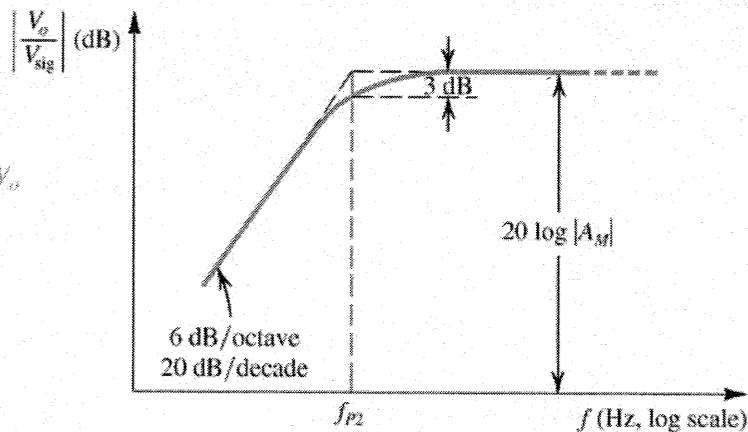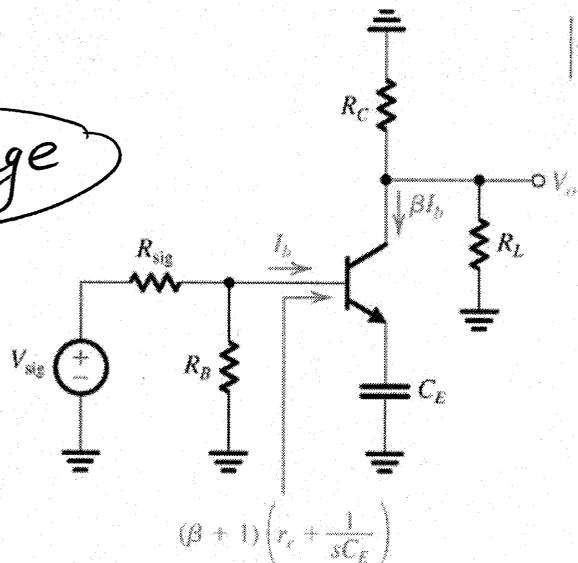
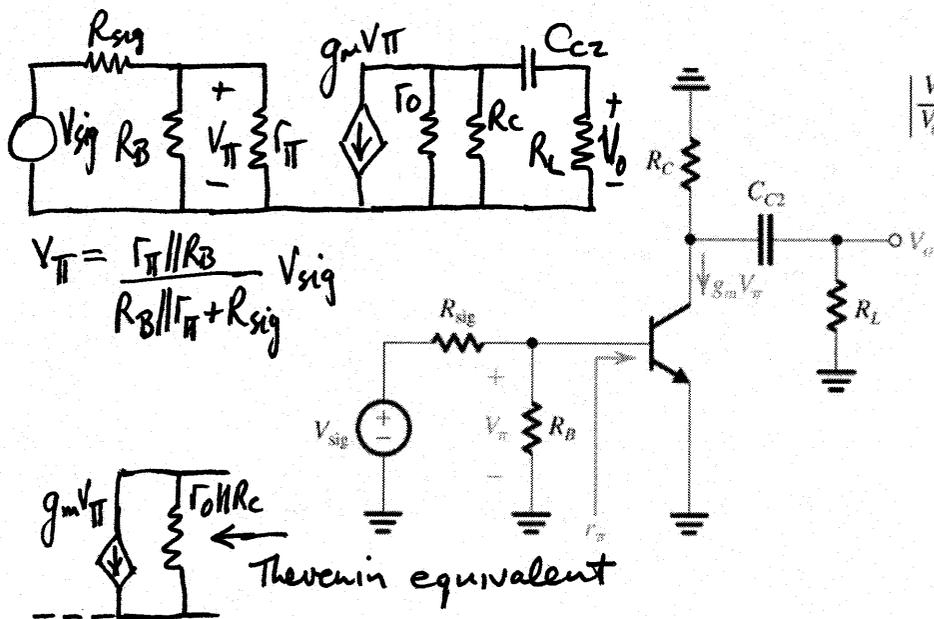
$$f_{p2} = 1/2\pi C_E \left[r_e + \frac{R_B // R_{sig}}{\beta + 1} \right]$$




(c)

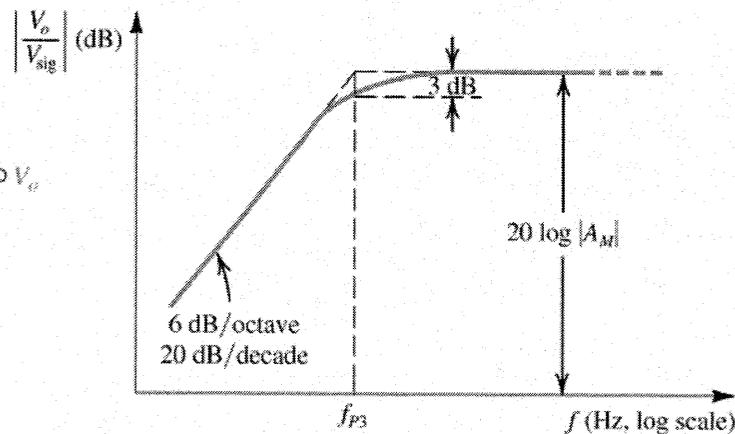

$$f_{p3} = 1/2\pi C_{C2} (R_C + R_L)$$

(d)


Figure 5.73 (Continued) (c) the effect of C_E is determined with C_{C1} and C_{C2} assumed to be acting as perfect short circuits; (d) the effect of C_{C2} is determined with C_{C1} and C_E assumed to be acting as perfect short circuits;

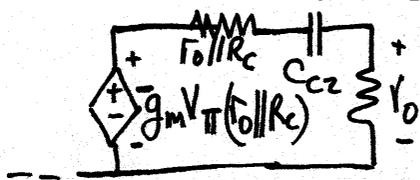

$$V_o = \frac{-R_L}{R_L + (r_o // R_c) + 1/sC_{C2}} g_m V_{\pi} (r_o // R_c) = -g_m \frac{R_L (r_o // R_c)}{R_L + (r_o // R_c)} \frac{1}{1 + 1/sC_{C2} [R_L + (r_o // R_c)]}$$


Hence $V_o/V_{sig} = A_{MB} \frac{s R_m C_{C2}}{1 + s R_m C_{C2}}$ where $R_m = R_L + r_o // R_c$

Emitter Case

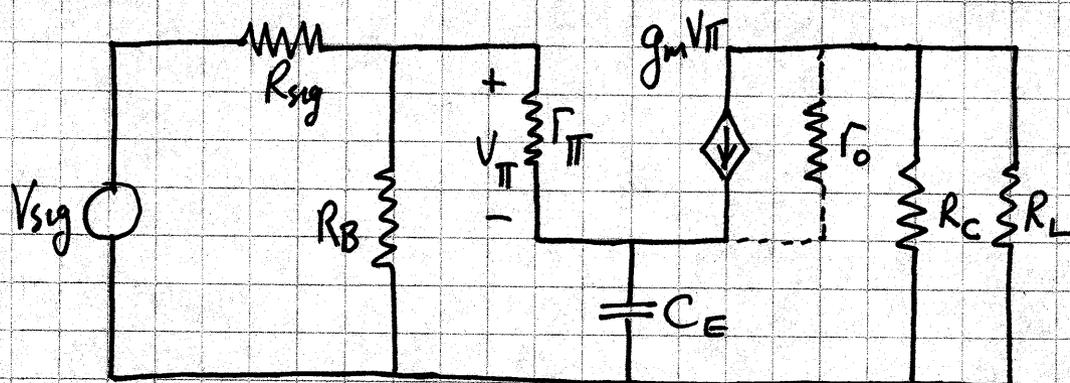

T-equivalent probably easier here.
Or even βi_b instead of V_{π} . But show any equivalent circuit will work.

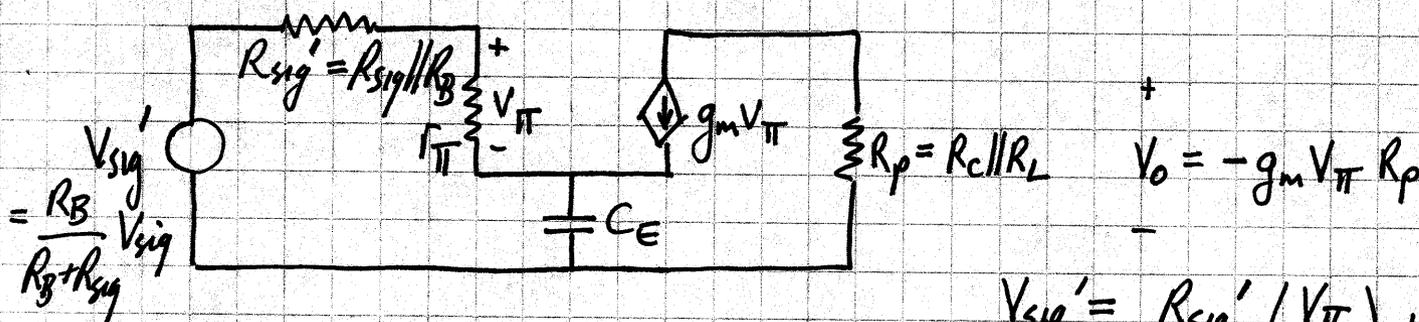However, neglect r_o or algebra gets much messier!




$$V_{sig}' = R_{sig}' \left(\frac{V_{\pi}}{r_{\pi}} \right) + \frac{1}{sC_E} \left(\frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) + V_{\pi}$$

$$\begin{aligned} \therefore \frac{V_o}{V_{sig}'} &= \frac{-g_m R_p}{\frac{R_{sig}'}{r_{\pi}} + \frac{1}{sC_E} \left(\frac{1}{r_{\pi}} + g_m \right) + 1} = -g_m R_p \frac{r_{\pi}}{r_{\pi} + R_{sig}' + \frac{1}{sC_E} \left(\frac{1}{r_{\pi}} + g_m \right)} \\ &= -g_m R_p \frac{r_{\pi}}{r_{\pi} + R_{sig}'} \frac{1}{1 + \frac{1}{sC_E} \cdot \frac{1 + g_m r_{\pi}}{r_{\pi} + R_{sig}'}} \Rightarrow A_{MB} \frac{sR'C_E}{1 + sR'C_E} \end{aligned}$$

But note assumed other two X_c 's = 0 for each case.
Must be wrong for two!!

$$\begin{aligned} \text{where } R' &= \frac{r_{\pi} + R_{sig}'}{1 + g_m r_{\pi}} = \frac{r_{\pi} + R_{sig}'}{1 + \beta} \\ &= r_e + \frac{R_B || R_{sig}}{1 + \beta} \end{aligned}$$

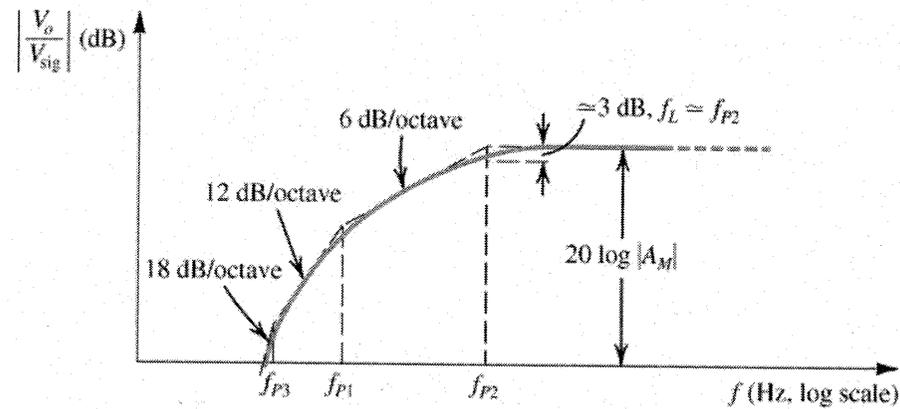



(e)

Note 3 corner frequencies $\rightarrow -60 \text{ dB/decade}$
at very low frequency.

Figure 5.73 (Continued) (e) sketch of the low-frequency gain under the assumptions that C_{C1} , C_E , and C_{C2} do not interact and that their break (or pole) frequencies are widely separated.

Exercise 5.51

Discrete Emitter Resistor Core

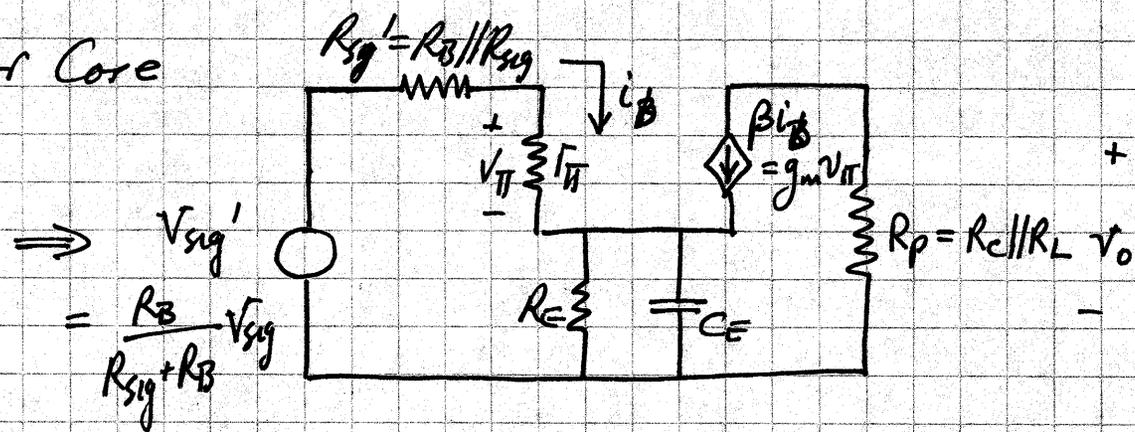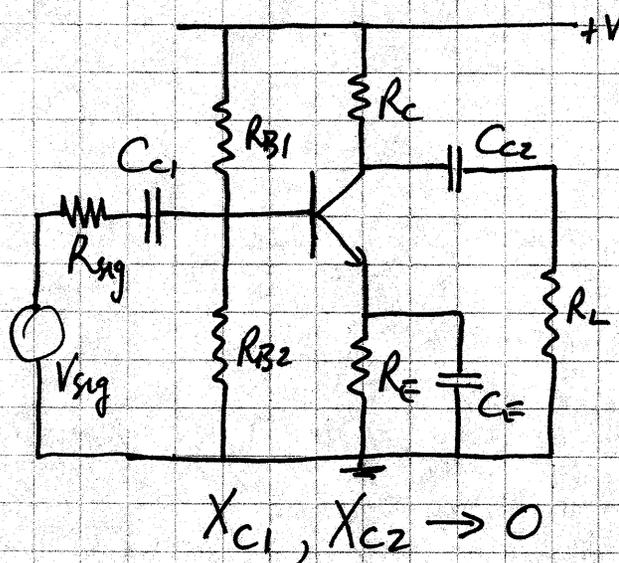

$$v_{\pi} = i_b r_{\pi} \quad v_E = (1+\beta) i_b (R_E \parallel C_E)$$

$$v_s = i_b (R_s' + r_{\pi} + (1+\beta)(R_E \parallel C_E))$$

$$= \frac{v_{\pi}}{r_{\pi}} (R_s' + r_{\pi} + (1+\beta)(R_E \parallel C_E))$$

$$\therefore v_o = -g_m v_{\pi} R_p = -g_m R_p v_s \frac{r_{\pi}}{R_s' + r_{\pi} + (1+\beta) R_E \parallel C_E} = -g_m R_p v_s \frac{r_{\pi}}{R_s' + r_{\pi}} \cdot \frac{1}{1 + \frac{(1+\beta) R_E \parallel C_E}{R_s' + r_{\pi}}}$$

$$\therefore \frac{v_o}{v_s} = A_{MB} \frac{1}{1 + \frac{(1+\beta) R_E \parallel C_E}{R_s' + r_{\pi}}} = A_{MB} \frac{1}{1 + \frac{1}{\Gamma_x} \frac{R_E}{1 + s R_E C_E}} \quad \text{where } \Gamma_x = \frac{R_s' + r_{\pi}}{1+\beta}$$


$$= A_{MB} \frac{1 + s R_E C_E}{1 + s R_E C_E + \frac{R_E}{\Gamma_x}} = A_{MB} \frac{1 + s R_E C_E}{1 + \frac{R_E}{\Gamma_x} + s \frac{R_E C_E}{1 + R_E / \Gamma_x}}$$

$$= A_{MB} \frac{\Gamma_x}{\Gamma_x + R_E} \cdot \frac{1 + s R_E C_E}{1 + s \frac{R_E \Gamma_x}{R_E + \Gamma_x} C_E}$$

$$\xrightarrow{\text{high freq}} A_{MB} \frac{\Gamma_x}{\Gamma_x + R_E} \frac{R_E C_E}{R_E \Gamma_x C_E} = A_{MB} \frac{R_E C_E}{\Gamma_x + R_E}$$

$$\xrightarrow{\text{low freq}} A_{MB} \frac{\Gamma_x + \frac{R_s'}{1+\beta}}{R_E + \Gamma_x + \frac{R_s'}{1+\beta}} \approx A_{MB} \frac{\Gamma_x}{R_E + \Gamma_x}$$

Bode Plot

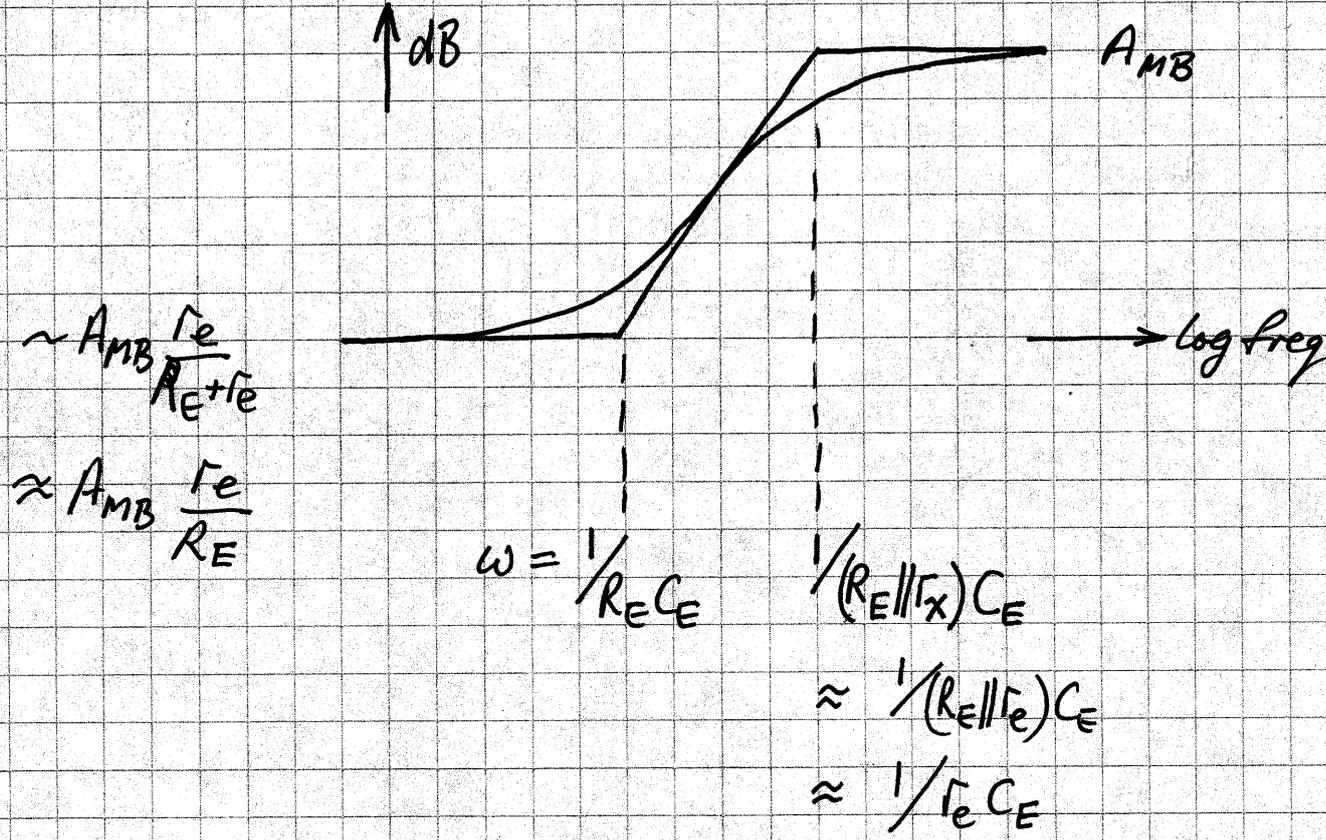

Note relevance to lab experiment

Ex 5.48 BJT $I_C = 1\text{mA}$, $V_{CB} = -2\text{V}$, $\tau_F = 20\text{ps}$, $C_{je0} = 20\text{pF}$, $C_{\mu 0} = 20\text{pF}$
 $V_{oc} = 0.9\text{V}$, $V_{oc} = 0.5\text{V}$, $m_{CBJ} = 0.33$

$$\text{Find } C_{de} = \frac{\tau_F I_C}{V_T} = \frac{20 \times 10^{-12} \times 10^{-3}}{25 \times 10^{-3}} = 0.8\text{pF}$$

$$C_{je} = 2C_{je0} = 40\text{pF}$$

$$C_{\pi} = C_{de} + C_{je} = 0.84\text{pF}$$

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{|V_{CB}|}{V_{oc}}\right)^{m_{CBJ}}} = \frac{20\text{pF}}{\left(1 + \frac{2\text{V}}{0.5\text{V}}\right)^{0.33}} \approx 12\text{pF}$$

$$f_T = g_m / 2\pi(C_{\pi} + C_{\mu}) = \frac{I_C}{V_T} \frac{1}{2\pi(C_{\pi} + C_{\mu})} = \frac{10^{-3} \times 10^{12}}{25 \times 10^{-3} \times 2\pi \times 0.852} \approx 7.5\text{GHz}$$

Ex 5.49 BJT $I_C = 1\text{mA}$, $C_{\mu} = 2\text{pF}$, $|h_{fe}| = 10$ at 50MHz , Find f_T & C_{π}

$$\therefore g_m = \frac{1\text{mA}}{25\text{mV}} = 40\text{mA/V} \quad f_T = 500\text{MHz} \quad \therefore C_{\pi} + C_{\mu} = g_m / 2\pi f_T = \frac{40 \times 10^{-3}}{2\pi \times 5 \times 10^8} = 12.7\text{pF}$$

$$\therefore C_{\pi} = 10.7\text{pF}$$

Ex 5.50 For the BJT of Ex 5.49: C_{π} includes approx constant C_{je} (depletion capac) = 2pF

Find f_T at $I_C = 0.1\text{mA}$

$$C_{de} = \tau_F g_m = \tau_F I_C / V_T$$

$$C_{\pi} = C_{de} + C_{je} \quad \therefore C_{de} = (10.7 - 2)\text{pF} = 8.7\text{pF} \text{ at } 1\text{mA}. \text{ So } C_{de}(0.1\text{mA}) = 0.87\text{pF}$$

$$\therefore C_{\pi}(0.1\text{mA}) = 2\text{pF} + 0.87\text{pF} = 2.87\text{pF} \quad \therefore f_T(I_C = 0.1\text{mA}) = g_m / 2\pi(C_{\pi} + C_{\mu}) = \frac{4 \times 10^{-3}}{2\pi(2.87 + 2) \times 10^{-12}} = 130.7\text{MHz}$$

Ex 5.51 For amplifier of Example 5.18, (\leftarrow refer to Example 5.18!)
 find R_L to halve A_{MB} ; what is new f_H ?

$$A_{MB} = -g_m R_L' \cdot \frac{r_{\pi} \parallel R_B}{R_{sig} + r_{\pi} \parallel R_B} \quad \leftarrow \text{halve } A_{MB} \text{ by halving } R_L'$$

$$R_L' = R_L \parallel R_C \parallel \tau_o = \frac{R_C R_L \tau_o}{R_C R_L + R_L \tau_o + \tau_o R_C} = \frac{8 \times 5 \times 100}{40 + 500 + 800} \approx 3 \text{K}\Omega$$

$\begin{cases} R_L = 5 \text{K} \\ R_C = 8 \text{K} \\ \tau_o = 100 \text{K} \end{cases}$

\therefore need $\frac{R_L \times 8 \times 100}{8R_L + 100R_L + 800} = 1.5 \Rightarrow R_L = 1.9 \text{K}\Omega$

$$\text{New } f_H = \frac{1}{2\pi C_{in} R_{sig}'}$$

$$R_{sig}' = 1.65 \text{K}\Omega \text{ from Example 5.18}$$

$$C_{in} = C_{\pi} + C_{\mu} (1 + g_m R_L')$$

$$= 7 \text{pF} + 1 \text{pF} (1 + 40 \times 10^{-3} \cdot 1.5 \cdot 10^3) = 68 \text{pF}$$

\uparrow from example 5.18 \uparrow new value

C_{in} dominates
 since $(1 + g_m R_L') C_{\mu} \gg C_{\pi}$

$$\therefore f_H = \frac{1}{2\pi \cdot 68 \times 10^{-12} \cdot 1.65 \times 10^3} = 1.42 \text{MHz}$$

\uparrow from Example 5.18