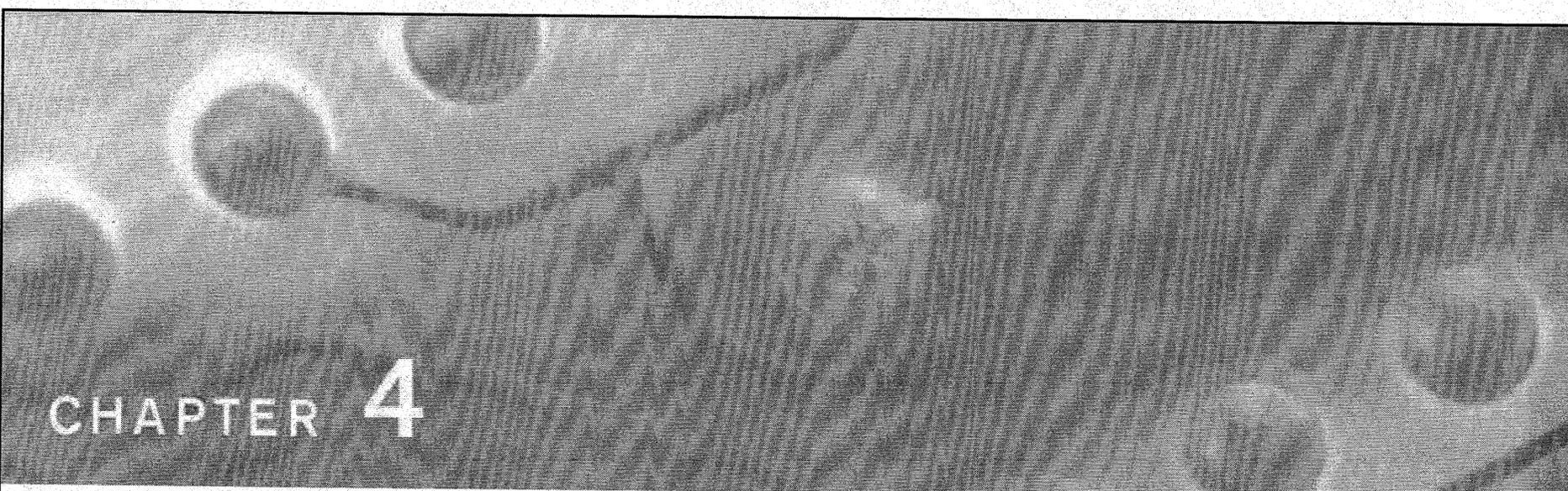


ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 16

21st November, 2006



CHAPTER 4

MOS Field-Effect Transistors (MOSFETs)


4.8 High Frequency Effects
(MOSFET parasitics)

4.9 CS Amplifier Frequency Response
(Bypass/coupling C's) ₂

MOSFET Parasitic Capacitors

Gate Capacitances


① Assume saturation:

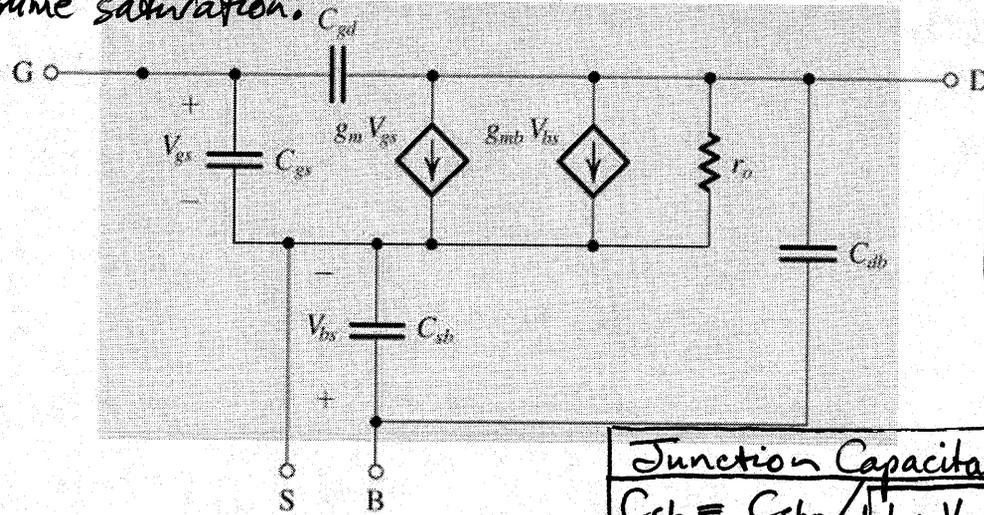

(a)

Junction Capacitances
 $C_{sb} = C_{sbo} / \sqrt{1 + V_{SB}/V_0}$
 $C_{db} = C_{dbo} / \sqrt{1 + V_{DB}/V_0}$
 Reverse biased

② Connect S to B:-

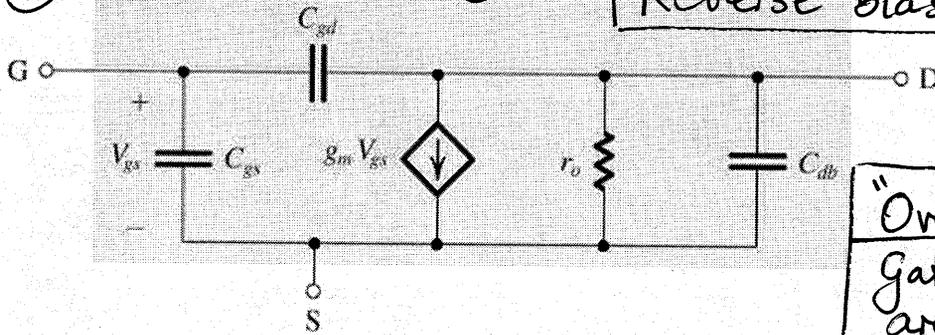

(b)

"Overlap" capacitances
 Gate overlaps S, D diffusion areas by $L_{ov} \sim 0.05$ to $0.1 L$
 $C_{ov} = W L_{ov} C_{ox}$


and $C_{gs}' \rightarrow C_{gs} + C_{ov}$, $C_{gd}' \rightarrow C_{gd} + C_{ov}$

Triode: $C_{gs} = C_{gd} = \frac{1}{2} W L C_{ox}$
 Gate "connects" through channel to S & D approx. equally.

Saturation: $C_{gs} \approx \frac{2}{3} W L C_{ox}$, $C_{gd} \approx 0$
 Channel pinched off at D

Cutoff: $C_{gs} = C_{gd} = 0$, $C_{gb} = W L C_{ox}$

③ High frequency model:

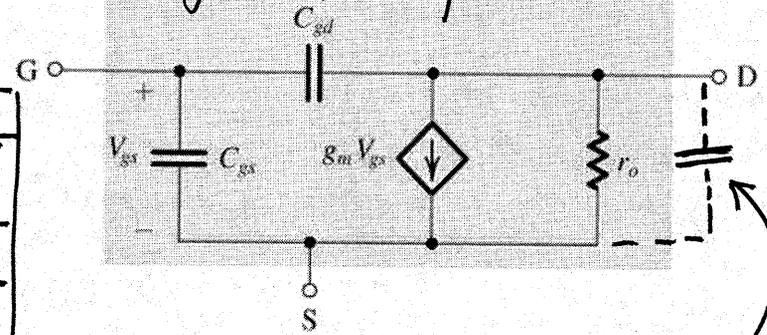


(c)

C_{db} (negligible)
 + approx C_{gd}
 (Miller Effect)

Figure 4.47 (a) High-frequency equivalent circuit model for the MOSFET. (b) The equivalent circuit for the case in which the source is connected to the substrate (body). (c) The equivalent circuit model of (b) with C_{db} neglected (to simplify analysis).

Note: In saturation, $C_{gd} \approx C_{ov}$ i.e. small.

Short Circuit Current gain I_o/I_i

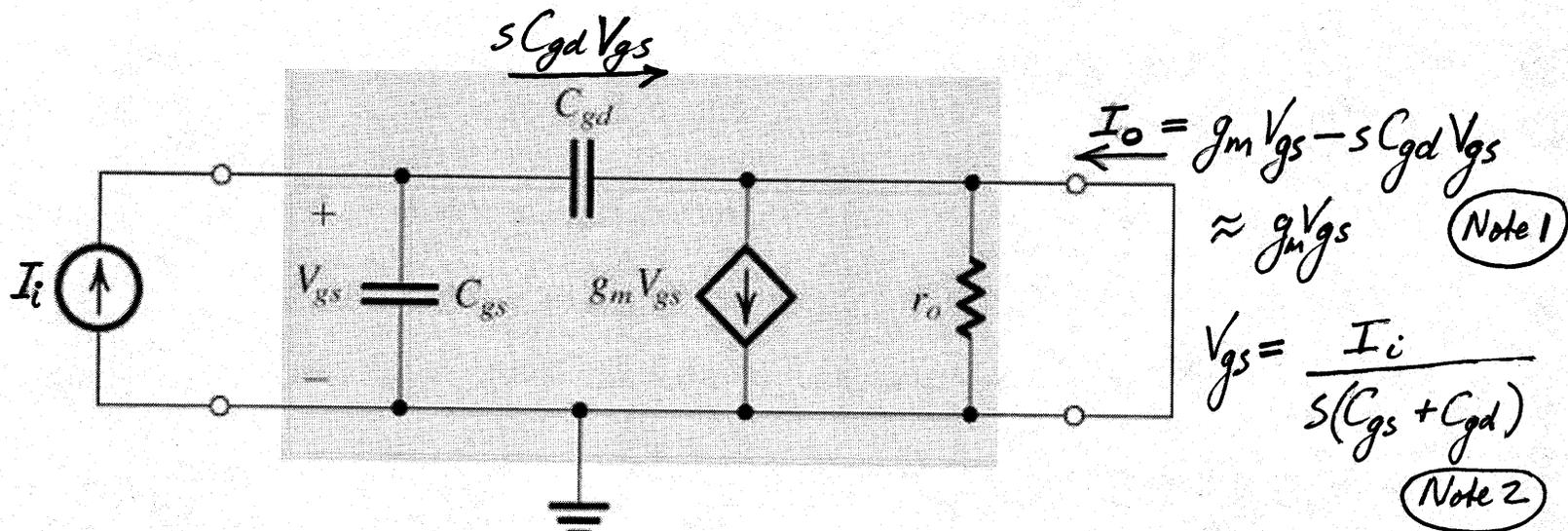

Note 1: $s C_{gd} V_{gs}$ neglected in comparison with $g_m V_{gs}$

Note 2: $s C_{gd} V_{gs}$ included

Valid if $g_m V_{gs} \gg I_i$
 ie. high current gain

Figure 4.48 Determining the short-circuit current gain I_o/I_i .

Note 1 is equivalent to ignoring the feedback effects.

See back to Miller Effect and BJT.

But here, output is short circuited \therefore voltage gain = 0

$$\therefore I_o/I_i = \frac{g_m}{s(C_{gs} + C_{gd})}$$

& $|I_o/I_i| \rightarrow 1$ when

$$\begin{aligned} \omega_T &= \frac{g_m}{C_{gs} + C_{gd}} * \\ &= k_n' \frac{W}{L} \frac{V_{ov}}{C_{gs} + C_{gd}} \\ &= \sqrt{2} k_n' \frac{W}{L} \sqrt{I_D} / (C_{gs} + C_{gd}) \\ &= (2 I_D / V_{ov}) / (C_{gs} + C_{gd}) \end{aligned}$$

Exercise 4.36


Exercise 4.37

MOSFET High Frequency Model Summary (Assume saturation)

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2 I_D}{V_{ov}}$$

$$g_{mb} = \chi g_m = g_m \frac{\gamma}{2 \sqrt{2 \phi_f + V_{SB}}}$$

$$r_o = V_A / I_D$$

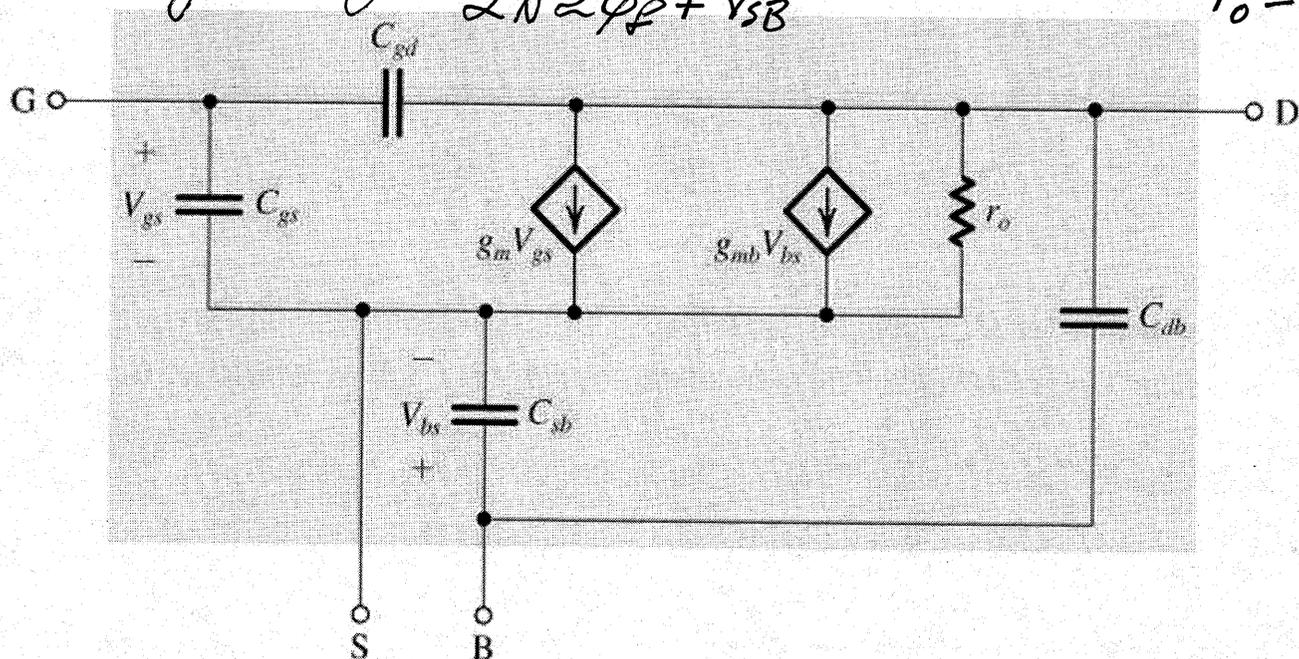

$$C_{gs} = \frac{2}{3} W L \cdot C_{ox} + W L_{ov} C_{ox}$$

$$C_{gd} = W L_{ov} C_{ox}$$

$$C_{sb} = C_{sbo} / \sqrt{1 + V_{SB}/V_0}$$

$$C_{db} = C_{dbo} / \sqrt{1 + V_{DB}/V_0}$$

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})}$$

Table 4.5

CS Frequency Response


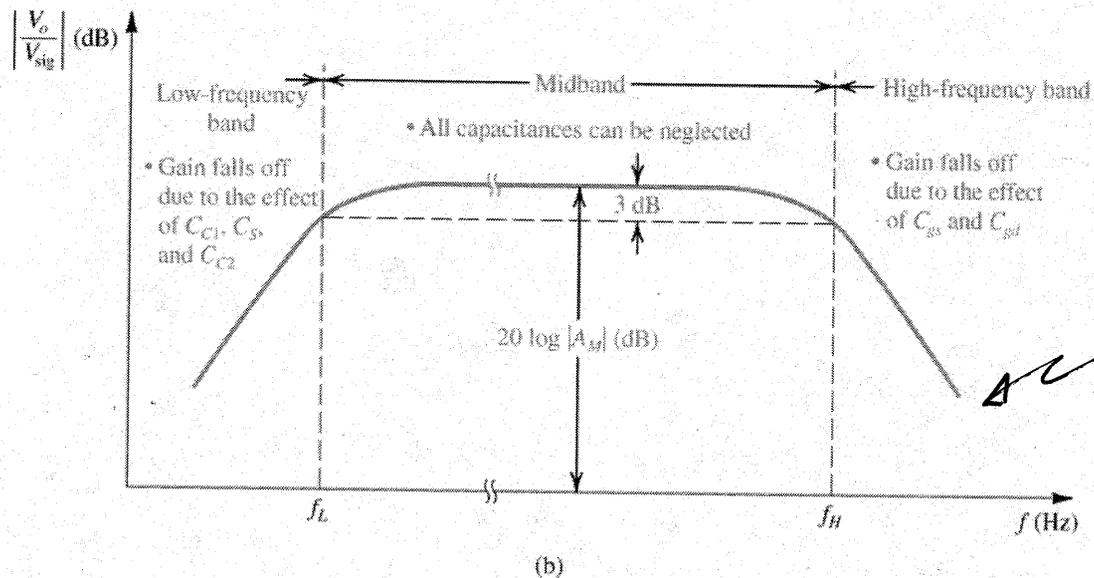
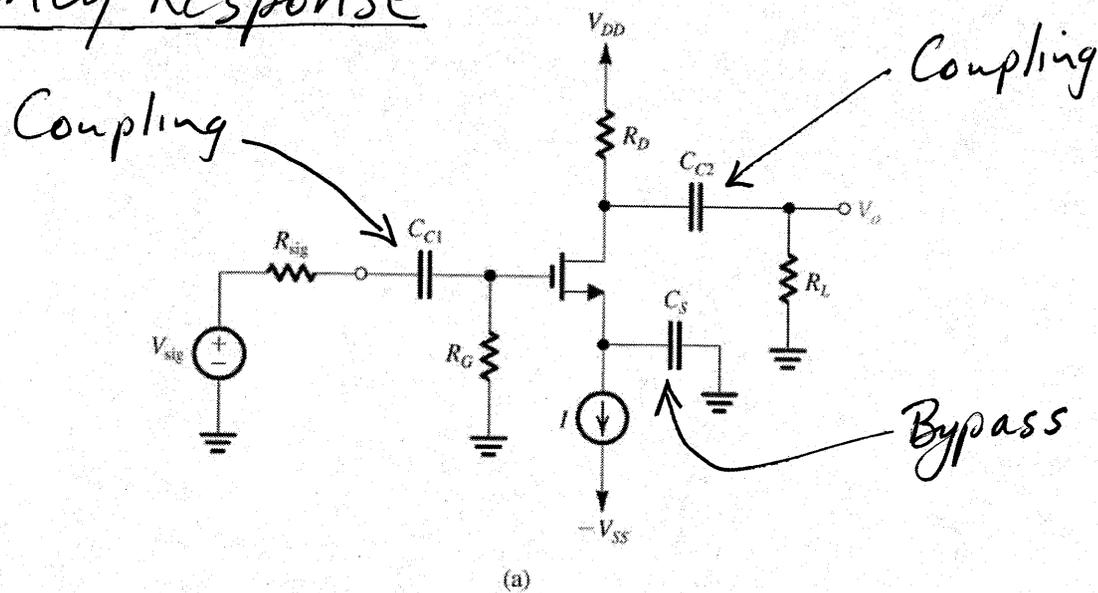
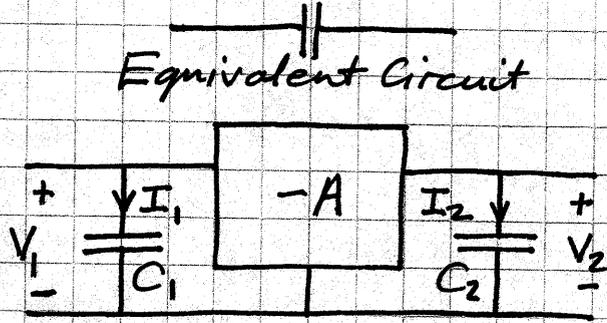


Figure 4.49 (a) Capacitively coupled common-source amplifier. (b) A sketch of the frequency response of the amplifier in (a) delineating the three frequency bands of interest.

Remember:
There is actually another higher frequency breakpoint due to $C_{gd} + C_{db}$ in output circuit.

Traditional Miller's Theorem treatment

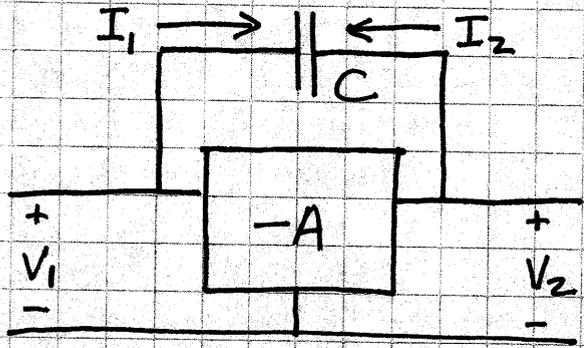Consider inverting amplifier of gain $-A$ with feedback capacitor C




$$\begin{aligned} I_2 &= sC(V_2 - V_1) \\ &= sC\left(V_2 - \frac{V_2}{-A}\right) \\ &= sC\left(1 + \frac{1}{A}\right)V_2 \end{aligned}$$

$$\begin{aligned} I_2 &= sC_2 V_2 \\ \therefore C_2 &= \left(1 + \frac{1}{A}\right)C \end{aligned}$$

$$\begin{aligned} I_1 &= sC(V_1 - V_2) \\ &= sC(V_1 - (-A)V_1) \\ &= sC(1 + A)V_1 \end{aligned}$$
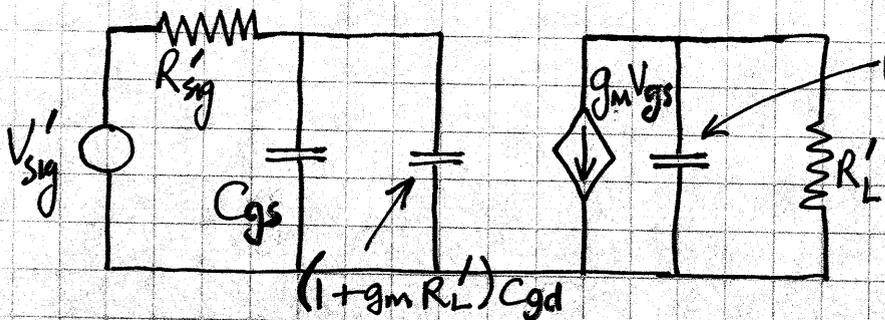
$$\begin{aligned} I_1 &= sC_1 V_1 \\ \therefore C_1 &= (1 + A)C \end{aligned}$$



$$\left(1 + \frac{1}{g_m R_L}\right) C_{gd} \approx C_{gd}$$


$$\omega_1 = (R_{sig}' C_{in})^{-1}$$

$$C_{in} = C_{gs} + (1 + g_m R_L') C_{gd}$$

$$\omega_2 = (R_L' C_{gd})^{-1}$$

But note "A" is varying with frequency too!

High-frequency roll-off

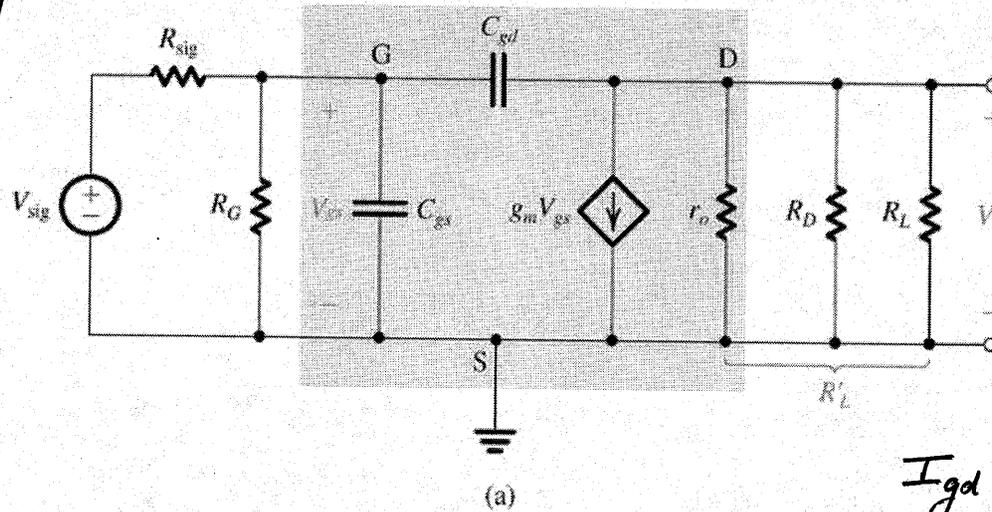

Mid-band:

$$V_o = V_{ds} = -g_m R_L' v_{gs}$$

Find the effect of C_{gd}

$$\begin{aligned} I_{gd} &= s C_{gd} (V_{gs} - V_o) \\ &= s C_{gd} V_{gs} (1 - (-g_m R_L')) \\ \text{using the mid-band gain} \\ &= s C_{gd} (1 + g_m R_L') V_{gs} \\ &= s C_{eq} V_{gs} \end{aligned}$$


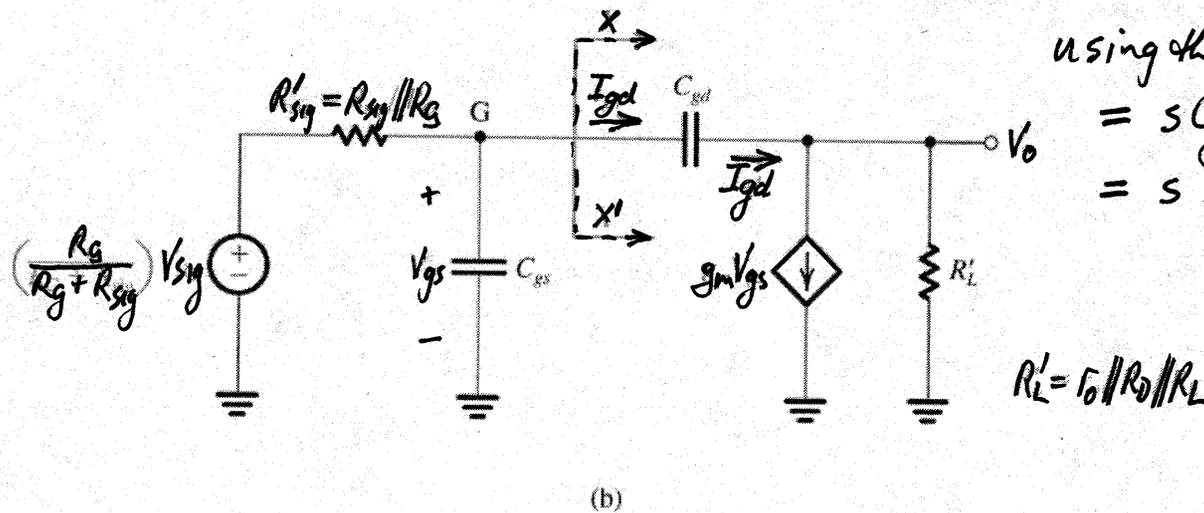



Figure 4.50 Determining the high-frequency response of the CS amplifier: (a) equivalent circuit; (b) the circuit of (a) simplified at the input and the output;

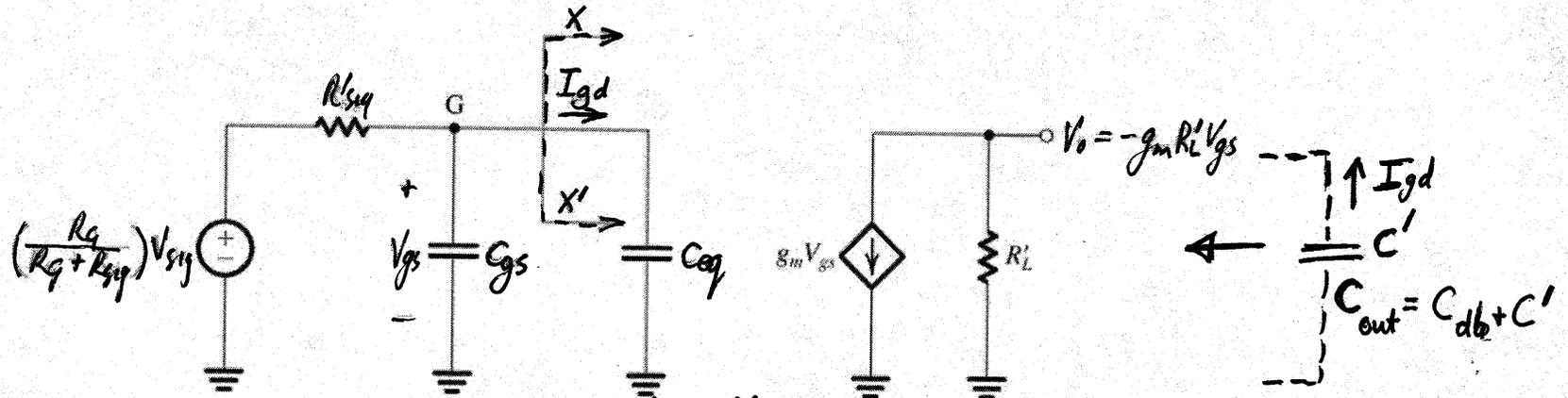

$$\frac{V_o}{V_{sig}} = -\frac{R_g}{R_g + R_{sig}} g_m R_L' \frac{1}{1 + s/\omega_H}$$

$$\left| \frac{V_o}{V_{sig}} \right| \text{ (dB)}$$

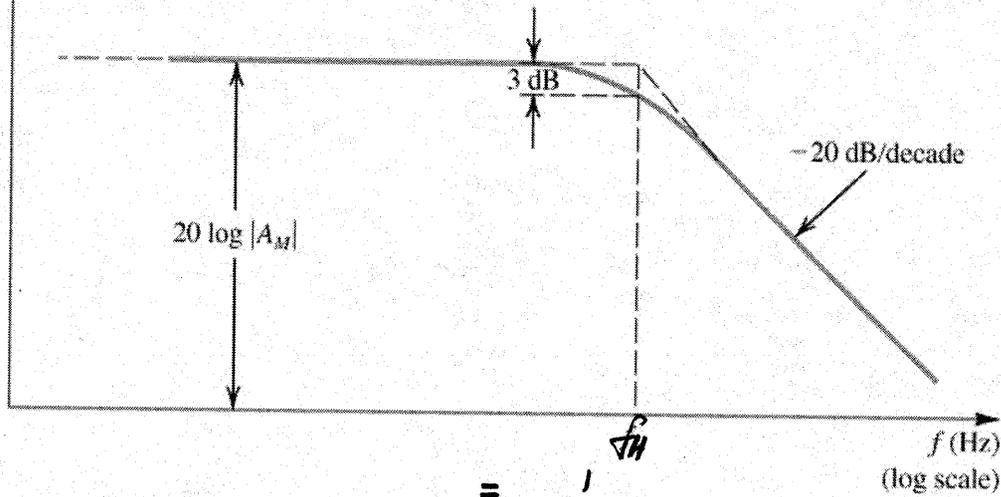This is effectively the Miller capacitance (C_{eq})



$$(d) = \frac{1}{2\pi R_{sig}' C_{in}}$$

Figure 4.50 (Continued) (c) the equivalent circuit with C_{gd} replaced at the input side with the equivalent capacitance C_{eq} ; (d) the frequency response plot, which is that of a low-pass single-time-constant circuit.

Could add the second Miller capacitance easily
 $I_{gd} = sC_{gd}(1 + g_m R_L') V_{gs}$
 $= -sC' V_o$
 $= sC_{gd}(V_{gs} - V_o)$
 $= -sC_{gd}(V_o - (-\frac{V_o}{g_m R_L'}))$
 $= -sV_o \left(1 + \frac{1}{g_m R_L'}\right) C_{gd}$
 $\therefore C' = C_{gd} \left(1 + \frac{1}{g_m R_L'}\right)$
 $\approx C_{gd}$
 as expected from the Miller formula.

Exercise 4.38


Exercise 4.39

Low Frequency Response

$$V_g = \frac{R_g}{R_g + R_{sig} + \frac{1}{sC_{c1}}} V_{sig}$$

$$\frac{V_g}{V_{sig}} = \frac{R_g}{R_g + R_{sig}} \frac{1}{1 + \frac{1}{sC_{c1}(R_g + R_{sig})}}$$
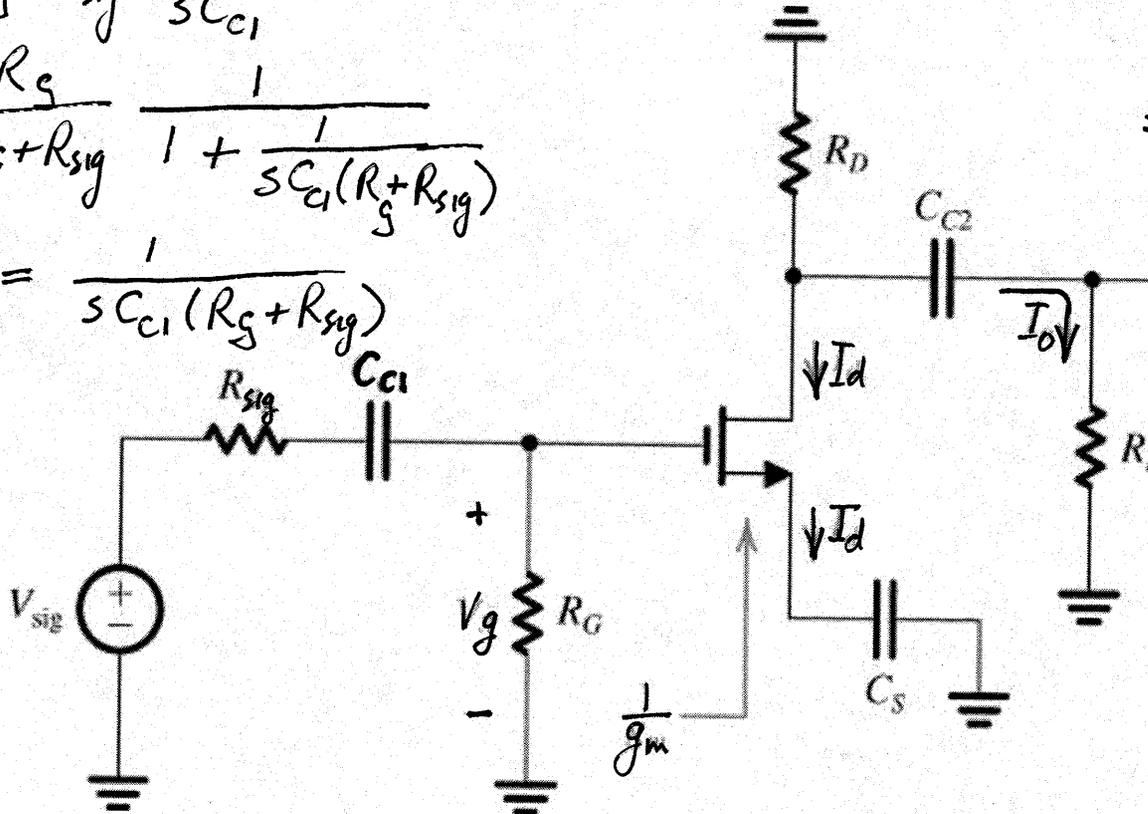
$$\therefore \omega_{p1} = \frac{1}{sC_{c1}(R_g + R_{sig})}$$



$$I_o = \frac{R_D}{R_D + R_L + \frac{1}{sC_{c2}}} (-I_D)$$

by current division

$$V_o = I_o R_L = - \frac{R_D R_L}{R_D + R_L + \frac{1}{sC_{c2}}} I_D$$

$$= - \left(\frac{R_D R_L}{R_D + R_L} \right) \frac{I_D}{1 + \frac{1}{sC_{c2}(R_D + R_L)}}$$

$$\therefore \omega_{p3} = \frac{1}{(R_D + R_L)C_{c2}}$$

From the T-equivalent circuit: $I_d = \frac{V_g}{\frac{1}{g_m} + \frac{1}{sC_s}} = \frac{g_m V_g}{1 + \frac{1}{sC_s(\frac{1}{g_m})}}$


$$\therefore \omega_{p2} = g_m / C_s$$

Figure 4.51 Analysis of the CS amplifier to determine its low-frequency transfer function. For simplicity, r_o is neglected.

$$\frac{V_o}{V_{sig}} = - \frac{R_g}{R_g + R_{sig}} g_m (R_D || R_L) \frac{s}{s + \omega_{p1}} \cdot \frac{s}{s + \omega_{p2}} \cdot \frac{s}{s + \omega_{p3}}$$

Typically $C_{c1} \sim C_{c2}$ and $1/g_m \ll R_g + R_{sig}, R_L + R_D$

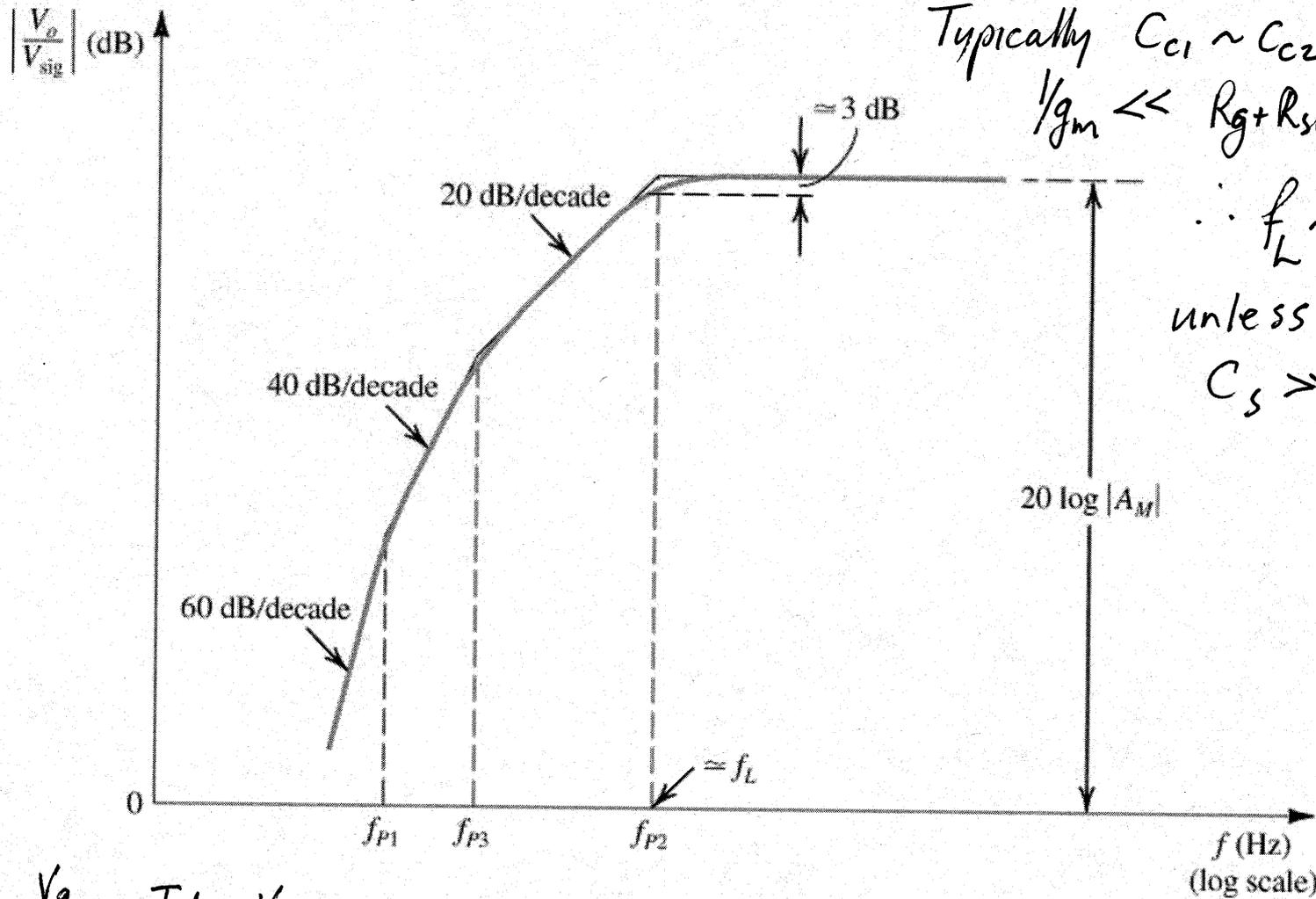$\therefore f_L \sim f_{p2}$
unless $C_s \gg C_{c1}, C_{c2}$



$$\frac{V_o}{V_{sig}} = \frac{V_g}{V_{sig}} \cdot \frac{I_d}{V_g} \cdot \frac{V_o}{I_d}$$

Figure 4.52 Sketch of the low-frequency magnitude response of a CS amplifier for which the three break frequencies are sufficiently separated for their effects to appear distinct.

1
2
3

Exercise 4.40

Assignment #8

***5.156**

5.159 & 5.160

4.92 & 4.93

4.101 & 4.102

Ex 4.36 n-channel MOSFET $t_{ox} = 10\text{nm}$ $L = 1.0\mu\text{m}$ $W = 10\mu\text{m}$
 $L_{ov} = 0.05\mu\text{m}$ $C_{sbo} = C_{dso} = 10\text{fF}$
 $V_{SB} = 1\text{V}$ $V_{DS} = 2\text{V}$
 $\uparrow V_{DB}?$

Calculate C_{ox} , C_{ov} , C_{gs} , C_{gd} , C_{sb} , C_{db}

Ex 4.37 Calculate f_T for MOSFET above, operating at $100\mu\text{A}$
with $k_n' = 160\mu\text{A}/\text{V}^2$

Ex 4.36

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11} \text{ F/m}}{10 \times 10^{-9} \text{ m}} = 3.45 \times 10^{-3} \text{ F/m}^2 \\ = 3.45 \text{ fF}/\mu\text{m}^2$$

$$C_{ov} = WL_{ov} C_{ox} = 10 \mu\text{m} \times 0.5 \mu\text{m} \times 3.45 \text{ fF}/\mu\text{m}^2 \\ = 1.725 \text{ fF}$$

$$C_{gs} = \frac{2}{3} WL C_{ox} + C_{ov} = \frac{2}{3} \cdot 10 \mu\text{m} \cdot 1 \mu\text{m} \cdot 3.45 \text{ fF}/\mu\text{m}^2 + 1.725 \text{ fF} \\ = 23 + 1.725 = 24.725 \text{ fF}$$

$$C_{gd} = C_{ov} = 1.725 \text{ fF}$$

$$C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_0}}} = \frac{10 \text{ fF}}{(1 + 1/6)^{1/2}} = 6.1 \text{ fF}$$

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}} = \frac{10 \text{ fF}}{(1 + 2/6)^{1/2}} = 4.1 \text{ fF}$$

Note
 $V_0 \sim 0.6 \text{ V}$
typ.

$$4.37 \quad f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})}$$

$$\frac{W}{L} = \frac{10 \mu\text{m}}{1 \mu\text{m}} = 10$$

$$g_m = \sqrt{2k_n' \frac{W}{L} I_D} = (2 \times 160 \times 10^{-6} \times 10 \times 100 \times 10^{-6})^{1/2}$$

$$= \sqrt{2} \times 4 \times 10^{-4} = 0.5656 \times 10^{-3}$$

$$= 565.6 \mu\text{A/V}$$

$$\therefore f_T = \frac{565.6 \times 10^{-6}}{2\pi (24.725 + 1.725) \times 10^{-15}} = \frac{565.6}{2\pi \times 26.45} \times 10^9$$

$$= 3.4 \text{ GHz} \quad \left(3.79 \text{ GHz in book because uses } \frac{W}{L} = 12 \right)$$

Ex 4.38

For a ^{CS} amplifier of Example 4.12, find A_m & f_H when R_{sig} reduced from $100\text{K}\Omega$ to $10\text{K}\Omega$.

$$R_g = 4.7\text{M}\Omega \quad R_D = R_L = 15\text{K}\Omega \quad g_m = 1\text{mA/V} \quad r_o = 150\text{K}\Omega$$

$$C_{gs} = 1\text{pF} \quad C_{gd} = 0.4\text{pF}$$

Ex 4.39

For same C_{gs} but smaller C_{gd} , what is max C_{gd} for $f_H \geq 1\text{MHz}$? ($R_{sig} = 100\text{K}\Omega$)

Ex 4.38

$$A_m = - \frac{R_g}{R_g + R_{sig}} g_m R_L'$$

From Example 4.12

$$\begin{array}{l} \uparrow \qquad \qquad \uparrow \\ 1 \text{ mA/V} \quad 7.14 \text{ K}\Omega \\ \tau_o \parallel R_L \parallel R_D \end{array}$$

$$= - \frac{4.7 \times 10^3}{4.7 \times 10^3 + 10 \times 10^3} \times 10^{-3} \times 7.14 \times 10^3$$

$$= - 7.14 \frac{4.7}{4.71} = - 7.12 \quad \left(\begin{array}{l} \text{compare} \\ -7 \text{ for} \\ R_{sig} = 100 \text{K} \end{array} \right)$$

$$f_H = \frac{1}{2\pi C_{in} (R_{sig} \parallel R_g)}$$

$$= \frac{1}{2\pi \cdot 4.26 \times 10^{-12} \cdot \frac{10 \times 4700}{47.10} \cdot 10^3}$$

$$= 3.7 \text{ MHz.}$$

$$\begin{aligned} C_m &= C_{gs} + (1 + g_m R_L') C_{gd} \\ &= 4.26 \text{ pF} \\ &\text{(unchanged from Example 4.12)} \end{aligned}$$

Ex 4.39 For $f_H \geq 1 \text{ MHz}$.

$$f_H = \frac{1}{2\pi C_{in} (R_{sig} \parallel R_g)}$$

$$= \frac{1}{2\pi (C_{gs} + C_{eq}) \frac{(1/4.7) \times 10^6}{4.8}}$$

$$\begin{aligned} C_{eq} &= (1 + g_m R_L') C_{gd} \\ &= (1 + 10^{-3} \times 7.14 \times 10^3) C_{gd} \\ &= 8.14 C_{gd} \\ &= 8.14 C_{gd}' \text{ pF} \end{aligned}$$

$$\therefore \frac{1}{2\pi \cdot 98 \cdot 10^3 \cdot 10^{-12} (1 + 8.14 C_{gd}')} \geq 10^6$$

$$\begin{aligned} C_{gd}' &\leq \left(\frac{10^3}{2\pi \cdot 98} - 1 \right) / 8.14 \\ &\leq 0.077 \text{ pF} = 77 \text{ fF} \end{aligned}$$

098

Ex 4.40

CS amplifier

$$C_{c1} = C_{c2} = C_s = 1 \mu\text{F}$$

$$R_g = 10 \text{ M}\Omega \quad R_{\text{sig}} = 100 \text{ K}\Omega$$

$$R_L = R_D = 10 \text{ K}\Omega \quad g_m = 2 \text{ mA/V}$$

Find A_m , f_{p1} , f_{p2} , f_{p3} , f_L

Ex. 4.40

$$\begin{aligned} A_m &= - \frac{R_g}{R_g + R_{sig}} \cdot g_m (R_L \parallel R_D) \\ &= - \frac{10M}{10M + 1M} \cdot 2 \times 10^{-3} \frac{10 \times 10^3}{10 + 10} \cdot 10^3 \\ &= - \frac{10}{10.1} \times 2 \frac{100^{10}}{20} \frac{10^{-3}}{10^{-3}} \cdot 10^3 = -9.9 \end{aligned}$$

$$f_{p1} = \frac{1}{2\pi C_{c1} (R_g + R_{sig})} = \frac{1}{2\pi \cdot 10^{-6} \cdot 10.1 \times 10^6} = \frac{1}{20.2\pi} = 0.015 \text{ Hz}$$

$$f_{p2} = \frac{g_m}{2\pi C_s} = \frac{2 \times 10^{-3}}{2\pi \cdot 10^{-6}} = \frac{10^3}{\pi} = 318.3 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_{c2} (R_L + R_D)} = \frac{1}{2\pi \cdot 10^{-6} \cdot 20 \times 10^3} = \frac{10^2}{4\pi} = 7.96 \text{ Hz}$$

$$\therefore f_L \approx f_{p2} = 318.3 \text{ Hz}$$