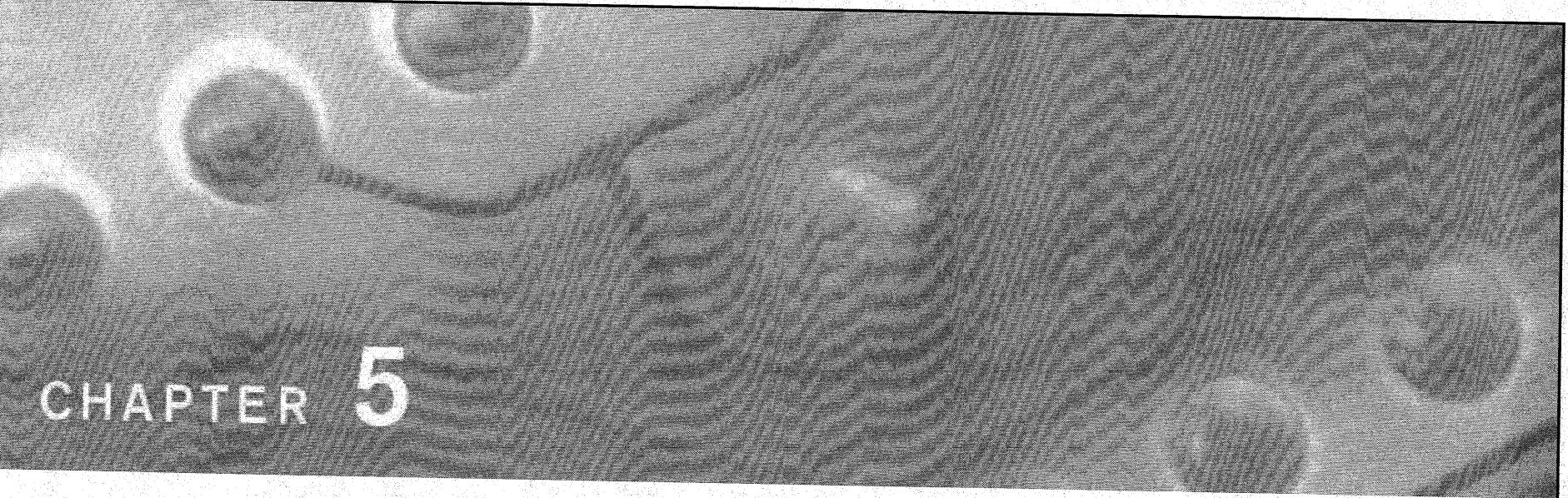


# **ECE321 ELECTRONICS I**

## **FALL 2006**

**PROFESSOR JAMES E. MORRIS**

Lecture 18  
30<sup>th</sup> November, 2006




## CHAPTER 5

# Bipolar Junction Transistors (BJTs)

5.10 BJT Inverter

5.11 SPICE


## BJT INVERTER

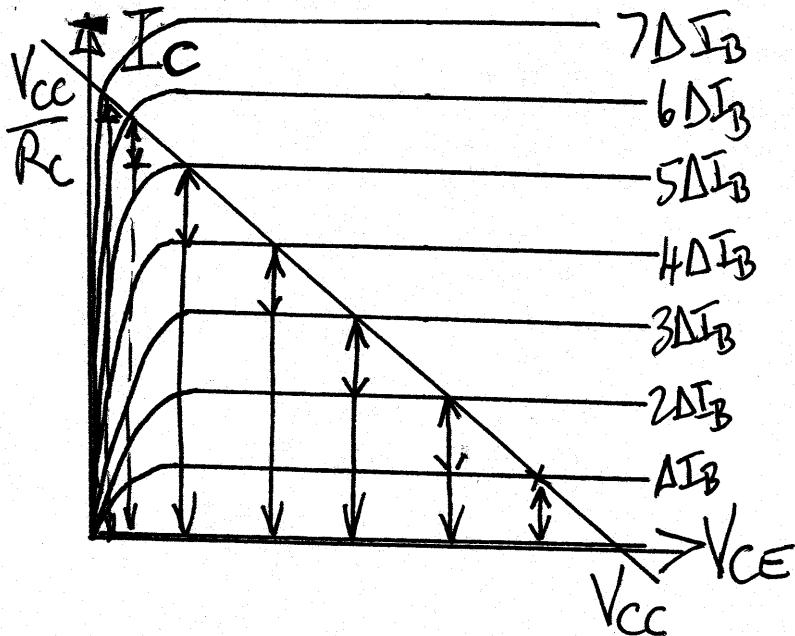

$I_c$  never reaches  $V_{cc}/R_c$  due to transistor saturation.

$$\text{Max } I_c = \frac{(V_{cc} - V_{ce})_{SAT}}{R_c}$$

slowly decreases as  $I_B$  increases.

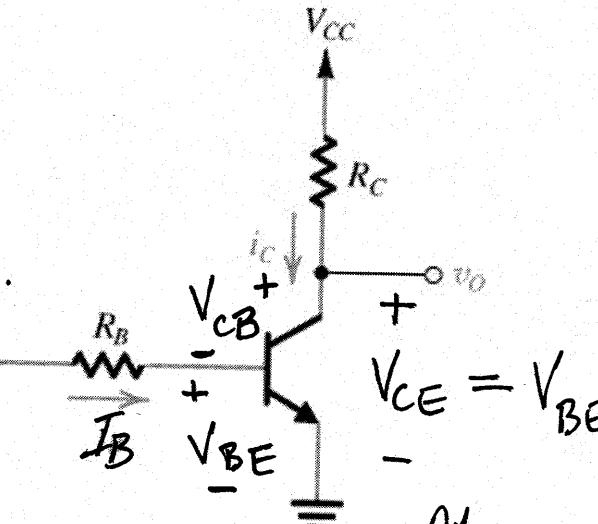

At onset of saturation

$$V_{ce} \approx 0.3V$$

$$V_{cb} \approx -0.4V$$

$$V_{be} \approx 0.7V$$

In saturation (for example)

$$V_{ce} \approx 0.25V$$

$$V_{cb} \approx -0.5V$$

$$V_{be} \approx 0.75V$$

$$\Delta I_c = \beta \Delta I_B$$

until  $5 \rightarrow 6 \Delta B$


&  $I_c$  characteristics enter non-linear region, i.e. saturation.

As  $I_B, I_c$  increase  $V_{ce}$  decreases towards zero as  $V_{be}$  increases and NEGATIVE  $V_{cb}$  decreases.

Figure 5.74 Basic BJT digital logic inverter.

$\text{BJT off}$   
"1" state

$\text{BJT saturated}$   
"0" state

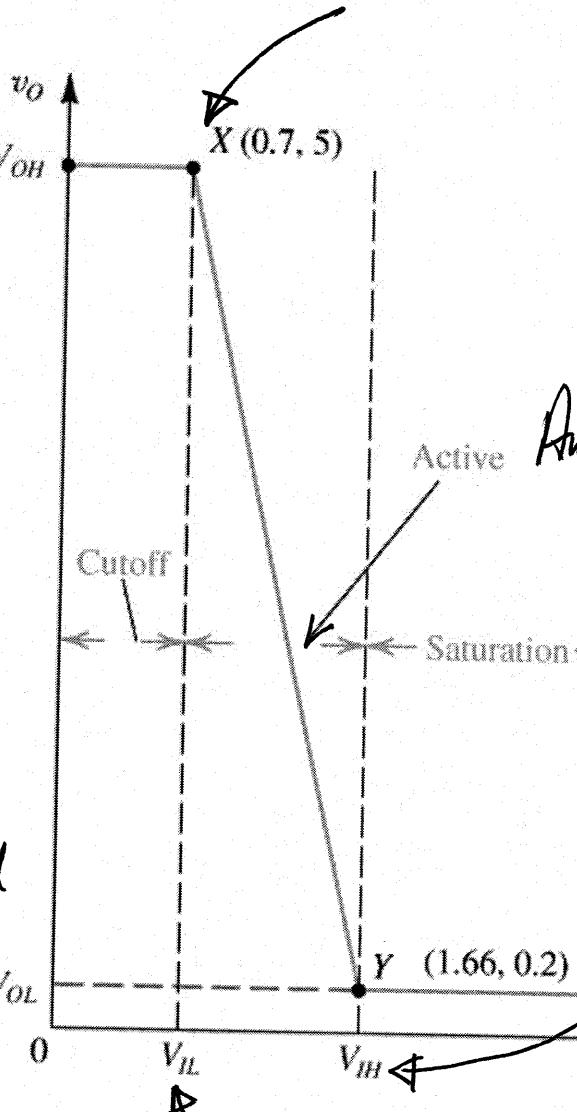

$V_I = 0.7$ , BJT starts to turn on.

Figure 5.75 Sketch of the voltage transfer characteristic of the inverter circuit of Fig. 5.74 for the case  $R_B = 10 \text{ k}\Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $\beta = 50$ , and  $V_{CC} = 5 \text{ V}$ . For the calculation of the coordinates of X and Y, refer to the text.

$$\text{Amplifier gain } \approx \beta \frac{R_C}{R_B + R_L}$$

$$V_{IN} \text{ for saturation} \approx \\ \text{Saturates when} \\ (V_{CC} - V_{CE})_{SAT} < \beta \frac{(V_I - V_{BE})}{R_B}$$

$$\therefore V_{IH} = \frac{R_B}{\beta R_C} [V_{CC} - V_{CE}]_{SAT} + V_{BE}$$

$$\frac{V_{CC} = 5}{R_C = 1 \text{ k}} \quad \frac{\beta = 50}{R_B = 10 \text{ k}} \Rightarrow 1.66 \text{ V}$$


$$\therefore \text{"Hi" noise margin} \\ \text{NM}_H = V_{OH} - V_{IH}$$

$$= 5 - 1.66$$

$$= 3.34 \text{ V}$$

$$\& NML = V_{IL} - V_{OL} \\ = 0.7 - 0.2 = 0.5 \text{ V}$$

# Stored base charge

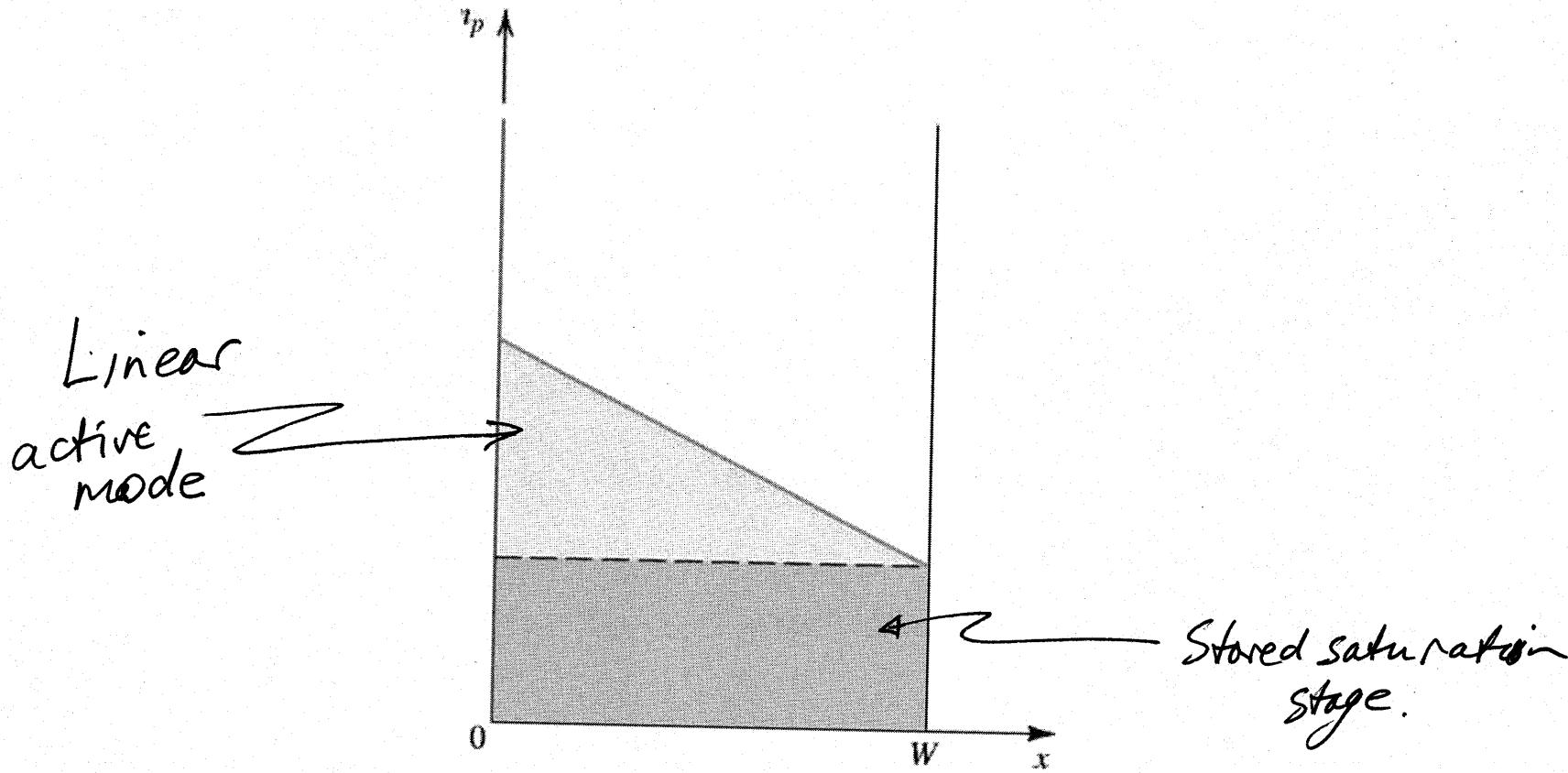


**Figure 5.76** The minority-carrier charge stored in the base of a saturated transistor can be divided into two components: That in blue produces the gradient that gives rise to the diffusion current across the base, and that in gray results from driving the transistor deeper into saturation.

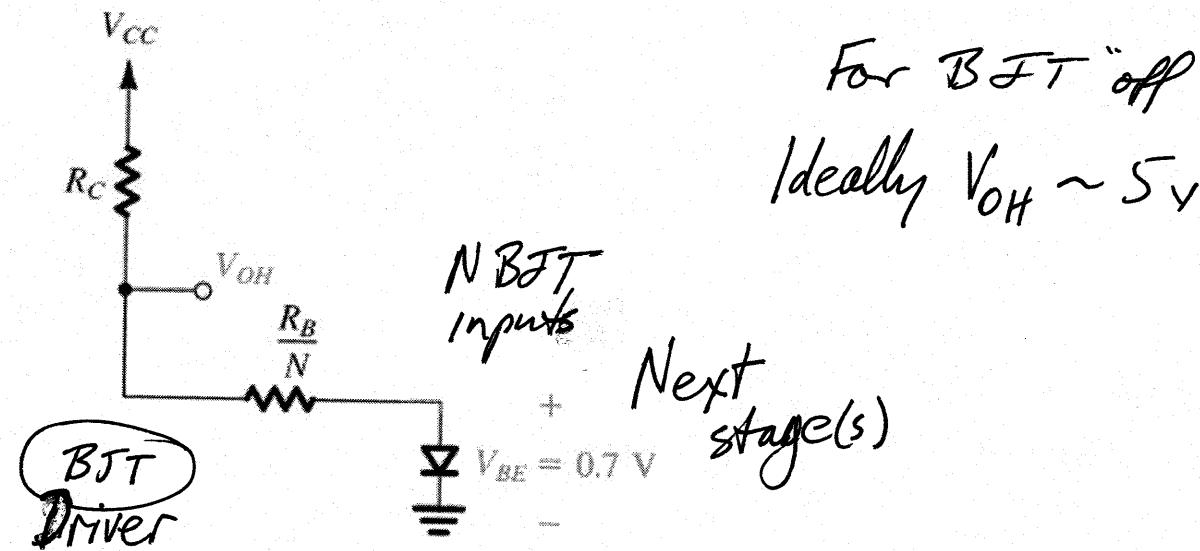For loading by  $N$  (multiple) gates

$$R_B = 10K\Omega \quad R_C = 1K\Omega \quad V_{CC} = 5V \quad N = 5$$


For



$$\begin{aligned} V_{OH} &= 0.7 + \frac{R_B}{N} \cdot \frac{V_{CC} - 0.7V}{\frac{R_B}{N} + R_C} \\ &\approx 3.6V \end{aligned}$$

Figure E5.53

# Transport Ebers Moll model

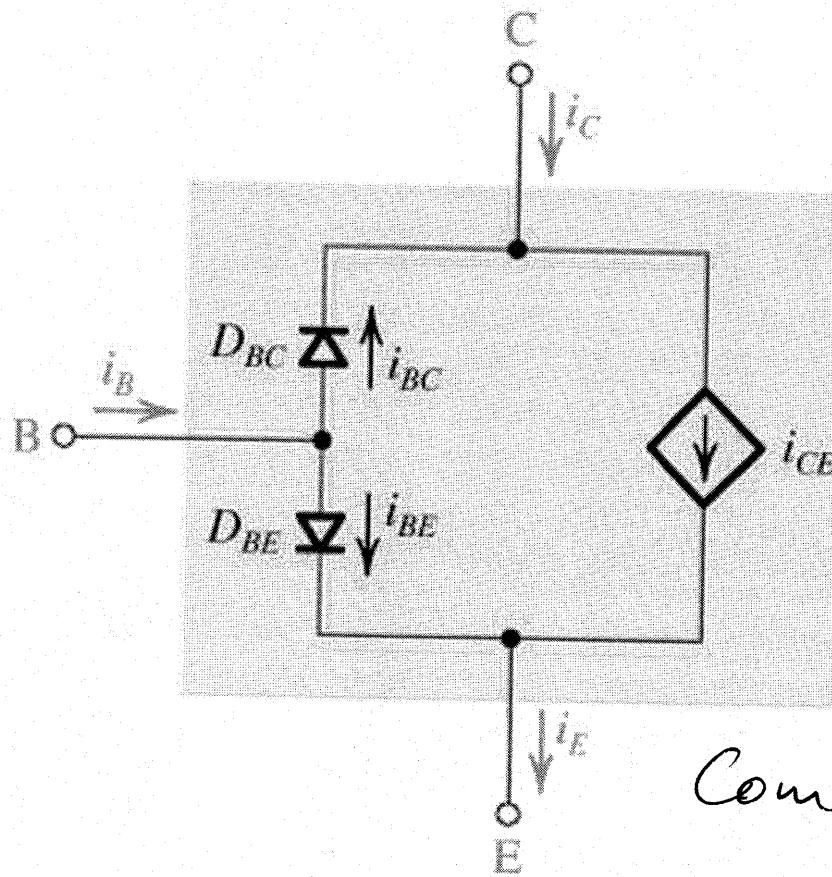

Compare Injection Ebers -Moll.


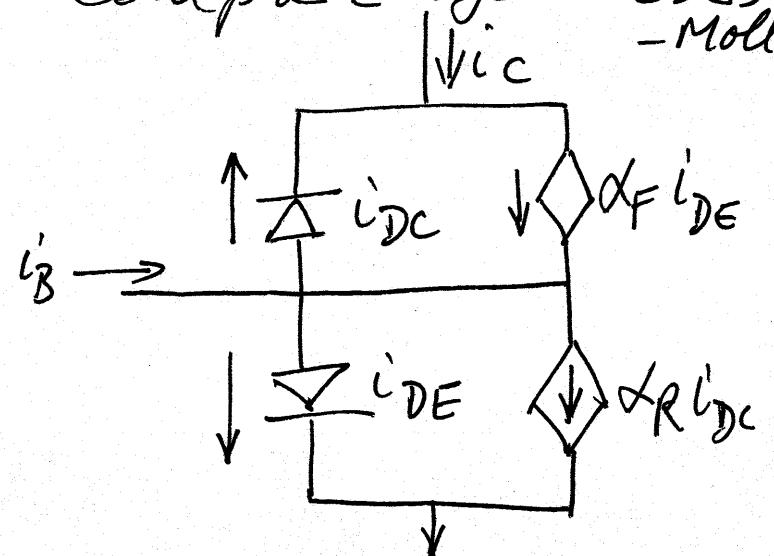


Figure 5.77 The transport form of the Ebers-Moll model for an *npn* BJT.

# HF Model

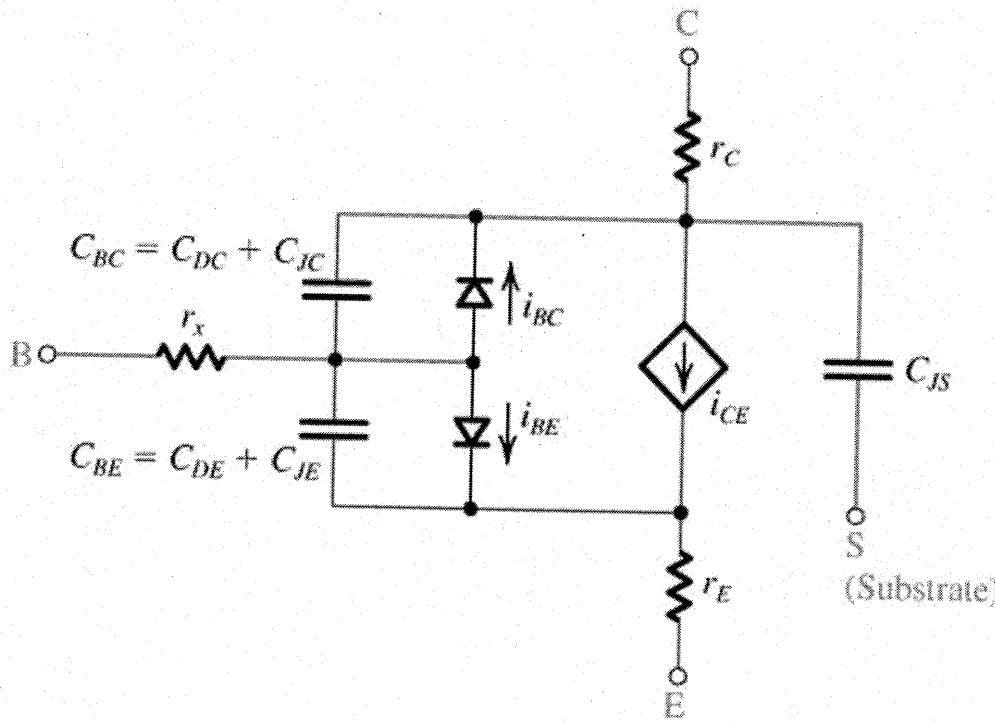

Ebers-Moll → Gummel-Poos circuit — SPICE  
 $I \propto Q_n$  Base charge  
 $\propto Q_B$


Switching base charge  
 $I \propto Q_B$ ) while base charge exists → turn-off Gummel-Poos

Figure 5.78 The SPICE large-signal Ebers-Moll model for an npn BJT.


PARAMETERS:

$IB = 10\mu$

$VCE = 2V$

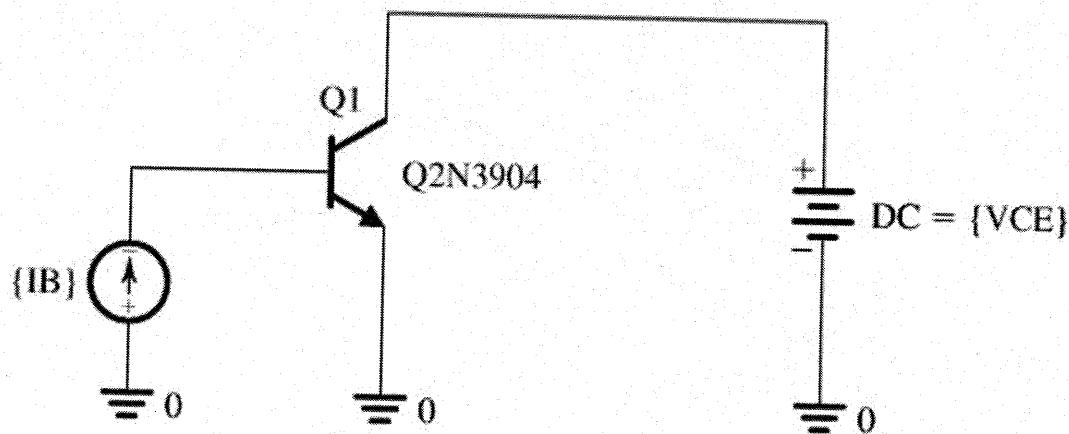

**Figure 5.79** The PSpice testbench used to demonstrate the dependence of  $\beta_{dc}$  on the collector bias current  $I_C$  for the Q2N3904 discrete BJT (Example 5.20).

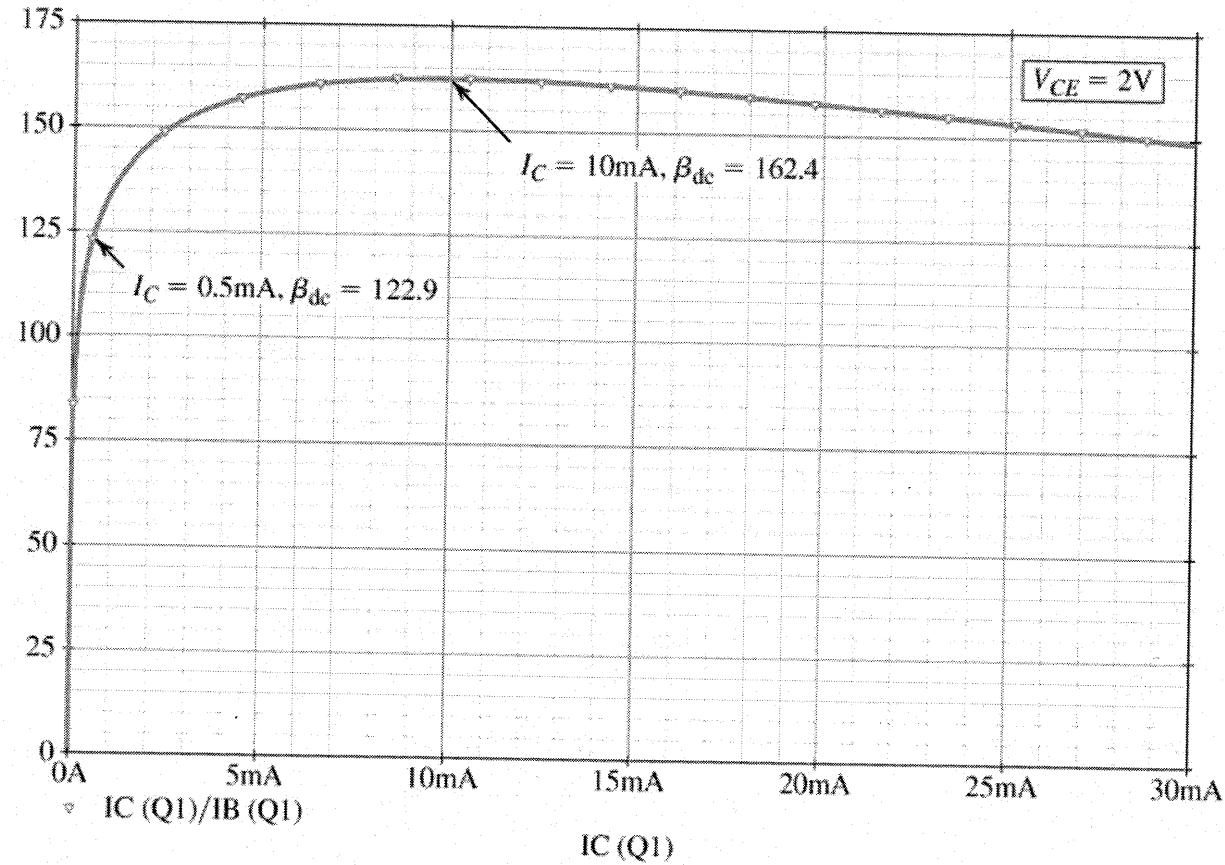

**Figure 5.80** Dependence of  $\beta_{dc}$  on  $I_C$  (at  $V_{CE} = 2\text{V}$ ) in the Q2N3904 discrete BJT (Example 5.20).

PARAMETERS:

$$CE = 10\mu$$

$$CCI = 10\mu$$

$$CCO = 10\mu$$

$$RC = 10K$$

$$RB = 340K$$

$$RE = 6K$$



$$Rce = 130$$

$$RL = 10K$$

$$Rsig = 10K$$


$$VCC = 5$$

$$VEE = -5$$

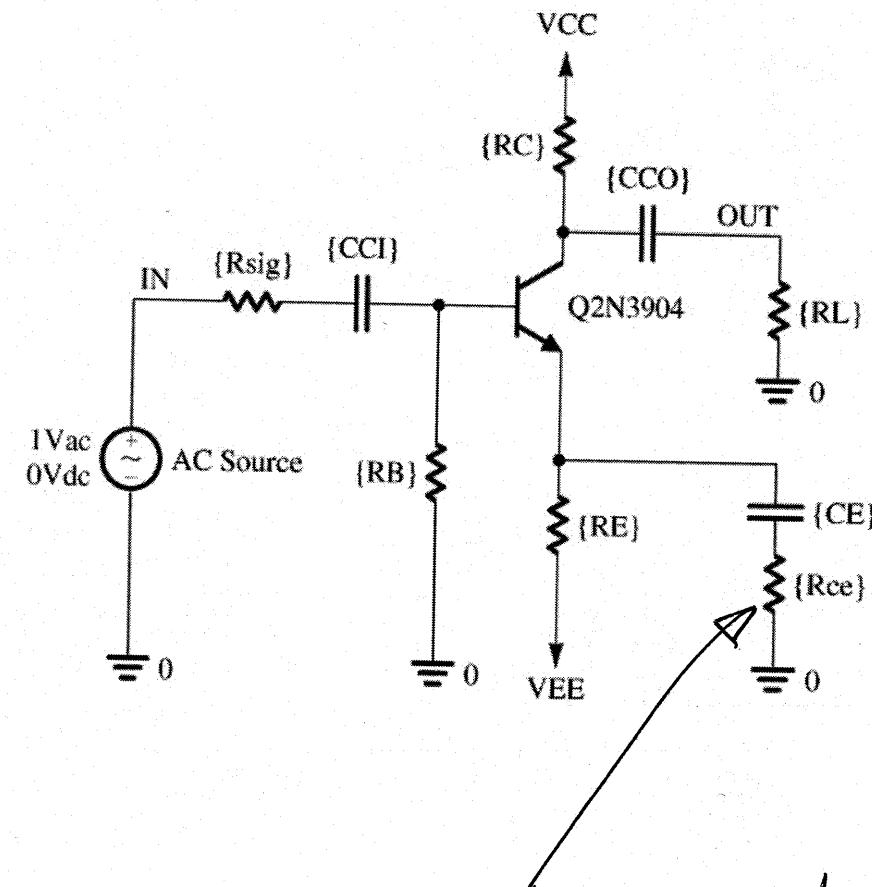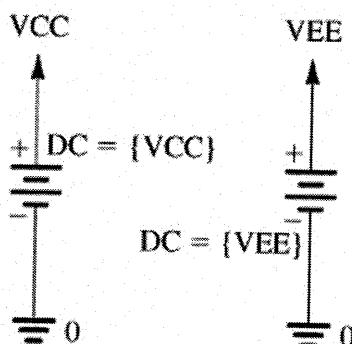

Use resistor to  
control f.b.

Figure 5.81 Capture schematic of the CE amplifier in Example 5.21.

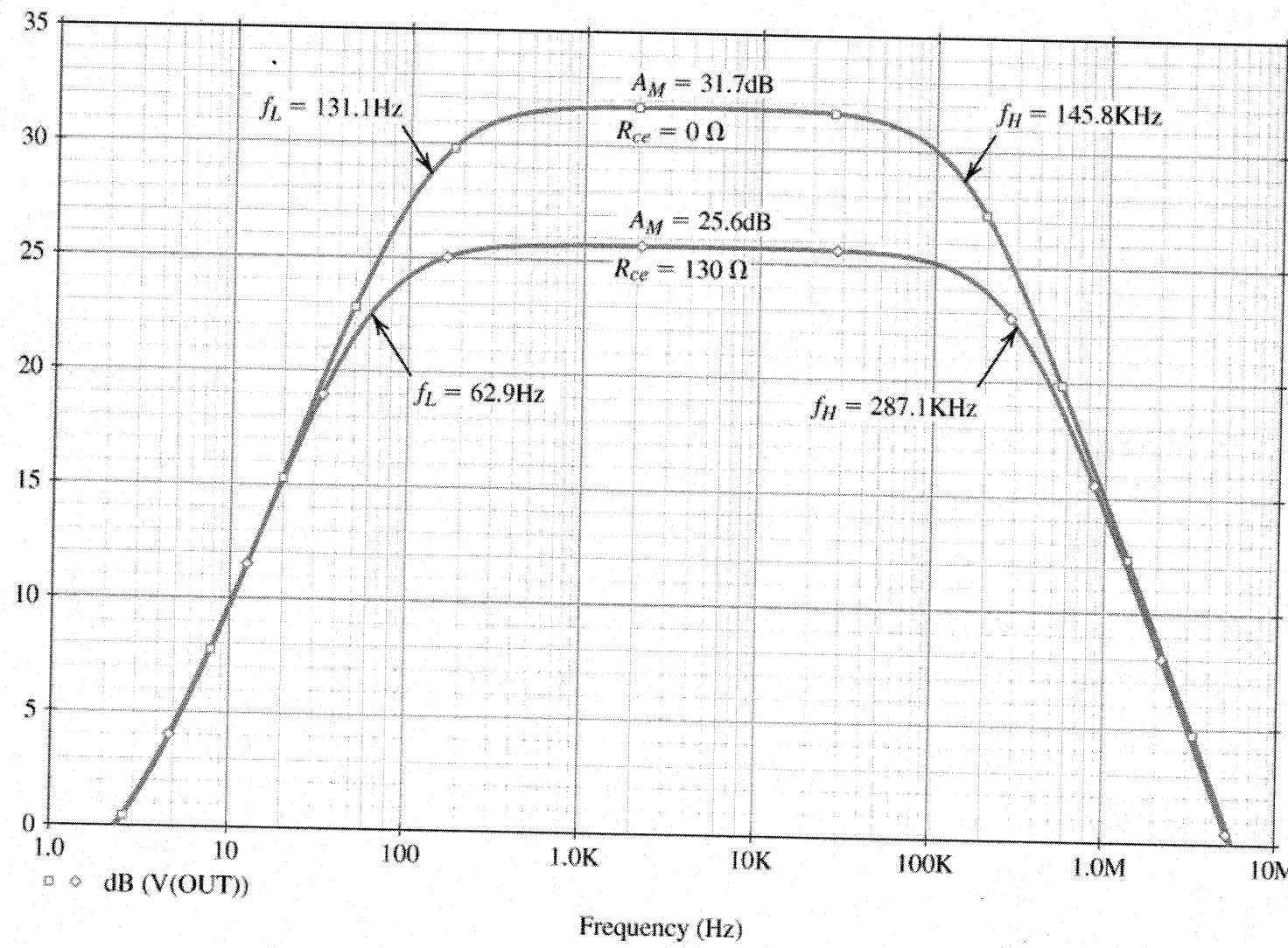

**Figure 5.82** Frequency response of the CE amplifier in Example 5.21 with  $R_{ce} = 0$  and  $R_{ce} = 130 \Omega$ .