

ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 2

28th September, 2006

CHAPTER 2

Operational Amplifiers

2.1 Ideal op-amps



Revision

2.2 Inverting Amplifier

2.3 Non-Inverting Amplifierr



*Revision
except*

2.2.2/2.3.3

Ideal Op-amp


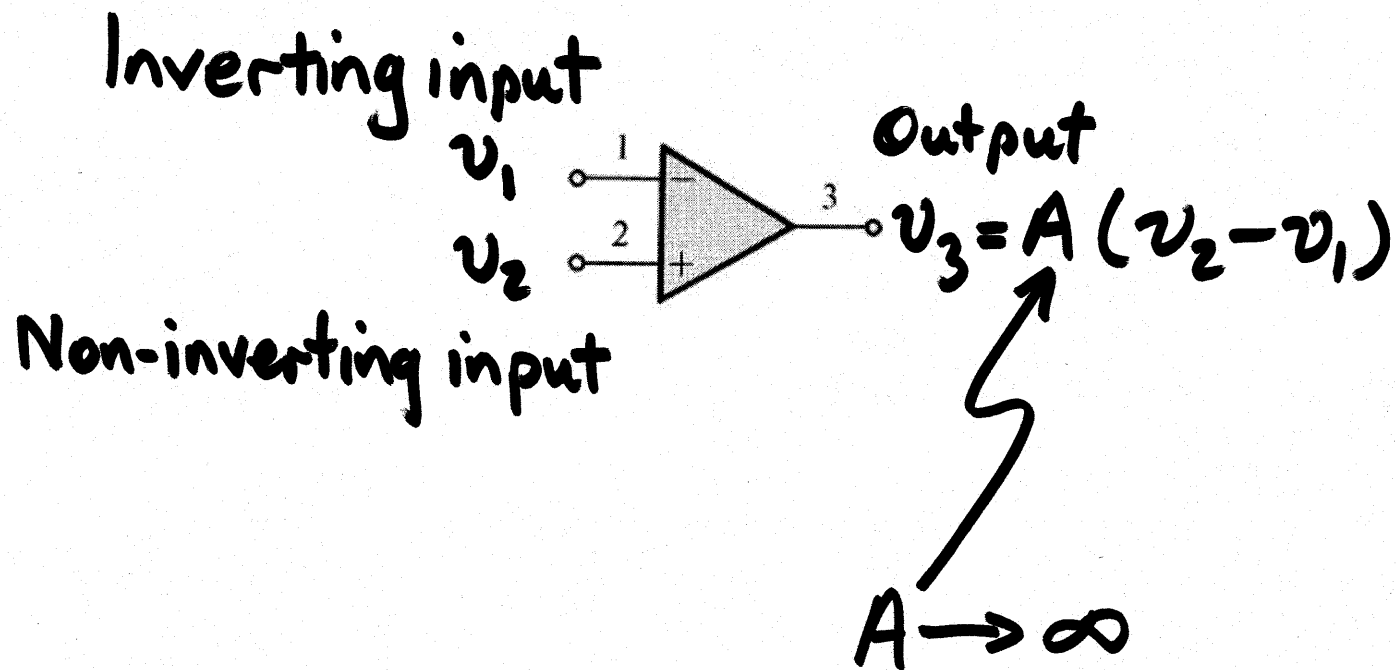


Figure 2.1 Circuit symbol for the op amp.


Implied Power Supply Connections

Conventional

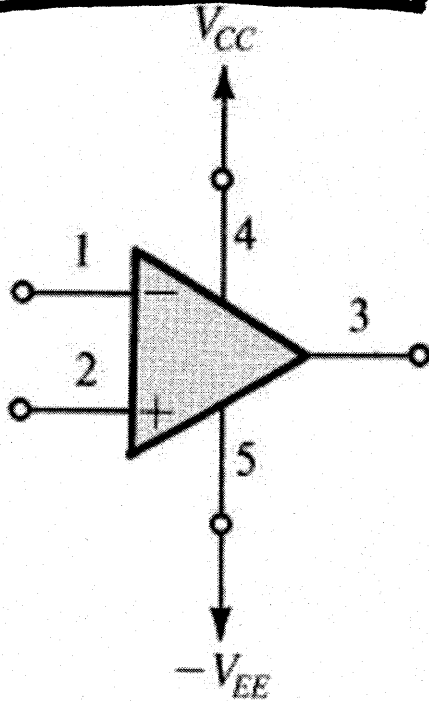

(a)

Actual

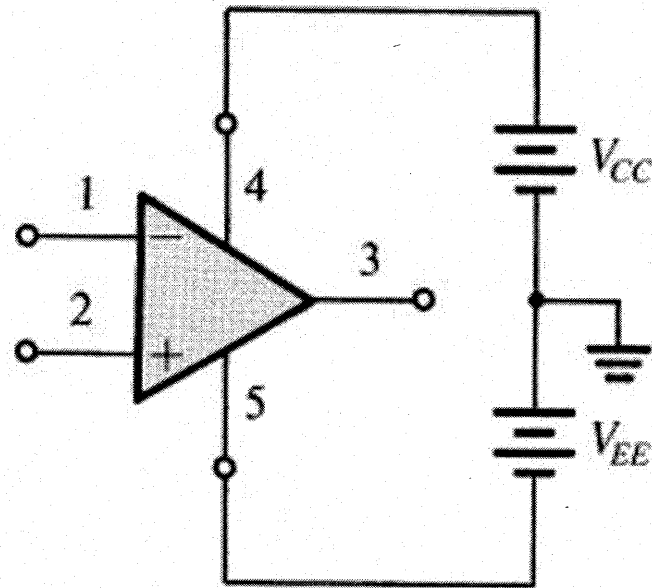


(b)

"Conventional" format common in transistor ckt's, etc but power supplies usually omitted entirely in op-amp circuit diagrams.

Figure 2.2 The op amp shown connected to dc power supplies

$$R_{in} = \infty$$
$$\text{So } i_1 \text{ \& } i_2 = 0$$

$$R_{out} = 0$$

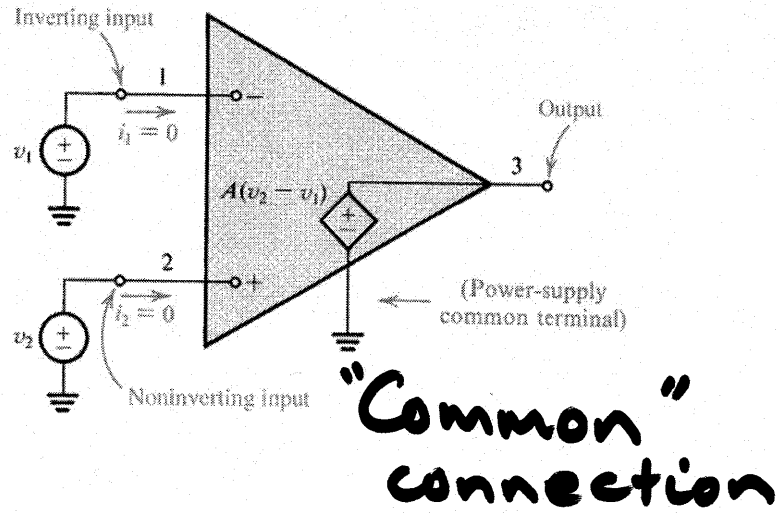

Ideal Op-amp equivalent circuit


Figure 2.3 Equivalent circuit of the ideal op amp.

Actually $A_v \longrightarrow A_d$ (differential gain) = v_{od}/v_{id}
 & A_{cm} (common-mode gain) = $v_o)_{cm} / v_{icm}$

Average values

$$v_{id} = v_2 - v_1$$

$$v_{icm} = \frac{v_2 + v_1}{2}$$

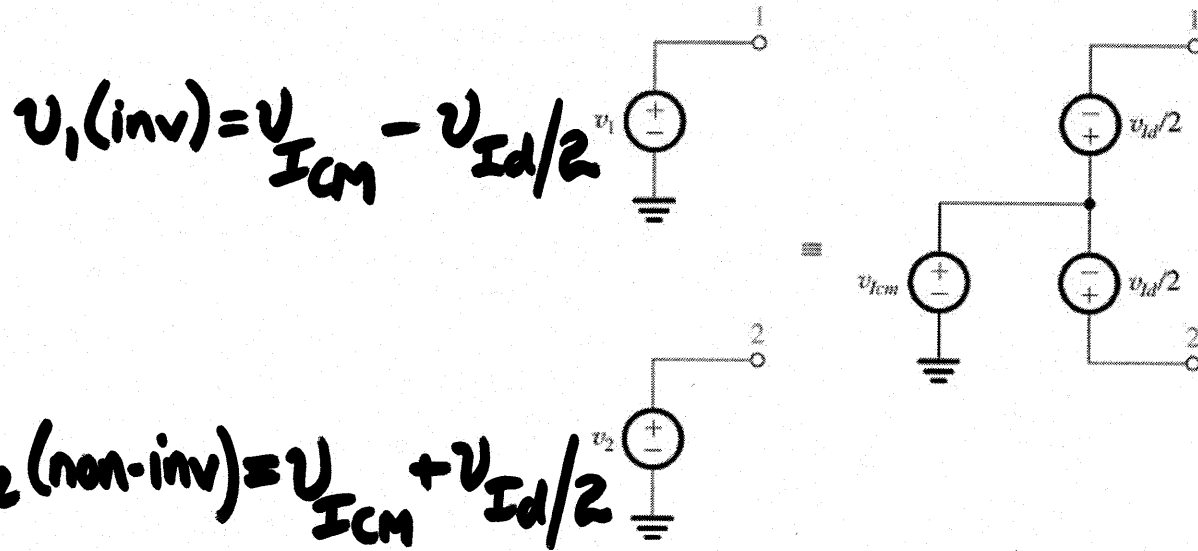

$$v_1(\text{inv}) = v_{icm} - v_{id}/2$$

$$v_2(\text{non-inv}) = v_{icm} + v_{id}/2$$

$A_{cm} \longrightarrow 0$ in the ideal opamp

Figure 2.4 Representation of the signal sources v_1 and v_2 in terms of their differential and common-mode components.

Ex. 2.2. Ideal op-amp, except OL gain $A = 10^3$.

Opamp used in a feedback amplifier; 2 voltages measured — find the third. (Identify CM & diff components of v_E)

Note: "Ideal" $\rightarrow A_{CM} = 0$

$$v_3 = A(v_2 - v_1)$$

$$\therefore v_1 = v_2 - v_3/A$$


$$\therefore v_2 = v_1 + v_3/A$$

	v_1	v_2	v_3	
(a)	?	0v	2v	$\therefore v_1 = -2\text{mV}$ $v_{Id} = v_2 - v_1 = 2\text{mV}$ $v_{cm} = (v_1 + v_2)/2 = -1\text{mV}$
(b)	?	+5v	-10v	$\therefore v_1 = +5.01\text{v}$ $v_{Id} = -10\text{mV}$ $v_{cm} = 5.005\text{v}$
(c)	1.002v	0.998v	?	$\therefore v_3 = -4\text{v}$ $v_{Id} = -4\text{mV}$ $v_{cm} = 1\text{v}$
(d)	-3.6v	?	-3.6v	$\therefore v_2 = -3.6036\text{v}$ $v_{Id} = -3.6\text{mV}$ $v_{ICM} = -3.6018\text{v}$

Ex. 2.3. Find $v_3(v_1, v_2)$. Find OL (open-loop) gain A for $g_m = 10 \text{ mA/V}$, $R = 10 \text{ k}\Omega$, $\mu = 100$.

$$v_3 = \mu v_d = \mu (g_m v_2 - g_m v_1) R$$

$$= \mu g_m R (v_2 - v_1)$$

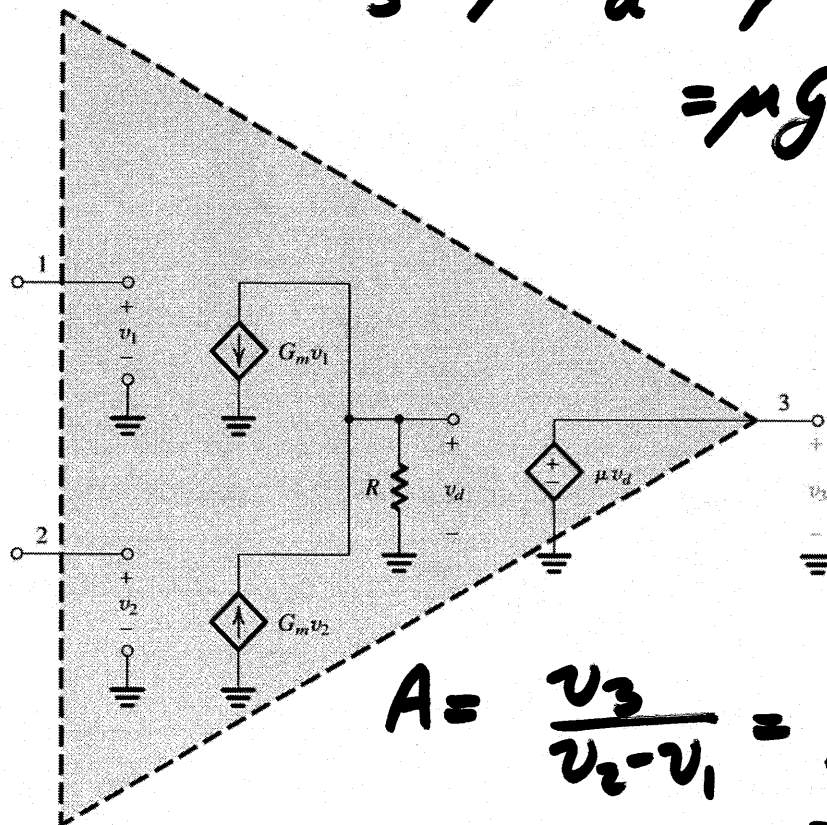

$$A = \frac{v_3}{v_2 - v_1} = \mu g_m R$$

$$= 100 \times 10^{-2} \times 10^4$$

$$= 10^4 \text{ V/V}$$

$$A |_{\text{dB}} = 20 \log_{10} 10^4 = 80 \text{ dB}$$

Figure E2.3

VIRTUAL SHORTCIRCUIT

$$v_3 = A(v_2 - v_1)$$

$$\therefore v_2 - v_1 = v_3/A \xrightarrow[\text{if } v_3 \text{ remains finite}]{A \rightarrow \infty} 0$$


$$\text{i.e. } v_1 = v_2$$

General analysis principle:

With negative feedback
(which keeps v_3 finite)

$$\& A \approx \infty$$

$$\text{then } v_1 \approx v_2$$

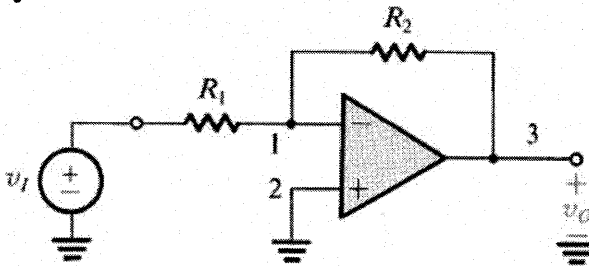

So v_1 sees a

"virtual short circuit"

or here a "virtual ground"

i.e. $v_2 = 0 \therefore v_1 = 0$
even with no physical connection

Figure 2.5 The inverting closed-loop configuration.

Inverting Amplifier



Ideal, so $R_{out} = 0 \Omega$

Negative feedback & OL gain $A = \infty$

$$\therefore v_1 = v_2 = 0$$

$$\therefore i_1 = v_I / R_1$$
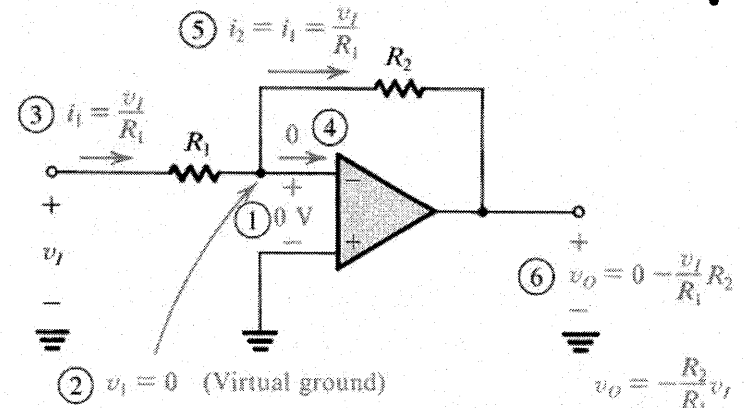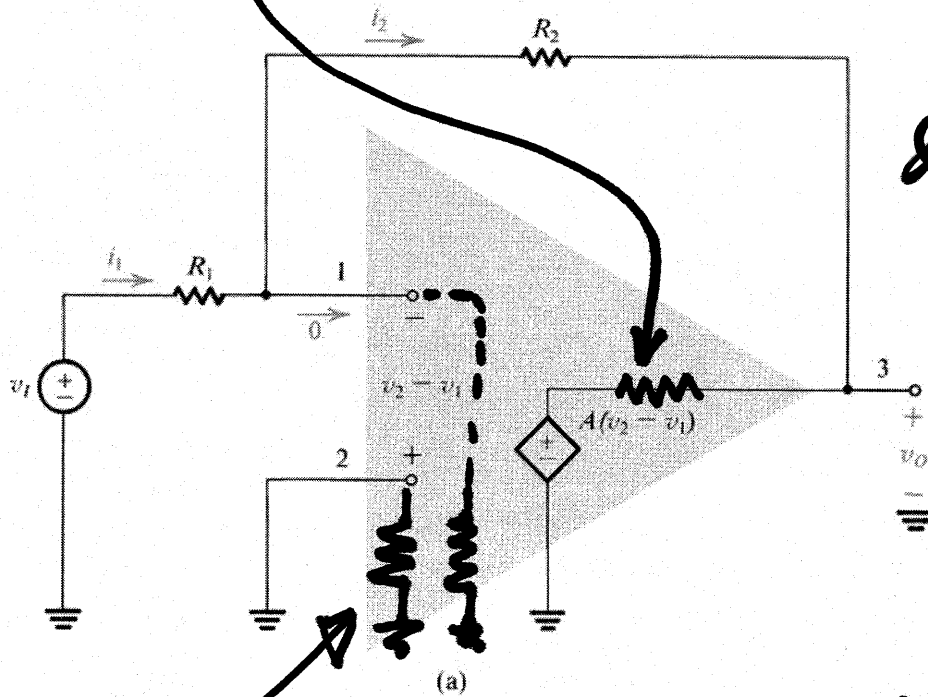
$$\& R_{in1} = \infty, \therefore i_2 = i_1 = v_I / R_1$$



Ideal, so $R_{in1} \& R_{in2} = \infty$

$$\begin{aligned} (R_{out} = 0) \Rightarrow v_O &= 0 - v_I - i_2 R_2 \\ &= 0 - i_2 R_2 \\ &= -\frac{R_2}{R_1} v_I \end{aligned}$$

$$\therefore \text{CL gain } v_O / v_I = -R_2 / R_1$$

Figure 2.6 Analysis of the inverting configuration. The circled numbers indicate the order of the analysis steps.

Trade high A for accuracy & designability. One op-amp eg 741 used in many applications

Another inverting op-amp application (Example 2.2)

① Neg. f.b. $\therefore v^- \approx 0$

② $\therefore i_1 = v_I / R_1$

③ $R_{in} = \infty$

④ $\therefore i_2 = i_1 = v_I / R_1$

⑤ $\therefore v_x = -\left(\frac{v_I}{R_1}\right) R_2$

⑥ $\therefore i_3 = \frac{v_I}{R_1} \frac{R_2}{R_3}$

⑦ $i_4 = i_2 + i_3$
 $= \frac{v_I}{R_1} \left(1 + \frac{R_2}{R_3}\right)$

⑧ $\therefore v_o = v_x - i_4 R_4 = -\frac{v_I}{R_1} \left(R_2 + R_4 + R_4 \frac{R_2}{R_3}\right)$

& $v_o / v_I = -\left(R_2 / R_1\right) \left(1 + R_4 / R_3 + R_4 / R_2\right)$

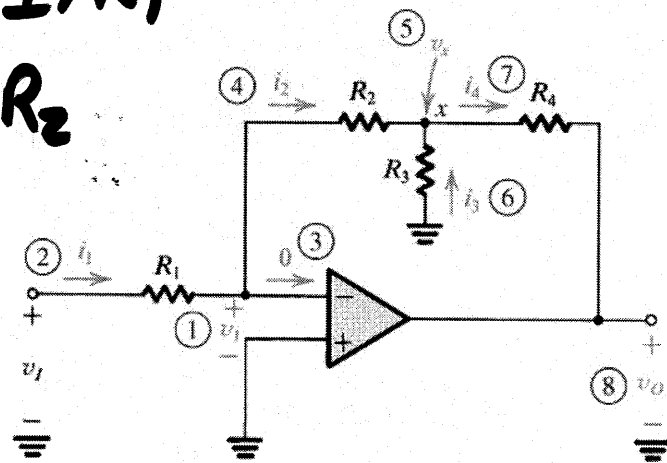


Figure 2.8 Circuit for Example 2.2. The circled numbers indicate the sequence of the steps in the analysis.

Note in previous circuit:

$$\begin{aligned} i_4 &= i_2 + i_3 \\ &= i_1 + \frac{R_2}{R_3} i_1 \end{aligned}$$

∴ As a current amplifier

$$A_i = \frac{i_4}{i_1} = 1 + \frac{R_2}{R_3}$$

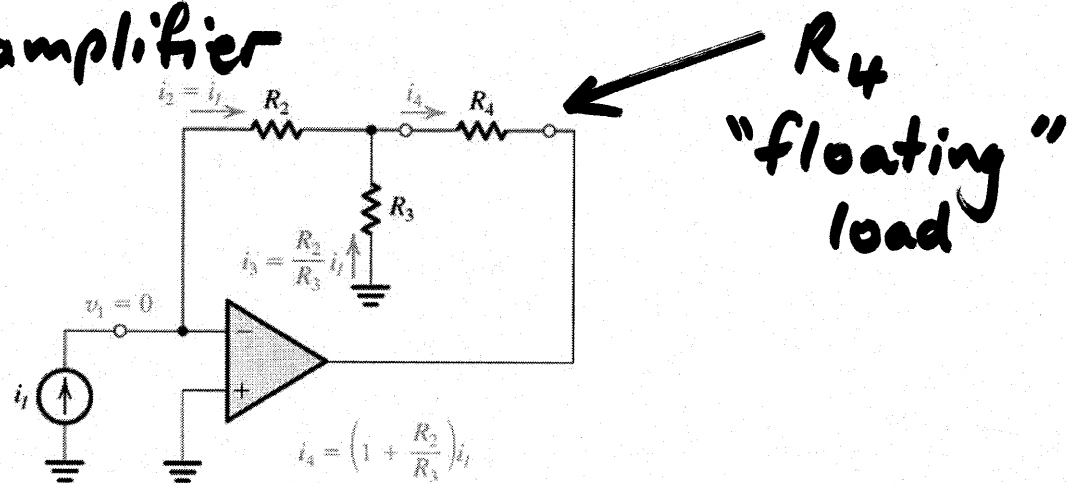



Figure 2.9 A current amplifier based on the circuit of Fig. 2.8. The amplifier delivers its output current to R_4 . It has a current gain of $(1 + R_2/R_3)$, a zero input resistance, and an infinite output resistance. The load (R_4), however, must be floating (i.e., neither of its two terminals can be connected to ground).

Transresistance Amplifier (Voltage out) Ex. 2.5.


(a) Find $R_{in} = v^- / i_I = 0$ (since $v^- = 0$)

Find $v_o = v^- - i' \cdot 10K = 0 - 10K \cdot i_I = -10^4 i_I$

Find $R_m = v_o / i_I = -10^4$

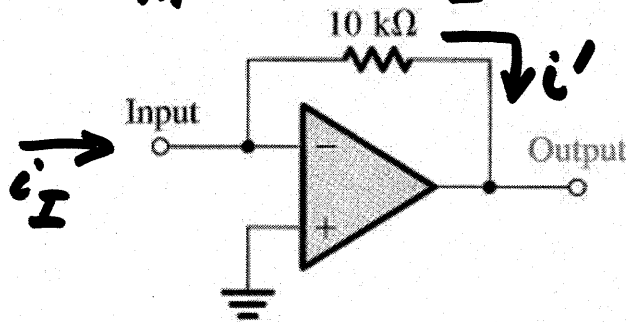

(a)

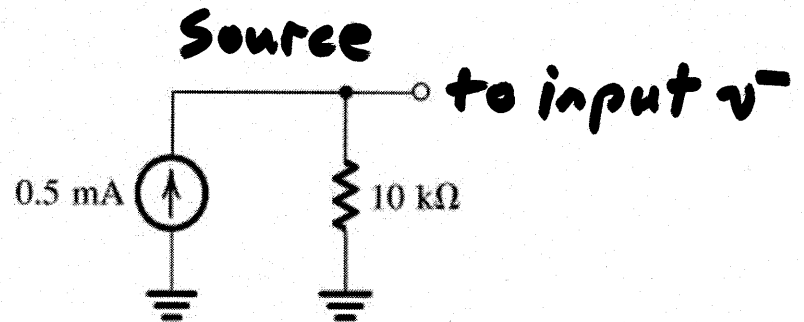

(b)

(b) $v^- = 0 \quad \therefore i_{10K} = 0 \quad \therefore i_I = 0.5 \text{ mA}$


$\therefore v_o = -10K \times 0.5 \text{ mA} = -5 \text{ V}$

Figure E2.5

Ex 2.6. Neg. f.b. $\therefore v_1 = 0 \therefore i_1 = 1\text{V}/1\text{k}\Omega = 1\text{mA}$

$R_{in} = \infty \therefore i_2 = 1\text{mA} \therefore v_o = -10\text{k}\Omega \times 1\text{mA} = -10\text{V}$

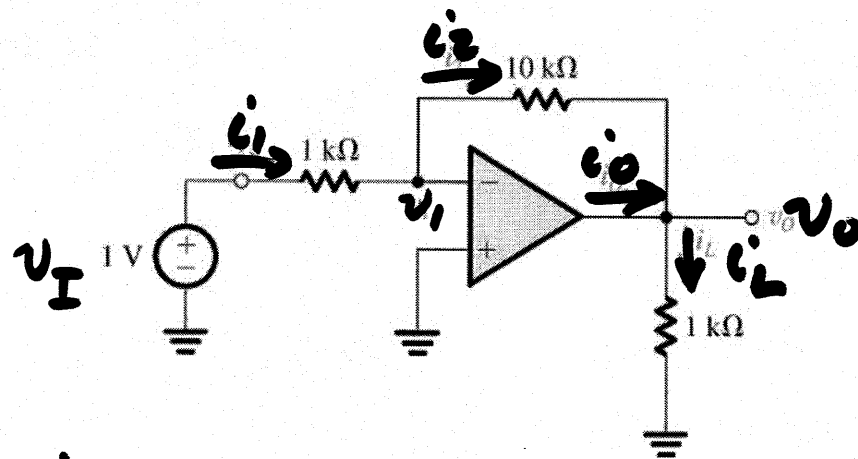$\therefore i_L = \frac{-10\text{V}}{1\text{k}} = -10\text{mA}$



$$i_o = i_L - i_2 = (-10\text{mA}) - (1\text{mA}) = -11\text{mA}$$

$$v_o/v_I = -10\text{V}/1\text{V} = -10 \longrightarrow 20\log 10 = 20\text{dB}$$

$$i_L/i_I = -10\text{mA}/1\text{mA} = -10 \longrightarrow 20\log 10 = 20\text{dB}$$

$$P_o/P_I = (-10 \times -10) = 100 \longrightarrow 10\log 100 = 20\text{dB}$$


Figure E2.6

Weighted Summing Circuit (D to A)

$$v^- = 0 \quad \therefore i_i = v_i / R_i \quad i = 1, \dots, n$$

$$\therefore i = \sum_n i_i = \sum_n v_i / R_i$$
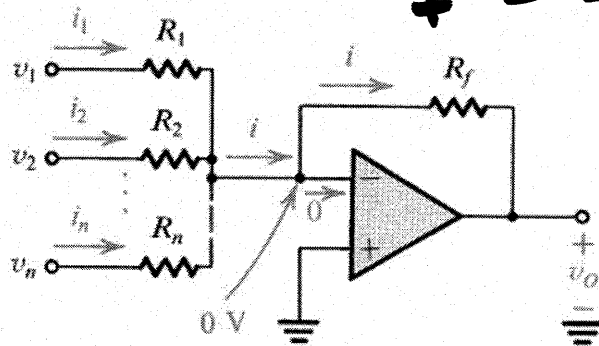
$$\& v_o = -i R_f = -R_f \sum_n v_i / R_i$$



$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$

Ex D2.7 $v_o = -(v_1 + 5v_2)$. Find R_1, R_2, R_f so $i \leq 1\text{mA}$ for $v_o \leq 10\text{V}$.

Say $v_o = 10\text{V}$ (max), then i (max) $= 1\text{mA} \Rightarrow R_f = 10\text{K}$
 $\therefore R_1 = 10\text{K}, R_2 = 2\text{K}$

Figure 2.10 A weighted summer.

But: DESIGN requirement $i \leq 1\text{mA} \rightarrow R_1 = R_f \geq 10\text{K}, R_2 = R_1/5$
 Also, preferred values $\rightarrow R_1 = R_f = 47\text{K}, R_2 = 10\text{K}$?
 Appendix G, 5% range $\rightarrow 11\text{K}, 2.2\text{K}$ or $12\text{K}, 2.4\text{K}$ or $15\text{K}, 3\text{K}$ or $18\text{K}, 3.6\text{K}$

If coefficients have different signs
→ cascade 2 inverting amps
for the positive coeffs.

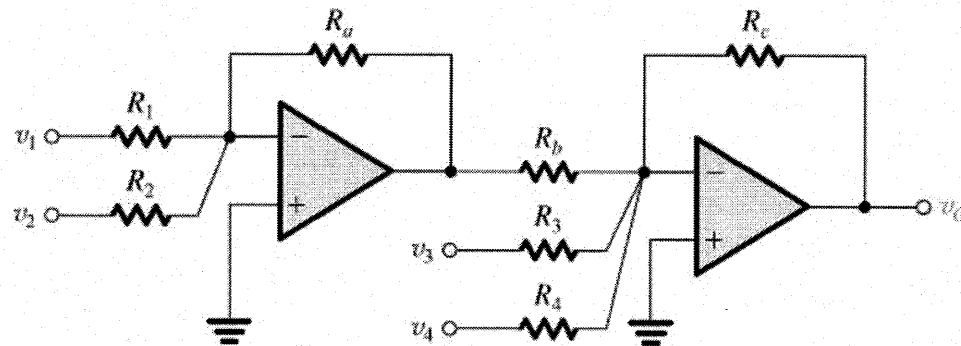


Figure 2.11 A weighted summer capable of implementing summing coefficients of both signs.

Non-Inverting Amplifier

$$v^- = v^+ = v_I$$

etc

Same approach

$$R_{in} = \infty$$
$$\therefore i_{m1} = i_{m2} = 0$$

etc

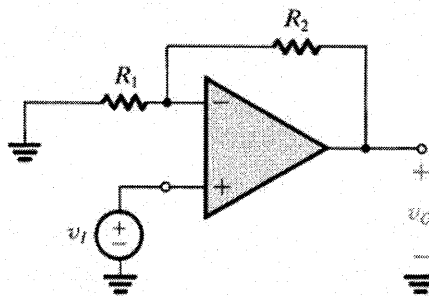



Figure 2.12 The noninverting configuration.

$$\textcircled{1} \quad v^- = v^+ \text{ for neg fb \& } A \rightarrow \infty$$

$$\textcircled{2} \quad \therefore v^- = v_I$$

$$\textcircled{3} \quad \therefore i_1 = v_I / R_1$$
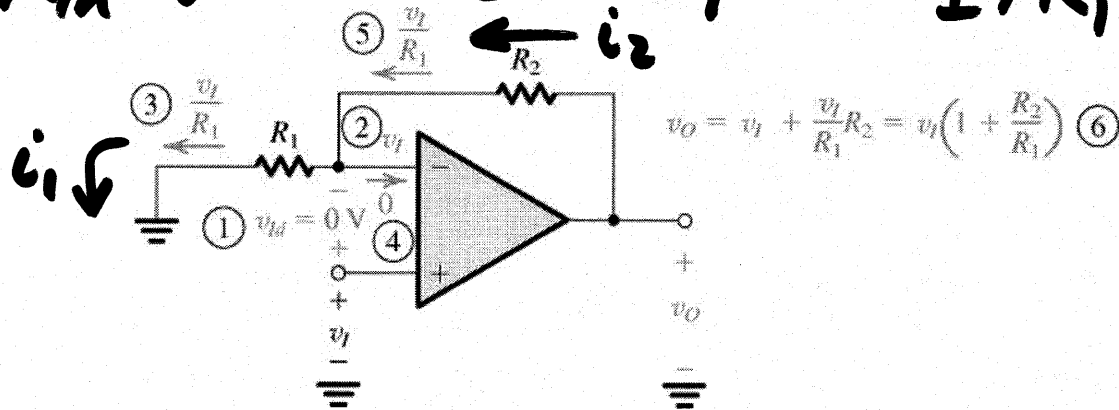
$$\textcircled{4} \quad R_{in} = \infty \quad \therefore i_2 = i_1 = v_I / R_1 \quad \textcircled{5}$$



$$\textcircled{6} \quad \therefore v_O = v^- + i_2 R_2 = v_I + \frac{v_I}{R_1} R_2 = v_I \left(1 + \frac{R_2}{R_1}\right)$$


Figure 2.13 Analysis of the noninverting circuit. The sequence of the steps in the analysis is indicated by the circled numbers.

$$\therefore A_{CL} = v_O / v_I = 1 + R_2 / R_1$$

VOLTAGE FOLLOWER


$$v_o = v^- = v^+ = v_i$$
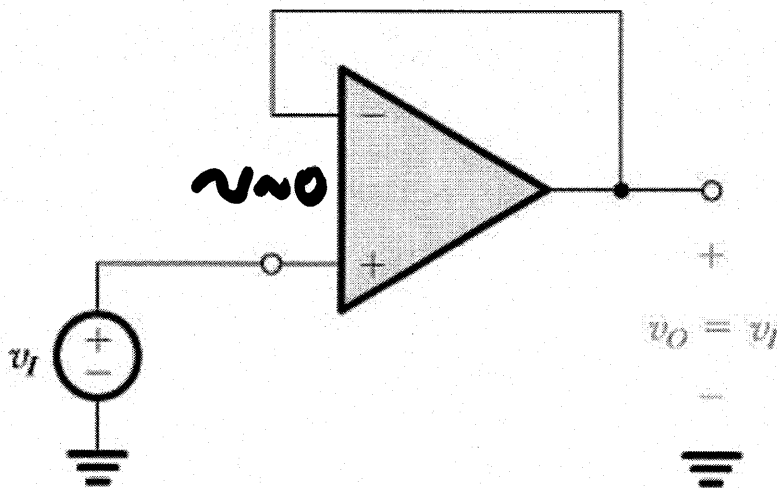
$$\therefore A_v = \frac{v_o}{v_i} = +1$$



(a)

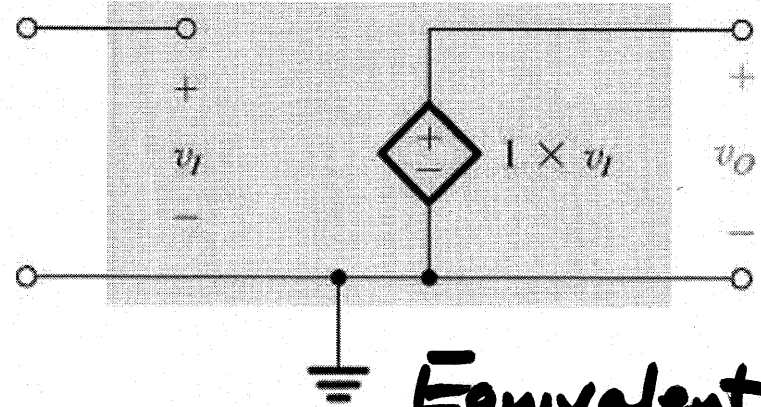So what's the point of $A=1$?
 Buffer $\rightarrow R_{in} = \infty$
 $R_{out} = 0$





(b) Equivalent circuit

$R_{in} = \infty$
 $R_{out} = 0$

Figure 2.14 (a) The unity-gain buffer or follower amplifier. (b) Its equivalent circuit model.

Ex 2.9 Superposition

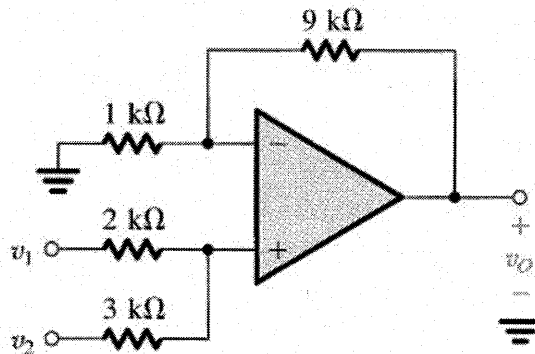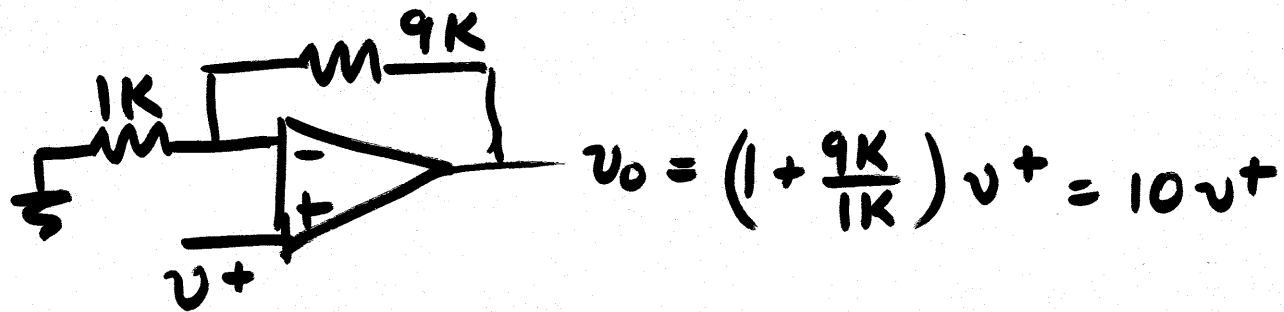

Find v^+



$$v_1 \text{ --- } \frac{2k}{2k} \text{ --- } v_1^+ = \frac{3}{5} v_1 \quad v_2 \text{ --- } \frac{3k}{3k} \text{ --- } v_2^+ = \frac{2}{5} v_2$$

$$\therefore v_o = 10 \left(\frac{3}{5} v_1 + \frac{2}{5} v_2 \right) = 6v_1 + 4v_2$$

Figure E2.9

Ex 2.14 Transducer $V_{oc} = 1\text{V}$, $R_{source} = 1\text{M}\Omega$

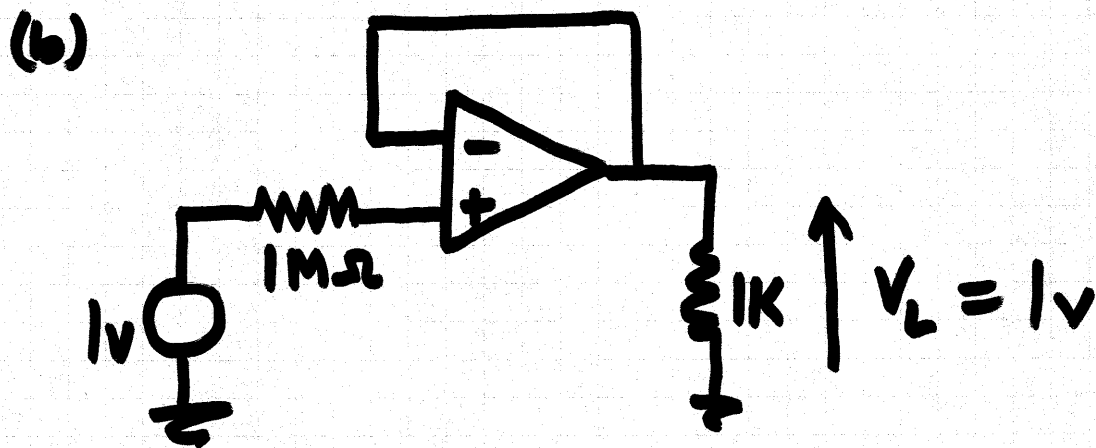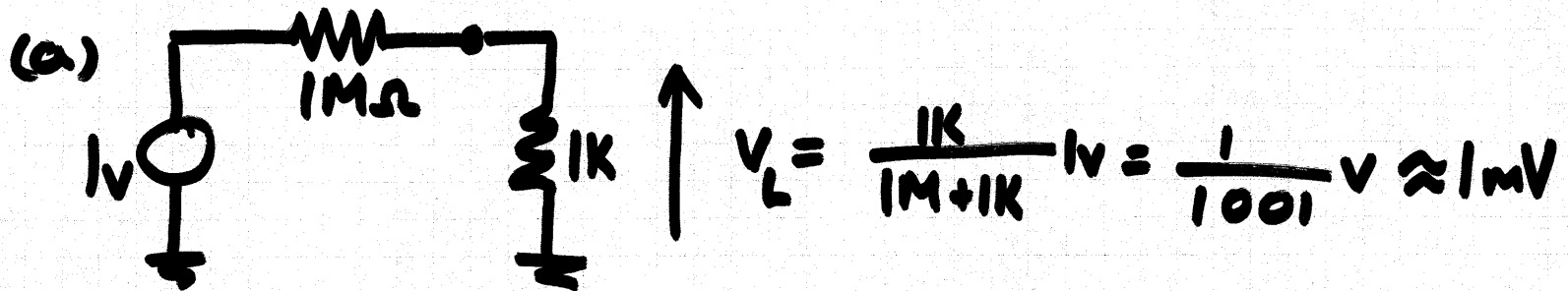Connect to $1\text{k}\Omega$ load (a) directly, & (b) with voltage follower



Inverting Amplifier: Op Amp Gain = A

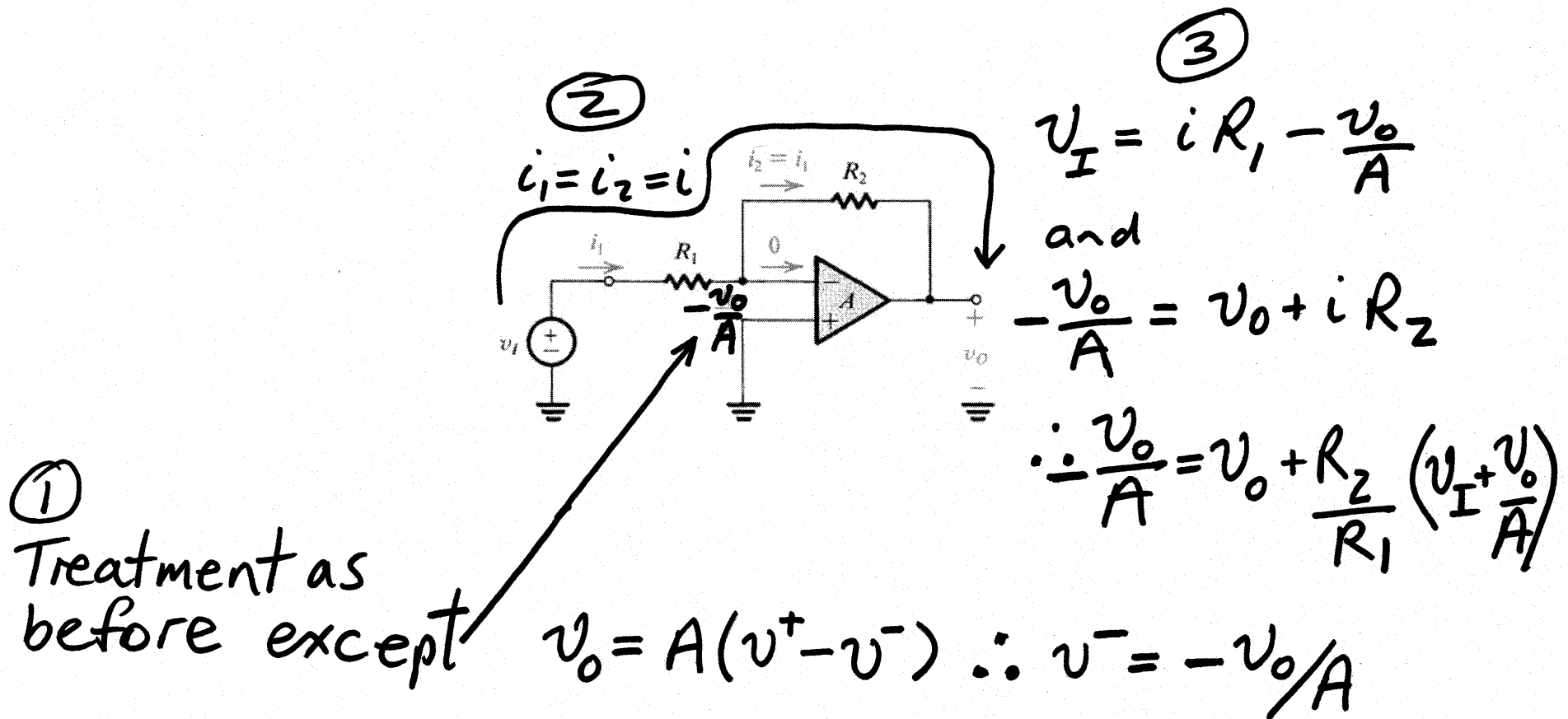


Figure 2.7 Analysis of the inverting configuration taking into account the finite open-loop gain of the op amp.

④ Rearrange $\frac{v_o}{v_I} = \frac{-R_2}{R_1} \left/ \left(1 + \frac{R_2}{AR_1} + \frac{1}{A} \right) \right.$

Continue: Inverting Amplifier ✓ Text's result Eqⁿ 2.5

$$\frac{v_o}{v_i} = \frac{-R_2/R_1}{1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1}\right)} \xrightarrow{A \rightarrow \infty} -\frac{R_2}{R_1}$$

check!

Let's rearrange a bit more


$$\Rightarrow \frac{-(R_2/R_1)A}{A + (R_1 + R_2)/R_1}$$

$$= \frac{-A}{1 + A \cdot \frac{R_1}{R_1 + R_2}} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{R_2}{R_1 + R_2} \cdot \frac{A}{1 + A\beta} \quad \text{where } \beta = \frac{R_1}{R_1 + R_2}$$

See significance later

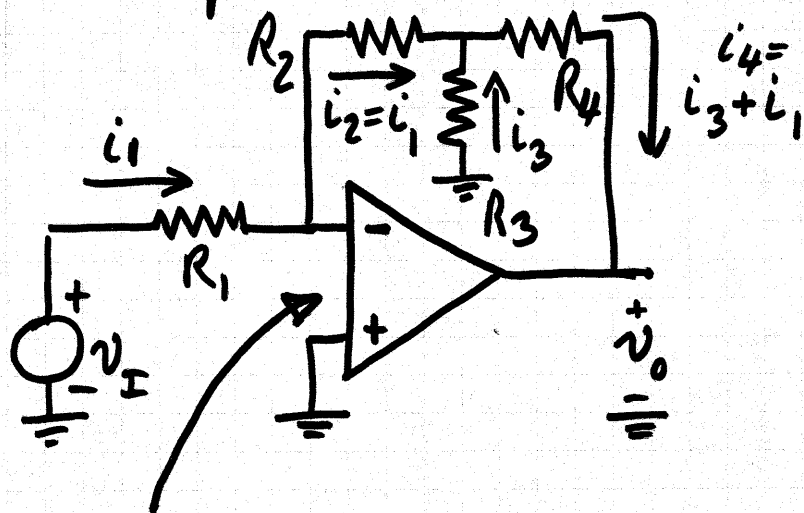Example 2.2. was covered earlier (Fig 2.2) with ideal op-amp



⑥ Rearrange \rightarrow

$$\frac{v_o}{v_I} = \frac{-(R_2/R_1 + R_4/R_1 + R_2 R_4 / R_1 R_3)}{1 + \left(1 + \frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} + \frac{R_4}{R_3}\right) / A}$$

$$\xrightarrow{A \rightarrow \infty} -(R_2/R_1 + R_4/R_1 + R_2 R_4 / R_1 R_3)$$

check

① Now $v^- = -v_o/A$

② $\therefore i_1 = \frac{v_I + v_o/A}{R_1} = i_2$

③ $\therefore v_x = -\frac{v_o}{A} - R_2 \left(\frac{v_I + v_o/A}{R_1} \right)$

④ $i_3 = -\frac{v_x}{R_3} = \left[\frac{v_o}{A} + \frac{R_2}{R_1} \left(v_I + \frac{v_o}{A} \right) \right] / R_3$


⑤ $\therefore v_o = v_x - (i_2 + i_3) R_4 = -\frac{v_o}{A} - \frac{R_2}{R_1} \left(v_I + \frac{v_o}{A} \right) - \frac{R_4}{R_1} \left(v_I + \frac{v_o}{A} \right) - \frac{R_4}{R_3} \left[\frac{v_o}{A} + \frac{R_2}{R_1} \left(v_I + \frac{v_o}{A} \right) \right]$

Non-Inverting Amplifier (Ex 2.12)

Again $v^+ - v^- = v_o/A \quad \therefore v^- = v_I - v_o/A$

Use voltage divider since current i continuous as shown
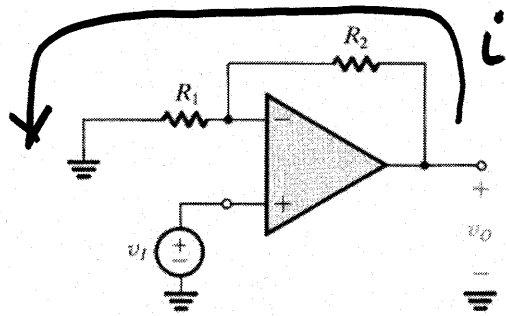
$$\therefore v^- = \frac{R_1}{R_1 + R_2} v_o \quad \left(\text{i.e. Negative feedback factor } \beta = \frac{R_1}{R_1 + R_2} \right)$$





$$\therefore v_I - \frac{v_o}{A} = \frac{R_1}{R_1 + R_2} v_o \implies v_o = v_I / \left(\frac{1}{A} + \frac{R_1}{R_1 + R_2} \right)$$

$$\text{i.e. } \frac{v_o}{v_I} = \frac{A}{1 + A\beta}$$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2}$$

Figure 2.12 The noninverting configuration.

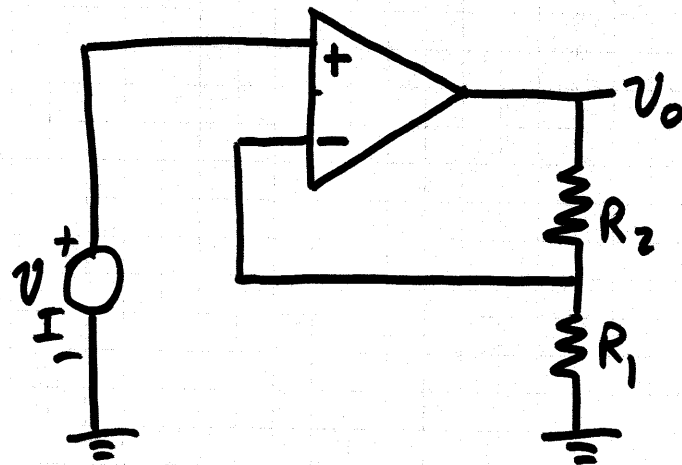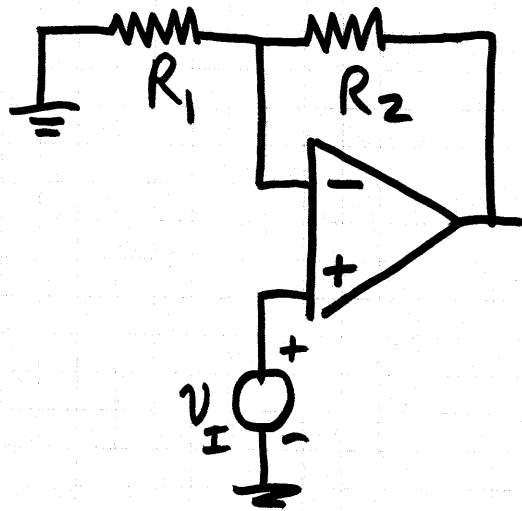
Different way of looking at the Non-Inverting Amplifier




$$v^- = \beta v_o = \frac{R_1}{R_1 + R_2} v_o$$

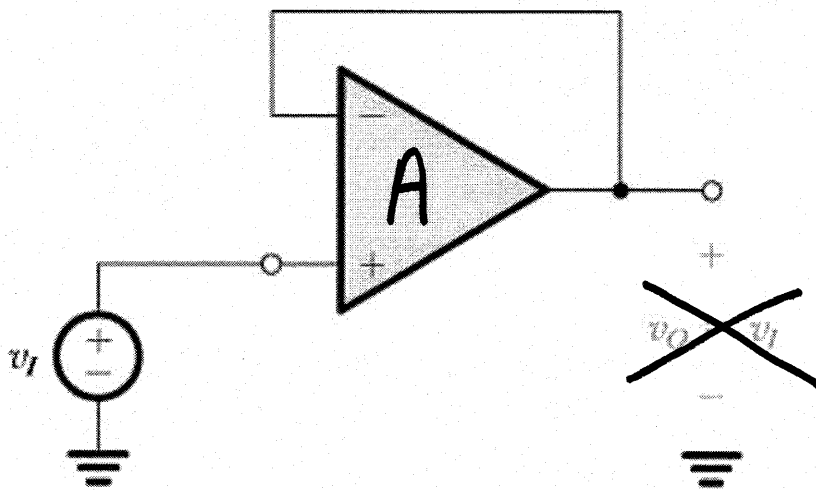Problem 2.54

Voltage Follower with finite gain
 $A = 1000, 100, 10$



(a)

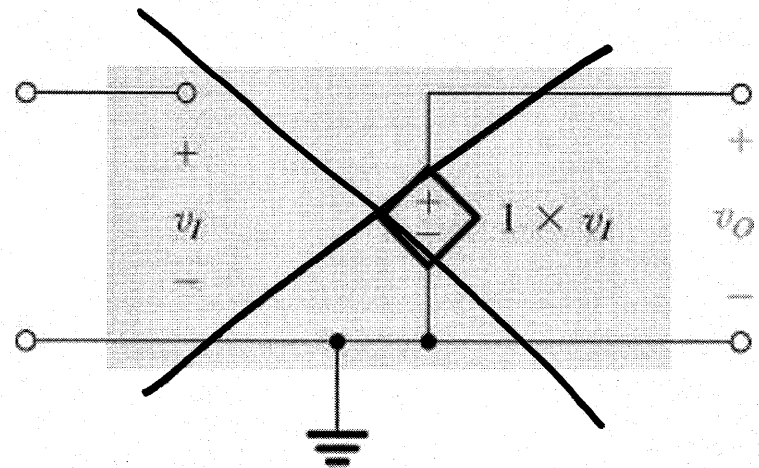

(b)

$$v_o = A(v^+ - v^-) = A(v_I - v_o) = \frac{A v_I}{1 + A} \xrightarrow{A \rightarrow \infty} v_I$$

For $A = 1000$	$v_o/v_I = 1000/1001 = 0.999$
$= 100$	$= 100/101 = 0.990$
$= 10$	$= 10/11 = 0.909$

Figure 2.14 (a) The unity-gain buffer or follower amplifier. (b) Its equivalent circuit model.

Assignment #1

Problems at
end of chapter

D* 1.44

1.58

1.63

2.8

D 2.33

D 2.46

D → "design" problem

* → harder than others

Selected answers in Appendix H (3 of this week's assignment)

Usually 5 problems/week