

ECE321 ELECTRONICS I
FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 6
12th October, 2006

CHAPTER 3

Diodes




3.4 Zener Diodes Reverse breakdown

3.5 Rectification Revisit & develop

3.6 Clipping & Clamping ← Capacitor effects

↑ Non-linear composites


Zener diode symbol

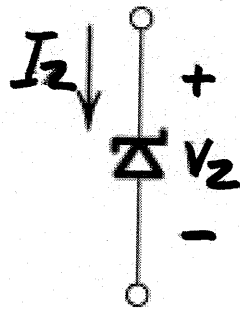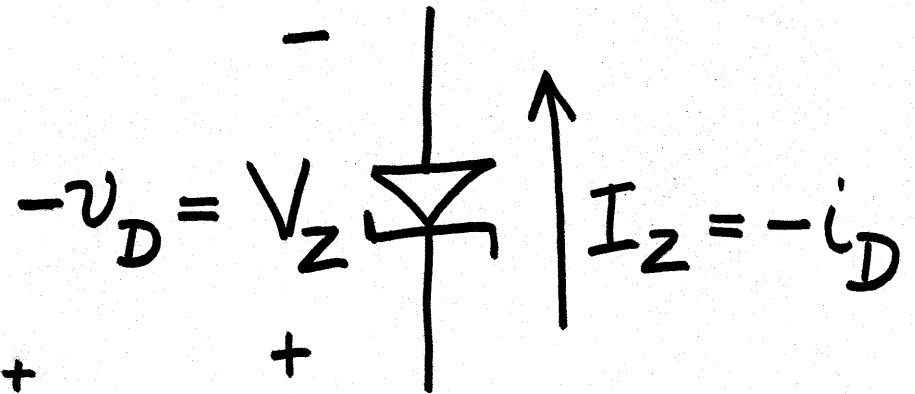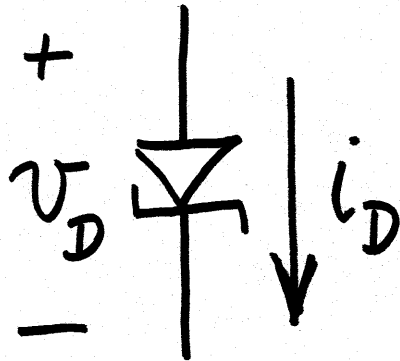

Breakdown diode
Avalanche diode
Reference diode

Figure 3.20 Circuit symbol for a zener diode.

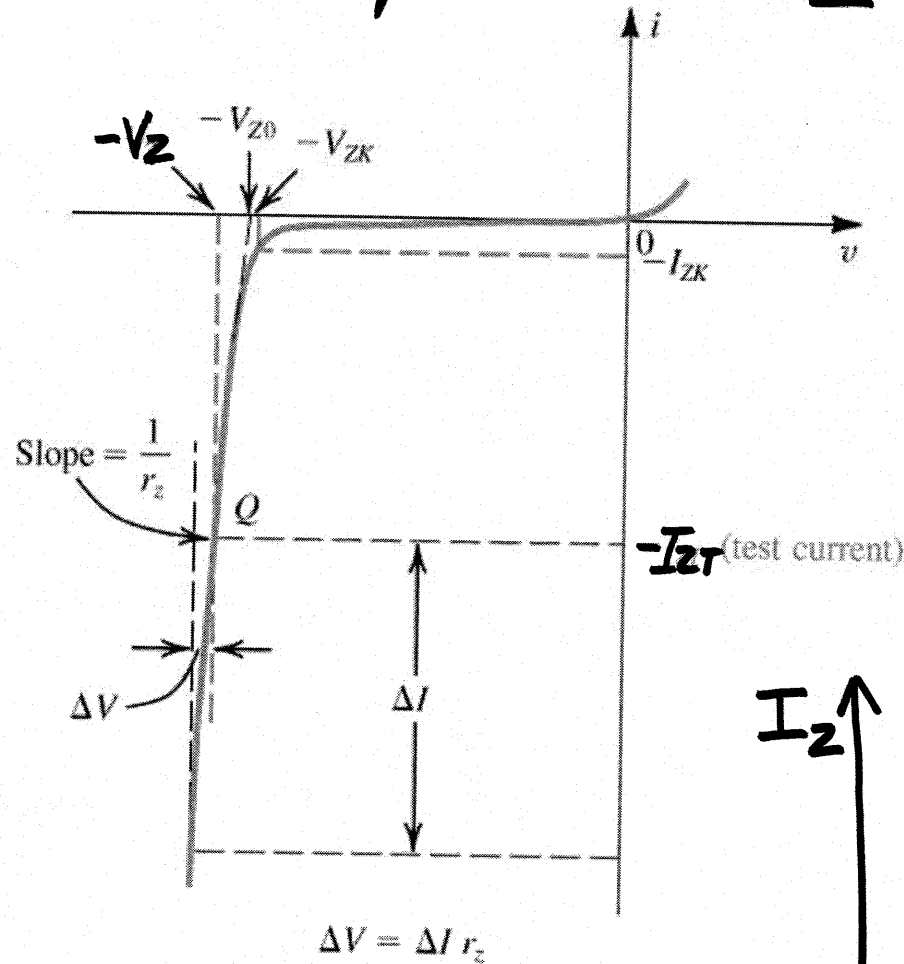Manufacturer specifies V_Z at test I_{ZT}



V_{ZK}, I_{ZK}
"Knee"
voltage/current

$$\Delta V = \Delta I \cdot r_z$$


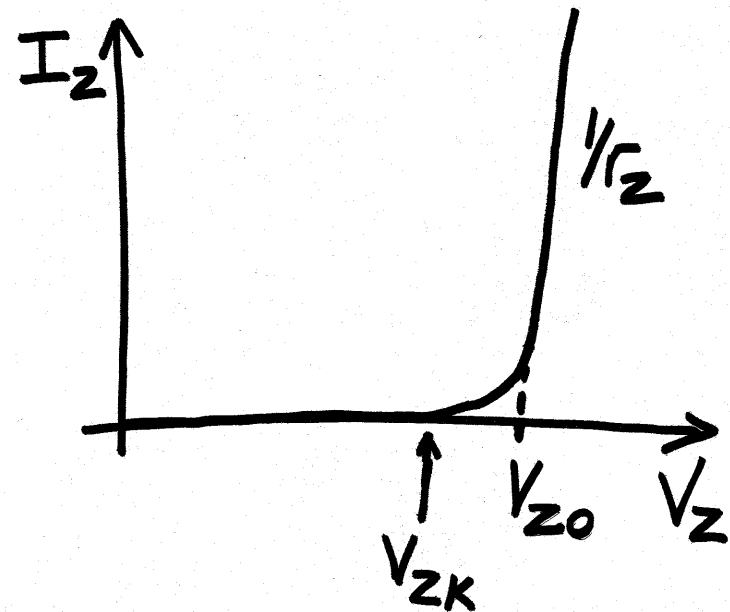


Figure 3.21 The diode $i-v$ characteristic with the breakdown region shown in some detail.

Linear Zener Model

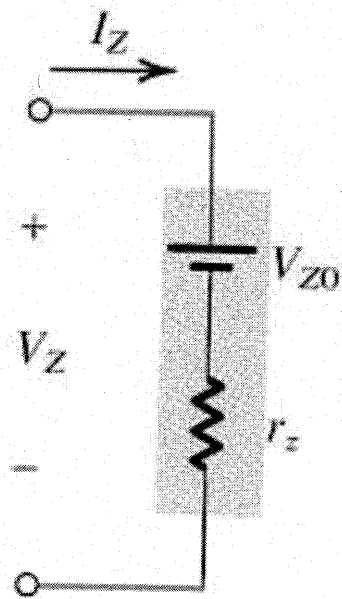

$$V_z = V_{z0} + I_z r_z$$

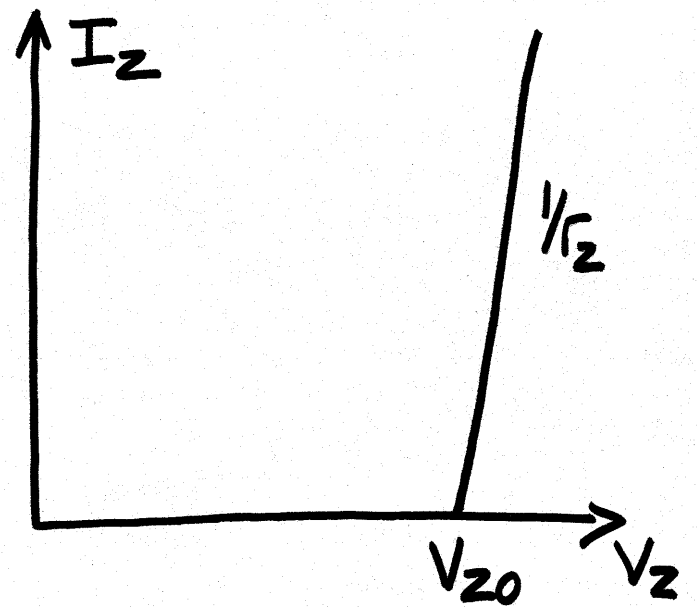


Figure 3.22 Model for the zener diode.

Example 3.8 Voltage regulation

Ex. 3.17

Ex. 3.18

Ex. 3.19

Thermal Effects

For $V_{z0} \lesssim 5\text{V}$ neg T.C. (Zener breakdown)

$V_{z0} \gtrsim 5\text{V}$ pos T.C. (Avalanche breakdown)

At $\sim 5\text{V}$, positive or negative temperature coefficient of V_{z0} can depend on bias point.

Use with series diode $V_{z0}' = V_{z0} + 0.7\text{V}$
(nominal)

Pos. TC ($\sim 2\text{mV}/^\circ\text{C}$)

Neg. TC $2\text{mV}/^\circ\text{C}$

Rectification

AC → DC
power conversion



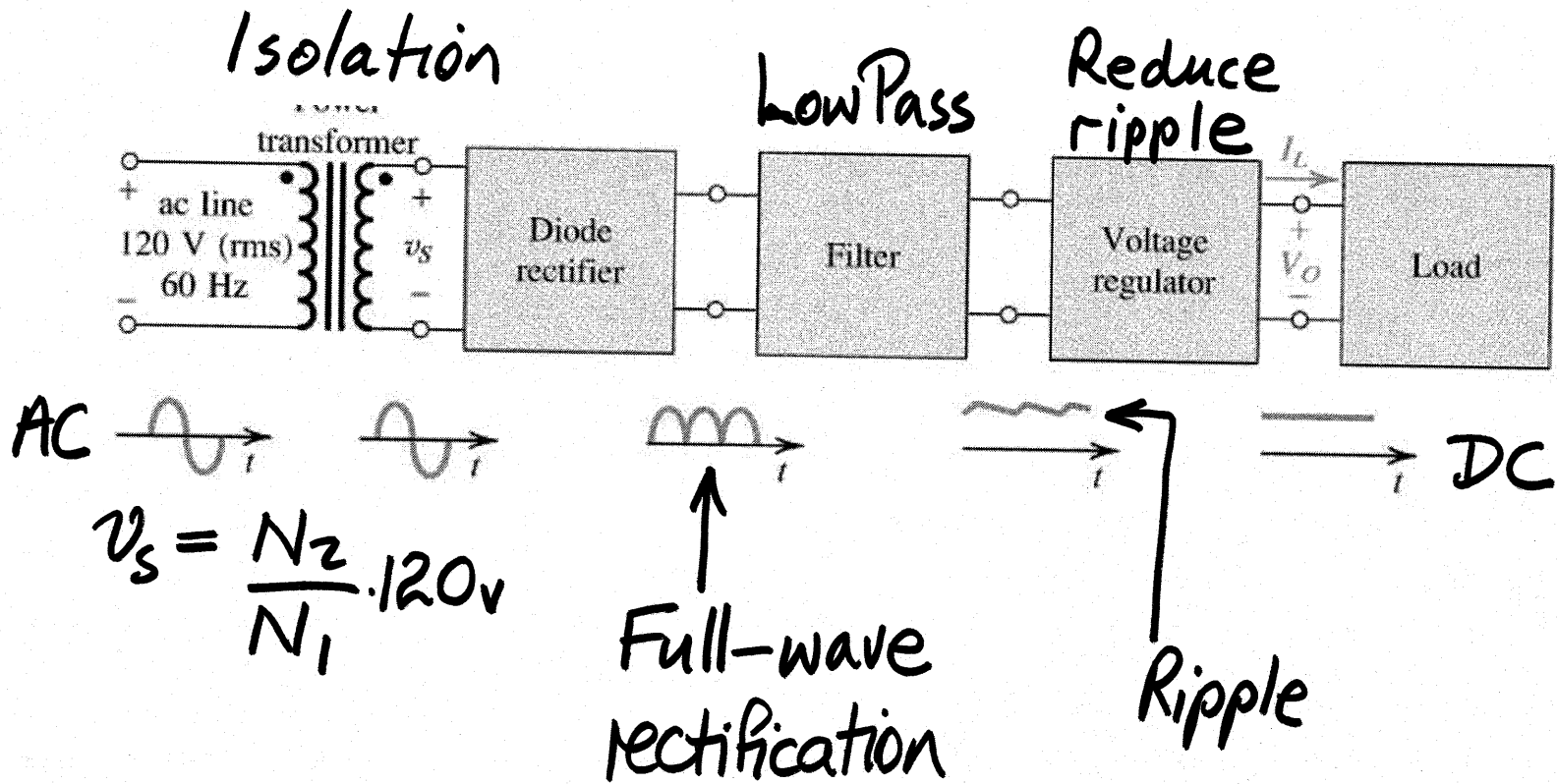


Figure 3.24 Block diagram of a dc power supply.

Half-Wave Rectifier

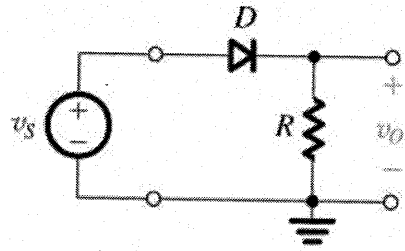


(a)

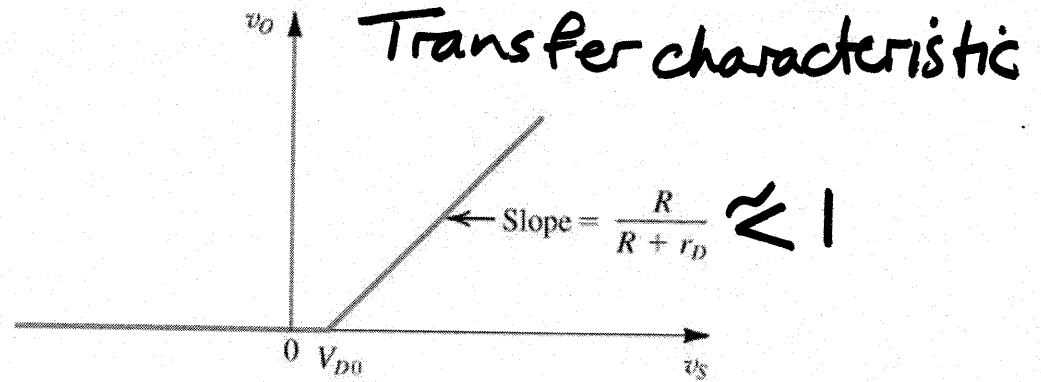


(c)

Equivalent circuit

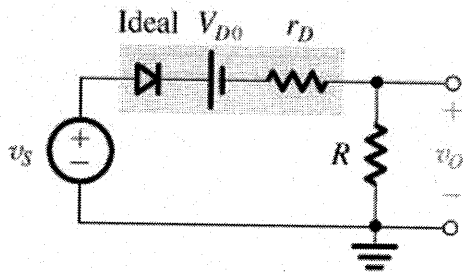

(b)

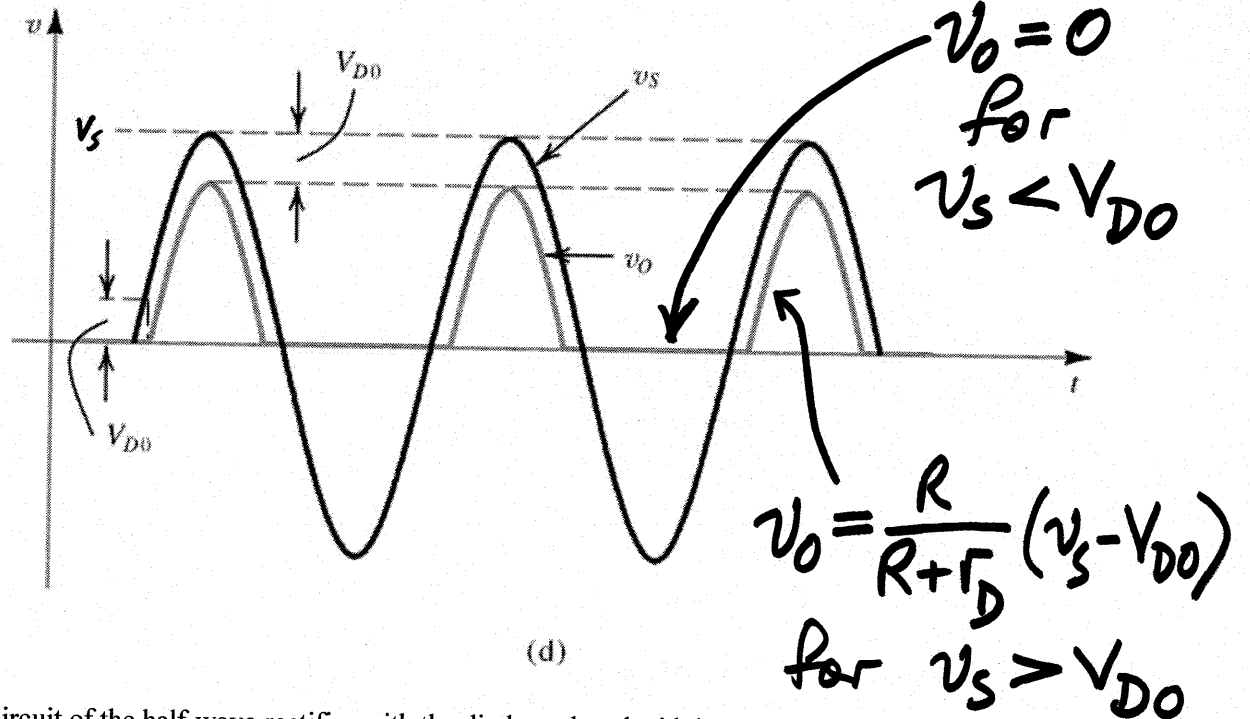

(d)

Figure 3.25 (a) Half-wave rectifier. (b) Equivalent circuit of the half-wave rectifier with the diode replaced with its battery-plus-resistance model. (c) Transfer characteristic of the rectifier circuit. (d) Input and output waveforms, assuming that $r_D \ll R$.


$r_D \ll R$

Notes:


- (1) Maximum diode current
- (2) Max PIV — peak inverse voltage across diode when reverse biased — here V_s

$\approx v_s - V_{D0}$


Full-wave Rectification

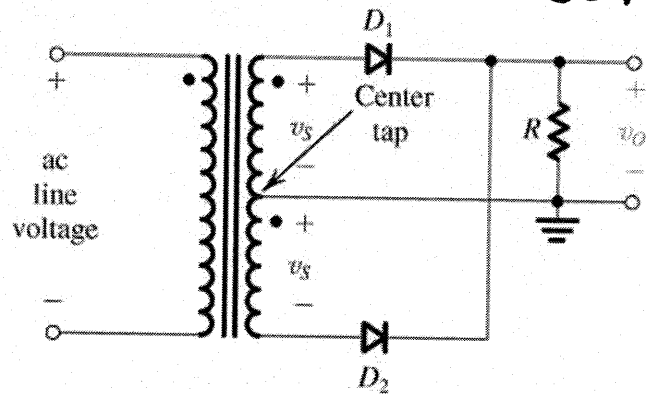

(a)

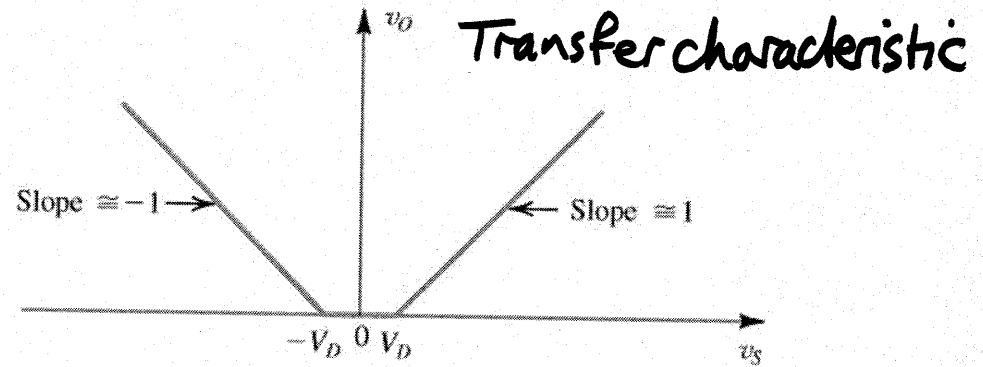

(b)

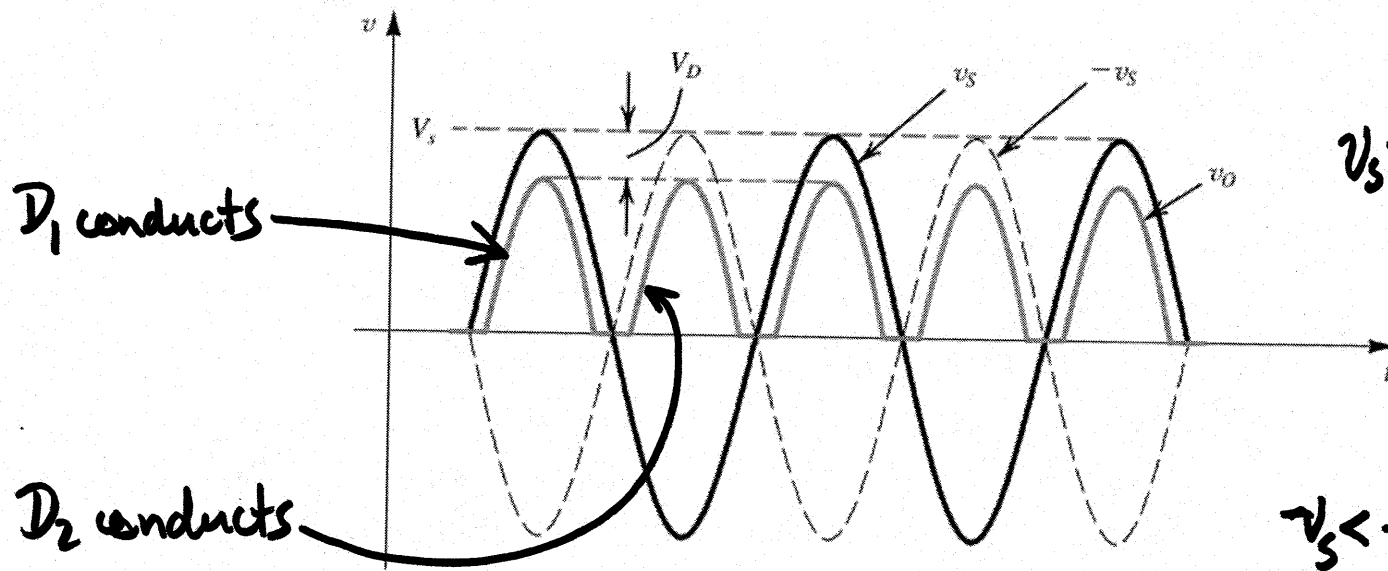

(c)


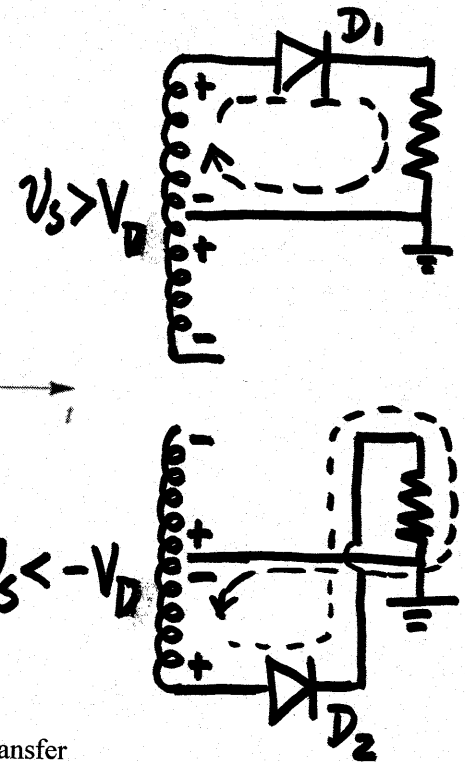


Figure 3.26 Full-wave rectifier utilizing a transformer with a center-tapped secondary winding: (a) circuit; (b) transfer characteristic assuming a constant-voltage-drop model for the diodes; (c) input and output waveforms.


PIV

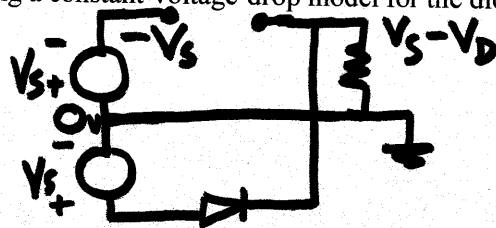


$$\begin{aligned} \text{PIV} &= (V_S - V_D) - (-V_S) \\ &= 2V_S - V_D \approx 2V_S \end{aligned}$$

Expensive:
2 windings,
CT transformer


Bridge Rectifier

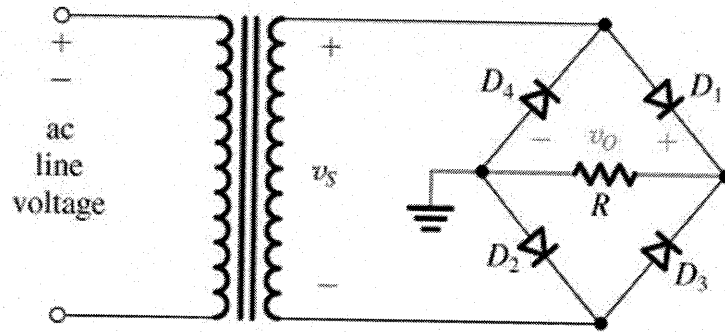

(a)

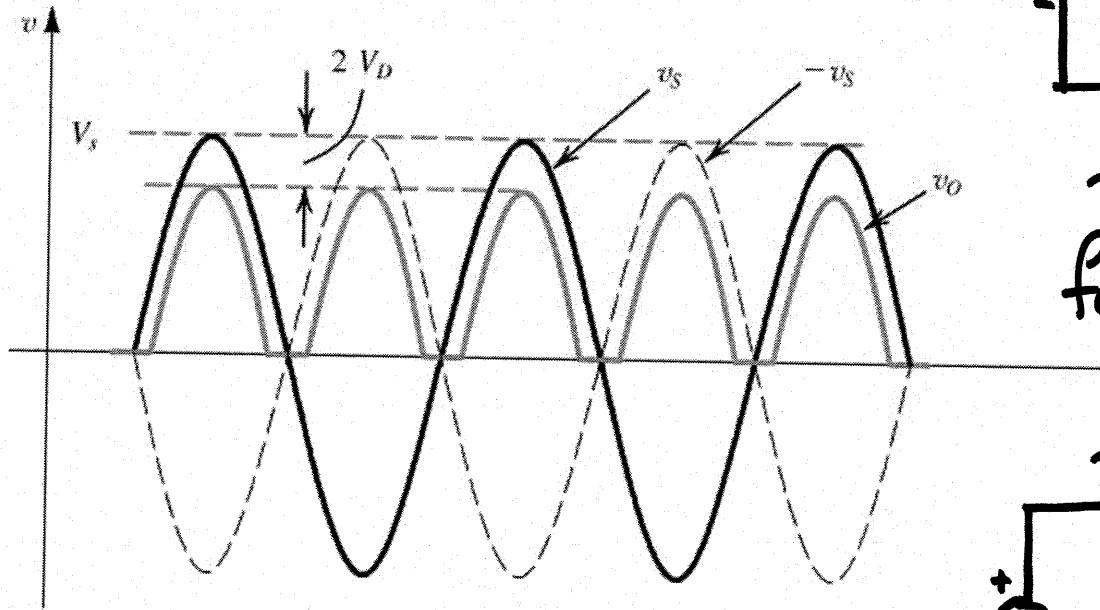


(b)

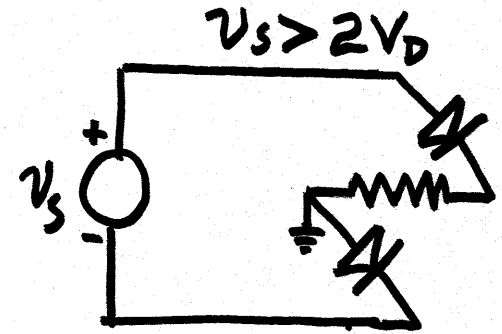


$$v_o = |v_s| - 2V_D$$

for $|v_s| > 2V_D$

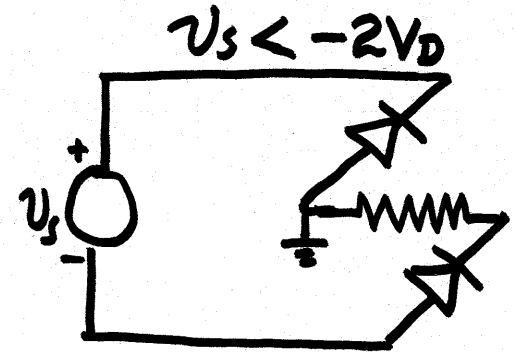


Extra diodes cheap.
Single package

Figure 3.27 The bridge rectifier: (a) circuit; (b) input and output waveforms.

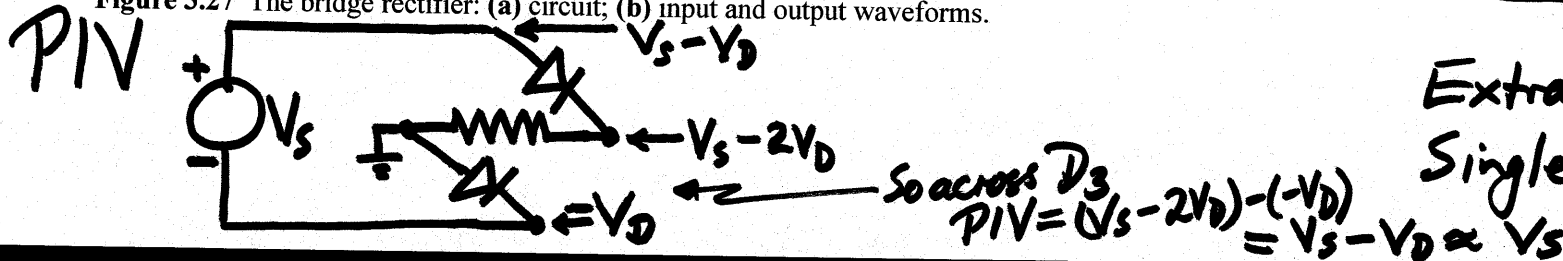

Peak Rectifier

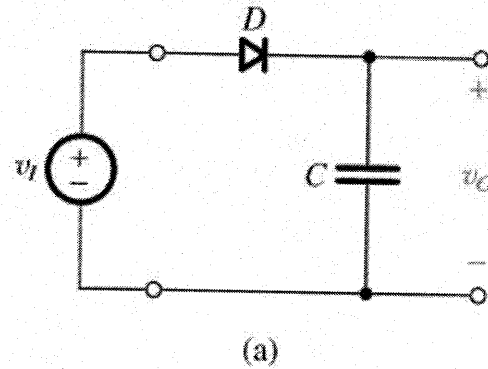

C charges to V_p
& then $v_s \leq v_o$
forever!



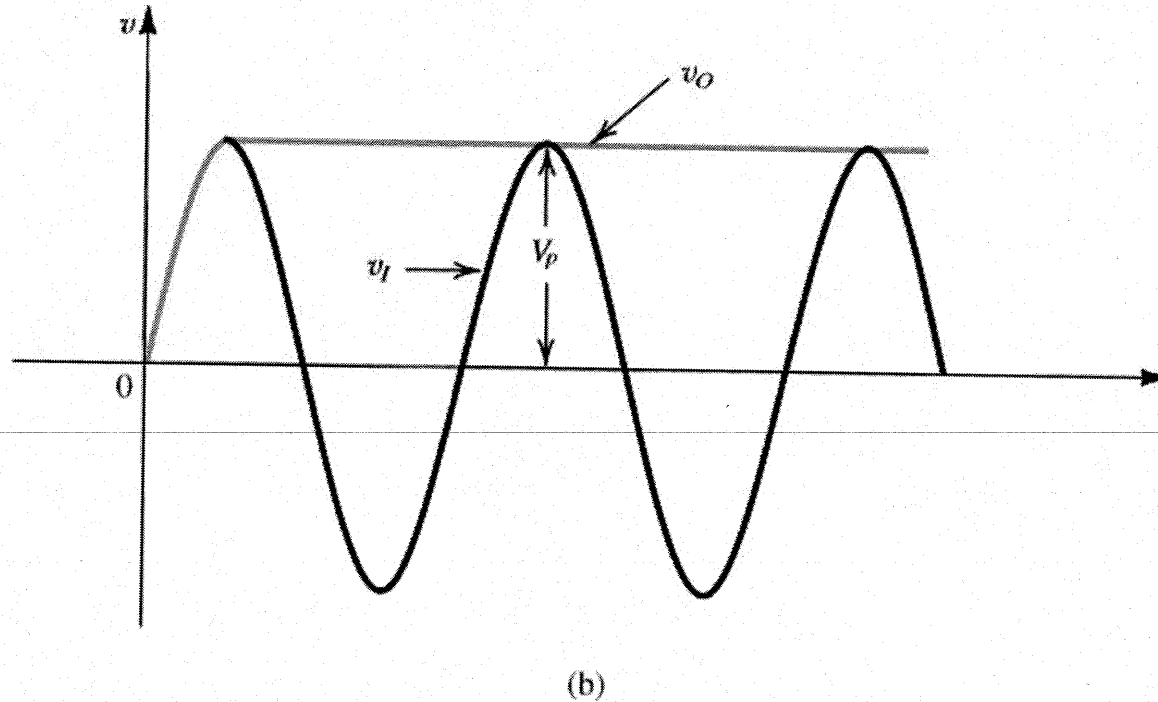
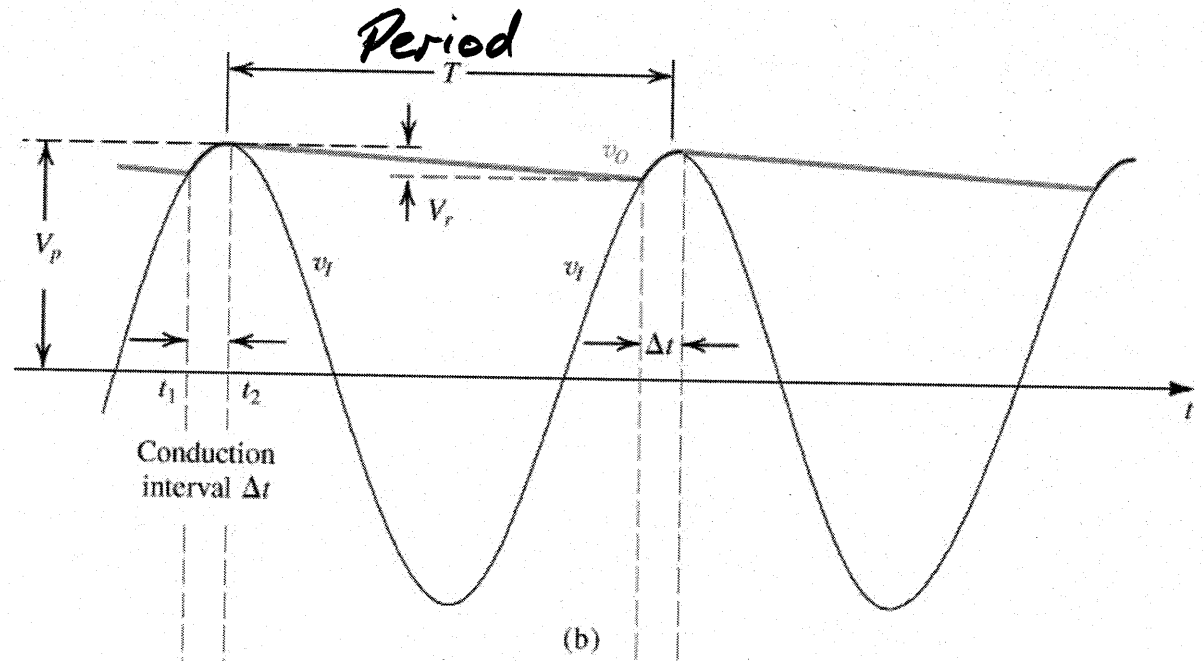


Figure 3.28 (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a peak rectifier or a peak detector.

Peak Rectifier with Load

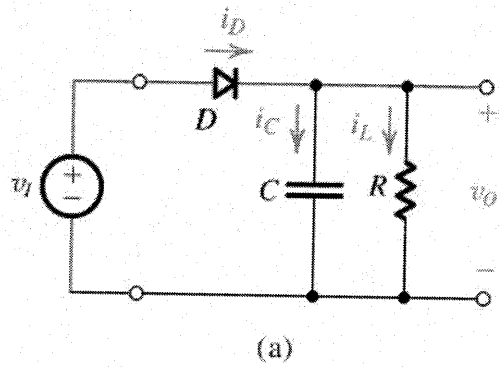

Charging current to capacitor

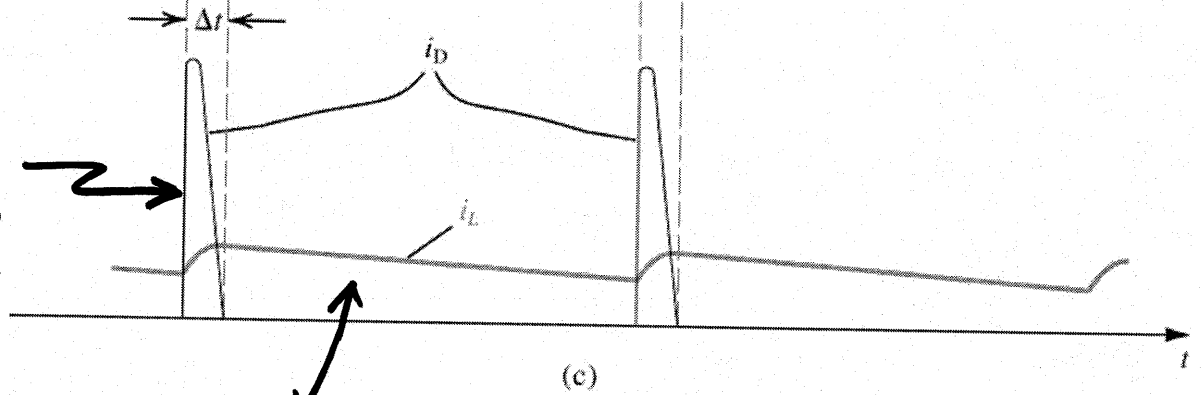


Load charge delivered

Figure 3.29 Voltage and current waveforms in the peak rectifier circuit with $CR \ll T$. The diode is assumed ideal.

Actually:


v_s decreasing

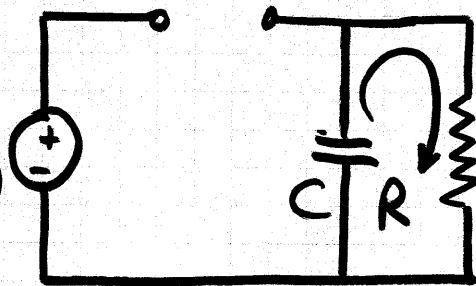

Assume 1/2 wave


$$v_o = V_p \exp^{-t/RC}$$

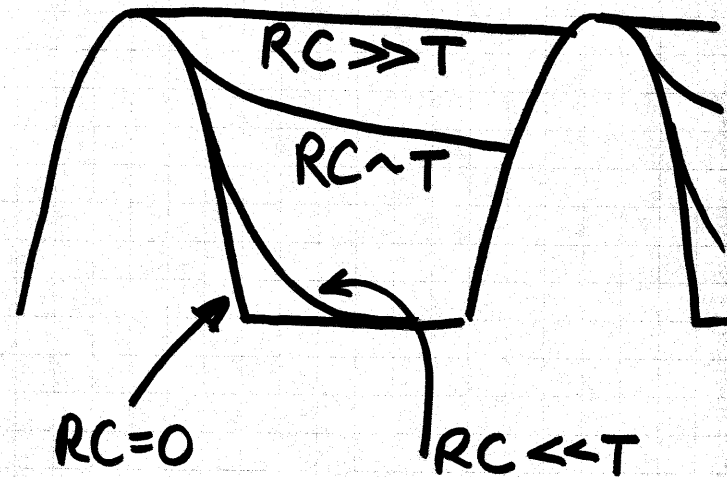Large load current $\rightarrow R_{\text{small}}$
 \therefore Large C needed



For $RC \gg T$, approx linear sag.

For small ripple:

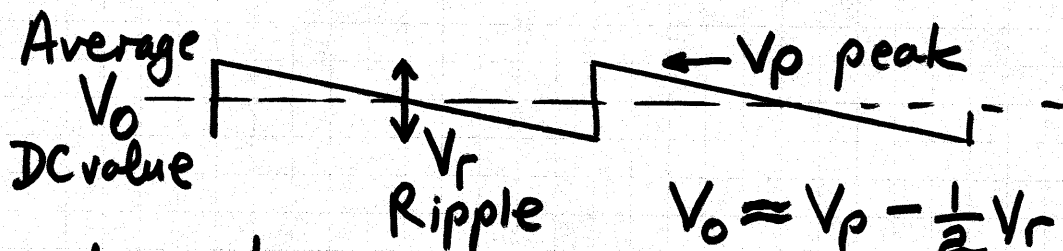

Discharge current = Load current
 (constant for linear approximation)


$$V_o \approx V_p - \frac{1}{2} V_r$$

assumes linear approxⁿ

$$i_c = C \frac{dv_c}{dt} = C \frac{V_r}{T} = \frac{V_o}{R} = \frac{V_p - 1/2 V_r}{R} \approx \frac{V_p}{R}$$

$$\therefore V_r = \frac{V_p}{RC/T + 1/2} \approx V_p T/RC$$

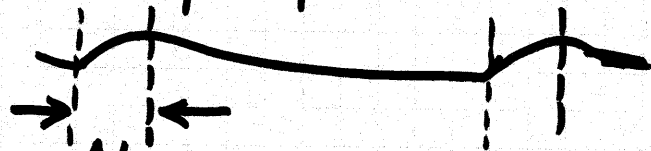Notes: This has approximated $v_o = V_p \exp -t/RC$



Assumes $\Delta t \approx 0$

i.e. at the end of the cycle

$$V_p - V_r \approx V_p \exp -T/RC$$

$$\text{gives } V_r \approx V_p (1 - T/RC)$$

$$V_r \approx V_p T/RC$$

For full wave or bridge $T \rightarrow T/2$

Conduction angle: time Δt $V_p \cos \omega \Delta t = V_p - V_r$

For $\omega \Delta t$ small $\cos \omega \Delta t \approx 1 - \frac{1}{2} (\omega \Delta t)^2$

$$\therefore 1 - V_r/V_p \approx 1 - \frac{1}{2} (\omega \Delta t)^2 \quad \therefore \omega \Delta t \approx \sqrt{2V_r/V_p}$$

Average diode current
during conduction
angle/pulse

Charge supplied to C = $i_C)_{AV} \cdot \Delta t$

Charge C supplies to R = $C V_r$


Also $i_C)_{AV} = i_D)_{AV} - i_L$

$$\therefore i_D)_{AV} = i_C)_{AV} + i_L = Q/\Delta t + i_L = \omega C V_r / \sqrt{2V_r/V_p} + i_L = i_L \left(1 + 2\pi \sqrt{\frac{V_p}{2V_r}} \right)$$

$$\omega C V_r = 2\pi C V_r / T = 2\pi C V_p T / RCT = 2\pi V_p / R \approx 2\pi i_L$$

$$= i_L \left(1 + \pi \sqrt{V_p/V_r} \right)$$

Full Wave Peak Rectifier (or Bridge)

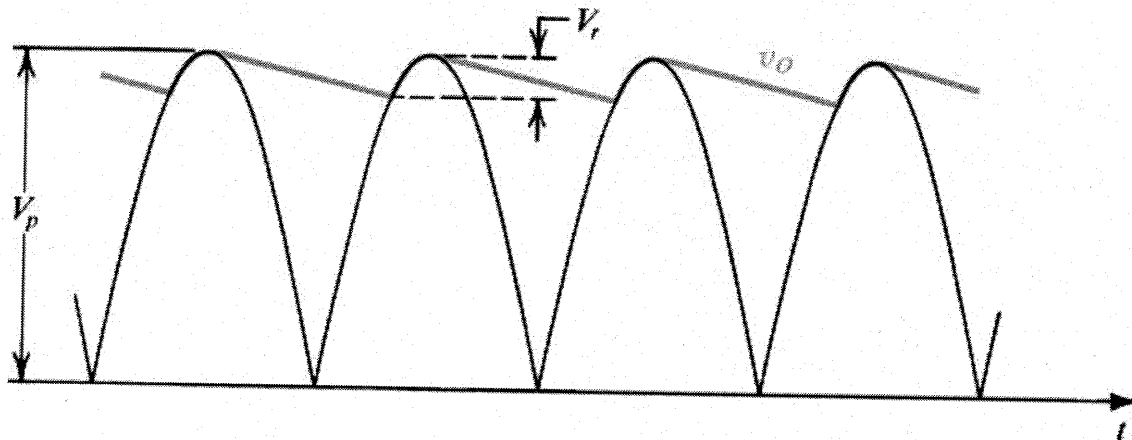

Full wave: Replace T above with $T/2$

$$\therefore V_r = \frac{V_p T}{RC} \implies \frac{V_p (T/2)}{RC} = \frac{V_p}{2fRC}$$

Conduction angle same (as function of V_r)


But charge delivered twice as often \therefore current pulse halved.

Figure 3.30 Waveforms in the full-wave peak rectifier.

$$\therefore (i_D)_{AV} = I_L (1 + \pi \sqrt{V_p / 2V_r})$$

&


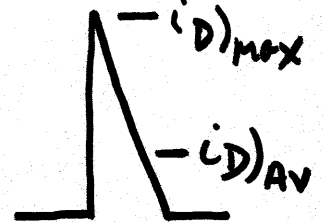
$$(i_D)_{max} = I_L (1 + 2\pi \sqrt{V_p / 2V_r})$$



Problem D3.24

Bridge rectification
with C smoothing filter

"Superdiode" or Precision Rectifier

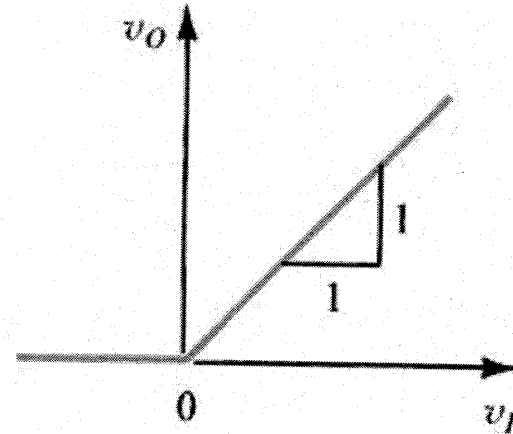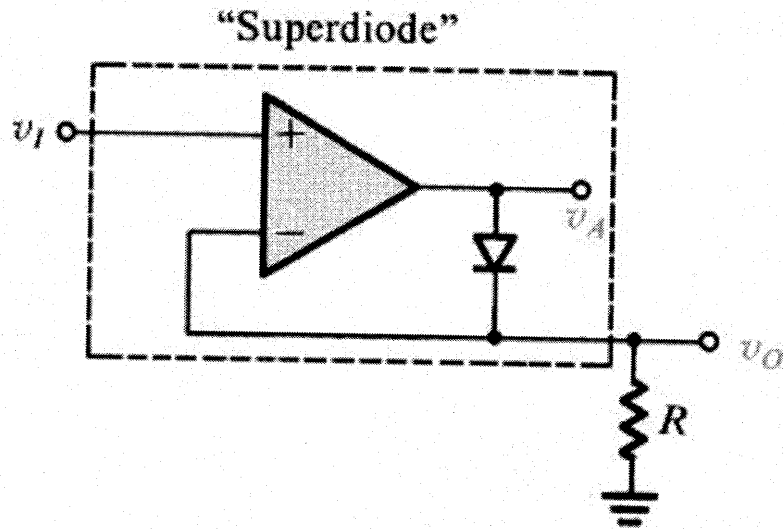


(a)
 $v_i > 0 \quad v_o \rightarrow \text{positive}$
 $\therefore D \text{ on} \quad \therefore \text{negative feedback}$
 $\therefore v_o \approx v_i$

(b)
 $v_i < 0$
 $v_o \rightarrow \text{negative}$
 $\therefore D \text{ off}$
 $\therefore v_o = 0$

Figure 3.31 The "superdiode" precision half-wave rectifier and its almost-ideal transfer characteristic. Note that when $v_i > 0$ and the diode conducts, the op amp supplies the load current, and the source is conveniently buffered, an added advantage. Not shown are the op-amp power supplies.

If op amp gain A finite
 Turn-on voltage = V_{ON}/A

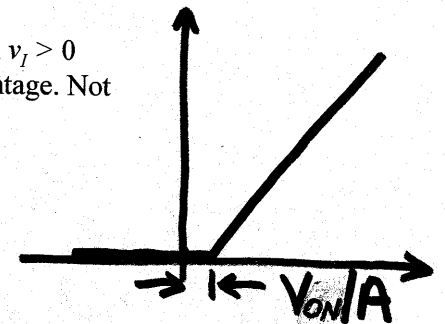


Ex 3.26

Superdiode

Limiting/Clipping Circuits

Transfer characteristic

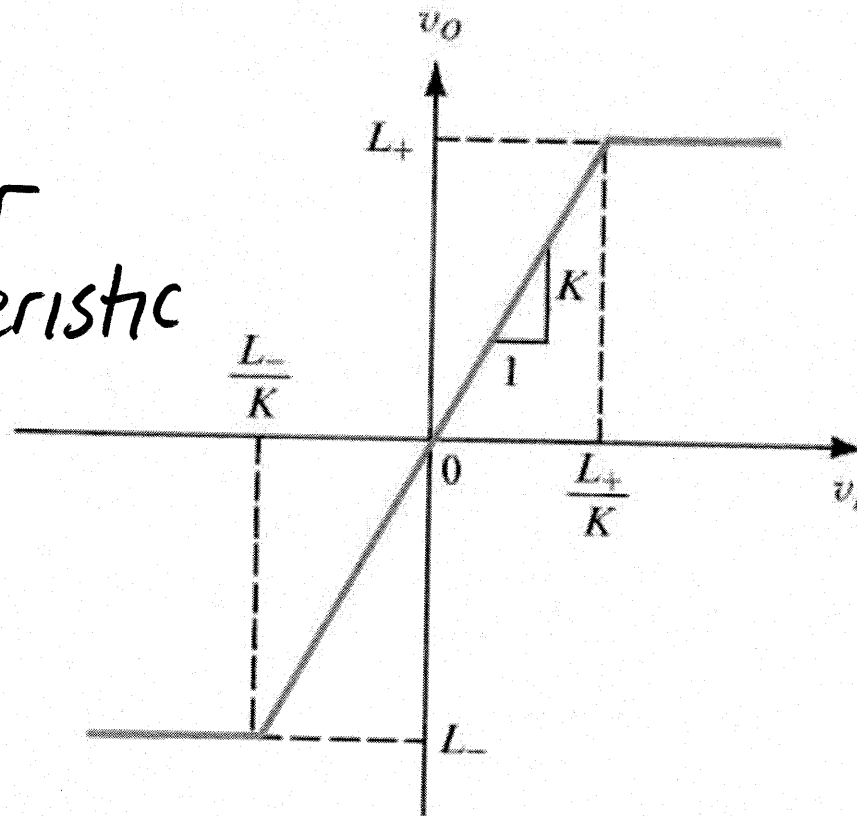

Note: Similar to saturated output op-amp circuits

Figure 3.32 General transfer characteristic for a limiter circuit.

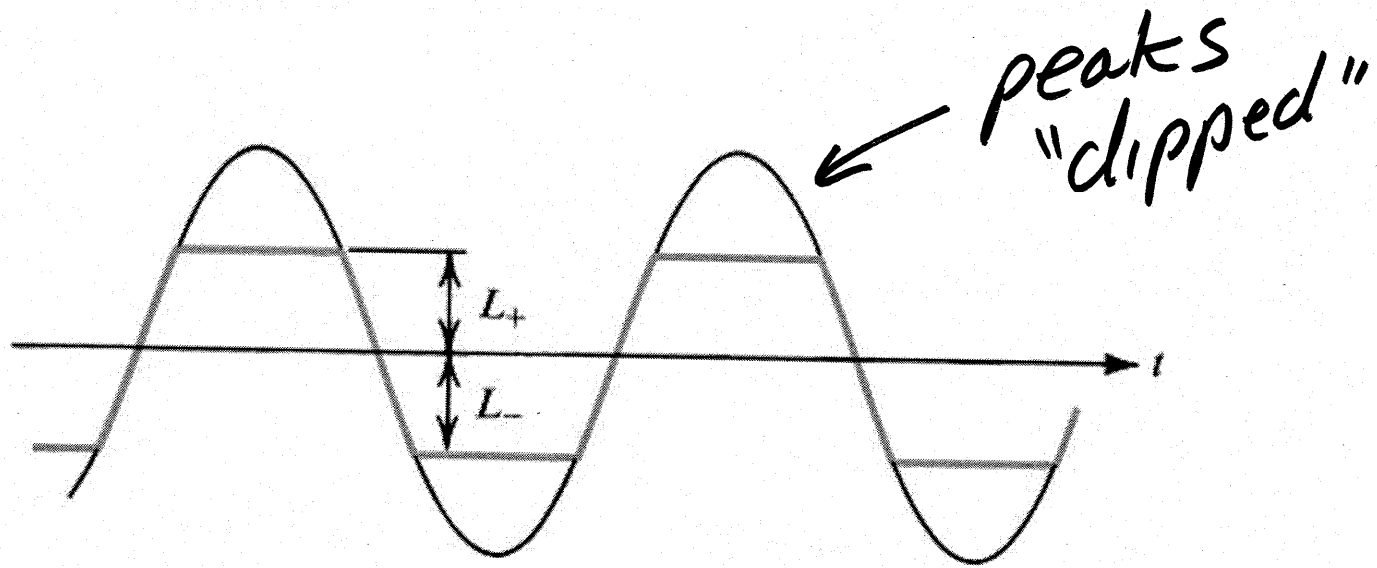


Figure 3.33 Applying a sine wave to a limiter can result in clipping off its two peaks.

"Soft" limiting


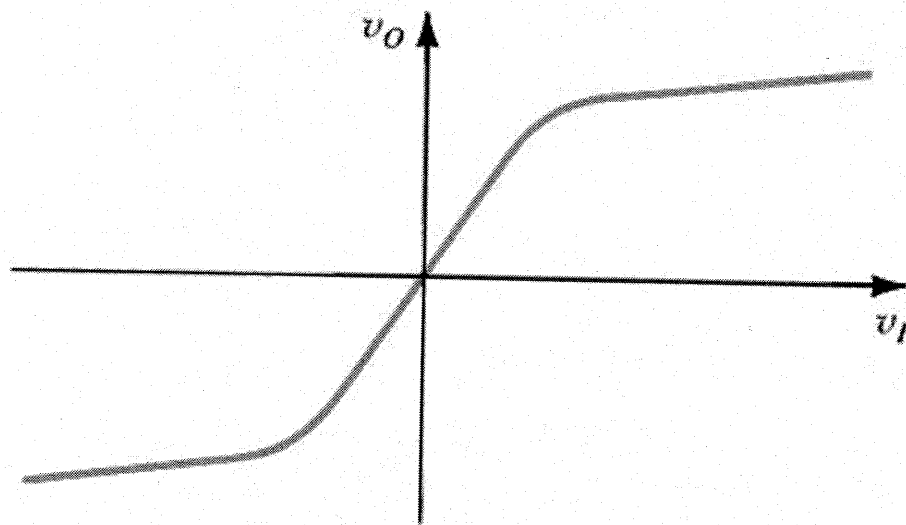


Figure 3.34 Soft limiting.

Diode Limiters

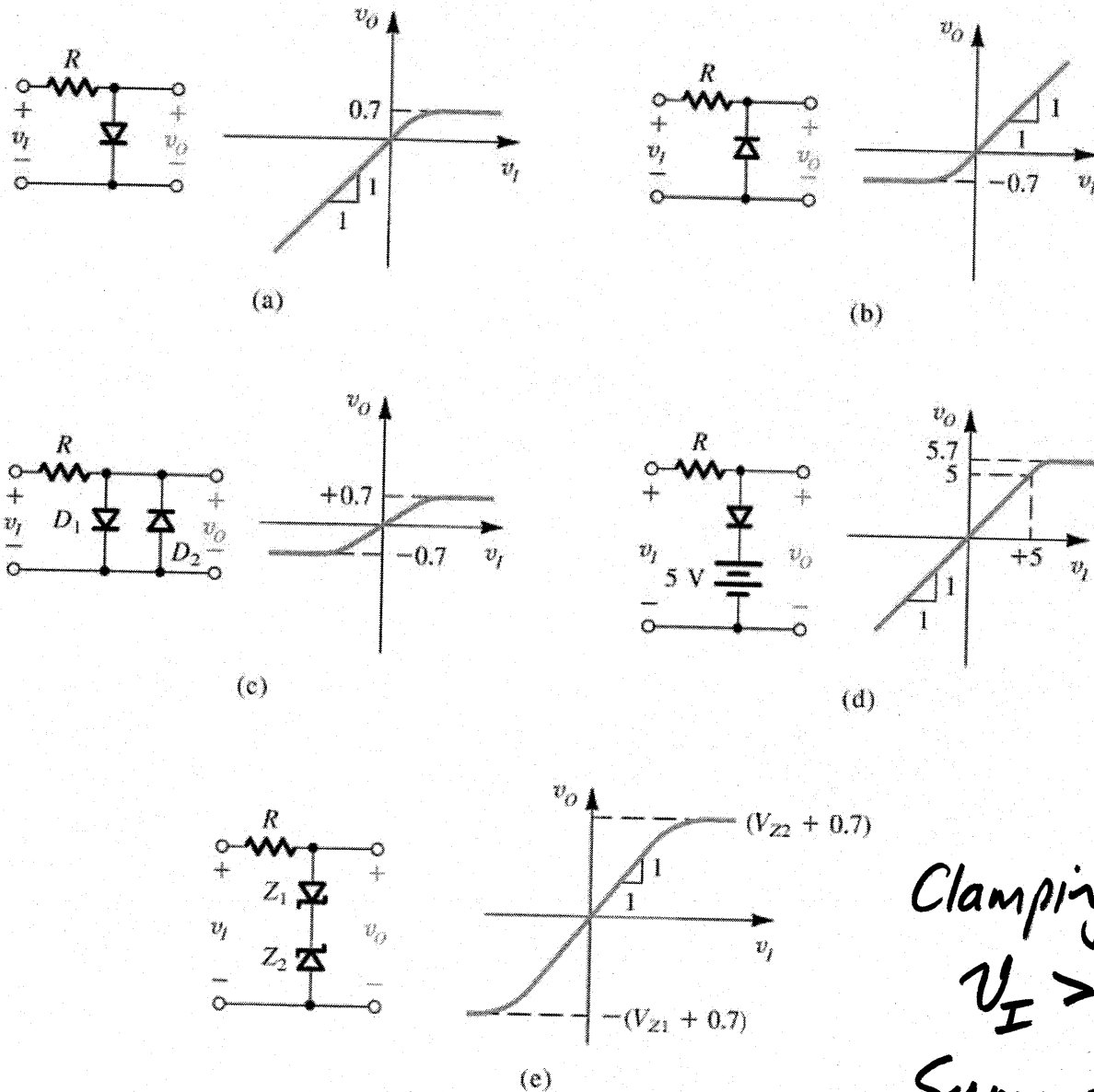

Clamping for
 $v_i > V_z + 0.7V$
 Symmetrical

Figure 3.35 A variety of basic limiting circuits.

Ex. 3.27

**Diode limiter
(diode clipping)**

DC Restorer



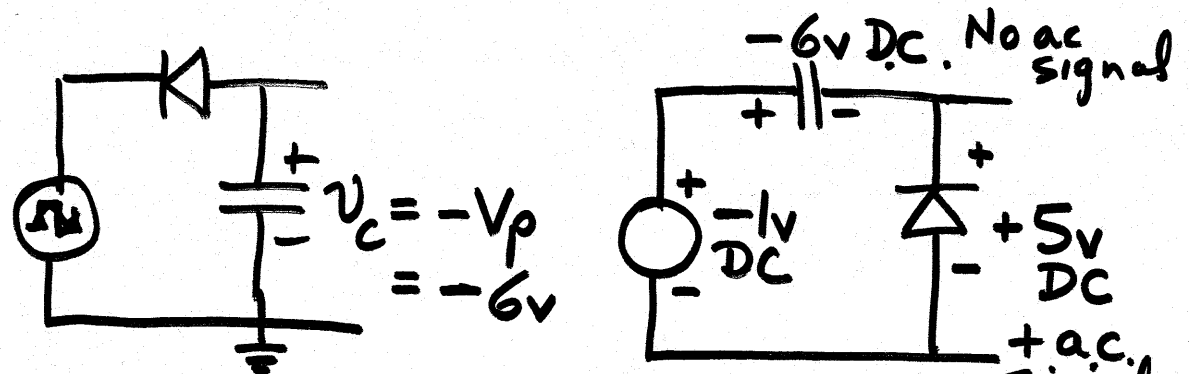
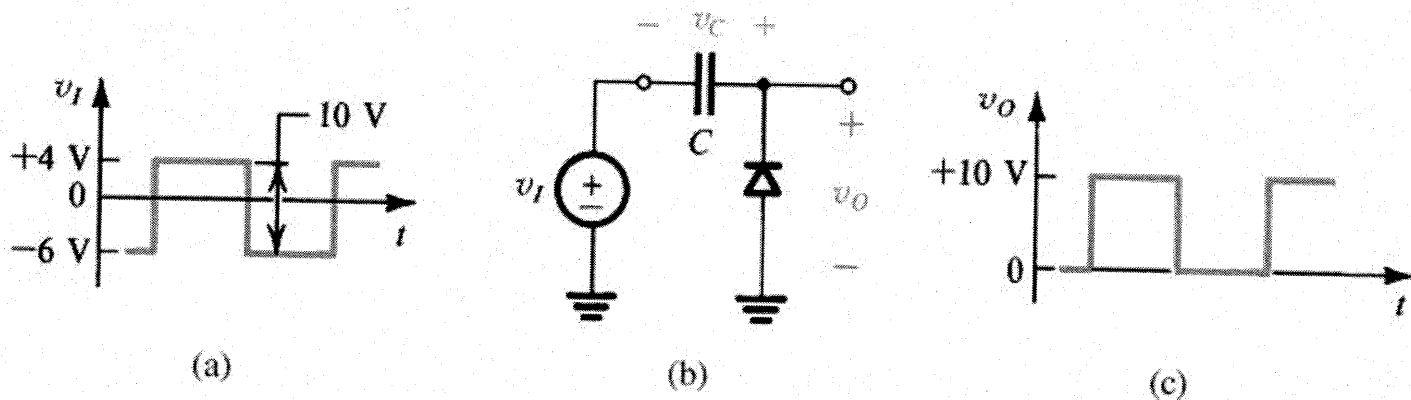
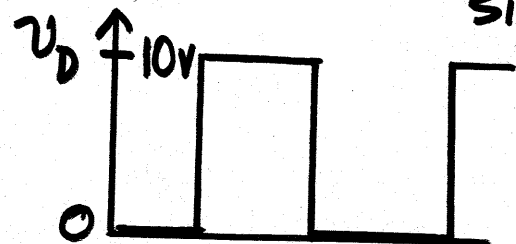
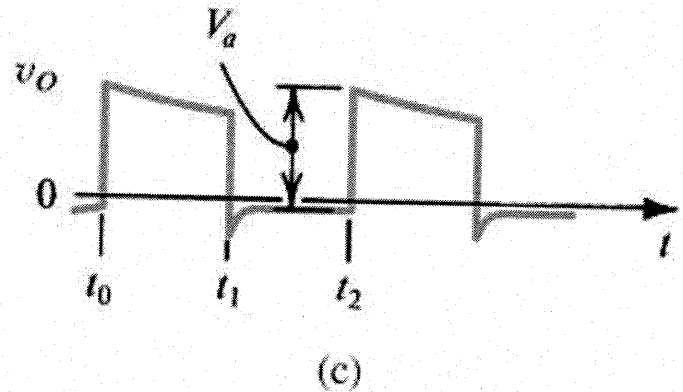


Figure 3.36 The clamped capacitor or dc restorer with a square-wave input and no load.

Diode clamps output to 0 v

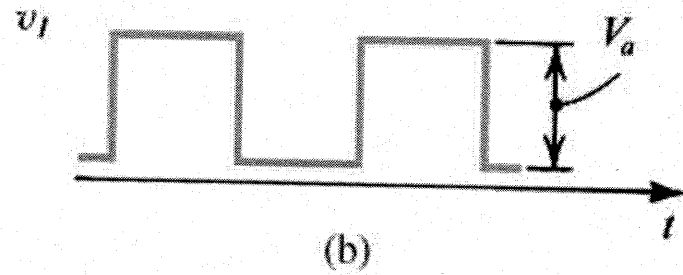

DC Restorer with Load

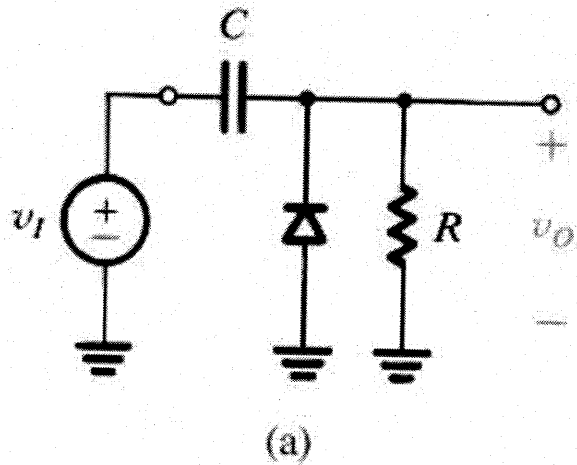


$v_0 \text{ DC} = +5\text{V}$

$\therefore I_R$ flows


Diode reverse biased, $\therefore I_R$ from C (discharges slowly)
 Then diode re-charges fast when input \rightarrow neg
 & turns diode on ($v_0 < 0$)

Figure 3.37 The clamped capacitor with a load resistance R.

Voltage Doubler

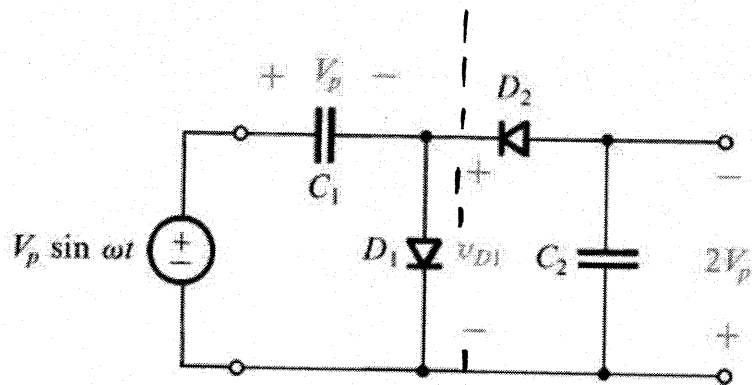

(a) **Clamp** | **Peak Rectifier**

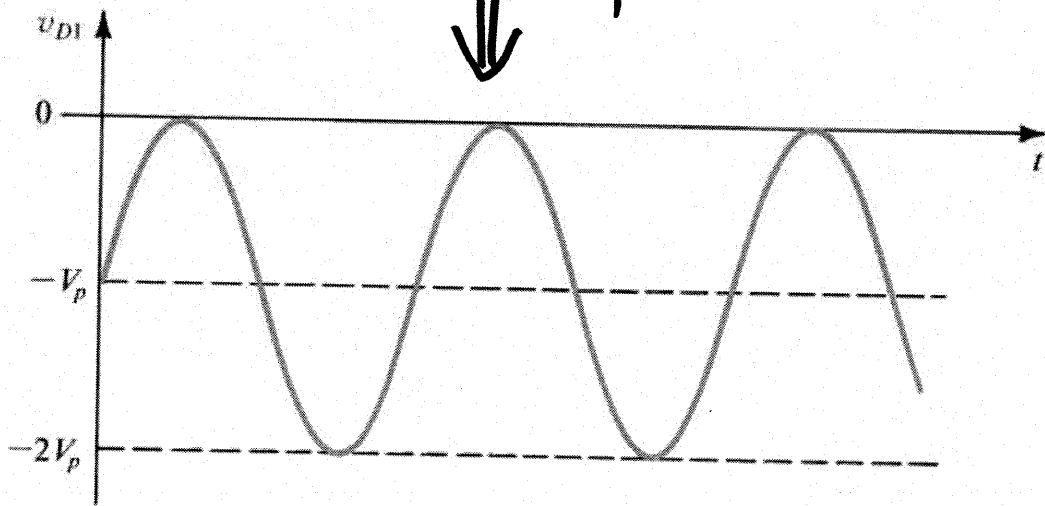

Clamps to 0V
 $v_{D1} < 0V$

(b)

Now rectifier
 $\rightarrow v_o = -2V_p$

Figure 3.38 Voltage doubler: (a) circuit; (b) waveform of the voltage across D_1 .

Assignment #3

3.29

D3.43

D3.68



3.85

3.102

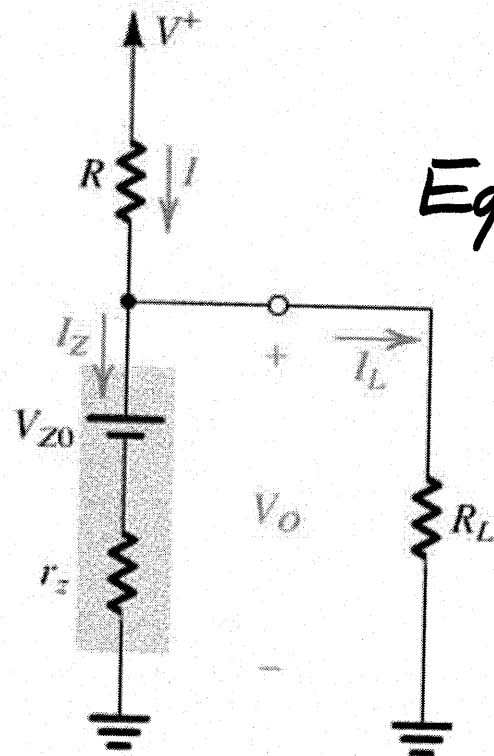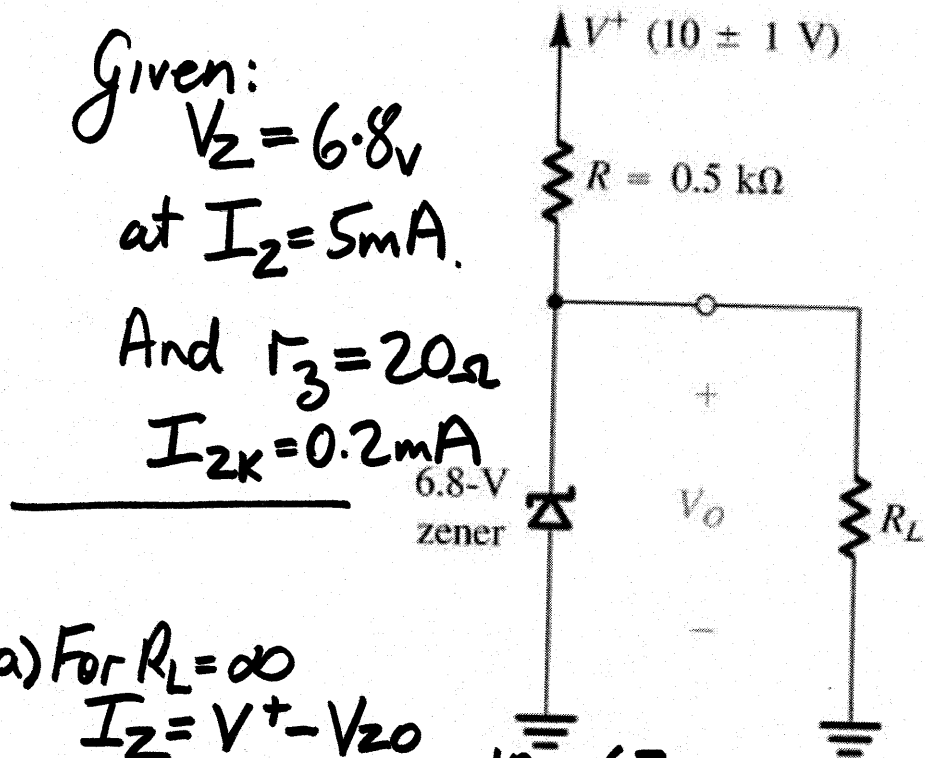Example 3.8 Voltage Regulation

Given:
 $V_Z = 6.8\text{V}$
 at $I_Z = 5\text{mA}$.

And $r_z = 20\Omega$
 $I_{ZK} = 0.2\text{mA}$



Equivalent circuit:

Need V_{Z0}

$$V_Z = V_{Z0} + I_Z r_z$$

$$\therefore V_{Z0} = 6.8\text{V} - 20\Omega \times 5\text{mA} = 6.7\text{V}$$

(a) For $R_L = \infty$

$$I_Z = \frac{V^+ - V_{Z0}}{R + r_z} = \frac{10 - 6.7}{520} = 6.35\text{mA} \therefore V_0 = 6.7 + 6.35 \times 10^{-3} \times 20 = 6.83\text{V}$$


(b) $\pm 1\text{V}$ change in $V^+ \longrightarrow \pm 1\text{V} \frac{r_z}{R + r_z}$ (for $R_L = \infty$) = $\frac{20}{520} = \pm 38.5\text{mV}$

"Line regulation" = $(\Delta V_0 / \Delta V^+) \times 100\% = 3.85\%$ or 38.5mV/V

Figure 3.23 (a) Circuit for Example 3.8. (b) The circuit with the zener diode replaced with its equivalent circuit model.

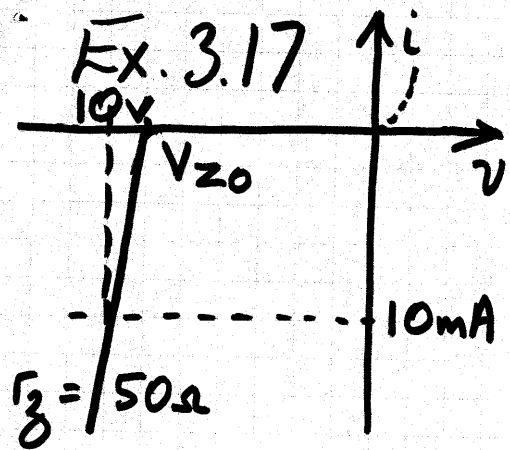(c) For $I_L = 1\text{mA}$, $I_Z \rightarrow 5.35\text{mA}$ But can find $\Delta V_0 = r_z \Delta I = 20 \times (-1\text{mA}) = -20\text{mV}$

"Load regulation" = $(\Delta V_0 / \Delta I_L) = -20\text{mV/mA} = -20\text{mV}$





Zener $10mA @ 10V$. $r_z = 50\Omega$

$$V_z \text{ for } 5mA? = 10V - 5mA \times 50\Omega = 9.75V$$

$$V_z \text{ for } 20mA? = 10V + 10mA \times 50\Omega = 10.5V$$
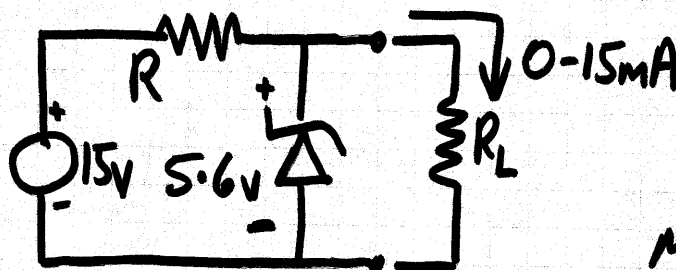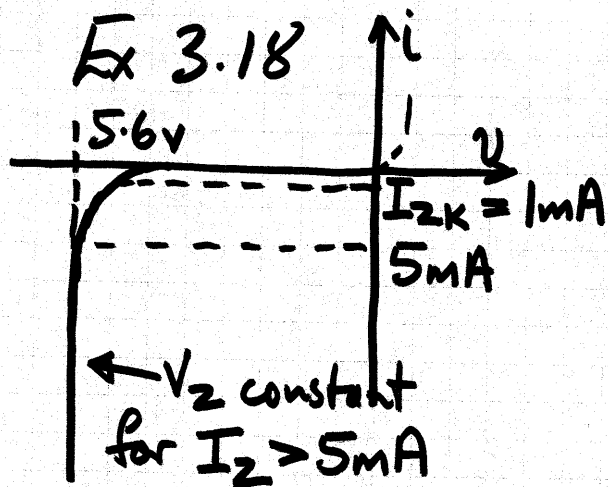
$$V_{zo}? = 10V - 10mA \times 50\Omega = 9.5V$$





For $V_z = 5.6V$,
 need $I_z \geq 5mA$.

Max $I_L = 15mA$

\therefore need $20mA$ through R
 so $I_z = 5 \uparrow 20mA$
 \uparrow max I_L \uparrow $I_L = 0$


$$\therefore R = \frac{15V - 5.6V}{20mA} = 470\Omega$$
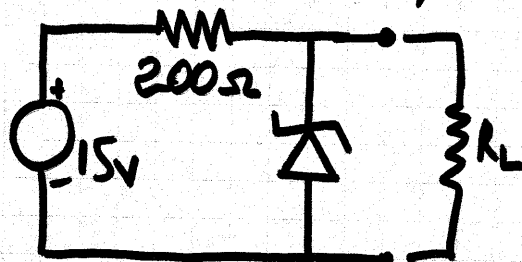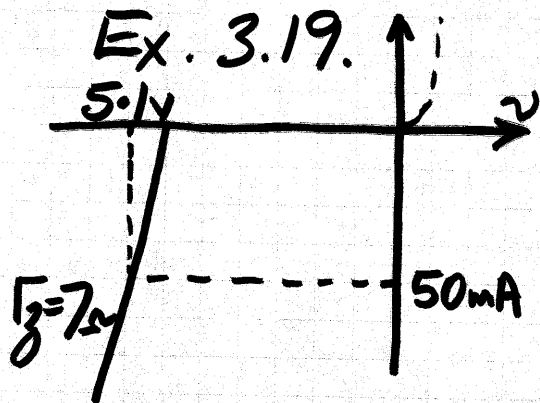
$$\text{Max zener power} = V_z I_{z,max} = 5.6V \times 20mA = 112mW$$



Assume $V_{zo} = 5.1V - 50mA \times 7\Omega = 4.75V$

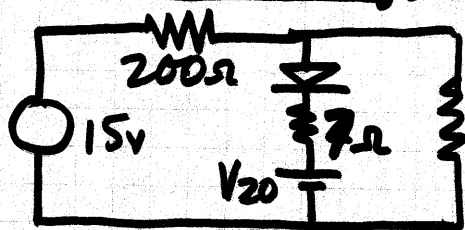No load: $V_z = 4.75V + 7\Omega \frac{15 - 4.75V}{200\Omega} = 4.75 + 0.359 = 5.11V$




Line regulation: $\frac{7}{7+200} V/V = 33.8mV/V$

Load regulation: $\frac{\Delta V}{\Delta I_L} = -\frac{\Delta I_L}{\Delta I_L} r_z = -7mV/mA$

D3.24

12V RMS
60Hz

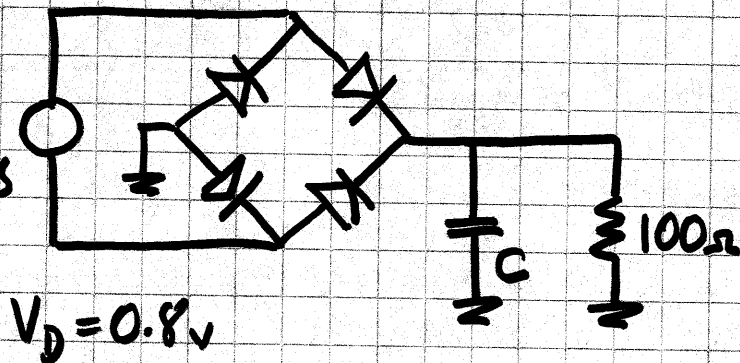

Find C for $V_r < 1V$ pk-pk

Find dc voltage V_0

Find load current

Find diode PIV

Specify diode I_{pk} and PIV.

$$12V_{RMS} \rightarrow 12\sqrt{2} \text{ pk} \quad \therefore V_p \approx 17.0V \quad \& \quad V_r = \frac{V_p}{2fRC}$$

$$\text{So } C \geq \frac{V_p}{V_r} \frac{1}{2fR} = \frac{17.0}{1.2 \cdot 60 \cdot 100} = 1,417 \mu F$$

Or more accurately: $V_p = 17 - 2V_D = 15.4V$

$$\therefore C \geq \frac{15.4}{12 \times 10^3} = 1,283 \mu F$$

So say $C = 1.5 \text{ mF}$

$$V_0 = 15.4 - V_r/2 = 14.9V$$


$$I_L = 14.9V / 100\Omega = 149 \text{ mA}$$

$$\text{Diode PIV} = V_s - V_D = 17 - 0.8 = 16.2V$$

$$I_{D,MAX} = I_L (1 + 2\pi \sqrt{(V_p - 2V_D) / 2V_r}) = 149 \text{ mA} (1 + 2\pi (15.4/2)^{1/2}) = 2.75A$$

Specify $I_{pk} \approx 3A$
 $PIV \approx 20V$


Ex 3.26

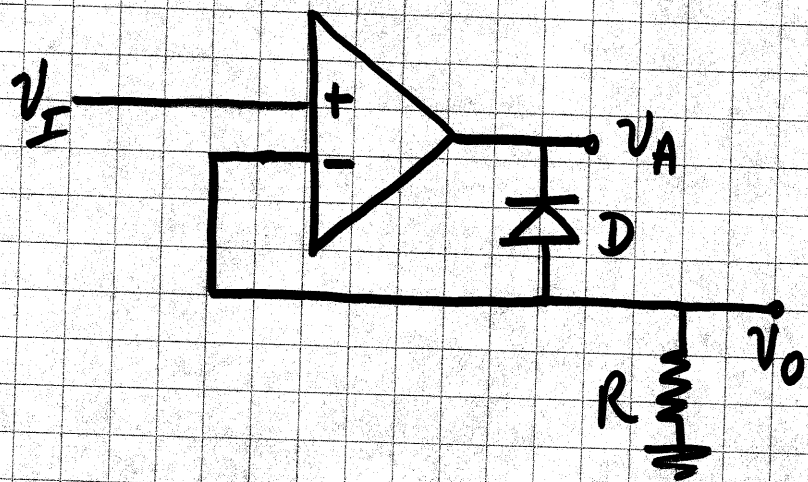



If $v_I > 0$ $v_A \rightarrow$ high D reverse biased (OFF)
 $\therefore v_O = 0$

If $v_I < 0$ $v_A \rightarrow$ low D forward biased (ON)
 (negative feedback)

$$\therefore v_O = v_I \quad (v_A = v_I - V_D)$$

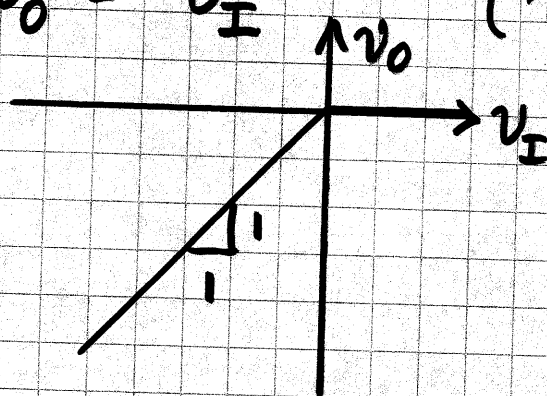

Ex 3.27

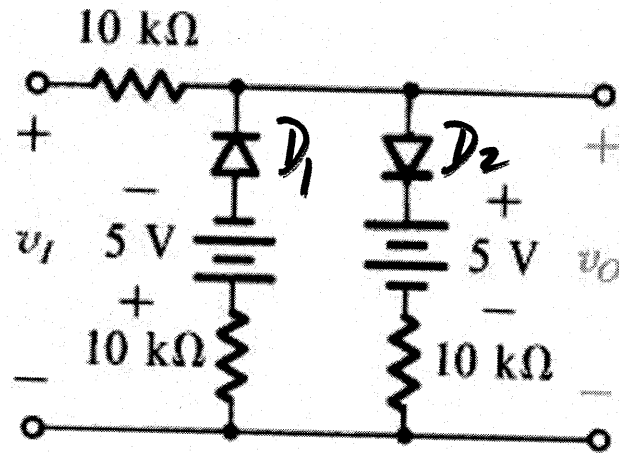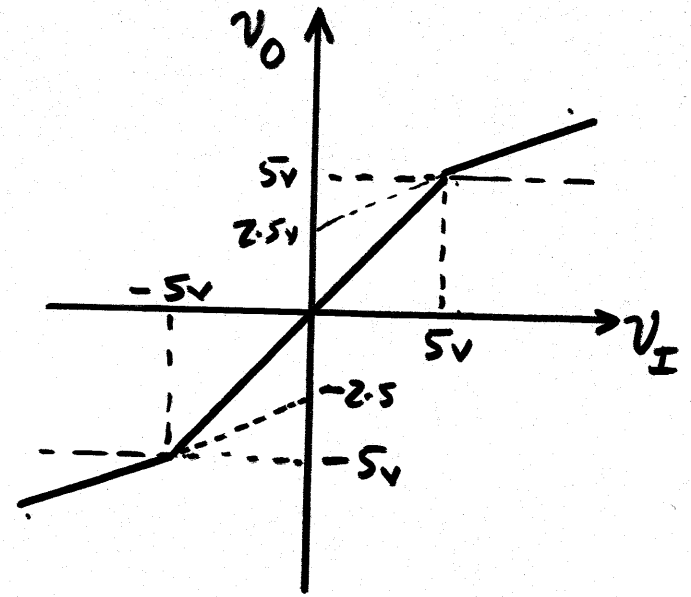

D_1 off unless $v_I < -5V$,

D_2 off unless $v_I > +5V$

$$v_o = +5 + \frac{1}{2}(v_I - 5V)$$

$$= v_I/2 + 2.5V$$

Figure E3.27

$-5V < v_I < 5V$, D_1 & D_2 off, $v_o = v_I$

$$v_o = -5V + \frac{v_I - (-5V)}{20K} \cdot 10K$$

$$= -5 + \frac{v_I}{2} + \frac{5}{2}$$

$$= v_I/2 - 2.5V$$