

ECE321 ELECTRONICS I

FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 9
24th October, 2006

CHAPTER 4

MOS Field-Effect Transistors (MOSFETs)

*By examples
(7 exercises)*

4.3 DC Circuits

4.4 MOSFET Amplifier & Switch

4.5 Biasing

Exercises

D4.10

D4.11

4.12

4.13


4.14

D4.15


4.16 ← & Example 4.7

LARGE SIGNAL OPERATION: TRANSFER CHARACTERISTIC

CS: Common Source circuit

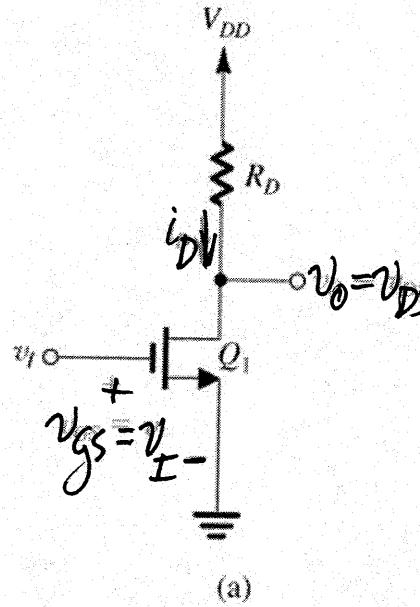

(a)

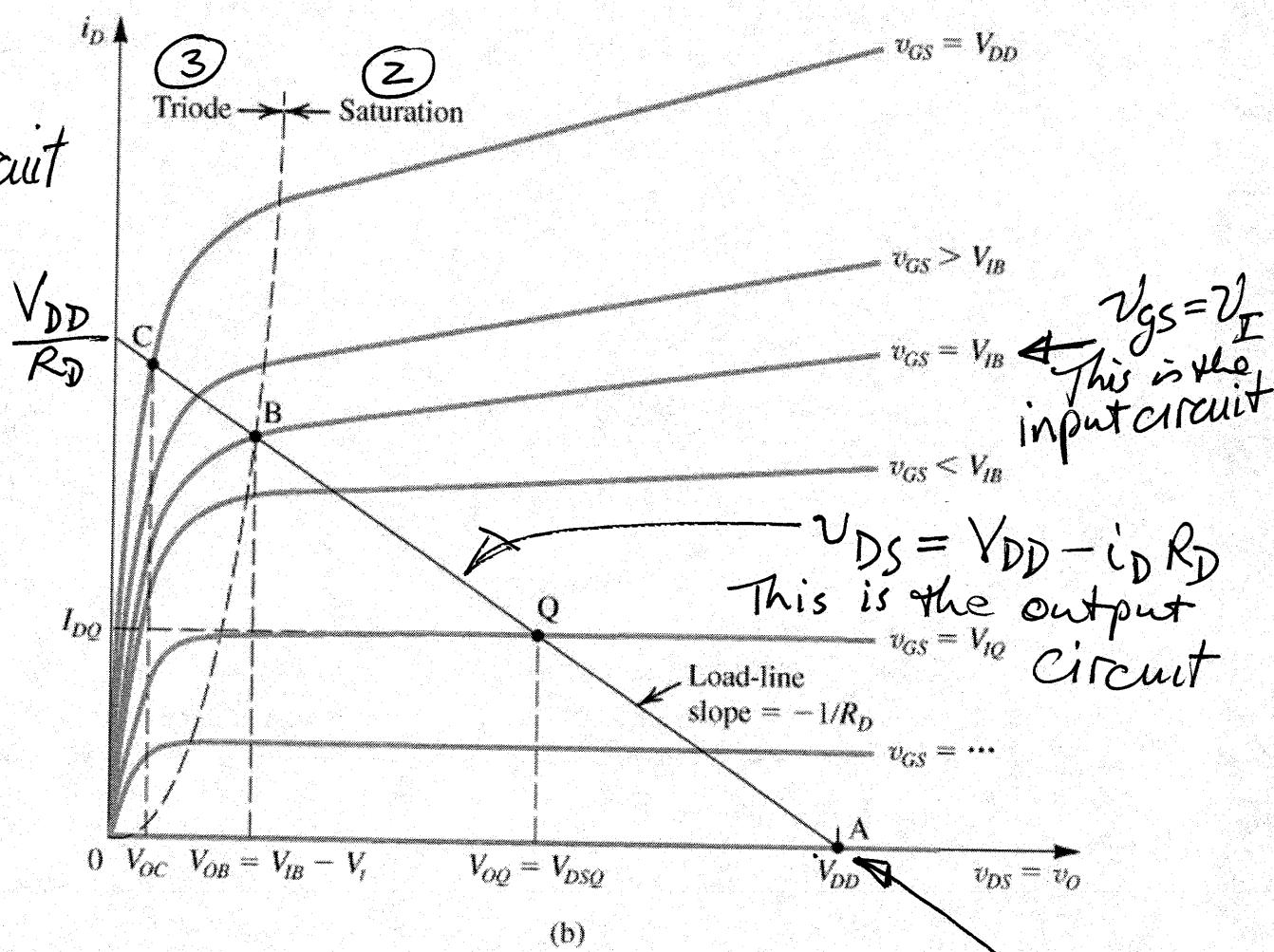

Amplifier and Switch Operation

Figure 4.26 (a) Basic structure of the common-source amplifier. (b) Graphical construction to determine the transfer characteristic of the amplifier in (a).

Choice of R_D for maximum signal swing

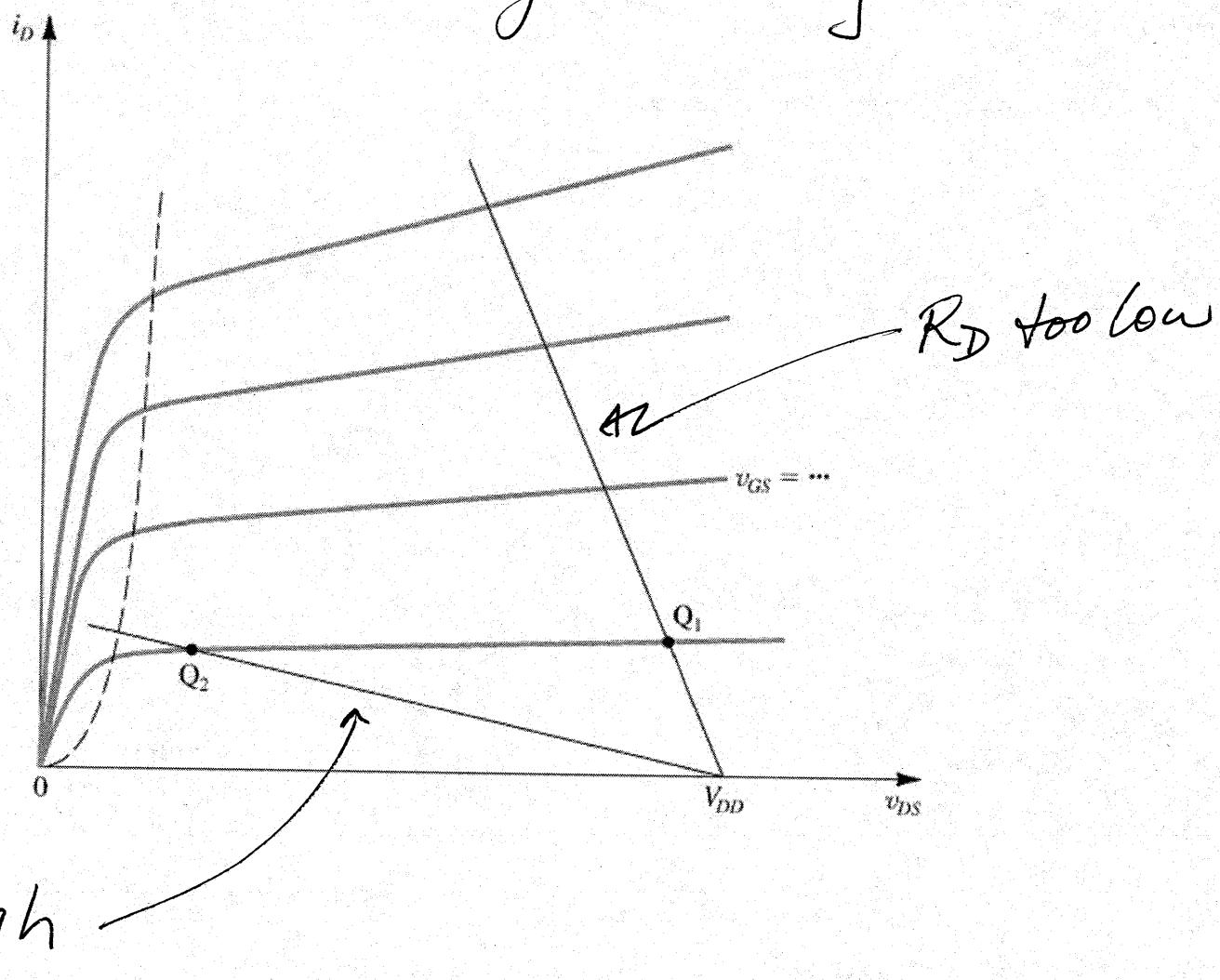



Figure 4.27 Two load lines and corresponding bias points. Bias point Q_1 does not leave sufficient room for positive signal swing at the drain (too close to V_{DD}). Bias point Q_2 is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.

TRANSFER CHARACTERISTIC (Assume $\lambda=0$)

① Cutoff
where
 $v_I < v_t$

$$I_D = 0$$

$$\& \quad v_o = V_{DD}$$

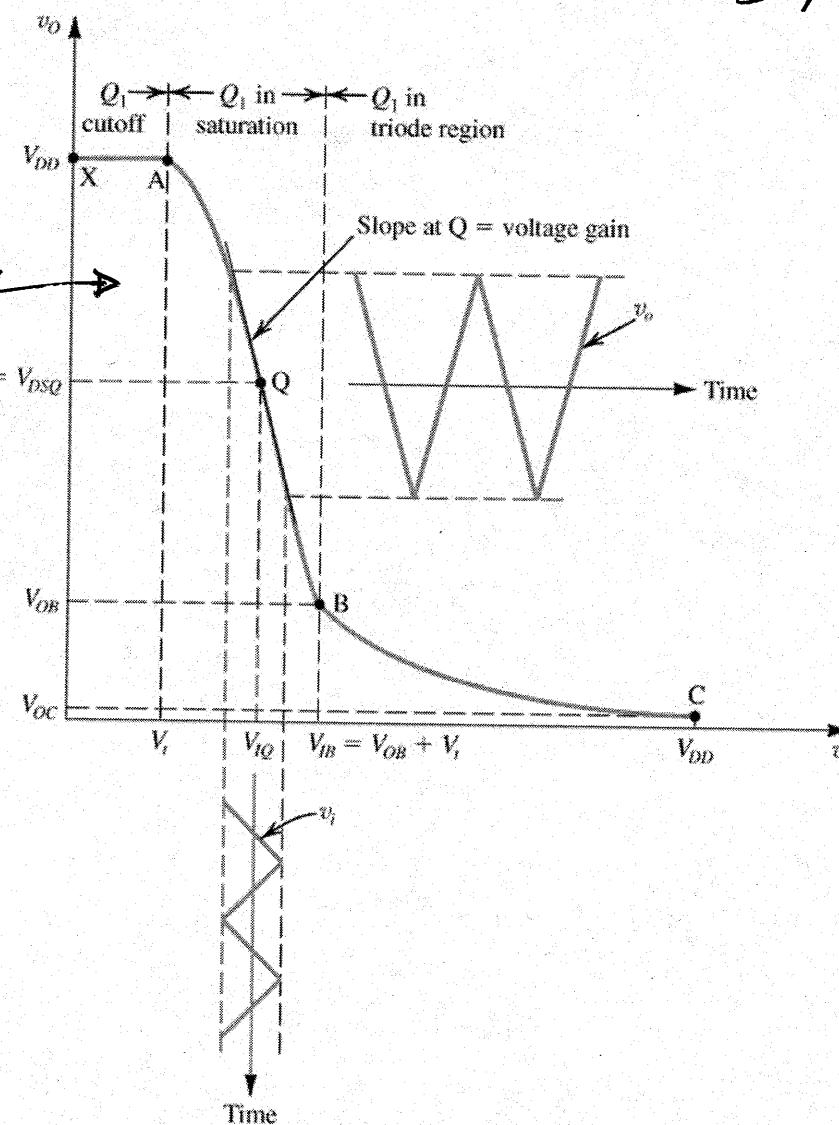

(c)

Figure 4.26 (Continued) (c) Transfer characteristic showing operation as an amplifier biased at point Q.

② Saturation:

$$V_I > V_t$$

$$V_o > V_I - V_t$$

$$V_{GS} > V_t$$

$$V_{DS} > V_{GS} - V_t$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_I - V_t)^2$$

and $V_o = V_{DD} - i_D R_D$

$$V_o = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_I - V_t)^2 \quad \text{ie. clearly non-linear}$$

$$(A_v = \frac{dV_o}{dV_I} = -\mu C_{ox} \frac{W}{L} R_D (V_{IQ} - V_t)) \quad " \quad " \quad " \quad " \quad)$$

Regions end point is where saturation \rightarrow triode region

i.e. $V_{DS} < V_{GS} - V_t$ for triode

$$V_o < V_I - V_t \Rightarrow V_I > V_o + V_t$$

V_{OB} point defined by

$$\begin{aligned} V_o &= V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_o - V_t)^2 \\ &\Rightarrow V_{DD} - \frac{1}{2} \lambda V_o^2 \end{aligned}$$

$$\therefore V_{OB}^2 + \lambda V_{OB} - \lambda V_{DD} = 0 \Rightarrow V_{OB} = \frac{-\lambda \pm \sqrt{\lambda^2 + 4\lambda V_{DD}}}{2} = \frac{\lambda}{2} \left(\sqrt{1 + \frac{4V_{DD}}{\lambda}} - 1 \right)$$

③ Triode

$$V_I > V_t$$

$$V_o < V_I - V_t$$

$$V_{DS} < V_{GS} - V_t$$

$$i_D = \mu_n C_{ox} \frac{W}{L} ((V_I - V_t) V_o - \frac{1}{2} V_o^2)$$

&

$$V_o = V_{DD} - i_D R_D = V_{DD} - \mu_n C_{ox} \frac{W}{L} R_D ((V_I - V_t) V_o - \frac{1}{2} V_o^2)$$

$$\text{so } V_o^2 \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D \right] + V_o \left[1 + \mu_n C_{ox} \frac{W}{L} R_D (V_I - V_t) \right] - V_{DD} = 0$$

Solve for $V_o(V_I) \rightarrow \text{non-linear}$

For V_o small, ie. $V_o \ll V_I - V_t$, drop the V_o^2 term

$$V_o \approx V_{DD} - \mu_n C_{ox} \frac{W}{L} R_D (V_I - V_t) V_o$$

$$\Rightarrow \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_I - V_t)}$$

$$\text{& for } f_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_I - V_t)}$$

$$V_o \rightarrow \frac{V_{DD}}{1 + \frac{R_D}{f_{DS}}} = V_{DD} \frac{f_{DS}}{R_D + f_{DS}}$$

Example 4.8 Non-linearity


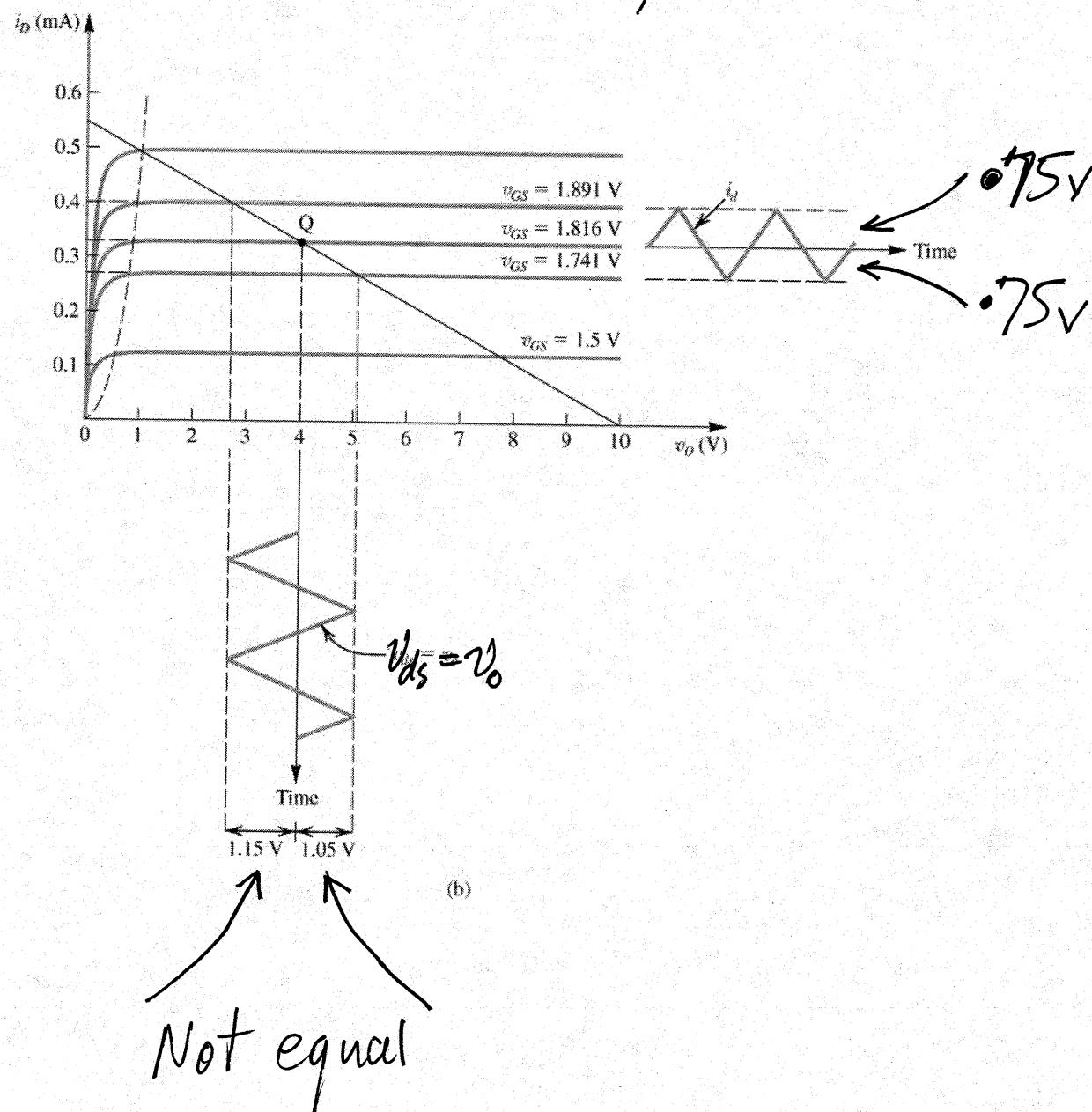


Figure 4.28 (Continued)

Exercise 4.17

Fixed Bias

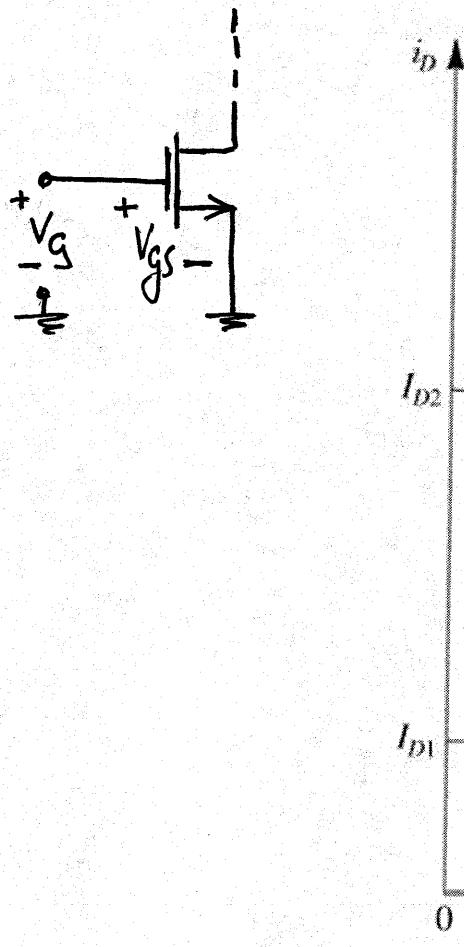

$$\text{Ex 4.19(a)} V_t = 1V, k_n \frac{W}{L} = 1mA/V^2 \\ \lambda = 0, V_{DD} = 15V$$

For $I_D = 0.5mA$

$$0.5 = \frac{1}{2} 1mA (V_{GS} - 1)^2 \\ \therefore V_{GS} = \sqrt{1} + 1 = 2V$$


$$(b) \text{ If } V_t \rightarrow 1.5V$$

$$I_D = 0.5mA (2 - 1.5)^2 \\ = 0.125mA$$


$$\therefore \Delta I = \frac{0.125 - 0.5}{0.5} 100\% \\ = -75\%$$

Figure 4.29 The use of fixed bias (constant V_{GS}) can result in a large variability in the value of I_D . Devices 1 and 2 represent extremes among units of the same type.

Self-Bias/Auto bias/Classic Bias

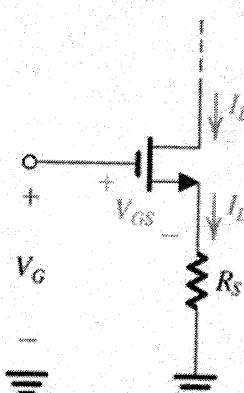


(a)

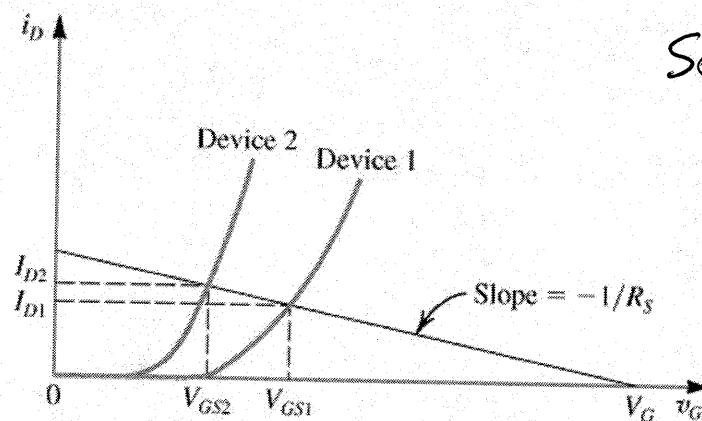


$$V_{GS} = V_G - i_D R_S$$

$$i_D = \frac{V_G - V_{GS}}{R_S}$$

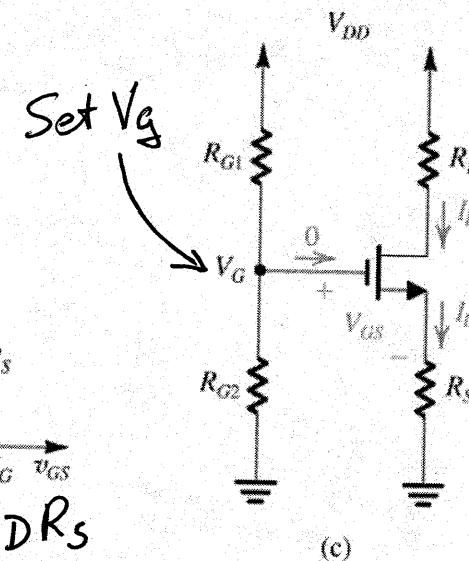


(c)

CS Amplifier
(Source & coupling capac.)

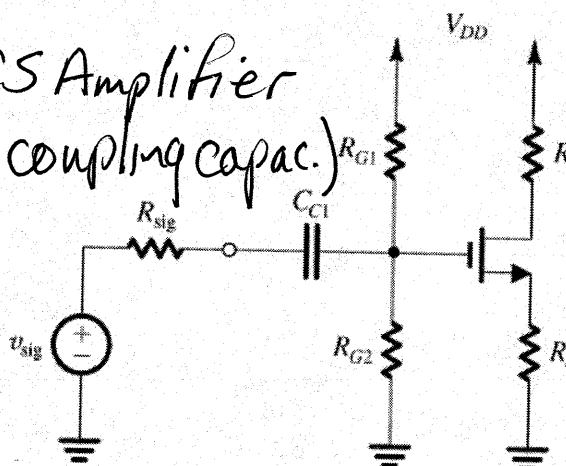

(d)

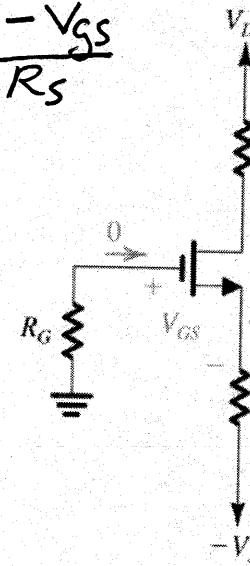

(e)

2 supplies



Figure 4.30 Biasing using a fixed voltage at the gate, V_G , and a resistance in the source lead, R_S : (a) basic arrangement; (b) reduced variability in I_D ; (c) practical implementation using a single supply; (d) coupling of a signal source to the gate using a capacitor C_{CI} ; (e) practical implementation using two supplies.

Compare Example 4.9 (Selfbias) 9% change as $V_t = kV \rightarrow 1.5V$
& Exercise 4.19 75% change for fixed bias

Exercise D4.20

Exercise D4.21

Constant Current Source Bias

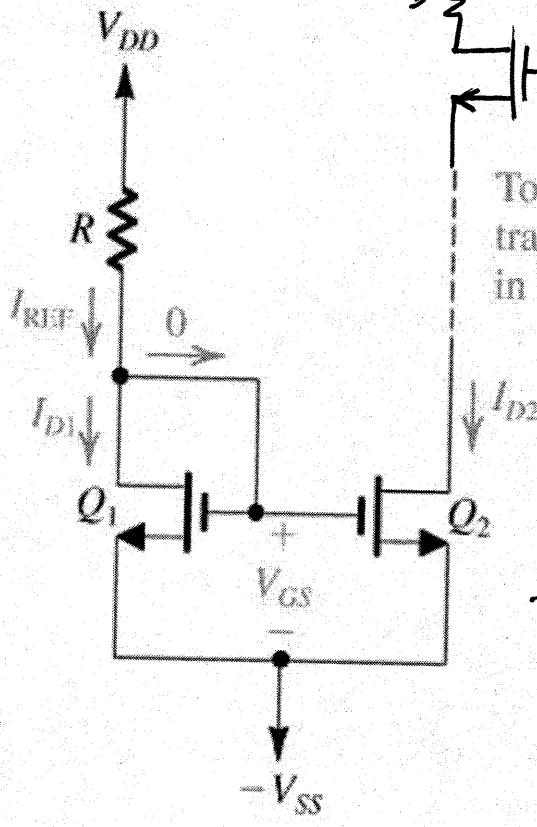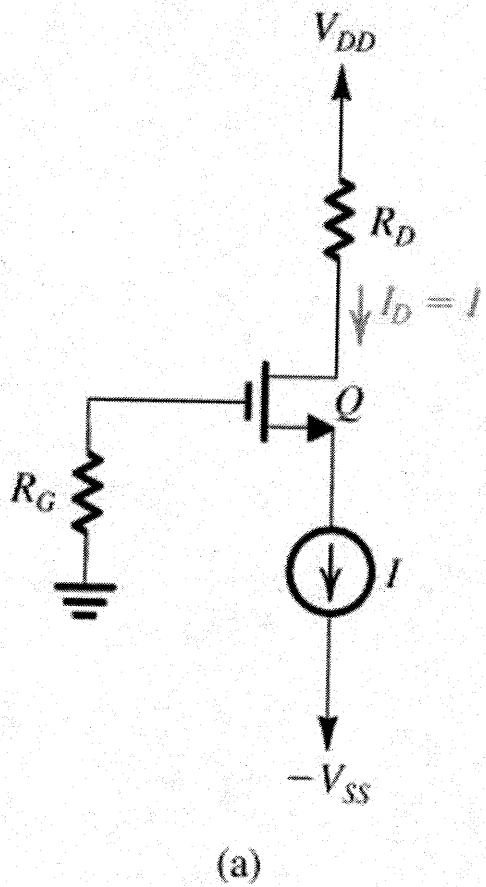

To source of
transistor Q
in Fig. 4.33 (a)

Q_1 saturated

$$\begin{aligned} \therefore I_{D1} &= \frac{1}{2} k_n' \left(\frac{W}{L} \right)_1 (V_{gs} - V_t)^2 \\ &= I_{REF} \\ &= \frac{V_{DD} - V_{gs} - (-V_{ss})}{R} \end{aligned}$$

$$I = I_{D2} = \frac{1}{2} k_n' \left(\frac{W}{L} \right)_2 (V_{gs} - V_t)^2$$

$$\therefore I = I_{REF} \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$

Figure 4.33 (a) Biasing the MOSFET using a constant-current source I . (b) Implementation of the constant-current source I using a current mirror.

Current Mirror

Exercise D4.22

Ex D4.10 Re-design circuit (Example 4.2) for $V_{DD} = -V_{SS} = 2.5V$
 $V_t = 1\text{ volt}$ $\mu_nC_{ox} = 60\mu\text{A}/\text{v}^2$ $W/L = 120\mu\text{m}/3\mu\text{m}$

$$V_{DD} = +2.5V$$

$$I_D = 0.3\text{mA} \quad V_D = +0.4V$$

i.e. Find R_s, R_D

$$V_D > V_g$$

∴ In saturation mode

$$R_D = \frac{(2.5 - 0.4)V}{0.3\text{mA}} = \frac{2.1}{0.3}K = 7K\Omega$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

$$\begin{aligned} \therefore V_{gs} &= V_t + \left(\frac{2I_D}{\mu_n C_{ox}} \frac{L}{W} \right)^{1/2} \\ &= 1V + \left(\frac{2 \times 0.3 \times 10^{-3}}{60 \times 10^{-6}} \frac{3}{120} \right)^{1/2} \\ &= 1V + (1/4)^{1/2} = 1.5V \end{aligned}$$

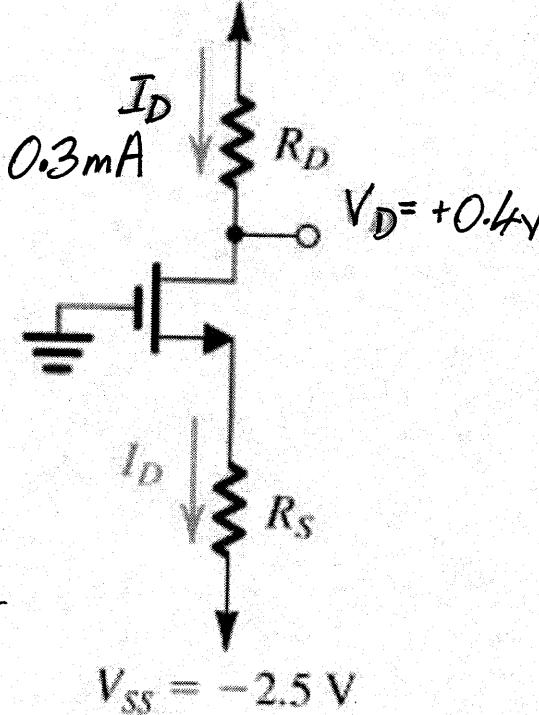


Figure 4.20 Circuit for Example 4.2.

$$\therefore V_s = -1.5V$$


$$\therefore R_s = \frac{-1.5V - (-2.5V)}{0.3\text{mA}} = \frac{1V}{0.3\text{mA}} = 3.3K\Omega$$

D4.11 Re-design the circuit (Example 4.3) to double I_D without changing V_D . ie. Find new values of $\frac{W}{L}$ and R .

i.e. $I_D = 160\mu A$ and $V_D = 1V$

$$\therefore R = \frac{2V}{160\mu A} = 12.5k\Omega \quad V_{DD} = +3V$$

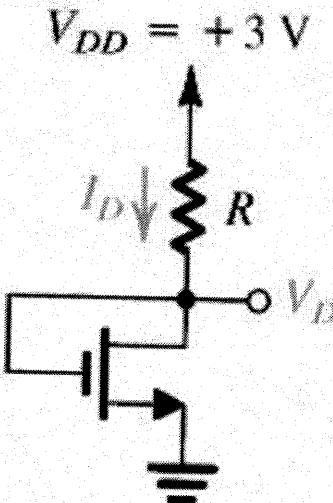$V_D = V_g \therefore$ In saturation mode



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

$$\text{so } \frac{W}{L} = \frac{2 I_D}{\mu_n C_{ox} (V_{gs} - V_t)^2} = \frac{320 \times 10^{-6}}{200 \times 10^{-6} (1 - 0.6)^2} = \frac{1.6}{16} = 10$$

Figure 4.21 Circuit for Example 4.3.

From Example 4.3

$$V_{gs} = V_D$$

Ex. 4.12

Q_1 designed in Example 4.3, i.e. $R=25K$, $V_D=1V$

$$I_{D1} = 80 \mu A \quad V_T = 0.6 V$$

$$\mu_{\text{Co}} = 200 \mu\text{A}/\text{V}^2$$

$$W/L = 5 \quad \lambda = 0$$

Q_1, Q_2 same, i.e. V_t 's same

$$V_{GS2} = V_{GS1} = V_D = 1\text{V}$$


Q_1 saturated ($V_G = V_D$)

Assume Q_2 also saturated

Then $I_{D2} = I_{D1} = 80\mu A$

$$\begin{aligned} \therefore V_{D2} &= 3_v - 80 \times 10^{-6} \times 20 \times 10^3 \\ &= 3 - 1.6 \text{ v} \\ &= 1.4 \text{ v} \end{aligned}$$

Figure E4.12

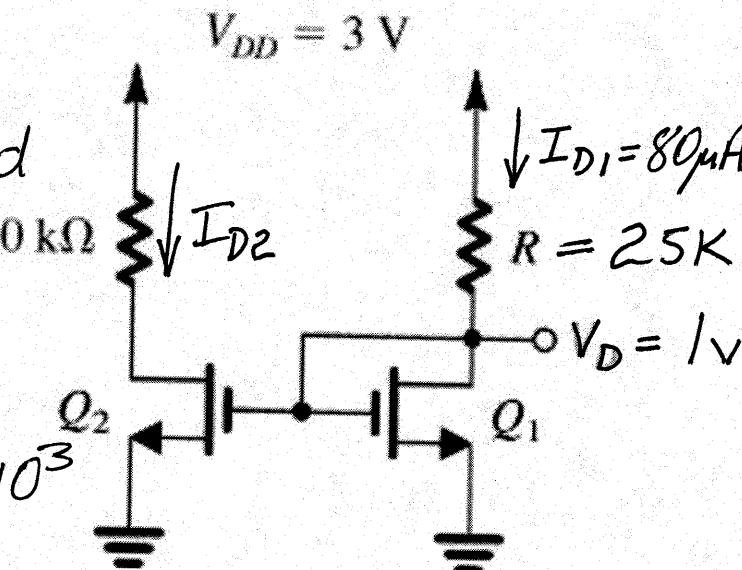

$\therefore V_{D2} > V_g$ & Q_2 saturation is confirmed

Note: If $R_2 = 40\text{ k}\Omega$, say, then $V_{D2} = 3 - 80\mu\text{A} \times 40\text{ k} = 3 - 3.2\text{ V} \rightarrow -0.2\text{ V}$ (Not poss.)
 i.e. $V_{D2} \neq V_{GS2} - V_t$ & Q_2 NOT saturated


Ex 4.13 Find approx. I_D and V_D if R_D doubled from Example 4.4.

$$V_t = 1V \quad k_n' W_L = 1mA/V^2$$

Note: there's a possible ambiguity since calculation in Example 4.4 gives $R_D = 12.4K \rightarrow 12K$ for nearest 5% value
 But the Example 4.4 final result uses 12.4K, so we will use:

$$R_D = 24.8K$$

$V_G \gg V_D$
 \therefore Triode region

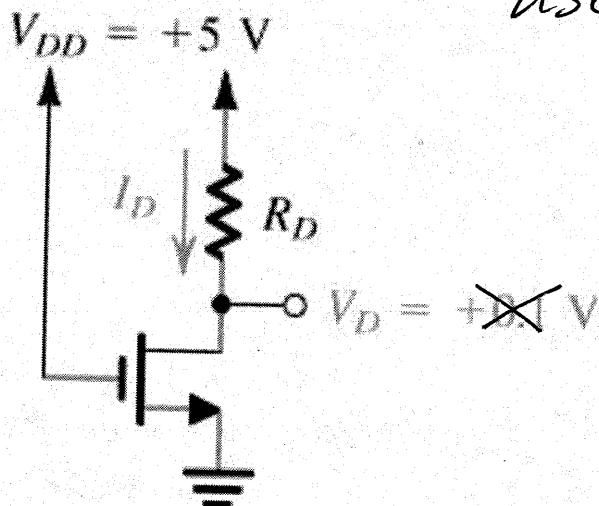

$$I_D = k_n' \frac{W}{L} [(V_{GS} - V_t)V_{DS} - V_{DS}^2/2]$$

$$= 10^{-3} ((5-1)V_{DS} - 0.5V_{DS}^2)$$

$$= 1mA (4V_{DS} - 0.5V_{DS}^2)$$

Figure 4.22 Circuit for Example 4.4.

$$\text{Also } V_D = 5 - I_D R_D = 5 - 24.8 I_D \times 10^3 \quad \left\{ \begin{array}{l} \\ \end{array} \right.$$

$$V_D = 5 - 24.8 (4V_D - 0.5V_D^2)$$



$$12.4V_D^2 - 100.2V_D + 5 = 0$$

$$V_D \approx \frac{1.25}{25} = 0.05V$$

$$\therefore I_D = 1mA (4 \times 0.05 - \frac{0.05^2}{2}) \approx 0.2mA$$

$$Ex. 4.14. \quad V_t = 1V \quad k_n' \frac{W}{L} = 1mA/V^2 \quad \lambda = 0 \quad \text{Max } R_D \text{ for sat.?}$$

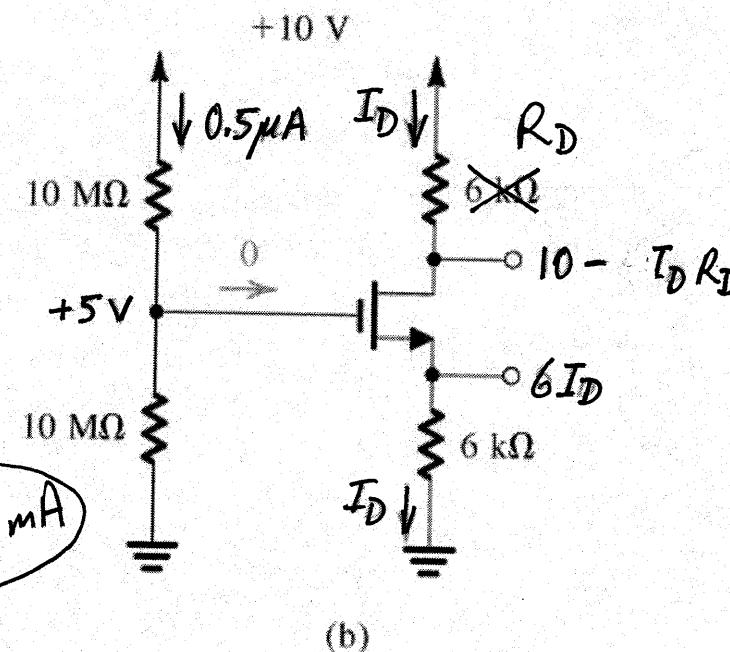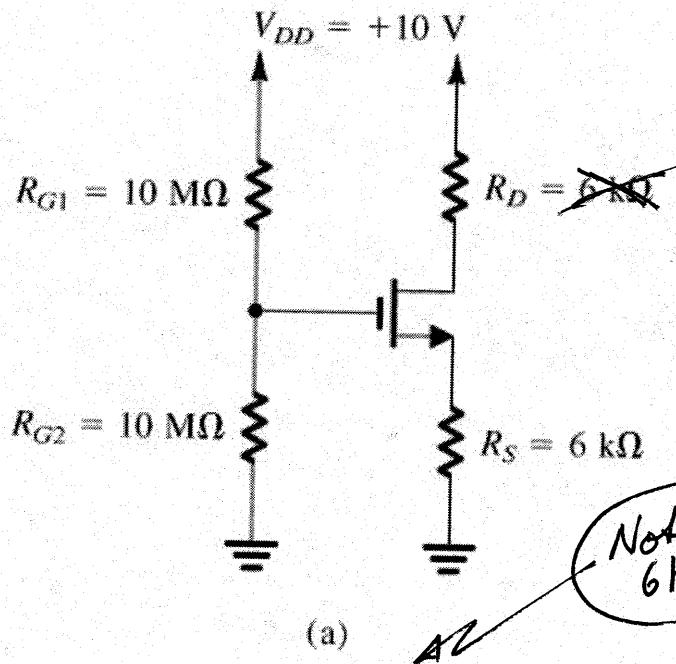$I_D = 0.5mA$ from Example 4.5,
independent of R_D if $\lambda = 0$ as long as saturated.



$$V_{GS} = 5 - 6I_D$$

$$V_D = 10 - I_D R_D$$

For saturation

$$V_D \geq V_G - V_t = 5 - 1 = 4V$$

$$\therefore 10 - I_D R_D \geq 4V$$

$$R_D \leq \frac{6V}{0.5} = 12k\Omega$$

in mA


Figure 4.23 (a) Circuit for Example 4.5. (b) The circuit with some of the analysis details shown.

D4.15

$$V_t = 1V$$

$$k_n' \frac{W}{L} = 1mA/V^2$$

$$\lambda = 0$$

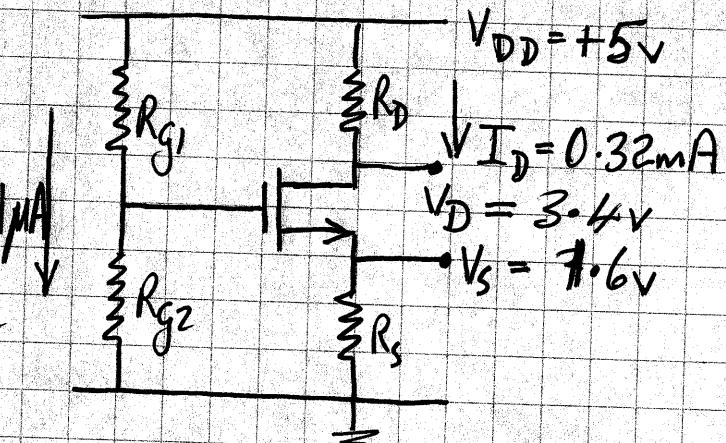

$$R_{G1} + R_{G2} = \frac{5V}{1\mu A} = 5M\Omega$$

$$R_s I_D = 1.6V$$

$$\therefore R_s = \frac{1.6}{32} K = 5K$$

$$5 - I_D R_D = 3.4V$$

$$\therefore R_D I_D = 1.6V$$

$$\therefore R_D = 5K$$

Assume saturation $\therefore I_D = \frac{1}{2} (V_g - V_S - 1)^2 = .32$

$$\text{i.e. } V_{GS} = (.64)^{1/2} + 1 = 1.8V$$

$$\therefore V_g = 1.6 + 1.8 = 3.4V$$

$$\therefore R_{G2} = 3.4 M\Omega$$

$$R_{G1} = 1.6 M\Omega$$

Check: $V_D = 3.4V$ $V_g = 3.4V$ $\therefore V_D > V_g - V_t$ Saturation confirmed

Ex 4.16 (Contrast with Example 4.7 → Drains to load)

$$k_n' \frac{W_n}{L_n} = k_p' \frac{W_p}{L_p} = 1 \text{ mA/V}^2$$

$$V_{tn} = -V_{tp} = 1 \text{ V} \quad \lambda = 0$$

Find i_{DN} , i_{DP} , v_o for $v_I = 0, +2.5, -2.5 \text{ V}$


(a) $v_I = v_g = 0$

Symmetrical $\therefore v_o = 0$

$$\therefore v_{DG} = 2.5 \text{ V}$$

$$v_{GS} = 0 < v_t$$


$\therefore Q_N, Q_P$ both off

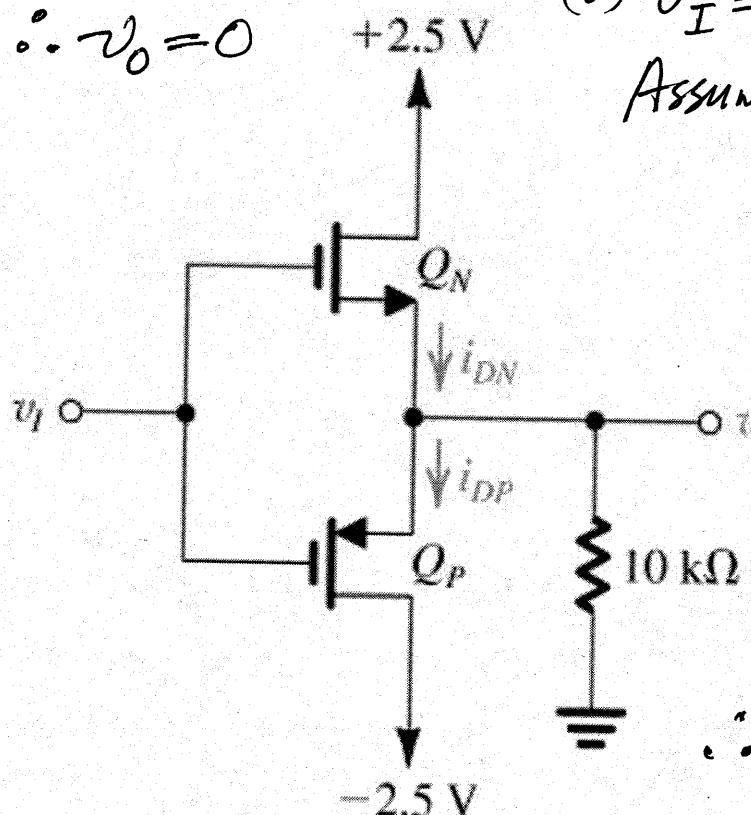

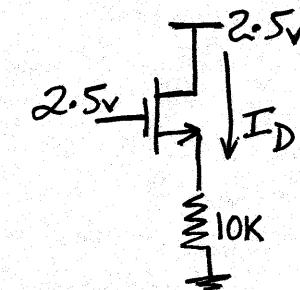(b) $v_I = v_g = +2.5 \text{ V}$

Assume $V_{GSN} > V_{tn} \therefore Q_N \text{ ON}$

$V_{GSP} > V_{tp} \therefore Q_P \text{ OFF}$



$v_{GS} = v_{DS} \therefore \text{Saturated}$

$$\begin{aligned} \therefore I_D &= \frac{1}{2} (2.5 - 10I_D - 1)^2 \\ &= \frac{1}{2} (1.5 - 10I_D)^2 \end{aligned}$$

$$2I_D = 2.25 - 30I_D + 100I_D^2$$

$$100I_D^2 - 32I_D + 2.25 = 0$$

$$I_D = \frac{32 \pm \sqrt{32^2 - 900}}{200} \sim \begin{cases} 0.215 \text{ mA} \rightarrow v_s = 2.15 \text{ V} \therefore v_{GS} = 0.35 \text{ V} < v_t \therefore \text{impossible} \\ 0.105 \text{ mA} \rightarrow v_s = 1.05 \text{ V} \therefore v_{GS} = 1.45 \text{ V} > v_t \therefore \text{OK} \end{cases}$$

Figure E4.16

Contrast with Exercise 4.16 (Example 4.7 in text)

Q_N, Q_P matched


$$k_n' \left(\frac{W_n}{L_n} \right) = k_p' \left(\frac{W_p}{L_p} \right) = 1 \text{ mA/V}^2$$

$$V_{tn} = -V_{tp} = 1 \text{ V}$$


$$\lambda = 0$$

Find i_{DN} & i_{DP} , v_o


for $v_I = 0, +2.5, -2.5 \text{ V}$

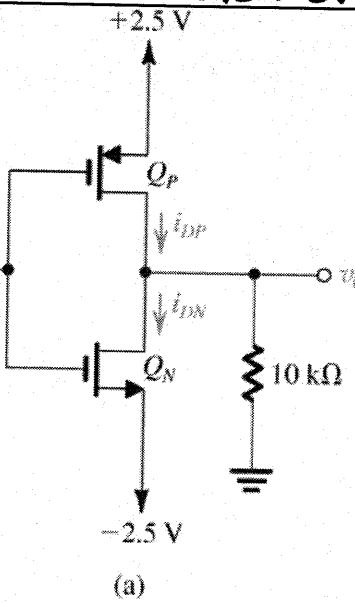


(a)

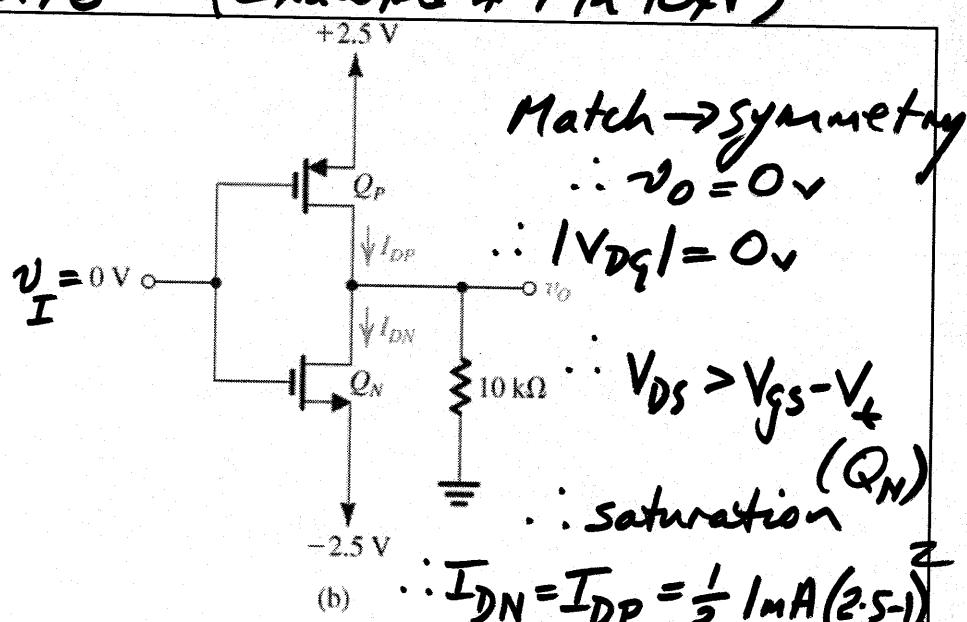

(b)

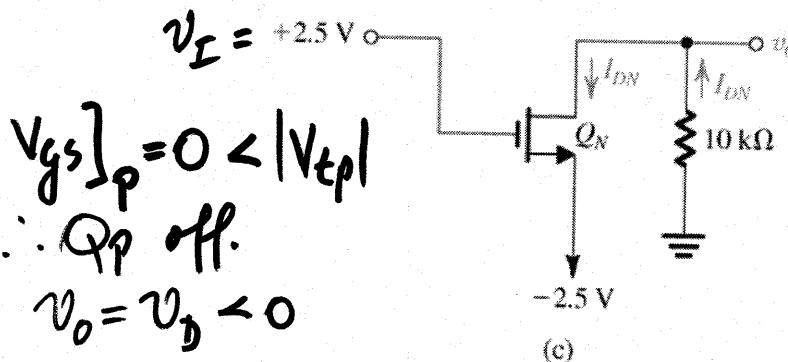

(c)

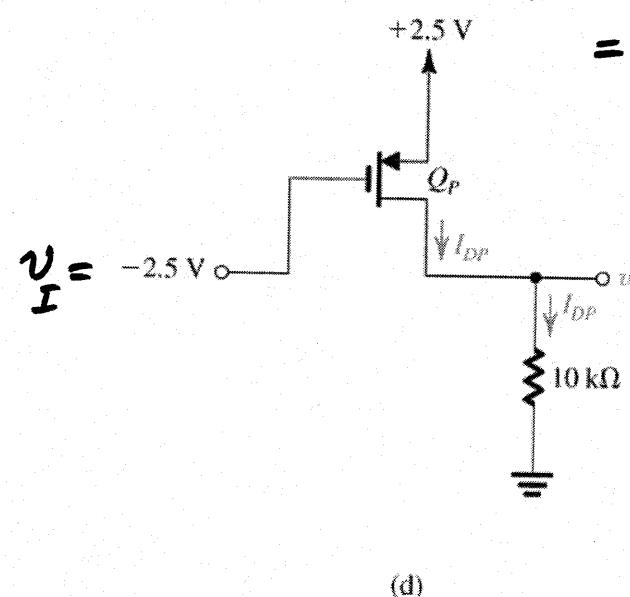

(d)

Figure 4.25 Circuits for Example 4.7.

$$I_{DN} \approx k_n' (W_n / L_n) (V_{gs} - V_t) V_{DS} \text{ for } V_{DS} \text{ small}$$


$$= 1 \text{ mA} [2.5 - (-2.5) - 1] [v_O - (-2.5)] \quad \& I_{DN} = -v_O / 10 \text{ k} \Rightarrow v_O = -2.44 \text{ V}$$

$$I_{DN} = 0.244 \text{ mA}$$

Ex 4.17 Fig 4.26
a & b

$$k_n'(\epsilon)/\hbar = \ln H/\sqrt{2}$$

$$\sqrt{\epsilon} = 1/\nu$$

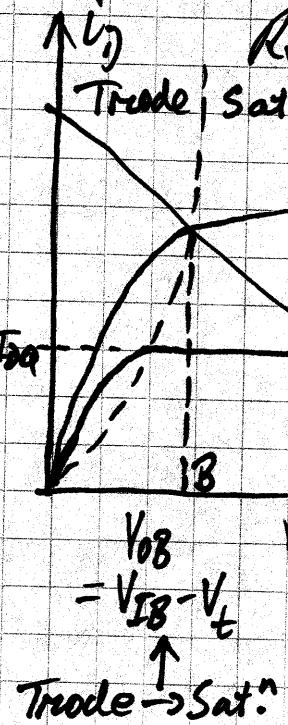

(a) Bias point: Output swing in sat

$$(b) \text{ Neg } V_0 \text{ max} = V_{QQ} - V_{QB} = 4 - 1 = 3 \text{ v}$$

$$(c) P_{os} V_{0\max} = V_{DD} - V_{OQ} = 10 - 4 = 6 \text{ V}$$

(d) $\frac{1}{10} \times \frac{1}{10} = \frac{1}{100}$

(d) \therefore Max input amplitude = $0.184V \rightarrow 3V$ output
 gives $A_v = 3V/0.184V = 16.3V/V$ (cf. $14.7V/V$ in Example 4.8)
 from differential at Q due to non-linearity)

$$\therefore V_{IQ} \rightarrow \frac{1}{3} \times 10^{-3} = \frac{1}{2} (10^{-3}) (V_{IQ} - 1)^2$$

$$\sqrt{IQ} = 1 + \sqrt{2/3} = 1 + \frac{1.414}{1.732} = 1.816$$

Refer Example 11.8. (a) V_{IQ} , V_{IB} , V_{OQ} , V_{OB} ?

$$V_{GS} = V$$

$V_{GS} = V_{IB}$ (b) Max neg pk of V_D & hence
max pos pk of V_I ?

$$v_{gs} = V$$

(c) --- pos --- v_0 ---
- V_{IQ} --- neg --- v_I ?

$$Y_m Y_0 =$$

$V_o = V_{DS}$ (d) Hence max V_o sinewave amplitude? & V_o ?

Hence A_V ? Why not $14.7V/V$ as for Example 14.8?

Pt B: Saturation / Triode

$$c_D = \frac{1}{2} \rho_n' \frac{w}{L} (V_{fs} - V_t)^2$$

$$V_{OB} = V_{IB} - V_t = V_{DD} - i_D R_D$$

$$\text{i.e. } V_{OB} = V_{DD} - \frac{R_D}{\Sigma} \left(k_n \frac{W}{L} \right) V_{OB}^2$$

$$= 10V - 9 \times 10^3 \times 10^{-3} V_{OB}^2$$

$$9V_{OB}^2 + V_{OB} - 10 = 0$$

$$(V_{OB} - 1)(V_{OB} + 10) = 0$$

$\therefore V_{OB} = 1 \text{ or } V_{OB} = -10$


$$\therefore V_{OB} = 1_V \wedge V_{IB} = L_V$$

Choose $V_{00} = 4\pi$ (See Example 4.8)

$$\leftarrow \therefore I_Q = (V_{DD} - V_{OQ}) / R_D$$

$$= (10 - 4) / 18 \text{ K} = 1/3 \text{ mA}$$

Ex DK. 20 (Fig K.30(e))

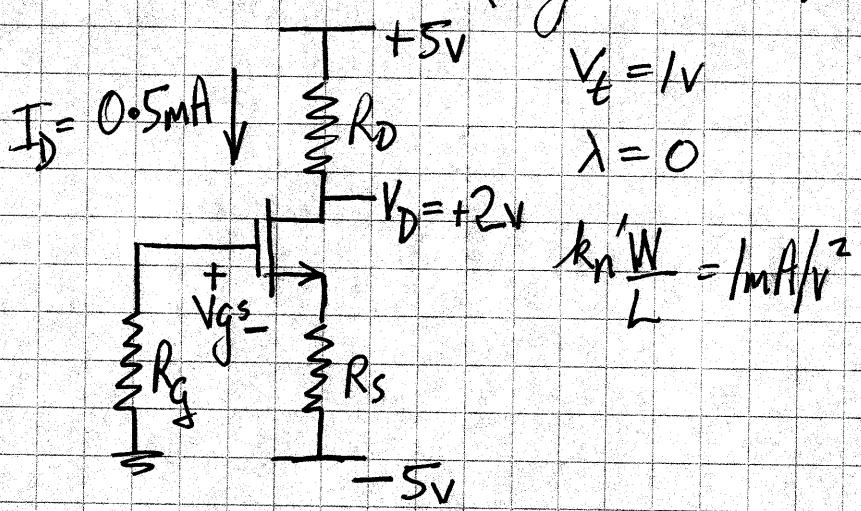

Design for $I_D = 0.5\text{mA}$ $V_D = 2\text{V}$
with standard 5% resistors.

$$R_D = 3\text{V} / 0.5\text{mA} = 6K$$

$\rightarrow 6.2K$ (5% preferred value)

Re-calculate for $R_S = R_D = 6.2K$

$$I_D = \frac{1}{2}\text{mA} \left(0 - (-5 + I_D 6.2K) - 1 \right)^2$$

$\uparrow V_g \quad \uparrow V_S \quad \uparrow V_t$

$$= \frac{1}{2} (4 - 6.2 I_D)^2$$

$$0.5\text{mA} = \frac{1}{2} \text{mA} (V_{gs} - V_t)^2$$

$$\therefore V_{gs} = \sqrt{1 + V_t} = 2\text{V} \quad \therefore V_S = -2\text{V}$$

$$\therefore R_S = 3\text{V} / 0.5\text{mA} = 6K \rightarrow 6.2K$$

$$2I_D = 16 - 49.6I_D + 38.44I_D^2$$

$$I_D = \frac{+51.6 \pm \sqrt{51.6^2 - 2460.16}}{76.88} = 0.856\text{mA} \quad \rightarrow I_D R_S = 5.3\text{V} \quad \therefore V_{gs} < 0 \text{ inconsistent}$$

or 0.486mA $\rightarrow = 3.013\text{V}$ $\therefore V_S = -1.987$

$V_{gs} \approx 2\text{V} > V_t$

Ex. D4.21 $k_n' \frac{W}{L} = 1 \text{ mA/V}^2$ $V_t = 1 \text{ V}$ $\lambda = 0$ 5% Standard Resistors

$$V_{DS} = V_{GS} \therefore \text{Saturation}$$

$$I_D = \frac{1}{2} 1 \text{ mA} (V_{GS} - V_t)^2 = 0.5 \text{ mA}$$

$$\therefore V_{GS} = V_t + \sqrt{I_D} = 2 \text{ V}$$

$$\therefore R_D = \frac{5 - 2}{0.5} K_n = 6K$$

$\rightarrow 6.2 \text{ K}$
preferred value

$$\therefore I_D = \frac{1}{2} \text{ mA} (5 - I_D 6.2 \text{ K} - 1)^2$$

$$2I_D = 16 - 24.8I_D + 38.44I_D^2$$

$$\Rightarrow 0.49 \text{ mA}$$

$$\& V_D = 5 - 6.2 \times 0.49 \\ = 1.962 \text{ V}$$

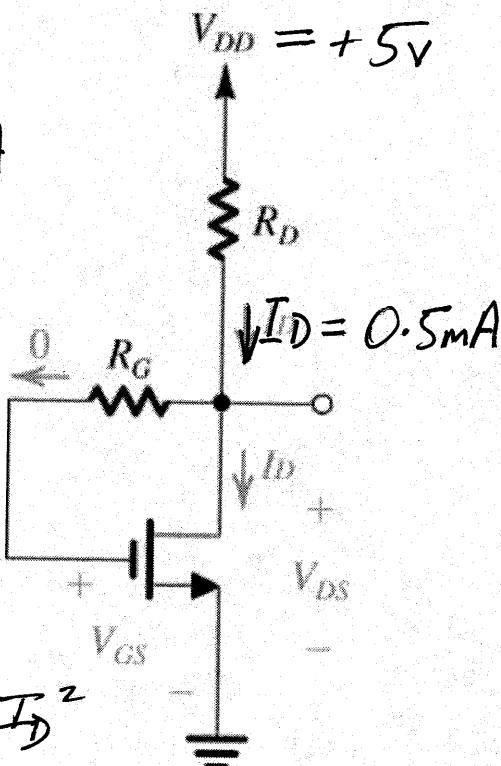


Figure 4.32 Biasing the MOSFET using a large drain-to-gate feedback resistance, R_G .

Ex DK. 22

$$L_1 = L_2$$

$$W_2 = 5 W_1$$

$$I = 0.5 \text{ mA}$$

$$k_n' \left(\frac{W}{L} \right)_1 = 0.8 \text{ mA/V}^2$$

$$\lambda = 0 \quad V_t = 1 \text{ V}$$

$$R = \frac{V_{DD} - V_{GS1} - (-V_{SS})}{I_{D1}} = \frac{10 - V_{GS}}{0.1 \text{ mA}}$$

$$V_{GS1} = V_{DS1} \quad \because \text{in saturation}$$


$$\text{and } I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right)_1 (V_{GS} - V_t)^2$$

$$\therefore 0.1 \text{ mA} = 0.4 \text{ mA} (V_{GS} - 1)^2$$

$$V_{GS} = 1 + (0.25)^{1/2} = 1.5 \text{ V}$$

$$\therefore V_{G1} = V_{G2} = -5 + 1.5 = -3.5 \text{ V}$$
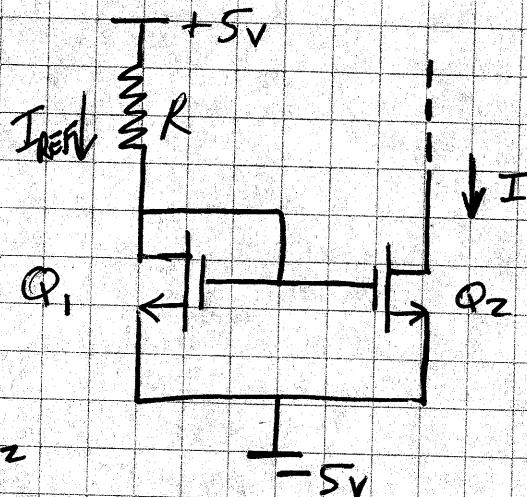
$$R = \frac{10 - 1.5}{0.1 \text{ mA}} = 85 \text{ k}\Omega$$



$$R = ? \quad V_{G1}, V_{G2} = ?$$

Minimum V_{D2} for Q_2 in saturation

$$\text{Note: } I = I_{D2} = 0.5 \text{ mA}$$

$$k_n' \left(\frac{W}{L} \right)_2 = 5 k_n' \left(\frac{W}{L} \right)_1 = 4 \text{ mA/V}^2$$

$$\therefore I_{D1} = I_{REF} = 0.1 \text{ mA}$$

lowest V_{D2} for Q_2 saturated?

$$V_{D2} > V_{G2} - V_t$$

$$> -3.5 \text{ V} - 1 \text{ V}$$

$$V_{D2} > -4.5 \text{ V}$$