

ECE321 ELECTRONICS I

FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 11
31st October, 2006





CHAPTER 5

Bipolar Junction Transistors (BJTs)

5.1 Device Structure & Physics

5.2 I-V Characteristics

Convert 5.1 information to circuit applications

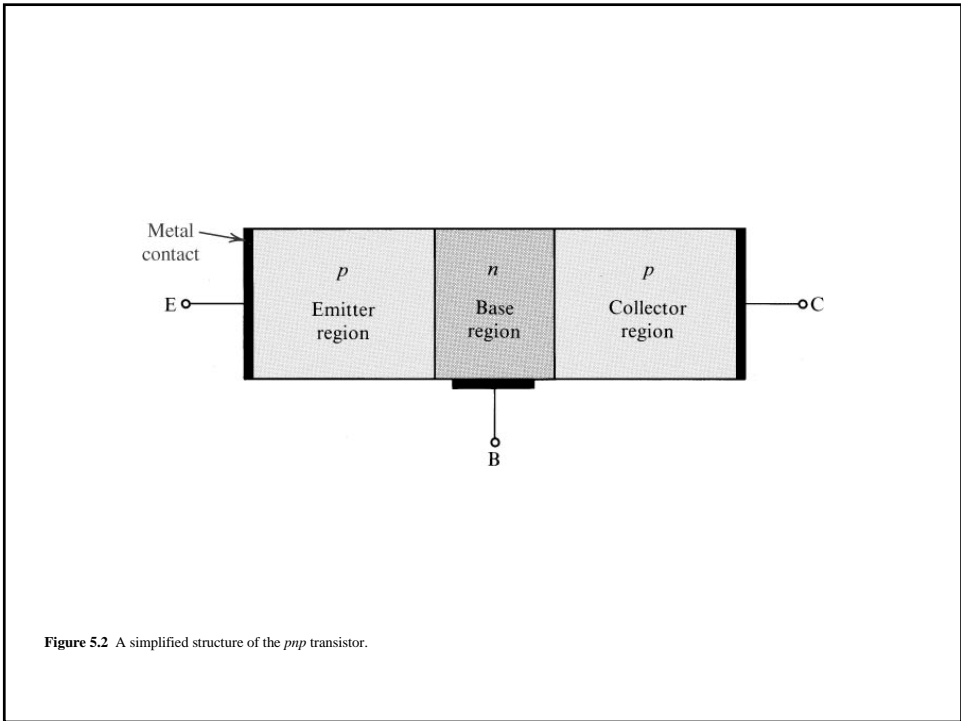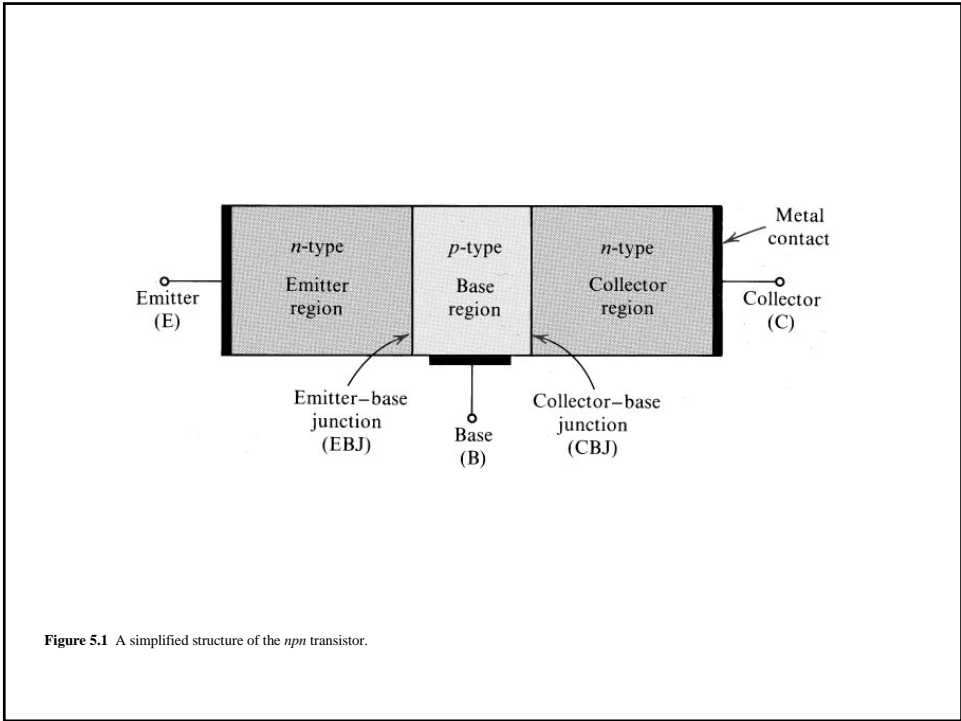

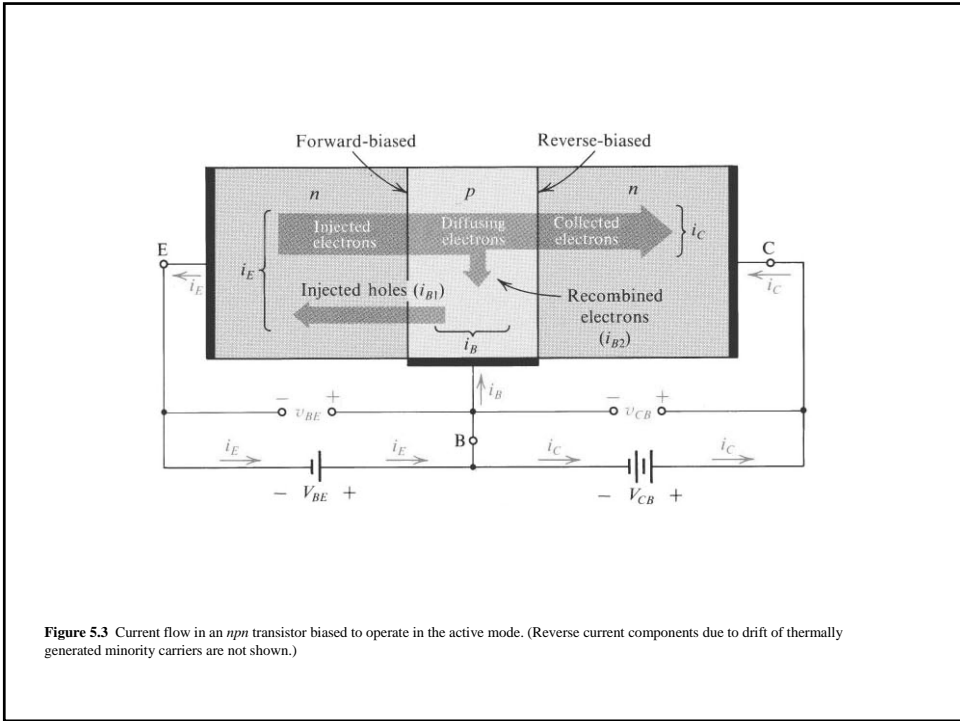


Figure 5.3 Current flow in an npn transistor biased to operate in the active mode. (Reverse current components due to drift of thermally generated minority carriers are not shown.)

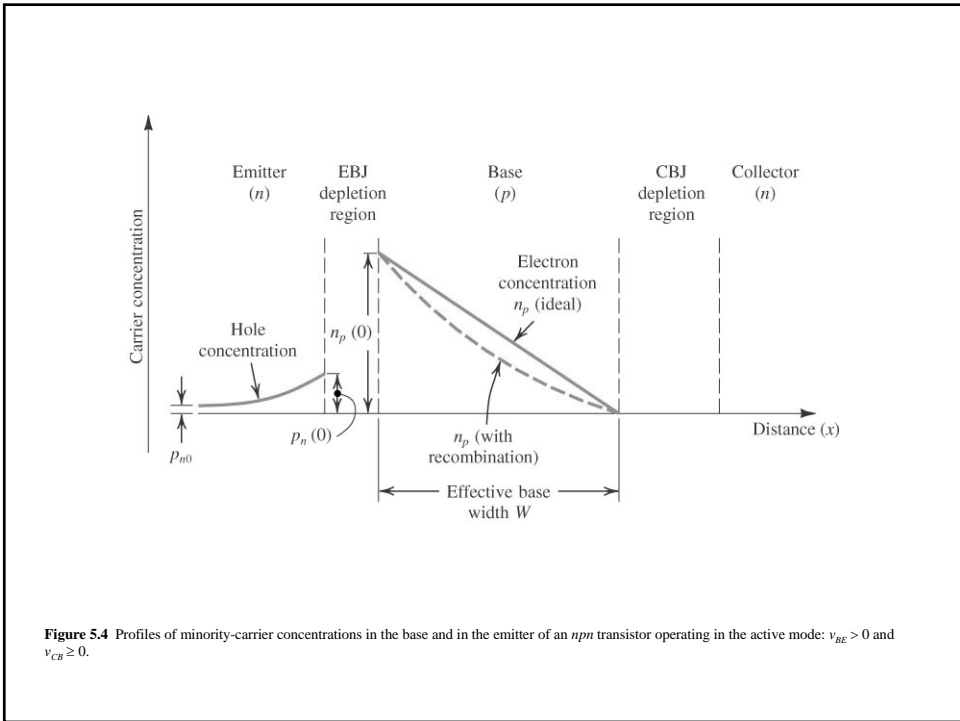


Figure 5.4 Profiles of minority-carrier concentrations in the base and in the emitter of an npn transistor operating in the active mode: $v_{BE} > 0$ and $v_{CB} \geq 0$.

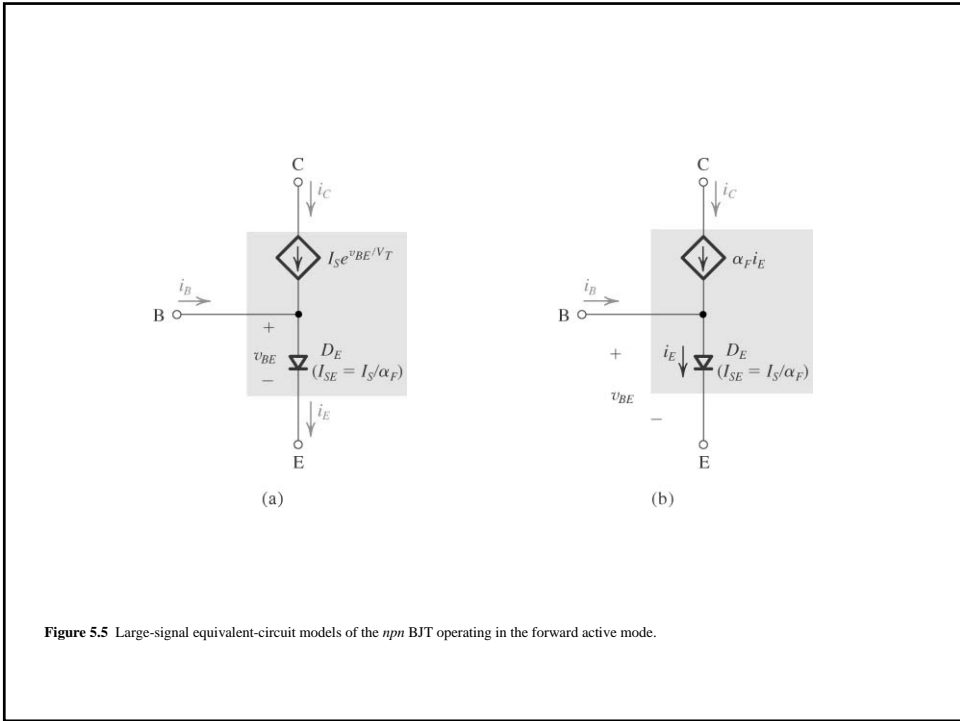


Figure 5.5 Large-signal equivalent-circuit models of the npn BJT operating in the forward active mode.

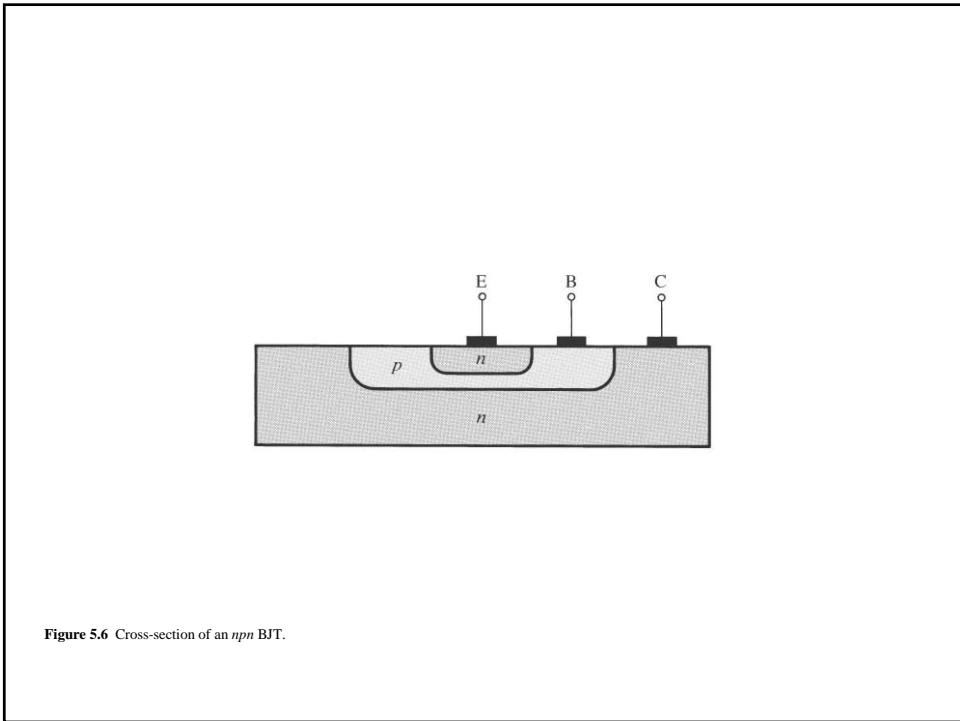


Figure 5.6 Cross-section of an npn BJT.

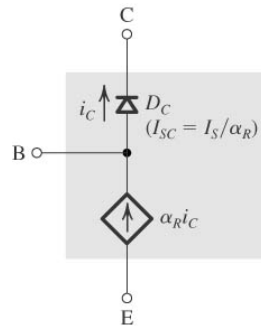


Figure 5.7 Model for the *npn* transistor when operated in the reverse active mode (i.e., with the CBJ forward biased and the EBJ reverse biased).

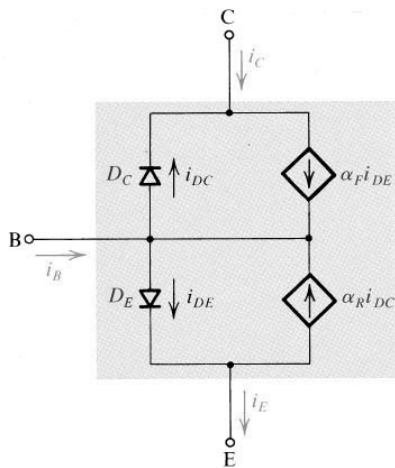


Figure 5.8 The Ebers-Moll (EM) model of the *npn* transistor.

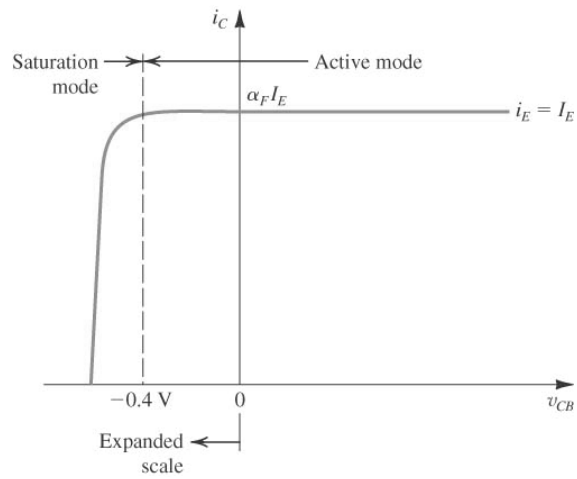


Figure 5.9 The i_C - v_{CB} characteristic of an *npn* transistor fed with a constant emitter current I_E . The transistor enters the saturation mode of operation for $v_{CB} < -0.4 \text{ V}$, and the collector current diminishes.

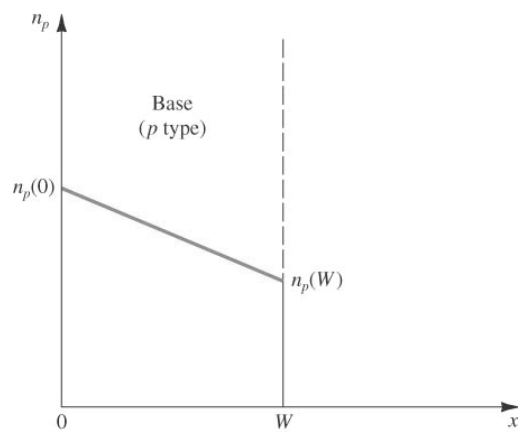


Figure 5.10 Concentration profile of the minority carriers (electrons) in the base of an *npn* transistor operating in the saturation mode.

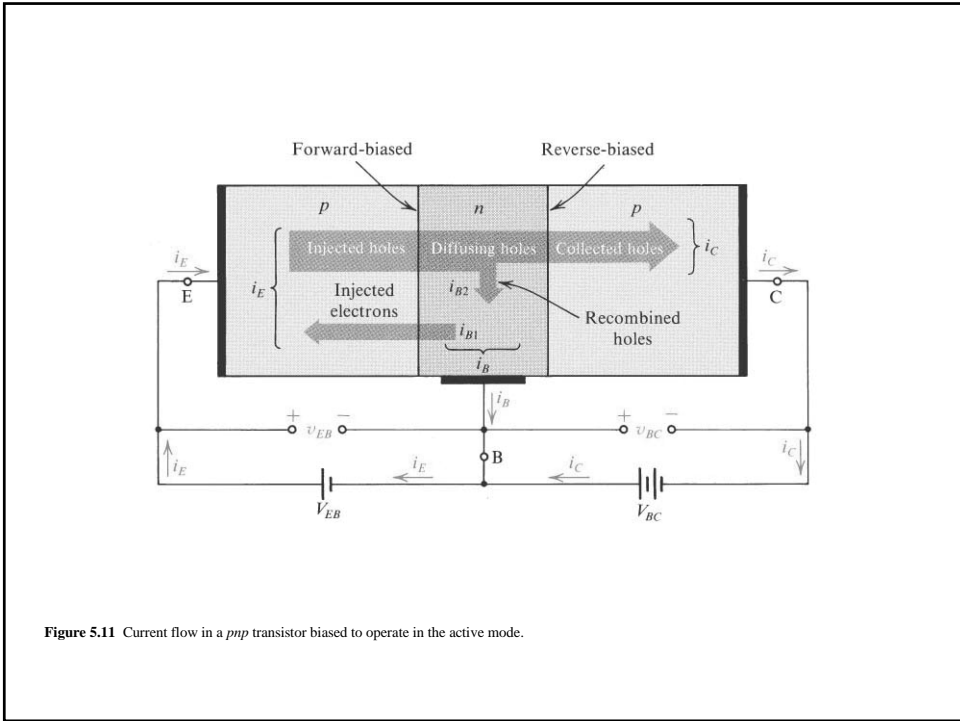


Figure 5.11 Current flow in a pnp transistor biased to operate in the active mode.

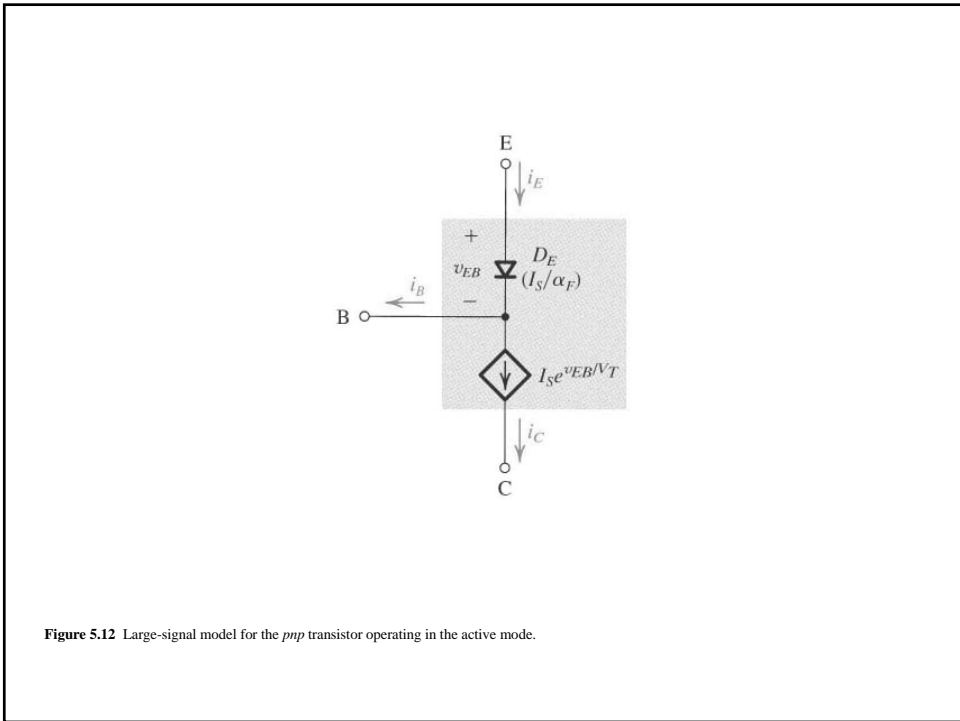


Figure 5.12 Large-signal model for the pnp transistor operating in the active mode.

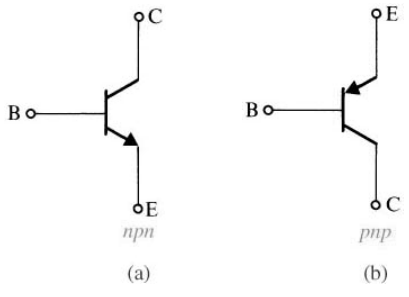


Figure 5.13 Circuit symbols for BJTs.

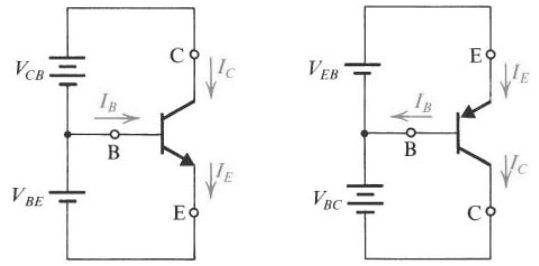


Figure 5.14 Voltage polarities and current flow in transistors biased in the active mode.

Circuit for Exercise 5.10, but ignore RHS values

$V_{CC} = -V_{EE} = 10\text{V}$, $R_C = 5\text{K}$, $R_E = 10\text{K}$, $\beta = 50$
Find I_E , I_B , I_C , V_C

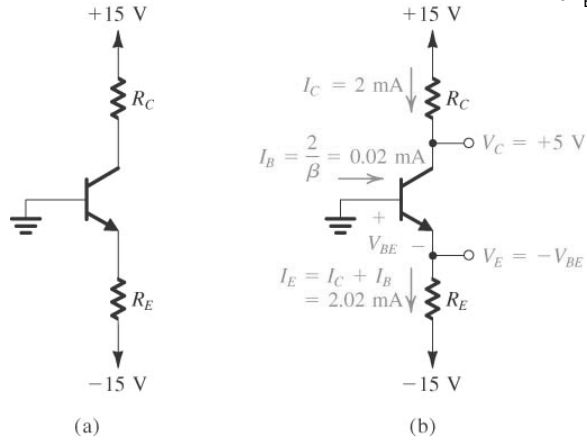


Figure 5.15 Circuit for Example 5.1.

Circuit for Exercise 5.11: $V_B = 1\text{V}$, $V_E = +1.7\text{V}$ Find α , β , V_C

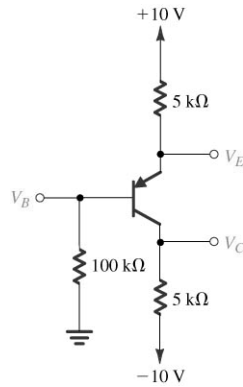


Figure E5.11

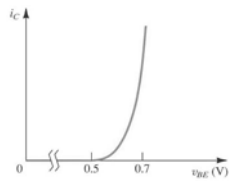


Figure 5.16 The i_c - v_{BE} characteristic for an npn transistor.

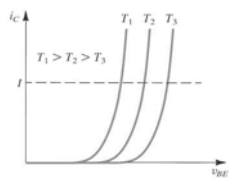


Figure 5.17 Effect of temperature on the i_c - v_{BE} characteristic. At a constant emitter current (broken line), v_{BE} changes by -2 mV/ $^{\circ}$ C.

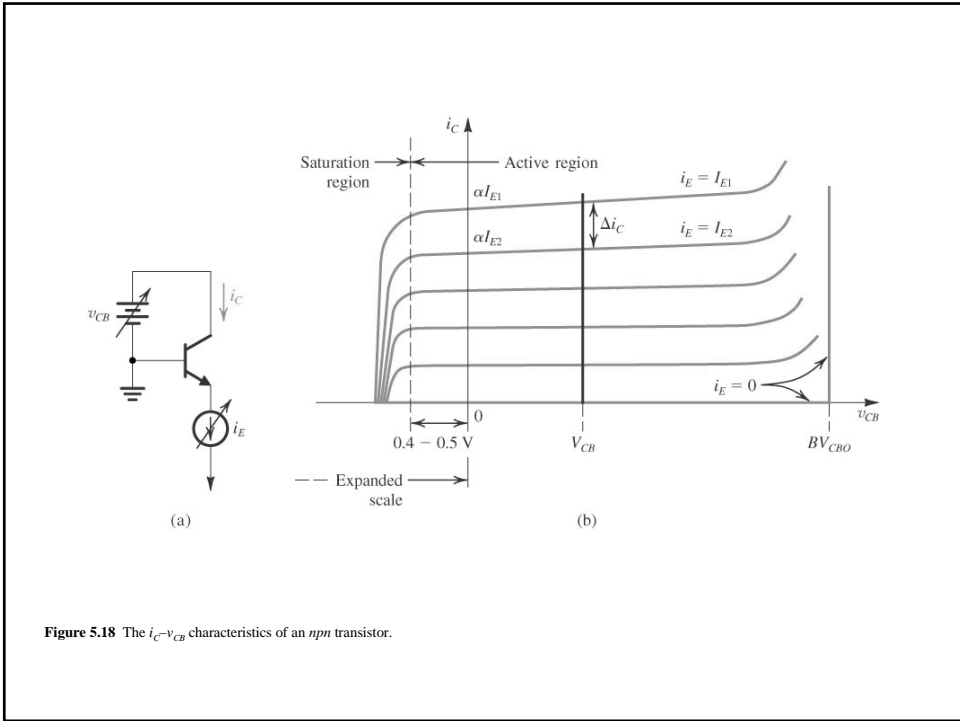


Figure 5.18 The i_C - v_{CB} characteristics of an npn transistor.

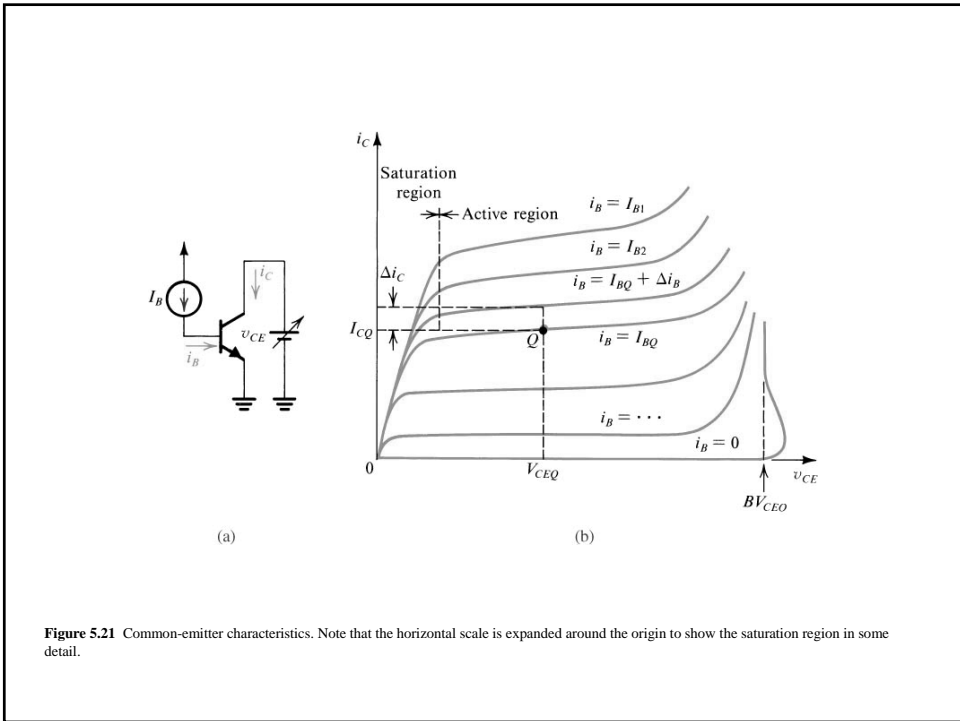


Figure 5.21 Common-emitter characteristics. Note that the horizontal scale is expanded around the origin to show the saturation region in some detail.

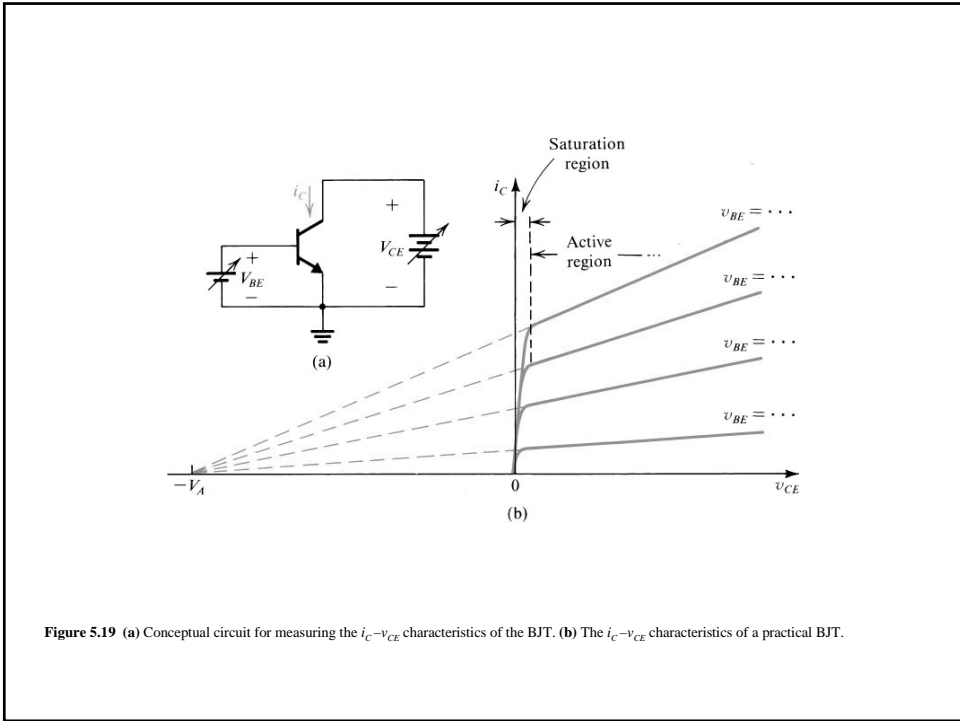


Figure 5.19 (a) Conceptual circuit for measuring the i_C - v_{CE} characteristics of the BJT. (b) The i_C - v_{CE} characteristics of a practical BJT.



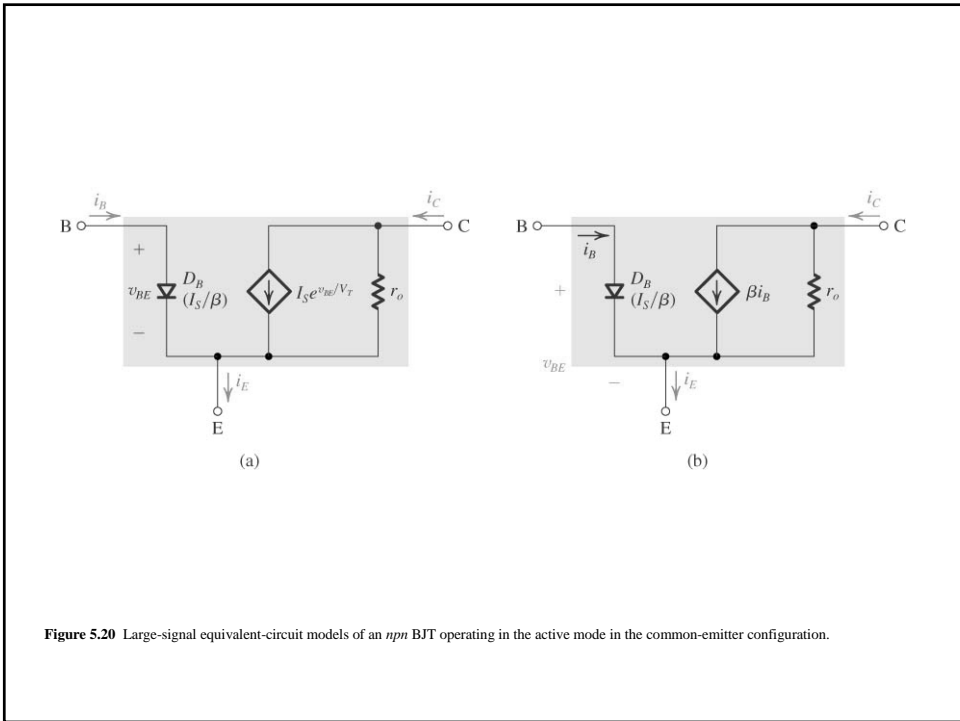
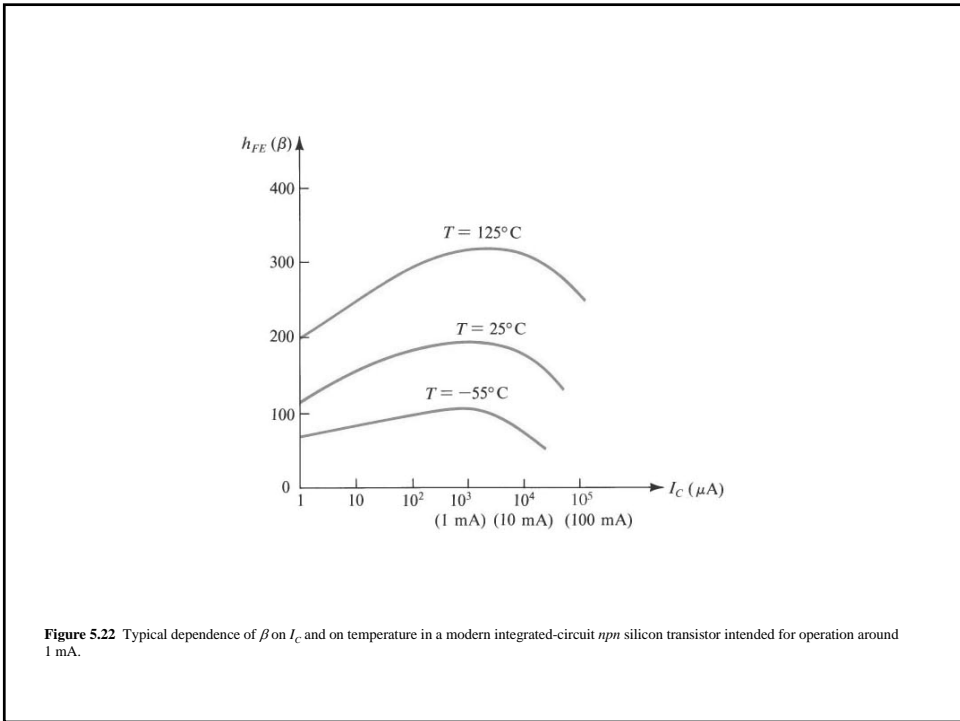
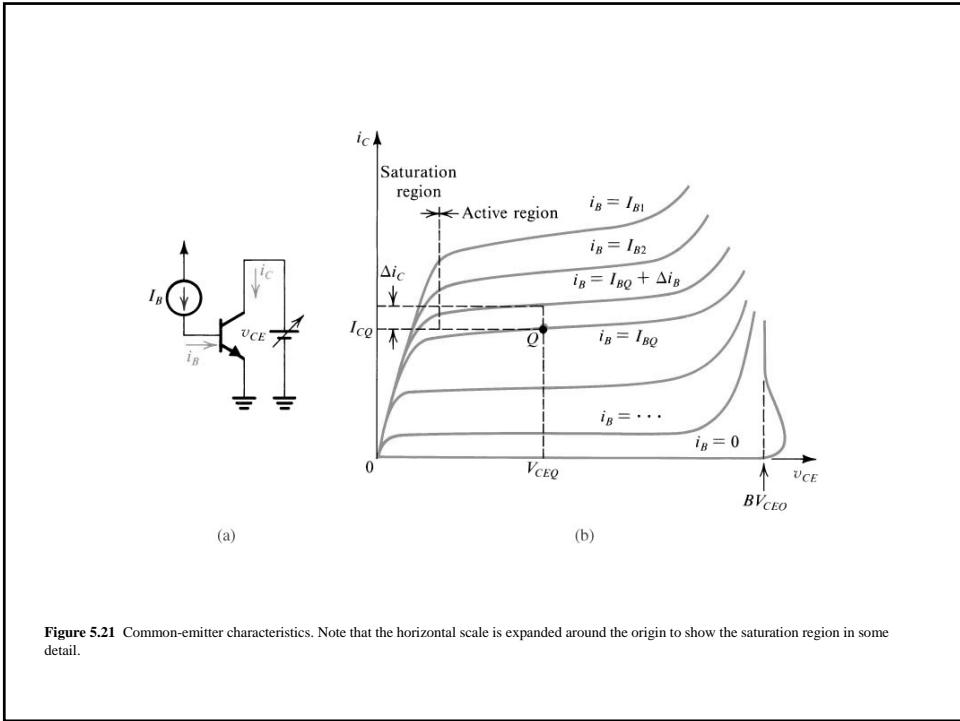


Figure 5.20 Large-signal equivalent-circuit models of an npn BJT operating in the active mode in the common-emitter configuration.

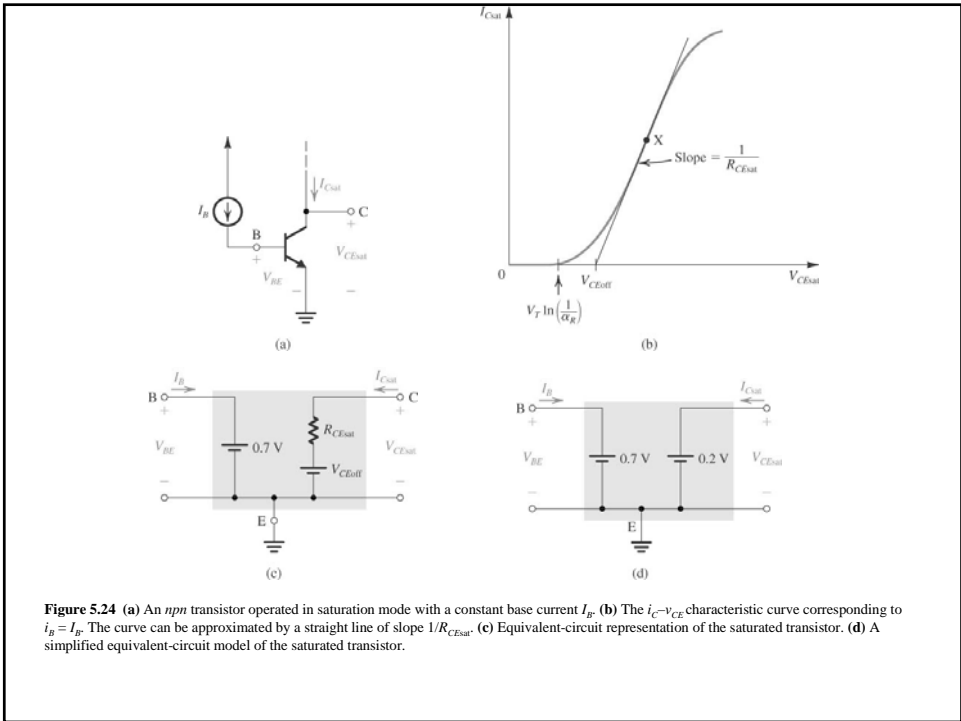

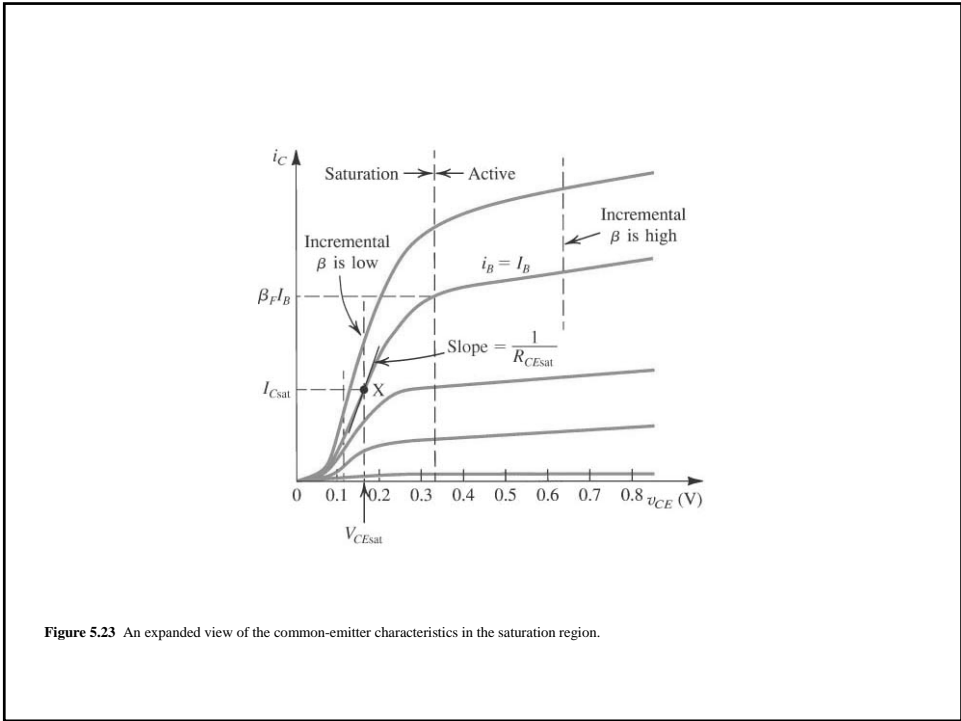

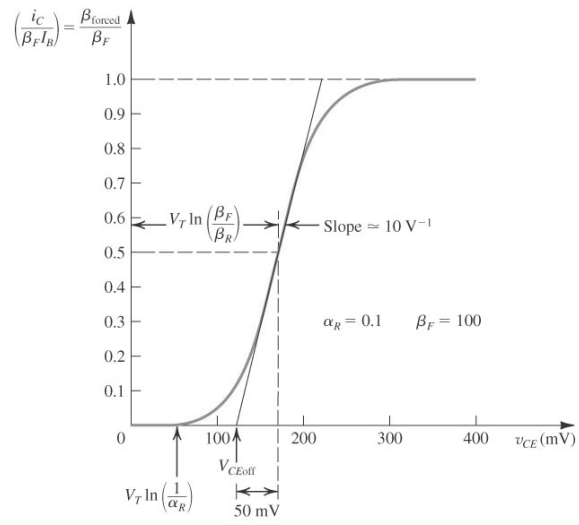


Figure 5.25 Plot of the normalized i_C versus v_{CE} for an *npn* transistor with $\beta_F = 100$ and $\alpha_R = 0.1$. This is a plot of Eq. (5.47), which is derived using the Ebers-Moll model.

Figure for Exercise 5.18: $BV_{CBO} = 70\text{V}$. Find V_O

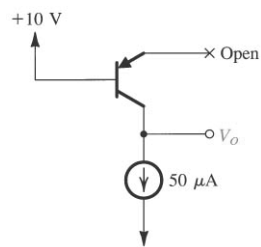


Figure E5.18

