

ECE321 ELECTRONICS I

FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 12
2nd November, 2006



CHAPTER 5

Bipolar Junction Transistors (BJTs)

5.3 Amplifiers & Switches (Basic circuits)

5.4 DC Circuits (Biasing)

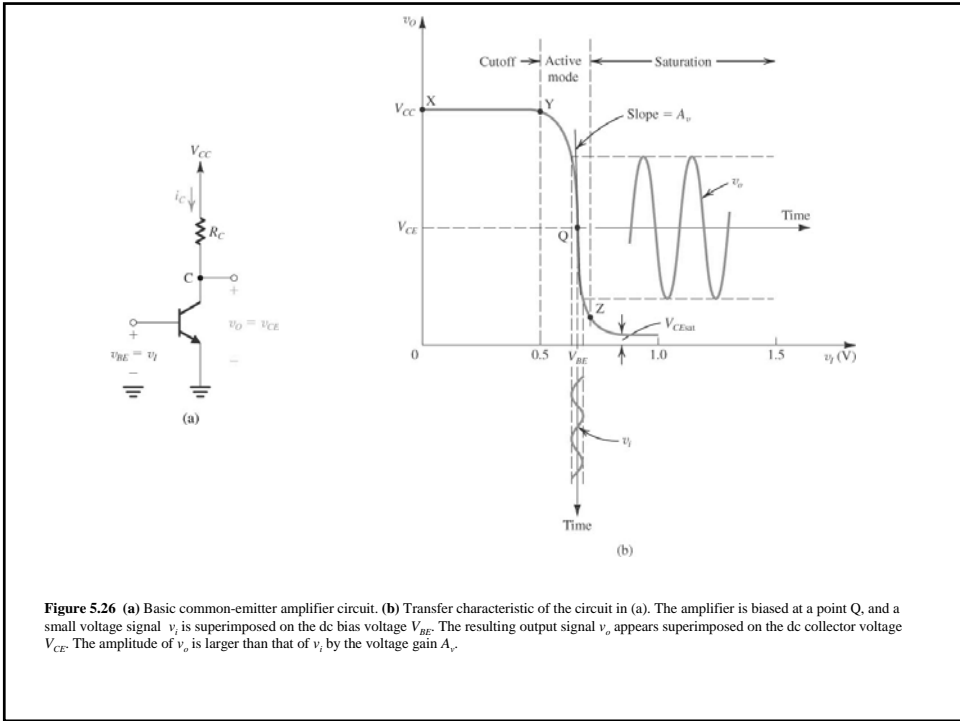


Figure 5.26 (a) Basic common-emitter amplifier circuit. (b) Transfer characteristic of the circuit in (a). The amplifier is biased at a point Q , and a small voltage signal v_i is superimposed on the dc bias voltage V_{BE} . The resulting output signal v_o appears superimposed on the dc collector voltage V_{CE} . The amplitude of v_o is larger than that of v_i by the voltage gain A_v .

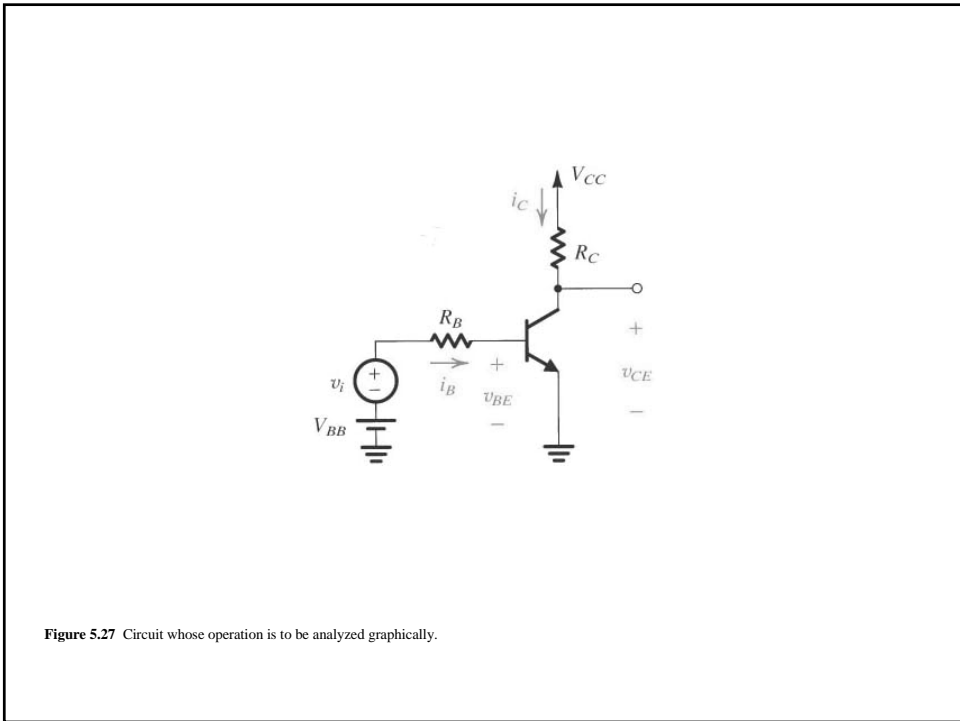


Figure 5.27 Circuit whose operation is to be analyzed graphically.

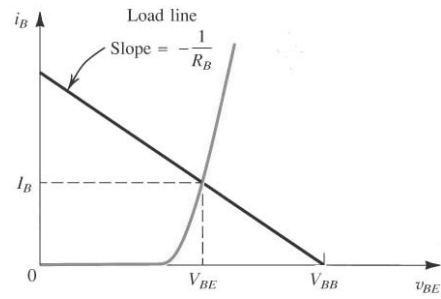


Figure 5.28 Graphical construction for the determination of the dc base current in the circuit of Fig. 5.27.




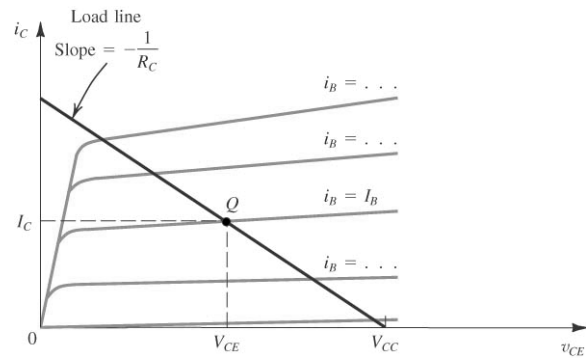
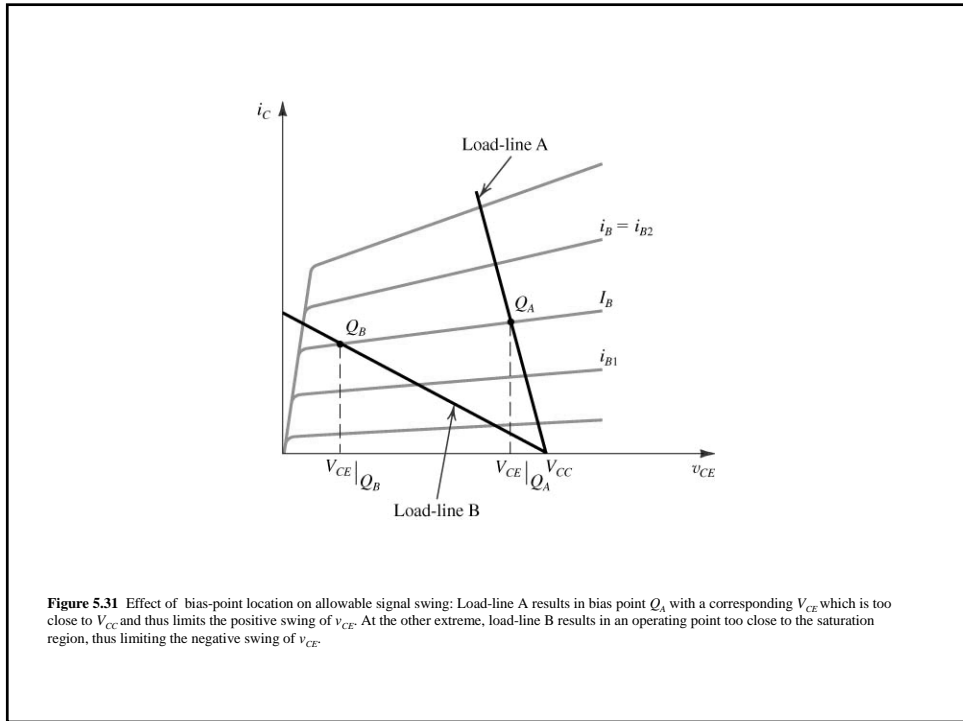
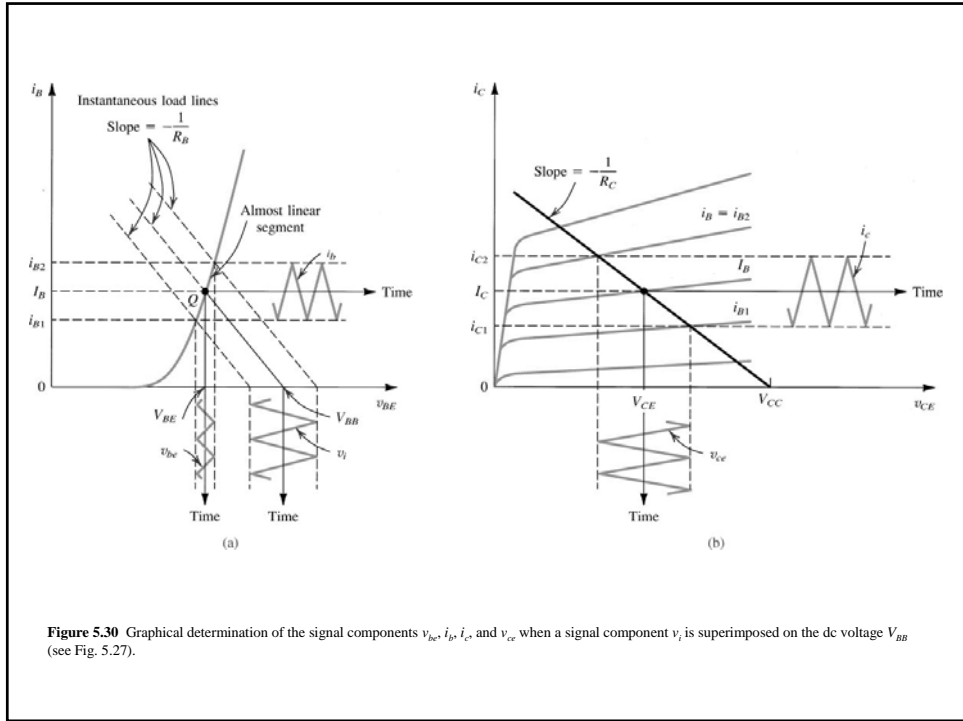
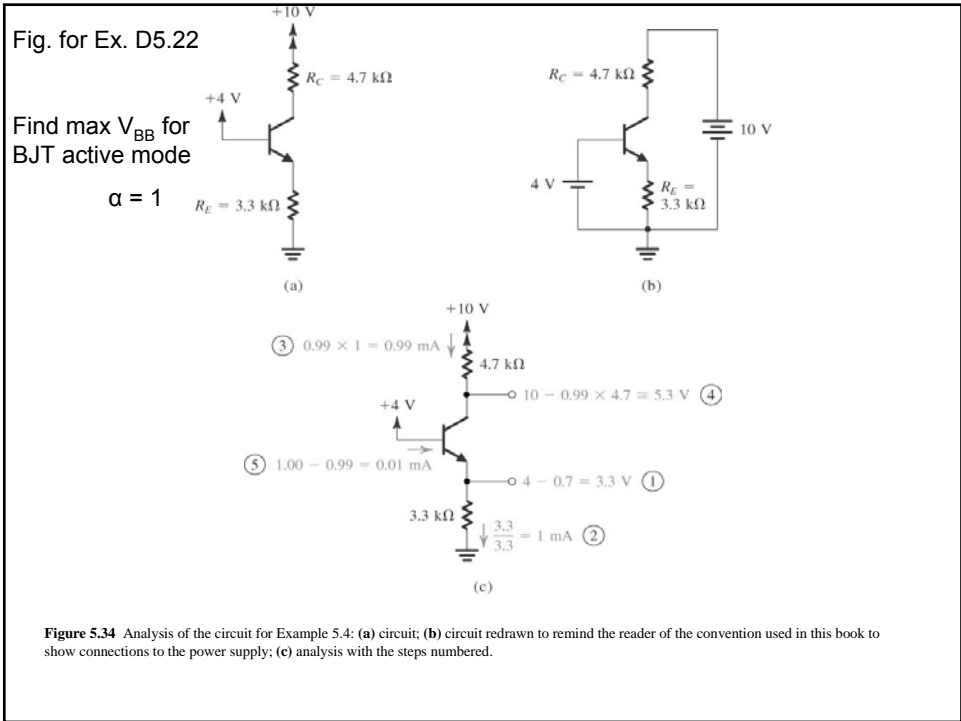


Figure 5.29 Graphical construction for determining the dc collector current I_C and the collector-to-emitter voltage V_{CE} in the circuit of Fig. 5.27.

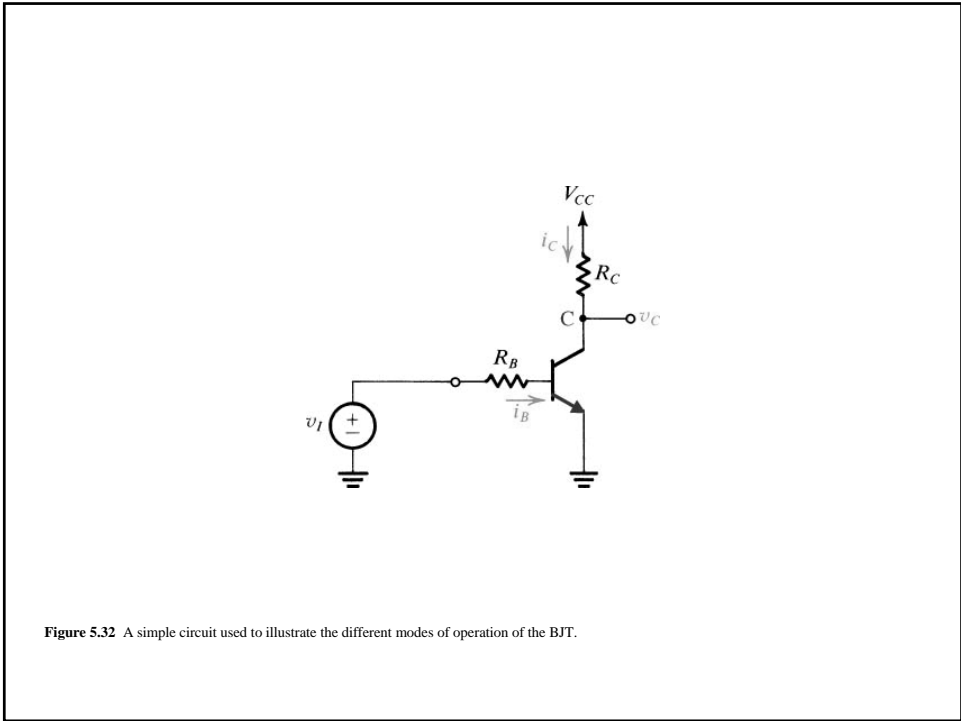

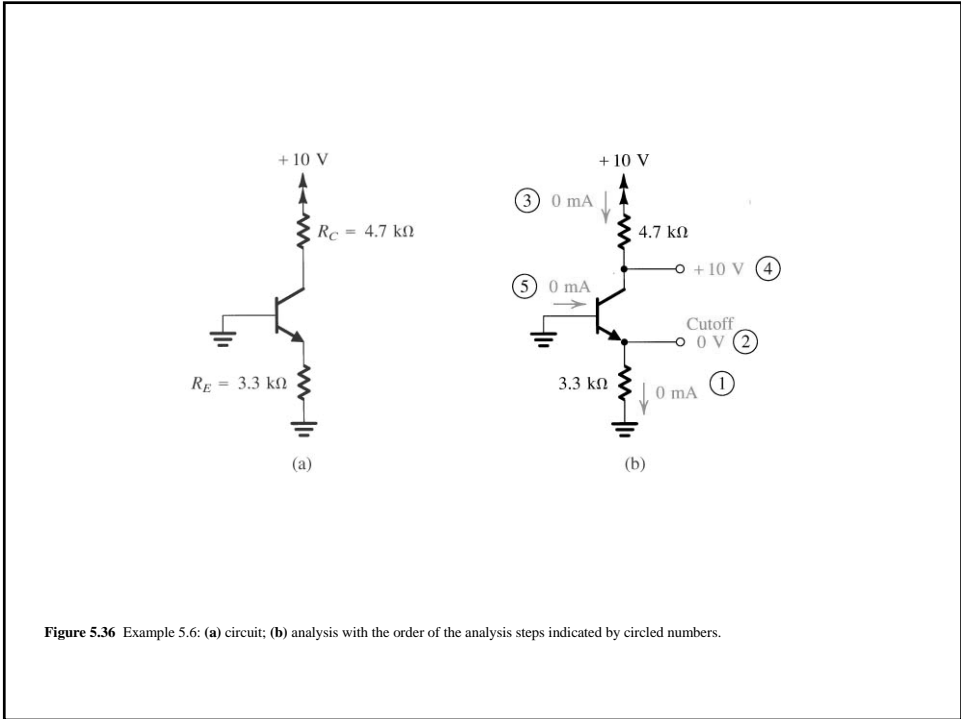

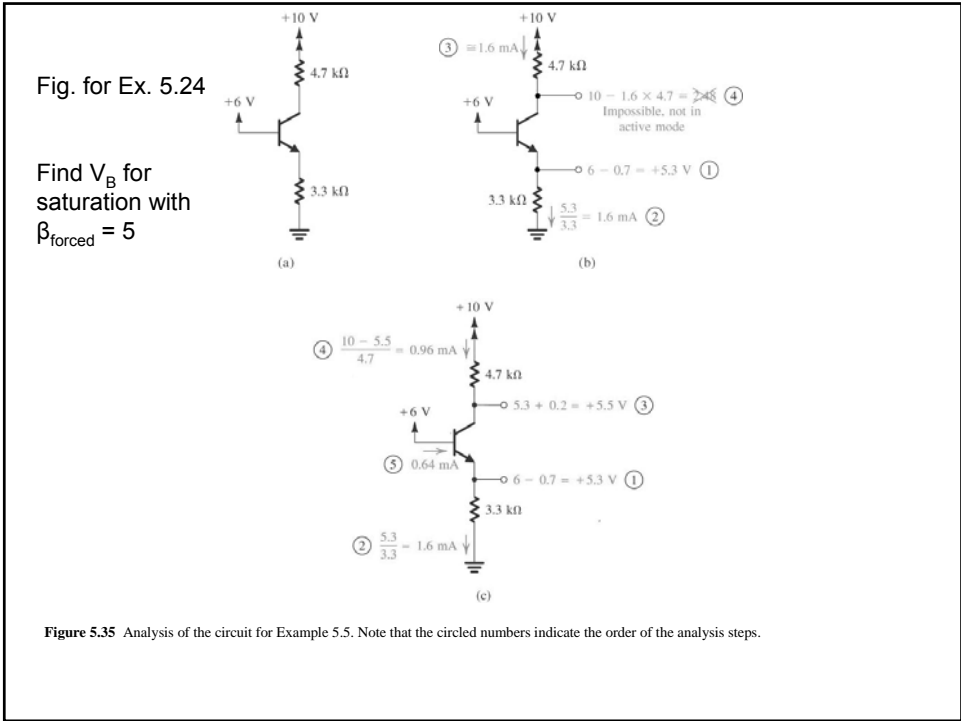

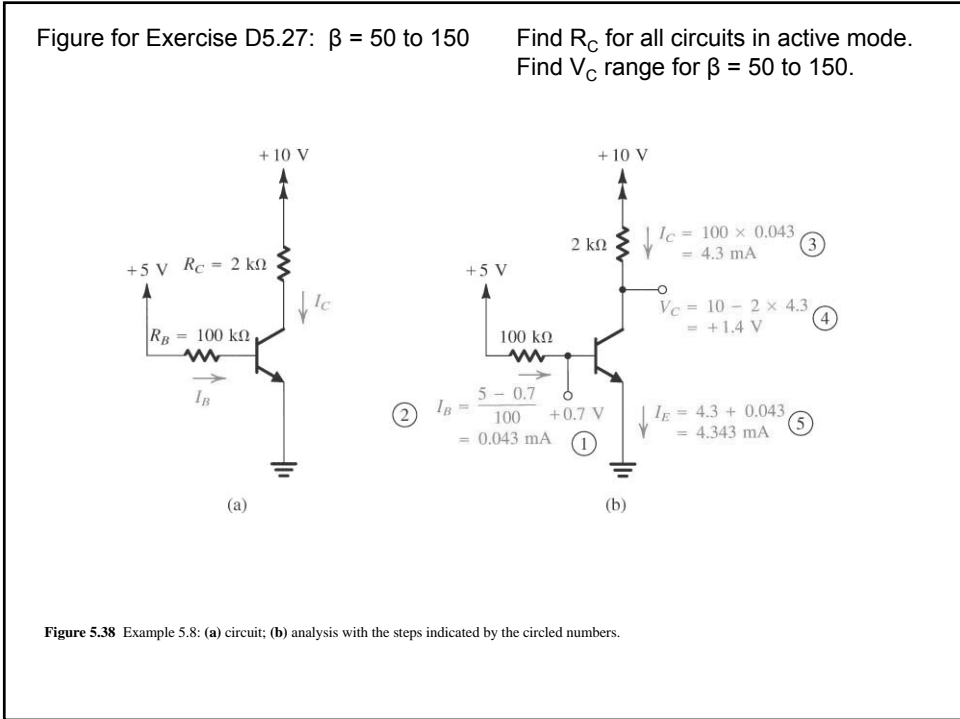
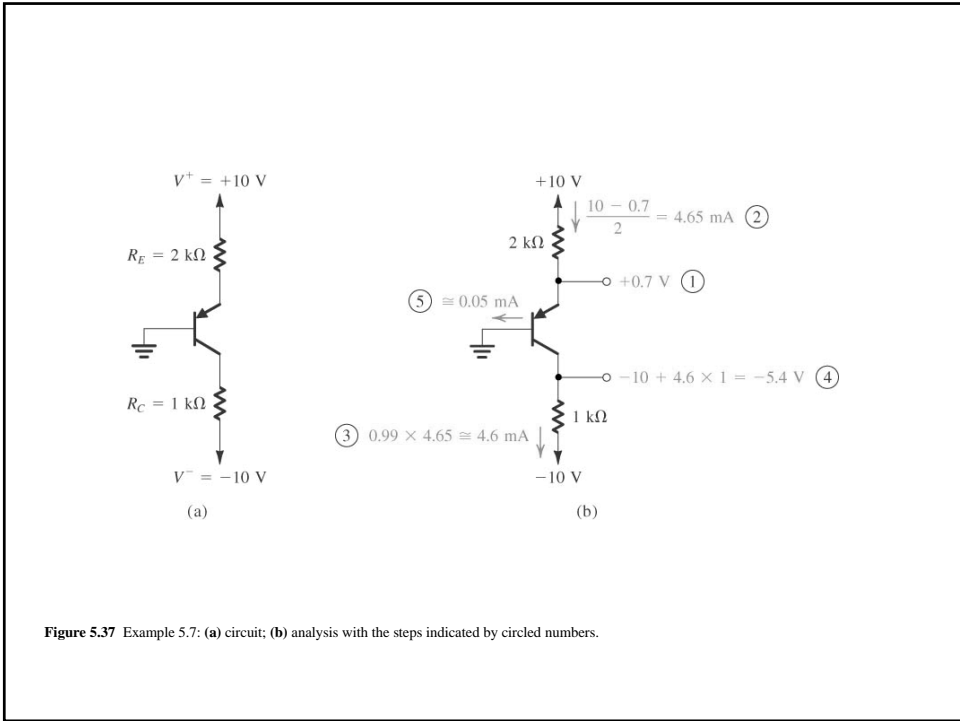


Fig. for Ex. 5.28

Example 5.10
calculates $I_C = 1.28\text{mA}$
for $\beta = 100$

Recalculate for $\beta = 50$

What is % change?

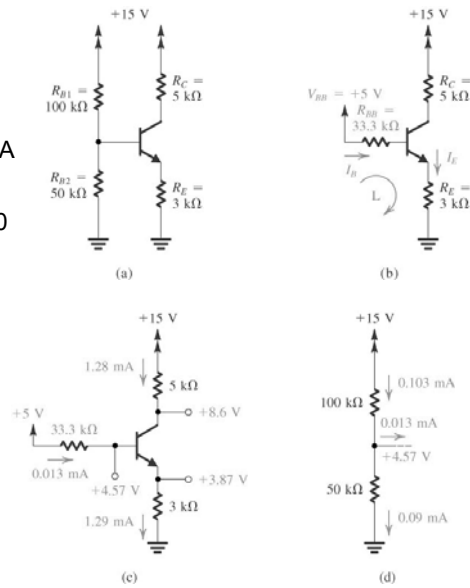


Figure 5.40 Circuits for Example 5.10.

Figure for Exercise 5.29: Find total current from power supply and power dissipation in the circuit. (See Example 5.11)

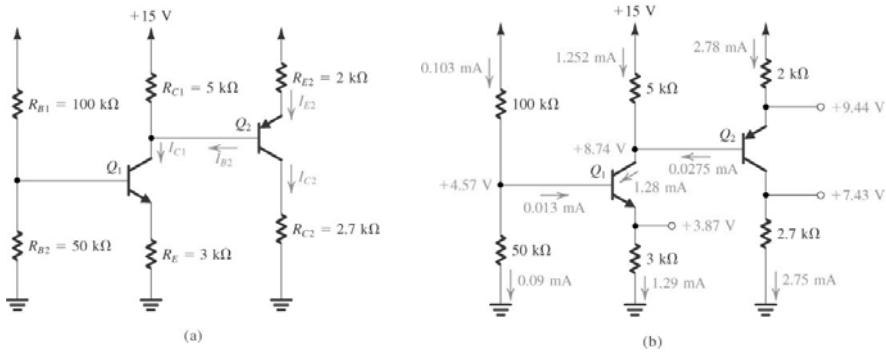


Figure 5.41 Circuits for Example 5.11.