

ECE321 ELECTRONICS I

FALL 2006

PROFESSOR JAMES E. MORRIS

Lecture 4
5th October, 2006

A decorative header for Chapter 2 featuring a cyan background with a faint, abstract circuit board pattern. The text 'CHAPTER 2' is overlaid on the left side.

CHAPTER 2

Operational Amplifiers (Real)

- 2.7 DC Imperfections
- 2.8 Integration & Differentiation
- 2.9 SPICE

 


Figure 2.28 Circuit model for an op amp with input offset voltage V_{OS} .

 


Figure E2.23 Transfer characteristic of an op amp with $V_{OS} = 5$ mV.

 


Figure 2.29 Evaluating the output dc offset voltage due to V_{OS} in a closed-loop amplifier.

 


Figure 2.30 The output dc offset voltage of an op amp can be trimmed to zero by connecting a potentiometer to the two offset-nulling terminals. The wiper of the potentiometer is connected to the negative supply of the op amp.

 


Figure 2.31 (a) A capacitively coupled inverting amplifier, and (b) the equivalent circuit for determining its dc output offset voltage V_{OS} .

 


Figure 2.32 The op-amp input bias currents represented by two current sources I_{B1} and I_{B2} .

 


Figure 2.33 Analysis of the closed-loop amplifier, taking into account the input bias currents.

 


Figure 2.34 Reducing the effect of the input bias currents by introducing a resistor R_3 .

 


Figure 2.35 In an ac-coupled amplifier the dc resistance seen by the inverting terminal is R_2 ; hence R_3 is chosen equal to R_2 .

 


Figure 2.36 Illustrating the need for a continuous dc path for each of the op-amp input terminals. Specifically, note that the amplifier will *not* work without resistor R_3 .

 


Figure 2.37 The inverting configuration with general impedances in the feedback and the feed-in paths.


 
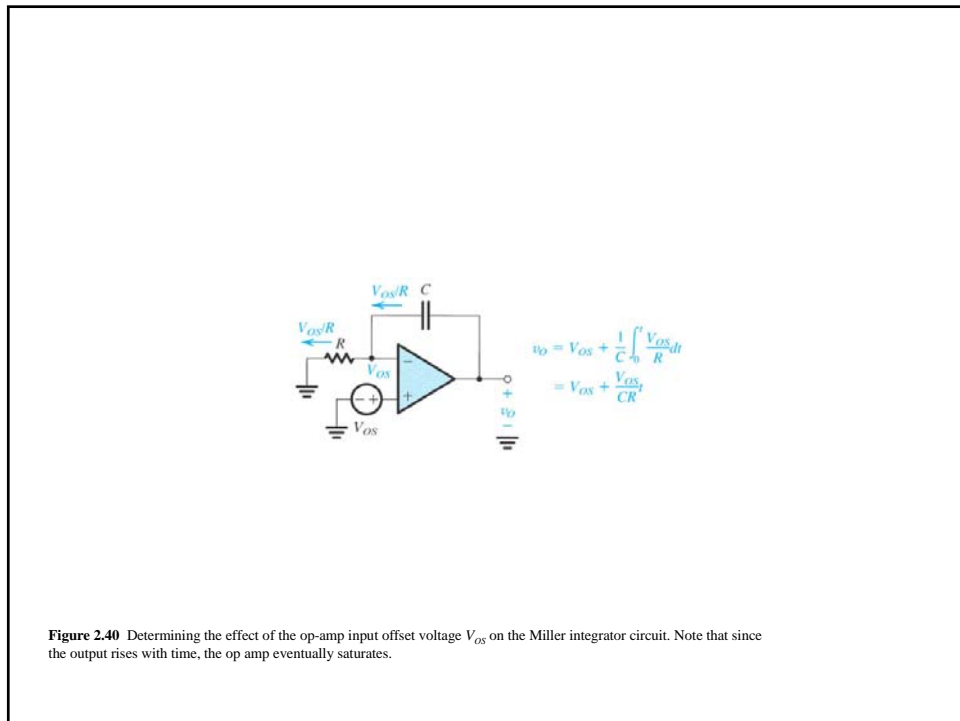


Figure 2.38 Circuit for Example 2.6.

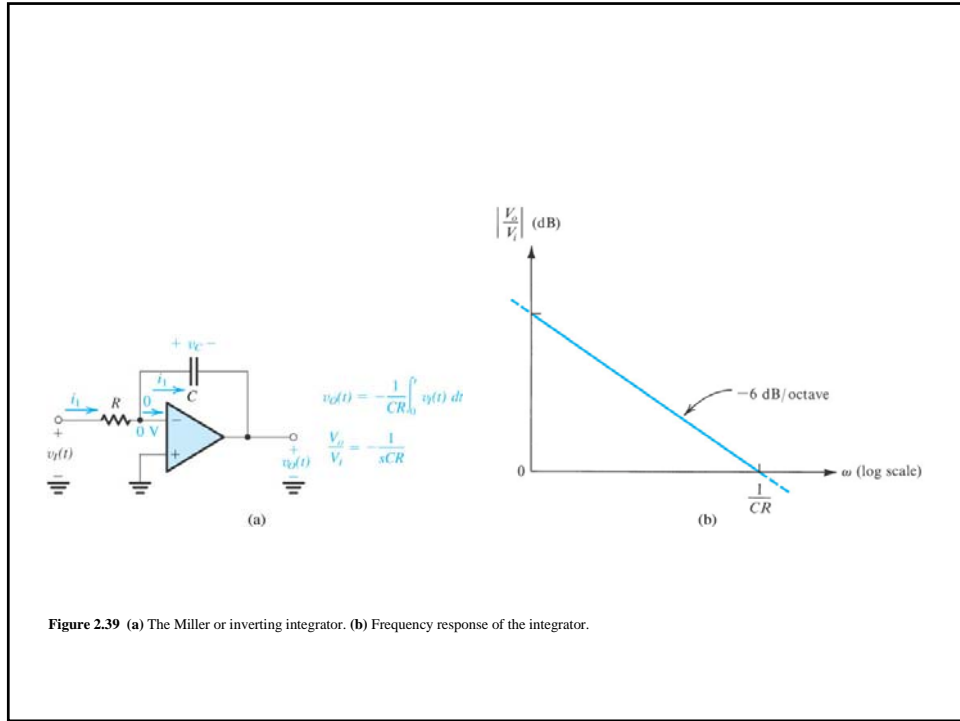

 


Figure 2.41 Effect of the op-amp input bias and offset currents on the performance of the Miller integrator circuit.


 
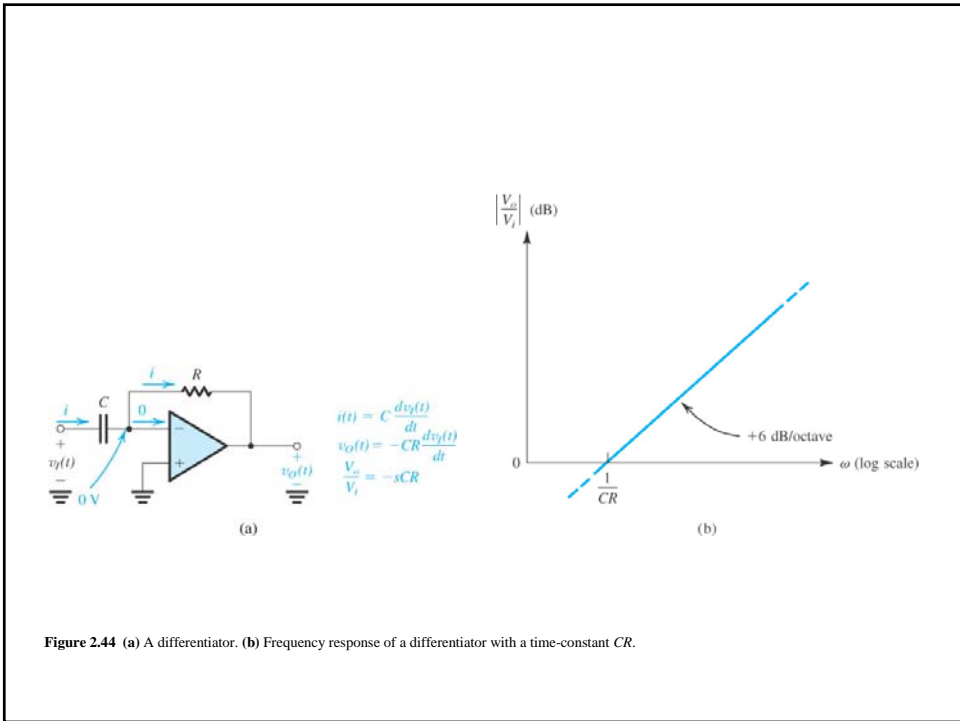


Figure 2.42 The Miller integrator with a large resistance R_f connected in parallel with C in order to provide negative feedback and hence finite gain at dc.

 

 


Figure 2.45 A linear macromodel used to model the finite gain and bandwidth of an internally compensated op amp.

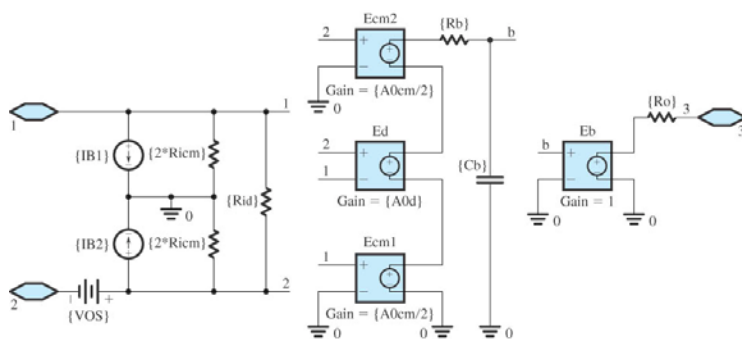


Figure 2.46 A comprehensive linear macromodel of an internally compensated op amp.

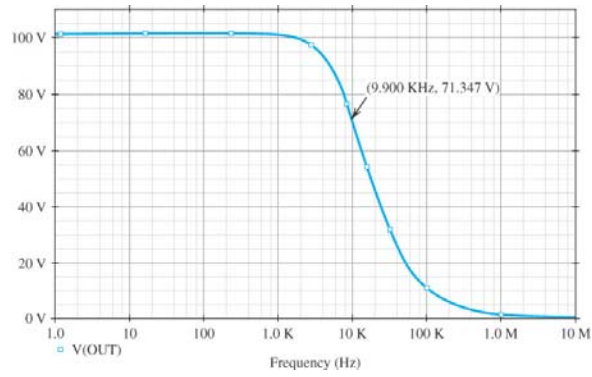


Figure 2.47 Frequency response of the closed-loop amplifier in Example 2.8.

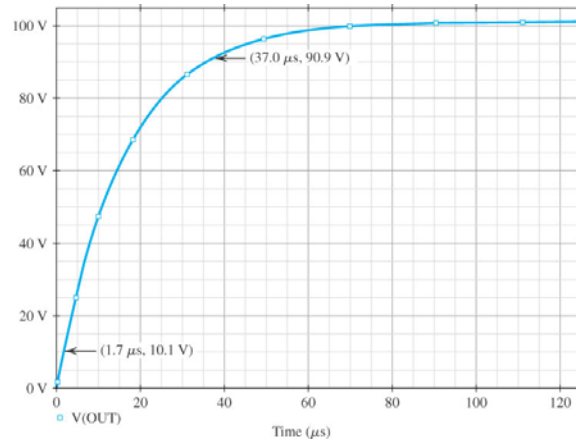


Figure 2.48 Step response of the closed-loop amplifier in Example 2.8.

 


Figure 2.49 Simulating the frequency response of the $\mu A741$ op-amp in Example 2.9.

 


Figure 2.50 Frequency response of the $\mu A741$ op amp in Example 2.9.

 


Figure 2.51 Circuit for determining the slew rate of the $\mu A741$ op amp in Example 2.9.

 


Figure 2.52 Square-wave response of the $\mu A741$ op amp connected in the unity-gain configuration shown in Fig. 2.51.